

A TEXTBOOK OF

Electrical Technology

(For M.D.U., G.J.U. and K.U., Haryana)



R. K. Rajput

Published by :
LAXMI PUBLICATIONS (P) LTD
113, Golden House, Daryaganj,
New Delhi-110002

Phone : 011-43 53 25 00
Fax : 011-43 53 25 28

www.laxmipublications.com
info@laxmipublications.com

Compiled by : Smt. Ramesh Rajput

© All rights reserved with the Author and Publishers.

No part of this publication may be reproduced, stored in a retrieval system, or transmitted in any form or by any means, electronic, mechanical, photocopying, recording or otherwise without the prior written permission of the publisher.

Price : Rs. 195.00 Only.

*First Edition : 2004
Reprint : 2006*

Offices :

India

- **Bangalore** (*Phone : 080-26 61 15 61*)
- **Chennai** (*Phone : 044-24 34 47 26*)
- **Cochin** (*Phone : 0484-239 70 04*)
- **Guwahati** (*Phones : 0361-254 36 69, 251 38 81*)
- **Hyderabad** (*Phone : 040-24 75 02 47*)
- **Jalandhar City** (*Phone : 0181-222 12 72*)
- **Kolkata** (*Phones : 033-22 27 37 73, 22 27 52 47*)
- **Lucknow** (*Phone : 0522-220 95 78*)
- **Mumbai** (*Phones : 022-24 91 54 15, 24 92 78 69*)
- **Ranchi** (*Phone : 0651-230 77 64*)

USA

- **Boston**
11, Leavitt Street, Hingham,
MA 02043, USA
Phone : 781-740-4487

CONTENTS

<i>Chapters</i>		<i>Pages</i>
Syllabus		(vi)
1. D.C. CIRCUITS AND NETWORK ANALYSIS		1—17
1. Definitions of Important Terms	...	1
2. Limitations of Ohm's Law	...	1
3. Kirchhoff's Laws	...	2
4. Applications of Kirchhoff's Laws	...	3
4.1. Branch-current method	...	3
4.2. Maxwell's loop (or mesh) current method	...	14
4.3. Nodal voltage method	...	17
5. Solving Equations by Determinants—Cramer's Rule	...	19
6. Superposition Theorem	...	19
7. Thevenin's Theorem	...	24
8. Norton's Theorem	...	29
9. Maximum Power Transfer Theorem	...	30
10. Delta Star Transformation	...	32
11. Compensation Theorem	...	39
12. Reciprocity Theorem	...	40
13. Millman's Theorem	...	40
<i>Highlights</i>	...	40
<i>Objective Type Questions</i>	...	41
<i>Theoretical Questions</i>	...	42
<i>Unsolved Examples</i>	...	42
2. A.C. CIRCUITS		48—128
1. Introduction to Alternating Current	...	48
2. Generation and Equations of Alternating Voltages and Currents	...	48
3. Alternating Voltage and Current	...	51
4. Single-phase Circuits	...	64
4.1. A.C. through pure ohmic resistance alone	...	64
4.2. A.C. through pure inductance alone	...	65
4.3. A.C. through pure capacitance alone	...	67
4.4. Phasor algebra	...	69
4.5. A.C. series circuits	...	73
4.6. A.C. parallel circuits	...	98
5. Transients	...	116
5.1. General aspects	...	116
5.2. D.C. transients	...	117
5.3. A.C. transients	...	118
<i>Highlights</i>	...	121
<i>Objective Type Questions</i>	...	122
<i>Theoretical Questions</i>	...	126
<i>Unsolved Examples</i>	...	127

<i>Chapters</i>	<i>Pages</i>
3. THREE-PHASE A.C. NETWORK	129—183
1. Introduction	129
2. Advantages of Polyphase Systems	129
3. Generation of Three-phase Voltages	130
4. Phase Sequence and Numbering of Phases	131
5. Inter-connection of Three Phases	132
6. Star or Wye (Y) Connection	132
7. Delta (Δ) or Mesh Connection	141
8. Comparison between Star and Delta Systems	143
9. Measurement of Power in 3-phase circuit	148
9.1. Three-wattmeters method	148
9.2. Two-wattmeters method	149
9.3. One-wattmeter method	155
10. Measurement of Reactive Volt Amperes	155
11. Types of Energy Meters	160
11.1. Motor meters	160
11.2. Motor-driven meter—watt-hour meter	160
11.3. Induction type watt-hour meter	161
11.4. Induction type single-phase energy meters	161
12. Power Factor Improvement	164
13. Earthing and Grounding	167
13.1. General aspects	167
13.2. Objects of earthing	168
13.3. Specifications required for earthing as per I.S.I.	168
13.4. Methods of earthing	168
13.5. Sizes of earth wire and earth plate for domestic and motor installations	171
13.6. Indian electricity rules	171
13.7. Measurement of earth resistance by earth tester	174
13.8. Earthing of a power system	175
<i>Highlights</i>	176
<i>Objective Type Questions</i>	176
<i>Theoretical Questions</i>	179
<i>Unsolved Examples</i>	180
4. TRANSFORMERS	184—280
1. General Aspects	184
2. Basic Definitions	185
3. Working Principle of a Transformer	185
4. Transformer Ratings	186
5. Kinds of Transformers	186
6. Transformer Construction	187
6.1. Core-type transformer	187
6.2. Shell type transformer	188
6.3. Spiral core transformer	190
7. Transformer Windings, Terminals, Tappings and Bushings	190
7.1. Transformer windings	190
7.2. Terminals and leads	192
7.3. Tappings	192
7.4. Bushings	192

<u>Chapters</u>	<u>Pages</u>
8. Transformer Cooling	192
8.1. Cooling methods	192
8.2. Transformer oil	194
8.3. Conservator and breather	194
9. Single phase Transformer	195
9.1. Elementary theory of an ideal transformer	195
9.2. E.M.F. equation of a transformer	196
9.3. Voltage transformation ratio (K)	196
9.4. Transformer with losses but no magnetic leakage	200
9.5. Resistance and magnetic leakage	203
9.6. Transformer with resistance and leakage reactance	204
9.7. Equivalent resistance and reactance	205
9.8. Total voltage drop in a transformer	207
9.9. Equivalent circuit	209
9.10. Transformer Tests	211
9.11. Regulation of a transformer	213
9.12. Percentage resistance and reactance	214
9.13. Transformer losses	215
9.14. Transformer efficiency	215
9.15. All-day efficiency	253
9.16. Transformer noise	254
9.17. Auto-transformer	254
9.18. Polarity of transformers	256
10. Three phase transformer	260
10.1. Three-phase transformer connections	260
10.2. Three-phase transformer construction	265
10.3. Parallel operation of 3-phase transformers	266
Highlights	267
Objective Type Questions	267
Theoretical Questions	273
Unsolved Examples	274

5. ROTATING MACHINES	281—450
1. Direct Current (D.C.) Machines	281
1.1. Construction of D.C. machines	281
1.2. E.m.f. equation of a generator	289
1.3. Types of D.C. generators	292
1.4. Parallel operation of D.C. generators	296
1.5. Direct current motor	298
2. Synchronous Machines	332
2.1. Synchronous generator or alternator	332
2.2. Synchronous motor	346
3. Polyphase Induction Motor	354
3.1. General aspects	354
3.2. Classification of A.C. motors	355
3.3. Constructional details	355
3.4. Production of rotating magnetic field	359
3.5. Theory of operation of an induction motor	362
3.6. Slip	363
3.7. Frequency of rotor current	364
3.8. Rotor e.m.f. and rotor current	364

<u>Chapters</u>	<u>Pages</u>
3.9. <u>Torque and power</u>	365
3.10. Effect of change in supply voltage on starting torque	367
3.11. Effect of change in supply voltage on torque and slip	367
3.12. <u>Full-load torque and maximum torque</u>	368
3.13. <u>Starting torque and maximum torque</u>	368
3.14. <u>Torque-slip and torque-speed curves</u>	369
3.15. Operating characteristics of a 3-phase squirrel-cage induction motor	370
3.16. <u>Operating characteristics of a wound-rotor (slip ring) induction motor</u>	371
3.17. <u>Starting of induction motors</u>	378
3.18. <u>Squirrel-cage motors—advantages, disadvantages and applications</u>	382
3.19. <u>Wound rotor (or slip ring) induction motors—advantages, disadvantages and applications</u>	383
3.20. Comparison of a squirrel-cage and a slip ring (or phase wound) induction motors	384
4. Single Phase Motors	384
4.1. General aspects	384
4.2. Types of single-phase motor	384
4.3. <u>Single-phase induction motors</u>	385
4.4. Split-phase motors	388
4.5. <u>Single-phase commutator motors</u>	397
4.6. Single-phase synchronous motors	406
5. <u>Insulating Materials</u>	409
6. <u>Rating and Heating of D.C. Machines</u>	411
6.1. <u>Rating</u>	411
6.2. <u>Heating</u>	412
6.3. Selection of D.C. generators and motors	413
6.4. Types of D.C. machine enclosures	413
7. <u>Rating Specifications of A.C. Machines</u>	414
8. <u>Duty Cycles</u>	416
9. <u>Cooling of Electrical Machines</u>	417
<u>Highlights—D.C. Machines</u>	417
<u>Objective Type Questions</u>	419
<u>Theoretical Questions</u>	424
<u>Unsolved Examples</u>	426
<u>Highlights—Synchronous Machines</u>	429
<u>Objective Type Questions</u>	429
<u>Theoretical Questions</u>	432
<u>Unsolved Examples</u>	433
<u>Highlights—Polyphase Induction Motor</u>	433
<u>Objective Type Questions</u>	434
<u>Theoretical Questions</u>	440
<u>Unsolved Examples</u>	441
<u>Highlights—Single Phase Motors</u>	444
<u>Objective Type Questions</u>	445
<u>Theoretical Questions</u>	449
<hr/> 6. MEASURING INSTRUMENTS	451—489
1. <u>Introduction and Classification</u>	451
2. <u>Electrical Principles of Operation</u>	452
3. <u>Electrical Indicating Instruments</u>	452
3.1. <u>Essential features</u>	453

<i>Chapters</i>	<i>Pages</i>
3.2. Deflecting device	453
3.3. Controlling devices	453
3.4. Damping devices	454
4. Moving-Iron Instruments (Ammeters and Voltmeters)	457
4.1. Attraction type	457
4.2. Repulsion type	458
4.3. Advantages and disadvantages of moving-iron instruments	460
4.4. Sources of errors	460
5. Moving-Coil Instruments	460
5.1. Permanent-magnet moving-coil type (PMMC) instruments	460
5.2. Electrodynamic or dynamometer instruments	467
6. Rectifier Instruments	471
7. Wattmeters	472
7.1. Dynamometer wattmeter	473
7.2. Induction wattmeters	474
8. Integrating Meters (Energy Meters)	475
8.1. Essential characteristics of energy meters	475
8.2. Types of energy meters	476
8.3. Motor meters	476
8.4. Motor-driven meter—watt-hour meter	476
8.5. Induction type watt-hour meter	477
9. Measurement of Resistance	480
9.1. Voltmeter-ammeter method	480
9.2. Substitution method	481
9.3. Measurement of resistance by the wheatstone bridge	482
10. The Potentiometer	482
11. Meggar	484
12. Instrument Transformers	484
12.1. Potential transformers (P.T.)	485
12.2. Current transformers (C.T.)	485
Highlights	487
Theoretical Questions	488
Unsolved Examples	489
<hr/> 7. MISCELLANY	490—535
1. Characteristics of D.C. Generators	490
1.1. Separately excited generator	491
1.2. Building up the voltage of self-excited shunt generator	493
1.3. Shunt generator characteristics	494
1.4. Series generator	499
1.5. Compound wound generator	501
1.6. Applications of D.C. generators	503
2. Speed Control of D.C. Motors	506
2.1. Factors controlling the speed	506
2.2. Field control method	507
2.3. Rheostatic control	513
2.4. Voltage control	517
3. Electromechanical Energy Conversion	520
3.1. Introduction	520
3.2. Principle of energy conversion	521
3.3. Faraday's laws of electromagnetic induction	522

<i>Chapters</i>	<i>Pages</i>
3.4. Singly and multiply-excited magnetic field systems	523
3.5. Torque production in rotating machines	526
3.6. General analysis of electromechanical system	527
<i>Highlights</i>	534
<i>Objective Type Questions</i>	534
<i>Theoretical Questions</i>	535
<i>Unsolved Examples</i>	535
MISCELLANEOUS EXAMINATIONS' QUESTIONS—WITH SOLUTIONS	537—567
LABORATORY EXPERIMENTS	569—619

TO ALMIGHTY

D.C. Circuits and Network Analysis

1. Definitions of important terms.
2. Limitations of Ohm's law.
3. Kirchhoff's laws.
4. Applications of Kirchhoff's laws : Branch-current method—Maxwell's loop (or mesh) current method—Nodal voltage method.
5. Solving equations by determinants—Cramer's rule.
6. Superposition theorem.
7. Thevenin's theorem.
8. Norton's theorem.
9. Maximum power transfer theorem.
10. Delta star transformation.
11. Compensation theorem.
12. Reciprocity theorem.
13. Millman's theorem—Highlights—Objective Type Questions—Theoretical Questions—Unsolved Examples.

1. DEFINITIONS OF IMPORTANT TERMS

1. **Circuit.** A *conducting path* through which an electric current either flows or is intended to flow is called a *circuit*. The various elements of an electric circuit are called *parameters* (e.g. resistance, inductance and capacitance). These parameters may be *distributed* or *lumped*.
2. **Linear circuit.** The circuit whose parameters are *constant* (i.e. they do not change with voltage or current) is called a *linear circuit*.
3. **Non-linear circuit.** The circuit whose parameters *change* with voltage or current is called a *non-linear circuit*.
4. **Unilateral circuit.** A unilateral circuit is one whose properties or characteristics change with the direction of its operation (e.g. *diode rectifier*).
5. **Bilateral circuit.** It is that circuit whose properties or characteristics are same in either direction (e.g. *transmission line*).
6. **Electric network.** An electric network arises when a number of parameters or electric elements coexist or combine in any manner or arrangement.
7. **Active network.** An *active network* is one which contains one or more than one sources of e.m.f.
8. **Passive network.** A *passive network* is one which does not contain any source of e.m.f.
9. **Node.** A *node* is a junction in a circuit where two or more circuit elements are connected together.
10. **Branch.** The part of a network which lies between two junctions is called **branch**.

2. LIMITATIONS OF OHM'S LAW

In a series circuit or in any branch of a simple parallel circuit the calculation of the current is easily effected by the direct application of Ohm's law. But such a simple calculation is not possible if one of the branches of a parallel circuit contains a source of e.m.f., or if the current is to be calculated in a part of a network in which sources of e.m.f. may be present in several meshes or loops forming the network. The treatment of such cases is effected by the application of fundamental principles of electric circuits. These principles were correlated by Kirchhoff many years ago and enunciated in the form of *two laws*, which can be considered as the foundations of circuit analysis. Other, later, methods

have been developed, which when applied to special cases considerably shorten the algebra and arithmetic computation compared with the original Kirchhoff's method.

3. KIRCHHOFF'S LAWS

For complex circuit computations, the following two laws first stated by Gutsav R. Kirchhoff (1824-87) are indispensable.

First law (Point or current law). *The sum of the currents entering a junction is equal to the sum of the currents leaving the junction.* Refer Fig. 1.

If the currents *towards* a junction are considered positive and those *away from* the same junction negative, then this law states that the *algebraic sum of all currents meeting at a common junction is zero.*

i.e. Σ Currents entering = Σ currents leaving

$$I_1 + I_3 = I_2 + I_4 + I_5 \quad \dots [1(a)]$$

$$\text{or} \quad I_1 + I_3 - I_2 - I_4 - I_5 = 0 \quad \dots [1(b)]$$

Second law (Mesh or voltage law). *The sum of the e.m.fs (rises of potential) around any closed loop of a circuit equals the sum of the potential drops in that loop.* Considering a rise of potential as positive (+) and a drop of potential as negative (-), the *algebraic sum of potential differences (voltages) around a closed loop of a circuit is zero :*

$$\Sigma E - \Sigma IR \text{ drops} = 0 \text{ (around closed loop)}$$

$$\text{i.e.} \quad \Sigma E = \Sigma IR \quad \dots [2(a)]$$

$$\text{or} \quad \Sigma \text{ Potential rises} = \Sigma \text{ potential drops} \quad \dots [2(b)]$$

To apply this law in practice, assume an arbitrary current direction for each branch current. The end of the resistor through which the current enters, is then positive, with respect to the other end. *If the solution for the current being solved turns out negative, then the direction of that current is opposite to the direction assumed.*

In tracing through any single circuit, whether it is by itself or a part of a network, the following rules must be applied :

1. A *voltage drop exists* when tracing through a resistance *with or in the same direction as the current*, or through a battery or generator against their voltage, that is from positive (+) to negative (-). Refer Fig. 2.

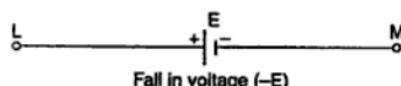
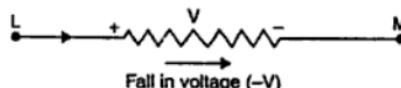


Fig. 2

2. A *voltage rise exists* when tracing through a resistance *against or in opposite direction to the current* or through a battery or a generator with their voltage that is from negative (-) to positive (+). Refer Fig. 3.

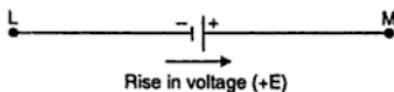
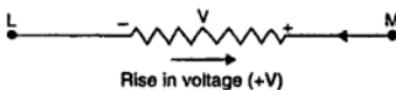


Fig. 3

Illustration. Consider a circuit shown in Fig. 4.

Considering the loop ABEFA, we get

$$-I_1 R_1 - I_3 R_3 + E_1 = 0$$

or $E_1 = I_1 R_1 + I_3 R_3$

(where $I_3 = I_1 + I_2$) ... (i)

Considering the loop BCDEB, we have

$$I_2 R_2 - E_2 + I_3 R_3 = 0 \quad \dots (ii)$$

or $E_2 = I_2 R_2 + I_3 R_3$

If E_1 , E_2 , R_1 , R_2 and R_3 are known, then I_1 , I_2 and I_3 can be calculated from eqns. (i) and (ii).

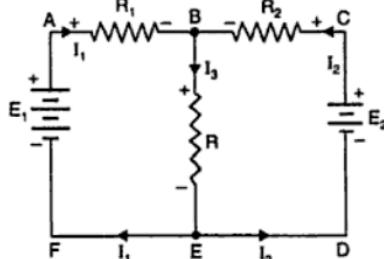


Fig. 4

4. APPLICATIONS OF KIRCHHOFF'S LAWS

Kirchhoff's laws may be employed in the following methods of solving networks :

1. Branch-current method
2. Maxwell's loop (or mesh) current method
3. Nodal voltage method.

4.1. Branch-Current Method

For a multi-loop circuit the following procedure is adopted for writing equations :

1. Assume currents in different branch of the network
2. Write down the smallest number of voltage drop loop equations so as to include all circuit elements ; these loop equations are independent.

If there are n nodes of three or more elements in a circuit, then write $(n - 1)$ equations as per current law.

3. Solve the above equations simultaneously.

The assumption made about the directions of the currents initially is arbitrary. In case the actual direction is opposite to the assumed one, it will be reflected as a negative value for that current in the answer.

The branch-current method (the most primitive one) involves more labour and is not used except for very simple circuits.

Example 1. In the circuit of Fig. 5, find the current through each resistor and voltage drop across each resistor.

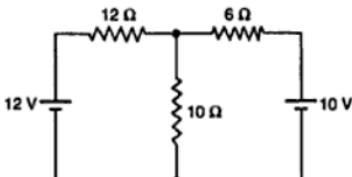


Fig. 5

Solution. Let the currents be as shown in Fig. 6.

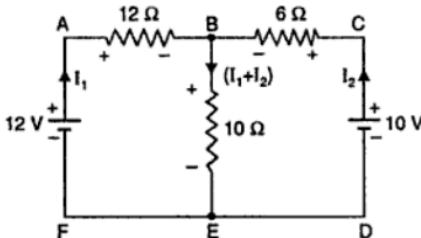


Fig. 6

Applying Kirchhoff's voltage law to the circuit ABEFA, we get

$$\begin{aligned} -12I_1 - 10(I_1 + I_2) + 12 &= 0 \\ -22I_1 - 10I_2 + 12 &= 0 \\ +11I_1 + 5I_2 - 6 &= 0 \end{aligned} \quad \dots(i)$$

or

Circuit BCDEB gives,

$$\begin{aligned} 6I_2 - 10 + 10(I_1 + I_2) &= 0 \\ 10I_1 + 16I_2 - 10 &= 0 \\ 5I_1 + 8I_2 - 5 &= 0 \end{aligned} \quad \dots(ii)$$

Multiplying eqn. (i) by 5 and eqn. (ii) by 11 and subtracting, we get

$$\begin{array}{r} 55I_1 + 25I_2 - 30 = 0 \\ 55I_1 + 88I_2 - 55 = 0 \\ \hline - & - & + \\ -63I_2 + 25 & = 0 \end{array}$$

$$I_2 = 0.397 \text{ A}$$

i.e.

Substituting this value in eqn. (i), we get

$$\begin{aligned} 11I_1 + 5 \times 0.397 - 6 &= 0 \\ I_1 &= 0.365 \text{ A} \end{aligned}$$

i.e.

Hence, Current through 12Ω resistor, $I_1 = 0.365 \text{ A. (Ans.)}$

Current through 6Ω resistor, $I_2 = 0.397 \text{ A. (Ans.)}$

Current through 10Ω resistor, $I_1 + I_2 = 0.762 \text{ A. (Ans.)}$

The voltage drop across :

12Ω resistor $= 0.365 \times 12 = 4.38 \text{ V. (Ans.)}$

6Ω resistor $= 0.397 \times 6 = 2.38 \text{ V. (Ans.)}$

10Ω resistor $= 0.762 \times 10 = 7.62 \text{ V. (Ans.)}$

Example 2. Find the magnitude and direction of currents in each of the batteries shown in Fig. 7.

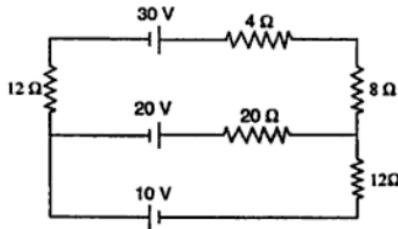


Fig. 7

Solution. Let the directions of currents I_1 , I_2 and I_3 in the batteries be as shown in Fig. 8.

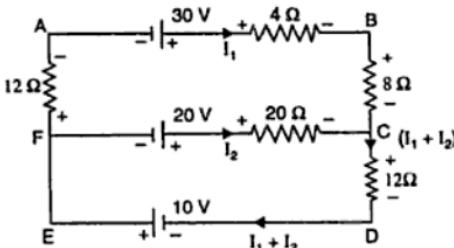


Fig. 8

Applying Kirchhoff's voltage law to the circuit ABCFA, we get

$$\begin{aligned} 30 - 4I_1 - 8I_1 + 20I_2 - 20 - 12I_1 &= 0 \\ -24I_1 + 20I_2 + 10 &= 0 \\ \text{or } 12I_1 - 10I_2 - 5 &= 0 \end{aligned} \quad \dots(i)$$

Circuit ECDEF gives,

$$\begin{aligned} 20 - 20I_2 - 12(I_1 + I_2) + 10 &= 0 \\ 20 - 20I_2 - 12I_1 - 12I_2 + 10 &= 0 \\ -12I_1 - 32I_2 + 30 &= 0 \\ \text{or } 6I_1 + 16I_2 - 15 &= 0 \end{aligned} \quad \dots(ii)$$

Multiplying eqn. (ii) by 2 and subtracting it from (i), we get

$$\begin{aligned} -42I_2 + 25 &= 0 \\ I_2 &= 0.595 \text{ A} \end{aligned}$$

Substituting this value of I_2 in eqn. (i), we get

$$\begin{aligned} 12I_1 - 10 \times 0.595 - 5 &= 0 \\ I_1 &= 0.912 \text{ A} \end{aligned}$$

or

Hence current through,

$$\begin{aligned} \text{30 V battery, } I_1 &= 0.912 \text{ A. (Ans.)} \\ \text{20 V battery, } I_2 &= 0.595 \text{ A. (Ans.)} \\ \text{10 V battery, } (I_1 + I_2) &= 1.507 \text{ A. (Ans.)} \end{aligned}$$

Example 3. The terminal resistances of batteries A and B are 2.5Ω and 2Ω respectively. The battery has an e.m.f. of 20 volts. A resistance of 10Ω is connected across the battery terminals. Calculate :

- (i) The discharge current of battery A, the discharge current of battery B being 1.75 A.
- (ii) The e.m.f. of battery B.
- (iii) The energy dissipated in 10Ω resistance in 40 minutes.

Solution. Refer Fig. 9.

(i) I_1 :

Applying Kirchhoff's voltage law to the circuit LMNPSQL

$$\begin{aligned} 20 - 2.5I_1 + 1.75 \times 2 - E_B &= 0 \\ E_B + 2.5I_1 - 23.5 &= 0 \end{aligned} \quad \dots(i)$$

i.e.

Circuit LMNPTL gives,

$$20 - 2.5I_1 - 10(I_1 + I_2) = 0$$

i.e.

$$20 - 2.5I_1 - 10(I_1 + 1.75) = 0$$

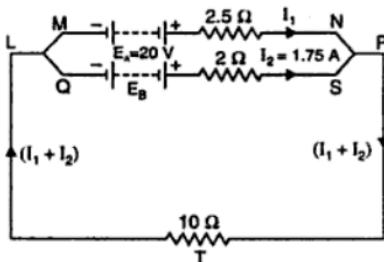


Fig. 9

or
or

Hence discharge current of battery A = $I_1 = 0.2\text{ A}$. (Ans.)

(ii) E_B :

Substituting the value of I_1 in eqn. (i), we get

$$E_B + 2.5 \times 0.2 - 23.5 = 0$$

$$E_B = 23\text{ V}$$

Hence e.m.f. of battery B, $E_B = 23\text{ V}$. (Ans.)

(iii) Energy dissipated in 10Ω resistor :

$$\begin{aligned} \text{Energy dissipated} &= I^2 R t \\ &= (I_1 + I_2)^2 \times 10 \times (40 \times 60) \text{ joules} \\ &= (0.2 + 1.75)^2 \times 10 \times (40 \times 60) \text{ joules} \\ &= 91260 \text{ joules. (Ans.)} \end{aligned}$$

Example 4. A battery having an e.m.f. of 110 V and an internal resistance of 0.2Ω is connected in parallel with another battery with e.m.f. of 100 V and a resistance of 0.25Ω . The two in parallel are placed in series with a regulating resistance of 5 ohms and connected across 220 V mains. Calculate :

(i) The magnitude and direction of the current in each battery.

(ii) The total current taken from the mains supply.

Solution. Refer Fig. 10.

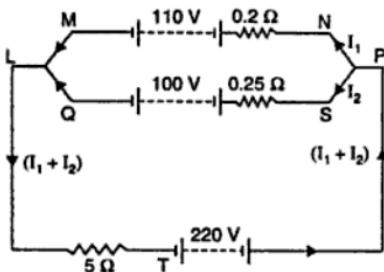


Fig. 10

(i) I_1 : , I_2 :Let the directions of flow of currents I_1 and I_2 be as shown in Fig. 10.

Applying Kirchhoff's voltage law to LMNPSQL, we get

$$\begin{aligned} 110 + 0.2I_1 - 0.25I_2 - 100 &= 0 \\ 0.2I_1 - 0.25I_2 &= -10 \\ I_1 - 1.25I_2 &= -50 \end{aligned} \quad \dots(i)$$

or

Circuit LMNPTL gives,

$$\begin{aligned} 110 + 0.2I_1 - 220 + 5(I_1 + I_2) &= 0 \\ 5.2I_1 + 5I_2 &= 110 \\ I_1 + 0.96I_2 &= 21.15 \end{aligned} \quad \dots(ii)$$

Subtracting (ii) from (i), we get

$$\begin{aligned} -2.21I_2 &= -71.15 \\ I_2 &= 32.19 \text{ A. (Ans.)} \\ I_1 &= -9.75 \text{ A. (Ans.)} \end{aligned}$$

and Since I_1 turns out to be negative, its actual direction of flow is *opposite* to that shown in Fig. 10. In other words it is *not a charging current but a discharging one*. However, I_2 is a *charging current*.(ii) $(I_1 + I_2)$:

The total current taken from the mains supply,

$$I_1 + I_2 = -9.75 + 32.19 = 22.44 \text{ A. (Ans.)}$$

Example 5. In the circuit shown in the Fig. 11 determine :

(i) All the currents in the network.

(ii) Voltages between the points.

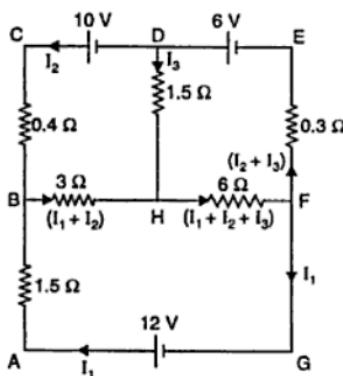
Solution. Refer Fig. 11.

Fig. 11

(i) All the currents in the network :

Let the directions of the currents be as shown in the Fig. 11.

Applying Kirchhoff's voltage law to the circuit BCDHB, we get

$$\begin{aligned} 0.4I_2 - 10 - 1.5I_3 + 3(I_1 + I_2) &= 0 \\ 3I_1 + 3.4I_2 - 1.5I_3 &= 10 \end{aligned} \quad \dots(i)$$

i.e.

Circuit HDEFH gives,

$$\begin{aligned} 1.5I_3 - 6 + 0.3(I_2 + I_3) + 6(I_1 + I_2 + I_3) &= 0 \\ 6I_1 + 6.3I_2 + 7.8I_3 &= 6 \end{aligned} \quad \dots(ii)$$

Circuit ABHFGA gives,

$$\begin{aligned} -1.5I_1 - 3(I_1 + I_2) - 6(I_1 + I_2 + I_3) + 12 &= 0 \\ -10.5I_1 - 9I_2 - 6I_3 + 12 &= 0 \\ 10.5I_1 + 9I_2 + 6I_3 &= 12 \end{aligned} \quad \dots(iii)$$

i.e.

Multiplying eqn. (ii) by 2 and subtracting eqn. (ii) from eqn. (i), we get

$$0.5I_2 - 10.8I_3 = 14 \quad \dots(iv)$$

Multiplying eqn. (ii) by 10.5 and eqn. (iii) by 6 and subtracting eqn. (iii) from eqn. (ii), we get

$$12.15I_2 + 45.9I_3 = -9 \quad \dots(v)$$

Multiplying eqn. (iv) by 12.15 and eqn. (v) by 0.5 and subtracting eqn. (v) from eqn. (iv), we get

$$-154.17I_3 = 174.6$$

$$I_3 = -1.132 \text{ A}$$

Substituting the value of I_3 in eqn. (iv), we get

$$0.5I_2 - 10.8 \times (-1.132) = 14$$

i.e.

$$I_2 = 3.549 \text{ A}$$

Substituting the values of I_2 and I_3 in eqn. (iii), we get

$$10.5I_1 + 9 \times 3.549 + 6 \times (-1.132) = 12$$

i.e.

$$I_1 = -1.252 \text{ A}$$

Hence the directions of I_1 and I_3 are actually opposite to the assumed directions.

The current between B and H = $I_1 + I_2 = -1.252 + 3.549 = 2.297 \text{ A}$. (Ans.)

The current between H and F = $I_1 + I_2 + I_3 = -1.252 + 3.549 - 1.132 = 1.165 \text{ A}$. (Ans.)

The current between H and F (and E) = $I_1 + I_3 = 3.549 - 1.132 = 2.417 \text{ A}$. (Ans.)

(ii) Voltage between the points :

Voltage across BH = $2.297 \times 3 = 6.891 \text{ V}$. (Ans.)

Voltage across HF = $1.165 \times 6 = 6.99 \text{ V}$. (Ans.)

Voltage across CE = $12 - (-1.252 \times 1.5) = 13.878 \text{ V}$. (Ans.)

Example 6. Determine the magnitude and direction of flow of current in the branch MN for the circuit shown in Fig. 12.

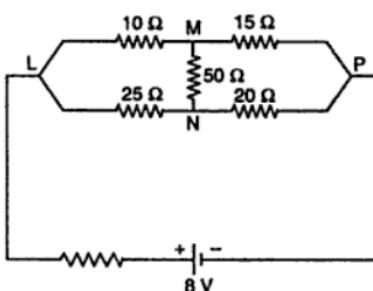


Fig. 12

Solution. Refer Fig. 13.

Let the directions and magnitudes of the currents flowing in the various circuits be as shown in Fig. 13.

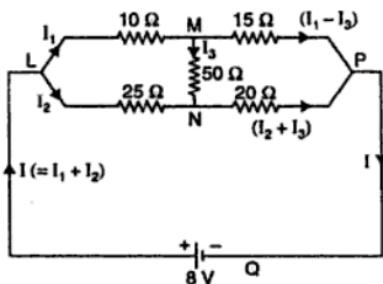


Fig. 13

Applying Kirchhoff's voltage law to the circuit LMNL, we get

$$\begin{aligned} -10I_1 - 50I_3 + 25I_2 &= 0 \\ I_1 - 2.5I_2 + 5I_3 &= 0 \end{aligned} \quad \dots(i)$$

or

Circuit MPNM gives,

$$\begin{aligned} -15(I_1 - I_3) + 20(I_2 + I_3) + 50I_3 &= 0 \\ -15I_1 + 20I_2 + 85I_3 &= 0 \\ I_1 - 1.33I_2 - 5.66I_3 &= 0 \end{aligned} \quad \dots(ii)$$

or

Circuit LNPQL gives,

$$\begin{aligned} -25I_2 - 20(I_2 + I_3) + 8 &= 0 \\ -45I_2 - 20I_3 + 8 &= 0 \\ I_2 + 0.44I_3 &= 0.177 \end{aligned} \quad \dots(iii)$$

or

Subtracting eqn. (ii) from eqn. (i), we get

$$\begin{aligned} -1.17I_2 + 10.66I_3 &= 0 \\ I_2 - 9.11I_3 &= 0 \end{aligned} \quad \dots(iv)$$

or

Subtracting eqn. (iv) from eqn. (iii), we get

$$\begin{aligned} 9.55I_3 &= 0.177 \\ I_3 &= 0.0185 \text{ A.} \end{aligned}$$

Hence magnitude of current (I_3) flowing through the branch MN = 0.0185 A (from M to N). (Ans.)

Example 7. Determine the current in the $4\ \Omega$ resistance of the circuit shown in Fig. 14.

(Indore University)

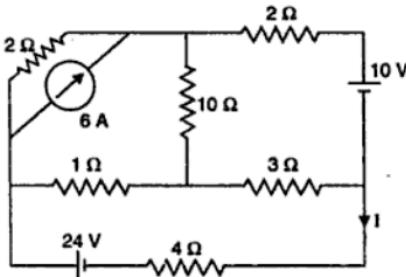


Fig. 14

Solution. Refer Fig. 15.

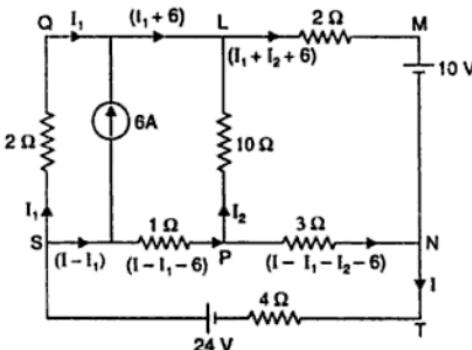


Fig. 15

Let the directions of various currents in different circuits be as shown in the Fig. 15.

Applying Kirchhoff's voltage law to the circuit **SQLPS**, we get

$$\begin{aligned} -2I_1 + 10I_2 + 1(I - I_1 - 6) &= 0 \\ I - 3I_1 + 10I_2 &= 6 \end{aligned} \quad \dots(i)$$

Circuit **LMNPL** gives,

$$\begin{aligned} -2(I_1 + I_2 + 6) - 10 + 3(I - I_1 - I_2 - 6) - 10I_2 &= 0 \\ 3I - 5I_1 - 15I_2 &= 40 \end{aligned} \quad \dots(ii)$$

Circuit **SPNTS** gives,

$$\begin{aligned} -1(I - I_1 - 6) - 3(I - I_1 - I_2 - 6) - 4I + 24 &= 0 \\ -8I + 4I_1 + 3I_2 &= -48 \\ 8I - 4I_1 - 3I_2 &= 48 \end{aligned} \quad \dots(iii)$$

or Multiplying eqn. (i) by 3 and subtracting eqn. (ii) from eqn. (i), we get

$$\begin{aligned} -4I_1 + 45I_2 &= -22 \\ I_1 - 11.25I_2 &= 5.5 \end{aligned} \quad \dots(iv)$$

Multiplying eqn. (i) by 8 and subtracting eqn. (iii) from eqn. (i), we get

$$-20I_1 + 83I_2 = 0 \quad \dots(v)$$

Multiplying eqn. (iv) by 20 and adding eqn. (v), we get

$$-142I_2 = 110$$

$$I_2 = -0.774 \text{ A}$$

$$I_1 = -3.212 \text{ A}$$

Substituting the values of I_1 and I_2 in eqn. (i), we get

$$I - 3 \times (-3.212) + 10 \times (-0.774) = 6$$

i.e.

$$I = 23.37 \text{ A. (Ans.)}$$

Example 8. Determine the current in each of the resistors of the network shown in the Fig. 16.

Solution. Refer Fig. 16.

Let the current directions be as shown in the Fig. 16.

Applying Kirchhoff's voltage law to the circuit ABDA, we get

$$-3I_1 - 8I_3 + 4I_2 = 0 \quad \dots(i)$$

$$\text{or} \quad 3I_1 - 4I_2 + 8I_3 = 0 \quad \dots(ii)$$

Circuit BCDB gives,

$$-5(I_1 - I_3) + 2(I_2 + I_3) + 8I_3 = 0$$

$$-5I_1 + 2I_2 + 15I_3 = 0 \quad \dots(iii)$$

$$5I_1 - 2I_2 - 15I_3 = 0$$

Circuit ADCEA gives,

$$-4I_2 - 2(I_2 + I_3) + 2 = 0$$

$$-6I_2 - 2I_3 = -2 \quad \dots(iv)$$

$$\text{or} \quad 3I_2 + I_3 = 1 \quad \dots(v)$$

Multiplying eqn. (i) by 5 and eqn. (ii) by 3 and subtracting (ii) from (i), we get

$$15I_1 - 20I_2 + 40I_3 = 0$$

$$15I_1 - 6I_2 - 45I_3 = 0$$

$$\underline{\underline{-}} \quad \underline{+} \quad \underline{+}$$

$$-14I_2 + 85I_3 = 0$$

$$14I_2 - 85I_3 = 0 \quad \dots(vi)$$

or Multiplying eqn. (iii) by 14 and eqn. (iv) by 3 and subtracting (iv) from (iii), we get

$$42I_2 + 14I_3 = 14$$

$$42I_2 - 255I_3 = 0$$

$$\underline{\underline{-}} \quad \underline{+}$$

$$269I_3 = 14$$

$$I_3 = 0.052 \text{ A}$$

From eqn. (iv), $I_2 = 0.316 \text{ A}$

From eqn. (i), $I_1 = 0.283 \text{ A}$

Hence, Current through 3Ω resistor = $I_1 = 0.283 \text{ A}$. (Ans.)

Current through 4Ω resistor = $I_2 = 0.316 \text{ A}$. (Ans.)

Current through 8Ω resistor = $I_3 = 0.052 \text{ A}$. (Ans.)

Current through 5Ω resistor = $I_1 - I_3 = 0.231 \text{ A}$. (Ans.)

Current through 2Ω resistor = $I_2 + I_3 = 0.368 \text{ A}$. (Ans.)

Example 9. Determine the branch currents in the network of Fig. 17.

Solution. Refer Fig. 17. Let the current directions be as shown.

Applying Kirchhoff's voltage law to the circuit ABDA, we get

$$5 - I_1 \times 1 - I_3 \times 1 + I_2 \times 1 = 0$$

$$I_1 - I_2 + I_3 = 5 \quad \dots(i)$$

or Circuit BCDB gives,

$$-(I_1 - I_3) \times 1 + 5 + (I_2 + I_3) \times 1 + I_3 \times 1 = 0$$

$$-I_1 + I_2 + 3I_3 = -5$$

$$I_1 - I_2 - 3I_3 = 5 \quad \dots(ii)$$

or Circuit ADCEA gives,

$$-I_2 \times 1 - (I_2 + I_3) \times 1 + 10 - (I_1 + I_2) \times 1 = 0$$

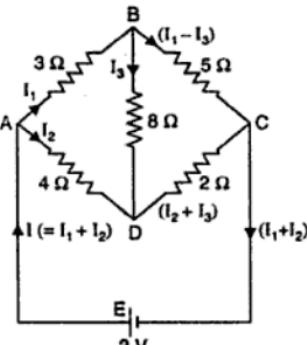


Fig. 16

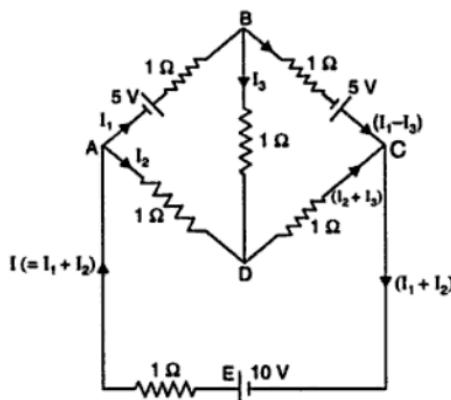


Fig. 17

$$-I_1 - 3I_2 - I_3 = -10$$

$$I_1 + 3I_2 + I_3 = 10$$

or

Subtracting (ii) from (i), we get,

$$I_3 = 0$$

...(iii)

From (i), we have,

$$I_1 - I_2 = 5$$

...(iv)

and

from (iii), we have,

$$I_1 + 3I_2 = 10$$

...(v)

By solving (iv) and (v), we get,

$$I_2 = 1.25 \text{ A}$$

$$I_1 = 6.25 \text{ A}$$

and

Hence, Current in branch AB = 6.25 A. (Ans.)

Current in branch BC = 6.25 A. (Ans.)

Current in branch BD = 0. (Ans.)

Current in branch AD = 1.25 A. (Ans.)

Current in branch DC = 1.25 A. (Ans.)

Current in branch CA = 7.5 A. (Ans.)

Example 10. Find the current in the galvanometer arm of the wheatstone bridge shown in Fig. 18.

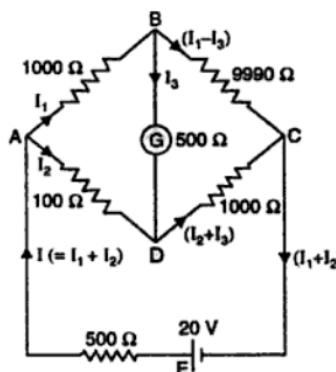


Fig. 18

Solution. Refer Fig. 18. Let the current directions be as shown.

Applying Kirchhoff's voltage law to the circuit ABDA, we get

$$\begin{aligned} -1000I_1 - 500I_3 + 100I_2 &= 0 \\ I_1 - 0.1I_2 + 0.5I_3 &= 0 \end{aligned} \quad \dots(i)$$

Circuit BCDB gives,

$$\begin{aligned} -9990(I_1 - I_3) + 1000(I_2 + I_3) + 500I_3 &= 0 \\ -9990I_1 + 1000I_2 + 11490I_3 &= 0 \\ I_1 - 0.1001I_2 - 1.15I_3 &= 0 \end{aligned} \quad \dots(ii)$$

Circuit ADCEA gives,

$$\begin{aligned} -100I_2 - 1000(I_2 + I_3) + 20 - 500(I_1 + I_2) &= 0 \\ -500I_1 - 1600I_2 - 1000I_3 &= -20 \\ I_1 + 3.2I_2 + 2I_3 &= 0.04 \end{aligned} \quad \dots(iii)$$

Subtracting (ii) from (i), we get

$$0.0001I_2 + 1.65I_3 = 0 \quad \dots(iv)$$

Subtracting (iii) from (ii), we get

$$+3.3001I_2 + 3.15I_3 = +0.04 \quad \dots(v)$$

Solving (iv) and (v), we get, $I_3 = 0.735 \times 10^{-6}$ A

Hence current in the galvanometer arm = $0.735 \mu\text{A}$. (Ans.)

Example 11. Determine the current supplied by the battery in the circuit shown in Fig. 19.
(Bombay University)

Solution. Refer Fig. 19.

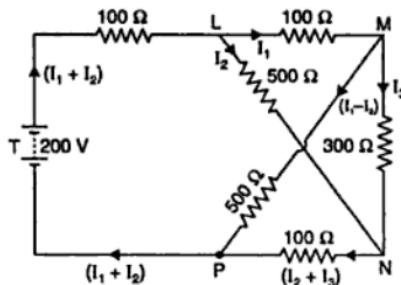


Fig. 19

Applying Kirchhoff's voltage law to the circuit LMNL, we get

$$\begin{aligned} -100I_1 - 300I_3 + 500I_2 &= 0 \\ I_1 - 5I_2 + 3I_3 &= 0 \end{aligned} \quad \dots(i)$$

Circuit MNPM gives,

$$\begin{aligned} -300I_3 - 100(I_2 + I_3) + 500(I_1 - I_3) &= 0 \\ 500I_1 - 100I_2 - 900I_3 &= 0 \\ I_1 - 0.2I_2 - 1.8I_3 &= 0 \end{aligned} \quad \dots(ii)$$

Circuit LMPTL gives,

$$-100I_1 - 500(I_1 - I_3) + 200 - 100(I_1 + I_2) = 0$$

$$\begin{aligned} -700I_1 - 100I_2 + 500I_3 &= -200 \\ I_1 + 0.143I_2 - 0.714I_3 &= 0.286 \end{aligned} \quad \dots(iii)$$

Multiplying (i) by 1.8 and (ii) by 3 and adding, we get

$$\begin{array}{r} 1.8I_1 - 9I_2 + 5.4I_3 = 0 \\ 3I_1 - 0.6I_2 - 5.4I_3 = 0 \\ \hline 4.8I_1 - 9.6I_2 = 0 \\ I_1 - 2I_2 = 0 \end{array}$$

or

... (iv)

Multiplying (ii) by 0.714 and (iii) by 1.8 and subtracting, we get

$$\begin{array}{r} 0.714I_1 - 0.143I_2 - 1.285I_3 = 0 \\ 1.8I_1 + 0.257I_2 - 1.285I_3 = 0.515 \\ \hline - & - & + & - \\ -1.086I_1 - 0.4I_2 & = -0.515 \\ I_1 + 0.368I_2 & = 0.474 \end{array}$$

or

... (v)

Subtracting (v) from (iv), we get $2.368I_2 = 0.474$

i.e.
and

$$I_2 = 0.2 \text{ A}$$

$$I_1 = 0.4 \text{ A}$$

\therefore Current supplied by the battery $= I_1 + I_2 = 0.2 + 0.46 = 0.6 \text{ A. (Ans.)}$

4.2. Maxwell's Loop (or Mesh) Current Method

The method of *loop* or *mesh* currents is generally used in solving networks having some degree of complexity. Such a degree of complexity already begins for a network of three meshes. It might even be convenient at times to use the method of loop or mesh currents for solving a two-mesh circuit.

The *mesh-current method* is preferred to the general or branch-current method because the unknowns in the initial stage of solving a network are equal to the number of meshes, i.e., the mesh currents. The necessity of writing the node-current equations, as done in the general or branch-current method where branch currents are used, is *obviated*. There are as many mesh-voltage equations as these are independent loop or mesh currents. Hence, the M-mesh currents are obtained by solving the M-mesh voltages or loop equations for M unknowns. After solving for the mesh currents, only a matter of resolving the confluent mesh currents into the respective branch currents by very simple algebraic manipulations is required.

This method eliminates a great deal of tedious work involved in branch-current method and is best suited when energy sources are voltage sources rather than current sources. This method can be used only for planar circuits.

The procedure for writing the equations is as follows :

1. Assume the smallest number of mesh currents so that at least one mesh current links every element. As a matter of convenience, all mesh currents are assumed to have a *clockwise direction*.

The number of mesh currents is equal to the number of meshes in the circuit.

2. For each mesh write down the Kirchhoff's voltage law equation. Where more than one mesh current flows through an element, the algebraic sum of currents should be used. The algebraic sum of mesh currents may be sum or the difference of the currents flowing through the element depending on the direction of mesh currents.

3. Solve the above equations and from the mesh currents find the branch currents.

Fig. 20 shows two batteries E_1 and E_2 connected in a network consisting of three resistors. Let the loop currents for two meshes be I_1 and I_2 (both clockwise-assumed). It is obvious that current through R_3 (when considered as a part of first loop) is $(I_1 - I_2)$. However, when R_3 is considered part of the second loop, current through it is $(I_2 - I_1)$.

Applying Kirchhoff's voltage law to the two loops, we get

$$E_1 - I_1 R_1 - R_3(I_1 - I_2) = 0$$

or $E_1 - I_1(R_1 + R_3) + I_2 R_3 = 0 \quad \dots\text{loop 1}$

Similarly, $-I_2 R_2 - E_2 - R_3(I_2 - I_1) = 0$

$$-I_2 R_2 - E_2 - I_2 R_3 + I_1 R_3 = 0$$

or $I_1 R_3 - I_2(R_2 + R_3) - E_2 = 0 \quad \dots\text{loop 2}$

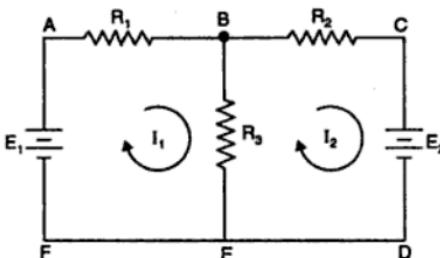


Fig. 20

The above two equations can be solved not only to find loop currents but branch currents as well.

Example 12. Determine the currents through various resistors of the circuit shown in Fig. 21 using the concept of mesh currents.

Solution. Refer Fig. 21.

Since there are two meshes, let the loop currents be as shown.

Applying Kirchhoff's law to loop 1, we get

$$24 - 4I_1 - 2(I_1 - I_2) = 0$$

$$-6I_1 + 2I_2 + 24 = 0$$

or $3I_1 - I_2 = 12 \quad \dots(i)$

For loop 2, we have

$$-2(I_2 - I_1) - 6I_2 - 12 = 0$$

$$2I_1 - 8I_2 - 12 = 0$$

$$I_1 - 4I_2 = 6 \quad \dots(ii)$$

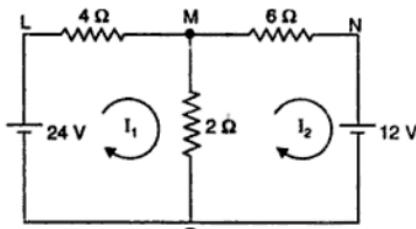


Fig. 21

Solving (i) and (ii), we get, $I_1 = \frac{42}{11} \text{ A}$

and

$$I_2 = -\frac{6}{11} \text{ A}$$

Hence Current through 4Ω resistor = $\frac{42}{11} \text{ A}$ (from L to M). (Ans.)

Current through 6Ω resistor = $\frac{6}{11} \text{ A}$ (from N to M). (Ans.)

Current through 2Ω resistor = $\frac{42}{11} - \left(-\frac{6}{11}\right) = \frac{48}{11} \text{ A}$ (from M to P). (Ans.)

Example 13. Determine the current supplied by each battery in the circuit shown in Fig. 22.
(Aligarh University)

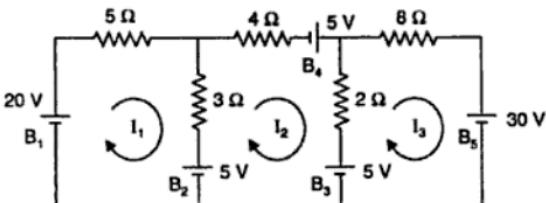


Fig. 22

Solution. Refer Fig. 22.

As there are three meshes, let the three loop currents be as shown.

Applying Kirchhoff's law to loop 1, we get

$$20 - 5I_1 - 3(I_1 - I_2) - 5 = 0$$

or

$$8I_1 - 3I_2 = 15 \quad \dots(i)$$

For loop 2, we have

$$-4I_2 + 5 - 2(I_2 - I_3) + 5 + 5 - 3(I_2 - I_1) = 0$$

$$3I_1 - 9I_2 + 2I_3 = -15 \quad \dots(ii)$$

For loop 3, we have

$$-8I_3 - 30 - 5 - 2(I_3 - I_2) = 0$$

$$2I_2 - 10I_3 = 35 \quad \dots(iii)$$

Eliminating I_1 from (i) and (ii), we get

$$63I_2 - 16I_3 = 165 \quad \dots(iv)$$

Solving (iii) and (iv), we get

$$I_2 = 1.82 \text{ A} \text{ and } I_3 = -3.15 \text{ A}$$

(- ve sign means direction of current is counter-clockwise)

Substituting the value of I_2 in (i), we get

$$I_1 = 2.56 \text{ A}$$

Current through battery B_1 (discharging current) = $I_1 = 2.56 \text{ A}$. (Ans.)

Current through battery B_2 (charging current) = $I_1 - I_2 = 2.56 - 1.82 = 0.74 \text{ A}$. (Ans.)

Current through battery B_3 (discharging current) = $I_2 + I_3 = 1.82 + 3.15 = 4.97 \text{ A}$. (Ans.)

Current through battery B_4 (discharging current) = $I_2 = 1.82 \text{ A}$. (Ans.)

Current through battery B_5 (discharging current) = $I_3 = 3.15 \text{ A}$. (Ans.)

Example 14. Determine the currents through the different branches of the bridge circuit shown in Fig. 23.

Solution. Refer Fig. 23.

The three mesh currents are assumed as shown.

The equations for the three meshes are :

$$\text{For loop 1 : } 240 - 20(I_1 - I_2) - 50(I_1 - I_3) = 0$$

$$\text{or } -70I_1 + 20I_2 + 50I_3 = -240 \quad \dots(i)$$

$$\text{or } 70I_1 - 20I_2 - 50I_3 = 240 \quad \dots(ii)$$

$$\text{For loop 2 : } -30I_2 - 40(I_2 - I_3) - 20(I_2 - I_1) = 0$$

$$\text{or } 20I_1 - 90I_2 + 40I_3 = 0$$

$$\text{or } 2I_1 - 9I_2 + 4I_3 = 0 \quad \dots(iii)$$

$$\text{For loop 3 : } -60I_3 - 50(I_3 - I_1) - 40(I_3 - I_2) = 0$$

$$50I_1 + 40I_2 - 150I_3 = 0$$

$$5I_1 + 4I_2 - 15I_3 = 0 \quad \dots(iv)$$

Solving these equations, we get

$$I_1 = 6.10 \text{ A}, I_2 = 2.56 \text{ A}, I_3 = 2.72 \text{ A}$$

Current through 30Ω resistor = $I_2 = 2.56 \text{ A}$ (A to B).

(Ans.)

Current through 60Ω resistor = $I_3 = 2.72 \text{ A}$ (B to C). (Ans.)

Current through 20Ω resistor = $I_1 - I_2 = 6.10 - 2.56 = 3.54 \text{ A}$ (A to D). (Ans.)

Current through 50Ω resistor = $I_1 - I_3 = 6.10 - 2.72 = 3.38 \text{ A}$ (D to C). (Ans.)

Current through 40Ω resistor = $I_3 - I_2 = 2.72 - 2.56 = 0.16 \text{ A}$ (D to B). (Ans.)

4.3. Nodal Voltage Method

Under this method the following procedure is adopted :

1. Assume the voltages of the different independent nodes.
2. Write the equations for each node as per Kirchhoff's current law.
3. Solve the above equations to get the node voltages.
4. Calculate the branch currents from the values of node voltages.

Let us consider the circuit shown in the Fig. 24 L and M are the two independent nodes ; M can be taken as the reference node. Let the voltage of node L (with respect to M) be V_L .

Using Kirchhoff's law, we get

$$I_1 + I_2 = I_3 \quad \dots(3)$$

$$\text{Ohm's law gives } I_1 = \frac{V_1}{R_1} = \frac{(E_1 - V_L)}{R_1} \quad \dots(4)$$

$$I_2 = \frac{V_2}{R_2} = \frac{(E_2 - V_L)}{R_2} \quad \dots(5)$$

$$I_3 = \frac{V_3}{R_3} = \frac{V_L}{R_3}$$

$$\frac{E_1 - V_L}{R_1} + \frac{E_2 - V_L}{R_2} = \frac{V_L}{R_3} \quad \dots(6)$$

Rearranging the terms, we get

$$V_L \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{E_1}{R_1} - \frac{E_2}{R_2} = 0 \quad \dots(6)$$

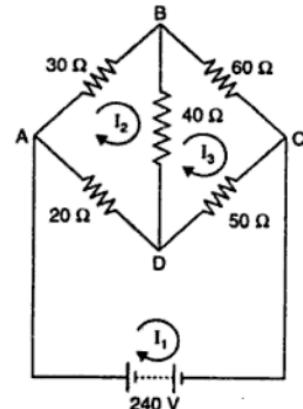


Fig. 23

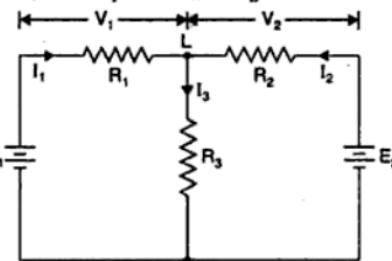


Fig. 24

It may be noted that the above nodal equation contains the following terms :

(i) The node voltage multiplied by the sum of all conductances connected to that anode. This term is *positive*.

(ii) The node voltage at the other end of each branch (connected to this node) multiplied by the conductance of branch. These terms are *negative*.

- In this method of solving a network the *number of equations required for the solution is one less than the number of independent nodes in the network.*
- In general the nodal analysis yields *similar solutions*.
- The nodal method is very suitable for *computer work*.

Example 15. For the circuit shown in Fig. 25 find the currents through the resistances R_3 and R_4 .

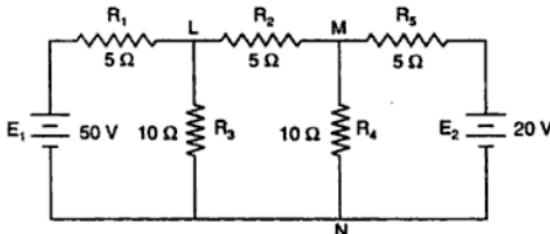


Fig. 25

Solution. Refer Fig. 25.

Let L , M and N = independent nodes, and

V_L and V_M = voltages of nodes L and M with respect to node N .

The nodal equations for the nodes L and M are :

$$V_L \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right] - \frac{E_1}{R_1} - \frac{V_M}{R_2} = 0 \quad \dots(i)$$

$$V_M \left[\frac{1}{R_2} + \frac{1}{R_4} + \frac{1}{R_5} \right] - \frac{E_2}{R_5} - \frac{V_L}{R_2} = 0 \quad \dots(ii)$$

Substituting the values in (i) and (ii) and simplifying, we get

$$V_L \left(\frac{1}{5} + \frac{1}{5} + \frac{1}{10} \right) - \frac{50}{5} - \frac{V_M}{5} = 0 \quad \dots(iii)$$

or $2.5V_L - V_M - 50 = 0 \quad \dots(iii)$

and $V_M \left(\frac{1}{5} + \frac{1}{10} + \frac{1}{5} \right) - \frac{20}{5} - \frac{V_L}{5} = 0 \quad \dots(iv)$

or $2.5V_M - V_L - 20 = 0 \quad \dots(iv)$

or $-V_L + 2.5V_M - 20 = 0 \quad \dots(iv)$

Solving (iii) and (iv), we get

$$V_L = 27.6 \text{ V}, \quad V_M = 19.05 \text{ V}$$

$$\text{Current through } R_3 = \frac{V_L}{R_3} = \frac{27.6}{10} = 2.76 \text{ A. (Ans.)}$$

$$\text{Current through } R_4 = \frac{V_M}{R_4} = \frac{19.05}{10} = 1.905 \text{ A. (Ans.)}$$

5. SOLVING EQUATIONS BY DETERMINANTS—CRAMER'S RULE

If the number of equations is more than two, it is easier to get the solution by using determinants.

If I_1 , I_2 and I_3 are the three unknowns in a system of three linear equations

$$\begin{aligned} a_{11}I_1 + a_{12}I_2 + a_{13}I_3 &= C_1 \\ a_{21}I_1 + a_{22}I_2 + a_{23}I_3 &= C_2 \\ a_{31}I_1 + a_{32}I_2 + a_{33}I_3 &= C_3 \end{aligned} \quad \dots(7)$$

Then, the system can be written in matrix form as follows :

$$\begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} c_1 \\ c_2 \\ c_3 \end{bmatrix} \quad \dots(8)$$

The values of I_1 , I_2 and I_3 are given by

$$I_1 = \frac{\begin{bmatrix} c_1 & a_{12} & a_{13} \\ c_2 & a_{22} & a_{23} \\ c_3 & a_{32} & a_{33} \end{bmatrix}}{\Delta} \quad \dots[9(a)]$$

$$I_2 = \frac{\begin{bmatrix} a_{11} & c_1 & a_{13} \\ a_{21} & c_2 & a_{23} \\ a_{31} & c_3 & a_{33} \end{bmatrix}}{\Delta} \quad \dots[9(b)]$$

$$I_3 = \frac{\begin{bmatrix} a_{11} & a_{12} & c_1 \\ a_{21} & a_{22} & c_2 \\ a_{31} & a_{32} & c_3 \end{bmatrix}}{\Delta} \quad \dots[9(c)]$$

where $\Delta = \begin{bmatrix} a_{11} & a_{12} & a_{13} \\ a_{21} & a_{22} & a_{23} \\ a_{31} & a_{32} & a_{33} \end{bmatrix}$

This is known as *Cramer's rule* and can be applied to any system of n linear equations provided Δ is not zero.

6. SUPERPOSITION THEOREM

This theorem is sometimes useful in solution of networks in which some branches may contain sources of e.m.f. It is applicable only to linear networks where current is linearly related to voltage as per Ohm's law.

This theorem may be stated as follows :

"In any network containing more than one source of e.m.f. the current in any branch is the algebraic sum of a number of individual fictitious currents (the number being equal to the number of sources of e.m.f.), each of which is due to the separate action of each source of e.m.f., taken in order, when the remaining sources of e.m.f. are replaced by conductors, the resistances of which are equal to the internal resistances of the respective sources".

The procedure of applying superposition theorem is as follows :

- Replace all but one of the sources by their internal resistances. If the internal resistance of any source is small as compared to other resistances present in the network, the source is replaced by a short circuit.

2. Find the currents in different branches by using Ohm's law.

3. Repeat the process using each of the e.m.fs. as the sole e.m.f. each time.

The total current in any branch of the circuit is the algebraic sum of currents due to each source.

When finding total current in any branch, it is necessary to take into account the directions of the currents caused by each individual source, currents flowing in the *same direction* being *additive*, currents flowing in *opposite directions* being *subtractive*.

Explanation :

- In Fig. 26, I_1 , I_2 and I represent the values of currents which are due to the simultaneous action of the two sources of e.m.f. in the network.
 - In the Fig. 27 are shown the current values which would have been obtained if left-hand side battery had acted alone.
 - Similarly Fig. 28 represents conditions obtained when right-hand side battery acts alone.
- By combining the current values of Fig. 27 and 28, the actual values of Fig. 26 can be obtained

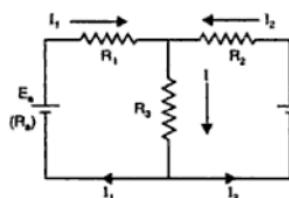


Fig. 26

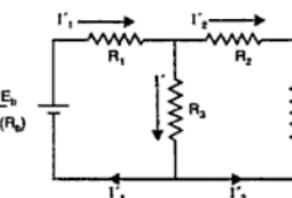


Fig. 27

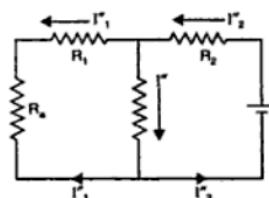


Fig. 28

Obviously,

$$I_1 = I_1' - I_1''$$

$$I_2 = I_2'' - I_2'$$

$$I = I' + I''.$$

Example 16. By using superposition theorem find the currents in the different branches of the network shown in Fig. 29.

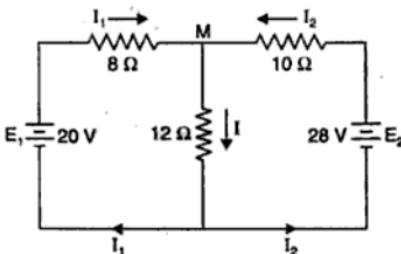


Fig. 29

Solution. I_1 : , I_2 : , I :

First step. Refer Fig. 30.

Take e.m.f. E_1 only and replace e.m.f. E_2 by its zero internal resistance, the circuit is shown in Fig. 30.

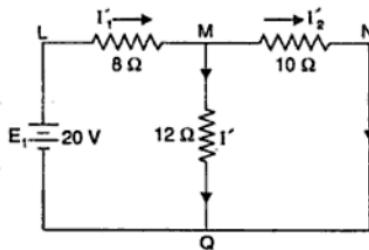


Fig. 30

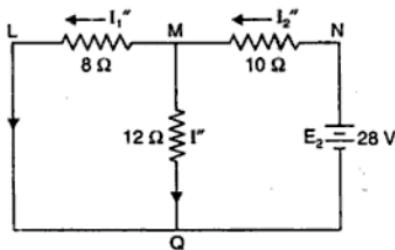


Fig. 31

$$\text{Total resistance} = 8 + \frac{10 \times 12}{10 + 12} = 13.45 \Omega$$

Current through 8 Ω resistance,

$$I_1' = \frac{20}{13.45} = 1.487 \text{ A}$$

Current through 10 Ω resistance,

$$I_2' = 1.487 \times \frac{12}{12 + 10} = 0.81 \text{ A}$$

Current through 6 Ω resistance,

$$I' = 1.487 \times \frac{10}{12 + 10} = 0.675 \text{ A}$$

Second step. Refer Fig. 31.

E.m.f. E_1 is removed/short circuited and current due to e.m.f. E_2 is found. The current is shown in the Fig. 31.

$$\text{Total resistance} = 10 + \frac{12 \times 8}{12 + 8} = 14.8 \Omega$$

Current through 10 Ω resistance,

$$I_2'' = \frac{28}{14.8} = 1.892 \text{ A}$$

Current through 8 Ω resistance,

$$I_1'' = 1.892 \times \frac{12}{12 + 8} = 1.135 \text{ A}$$

Current through 12 Ω resistance,

$$I'' = 1.892 \times \frac{8}{12 + 8} = 0.757 \text{ A}$$

The total currents in different branches are :

Current through 8 Ω resistance,

$$I_1 = I_1' - I_1'' = 1.487 - 1.135 = 0.352 \text{ A (from L to M). (Ans.)}$$

Current through 10 Ω resistance,

$$I_2 = I_2'' - I_2' = 1.892 - 0.81 = 1.082 \text{ A (from N to M). (Ans.)}$$

Current through 12 Ω resistance,

$$I = I' + I'' = 0.675 + 0.757 = 1.432 \text{ A (from M to Q). (Ans.)}$$

Example 17. By using superposition theorem, find the current in 2Ω resistance shown in Fig. 32. Internal resistances of the cells are negligible.

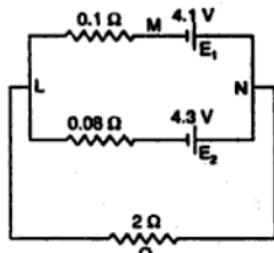


Fig. 32

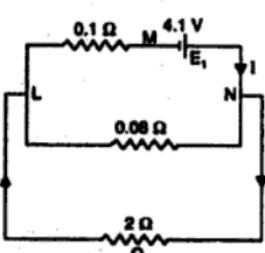


Fig. 33

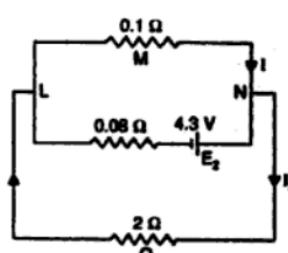


Fig. 34

Solution. First step. Refer Fig. 33.

- E_2 has been removed.
- Resistances 2Ω and 0.08Ω are in parallel across points L and N .

$$\therefore R_{LN} = \frac{2 \times 0.08}{2 + 0.08} = 0.076 \Omega$$

This resistance is in series with 0.1Ω .

Hence, total resistance offered to battery E_1 ,

$$= 0.1 + 0.076 = 0.176 \Omega$$

$$\therefore \text{Current, } I = \frac{4.1}{0.176} = 23.3 \text{ A}$$

Current through 2Ω resistance,

$$I_1 = 23.3 \times \frac{0.08}{0.08 + 2} = 0.896 \text{ A (from } N \text{ to } L)$$

Second step. Refer Fig. 34.

- E_1 has been removed.
- Combined resistance of paths NML and NQL

$$= \frac{2 \times 0.1}{2 + 0.1} = 0.095 \Omega$$

Total resistance offered to $E_2 = 0.095 + 0.08 = 0.175 \Omega$

$$\therefore \text{Current } I = \frac{4.3}{0.175} = 24.57 \text{ A}$$

$$\text{Again, } I_2 = 24.57 \times \frac{0.1}{0.1 + 2} = 1.17 \text{ A}$$

Hence total current through the 2Ω resistance when both batteries are present

$$= I_1 + I_2 = 0.896 + 1.17 = 2.066 \text{ A. (Ans.)}$$

Example 18. Using superposition theorem, find the currents in the circuit shown in the Fig. 35.

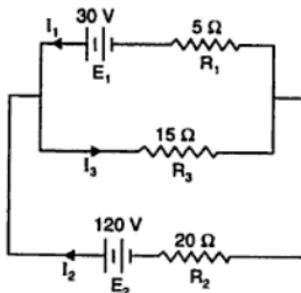


Fig. 35

Solution. First step. Refer Fig. 36.

— E_2 has been removed.

— Resistances R_2 and R_3 are in parallel,

$$\therefore R_{\text{parallel}} = \frac{R_2 R_3}{R_2 + R_3} = \frac{20 \times 15}{20 + 15} = 8.57 \Omega$$

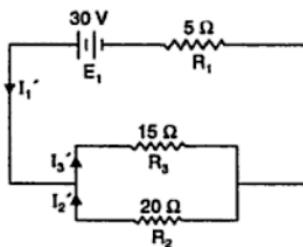


Fig. 36

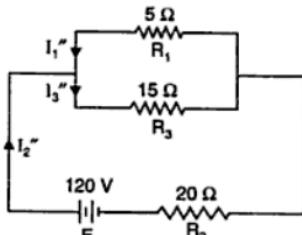


Fig. 37

This resistance is in series with R_1 .

\therefore Total resistance offered to battery E_1

$$= 8.57 + 5 = 13.57 \Omega$$

Current $I_1' = \frac{30}{13.57} = 2.21 \text{ A}$

Current $I_2' = -2.21 \times \frac{15}{20 + 15} = -0.947 \text{ A}$

Current $I_3' = 2.21 \times \frac{20}{20 + 15} = 1.263 \text{ A}$.

Second step. Refer Fig. 37.

— E_1 has been removed.

— Resistances R_1 and R_3 are in parallel.

$$\therefore R_{\text{parallel}} = \frac{R_1 R_3}{R_1 + R_3} = \frac{5 \times 15}{5 + 15} = 3.75 \Omega$$

This resistance is in series with 20Ω resistance.

∴ Total resistance offered to E_2

$$= 3.75 + 20 = 23.75 \Omega$$

Current $I_2'' = \frac{120}{23.75} = 5.05 \text{ A}$

Current $I_1'' = -5.05 \times \frac{15}{5+15} = -3.79 \text{ A}$

Current $I_3'' = 5.05 \times \frac{5}{5+15} = 1.262 \text{ A}$

Now superimposing the results, we get

$$I_1 = I_1' + I_1'' = 2.21 + (-3.79 \text{ A}) = -1.58 \text{ A. (Ans.)}$$

$$I_2 = I_2' + I_2'' = -0.947 + 5.05 = 4.1 \text{ A. (Ans.)}$$

$$I_3 = I_3' + I_3'' = 1.263 + 1.262 = 2.52 \text{ A. (Ans.)}$$

7. THEVENIN'S THEOREM

Thevenin's theorem is quite useful when the current in one branch of a network is to be determined or when the current in an added branch is to be calculated.

"It states that for the purpose of determining the current in a resistor, R_L connected across two terminals of a network which contains sources of e.m.f. and resistors, the network can be replaced by a single source of e.m.f. and a series resistor, R_{th} . This e.m.f., E_{th} is equal to potential difference between the terminals of the network when the resistor, R , is removed : the resistance of series resistor, R_{th} , is equal to the equivalent resistance of the network with the resistor, R , removed (or as it is sometimes called, "the resistance of the network when viewed from the terminals under consideration")".

Hence

$$I = \frac{E}{(R_L + R_{th})} \quad \dots(10)$$

Explanation. Let us consider the circuit shown in Fig. 38 (a). The following steps are required to find current through the load resistance R_L .

1. Remove R_L from the circuit terminals A and B and redraw the circuit as shown in Fig. 38 (b). Obviously the terminals have been open circuited.

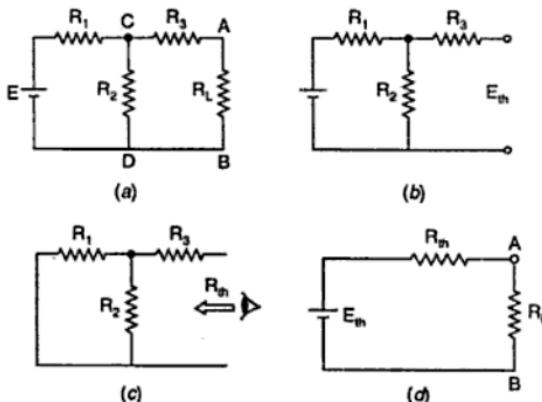


Fig. 38

2. Calculate the open-circuit voltage ($V_{oc} = E_{th}$) which appears across terminals A and B, when they are open i.e. when R_L is removed. This voltage is E_{th} (Thevenin's voltage). A little thought will reveal that

$$E_{th} = \frac{ER_2}{R_1 + R_2} \quad \dots(11)$$

$$\left[\because I = \frac{E}{R_1 + R_2} \text{ and } E_{th} = IR_2 = \frac{ER_2}{R_1 + R_2} \right]$$

3. Short circuit the battery and find the Thevenin resistance R_{th} of the network as seen from the terminals A and B [Fig. 38 (c)]

$$R_{th} = \frac{R_1 \times R_2}{R_1 + R_2} + R_3 \quad \dots(12)$$

4. Connect R_L back across the terminals A and B from where it was temporarily removed earlier [Fig. 38 (d)]. Current through R_L is given by

$$I = \frac{E_{th}}{(R_{th} + R_L)} \quad \dots(13)$$

Example 19. With reference to the network shown in Fig. 39, by using Thevenin's theorem find the following :

- (i) The equivalent e.m.f. of the network when viewed from terminals L and M.
- (ii) The equivalent resistance of the network when looked into from terminals L and M.
- (iii) Current in the load resistance R_L of 30 Ω .

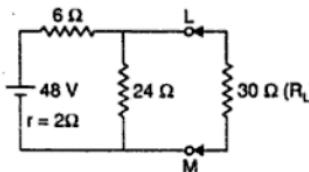


Fig. 39

Solution. (i) Equivalent e.m.f. of the network :

Refer Fig. 39.

Current in the network before load resistance (R_L) is connected

$$= \frac{48}{24 + 6 + 2} = 1.5 \text{ A}$$

∴ Voltage across terminals LM,

$$V_{oc} = E_{th} = 24 \times 1.5 = 36 \text{ V.}$$

Hence, so far as terminals L and M are connected, the network has an e.m.f. of 36 V (and not 48 V). (Ans.)

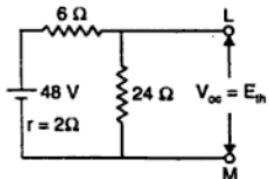


Fig. 40

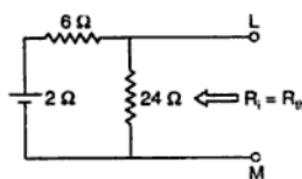


Fig. 41

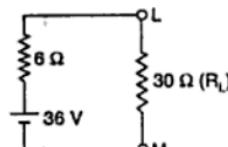


Fig. 42

(ii) Equivalent resistance of the network :

There are two parallel paths between points L and M . Imagine that battery of 48 V is removed but not its internal resistance. Then, resistance of the circuit as looked into from points L and M is (Fig. 41)

$$R_i = R_{th} = \frac{24 \times (6 + 2)}{24 + (6 + 2)} = 6 \Omega. \quad (\text{Ans.})$$

(iii) Current in R_L , I :

Refer Fig. 42.

$$I = \frac{E_{th}}{R_{th} + R_L} = \frac{36}{6 + 30} = 1 \text{ A.} \quad (\text{Ans.})$$

Example 20. Find the current through 50 ohms resistance in the circuit shown in the Fig. 43. Use Thevenin's theorem.

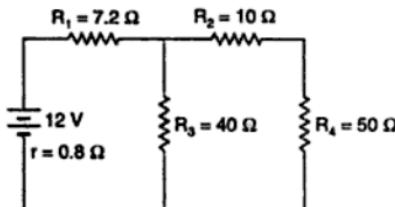


Fig. 43

Solution. To solve the problem of the network shown in Fig. 43 by Thevenin's theorem, let R_4 be assumed as disconnected as shown in Fig. 44.

With the resistance R_4 disconnected, the current in the closed circuit consisting of R_1 , R_3 and r is,

$$I = \frac{E}{R_1 + R_3 + r} = \frac{12}{7.2 + 40 + 0.8} = 0.25 \text{ A.}$$

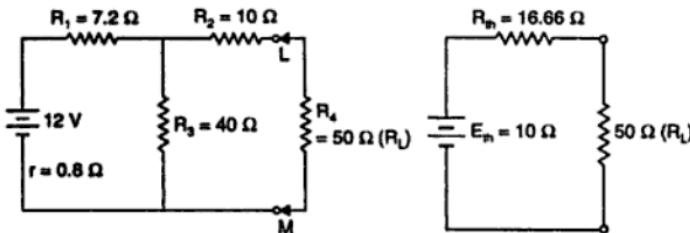


Fig. 44

Fig. 45

$$\text{Voltage across terminals } LM = V_{oc} = E_{th} = 0.25 \times 40 = 10 \text{ V}$$

The equivalent internal resistance of the network between the terminals L and M with R_4 disconnected,

$$\begin{aligned} R_i &= R_{th} = R_2 + \frac{R_3(R_1 + r)}{R_3 + (R_1 + r)} \\ &= 10 + \frac{40(7.2 + 0.8)}{40 + 7.2 + 0.8} = 10 + \frac{40 \times 8}{48} = 16.66 \Omega. \end{aligned}$$

\therefore Current through $50\ \Omega (R_L)$ resistance (Refer Fig. 45),

$$I = \frac{E_{th}}{R_{th} + R_L} = \frac{10}{16.66 + 50} = 0.15\ A. \text{ (Ans.)}$$

Example 21. Using Thevenin's theorem find the current through the $2.5\ \Omega$ resistance in the circuit shown in the Fig. 46.

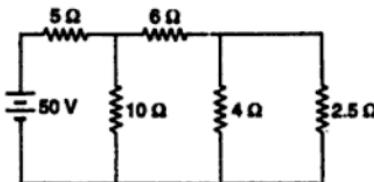


Fig. 46

Solution. To solve the problem by using Thevenin's theorem, let $2.5\ \Omega$ resistance be shown disconnected as shown in Fig. 47.

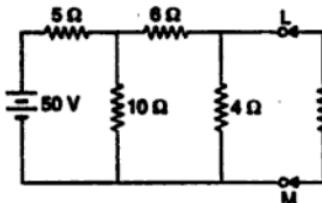


Fig. 47

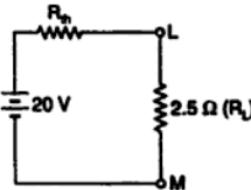


Fig. 48

With the $2.5\ \Omega$ resistance disconnected, the current in the closed circuit [Consisting of $5\ \Omega$ resistance connected in series with combined resistance of $(6\ \Omega + 4\ \Omega)$ and $10\ \Omega$ (connected in parallel)],

$$I = \frac{50}{5 + \frac{(6+4) \times 10}{(6+4)+10}} = \frac{50}{5+5} = 5\ A$$

Voltage across terminals LM $= V_{oc} = E_{th} = 5 \times 4 = 20\ V$

The equivalent internal resistance of the network between the terminals L and M (with $2.5\ \Omega$ disconnected),

[Here R_{th} (or R_i) comprises of : $5\ \Omega$ and $10\ \Omega$ in parallel ; this combined resistance (i.e. $\frac{5 \times 10}{5+10}\ \Omega$) is in series with $6\ \Omega$. This total resistance, then, is in parallel with $4\ \Omega$ resistance.]

$$R_i = R_{th} = \frac{\left[\frac{5 \times 10}{5+10} + 6 \right] \times 4}{\left[\left(\frac{5 \times 10}{5+10} + 6 \right) + 4 \right]} = \frac{9.33 \times 4}{13.33} = 2.8\ \Omega$$

\therefore Current through $2.5\ \Omega$ resistance (Refer Fig. 48),

$$I = \frac{E_{th}}{R_{th} + R_L} = \frac{20}{2.8 + 2.5} = 3.77\ A. \text{ (Ans.)}$$

Example 22. Using Thevenin's theorem, calculate the potential difference across terminals L and M in Fig. 49.

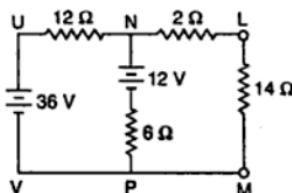


Fig. 49

Solution. First-step : To find V_{oc} :

Remove $14\ \Omega$ resistance thereby open-circuiting terminals L and M (see Fig. 50). Obviously there is no current in through $2\ \Omega$ resistor and hence no drop across it.

$$V_{LM} = V_{OC} = V_{NP}$$

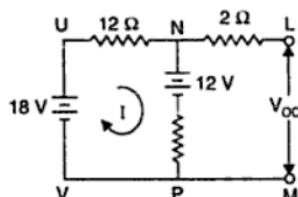


Fig. 50

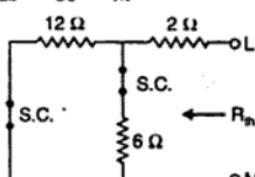


Fig. 51

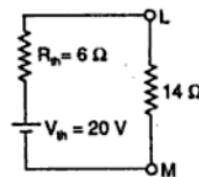


Fig. 52

As seen, current I flows due to the combined action of the two batteries. Net voltage in NPVU circuit = $36 - 12 = 24\text{ V}$.

$$\text{--- Total resistance} = 12 + 6 = 18\ \Omega$$

$$\text{Hence } I = \frac{24}{18} = \frac{4}{3}\text{ A}$$

$$\begin{aligned} V_{NP} &= 12 + \text{drop across } 6\ \Omega \text{ resistor} \\ &= 12 + 6 \times \frac{4}{3} = 20\ \text{V} \end{aligned}$$

$$\therefore V_{OC} = V_{th} = 20\ \text{V}$$

Second step : To find R_i or R_{th}

As shown in Fig. 51, the two batteries have been replaced by short-circuits (S.C.) since their internal resistances are zero.

$$\text{As seen, } R_i = R_{th} = 2 + 6 \parallel 12 = 2 + \frac{12 \times 6}{12 + 6} = 6\ \Omega$$

The Thevenin's equivalent circuit is shown in Fig. 52 where the $14\ \Omega$ resistance has been reconnected across terminals L and M.

Third step : To find p.d. across L and M

The p.d. across L and M can be found with the help of *Proportional Voltage Formula*,

$$\text{p.d. across L and M} = 20 \times \frac{14}{14 + 6} = 14\ \text{V} \quad (\text{Ans.})$$

$$\left[\begin{array}{l} \text{Alternatively : } I = \frac{20}{6 + 14} = 1\ \text{A} \\ \therefore \text{p.d. across } 14\ \Omega \text{ resistance} = 1 \times 14 = 14\ \text{V.} \end{array} \right]$$

8. NORTON'S THEOREM

Whereas Thevenin's theorem was used to simplify a network to a constant-voltage source and a series resistance, Norton's theorem can be used to resolve a network into a constant-current source and a parallel resistance. The interchange of voltage sources and current sources by use of Thevenin's and Norton's theorems is sometimes useful in circuit analysis.

The theorem may be stated as follows :

"Any two-terminal linear network containing independent voltage and current sources may be replaced by an equivalent current I_N in parallel with a resistance R_N where I_N is the short circuit current at network terminals and R_N is the equivalent resistance of network as seen from the terminals but with all voltage sources short circuited and all current sources open circuited."

The following procedure may be adopted to determine the Norton's equivalent circuit :

1. Calculate the short circuit current (I_N) at the network terminals.
2. Redraw the network with each voltage source replaced by a short circuit in series with its internal resistance and each current source by an open circuit in parallel with its internal resistance.
3. Calculate the resistance (R_N) of the redrawn network as seen from the network terminals. (The resistance R_N is the same value as used in Thevenin's equivalent circuit).

Example 23. By using Norton's theorem find the current in the $12\ \Omega$ resistance of the circuit shown in Fig. 53.

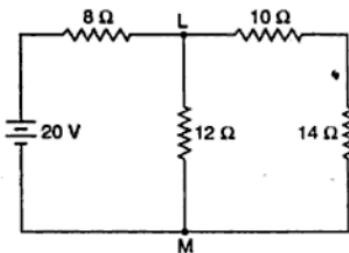


Fig. 53

Solution.

- With $12\ \Omega$ resistance removed and terminals L-M short circuited, short-circuit current,

$$I_N = \frac{20}{8} = 2.5\text{ A.}$$

- With 20 V battery replaced by a short circuit, the resistance of the network as seen from terminals L and M is

$$R_N = \frac{8(10 + 14)}{8 + (10 + 14)} = 6\ \Omega$$

- The Norton's equivalent circuit is shown in Fig. 54. The current through $12\ \Omega$ resistance is

$$I = 2.5 \times \frac{6}{6 + 12} = 0.833\text{ A. (Ans.)}$$

Example 24. For the network shown in Fig. 55 derive Norton's equivalent circuit and find the current through $24\text{ k}\Omega$ resistance.

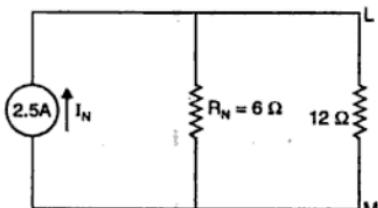


Fig. 54

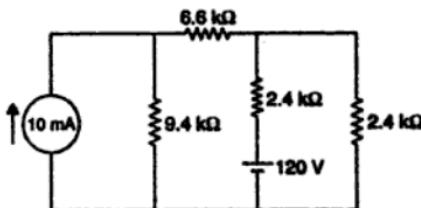


Fig. 55

Solution. With 24 kΩ resistance removed and terminals L-M short circuited, superposition theorem gives,

$$I_N = I_1 + I_2$$

From Fig. 56 (a),

$$I_1 = 10 \times \frac{9.4}{9.4 + 6.6} = 5.8 \text{ mA}$$

From Fig. 56 (b),

$$I_2 = \frac{120}{2.4 \times 1000} = 0.05 \text{ A or } 50 \text{ mA}$$

∴

$$I_N = I_1 + I_2 = 5.8 + 50 = 55.8 \text{ mA}$$

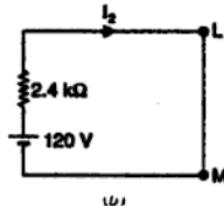
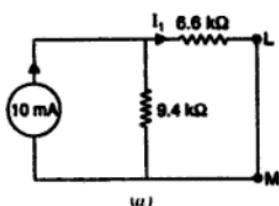


Fig. 56

$$R_N = \frac{2.4 \times (9.4 + 6.6)}{2.4 + (9.4 + 6.6)} = 2.08 \Omega$$

The Norton's equivalent circuit is shown in Fig. 57. Current through 12 kΩ resistance,

$$\begin{aligned} I &= 55.8 \times \frac{2.08}{2.08 + 24} \\ &= 4.45 \text{ A. (Ans.)} \end{aligned}$$

9. MAXIMUM POWER TRANSFER THEOREM

This theorem is particularly useful for analysing communication networks. It is stated as follows :

"Maximum power output is obtained from a network when the load resistance is equal to the output resistance of the network as seen from the terminals of the load".

Any network can be converted into a single voltage source by the use of Thevenin's theorem (Fig. 58). The maximum power transfer theorem aims at finding R_L such that the power dissipated in R_L is maximum.

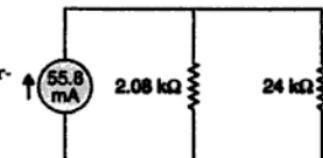


Fig. 57

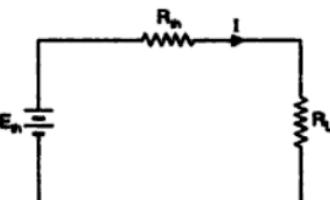


Fig. 58

$$P = I^2 R_L$$

$$= \left(\frac{E_{th}}{R_{th} + R_L} \right)^2 R_L \quad \dots(14)$$

For P to be maximum, $\frac{dP}{dR_L} = 0$

Differentiating eqn. (14), we have

$$\frac{dP}{dR_L} = \frac{\frac{E_{th}^2}{(R_{th} + R_L)^2} [(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)]}{(R_{th} + R_L)^4}$$

$$\therefore \frac{E_{th}^2 [(R_{th} + R_L)^2 - 2R_L(R_{th} + R_L)]}{(R_{th} + R_L)^4} = 0$$

From which,

$$R_L = R_{th} \quad \dots(15)$$

It is worth noting that under these conditions the voltage across the load is half the open-circuit voltage at the terminals L and M .

\therefore Maximum power, $P_{max} = \left[\frac{E_{th}}{(R_L + R_{th})} \right]^2 R_L = \frac{E_{th}^2}{4R_{th}}$...[15 (a)]

The process of adjusting the load resistance for maximum power transfer is called '*load matching*'. This is done in the following typical cases :

(i) *Motor cars*—here starter motor is matched to the battery.

(ii) *Telephone lines and TV aerial leads*—these are matched to the telephone instrument and TV receiver respectively.

Example 25. For the circuit shown in Fig. 59, find the current through R_L when it takes on values of 5Ω and 25Ω . Also, calculate the value of R_L for which the power dissipated in it would be maximum and find this power.

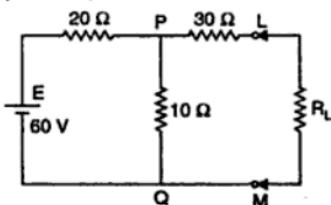


Fig. 59

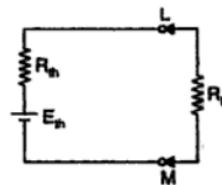


Fig. 60

Solution. The open circuit voltage V_{oc} (also called Thevenin's voltage E_{th}) which appears across terminals L and M is equal to the voltage drop across 10Ω resistance.

$$\text{Current flowing through the circuit } EPQ = \frac{60}{20 + 10} = 2 \text{ A}$$

$$\therefore \text{Voltage drop over } 10\Omega \text{ resistance} = 2 \times 10 = 20 \text{ V}$$

$$\text{Hence } V_{oc} = E_{th} = 20 \text{ V}$$

The resistance of the circuit as looked into the network from points L and M (when battery has been removed),

$$R_i = R_{th} = 30 + 10 \parallel 20 = 30 + \frac{10 \times 20}{10 + 20} = 36.67 \Omega$$

The whole circuit up to LM can now be replaced by a single source of e.m.f. and single resistance as shown in Fig. 60.

$$(i) \text{ When } R_L = 5 \Omega, \quad I = \frac{E_{th}}{R_{th} + R_L} = \frac{20}{36.67 + 5} = 0.48 \text{ A. (Ans.)}$$

$$(ii) \text{ When } R_L = 25 \Omega, \quad I = \frac{20}{36.67 + 25} = 0.324 \text{ A. (Ans.)}$$

According to the maximum power transfer theorem, power drawn by R_L would be maximum when $R_L = R_i$ or when $R_L = 36.67 \Omega$

\therefore Maximum power drawn by R_L

$$\begin{aligned} &= I^2 R_L = \left(\frac{E_{th}}{R_{th} + R_L} \right)^2 R_L \\ &= \left(\frac{E_{th}}{R_L + R_L} \right)^2 R_L = \frac{E_{th}^2}{4R_L} \\ &= \frac{20^2}{4 \times 36.67} = 2.72 \text{ W. (Ans.)} \end{aligned} \quad (\because R_{th} = R_L)$$

10. DELTA STAR TRANSFORMATION

When networks having a large number of branches are to be solved by the use of Kirchhoff's law, a great difficulty is experienced in solving several simultaneous equations. Such complicated networks, however, can be simplified by successively replacing delta meshes by equivalent star systems and vice versa.

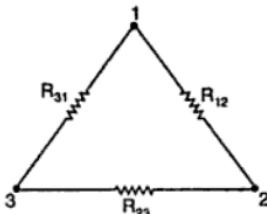


Fig. 61

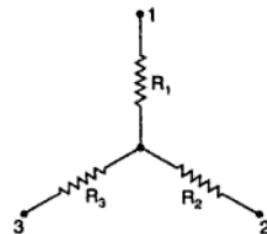


Fig. 62

Consider the two circuits shown in the Figs. 61 and 62. They will be *equivalent* if the resistance measured between any two of the terminals 1, 2 and 3 is the same in the two cases.

$$[R_{12}]_\gamma = [R_{12}]_\Delta \quad \dots(16)$$

$$\text{or} \quad R_1 + R_2 = \frac{R_{12}(R_{23} + R_{31})}{R_{12} + R_{23} + R_{31}} \quad \dots(17)$$

$$\text{Similarly} \quad R_2 + R_3 = \frac{R_{23}(R_{31} + R_{12})}{R_{12} + R_{23} + R_{31}} \quad \dots(18)$$

$$\text{and} \quad R_3 + R_1 = \frac{R_{31}(R_{12} + R_{23})}{R_{12} + R_{23} + R_{31}} \quad \dots(19)$$

Solving eqns. (17), (18) and (19) simultaneously, we get

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} \quad \dots(20)$$

$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}} \quad \dots(21)$$

$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}} \quad \dots(22)$$

From above it may be noted that resistance of each arm of the star is given by the product of the resistances of the two delta sides that meet at its end divided by the sum of the three delta resistances.

From eqns. (17) to (19), eqns. for star to delta conversion can also be obtained. These are as follows :

$$R_{12} = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_3} \quad \dots(23)$$

$$R_{23} = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_1} \quad \dots(24)$$

$$R_{31} = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_2} \quad \dots(25)$$

In electronics, star and delta circuits are generally referred to as τ and π circuits respectively.

Example 26. Fig. 63 shows a number of resistances connected in delta and star. Using star/delta conversion method complete the network resistance measured between (i) L and M (ii) M and N and (iii) N and L.

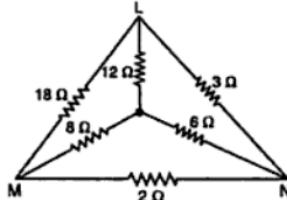


Fig. 63

Solution. Three resistances 12 Ω , 6 Ω and 8 Ω are star connected. Transform them into delta with ends at the same points as before.

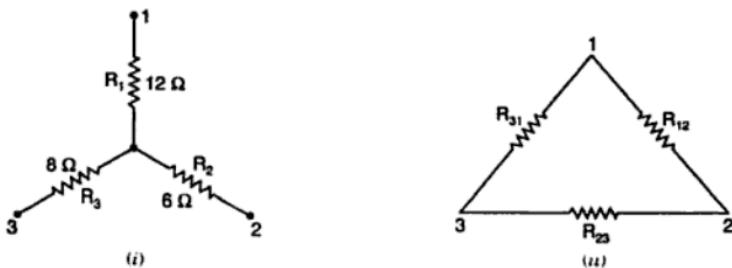


Fig. 64

Refer Fig. 64.

$$\begin{aligned} R_{12} &= \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_3} \\ &= \frac{12 \times 6 + 6 \times 8 + 8 \times 12}{8} = 27 \Omega \end{aligned}$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1}$$

$$= \frac{12 \times 6 + 6 \times 8 + 8 \times 12}{12} = 18 \Omega$$

Similarly

$$R_{31} = \frac{12 \times 6 + 6 \times 8 + 8 \times 12}{6} = 36 \Omega.$$

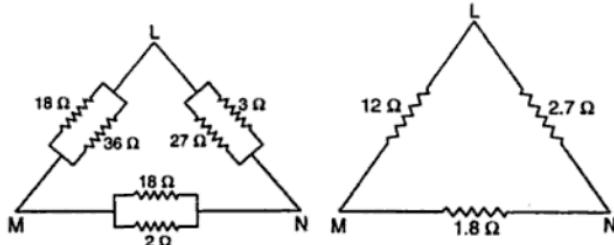


Fig. 65

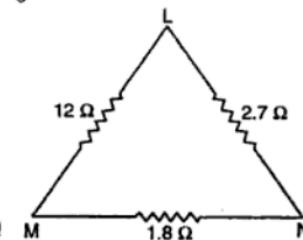


Fig. 66

Fig. 65 shows this transformed circuit connected to original delta connected resistances in the circuit 18Ω , 3Ω and 2Ω .

Here 18Ω and 36Ω are in parallel ;
 3Ω and 27Ω are in parallel, and
 2Ω and 18Ω are in parallel.

These resistances are equivalent to :

$$\frac{18 \times 36}{18 + 36} = 12 \Omega; \frac{3 \times 27}{3 + 27} = 2.7 \Omega \text{ and } \frac{2 \times 18}{2 + 18} = 1.8 \Omega$$

This is shown in Fig. 66.

(i) Resistance between L and M ,

$$R_{LM} = \frac{12 \times (2.7 + 1.8)}{12 + (2.7 + 1.8)} = 3.27 \Omega. \text{ (Ans.)}$$

(ii) Resistance between M and N ,

$$R_{MN} = \frac{1.8 \times (12 + 2.7)}{1.8 + 12 + 2.7} = 1.6 \Omega. \text{ (Ans.)}$$

(iii) Resistance between N and L ,

$$R_{NL} = \frac{2.7 \times (12 + 1.8)}{2.7 + (12 + 1.8)} = 2.25 \Omega. \text{ (Ans.)}$$

Example 27. In the circuit shown in Fig. 67, find the resistance between M and N .

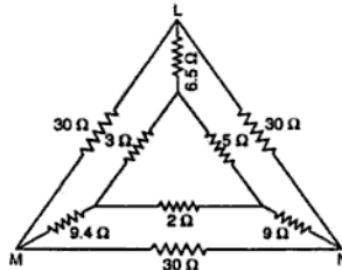


Fig. 67


Solution. Connecting the 1 2 3 delta [Fig. 68 (i)] to equivalent star [Fig. 68 (ii)]

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{5 \times 3}{5 + 2 + 3} = 1.5 \Omega$$


$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{2 \times 5}{5 + 2 + 3} = 1 \Omega$$

and
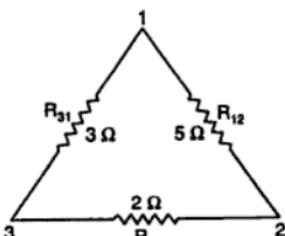
$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{3 \times 2}{5 + 2 + 3} = 0.6 \Omega$$



(i)

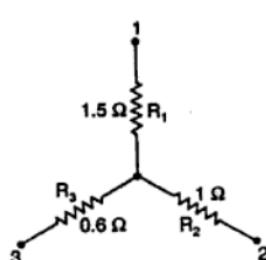

(ii)

Fig. 68

Thus the original circuit reduces to that shown in Fig. 69 which further reduces to the circuit shown in Fig. 70.

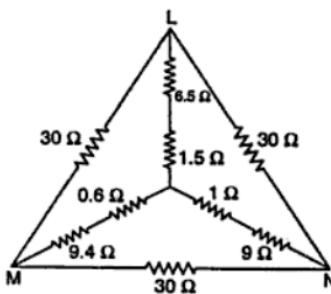


Fig. 69

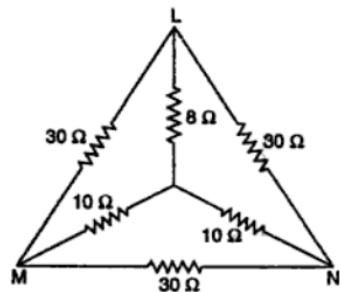


Fig. 70

Now, the inner star circuit of Fig. 69 shown as Fig. 71 (i) is equivalent to the delta circuit shown in Fig. 71 (ii) as appears from calculations given below :

$$R_{12} = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_3} = \frac{8 \times 10 + 10 \times 10 + 10 \times 8}{10} = 26 \Omega$$

$$R_{23} = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_1} = \frac{8 \times 10 + 10 \times 10 + 10 \times 8}{8} = 32.5 \Omega$$

$$R_{31} = \frac{R_1R_2 + R_2R_3 + R_3R_1}{R_2} = \frac{8 \times 10 + 10 \times 10 + 10 \times 8}{10} = 26 \Omega.$$

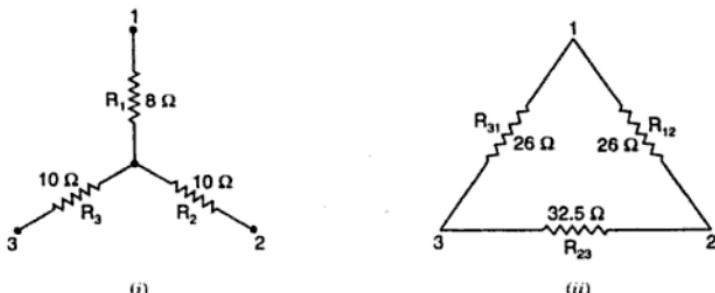


Fig. 71

The given circuit thus ultimately reduces to the circuit shown in Fig. 72 which in turn is equivalent to the circuit given in Fig. 73.

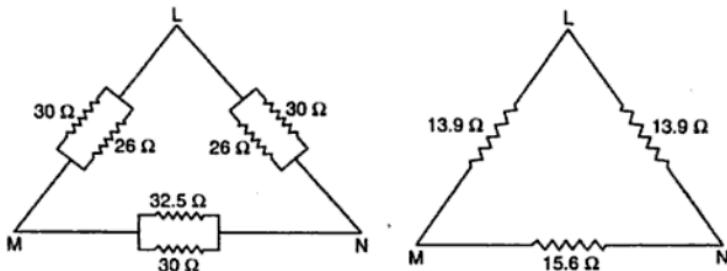


Fig. 72

Fig. 73

In Fig. 72, the observe that :

$30\ \Omega$ and $26\ \Omega$ are in parallel and are equivalent to :

$$\frac{30 \times 26}{30 + 26} = 13.9 \Omega.$$

30 and $26\ \Omega$ are in parallel and are equivalent to : $13.9\ \Omega$ (as above)

32.5 Ω and 30 Ω are in parallel and are equivalent to :

$$\frac{32.5 \times 30}{32.5 + 30} = 15.6 \Omega$$

Hence total resistance between M and N .

$$R_{MN} = \frac{15.6 \times (13.9 + 13.9)}{15.6 + (13.9 + 13.9)} \\ = \frac{433.68}{43.4} = 9.99 \Omega. \quad (\text{Ans.})$$

Example 28. Find the current I supplied by the battery for Fig. 74, using delta/star transformation.



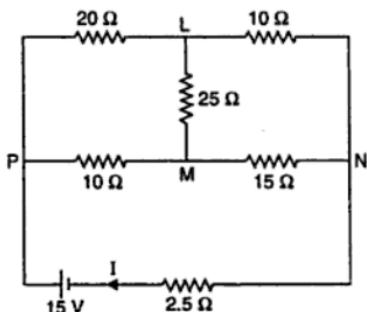


Fig. 74

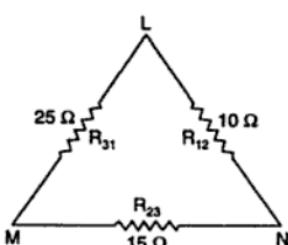Solution. Delta connected resistances 25Ω , 10Ω and 15Ω are transformed to equivalent star as given below : (See Fig. 75)



(i)

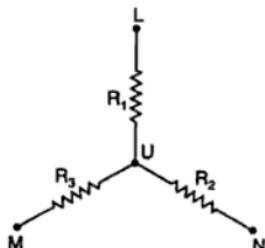

(ii)

Fig. 75

$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{10 \times 25}{10 + 15 + 25} = 5 \Omega$$

$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{15 \times 10}{10 + 15 + 25} = 3 \Omega$$

$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{25 \times 15}{10 + 15 + 25} = 7.5 \Omega$$

The given circuit thus reduces to the circuit shown in Fig. 76.

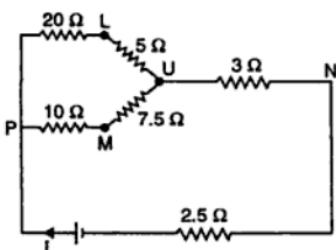


Fig. 76

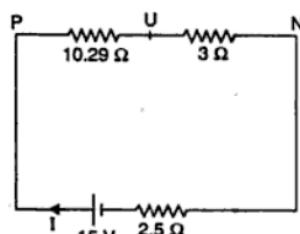


Fig. 77

The equivalent resistance of

$$(20 + 5) \Omega \parallel (10 + 7.5) \Omega = \frac{25 \times 17.5}{25 + 17.5} = 10.29 \Omega$$

Thus the given circuit ultimately reduces to the circuit shown in Fig. 77.

Total resistance = $10.29 + 3 + 2.5 = 15.79 \Omega$

Hence current through the battery,

$$I = \frac{15}{15.79} = 0.95 \text{ A. (Ans.)}$$

Example 29. Find the current in the galvanometer arm in the network shown in Fig. 78, using delta/star transformation.

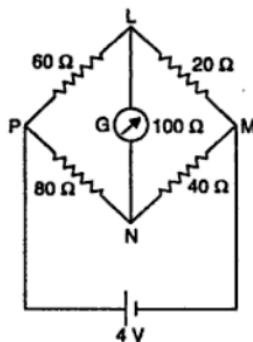



Fig. 78

Solution. Delta connected resistances 100Ω , 20Ω and 40Ω are transformed to equivalent star as given below : (See Fig. 79)


$$R_1 = \frac{R_{12}R_{31}}{R_{12} + R_{23} + R_{31}} = \frac{20 \times 100}{20 + 40 + 100} = 12.5 \Omega$$

$$R_2 = \frac{R_{23}R_{12}}{R_{12} + R_{23} + R_{31}} = \frac{40 \times 20}{20 + 40 + 100} = 5 \Omega$$
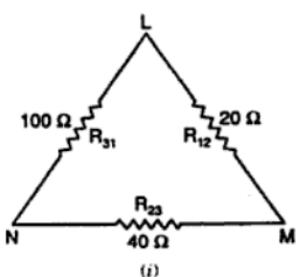
$$R_3 = \frac{R_{31}R_{23}}{R_{12} + R_{23} + R_{31}} = \frac{100 \times 40}{20 + 40 + 100} = 25 \Omega$$



(i)

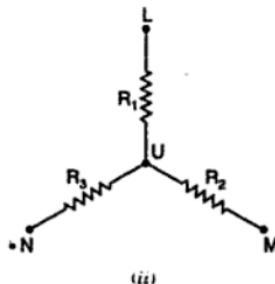

(iii)

Fig. 79

The given circuit thus reduces to the circuit shown in Fig. 80.

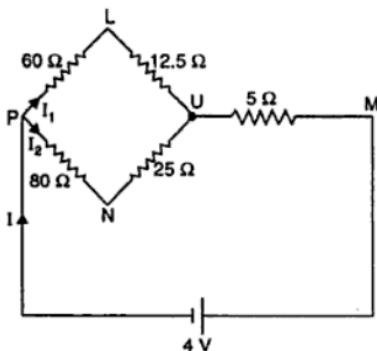


Fig. 80

The equivalent resistance,

$$R_{PU} = \frac{(60 + 12.5) \times (80 + 25)}{(60 + 12.5) + (80 + 25)} = 42.9 \Omega$$

∴ Total resistance of the circuit,

$$R_{PM} = 42.9 + 5 = 47.9 \Omega$$

∴ The main current, $I = \frac{4}{47.9} = 0.0835 \text{ A}$

Let I_1 = current in the arm NLP ,

I_2 = current in the arm LP , and

I_3 = current in the galvanometer.

Then,

$$I_1 = 0.0835 \times \left[\frac{(80 + 25)}{(80 + 25) + (60 + 12.5)} \right] = 0.0494 \text{ A}$$

and

$$I_2 = 0.0835 \times \left[\frac{(60 + 12.5)}{(80 + 25) + (60 + 12.5)} \right] = 0.0341 \text{ A.}$$

∴ Potential difference between L and P

$$= 0.0494 \times 60 = 2.964 \text{ V}$$

and between P and N

$$= 0.0341 \times 80 = 2.728 \text{ V}$$

and between L and N

$$= 2.964 - 2.728 = 0.236 \text{ V}$$

Hence the current flowing through the galvanometer,

$$I_3 = \frac{0.236}{100} = 0.00236 \text{ A. (Ans.)}$$

11. COMPENSATION THEOREM

The compensation theorem is particularly useful for the following purposes :

(i) To calculate the sensitivity of a bridge network.

(ii) To analyse those networks where the values of the branch elements are varied and for studying the effect of tolerance on such values.

This theorem is stated as follows :

"If a change, say ΔR , is made in the resistance of any branch of a network when the current was originally I , then the change of current at any other point in the network may be calculated by assuming that an e.m.f. $- I \Delta R$ has been introduced into the changed branch while all other sources have their e.m.fs. suppressed and are represented by their internal resistances only".

12. RECIPROCITY THEOREM

The theorem is stated as follows :

"In any linear bilateral network, if a source of e.m.f. E in any branch produces a current I in any other branch, then the same e.m.f. acting in the second branch would produce the same current I in the first branch".

In other words, it simply means that E and I are mutually transferrable. The ratio E/I is known as the transfer resistance (or impedance in a.c. systems).

13. MILLMAN'S THEOREM

The theorem can be applied to a network having a combination of voltage and current sources since voltage source can be converted into a current source and vice-versa.

The theorem is applicable only to two sources connected directly in parallel. It is not applicable where there are resistance elements between the sources.

The theorem is stated in the following manner :

"Any number of current sources in parallel may be replaced by a single current source whose current is the algebraic sum of individual source currents and source resistance is the parallel combination of individual source resistances".

HIGHLIGHTS

1. Kirchhoff's laws :

First law : Σ currents entering = Σ currents leaving

Second law : Σ potential rises = Σ potential drops.

2. Applications of Kirchhoff's laws include the following :

(i) Branch-current method

(ii) Maxwell's loop (or mesh) current method

(iii) Nodal voltage method.

3. The solutions of the networks involve the use of the following theorems :

- Superposition theorem

- Thevenin's theorem

- Norton's theorem

- Maximum power transfer theorem

- Delta star transformation

- Compensation theorem

- Reciprocity theorem

- Millman's theorem.

OBJECTIVE TYPE QUESTIONS

Choose the Correct Answer

1. Kirchhoff's current law states that
 - (a) net current flow at the junction is positive
 - (b) algebraic sum of the currents meeting at the junction is zero
 - (c) no current can leave the junction without some current entering it
 - (d) total sum of currents meeting at the junction is zero.
 2. According to Kirchhoff's voltage law, the algebraic sum of all IR drops and e.m.fs. in any closed loop of a network is always
 - (a) negative
 - (b) positive
 - (c) determined by battery e.m.fs.
 - (d) zero.
 3. Kirchhoff's current law is applicable to only
 - (a) junction in a network
 - (b) closed loops in a network
 - (c) electric circuits
 - (d) electronic circuits.
 4. Kirchhoff's voltage law is related to
 - (a) junction voltages
 - (b) battery e.m.fs.
 - (c) IR drops
 - (d) both (a) and (b)
 - (e) none of the above.
 5. Superposition theorem can be applied only to circuits having
 - (a) resistive elements
 - (b) passive elements
 - (c) non-linear elements
 - (d) linear bilateral elements.
 6. The concept on which superposition theorem is based is
 - (a) reciprocity
 - (b) duality
 - (c) non-linearity
 - (d) linearity.
 7. Thevenin resistance R_{th} is found
 - (a) by removing voltage sources along with their internal resistances
 - (b) by short-circuiting the given two terminals
 - (c) between any two 'open' terminals
 - (d) between same open terminals as for E_{th} .
 8. An ideal voltage source should have
 - (a) large value of e.m.f.
 - (b) small value of e.m.f.
 - (c) zero source resistance
 - (d) infinite source resistance.
 9. For a voltage source
 - (a) terminal voltage is always lower than source e.m.f.
 - (b) terminal voltage cannot be higher than source e.m.f.
 - (c) the source e.m.f. and terminal voltage are equal.
 10. To determine the polarity of the voltage drop across a resistor, it is necessary to know
 - (a) value of current through the resistor
 - (b) direction of current through the resistor
 - (c) value of resistor
 - (d) e.m.fs. in the circuit.

ANSWERS

1. (b) 2. (d) 3. (a) 4. (d) 5. (d) 6. (d) 7. (d)

8. (c) 9. (b) 10. (b).

THEORETICAL QUESTIONS

1. Define the following terms :
Circuit, Electrical network, Active network, Node and Branch.
2. What are the limitations of Ohm's law ?
3. State and explain Kirchhoff's laws.
4. Discuss briefly application of Kirchhoff's laws.
5. Explain the nodal voltage method for solving networks. How are the nodal equations written ?
6. Explain Cramer's rule used for solving equations by determinants.
7. State and explain superposition theorem.
8. State Norton's theorem. List the steps for finding the current in a branch of a network with the help of this theorem.
9. State Thevenin's theorem.
10. State the maximum power transfer theorem and explain its importance.
11. State the compensation theorem and discuss its application.
12. State Millman's theorem.

UNSOLVED EXAMPLES

1. Determine the magnitude and direction of the current in each of the batteries L, M and N shown in the Fig. 81.

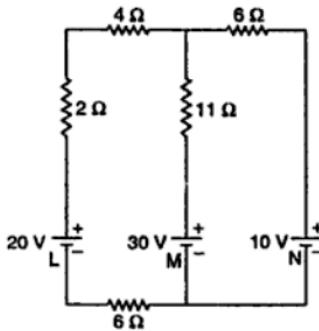


Fig. 81

2. Two batteries are connected in parallel. The e.m.f. and internal resistance of one are 110 V and 6 Ω respectively and the corresponding values for other are 130 V and 4 Ω respectively. A resistance of 20 Ω is connected across the parallel combination. Calculate :
 - (i) The value and direction of the current in each battery.
 - (ii) The terminal voltage.

[Ans. (i) 0.1786 A, 5.2678 A (ii) 108.928 V]

[Hint. Terminal voltage = $(I_1 + I_2)R$]
3. Two cells A and B are connected in parallel, unlike poles being joined together. The terminals of the cells are then joined by two resistors of 4 Ω and 2 Ω in parallel. The e.m.f. of A is 2 V, its internal resistance is 1 Ω ; the e.m.f. of B is 1 V, its internal resistance is 2 Ω. Find the current in each of the four branches of the circuit.

[Ans. 4/3 A, 5/6 A, 1/6 A, 1/3 A]

4. What is the equivalent resistance of the network shown in Fig. 82?

[Ans. 600 Ω] (B.T.E. Delhi)

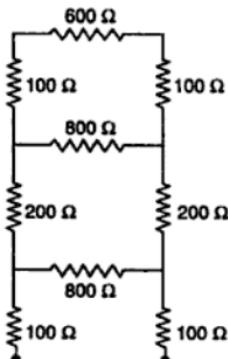


Fig. 82

5. Determine the currents in the three batteries (*L*, *M* and *N*) in the network shown in Fig. 83 and show their values and direction of flow on the diagram. Neglect the internal resistance of batteries.

[Ans. 2 A, 1 A, 0 A]

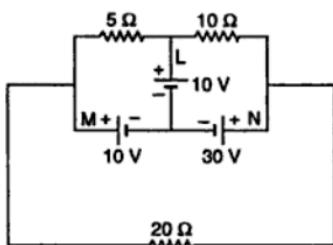


Fig. 83

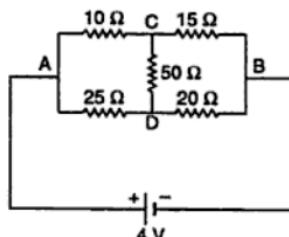


Fig. 84

6. Determine the magnitude and direction of flow of current in the branch *CD* for the circuit shown in the above Fig. 84.

[Ans. 7/75 A from *C* to *D*]

7. For the lattice-type network shown in Fig. 85, calculate the current in each branch of the network.

(Bangladesh University)

$$\left[\begin{aligned} \text{Ans. } I_{ab} &= \frac{1}{50} \text{ A} ; I_{bfe} &= \frac{1}{100} \text{ A} ; I_{bc} &= \frac{1}{100} \text{ A} ; \\ I_{ad} &= \frac{1}{100} \text{ A} ; I_{de} &= \frac{1}{50} \text{ A} ; I_{efg} &= \frac{3}{100} \text{ A} \end{aligned} \right]$$

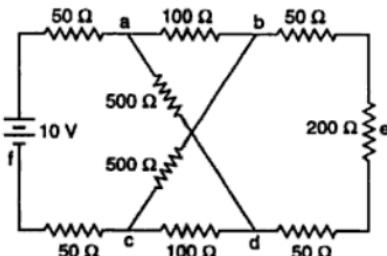


Fig. 85

8. Two storage batteries, *A* and *B*, are connected in parallel to supply a load the resistance of which is $1.2\ \Omega$. Calculate :
 (i) The current in this load.
 (ii) The current supplied by each battery if the open-circuit e.m.f. of *A* is 12.5 V and that of *B* is 12.8 V , the internal resistance of *A* being $0.05\ \Omega$ and that of *B* $0.08\ \Omega$. *(London University)*
 [Ans. (i) 10.25 A (ii) 4 A (*A*), 6.25 A (*B*)]
9. A load having a resistance of $0.1\ \Omega$ is fed by two storage batteries connected in parallel. The open circuit e.m.f. of one battery (*A*) is 12.1 V and that of the other battery (*B*) is 11.8 V . The internal resistances are $0.03\ \Omega$ and $0.04\ \Omega$ respectively. Calculate :
 (i) The current supplied to the load
 (ii) The current in each battery
 (iii) The terminal voltage of each battery. *(London University)*
 [Ans. (i) 102.2 A , (ii) 62.7 A (*A*), 39.5 A (*B*), (iii) 10.22 V]
10. A battery having an e.m.f. of 110 V and an internal resistance of $0.2\ \Omega$ is connected in parallel with another battery having an e.m.f. of 100 V and internal resistance $0.25\ \Omega$. The two batteries in parallel are placed in series with a regulating resistance of $5\ \Omega$ and connected across 200 V mains. Calculate :
 (i) The magnitude and direction of the current in each battery.
 (ii) The total current taken from the supply mains. *(Sumbhal University)*
 [Ans. (i) 11.96 A (discharge); 30.43 A (charge) (ii) 18.47 A]
11. A wheatstone bridge *ABCD* is arranged as follows : $AB = 50\text{ ohms}$, $BC = 100\text{ ohms}$ and $CD = 101\text{ ohms}$. A galvanometer of 1000 ohms resistance is connected between *B* and *D*. A 2-volt battery having negligible resistance is connected across *A* and *C*. Estimate the current flowing through the galvanometer.
 [Ans. $4.14\ \mu\text{A}$ from *D* to *B*]
12. Determine the current through the galvanometer *G* in the wheatstone bridge network of the given Fig. 86. *[Ans. 0.52 mA]*

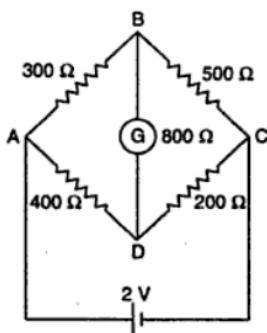


Fig. 86

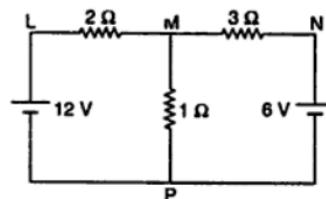


Fig. 87

13. Determine the currents through various resistors of the circuit shown in above Fig. 87.

$$\left[\text{Ans. } \frac{42}{11}\text{ A (L to M)} ; \frac{6}{11}\text{ A (N to M)} ; \frac{48}{11}\text{ A (M to P)} \right]$$

14. Find I_1 , I_2 and I_3 in the network shown in Fig. 88, using loop-current method.

[Ans. 1 A, 2 A, 3 A]

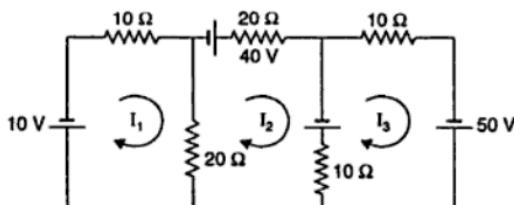


Fig. 88

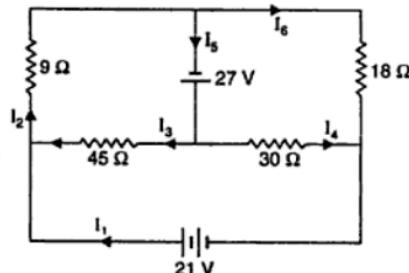


Fig. 89

15. Find the currents in the branches of network of Fig. 89 using nodal voltage method.

[Ans. $I_1 = 1.42$ A, $I_2 = 1.68$ A, $I_3 = 0.26$ A, $I_4 = 1.1$ A, $I_5 = 1.36$ A, $I_6 = 0.32$ A]

16. Using superposition theorem find the currents in the different branches of the network shown in Fig. 90.

[Ans. $I_1 = 0.352$ A, $I_2 = 1.082$ A, $I = 1.432$ A]

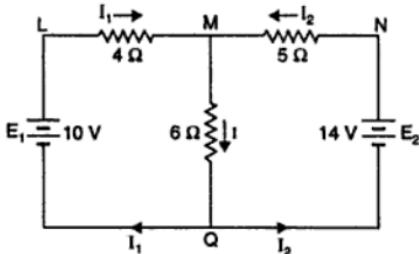


Fig. 90

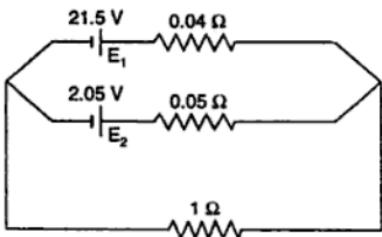


Fig. 91

17. By using superposition theorem, find the current in 1Ω resistance in Fig. 91. Internal resistances of the cells are negligible.

[Ans. 2.066 A]

18. Using superposition theorem find the current in 20Ω resistor of the circuit shown in Fig. 92.

[Ans. 0.443 A]

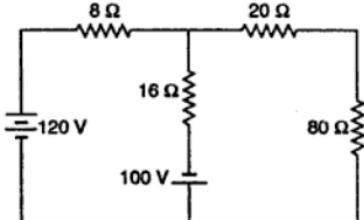


Fig. 92

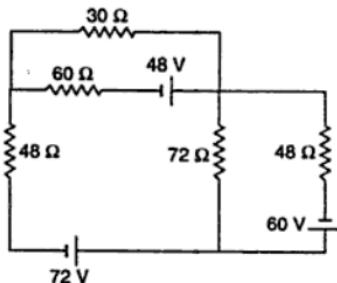


Fig. 93

19. Find the current in the 30Ω resistor of the circuit shown in Fig. 93, using superposition theorem.

[Ans. 0.662 A]

20. With reference to the network of Fig. 94, by applying Thevenin's theorem find the following : (i) The equivalent e.m.f. of the network when viewed from terminals A and B (ii) The equivalent resistance of the network when looked into from terminals A and B, and (iii) Current in the load resistance R_L of 15Ω .
 [Ans. 1 A]

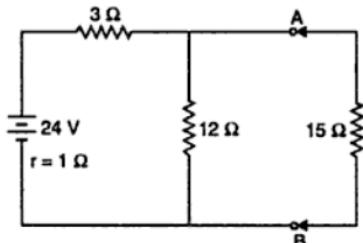


Fig. 94

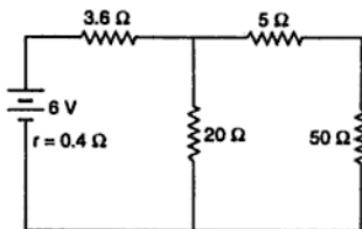


Fig. 95

21. Find the current through 50Ω resistance in the circuit shown in Fig. 95. Use Thevenin's theorem.
 [Ans. 0.086 A]
22. Calculate the current in the 8Ω resistor of Fig. 96 by using Thevenin's theorem.
 [Ans. 0.8 A]

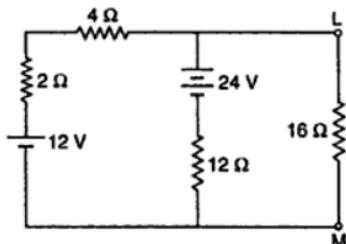


Fig. 96

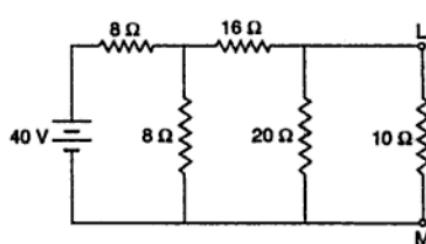


Fig. 97

23. Use Norton's theorem to calculate current flowing through 10Ω resistor of Fig. 97.
 24. Fig. 98 shows network with the value of load resistance $R_L = 50 \Omega$. Develop Norton's equivalent circuit and determine the current and power delivered to R_L .
 [Ans. 0.114 A ; 0.65 W]

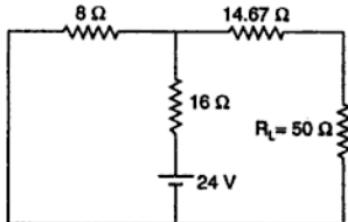


Fig. 98

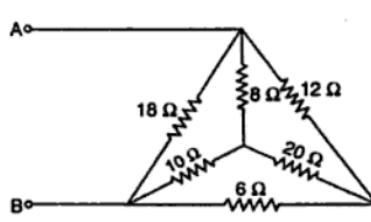


Fig. 99

25. Fig. 99 shows a number of resistances connected in delta and star. Find the resistance across the terminals A and B. Use star/delta conversion method.
 [Ans. 2.96 Ω]

26. In the given circuit, find the resistance between the points *B* and *C* (Fig. 100).

[Ans. 5 Ω]

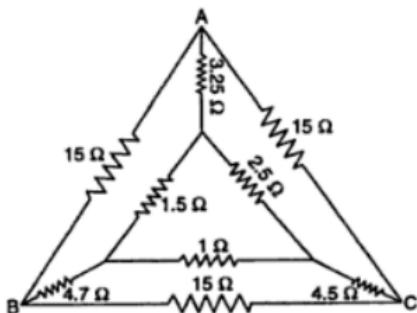


Fig. 100

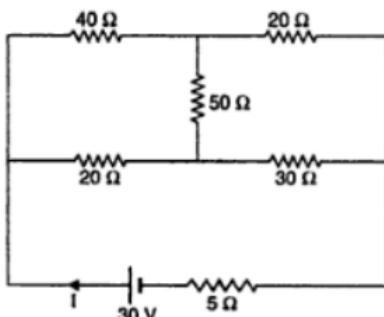


Fig. 101

27. By using delta/star transformation for Fig. 101, find the current *I* supplied by the battery.

[Ans. 0.95 A]

28. Find the current in the galvanometer arm in the network shown in the Fig. 102, using delta/star transformation.

[Ans. 0.236 A]

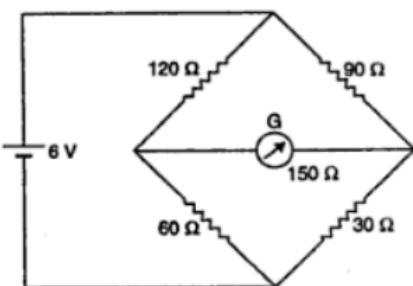


Fig. 102

29. A bridge network *ABCD* has arms *AB*, *BC*, *CD* and *DA* of resistances 2, 2, 4 and 2 ohms respectively. If the detector *AC* has a resistance of 2 ohms, determine by star/delta transformation, the network resistance as viewed from the battery terminals *BD*.

[Ans. 4.38 Ω]



A.C. Circuits

1. Introduction to alternating current.
 2. Generation and equations of alternating voltages and currents.
 3. Alternating voltage and current.
 4. Single phase circuits—A.C. through pure ohmic resistance alone—A.C. through pure inductance alone—A.C. through pure capacitance alone—Phasor algebra—A.C. series circuit—R-L circuit—R-C. circuit—R-L-C circuit—A.C. parallel circuits.
 5. Transients—General aspects—D.C. transients—A.C. transients—Highlights—Objective Type Questions—Theoretical Questions—Unsolved Examples.
-

1. INTRODUCTION TO ALTERNATING CURRENT

A.C. means alternating current—*The current or voltage which alternates its direction and magnitude every time.* Now a days 95% of the total energy is produced, transmitted and distributed in A.C. supply.

The *reasons* are the following :

- (i) More voltage can be generated (upto 33000 V) than D.C. (650 V only).
- (ii) A.C. voltage can be increased and decreased with the help of a static machine called the 'transformer'.
- (iii) A.C. transmission and distribution is more economical as line material (say copper) can be saved by transmitting power at higher voltage.
- (iv) A.C. motors for the same horse power as of D.C. motors are cheaper, lighter in weight, require less space and require lesser attention in operation and maintenance.
- (v) A.C. can be converted to D.C. (direct current) easily, when and where required but D.C. cannot be converted to A.C. so easily and it will not be economical.

However, D.C. entails the following *merits* and hence finds wide applications.

- (i) D.C. series motors are most suitable for traction purposes in tramway, railways, crains and lifts.
- (ii) For electroplating, electrolytic and electrochemical processes (battery charging etc.), D.C. is required.
- (iii) Arc lamps for search lights and cinema projectors work on D.C.
- (iv) Arc welding is better than on A.C.
- (v) Relay and operating time switches, etc., and circuit-breakers, D.C. works more efficiently.
- (vi) In rolling mills, paper mills, colliery winding, etc., where fine speed control of speeds in both directions is required, D.C. motors are required.

2. GENERATION AND EQUATIONS OF ALTERNATING VOLTAGES AND CURRENTS

Generation of Alternating Voltages and Currents

Alternating voltages may be generated in the following two ways :

1. By *rotating a coil in a stationary magnetic field*, as shown in Fig. 1.
2. By *rotating a magnetic field within a stationary coil*, as shown in Fig. 2.

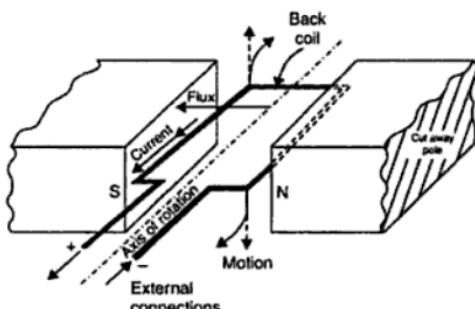


Fig. 1. Rotating a coil in a stationary magnetic field.

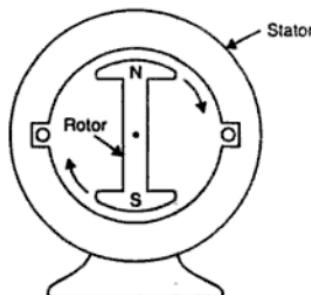


Fig. 2. Rotating a magnetic field within a stationary coil.

The value of the voltage generated in each case depends upon the following factors :

- (i) The number of turns in the coils ;
- (ii) The strength of the field ;
- (iii) The speed at which the coil or magnetic field rotates.
- Out of the above two methods the *rotating-field method is mostly used in practice.*

Equations of Alternating Voltages and Currents

Fig. 3 shows a rectangular coil of N turns rotating clockwise with an angular velocity ω radians per second in a uniform magnetic field.

Since by Faraday's law, the voltage is proportional to the rate at which the conductor cuts across the magnetic field or to the rate of change of flux linkages, the shape of the wave of voltage applied to the external circuit will be determined by the *flux distribution in the air gap*. For a uniform field between the poles it is evident that maximum flux will link with the coil when its plane is in *vertical position i.e., perpendicular to the direction of flux between the poles*. Also it is obvious that when the plane of coil is *horizontal no flux will link with the coil*.

If the position of the coil with reference to the vertical axis be denoted by θ the flux linking with the coil at any instant, as the coil rotates may be determined from the relation,

$$\phi = \phi_{\max} \cos \theta \\ = \phi_{\max} \cos \omega t \quad \dots(i) \quad (\because \theta = \omega t)$$

where, ϕ_{\max} = Maximum flux which can link with the coil, and

t = Time taken by the coil to move through an angle θ from vertical position.

Using Faraday's law to eqn. (i), in order to determine the voltage equation,

$$e = -N \frac{d\phi}{dt} \quad \text{(where } e \text{ is the instantaneous value of the induced e.m.f.)}$$

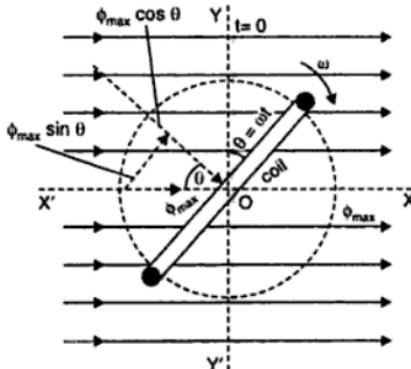


Fig. 3. A coil rotating in a magnet field.

$$= -N \frac{d}{dt} (\phi_{max} \cos \omega t) = \omega N \phi_{max} \sin \omega t$$

or

$$e = \omega N \phi_{max} \sin \theta \quad \dots(ii)$$

As the value of e will be maximum when $\sin \theta = 1$,

$$E_{max} = \omega N \phi_{max}$$

The eqn. (ii) can be written in simpler form as

$$e = E_{max} \sin \theta$$

Similarly the equation of induced alternating current (instantaneous value) is

$$i = I_{max} \sin \theta \quad \text{(if the load is resistive)} \quad \dots(iv)$$

Waveforms. A waveform (or wave-shape) is the shape of a curve obtained by plotting the instantaneous values of voltage or current as ordinate against time as abscissa.

Fig. 4 (a, b, c, d, e) shows irregular waveforms, but each cycle of current/voltage is an exactly replica of the previous one. Alternating e.m.fs and currents produced by machines usually both have positive and negative half waves, the same shape as shown. Fig. 4(f) represents a sine wave of A.C. This is the simplest possible waveform, and alternators are designed to give as nearly as possible a sine wave of e.m.f.

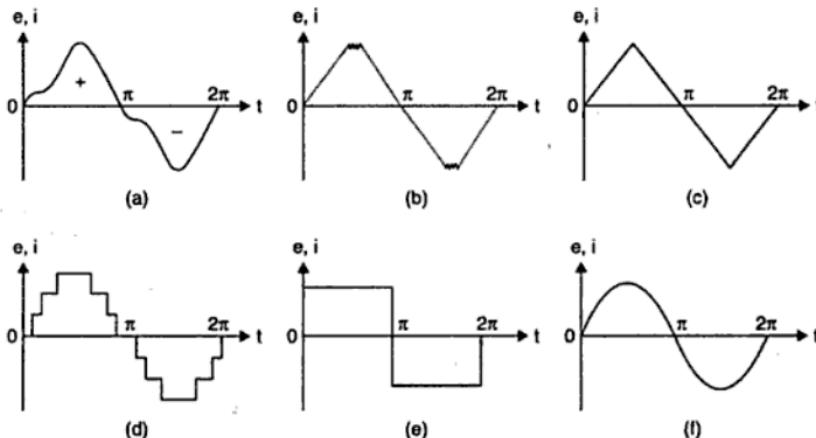


Fig. 4. Waveforms.

- In general, an *alternating current or voltage is one the circuit direction of which reverses at regularly recurring intervals.*
- The waves deviating from the standard sine wave are termed as *distorted waves*.
- *Complex waves* are those which depart from the ideal sinusoidal form. All alternating complex waves, which are periodic and have equal positive and negative half cycles can be shown to be made up of a number of pure sine waves, having different frequencies but all these frequencies are integral multiples of that of the lowest alternating wave, called the *fundamental* (or first harmonic). These waves of higher frequencies are called *harmonics*.

3. ALTERNATING VOLTAGE AND CURRENT

Modern alternators produce an e.m.f. which is for all practical purposes sinusoidal (i.e., a sine curve), the equation between the e.m.f. and time being

$$e = E_{\max} \sin \omega t \quad \dots(1)$$

where, e = Instantaneous voltage ; E_{\max} = Maximum voltage ;

ωt = Angle through which the armature has turned from neutral.

Taking the frequency as f hertz (cycles per second), the value of ω will be $2\pi f$, so that the equation reads

$$e = E_{\max} \sin (2\pi f t).$$

The graph of the voltage will be as shown in Fig. 5.

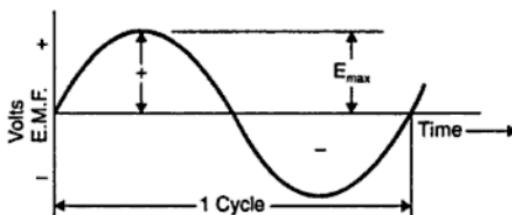


Fig. 5. The graph of the sinusoidal voltage.

1. Cycle. One complete set of positive and negative values of an alternating quantity is known as a *cycle*. A cycle may also sometimes be specified in terms of angular measure. In that case, one complete cycle is said to spread over 360° or 2π radians.

2. Amplitude. The maximum value, positive or negative, of an alternating quantity, is known as its *amplitude*.

3. Frequency (f). The number of cycles/second is called the frequency of the alternating quantity.

Its unit is *hertz* (Hz).

4. Time Period (T). The time taken by an alternating quantity to complete the cycle is called its *time period*. For example, a 50 hertz (Hz) alternating current has a time period of $\frac{1}{50}$ second.

Time period is reciprocal of frequency.

$$\text{i.e.,} \quad T = \frac{1}{f} \quad \text{(or} \quad f = \frac{1}{T} \quad \dots(2)$$

5. Root mean square (R.M.S.) value. The r.m.s. (or effective) value of an alternating current is given by that steady (D.C.) current which when flowing through a given circuit for a given time produces the same heat as produced by the alternating current when flowing through the same circuit for the same time.

R.M.S. value is the value which is taken for power purposes of any description. This value is obtained by finding the square root of the mean value of the squared ordinates for a cycle or half-cycle (See Fig. 5).

This is the value which is used for all power, lighting and heating purposes, as in these cases the power is proportional to the square of the voltage.

Refer Fig. 5.

The equation of sinusoidal alternating current is given as :

$$i = I_{\max} \sin \theta$$

The mean of squares of the instantaneous values of current over half cycle is

$$I^2 = \int_0^\pi \frac{i^2 d\theta}{(\pi - 0)}$$

$$\begin{aligned} I^2 &= \frac{1}{\pi} \int_0^\pi i^2 d\theta = \frac{1}{\pi} \int_0^\pi (I_{\max} \sin \theta)^2 d\theta \\ &= \frac{1}{\pi} \int_0^\pi I_{\max}^2 \sin^2 \theta d\theta = \frac{I_{\max}^2}{\pi} \int_0^\pi \left(\frac{1 - \cos 2\theta}{2} \right) d\theta \\ &= \frac{I_{\max}^2}{2\pi} \int_0^\pi (1 - \cos 2\theta) d\theta = \frac{I_{\max}^2}{2\pi} \left| \theta - \frac{\sin 2\theta}{2} \right|_0^\pi \\ &= \frac{I_{\max}^2}{2\pi} \times \pi = \frac{I_{\max}^2}{2} \quad \text{or} \quad I = \sqrt{\frac{I_{\max}^2}{2}} = \frac{I_{\max}}{\sqrt{2}} \end{aligned}$$

or

$$I = 0.707 I_{\max} \quad \dots(3)$$

Note. While solving problems, the values of given current and voltage should always be taken as the r.m.s. values, unless indicated otherwise.

6. Average or mean value. The average value of an alternating current is expressed by *that steady current which transfers across any circuit the same charge as is transferred by that alternating current during the same time*.

The mean value is only of use in connection with processes where the results depend on the current only, irrespective of the voltage, such as electroplating or battery charging.

Refer Fig. 6.

The value of instantaneous current is given by

$$i = I_{\max} \sin \theta$$

Refer Fig. 6. The value of instantaneous current is given by :

$$i = I_{\max} \sin \theta \quad [\theta = \omega t]$$

$$I_{av} = \frac{1}{(\pi - 0)} \int_0^\pi id\theta$$

Limits are taken from 0 to π , since only first half cycle is considered.
For whole cycle, the average value of sine wave is zero.

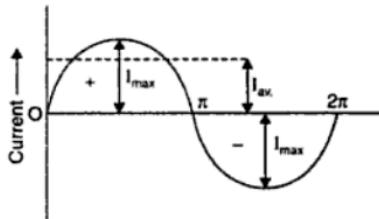


Fig. 6

$$\begin{aligned} &= \frac{1}{\pi} \cdot \int_0^\pi I_{\max} \cdot \sin \theta d\theta = \frac{1}{\pi} \cdot I_{\max} \left| -\cos \theta \right|_0^\pi \\ &= \frac{1}{\pi} \cdot I_{\max} [1 - (-1)] = \frac{2}{\pi} \cdot I_{\max} \end{aligned}$$

or




$$I_{av} = 0.637 I_{\max} \quad \dots(4)$$



Note. In case of unsymmetrical alternating current viz. half-wave rectified current the average value must always be taken over the whole cycle.

7. Form and Peak Factors

Form factor. The ratio of r.m.s. (or effective) value to average value is the form factor (K_f) of the wave form. It has use in voltage generation and instrument correction factors.

Peak factor. The ratio of maximum value to the r.m.s. value is the peak factor (K_p) of the wave form.

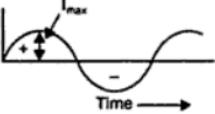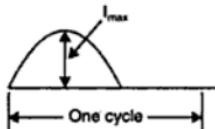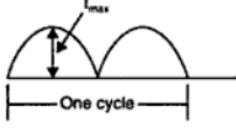S. No.	Wave form	Form factor (K_f) $= \frac{\text{r.m.s. value}}{\text{average value}}$	Peak factor (K_p) $= \frac{\text{max. value}}{\text{r.m.s. value}}$
1.	Sine wave :  Fig. 7		
	$\text{R.M.S. value} = \frac{I_{\max}}{\sqrt{2}} = 0.707 I_{\max}$ $\text{Average value} = \frac{2}{\pi} I_{\max} = 0.637 I_{\max}$	$K_f = \frac{0.707 I_{\max}}{0.637 I_{\max}} = 1.11$	$K_p = \frac{I_{\max}}{0.707 I_{\max}} = 1.41$
2.	Half wave rectified sine wave :  Fig. 8		
	$\text{R.M.S. value} = \frac{I_{\max}}{2} = 0.5 I_{\max}$ $\text{Average Value} = \frac{1}{\pi} I_{\max} = 0.318 I_{\max}$	$K_f = \frac{0.5 I_{\max}}{0.318 I_{\max}} = 1.57$	$K_p = \frac{I_{\max}}{0.5 I_{\max}} = 2.0$
3.	Full wave rectified sine wave :  Fig. 9		
	$\text{R.M.S. value} = \frac{I_{\max}}{\sqrt{2}} = 0.707 I_{\max}$ $\text{Average value} = \frac{2}{\pi} I_{\max} = 0.637 I_{\max}$	$K_f = \frac{0.707 I_{\max}}{0.637 I_{\max}} = 1.11$	$K_p = \frac{I_{\max}}{0.707 I_{\max}} = 1.41$

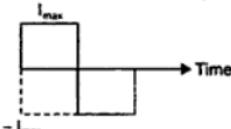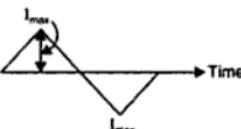S. No.	Wave form	Form factor (K_f) $= \frac{r.m.s. value}{average value}$	Peak factor (K_p) $= \frac{max. value}{r.m.s. value}$
4.	Rectangular wave :		
	 <p>Fig. 10 R.M.S. value = I_{max} Average value = I_{max}</p>	$K_f = 1$	$K_p = 1$
5.	Triangular wave :		
	 <p>Fig. 11 R.M.S. = $\frac{I_{max}}{\sqrt{3}} = 0.578 I_{max}$ Average value = $\frac{I_{max}}{2} = 0.5 I_{max}$</p>	$K_f = \frac{0.578 I_{max}}{0.5 I_{max}} = 1.16$	$K_p = \frac{I_{max}}{0.578 I_{max}} = 1.73$

Reasons for using alternating current (or voltage) of sinusoidal form :

An alternating current (or voltage) of sinusoidal form is normally used because of the following reasons :

1. Mathematically, it is quite simple.
2. Its integrals and differentials both are sinusoidal.
3. It lends itself to vector representation.
4. A complex waveform can be analysed into a series of sine waves of various frequencies, and each such component can be dealt with separately.
5. This waveform is desirable for power generation, transmission and utilisation.

8. Phase and phase angle. The 'phase' of an

A.C. wave may be defined as its position with respect to a reference axis or reference wave and 'phase angle' as the angle of lead or lag with respect to the reference axis or with respect to another wave.

Examples. The phase of current at point L is

$\frac{T}{4}$ second where T is the time period or expressed in

terms of angle θ , it is $\frac{\pi}{2}$ radian (Fig. 12). Similarly

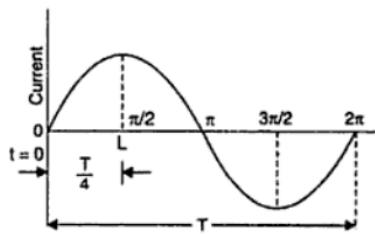


Fig. 12

phase of the rotating coil at the instant shown in Fig. 13 is ωt which is therefore called its *phase angle*.

The e.m.fs. induced in both the coils (Fig. 13) will be of the same frequency and of sinusoidal shape, although the values of instantaneous e.m.f. induced will be different. However, the alternating e.m.fs. would reach their maximum and zero values at the *same time* as shown in Fig. 13 (b). Such alternating voltages or curve are said to *in phase* with each other.

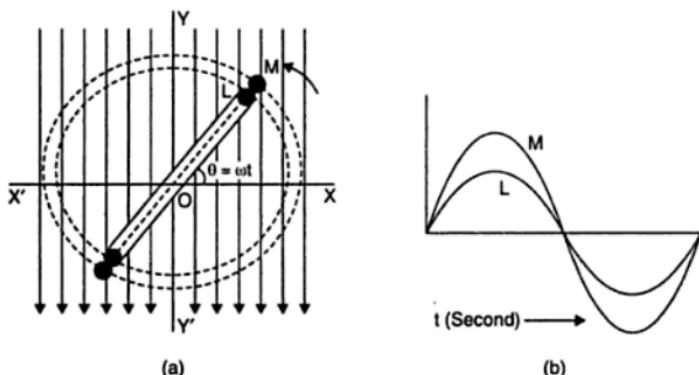


Fig. 13

Refer Fig. 14. M lags behind L by β and N lags behind L by $(\alpha + \beta)$ because they reach their maximum later.

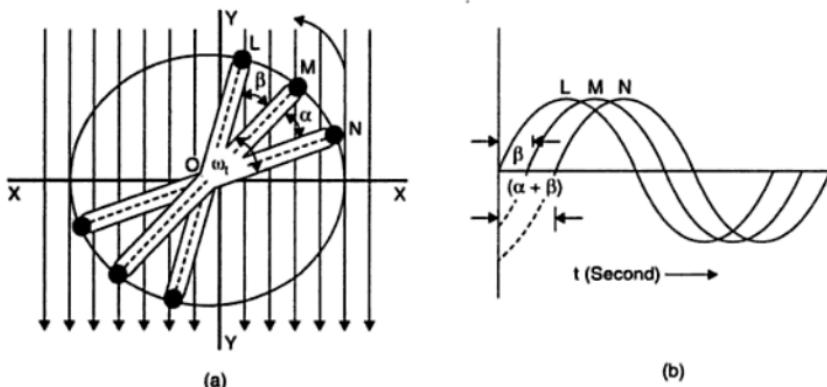


Fig. 14

Example 1. (a) What is the equation of a 25 cycle current sine wave having r.m.s. value of 30 amps?

(b) A 60 cycle engine-driven alternator has a speed of 1200 r.p.m. How many poles are there in the alternator?

Solution. We know that, $i = I_{\max} \sin \omega t$

$$\begin{aligned} &= I_{\max} \sin 2\pi f t \\ &= 30 \times \sqrt{2} \cdot \sin (2\pi \times 25 \times t) \\ &= 42.42 \sin 157 t. \text{ (Ans.)} \end{aligned}$$

$\left(\because \frac{\text{R.M.S. value}}{\text{Max. value}} = \frac{1}{\sqrt{2}} \right)$

Using the relation, $f = \frac{Np}{120}$

where, f = frequency, N = speed in r.p.m., and

p = No. of poles

$$\therefore 60 = \frac{1200 p}{120} \quad \text{or } p = 6. \text{ (Ans.)}$$

Example 2. An alternating current varying sinusoidally with a frequency of 50 Hz has an r.m.s. value of 40 A. Find :

(i) The instantaneous value 0.0025 seconds after passing through maximum positive value, and

(ii) The time measured from a maximum value when the instantaneous current is 14.14 A.

Solution.

$$I_{\max} = \sqrt{2} \times 40 = 56.56 \text{ A}$$

$$\omega = 2\pi f = 2\pi \times 50 = 100\pi \text{ radians}$$

(i)

$$\begin{aligned} i &= I_{\max} \cos \omega t \\ &= 56.56 \cos 100\pi t \\ &= 56.56 \cos (100\pi \times 0.0025) \\ &= 56.56 \cos 45^\circ \\ &= 40 \text{ A. (Ans.)} \end{aligned}$$

... (Taking $\pi = 180^\circ$)

(ii)

$$14.14 = 56.56 \cos (100 \times 180 \times t)$$

$$\frac{14.14}{56.56} = \cos (100 \times 180 \times t)$$

or

$$\cos^{-1}(0.25) = 100 \times 180 \times t$$

or

$$75.5^\circ = 100 \times 180 \times t$$

$$\therefore t = 0.00419 \text{ s. (Ans.)}$$

Example 3. A sinusoidal alternating voltage of 50 Hz has an r.m.s. value of 200 V. Write down the equation for the instantaneous value and find this value 0.0125 sec. after passing through a positive maximum value. At what time measured from a positive maximum value will the instantaneous voltage be 141.4 volts ?

Solution. Refer Fig. 15.

$$V_{\max} = \sqrt{2} \times 200 = 282.2 \text{ volts}$$

$$\omega = 2\pi f = 2\pi \times 50 = 100\pi \text{ rad/sec.}$$

∴ Equation for the instantaneous voltage.

$$\begin{aligned} V &= V_{\max} \sin \omega t \text{ (with reference to point O)} \\ &= 282.2 \sin 100\pi t \end{aligned} \quad \dots(i)$$

Since the time (0.0125 sec.) is given from the point L (i.e., from positive maximum value) the equation (i) when referred to point L can be written as

$$v = 282.2 \sin (90^\circ + 100\pi t)$$

$$= 282.2 \cos 100\pi t$$

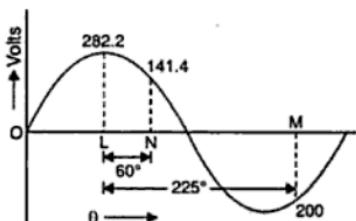


Fig. 15

Hence instantaneous value of the voltage 0.0125 sec. after passing through + ve maximum value,

$$\begin{aligned} v &= 282.2 \cos(100\pi \times 0.0125) && \dots(\text{angle in radians}) \\ &= 282.2 \cos(100 \times 180 \times 0.0125) && \dots(\text{angle in degrees}) \\ &= 282.2 \cos 225^\circ = 280.2 \times \left(-\frac{1}{\sqrt{2}}\right) \\ &= -200 \text{ V (point M). (Ans.)} \end{aligned}$$

Also

$$v = 141.4 \text{ V}$$

$$\therefore 141.4 = 282.2 \cos(100 \times 180 \times t)$$

or

$$0.5 = \cos(100 \times 180 \times t)$$

or

$$\cos^{-1}(0.5) = 100 \times 180 \times t$$

or

$$60^\circ = 100 \times 180 \times t$$

or

$$t = \frac{1}{300} \text{ sec. (point N). (Ans.)}$$

Example 4. (a) What is the peak value of a sinusoidal alternating current of 4.78 r.m.s. amps?

(b) What is the r.m.s. value of a rectangular wave with an amplitude of 9.87 volts?

(c) What is the average value over half a cycle of a sinusoidal alternating current whose r.m.s. value is 31 A?

Solution. (a) Peak value, $I_{max} = \sqrt{2} \times 4.78 = 6.76 \text{ A. (Ans.)}$

(b) Refer Fig. 16. If the first half-cycle is divided into n equal parts each of value V , then

$$\begin{aligned} \text{r.m.s. value} &= \left(\frac{V^2 + V^2 + V^2 + \dots}{n} \right)^{1/2} \\ &= V = 9.87 \text{ volts. (Ans.)} \end{aligned}$$

(c) $I_{r.m.s.} = 31 \text{ A}$

$$\begin{aligned} I_{av} &= \frac{I_{r.m.s.}}{\text{form factor}} \\ &= \frac{31}{1.11} = 27.93 \text{ A. (Ans.)} \end{aligned}$$

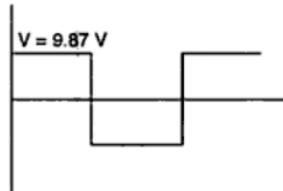


Fig. 16

Example 5. The graph in Fig. 17 shows the variation of voltage with time. Use the graph to calculate the average and r.m.s. value of the voltage. What is the frequency of the voltage? What would be the r.m.s. value of sine wave having the same peak value?

Solution. Refer Fig. 17.

As the graph is symmetrical about time axis, considering only the positive half cycle.

$$\begin{aligned} \text{Average value, } V_{av} &= \frac{0 + 10 + 20 + 40 + 100 + 120 + 100 + 40 + 20 + 10}{10} \\ &= 46 \text{ V. (Ans.)} \end{aligned}$$

$$\begin{aligned} \text{R.M.S. value, } V &= \sqrt{\frac{0^2 + 10^2 + 20^2 + 40^2 + 100^2 + 120^2 + 100^2 + 40^2 + 20^2 + 10^2}{10}} \\ &= \sqrt{\frac{0 + 100 + 400 + 1600 + 10000 + 14400 + 10000 + 1600 + 400 + 100}{10}} \end{aligned}$$

$$= \sqrt{\frac{38600}{10}} = \sqrt{3860} = 62.1 \text{ V. (Ans.)}$$

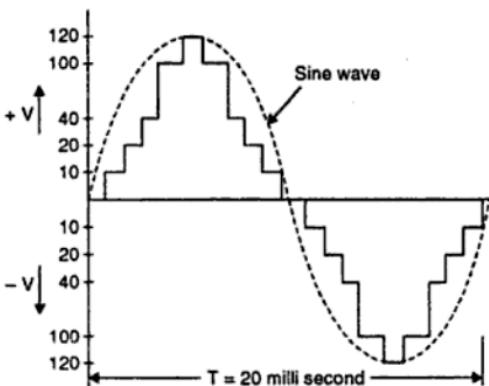


Fig. 17

Since the time period 'T' is 20 millisec.

$$\therefore \text{Frequency } f = \frac{1}{T} = \frac{1}{20 \times 10^{-3}} = 50 \text{ Hz. (Ans.)}$$

$$\begin{aligned} \text{R.M.S. value of a sine wave of the same peak value} \\ = 0.707 \times 120 = 84.84 \text{ V. (Ans.)} \end{aligned}$$

Example 6. Prove that if a D.C. current of I_{amps} is superposed in a conductor by an A.C. current of max. value I amps, the r.m.s. value of the resultant is $\sqrt{\frac{3}{2}} I$.

Solution. Let the A.C. current be $i = I \sin \theta$ where i is the instantaneous value of the A.C. current and I the D.C. current.

The r.m.s. value of $(I + i)$ over one complete cycle is,

$$\begin{aligned} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (I + I \sin \theta)^2 d\theta} \\ &= I \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (I + 2 \sin \theta + \sin^2 \theta)} \\ &= I \sqrt{\left\{ \frac{1}{2\pi} \int_0^{2\pi} 1 + 2 \sin \theta + \left(\frac{1 - \cos 2\theta}{2} \right) \right\}} \\ &= I \sqrt{\frac{1}{2\pi} \left| \theta - 2 \cos \theta + \frac{\theta}{2} - \frac{\sin 2\theta}{4} \right|_0^{2\pi}} \\ &= I \sqrt{\frac{1}{2\pi} (2\pi - 2 + \pi + 2)} \\ &= I \cdot \sqrt{\frac{3}{2}} . \quad (\text{Ans.}) \end{aligned}$$

Example 7. A resultant current wave is made up of two components : a 4A D.C. component and a 50 Hz A.C. component, which is of sinusoidal waveform and which has a maximum value of 4A.

(i) Sketch the resultant wave.

(ii) Write an analytical expression for the current wave, reckoning $t = 0$ at a point where the A.C. component is at zero value and where di/dt is positive.

(iii) What is the average value of the resultant current over a cycle ?

(iv) What is the effective or r.m.s. value of the resultant current ?

Solution. (i) Sketch of the resultant wave :

The two current components and the resultant current wave are shown in Fig. 18. (Ans.)

(ii) **Analytical expression.** The instantaneous value of the resultant current is given by

$$i = (4 + 4 \sin \omega t) = (4 + 4 \sin \theta). \quad (\text{Ans.})$$

(iii) **Average value.** Since the average value of the alternating current over one complete cycle is zero, hence the *average value of the resultant current is equal to the value of D.C. component i.e., 4A* (Ans.)

(iv) **Effective or r.m.s. value :**

Mean value of i^2 over complete cycle is

$$\begin{aligned} &= \frac{1}{2\pi} \int_0^{2\pi} i^2 d\theta = \frac{1}{2\pi} \int_0^{2\pi} (4 + 4 \sin \theta)^2 d\theta \\ &= \frac{1}{2\pi} \int_0^{2\pi} (16 + 32 \sin \theta + 16 \sin^2 \theta) d\theta \\ &= \frac{1}{2\pi} \int_0^{2\pi} \left[16 + 32 \sin \theta + 16 \left(\frac{1 - \cos 2\theta}{2} \right) \right] d\theta \\ &= \frac{1}{2\pi} \int_0^{2\pi} (24 + 32 \sin \theta - 8 \cos 2\theta) d\theta \\ &= \frac{1}{2\pi} \left(24\theta - 32 \cos \theta - 8 \times \frac{\sin 2\theta}{2} \right)_0^{2\pi} \\ &= \frac{1}{2\pi} [(48\pi - 32 \cos 2\pi - 4 \sin 4\pi) - (-32)] = \frac{48\pi}{2\pi} = 24 \text{ A} \end{aligned}$$

$$\therefore \text{R.M.S. value, } I = \sqrt{24} = 4.9 \text{ A. (Ans.)}$$

Example 8. Determine the average and effective values of the saw-tooth waveform shown in Fig. 19. (N.U.)

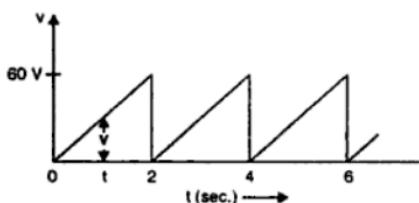


Fig. 19

Solution. Refer Fig. 19.

Since the voltage increases linearly, therefore,

$$V_{av} = \frac{60+0}{2} = 30 \text{ V. (Ans.)}$$

The slope, for the interval $0 < t < 2$ is given by :

$$\text{Slope} = \frac{60}{2} = 30$$

∴ Instantaneous voltage, $v = 30t$ volts

The r.m.s. or effective value of the voltage,

$$V_{r.m.s.}^2 = \frac{1}{T} \int_0^T v^2 dt = \frac{1}{2} \int_0^2 (30t)^2 dt = 450 \int_0^2 t^2 dt = 450 \left| \frac{t^3}{3} \right|_0^2 = 1200$$

or

$$V_{r.m.s.} = 34.64 \text{ V. (Ans.)}$$

Example. 9. Determine the r.m.s. and average values of the waveform shown in Fig. 20.

[Indore University]

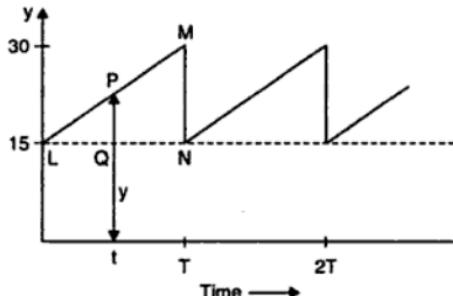


Fig. 20

Solution. Refer Fig. 20.

$$\text{The slope of the curve } LM = \frac{MN}{LN} = \frac{30-15}{T} = \frac{15}{T}$$

Now consider the function y at any time ' t '. We have,

$$\therefore \frac{PQ}{LQ} = \frac{MN}{LN} = \frac{15}{T}$$

$$\frac{y - 15}{t} = \frac{15}{T} \quad \text{or} \quad y = 15 + \left(\frac{15}{T} \right) t$$

This gives the equation for the function for one cycle.

$$Y_{av} = \frac{1}{T} \int_0^T \left[15 + \left(\frac{15}{T} \right) t \right] dt = \frac{1}{T} \int_0^T \left[15 dt + \frac{15}{T} \cdot t \cdot dt \right]$$

$$\text{or} \quad Y_{av} = \frac{1}{T} \left[15 t + \frac{15 t^2}{2T} \right]_0^T = \frac{1}{T} [15 T + 7.5 T] = 22.5. \quad (\text{Ans.})$$

Mean square value

$$= \frac{1}{T} \int_0^T y^2 dt = \frac{1}{T} \int_0^T \left\{ 15 + \left(\frac{15}{T} \right) t \right\}^2 dt$$

$$\begin{aligned}
 &= \frac{1}{T} \int_0^T \left(225 + \frac{225t^2}{T^2} + \frac{450}{T} \cdot t \right) dt \\
 &= \frac{1}{T} \left| 225t + \frac{225t^3}{3T^2} + \frac{450t^2}{2T} \right|_0^T \\
 &= \frac{1}{T} | 225T + 75T + 225T | = 525 \\
 \therefore \text{R.M.S. value} &= \sqrt{525} = 22.9. \quad (\text{Ans.})
 \end{aligned}$$

Example 10. Find the r.m.s. and average value of the trapezoidal current wave-form shown in the Fig. 21. [Bangalore University]

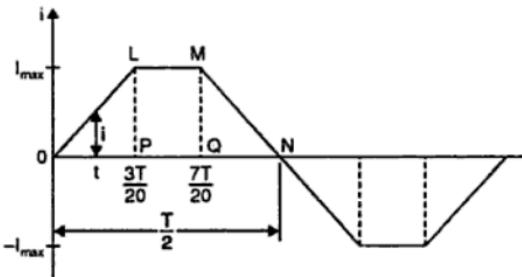


Fig. 21

Solution. Refer Fig. 21. The equation of the current for $0 < t < \frac{3T}{20}$ can be found from the relation,

$$\frac{i}{t} = \frac{I_{\max}}{(3T/20)} \quad \text{or} \quad i = \frac{20I_{\max}}{3T} \cdot t$$

The equation of the current for $\frac{3T}{20} < t < \frac{7T}{20}$ is given by $i = I_{\max}$. Remembering that ΔOLP is identical with MQN ,

$$\begin{aligned}
 \text{R.M.S. value of current, } I_{r.m.s.} &= \sqrt{\frac{1}{(T/2)} \left[2 \int_0^{3T/20} i^2 dt + \int_{3T/20}^{7T/20} I_{\max}^2 dt \right]} \\
 &= \sqrt{\frac{2}{T} \left[2 \left\{ \left(\frac{20I_{\max}}{3T} \right)^2 \int_0^{3T/20} t^2 dt \right\} + I_{\max}^2 \int_{3T/20}^{7T/20} dt \right]} \\
 &= \sqrt{\frac{2}{T} \left[2 \left\{ \left(\frac{20I_{\max}}{3T} \right)^2 \left| \frac{t^3}{3} \right|_0^{3T/20} \right\} + I_{\max}^2 \left| t \right|_{3T/20}^{7T/20} \right]} \\
 &= \sqrt{\frac{2}{T} \left[2 \times \frac{400I_{\max}^2}{9T^2} \times \frac{27}{3 \times 8000} T^3 + I_{\max}^2 \times \left(\frac{7T}{20} - \frac{3T}{20} \right) \right]}
 \end{aligned}$$

$$= \sqrt{\frac{2}{T} \left(0.1 I_{max}^2 T + 0.2 I_{max}^2 T \right)} = \sqrt{0.6 I_{max}^2} = 0.775 I_{max}. \quad (\text{Ans.})$$

Average value of current,

$$\begin{aligned} I_{av} &= \frac{1}{T/2} \left[2 \int_0^{3T/20} idt + \int_{3T/20}^{7T/20} I_{max} dt \right] = \frac{2}{T} \left[2 \int_0^{3T/20} \left(\frac{20 I_{max}}{3T} \right) t dt + I_{max} \int_{3T/20}^{7T/20} dt \right] \\ &= \frac{2}{T} \left[2 \left(\frac{20 I_{max}}{3T} \right) \left| \frac{t^2}{2} \right| \Big|_{3T/20}^{3T/20} + I_{max} \left| t \right| \Big|_{3T/20}^{7T/20} \right] \\ &= \frac{2}{T} \left[2 \left(\frac{20 I_{max}}{3T} \right) \times \frac{1}{2} \left(\frac{3T}{20} \right)^2 + I_{max} \left(\frac{7T}{20} - \frac{3T}{20} \right) \right] \\ &= \frac{2}{T} \left[2 \left(\frac{20 I_{max}}{3T} \right) \times \frac{1}{2} \left(\frac{9T}{400} \right)^2 + I_{max} \times \frac{T}{5} \right] \\ I_{av} &= \frac{2}{T} [0.15 I_{max} \times T + 0.2 I_{max} \times T] = 0.7 I_{max}. \quad (\text{Ans.}) \end{aligned}$$

Example 11. A half wave single anode rectifier has a voltage given by $100 \sin \omega t$ applied to it. Estimate the average value on the d.c. side.

Solution. The wave form on the d.c. side is as shown in Fig. 22.

Mean/Average d.c. voltage will be :

$$\begin{aligned} I_{av} &= \frac{1}{2\pi} \int_0^\pi 100 \sin \theta . d\theta \\ &= \frac{100}{2\pi} \left[-\cos \theta \right]_0^\pi \\ &= 31.83 \text{ V. (Ans.)} \end{aligned}$$

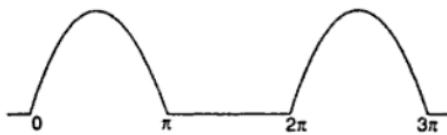


Fig. 22

Example 12. Calculate from the first principles, the reading which would be indicated by a hot-wire ammeter in a circuit whose current waveform is given by $10 \sin \omega t + 3 \sin 3\omega t + 2 \sin 5\omega t$.

Solution. The expression for instantaneous current is :

$$i = 10 \sin \omega t + 3 \sin 3\omega t + 2 \sin 5\omega t$$

The hot-wire ammeter will read the "r.m.s. value" of the wave form.

$$\text{Now } i^2 = (10 \sin \omega t + 3 \sin 3\omega t + 2 \sin 5\omega t)^2$$

$$\begin{aligned} \therefore \text{R.M.S. value of the current} &= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} i^2 d(\omega t)} \\ &= \left[\frac{1}{2\pi} \int_0^{2\pi} [(10 \sin \omega t + 3 \sin 3\omega t + 2 \sin 5\omega t)^2 d(\omega t)] \right]^{1/2} \\ &= \left[\frac{1}{2\pi} \int_0^{2\pi} (10^2 \sin^2 \omega t + 3^2 \sin^2 3\omega t + 2^2 \sin^2 5\omega t + 2 \times 10 \times 3 \sin \omega t \sin 3\omega t \right. \\ &\quad \left. + 2 \times 10 \times 2 \sin \omega t \sin 5\omega t + 2 \times 3 \times 2 \sin 3\omega t \cdot \sin 5\omega t) d(\omega t) \right]^{1/2} \end{aligned}$$

$$= \left[\frac{1}{2\pi} \int_0^{2\pi} \left\{ \frac{10^2 (1 - \cos 2\omega t)}{2} + \frac{3^2}{2} (1 - \cos 6\omega t) + \frac{2^2}{2} (1 - \cos 10\omega t) + * \text{etc.} \right\} d(\omega t) \right]^{1/2}$$

*All the terms containing the product of two sines when integrated over the range 0 to 2π disappear. This is easily seen by splitting such terms into the difference of two cosines.

$$= \left[\frac{1}{2\pi} \frac{(10^2 + 3^2 + 2^2) \cdot 2\pi}{2} \right]^{1/2} = \left(\frac{10^2 + 3^2 + 2^2}{2} \right)^{1/2} = \left(\frac{113}{2} \right)^{1/2}$$

$$= (56.5)^{1/2} = 7.52. \text{ (Ans.)}$$

Example 13. Four branches A, B, C, D in an A.C. circuit meet at a junction point P. The currents in branches A, B, C flow towards P while the current in branch D flows away from P. The currents in branches A, B and C are

$$i_A = 20 \sin 628t$$

$$i_B = 15 \sin (628t - \pi/6)$$

$$i_C = 25 \sin (628t + \pi/3)$$

Find an expression for the instantaneous value of current in branch D, and calculate (i) its frequency, and (ii) the heat (watts) that it would produce when flowing in a resistance of 5 ohms.

Solution.

Analytical method. Let the current flowing in the branch D be, $i_D = I_D \sin (628t + \phi)$

$$\begin{aligned} \Sigma H &= I_{A_{max}} \cos \phi_1 + I_{B_{max}} \cos \phi_2 + I_{C_{max}} \cos \phi_3 + I_{D_{max}} \cos \phi \\ &= 20 \cos 0^\circ + 15 \cos (-\pi/6) + 25 \cos \pi/3 + I_{D_{max}} \cos \phi \\ &= 20 + 15 \times \frac{\sqrt{3}}{2} + 25 \times \frac{1}{2} + I_{D_{max}} \cos \phi \\ &= 20 + 13 + 12.5 + I_{D_{max}} \cos \phi = 45.5 + I_{D_{max}} \cos \phi \\ \Sigma V &= I_{A_{max}} \sin \phi_1 + I_{B_{max}} \sin \phi_2 + I_{C_{max}} \sin \phi_3 + I_{D_{max}} \sin \phi \\ &= 20 \sin 0^\circ + 15 \sin (-\pi/6) + 25 \sin \pi/3 + I_{D_{max}} \sin \phi \\ &= 0 - 15 \times \frac{\sqrt{3}}{2} + 25 \times \frac{\sqrt{3}}{2} + I_{D_{max}} \sin \phi \\ &= -7.5 + 21.65 + I_{D_{max}} \sin \phi = 14.15 + I_{D_{max}} \sin \phi \end{aligned}$$

Since all the currents are meeting at point P,

$$\therefore \Sigma H = 0$$

$$i.e., \quad 45.5 + I_{D_{max}} \cos \phi = 0 \quad \text{or} \quad I_{D_{max}} \times \cos \phi = -45.5 \quad \dots(i)$$

$$\text{and} \quad \Sigma V = 0$$

$$i.e., \quad 14.15 + I_{D_{max}} \sin \phi = 0 \quad \text{or} \quad I_{D_{max}} \times \sin \phi = -14.15 \quad \dots(ii)$$

$$\text{From (i) and (ii), } I_{D_{max}} = (-45.5)^2 + (-14.15)^2 = 47.6 \text{ A.}$$

$$\phi = \tan^{-1} \frac{-14.15}{-45.5} = 197^\circ \text{ or } 3.44^\circ$$

Hence the current in branch D follows the relation,

$$i_D = 47.6 \sin (678t + 3.44). \text{ (Ans.)}$$

$$(i) \text{ Frequency} = \frac{\omega}{2\pi} = \frac{628}{2\pi} = 100 \text{ Hz. (Ans.)}$$

$$(ii) \text{ Heat produced} = \left(\frac{I_{D_{max}}}{\sqrt{2}} \right)^2 \times R = \left(\frac{47.6}{\sqrt{2}} \right)^2 \times 5 = 5620 \text{ W. (Ans.)}$$

4. SINGLE PHASE CIRCUITS

The study of circuits involves three basic types of units (R , L , C i.e., resistance, reactance and capacitance respectively) and four possible series combination of them. The latter, in turn, may be arranged in many kinds of parallel, series-parallel, parallel-series or other complex circuits.

4.1. A.C. Through Pure Ohmic Resistance Alone

The circuit containing a pure resistance R is shown in Fig. 23 (a). Let the applied voltage be given by the equation,

$$v = V_{\max} \sin \theta = V_{\max} \sin \omega t \quad \dots(i)$$

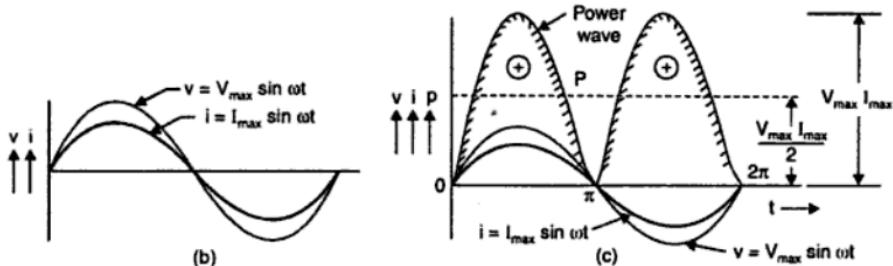
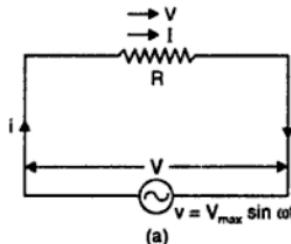


Fig. 23. A.C. through pure ohmic resistance alone.

Then the instantaneous value of current flowing through the resistance R will be,

$$i = \frac{v}{R} = \frac{V_{\max} \sin \omega t}{R} \quad \dots(ii)$$

The value of current will be maximum

when $\sin \omega t = 1$ or ($\omega t = 90^\circ$)

$$I_{\max} = \frac{V_{\max}}{R}$$

Substituting this value in eqn. (ii), we get

$$i = I_{\max} \sin \omega t \quad \dots(iii)$$

Comparing (i) and (iii), we find that alternating voltage and current are in phase with each other as shown in Fig. 23 (b), also shown vectorially in Fig. 23 (c).

Power. Refer Fig. 23 (c)

Instantaneous power,

$$\begin{aligned} p &= vi = V_{\max} \sin \omega t \times I_{\max} \sin \omega t = V_{\max} I_{\max} \sin^2 \omega t \\ &= \frac{V_{\max} I_{\max}}{2} \times 2 \sin^2 \omega t = \frac{V_{\max} I_{\max}}{2} (1 - \cos 2\omega t) \\ &= \frac{V_{\max}}{\sqrt{2}} \cdot \frac{I_{\max}}{\sqrt{2}} - \frac{V_{\max}}{\sqrt{2}} \cdot \frac{I_{\max}}{\sqrt{2}} \cos 2\omega t \\ &\text{(Constant part) (Fluctuating part)} \end{aligned}$$

For a complete cycle the average of $\frac{V_{\max}}{\sqrt{2}} \cdot \frac{I_{\max}}{\sqrt{2}} \cos 2\omega t$ is zero.

Hence, power for the whole cycle,

$$P = \frac{V_{\max}}{\sqrt{2}} \cdot \frac{I_{\max}}{\sqrt{2}} = V_{r.m.s.} \cdot I_{r.m.s.}$$

or

where V = R.M.S. value of applied voltage, and

I = R.M.S. value of the current.

It may be observed from the Fig. 23 (c) that no part of the power cycle at any time becomes negative. In other words the power in a purely resistive circuit *never becomes zero*.

Hence in **pure resistive circuit** we have :

1. Current is in phase with the voltage.

2. Current $I = \frac{V}{R}$ where I and V are r.m.s. values of current and voltage.

3. Power in the circuit, $P = VI = I^2R$.

4.2. A.C. Through Pure Inductance Alone

Fig. 24 (a) shows the circuit containing a pure inductance of L henry.

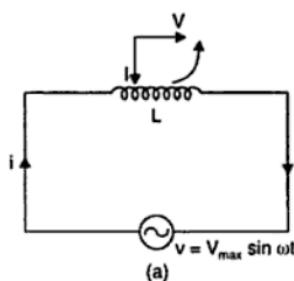


Fig. 24 (a)

Let the alternating voltage applied across the circuit be given by the equation,

$$v = V_{\max} \sin \omega t$$

...(i)

Whenever an alternating voltage is applied to a purely inductive coil, a back e.m.f. is produced due to the self-inductance of the coil. This back e.m.f. opposes the rise or fall of the current through the coil. Since there is no ohmic drop in this case, therefore, the applied voltage has to overcome this induced e.m.f. only. Thus at every step,

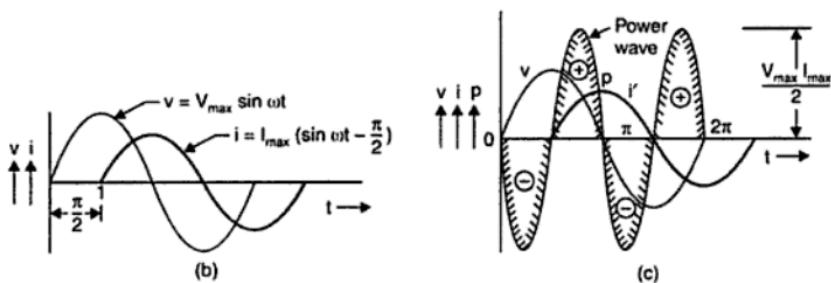


Fig. 24 (b), (c). A.C. through pure inductance alone. Resultant power zero.

$$v = L \frac{di}{dt}$$

or $V_{max} \sin \omega t = L \frac{di}{dt}$

or $di = \frac{V_{max}}{L} \sin \omega t dt$

Integrating both sides, we get

$$\int di = \int \frac{V_{max}}{L} \sin \omega t dt$$

or $i = \frac{V_{max}}{L} \left(-\frac{\cos \omega t}{\omega} \right) = \frac{V_{max}}{\omega L} \sin \left[\omega t - \frac{\pi}{2} \right]$

or $i = \frac{V_{max}}{X_L} \sin \left[\omega t - \frac{\pi}{2} \right] \quad \dots(ii)$

where $X_L = \omega L$ (opposition offered to the flow of alternating current by a pure inductance) and is called **Inductive reactance**. It is given in ohms if L is in henry and ω is in radian/second.

The value of current will be maximum when $\sin \left(\omega t - \frac{\pi}{2} \right) = 1$

$$\therefore I_{max} = \frac{V_{max}}{X_L}$$

Substituting this value in eqn. (ii), we get

$$i = I_{max} \sin \left(\omega t - \frac{\pi}{2} \right) \quad \dots(iii)$$

Power. Refer Fig. 24 (c)

$$\begin{aligned} \text{Instantaneous power, } p &= vi = V_{max} \sin \omega t \times I_{max} \sin \left(\omega t - \frac{\pi}{2} \right) \\ &= -V_{max} I_{max} \sin \omega t \cdot \cos \omega t \\ &= -\frac{V_{max} I_{max}}{2} \times 2 \sin \omega t \cos \omega t \\ &= -\frac{V_{max}}{\sqrt{2}} \cdot \frac{I_{max}}{\sqrt{2}} \cdot \sin 2\omega t \end{aligned}$$

$$\therefore \text{Power for the whole cycle, } P = -\frac{V_{max}}{\sqrt{2}} \frac{I_{max}}{\sqrt{2}} \int_0^{2\pi} \sin 2\omega t = 0$$

Hence *average power consumed in a pure inductive circuit is zero.*

Hence in a **pure inductive circuit**, we have :

$$1. \text{ Current } I = \frac{V}{X_L} = \frac{V}{\omega L} = \frac{V}{2\pi f L} \text{ amp.}$$

2. Current always lags behind the voltage by 90° .

3. Average power consumed is zero.

Variation of X_L and f :

Since $X_L = \omega L = 2\pi f L$, and here if L is constant, then

$$X_L \propto f$$

Fig. 25, shows the variation. As frequency is increased X_L increases and the current taken by the circuit decreases.

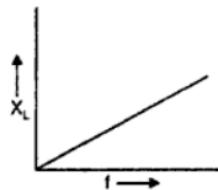


Fig. 25. Variation of X_L with f .

4.3. A.C. Through Pure Capacitance Alone

The circuit containing a pure capacitor of capacitance C farad is shown in Fig. 26 (a). Let the alternating voltage applied across the circuit be given by the equation,

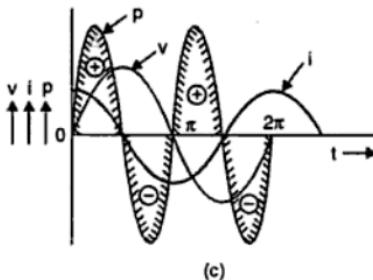
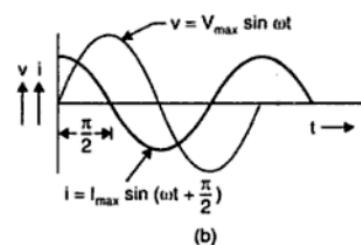
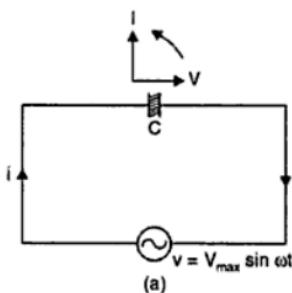


Fig. 26. A.C. through pure capacitance alone. Resultant power is zero.

$$v = V_{max} \sin \omega t$$

Charge on the capacitor at any instant,

$$q = C v$$

...(i)

Current through the circuit,

$$i = \frac{dq}{dt} = \frac{d}{dt} (CV_{max} \sin \omega t) = \omega CV_{max} \cos \omega t$$

or $i = \frac{V_{max}}{1/\omega C} \sin \left(\omega t + \frac{\pi}{2} \right)$

$$\therefore i = \frac{V_{max}}{X_C} \sin \left(\omega t + \frac{\pi}{2} \right) \quad \dots(ii)$$

The denominator $X_C = \frac{1}{\omega C}$ (opposition offered to the flow of alternating current by a pure capacitor) is known as *capacitive reactance*.

It is given in ohms if C is in farad and ω in radian/second.

The value of current will be maximum when $\sin \left(\omega t + \frac{\pi}{2} \right) = 1$

$$\therefore I_{max} = \frac{V_{max}}{X_C}$$

Substituting this value in eqn. (ii), we get

$$i = I_{max} \sin \left(\omega t + \frac{\pi}{2} \right) \quad \dots(iii)$$

Power. Refer Fig. 26 (c)

Instantaneous power,

$$\begin{aligned} p &= vi = V_{max} \sin \omega t \times I_{max} \sin \left(\omega t + \frac{\pi}{2} \right) \\ &= V_{max} I_{max} \sin \omega t \cos \omega t = \frac{V_{max}}{\sqrt{2}} \cdot \frac{I_{max}}{\sqrt{2}} \sin 2\omega t \end{aligned}$$

$$\text{Power for the whole cycle} = \frac{V_{max}}{\sqrt{2}} \cdot \frac{I_{max}}{\sqrt{2}} \int_0^{2\pi} \sin 2\omega t = 0$$

This fact is graphically illustrated in Fig. 26 (c). It may be noted that, during the first quarter cycle, what so ever power or energy is supplied by the source is stored in the electric field set-up between the capacitor plates. During the next quarter cycle, the electric field collapses and the power or energy stored in the field is returned to the source. The process is repeated in each alternation and this circuit does not absorb any power.

Hence in a *pure capacitive circuit*, we have

$$1. I = \frac{V}{X_C} = V \times 2\pi f C \text{ amps.}$$

2. Current always leads the applied voltage by 90° .

3. Power consumed is zero.

Variation of X_C and f :

Since $X_C = \frac{1}{2\pi f C}$ and if C is kept constant, then

$$X_C \propto \frac{1}{f}$$

Fig. 27. shows the variation. As the frequency increases X_C decreases, so the current increases.

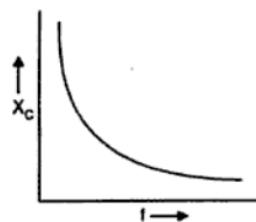


Fig. 27

4.4. Phasor Algebra

The following are the methods of representing vector quantities :

1. Symbolic notation 2. Trigonometrical form
3. Exponential form 4. Polar form.

A vector as shown in Fig. 28 may be described in the above forms as follows :

1. *Symbolic notation* :

$$E = a + jb$$

2. *Trigonometrical form* :

$$\begin{aligned} E &= \sqrt{a^2 + b^2} (\cos \theta + j \sin \theta) \\ &= \sqrt{a^2 + b^2} (\cos \theta \pm j \sin \theta) \end{aligned}$$

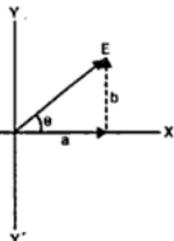


Fig. 28

.....in general

$$\begin{aligned} 3. \text{ *Exponential form*} : E &= \sqrt{a^2 + b^2} e^{j\theta} \\ &= \sqrt{a^2 + b^2} e^{\pm j\theta} \end{aligned}$$

.....in general

$$\begin{aligned} 4. \text{ *Polar form*} : E &= \sqrt{a^2 + b^2} \angle \theta \\ &= \sqrt{a^2 + b^2} \angle \pm \theta \end{aligned}$$

.....in general

Significance of operator j . The letter j used in the above expressions is a symbol of an operation. It is used to indicate the counter-clockwise rotation of a vector through 90° . It is assigned a value of $\sqrt{-1}$. The double operation of j on a vector rotates it counter-clockwise (CCW) through 180° and hence reverses its sense because, $j \times j = j^2 = \sqrt{(-1)^2} = -1$.

In general, each successive multiplication of j , rotates the phasor further by 90° as given below (Refer Fig. 29)

$$j = \sqrt{-1}$$

... 90° CCW rotation from OX -axis

$$j^2 = (\sqrt{-1})^2 = -1$$

... 180° CCW rotation from OX -axis

$$j^3 = (\sqrt{-1})^3 = -\sqrt{-1} = -j$$

... 270° CCW rotation from OX -axis

$$j^4 = (\sqrt{-1})^4 = +1$$

... 360° CCW rotation from X -axis

It should also be noted that,

$$\frac{1}{j} = \frac{j}{j^2} = \frac{j}{-1} = -j.$$

Example 14. Write the equivalent potential and polar forms of vector $6 + j8$. Also illustrate the vector by means of diagram.

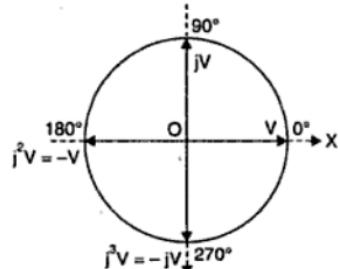


Fig. 29

Solution. Refer Fig. 30.

$$\text{Magnitude of the vector} = \sqrt{6^2 + 8^2} = 10, \tan \theta = \frac{8}{6}$$

$$\therefore \theta = \tan^{-1}\left(\frac{8}{6}\right) = 53.1^\circ$$

$$\therefore \text{Exponential form} = 10 e^{j53.1^\circ}. \quad (\text{Ans.})$$

The angle may also be expressed in radians.

$$\text{Polar form} = 10 \angle 53.1^\circ. \quad (\text{Ans.})$$

The vector is illustrated by means of diagram in Fig. 30.

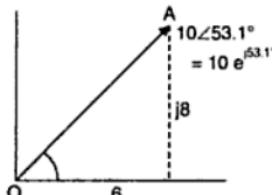


Fig. 30

Example 15. A vector is represented by $30e^{-j2\pi/3}$. Write down the various equivalent forms of the vector and illustrate by means of a vector diagram, the magnitude and position of the above vector.

Solution. Refer Fig. 31. Draw the vector in a direction

making an angle of $\frac{2\pi}{3} = \frac{2 \times 180}{3} = 120^\circ$ in the clockwise direction (since the angle is negative).

(i) **Rectangular form :**

$$a = 30 \cos(-120^\circ) = -15$$

$$b = 30 \sin(-120^\circ) = -25.98$$

$$\therefore \text{Expression is } = (-15 - j 25.98). \quad (\text{Ans.})$$

$$(ii) \text{Polar form} = 30 \angle -120^\circ. \quad (\text{Ans.})$$

Addition and subtraction of vector quantities :

For addition and subtraction of vector quantities rectangular form is best suited. Consider two voltage phasors represented as :

$$\bar{V}_1 = a_1 + jb_1 \text{ and } \bar{V}_2 = a_2 + jb_2$$

$$\text{Addition. } \bar{V} = \bar{V}_1 + \bar{V}_2 = (a_1 + jb_1) + (a_2 + jb_2) = (a_1 + a_2) + j(b_1 + b_2)$$

$$\text{The magnitude of the resultant vector } \bar{V} = \sqrt{(a_1 + a_2)^2 + (b_1 + b_2)^2}$$

$$\text{The position of } \bar{V} \text{ with respect to X-axis is } \theta = \tan^{-1}\left(\frac{b_1 + b_2}{a_1 + a_2}\right)$$

$$\text{Subtraction. } \bar{V} = \bar{V}_1 - \bar{V}_2 = (a_1 + jb_1) - (a_2 + jb_2) = (a_1 - a_2) + j(b_1 - b_2)$$

$$\text{The magnitude of the resultant vector } \bar{V} = \sqrt{(a_1 - a_2)^2 + (b_1 - b_2)^2}$$

$$\text{The position of } \bar{V} \text{ with respect to X-axis is } \theta = \tan^{-1}\left(\frac{b_1 - b_2}{a_1 - a_2}\right)$$

Multiplication and division of vector quantities :

If the vectors are represented in the polar exponential form, their multiplication and division becomes very easy and simple.

Consider two voltage phasors represented as

$$\bar{V}_1 = a_1 + jb_1 = V_1 \angle \theta_1, \text{ where } \theta_1 = \tan^{-1}\left(\frac{b_1}{a_1}\right)$$

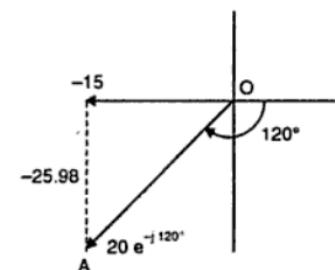


Fig. 31

$$\bar{V}_2 = a_2 + jb_2 = V_2 \angle \theta_2, \text{ where } \theta_2 = \tan^{-1} \left(\frac{b_2}{a_2} \right)$$

Multiplication. When the phasor quantities are represented in polar form, while multiplying their magnitudes are multiplied and their angles added algebraically,

i.e., $\bar{V}_1 \times \bar{V}_2 = V_1 \angle \theta_1 \times V_2 \angle \theta_2 = V_1 V_2 \angle (\theta_1 + \theta_2)$

Division. In this case, the magnitudes of phasor quantities (expressed in polar form) are divided and their angles subtracted algebraically

$$\text{i.e. } \frac{\bar{V}_1}{\bar{V}_2} = \frac{V_1 \angle \theta_1}{V_2 \angle \theta_2} = \frac{V_1}{V_2} \angle (\theta_1 - \theta_2).$$

Example 16. Perform the following operation and express the final result in polar form :

$$10 \angle 30^\circ + 16 \angle -30^\circ.$$

Solution. $10 \angle 30^\circ = 10 (\cos 30^\circ + j \sin 30^\circ) = 8.66 + j5$

$$16 \angle -30^\circ = 16 [\cos (-30^\circ) + j \sin (-30^\circ)] = 13.86 - j8$$

$$\therefore 10 \angle 30^\circ + 16 \angle -30^\circ = (8.66 + j5) + (13.86 - j8) = 22.52 - j3$$

$$= (\sqrt{22.52^2 + 3^2}) \tan^{-1} (-3/22.52)$$

$$= 22.72 \tan^{-1} (-3/22.52) = 22.72 \angle -7.6^\circ. \quad (\text{Ans.})$$

Example 17. Subtract the following given vectors from one another.

$$\bar{A} = 15 + j26 \text{ and } \bar{B} = -19.75 - j7.18.$$

Solution. $\bar{A} - \bar{B} = \bar{C} = (15 + j26) - (-19.75 - j7.18) = 34.75 + j33.18$

$$\therefore \text{Magnitude of } \bar{C} = \sqrt{34.75^2 + 33.18^2} = 48$$

$$\text{Slope of } \bar{C} = \tan^{-1} (33.18/34.75) = 43.68^\circ$$

$$\therefore \bar{C} = 48 \angle 43.68^\circ. \quad (\text{Ans.})$$

Example 18. Perform the operation $\frac{\bar{AB}}{\bar{C}}$ and express the final result in polar form for the vectors given below :

$$\bar{A} = 10 + j10; \bar{B} = 15 \angle -120^\circ; \bar{C} = 5 + j0.$$

Solution. Rearranging vectors \bar{A} and in polar form, we have

$$\bar{A} = 10 + j10 = \sqrt{10^2 + 10^2} \tan^{-1} (10/10) = 14.14 \angle 45^\circ$$

$$\bar{C} = 5 + j0 = \sqrt{5^2 + 0^2} \tan^{-1} (0/5) = 5 \angle 0^\circ$$

$$\therefore \frac{\bar{AB}}{\bar{C}} = \frac{14.14 \angle 45^\circ \times 15 \angle -120^\circ}{5 \angle 0^\circ} = \frac{14.14 \times 15}{5} \angle (45^\circ - 120^\circ - 0^\circ)$$

$$= 42.42 \angle -75^\circ. \quad (\text{Ans.})$$

Example 19. The instantaneous values of two currents i_1 and i_2 are given as :

$$i_1 = 5 \sin \left(\omega t + \frac{\pi}{4} \right) \text{ and } i_2 = 2.5 \cos \left(\omega t - \frac{\pi}{2} \right)$$

Find the r.m.s. value of $i_1 + i_2$ using complex number representation.

(Kerala University)

Solution. Given : $i_1 = 5 \sin \left(\omega t + \frac{\pi}{4} \right)$,

$$i_2 = 2.5 \cos \left(\omega t - \frac{\pi}{2} \right) = 2.5 \sin \left[90^\circ + \left(\omega t - \frac{\pi}{2} \right) \right] = 2.5 \sin \omega t$$

$$\therefore I_{1(\max)} = 5 (\cos 45^\circ + j \sin 45^\circ) = (3.53 + j3.53)$$

$$I_{2(\max)} = 2.5 (\cos 0^\circ + j \sin 0^\circ) = (2.5 + j0)$$

The maximum value of resultant current is

$$I_{\max} = (3.53 + j3.53) + (2.5 + j0) = 6.03 + j3.53 = 6.987 \angle 30.34^\circ$$

$$\therefore \text{R.M.S. value} = \frac{6.987}{\sqrt{2}} = 4.94 \text{ A. (Ans.)}$$

Conjugate complex numbers

Two numbers are said to be conjugate if they differ only in the algebraic sign of their quadrature components. Accordingly, the numbers $(a + jb)$ and $(a - jb)$ are conjugate.

- The sum of two conjugate numbers gives in-phase or active component and their difference gives quadrature or reactive component.

i.e. $(a + jb) + (a - jb) = 2a$ (i.e., active component), and
 $(a + jb) - (a - jb) = j2b$ (i.e., reactive component).

The resultant is the sum of two vertical components only.

- The resultant arising out of the multiplication of two conjugate numbers contains no quadrature component.

i.e., $(a + jb) \times (a - jb) = a^2 - j^2 b^2 = a^2 + b^2$

The conjugate of a complex number is used to determine the apparent power of an A.C. circuit in complex form.

Power and roots of vectors/phasors

The powers and roots of vectors can be found conveniently in polar form. If the vector are not in polar form, these should be converted into polar form before carrying out the algebraic operations, as mentioned below.

Powers. Consider a vector phasor quantity represented in polar form as $\bar{A} = A \angle \theta$,

Then $(\bar{A})^n = A^n \angle (n \times \theta)$

Example. Suppose it is required to find cube of the vector $4 \angle 12^\circ$

Then, $(4 \angle 12^\circ)^3 = (4)^3 \angle (3 \times 12^\circ) = 64 \angle 36^\circ$

Roots. Consider a vector (phasor) quantity represented in polar form as $(\bar{A})^{1/n} = (A)^{1/n} \angle \theta/n$.

Example. Suppose it is required to find cube root of $125 \angle 60^\circ$

Then, $(125 \angle 60^\circ)^{1/3} = (125)^{1/3} \angle 60^\circ/3 = 5 \angle 20^\circ$.

The 120° operator

In case of 3-phase work, where voltage vectors are displaced by 120° from one another (Fig. 32) it is convenient to use an operator, which rotates a vector/phasor through 120° toward or backwards without altering its length. This operator is 'a' and any operator which is multiplied by 'a' remains unaltered in magnitude but is rotated in CCW (counter-clockwise) direction by 120° .

∴

In cartesian form,

$$a = 1 \angle 120^\circ$$

$$a = \cos 120^\circ + j \sin 120^\circ$$

$$= -0.5 + j0.866$$

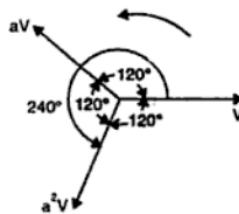


Fig. 32

Similarly, $a^2 = 1 \angle 120^\circ \times 1 \angle 120^\circ = 1 \angle 240^\circ = \cos 240^\circ + j \sin 240^\circ = -0.5 - j 0.866$

Hence the operator 'a' will rotate the in CCW by 240° which is the same as rotating the vector in CW(clock-wise) direction by 120° .

$$\therefore a^2 = 1 \angle -120^\circ$$

$$\text{Similarly } a^3 = 1 \angle 360^\circ = 1$$

(Numerically, a is equivalent to the cube root of unity.)

4.5. A.C. Series Circuits

Under this heading we shall discuss $R-L$, $R-C$ and $R-L-C$ series circuits.

4.5.1. R-L circuit (Resistance and inductance in series)

Fig. 33 (a) shows a pure resistance R and a pure inductive coil of inductance L connected in series. Such a circuit is known as $R-L$ circuit (usually met a cross in practice).

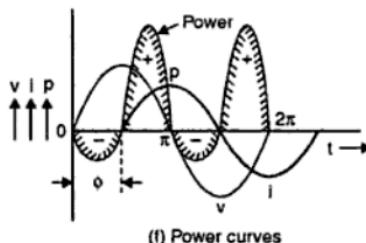
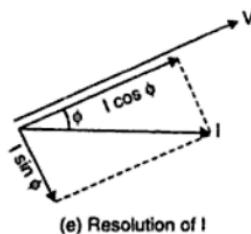
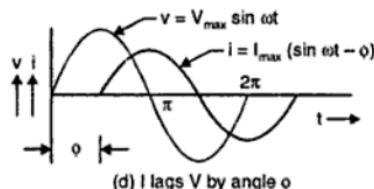
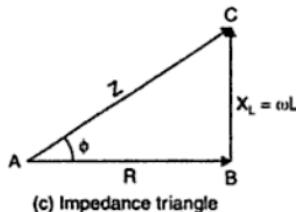
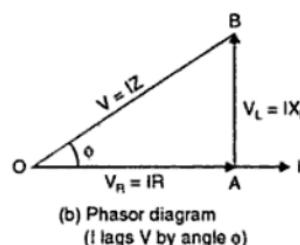
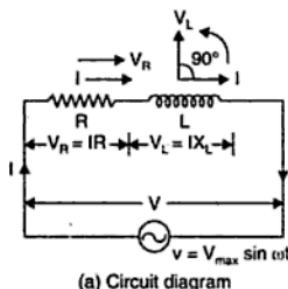


Fig. 33. $R-L$ circuit (Resistance and inductance in series).

Let V = R.M.S. value of the applied voltage,

I = R.M.S. value of the resultant current,

$V_R = IR$ = Voltage drop across R (*in phase with I*), and

$V_L = IX_L$ = Voltage drop across L (coil), *ahead of I by 90°*.

The voltage drop V_R and V_L are shown in voltage triangle OAB in Fig. 33 (b), I being taken as the reference vector in the phasor diagram. Vector OA represents ohmic drop V_R and AB represents inductive drop V_L . Vector OB represents the applied voltage V which is the vector sum of the two (i.e., V_R and V_L).

$$\therefore V = \sqrt{V_R^2 + V_L^2} = \sqrt{(IR)^2 + (IX_L)^2} = I\sqrt{(R^2 + X_L^2)}$$

or

$$I = \frac{V}{\sqrt{R^2 + (X_L)^2}} = \frac{V}{Z}$$

where $Z = \sqrt{R^2 + X_L^2}$ (total opposition offered to the flow of alternating current by $R-L$ series circuit) is known as **impedance** of the circuit.

As seen from the "impedance triangle" ABC [Fig. 33 (c)],

$$Z^2 = R^2 + X_L^2$$

i.e., (Impedance)² = (Resistance)² + (Inductive reactance)²

From Fig. 33 (b) it is evident that voltage V leads the current by an angle ϕ such that,

$$\tan \phi = \frac{V_L}{V_R} = \frac{IX_L}{IR} = \frac{X_L}{R} = \frac{\text{Inductive reactance}}{\text{Resistance}}$$

$$\therefore \phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$

The same is illustrated graphically in Fig. 33 (d).

In other words I lags V by an angle ϕ .

$$\text{Power factor, } \cos \phi = \frac{R}{Z} \quad [\text{From Fig. 33 (c)}]$$

Thus, if the applied voltage is given by $v = V_{\max} \sin \omega t$, then current equation is given as,

$$i = I_{\max} \sin(\omega t - \phi),$$

$$\text{where } I_{\max} = \frac{V_{\max}}{Z}$$

In the Fig. 33 (e), I has been shown resolved into two components, $I \cos \phi$ along V and $I \sin \phi$ in quadrature (i.e., perpendicular) with V .

Mean power consumed by the circuit

$$= V \times I \cos \phi \quad (\text{i.e., component of } I \text{ which is in phase with } V)$$

$$\text{i.e., } P = VI \cos \phi \quad (= \text{r.m.s. voltage} \times \text{r.m.s. current} \times \cos \phi)$$

The term ' $\cos \phi$ ' is called the **power factor** ($= \frac{R}{Z}$) of the circuit

It may be noted that :

— In A.C. circuit the product of r.m.s. volts and r.m.s. amperes gives volt-amperes (i.e., VA) and *not true power in watts*. True power (W) = volt-amperes (VA) \times power factor

$$\text{or} \quad \text{Watts} = \text{VA} \times \cos \phi$$

— The *power consumed is due to ohmic resistance only* since pure inductance consumes no power.

i.e.

$$P = VI \cos \phi = VI \times \frac{R}{Z} = \frac{V}{Z} IR = I \times IR = I^2 R, \text{ watts}$$

$$\therefore \cos \phi = R/Z \text{ and } \frac{V}{Z} = I$$

This shows that power is actually consumed in *resistance only*; the *inductor does not consume any power*.

The power consumed in *R-L circuit* is shown graphically in Fig. 33 (f).

Thus in *R-L circuit* we have :

1. Impedance, $Z = \sqrt{R^2 + X_L^2}$ (where $X_L = \omega L = 2\pi f L$)

2. Current, $I = \frac{V}{Z}$

3. Power factor, $\cos \phi = \frac{R}{Z} \left(= \frac{\text{True power}}{\text{Apparent power}} = \frac{W}{VA} \right)$

[or angle of lag, $\phi = \cos^{-1}(R/Z)$]

4. Power consumed, $P = VI \cos \phi \left(= IZ \times I \times \frac{R}{Z} = I^2 R \right)$

Symbolic Notation :

$$Z = R + j X_L$$

The numerical value of impedance vector $= \sqrt{R^2 + X_L^2}$

The phase angle with the reference axis, $\phi = \tan^{-1}(X_L/R)$.

In *polar form* : $\bar{Z} = Z \angle \phi^\circ$.

Apparent, Active (True or real) and Reactive Power :

Every circuit current has two components : (i) Active component and (ii) Reactive component.

"Active component" consumes power in the circuit while "reactive component" is responsible for the field which lags or leads the main current from the voltage.

In Fig. 34. active component is $I_{\text{active}} = I \cos \phi$, and reactive component is $I_{\text{reactive}} = I \sin \phi$

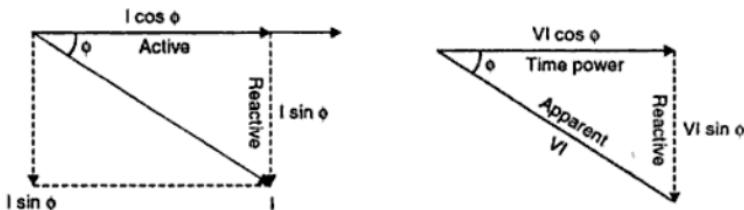


Fig. 34. Active and reactive components of circuit current I.

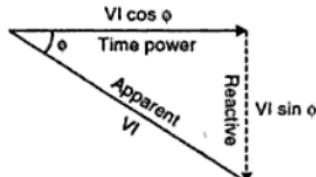


Fig. 35. Apparent, true and reactive power.

So,

$$I = \sqrt{(I_{\text{active}})^2 + (I_{\text{reactive}})^2}$$

Refer Fig. 35.

(i) **Apparent power (S).** It is given by the product of r.m.s. values of applied voltage and circuit current.

$$\therefore S = V I = (I \times Z) \cdot I = I^2 Z \text{ volt-amperes (VA)}$$

(ii) **Active or true or real power (P or W).** It is the power which is actually dissipated in the circuit resistance.

$$P = I^2 R = VI \cos \phi \text{ watts}$$

(iii) **Reactive power (Q).** A pure inductor and a pure capacitor do not consume any power, since in a half cycle what so ever power is received from the source by these components the same is returned to the source. This power which flows back and forth (i.e., in both directions in the circuit) or reacts upon itself is called "reactive power."

It may be noted that the current in phase with the voltage produces active or true or real power while the current 90° out of phase with the voltage contributes to reactive power.

In a R-L circuit, reactive power which is the power developed in the inductive reactance of the circuit, is given as :

$$\begin{aligned} Q &= I^2 X_L = I^2 Z \sin \phi = I \cdot (IZ) \sin \phi \\ &= VI \sin \phi \text{ volt-amperes-reactive (VAR)} \end{aligned}$$

These three powers are shown in Fig. 35

Relation between VA, W and VR

$$W = VA \cos \phi \quad \dots(i)$$

$$VAR = VA \sin \phi \quad \dots(ii)$$

$$\therefore VA = \frac{W}{\cos \phi} \quad \dots[\text{From (i)}]$$

$$\text{and, } VA = \frac{VAR}{\sin \phi} \quad \dots[\text{From (ii)}]$$

$$\text{Power factor (p.f.)} = \frac{W}{VA} = \frac{\text{True power}}{\text{Apparent power}}$$

The larger bigger units of apparent, true and reactive power are kVA (or MVA), kW (or MW) and kVAR (or MVAR) respectively.

The power factor depends on the reactive power component. If it is made equal to the active power component, the power factor becomes unity.

Example 20. A coil takes 2.5 amps. when connected across 200 volt 50 Hz mains. The power consumed by the coil is found to be 400 watts. Find the inductance and the power factor of the coil.

Solution. Current taken by the coil, $I = 2.5 \text{ A}$

Applied voltage, $V = 200 \text{ volts}$

Power consumed, $P = 400 \text{ W}$

We know that $P = VI \cos \phi$

$$\text{or } 400 = 200 \times 2.5 \times \cos \phi \text{ or } \cos \phi = \frac{400}{200 \times 2.5} = 0.8$$

Hence power factor of coil is 0.8. (Ans.)

$$\text{Impedance of the coil, } Z = \frac{V}{I} = \frac{200}{2.5} = 80 \Omega$$

$$\text{Also } \frac{X_L}{Z} = \sin \phi$$

$$\therefore X_L = Z \sin \phi$$

$$= 80 \sin \phi = 80 \sqrt{1 - \cos^2 \phi}$$

$$= 80 \sqrt{1 - 0.8^2} = 80 \times 0.6 = 48 \Omega$$

But

$$X_L = 2\pi f L$$

∴

$$L = \frac{X_L}{2\pi f} = \frac{48}{2\pi \times 50} = 0.1529 \text{ H (henry). (Ans.)}$$

Example 21. A 100 V, 80 W lamp is to be operated on 230 volts, 50 Hz A.C. supply. Calculate the inductance of the choke required to be connected in series with lamp for its operation. The lamp can be taken as equivalent to a non inductive resistance.

Solution. Current through the lamp when connected across 100 V supply,

$$I = \frac{W}{V} = \frac{80}{100} = 0.8 \text{ A}$$

$$\text{Resistance of the lamp, } R = \frac{V}{I} = \frac{100}{0.8} = 125 \Omega$$

If a choke of inductance L henry is connected in series with the lamp to operate it on 230 V, the current through the choke will also be 0.8 A.

The impedance of the circuit when choke is connected in series with the lamp,

$$Z = \frac{V}{I} = \frac{230}{0.8} = 287.5 \Omega$$

$$\text{Reactance of choke coil, } X_L = \sqrt{Z^2 - R^2} = \sqrt{287.5^2 - 125^2} = 258.5 \Omega$$

$$\text{But } X_L = 2\pi f L$$

$$\text{or } L = \frac{X_L}{2\pi f} = \frac{258.5}{2\pi \times 50} = 0.825 \text{ H}$$

Hence inductance of choke coil, $L = 0.825 \text{ H. (Ans.)}$

Example 22. A coil has a resistance of 5 Ω and an inductance of 31.8 mH. Calculate the current taken by the coil and power factor when connected to 200 V, 50 Hz supply.

Draw the vector diagram.

If a non-inductive resistance of 10 Ω is then connected in series with coil, calculate the new value of current and its power factor.

Solution.

$$R = 5 \Omega$$

$$L = 31.8 \text{ mH or } 0.0318 \text{ H}$$

∴

$$X_L = 2\pi f L$$

$$= 2\pi \times 50 \times 0.0318 = 10 \Omega$$

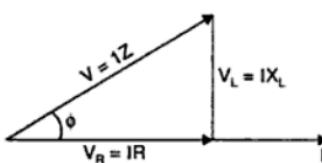
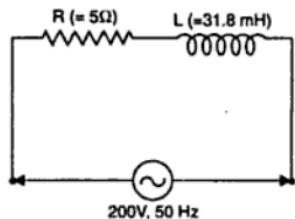


Fig. 36

Impedance of the coil.

$$Z = \sqrt{R^2 + X_L^2} \\ = \sqrt{5^2 + 10^2} = 11.18 \Omega$$

\therefore Current taken by the coil, $I = \frac{V}{Z} = \frac{200}{11.18} = 17.9 \text{ A. (Ans.)}$

Power factor, $\cos \phi = \frac{R}{Z} = \frac{5}{11.18} = 0.4475. \text{ (Ans.)}$

Fig. 36 (b) shows the vector diagram.

When non-inductive resistance of 10Ω is connected in series with the coil :

Total resistance in the circuit, $R' = 5 + 10 = 15 \Omega$

Reactance in the circuit, $X_L' = X_L = 10 \Omega$

Impedance of the circuit, $Z' = \sqrt{R'^2 + X_L'^2} = \sqrt{15^2 + 10^2} = 18 \Omega$

Current through the circuit, $I' = \frac{V}{Z'} = \frac{200}{18} = 11.11 \text{ A. (Ans.)}$

Power factor of the circuit, $\cos \phi = \frac{R'}{Z'} = \frac{15}{18} = 0.833. \text{ (Ans.)}$

Example 23. A current of 5A flows through a non-inductive resistance in series with a choking coil when supplied at 250V , 50Hz . If the voltage across the resistance is 125V and across the coil 200V , calculate :

(i) Impedance, reactance and resistance of the coil,

(ii) The power absorbed by the coil,

(iii) The total power.

Draw the vector diagram.

(Elect. Engg. Madras Univ.)

Solution. Non-inductive resistance connected in series with coil $= \frac{125}{5} = 25 \Omega$

Refer Fig. 37 (b).

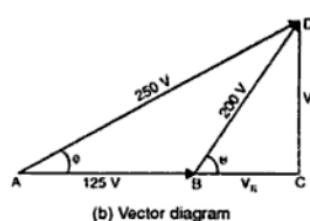
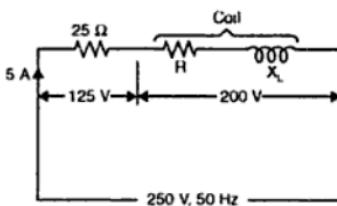


Fig. 37

$$BC^2 + CD^2 = (200)^2 = 40000 \quad \dots(i)$$

$$(125 + BC)^2 + CD^2 = (250)^2 = 62500 \quad \dots(ii)$$

Subtracting eqn. (i) from eqn. (ii), we get

$$(125 + BC)^2 - BC^2 = 62500 - 40000 = 22500$$

$$15625 + BC^2 + 250BC - BC^2 = 22500$$

$$\therefore BC = 27.5 \text{ V}; CD = \sqrt{(200)^2 - (27.5)^2} = 198.1 \text{ V}$$

(i) **Coil impedance,** $Z = \frac{200}{5} = 40 \Omega.$ (Ans.)

$$V_R = IR = BC = 27.5 \quad \text{or} \quad 5R = 27.5$$

$$R = \frac{27.5}{5} = 5.5 \Omega \quad (\text{Ans.})$$

Also, $V_L = IX_L = CD = 198.1$

$$\therefore X_L = \frac{198.1}{5} = 39.62 \Omega. \quad (\text{Ans.})$$

(ii) **Power absorbed by the coil,**

$$P = I^2 R = 5^2 \times 5.5 = 137.5 \text{ W.} \quad (\text{Ans.})$$

(iii) **The total power** $= VI \cos \phi = 250 \times 5 \times \frac{AC}{AD}$
 $= 250 \times 5 \times \frac{(125 + 27.5)}{250} = 762.5 \text{ W.} \quad (\text{Ans.})$

The vector diagram is shown in Fig. 37 (b). (Ans.)

Example 24. An iron-cored coil has a D.C. resistance of 6 ohms. When it is connected to 230 V, 50 Hz mains, the current taken is 3.5 A at a power factor of 0.5. Determine :

(i) Effective resistance of the coil.

(ii) Inductance of the coil.

(iii) Resistance which represents the effect of the iron loss.

Solution. Given : D.C. resistance (True resistance), $R = 6 \Omega$; supply voltage = 230 V, $f = 50 \text{ Hz}$, $I = 3.5 \text{ A}$; p.f. = 0.5.

(i) **Effective resistance of the coil, R_e :**

Total power consumed by the iron-cored choke coil,

$$P = \text{Power loss in ohmic resistance} + \text{Iron loss in core} = I^2 R + P_i$$

or $\frac{P}{I^2} = R + \frac{P_i}{I^2}$, where $\frac{P}{I^2}$ is known as effective resistance of the coil.

$$\therefore \text{Effective resistance, } R_e = \frac{P}{I^2} = \frac{VI \cos \phi}{I^2} = \frac{230 \times 3.5 \times 0.5}{(3.5)^2} = 32.86 \Omega. \quad (\text{Ans.})$$

(ii) **Inductance of the coil, L :**

$$\text{Impedance of the coil, } Z = \frac{V}{I} = \frac{230}{3.5} = 65.7 \Omega$$

Inductive reactance of the coil,

$$X_L = \sqrt{Z^2 - R_e^2} = \sqrt{(65.7)^2 - (32.86)^2} = 56.9 \Omega$$

$$\therefore L = \frac{X_L}{2\pi f} = \frac{56.9}{2\pi \times 50} = 0.1811 \text{ H.} \quad (\text{Ans.})$$

(iii) **Resistance representing iron loss :**

Since $\frac{P}{I^2} = R + \frac{P_i}{I^2}$

Effective resistance, R_e = True resistance + Resistance representing iron loss

$32.86 = 6 + \text{Resistance representing iron loss}$

$$\therefore \text{Resistance representing iron loss} = 32.86 - 6 = 26.86 \Omega. \quad (\text{Ans.})$$

Example 25. Three coils connected in series across a 100 V, 50 Hz supply have the following parameters :

$$R_1 = 18 \Omega, L_1 = 0.012 \text{ H}; R_2 = 12 \Omega, L_2 = 0.036 \text{ H}; R_3 = 3.6 \Omega, L_3 = 0.072 \text{ H}$$

Determine the potential drop and phase angle for each coil.

Solution. Fig. 38. shows the circuit diagram.

$$\text{Total resistance in the circuit, } R = R_1 + R_2 + R_3 = 18 + 12 + 3.6 = 33.6 \Omega$$

$$\text{Total inductance in the circuit, } L = L_1 + L_2 + L_3 = 0.012 + 0.036 + 0.072 = 0.12 \text{ H}$$

$$\text{Impedance of coil-1, } Z_1 = \sqrt{R_1^2 + (2\pi f L_1)^2} = \sqrt{(18)^2 + (2\pi \times 50 \times 0.012)^2} = 18.39 \Omega$$

$$\text{Impedance of coil-2, } Z_2 = \sqrt{R_2^2 + (2\pi f L_2)^2} = \sqrt{(12)^2 + (2\pi \times 50 \times 0.036)^2} = 16.49 \Omega$$

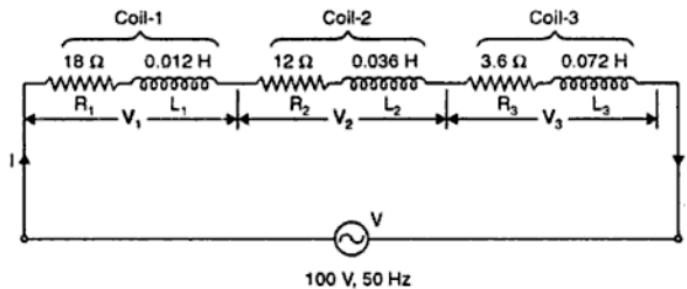


Fig. 38. Circuit diagram.

$$\text{Impedance of coil-3, } Z_3 = \sqrt{R_3^2 + (2\pi f L_3)^2} = \sqrt{(3.6)^2 + (2\pi \times 50 \times 0.072)^2} = 22.90 \Omega$$

$$\text{Impedance of the whole circuit, } Z = \sqrt{R^2 + (2\pi f L)^2} = \sqrt{(33.6)^2 + (2\pi \times 50 \times 0.12)^2} = 50.5 \Omega$$

$$\text{Current through the circuit, } I = \frac{V}{Z} = \frac{100}{50.5} = 1.98 \text{ A}$$

$$\text{Potential drop across coil-1, } V_1 = IZ_1 = 1.98 \times 18.39 = 36.41 \text{ V (Ans.)}$$

$$\text{Potential drop across coil-2, } V_2 = IZ_2 = 1.98 \times 16.49 = 32.65 \text{ V (Ans.)}$$

$$\text{Potential drop across coil-3, } V_3 = IZ_3 = 1.98 \times 22.90 = 45.34 \text{ V (Ans.)}$$

$$\text{Phase angle of coil-1, } \phi_1 = \cos^{-1}(R_1/Z_1) = \cos^{-1}(18/18.39) = 11.82^\circ. \text{ (Ans.)}$$

$$\text{Phase angle of coil-2, } \phi_2 = \cos^{-1}(R_2/Z_2) = \cos^{-1}(12/16.49) = 43.3^\circ. \text{ (Ans.)}$$

$$\text{Phase angle of coil-3, } \phi_3 = \cos^{-1}(R_3/Z_3) = \cos^{-1}(3.6/22.90) = 80.96^\circ. \text{ (Ans.)}$$

Example 26. An alternating voltage of $(176 + j132)$ is applied to a circuit and the current in the circuit is given by $(6.6 + j 8.8)$ A. Determine :

(i) Values of elements of the circuit.

(ii) Power factor of the circuit.

(iii) Power consumed.

Solution. Given : Supply voltage, $\bar{V} = 176 + j132 = 220 \angle 36.87^\circ$

$$\text{Circuit current, } \bar{I} = 6.6 + j 8.8 = 11 \angle 53.13^\circ$$

(i) Values of elements of the circuit, R, C :

$$\text{Circuit impedance, } \bar{Z} = \frac{\bar{V}}{\bar{I}} = \frac{220 \angle 36.87^\circ}{11 \angle 53.13^\circ} = 20 \angle -16.26^\circ \\ = 20 [\cos(-16.26^\circ) + j \sin(-16.26^\circ)] \\ = 20 (0.96 - j 0.28) = (19.2 - j 5.6) \Omega$$

$$\therefore R = 19.2 \Omega \quad (\text{Ans.})$$

$$X_C = 5.6 \Omega \text{ or } C = \frac{1}{2\pi f X_C} = \frac{1}{2\pi \times 50 \times 5.6} \text{ F} = 568.4 \mu\text{F.} \quad (\text{Ans.})$$

(ii) Power factor of the circuit ; $\cos \phi$:

$$\cos \phi = \frac{R}{Z} = \frac{19.2}{20} = 0.96 \text{ (leading).} \quad (\text{Ans.})$$

(iii) Power (true) consumed, P :

$$\begin{aligned} \text{Apparent power, } \bar{S} &= \bar{V} \times \bar{I} \\ &= 220 \angle 36.87^\circ \times 11 \angle -53.13^\circ = 2420 \angle -16.26^\circ \\ &= 2323.2 - j 677.6 \end{aligned}$$

$$\therefore \text{True power, } P = 2323.2 \text{ W.} \quad (\text{Ans.})$$

(Alternatively : $P = VI \cos \phi = 220 \times 11 \times 0.96 = 2323.2 \text{ W.}$)

Example 27. In a circuit, the equations for instantaneous voltage and current are given by,

$$v = 141.4 \sin \left(\omega t - \frac{2\pi}{3} \right), \text{ volt and}$$

$$i = 7.07 \sin \left(\omega t - \frac{\pi}{2} \right), \text{ amp, where } \omega = 314 \text{ rad/sec.}$$

(i) Sketch a neat phasor diagram for the circuit

(ii) Use polar notation to calculate impedance with phase angle.

(iii) Calculate average power.

(iv) Calculate the instantaneous power at the instant $t = 0$

(Pune University)

Solution. Given : $v = 141.4 \sin \left(\omega t - \frac{2\pi}{3} \right)$, and $i = 7.07 \sin \left(\omega t - \frac{\pi}{2} \right)$, where $\omega = 314 \text{ rad/s.}$

(i) **Phasor diagram :**

From the voltage equation, it is seen that the voltage lags behind the reference quantity by

$\frac{2\pi}{3}$ rad or $2 \times \frac{180}{3} = 120^\circ$. Similarly, current lags behind the reference quantity by $\frac{\pi}{2}$ rad or $\frac{180}{2} = 90^\circ$. Between themselves, voltage lags behind the current by $(120^\circ - 90^\circ) = 30^\circ$ as shown in Fig. 39 (b).

(ii) **Impedance with phase angle (polar notation)**

$$V = \frac{V_{\max}}{\sqrt{2}} = \frac{141.4}{\sqrt{2}} = 100 \text{ V;}$$

$$I = \frac{I_{\max}}{\sqrt{2}} = \frac{7.07}{\sqrt{2}} = 5 \text{ A.}$$

$$\therefore V = 100 \angle -120^\circ \text{ and } I = 5 \angle -90^\circ$$

$$\therefore Z = \frac{V}{I} = \frac{100 \angle -120^\circ}{5 \angle -90^\circ} = 20 \angle -30^\circ \Omega \quad (\text{Ans.})$$

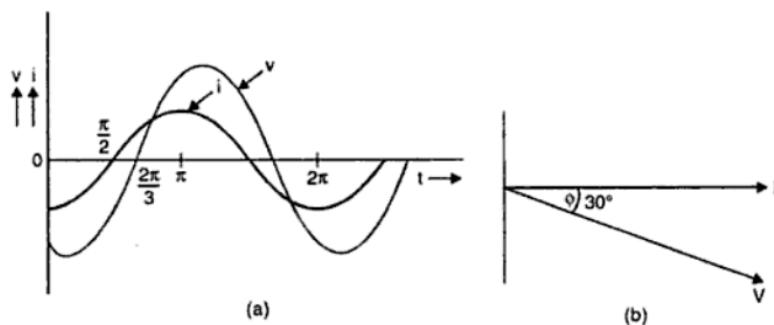


Fig. 39

(iii) Average power :

$$\begin{aligned} \text{Average power} &= VI \cos \phi \\ &= 100 \times 5 \times \cos 30^\circ = 433 \text{ W. (Ans.)} \end{aligned}$$

(iv) Instantaneous power at $t = 0$:

$$\begin{aligned} \text{At } t = 0; v &= 141.4 \sin(0 - 120^\circ) = -122.45 \text{ V} \\ i &= 7.07 \sin(0 - 90^\circ) = -7.07 \text{ A} \end{aligned}$$

$$\therefore \text{Instantaneous power at } t = 0,$$

$$p = v_i = (-122.45) \times (-7.07) = 865.7 \text{ W. (Ans.)}$$

Example 28. A voltage $v(t) = 100 \sin 314t$ is applied to a series circuit consisting of 10 ohms resistance, 0.0318 henry inductance and a capacitor of $63.6 \mu\text{F}$. Determine :

(i) Expression for $i(t)$.

(ii) Phase angle between voltage and current.

(iii) Power factor.

(iv) Active power consumed.

(v) Peak value of pulsating energy.

(Indore University)

Soution. Given : $v(t) = 100 \sin 314t$, $R = 10 \Omega$, $L = 0.0318 \text{ H}$, $C = 63.6 \mu\text{F} = 63.6 \times 10^{-6} \text{ F}$.

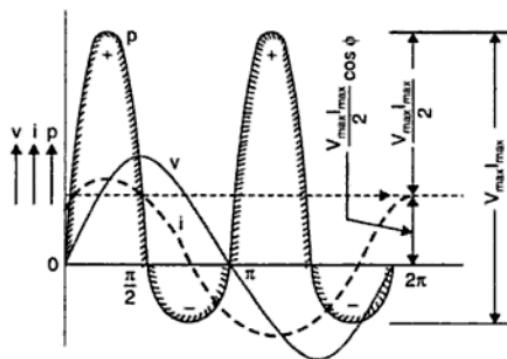


Fig. 40

Here $\omega = 314 \text{ rad/s}$; $X_L = \omega L = 314 \times 0.0318 = 10 \Omega$; $X_C = \frac{1}{\omega C} = \frac{1}{314 \times 63.6 \times 10^{-6}} = 50 \Omega$;

$$X = X_L - X_C = 10 - 50 = -40 \Omega \text{ (capacitive)}$$

$$\bar{Z} = 10 - j40 = 41.2 \angle -76^\circ; \bar{I} = \frac{\bar{V}}{\bar{Z}} = \frac{(100/\sqrt{2}) \angle 0^\circ}{41.2 \angle -76^\circ} = 1.716 \angle 76^\circ$$

$$I_{\max} = I \times \sqrt{2} = 1.716 \times \sqrt{2} = 2.43 \text{ A}$$

(i) Expression for $i(t)$:

$$i(t) = 2.43 \sin(314t + 76^\circ). \quad (\text{Ans.})$$

(ii) Phase angle between voltage and current, ϕ :

$$\phi = 76^\circ \text{ with current leading.}$$

(iii) Power factor, $\cos \phi$:

$$\cos \phi = \cos 76^\circ = 0.24 \text{ (lead).} \quad (\text{Ans.})$$

(iv) Active power consumed, P :

$$P = VI \cos \phi = (100/\sqrt{2})(2.43/\sqrt{2}) \times 0.24 = 29.16 \text{ W.} \quad (\text{Ans.})$$

(v) Peak value of pulsating energy:

Refer. Fig. 40. The peak value of pulsating energy

$$= \frac{V_{\max} I_{\max}}{2} + \frac{V_{\max} I_{\max}}{2} \cos \phi$$

$$= \frac{V_{\max} I_{\max}}{2} (1 + \cos \phi) = \frac{100 \times 2.43}{2} (1 + 0.24) = 150.66 \text{ W.} \quad (\text{Ans.})$$

4.5.2. R-C circuit (Resistance and capacitance in series)


Fig. 41. (a) shows a pure resistance R (ohms) and a pure capacitor of capacitance C (farads) connected in series. Such a circuit is known as $R-C$ circuit.

Let, V = R.M.S. value of the applied voltage,


I = R.M.S. value of the resultant current,

$V_R = IR$ = Voltage drop across R (in phase with I) and

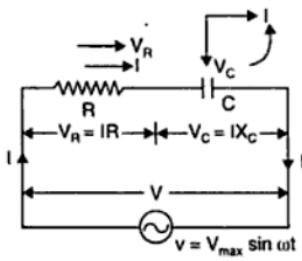
$V_C = IX_C$ = Voltage drop across C , lagging I by 90° .




(a) Circuit diagram

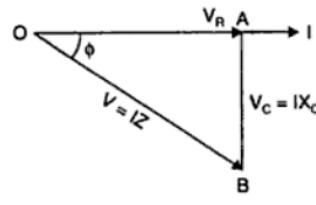

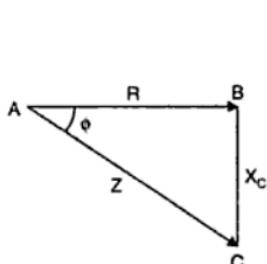(b) Phasor diagram
(I leads V by angle ϕ)



(c) Impedance triangle

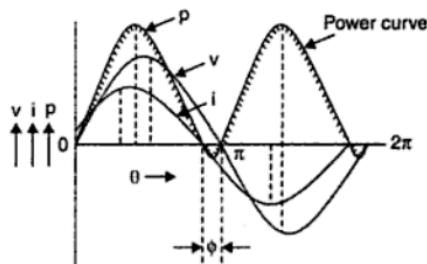

(d) Power curve

Fig. 41. *R-C* circuit (Resistance and capacitance in series).

Voltage drops V_R and V_L are shown in voltage triangle OAB in Fig. 41 (b) I being taken as the reference vector in the phasor diagram. Vector OA represents ohmic drop V_R and AB represents the capacitive drop V_C . Vector OB represents the applied voltage V , which is the vector sum of the V_R and V_C .

$$\therefore V = \sqrt{V_R^2 + V_C^2} = \sqrt{(IR)^2 + (IX_C)^2} = I \sqrt{R^2 + X_C^2}$$

$$\text{or} \quad I = \frac{V}{\sqrt{R^2 + X_C^2}} = \frac{V}{Z}$$

where $Z = \sqrt{R^2 + X_C^2}$ (total opposition offered to the flow of alternating current by $R-C$ series circuit) is known as the **impedance** of the circuit.

As seen from the "impedance triangle" ABC [Fig. 41 (c)],

$$Z^2 \equiv R^2 + X_0^{-2}$$

$$\text{i.e., } (\text{Impedance})^2 = (\text{Resistance})^2 + (\text{Capacitive reactance})^2$$

From Fig. 41 (b) it is evident that I leads the voltage V by an angle ϕ such that,

$$\tan \phi = \frac{V_C}{V_R} = \frac{IX_C}{IR} = \frac{X_C}{R} = \frac{(1/\omega C)}{R} = \frac{\text{Capacitive reactance}}{\text{Resistance}}$$

$$\phi = \tan^{-1} \left(\frac{X_C}{R} \right)$$

The same is illustrated graphically in Fig. 41 (d).

In other words I leads V_B by an angle ϕ .

$$\text{Power factor, } \cos \phi = \frac{R}{Z} \quad [\text{From Fig. 41 (c)}]$$

Power. Refer Fig. 41 (d).

$$\begin{aligned}\text{Instantaneous power, } p &= vi = V_{max} \sin \omega t \times I_{max} \sin (\omega t + \phi) \\&= \frac{V_{max} I_{max}}{2} \times 2 \sin(\omega t + \phi) \sin \omega t \\&= \frac{V_{max}}{\sqrt{2}} \times \frac{I_{max}}{\sqrt{2}} [\cos \phi - \cos(2\omega t + \phi)]\end{aligned}$$

Average power consumed in the circuit over a complete cycle,

$$P = \text{Average of } \frac{V_{max}}{\sqrt{2}} \cdot \frac{I_{max}}{\sqrt{2}} \cos \phi - \text{Average of } \frac{V_{max}}{\sqrt{2}} \cdot \frac{I_{max}}{\sqrt{2}} \cos (2\omega t + \phi)$$

or

$$P = \frac{V_{max}}{\sqrt{2}} \cdot \frac{I_{max}}{\sqrt{2}} \cos \phi - \text{zero.}$$

or

$$P = V_{r.m.s.} \times I_{r.m.s.} \cos \phi = VI \cos \phi$$

where $\cos \phi$ is the power factor of the circuit :

Alternatively, $P = VI \cos \phi = IZ \times I \times \frac{R}{Z} = I^2 R$

This shows that power is actually consumed in resistance only ; the capacitor does not consume any power.

Thus in **R-C circuit**, we have :

1. Impedance, $Z = \sqrt{R^2 + X_C^2}$ (where $X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$, C being in farad)

2. Current, $I = \frac{V}{Z}$

3. Power factor, $\cos \phi = \frac{R}{Z} \left(= \frac{\text{True power}}{\text{Apparent power}} = \frac{W}{VA} \right)$

[or angle of lead, $\phi = \cos^{-1}(R/Z)$]

4. Power consumed, $P = VI \cos \phi (= I^2 R)$.


Example 29. A capacitance of $20 \mu\text{F}$ and a resistance of 100 ohms are connected in series across $120 \text{ V}, 60 \text{ Hz}$ mains. Determine the average power expended in the circuit.

Also draw the vector diagram.


Solution.

$$R = 100 \Omega$$
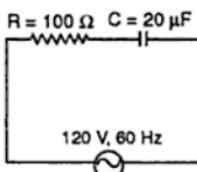
$$C = 20 \mu\text{F} = 20 \times 10^{-6} \text{ F (farad)}$$



(a) R-C circuit

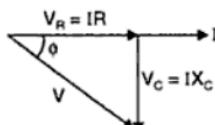

(b) Vector/phasor diagram

Fig. 42

Capacitive reactance, $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 20 \times 10^{-6}} = 159 \Omega$

Impedance of the circuit, $Z = \sqrt{R^2 + X_C^2} = \sqrt{100^2 + 150^2} = 188 \Omega$

Current through the circuit $I = \frac{V}{Z} = \frac{120}{188} = 0.638 \text{ A}$

Power factor, $\cos \phi = \frac{R}{Z} = \frac{100}{188} = 0.532$

Average power expended in the circuit,

$$\begin{aligned} P_{av} &= VI \cos \phi \\ &= 120 \times 0.638 \times 0.532 = 40.75 \text{ W. (Ans.)} \end{aligned}$$

Fig. 42 (b) shows the vector/phasor diagram.

Example 30. A voltage $v = 100 \sin 314t - 50 \cos 314t$, is applied to a circuit having $R = 20 \Omega$ in series with $C = 100 \mu F$. Obtain expression for instantaneous current, r.m.s. value of current and the power in the circuit. (PTU, 1999)

Solution. Given : $v = 100 \sin 314t - 50 \cos 314t$; $R = 20 \Omega$; $C = 100 \mu F$.

The R-C circuit and the phasor diagram for the given instantaneous voltage are shown in Figs. 43 and 44 respectively.

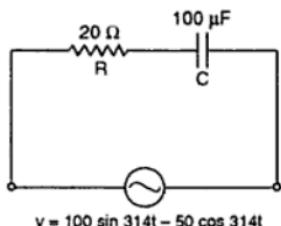


Fig. 43

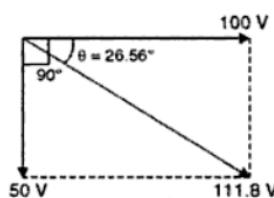


Fig. 44

Resultant voltage,

$$V_{max(R)} = \sqrt{(100)^2 + (50)^2} = 111.8 \text{ V}$$

Phase angle with the horizontal, $\theta = \tan^{-1} \left(-\frac{50}{100} \right) = -26.56^\circ$

$$\therefore v = 111.8 \sin(314t - 26.56^\circ)$$

Now, $\omega t = 314 t$ or $\omega = 314$

$$\therefore \text{Capacitive reactance, } X_C = \frac{1}{\omega C} = \frac{1}{314 \times 100 \times 10^{-6}} = 31.85 \Omega$$

$$\text{Circuit impedance, } Z = \sqrt{R^2 + X_C^2} = \sqrt{(20)^2 + (31.85)^2} = 37.6 \Omega$$

$$\text{Maximum value of current, } I_{max} = \frac{V_{max}}{Z} = \frac{111.8}{37.6} = 2.97 \text{ A}$$

Phase difference between voltage and current,

$$\phi = \cos^{-1} \left(\frac{R}{Z} \right) = \cos^{-1} \left(\frac{20}{37.6} \right) = 57.86^\circ \text{ (leading)}$$

∴ Instantaneous value of current

$$i = 2.97 \sin(314t - 26.56^\circ + 57.86^\circ) = 2.97 \sin(314t + 31.3^\circ)$$

$$i = 2.97 [\sin 314t \cdot \cos 31.3^\circ + \cos 314t \cdot \sin 31.3^\circ]$$

$$i = 2.54 \sin 314t + 1.54 \cos 314t. \quad (\text{Ans.})$$

$$\text{RMS value of the current, } I = \frac{I_{max}}{\sqrt{2}} = \frac{2.97}{\sqrt{2}} = 2.1 \text{ A.} \quad (\text{Ans.})$$

Power in the circuit, $P = VI \cos \phi$

$$= \frac{V_{max(R)}}{\sqrt{2}} \times I \cos \phi = \frac{111.8}{\sqrt{2}} \times 2.1 \times \cos(57.86^\circ) = 88.32 \text{ W (Ans.)}$$

Example 31. A two element series circuit is connected across an A.C. source $e = 200\sqrt{2} \sin(\omega t + 20^\circ)$ V. The current in the circuit then is found to be $i = 10\sqrt{2} \cos(314t - 25^\circ)$ A. Determine parameters of the circuit. (Allahabad University)

Solution. Given :

$$e = 200\sqrt{2} \sin(\omega t + 20^\circ)$$

$$i = 10\sqrt{2} \cos(314t - 25^\circ)$$

Parameters of the circuit, $\cos \phi$, R , X_C and C :

The current i can be written as,

$$i = 10\sqrt{2} \sin(314t - 25^\circ + 90^\circ) = 10\sqrt{2} \sin(314t + 65^\circ)$$

It is seen that applied voltage leads by 20° and current leads by 65° with regards to the reference quantity, their mutual difference is $65^\circ - 20^\circ = 45^\circ$.

Hence, p.f.

$$\cos \phi = \cos 45^\circ = 0.707 \text{ (lead). (Ans.)}$$

Now,

$$V_{max} = 200\sqrt{2} \text{ and } I_{max} = 10\sqrt{2}$$

∴

$$Z = \frac{V_{max}}{I_{max}} = \frac{200\sqrt{2}}{10\sqrt{2}} = 20 \Omega$$

∴

$$R = Z \cos \phi = 20 \times 0.707 = 14.14 \Omega. \text{ (Ans.)}$$

$$X_C = Z \sin \phi = 20 \times 0.707 = 14.14 \Omega. \text{ (Ans.)}$$

Also,

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C} = 14.14$$

where

$$f = \frac{314}{2\pi} = 50 \text{ Hz}$$

∴

$$X_C = 14.14 = \frac{1}{2\pi \times 50 \times C}$$




or

$$C = \frac{1}{14.14 \times 2\pi \times 50} F = 225.1 \mu\text{F}. \text{ (Ans.)}$$


Hence the given circuit is an R-C circuit.

4.5.3. R-L-C circuit (Resistance, inductance and capacitance in series)

Fig. 45 shows a R-L-C circuit.

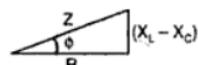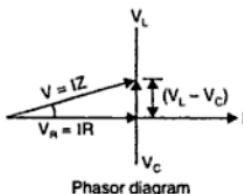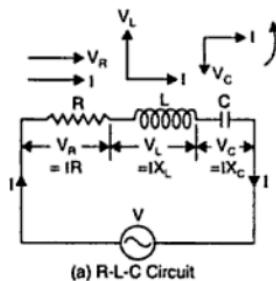

(b) $X_L > X_C$

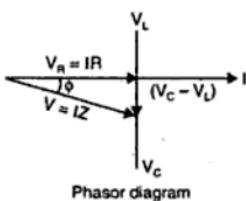

Impedance triangle

(c) $X_C > X_L$



Fig. 45. Resistance, inductance and capacitance in series.

Important formulae :

1. Impedance, $Z = \sqrt{R^2 + (X_L - X_C)^2}$

[where $X_L = 2\pi f L$, L in henry and $X_C = \frac{1}{2\pi f C}$, C in farad]

2. Current, $I = \frac{V}{Z}$

3. Power factor, $\cos \phi = \frac{R}{Z}$

[angle of lag (when $X_L > X_C$) or lead (when $X_C > X_L$), $\phi = \cos^{-1} \frac{R}{Z}$]

4. Power consumed $= VI \cos \phi (= I^2 R)$

Resonance in R-L-C circuits

Refer Fig. 45 (a).

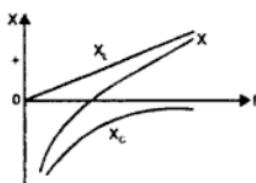


Fig. 46. Reactance (X) v/s frequency (f).

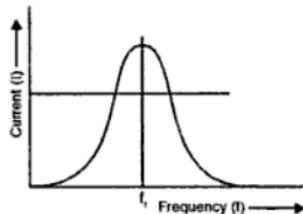


Fig. 47. Current in R-L-C circuit v/s frequency.

The frequency of the voltage which gives the maximum value of the current in the circuit is called **resonant frequency**, and the circuit is said to be **resonant**.

At resonance, $X_L = X_C$

(i.e., $Z = R$)

i.e., $2\pi f_r L = \frac{1}{2\pi f_r C}$

$$f_r = \frac{1}{2\pi\sqrt{LC}} \quad \dots(5)$$

where f_r = Resonance frequency in Hz ; L = Inductance in henry ; and C = Capacitance in farad.

Fig. 46 shows variation of X_L , X_C and X (total reactance = $X_L - X_C$) with variation of frequency f .

Fig. 47 shows the variation of current (I) with frequency (f).

At series resonance, it is seen that :

1. Net reactance of the circuit is zero i.e., $X_L - X_C = 0$ or $X = 0$.

2. The impedance of the circuit is *minimum* and equal to the resistance (R) of the circuit

(i.e., $I = \frac{V}{R}$). Consequently *circuit admittance is maximum*.

3. The current drawn is maximum (i.e., $I_r = I_{max}$).

4. The phase angle between the current and voltage is zero ; the *power factor is unity*.

5. The resonant frequency is given by $f_r = \frac{1}{2\pi\sqrt{LC}}$; if the frequency is below the resonant frequency the net reactance in the circuit is *capacitive* and if the frequency is above the resonant frequency, the net reactance in the circuit is *inductive*.

6. Although $V_L = V_C$, yet V_{coil} is greater than V_C because of its resistance.

Half power frequencies, Bandwidth and Selectivity

Half power (cut-off) frequencies :

The half power frequencies are those frequencies at which the power dissipation in the circuit is half of the power dissipation at resonant frequency f_r . They are the corresponding frequencies f_1 and f_2 at the value of current $I = I_r/\sqrt{2}$; where I_r is the current at resonance in $R-L-C$ series circuit (Refer Fig. 48).

Hence power, P_r , drawn by the circuit at the resonance is

$$P_r = I_r^2 R \quad \dots(6)$$

$$\text{Power in the circuit at } f_1 = \left(\frac{I_r}{\sqrt{2}}\right)^2 R = \frac{1}{2} I_r^2 R$$

$$\text{Power in the circuit at } f_2 = \left(\frac{I_r}{\sqrt{2}}\right)^2 R = \frac{1}{2} I_r^2 R$$

Also,

$$f_1 = f_r - \frac{R}{4\pi L}$$

$$f_2 = f_r + \frac{R}{4\pi L}$$

$$f_2 - f_1 = \frac{R}{2\pi L}$$

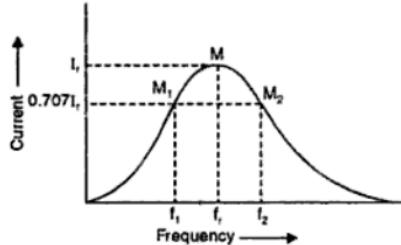


Fig. 48

(= half the power at resonance)

(= half the power at resonance)

Bandwidth and Selectivity :

The difference ($f_2 - f_1$) is called the *bandwidth* (B_{hp}) of the resonant network.

The ratio of the bandwidth to the resonant frequency is defined as the *selectivity* of the circuit.

When frequency is varied in $R-L-C$ circuit, the selectivity becomes

$$\frac{* (f_2 - f_1)}{f_r} = \frac{1}{Q} \quad \dots(7)$$

where Q_r is the *quality factor* of the resonant circuit.

*Relation between bandwidth and quality factor in series resonant conditions :

A series $R-L-C$ circuit is considered. The resonant frequency and angular frequency are expressed by f_r and ω_r respectively. In the above circuit, the current (I) can be described as follows :

$$I = \frac{V}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

where V , R , L and C are the source voltage, resistance, inductance and capacitance of the circuit respectively.

The current, at a power, half of the maximum power developed at resonant frequency, is $\frac{1}{\sqrt{2}} I_r$, where I_r is the series resonant current i.e. $\frac{V}{R}$.

According to the definition of bandwidth,

$$\frac{\frac{1}{\sqrt{2}} \frac{V}{R}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\text{or } \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2} = \sqrt{2}R \quad \text{or} \quad R^2 = \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\text{or } \omega L - \frac{1}{\omega C} = \pm R.$$

According to Fig. 48

$$\omega_2 L - \frac{1}{\omega_2 C} = R \quad \dots(i) \quad \omega_1 L - \frac{1}{\omega_1 C} = -R \quad \dots(ii)$$

Adding equations (i) and (ii), we get

$$(\omega_1 + \omega_2)L - \frac{1}{C} \left(\frac{1}{\omega_1} + \frac{1}{\omega_2} \right) = 0$$

$$\text{or } (\omega_1 + \omega_2)L - \frac{1}{C} \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right) = 0$$

$$\text{Since } \omega_1 + \omega_2 \neq 0, \omega_1 \omega_2 = \frac{1}{LC}.$$

Again $\omega_r^2 = \frac{1}{LC}$, [ω_r is the angular frequency at resonant condition.]

Subtracting equations (i) and (ii), we have

$$L(\omega_2 - \omega_1) + \frac{1}{C} \left(\frac{\omega_2 - \omega_1}{\omega_2 \omega_1} \right) = 2R$$

$$\text{or } (\omega_2 - \omega_1) + \frac{1}{LC} \frac{(\omega_2 - \omega_1)}{\omega_2 \omega_1} = \frac{2R}{L}$$

$$\text{or } (\omega_2 - \omega_1) + \omega_1 \omega_2 \cdot \frac{(\omega_2 - \omega_1)}{\omega_1 \omega_2} = \frac{2R}{L} \quad \left[\because \omega_1 \omega_2 = \frac{1}{LC} \right]$$

$$\text{or } (\omega_2 - \omega_1) = \frac{R}{L}$$

$$\text{or } \frac{\omega_2 - \omega_1}{\omega_0} = \frac{R}{\omega_0 L}$$

[ω_0 is the angular frequency at resonant condition]

$$\text{or } \omega_2 - \omega_1 = \omega_0 \times \frac{1}{\omega_0 L}$$

$$\text{or } \omega_2 - \omega_1 = \frac{\omega_0}{Q} \quad \left[\because Q = \frac{\omega_1 L}{R} \right]$$

or

$$f_2 - f_1 = \frac{f_r}{Q}$$

$$\therefore \omega = 2\pi f$$

or *Bandwidth at series resonant condition* = $\frac{f_r}{Q}$.

$$\left[Q = \frac{\omega_r}{\text{bandwidth}} = \frac{\omega_r}{\omega_2 - \omega_1} = \frac{\omega_r}{R/L} = \frac{\omega_r L}{R} = \frac{L}{R\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}} \right]$$

Q-factor of a resonant series circuit :

The Q-factor of an R-L-C series circuit can be defined in the following different ways :

(i) **Q-factor is defined as the voltage magnification in the circuit at the time of resonance.**

Since at resonance current is maximum i.e., $I_r = \frac{V}{R}$, the voltage across either coil or capacitor = $I_r X_{Lr}$ or $I_r X_{Cr}$ and supply voltage, $V = I_r R$.

$$\therefore \text{Voltage magnification} = \frac{V_{Lr}}{V} = \frac{I_r X_{Lr}}{I_r R} = \frac{X_{Lr}}{R} = \frac{\omega_r L}{R} = \frac{\text{Reactance}}{\text{Resistance}}$$

or $\frac{V_{Cr}}{V} = \frac{I_r \times C_r}{I_r R} = \frac{X_{Cr}}{R} = \frac{\text{Reactance}}{\text{Resistance}} = \frac{1}{\omega_r CR}$

$$\therefore \text{Q-factor} = \frac{\omega_r L}{R} = \frac{2\pi f_r L}{R} = \tan \theta \quad \dots [8(a)]$$

where θ is the circuit power factor angle of the coil.

(At resonance, circuit phase angle $\theta = 0$, and $Q = \tan \theta = 0$)

(ii) The Q-factor may also be defined as under :

$$\text{Q-factor} = 2\pi \frac{\text{maximum stored energy}}{\text{energy dissipated per cycle}} \quad \dots \text{in the circuit}$$

$$= 2\pi \frac{\frac{1}{2} L I_r^2}{I^2 R T_r} = 2\pi \frac{\frac{1}{2} L (\sqrt{2} I)^2}{I^2 R (1/f_r)} = \frac{I^2 \times 2\pi f_r L}{I^2 R} = \frac{\omega_r L}{R} \left(= \frac{1}{\omega_r CR} \right) \quad \left(\because T_r = \frac{1}{f_r} \right)$$

$$\text{But resonant frequency, } f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{or} \quad 2\pi f_r = \frac{1}{\sqrt{LC}}$$

Putting this value in eqn. 8(a), we get

$$\text{Q-factor} = \frac{2\pi f_r L}{R} = \frac{L}{R} \times \frac{1}{\sqrt{LC}} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \dots [8(b)]$$

In series resonance, higher quality factor i.e., Q-factor means higher voltage magnification as well as higher selectivity of the tuning coil.

Example 32. A resistance 12 Ω, an inductance of 0.15 H and a capacitance of 100 μF are connected in series across a 100 V, 50 Hz supply. Calculate :

(i) The current.

(ii) The phase difference between current and the supply voltage.

(iii) Power consumed.


Draw the vector diagram of supply voltage and the line current.

Solution. Given : $R = 12 \Omega$, $L = 0.15 \text{ H}$ or $X_L = 2\pi f L$


$$= 2\pi \times 50 \times 0.15 = 47.1 \Omega$$

$$C = 100 \mu\text{F} = 100 \times 10^{-6}\text{F}$$

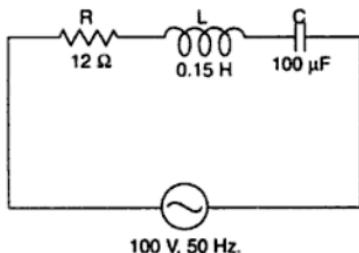or $X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.8 \Omega$



(a) R-L-C circuit

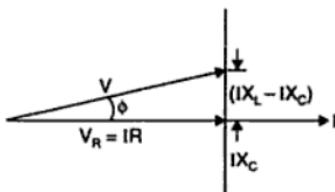

(b) Vector/phasor diagram

Fig. 49

$$(i) \text{The current, } I : \quad Z = \sqrt{R^2 + (X_L - X_C)^2} \\ = \sqrt{12^2 + (47.1 - 31.8)^2} = 19.43 \Omega$$

$$\text{Current, } I = \frac{V}{Z} = \frac{100}{19.43} = 5.15 \text{ A. (Ans.)}$$

(ii) Phase difference, ϕ :

$$\phi = \cos^{-1} \frac{R}{Z} \left[\text{or } \tan^{-1} \frac{X_L - X_C}{R} \right] \\ = \cos^{-1} \frac{12}{19.43} \left[\text{or } \tan^{-1} \frac{15.3}{12.0} \right] = 52^\circ \text{ (lag)}$$

Hence current lags supply voltage by 52° . (Ans.)

(iii) Power consumed, P :

$$P = VI \cos \phi \\ = 100 \times 5.15 \times \cos 52^\circ = 371.1 \text{ W. (Ans.)}$$


Fig. 49 (a), (b) show the circuit and vector/phasor diagrams respectively.

Example 33. For the circuit shown in Fig. 50 find the values of (i) current I, (ii) V_1 and V_2 and (iii) p.f.


Draw the vector diagram.

(Bangalore University)

Solution. Refer Fig. 50

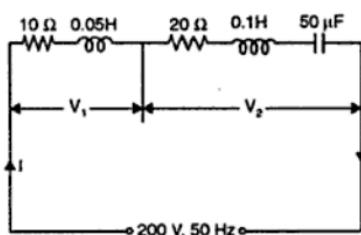

(a) Series circuit

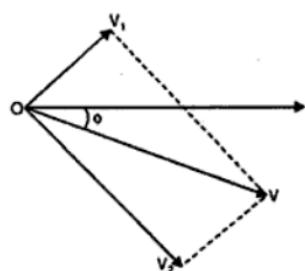

(b) Vector diagram

Fig. 50

$$R = 10 + 20 = 30 \Omega$$

$$L = 0.05 + 0.1 = 0.15 \text{ H}$$

$$\therefore X_L = 2\pi f L = 2\pi \times 50 \times 0.15 = 47.1 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 10^{-6} \times 50} = 63.7 \Omega$$

$$X = 47.1 - 63.7 = -16.6 \Omega$$

$$Z = \sqrt{R^2 + X^2} = \sqrt{(30)^2 + (-16.6)^2} = 34.3 \Omega$$

$$(i) I = \frac{V}{Z} = \frac{200}{34.3} = 5.83 \text{ A. (Ans.)}$$

$$(ii) X_{L1} = 2\pi \times 50 \times 0.05 = 15.7 \Omega$$

$$Z_1 = \sqrt{10^2 + 15.7^2} = 18.6 \Omega$$

$$\therefore V_1 = IZ_1 = 5.83 \times 18.6 = 108.4 \text{ V. (Ans.)}$$

$$\phi_1 = \cos^{-1}(10/18.6) = 57.5^\circ \text{ (lag)}$$

$$X_{L2} = 2\pi \times 50 \times 0.1 = 31.4 \Omega$$

$$X = 31.4 - 63.7 = -32.3 \Omega$$

$$Z_2 = \sqrt{20^2 + (-32.3)^2} = 38 \Omega$$

$$\therefore V_2 = IZ_2 = 5.83 \times 38 = 221.5 \text{ V. (Ans.)}$$

$$\phi_2 = \cos^{-1}(20/38) = 58.2^\circ \text{ (lead)}$$

$$(iii) \text{ Combined p.f. } = \cos \phi = \frac{R}{Z} = \frac{30}{34.3} = 0.875 \text{ (lead)}$$

Vector diagram is shown in Fig. 50 (b).

Example 34. For the circuit shown in Fig. 51. Calculate :

- (i) Current ; (ii) Voltage drops V_1 , V_2 and V_3 ;
- (iii) Power absorbed by each importance ; (iv) Total power absorbed by the circuit.

Take voltage vector along the reference axis.

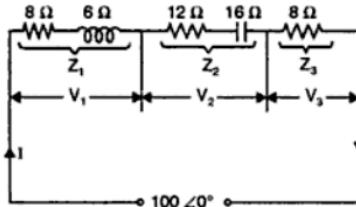


Fig. 51

(Pune University)

Solution.

$$Z_1 = (8 + j6) \Omega ; Z_2 = (12 - j16) \Omega ; Z_3 = (8 + j0)$$

$$Z = Z_1 + Z_2 + Z_3 = (8 + j6) + (12 - j16) + (8 + j0) = (28 - j10) \Omega$$

Taking

$$V = V \angle 0^\circ = 200 \angle 0^\circ = (200 + j0)$$

\therefore

$$I = \frac{V}{Z} = \frac{100}{(28 - j10)} = \frac{200(28 + j10)}{(28 - j10)(28 + j10)} = \frac{100(28 + j10)}{(28)^2 + (10)^2}$$

$$= \frac{200(28 + j10)}{884} = 3.17 + j1.13$$

$$(i) \text{ Magnitude of current } = \sqrt{(3.17)^2 + (1.13)^2} = 3.36 \text{ A. (Ans.)}$$

$$\begin{aligned} (ii) \quad V_1 &= IZ_1 = (3.17 + j1.13)(8 + j6) \\ &= 3.17 \times 8 + 3.17 \times j6 + 8 \times j1.13 + j1.13 \times j6 \\ &= 25.36 + j19.02 + j9.04 - 6.78 = 18.58 + j28.06. \text{ (Ans.)} \end{aligned}$$

$$\begin{aligned} V_2 &= IZ_2 = (3.17 + j1.13)(12 - j16) \\ &= 38.04 - j50.72 + j13.56 + 18.08 = 56.12 - j37.16. \text{ (Ans.)} \\ V_3 &= IZ_3 = (3.17 + j1.13)(8 + j0) = 25.36 + j9.04. \text{ (Ans.)} \\ [V &= V_1 + V_2 + V_3 = (18.58 + j28.06) + (56.12 - j37.16) \\ &\quad + (25.36 + j9.04) = 100 + j0 \text{ (check)}] \end{aligned}$$

Example 35. Fig. 52 shows a circuit connected to a 230 V, 50 Hz supply. Determine the following :

- (i) Current drawn
- (ii) Voltages V_1 and V_2
- (iii) Power factor.

Draw also the phasor diagram.

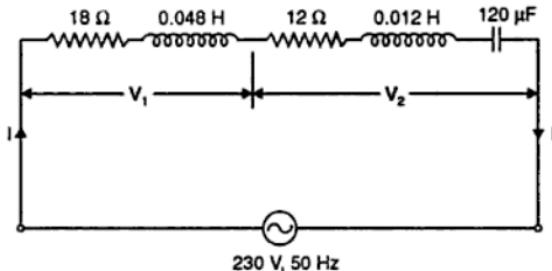


Fig. 52

(Pune University)

Solution. Refer Fig. 52.

$$\begin{aligned} \text{Given : } R_1 &= 18 \Omega, L_1 = 0.048 \text{ H} ; R_2 = 12 \Omega, L_2 = 0.012 \text{ H} ; C = 120 \mu\text{F} = 120 \times 10^{-6} \text{ F.} \\ \therefore X_{L1} &= 2\pi f L_1 = 2\pi \times 50 \times 0.048 = 15.08 \Omega ; X_{L2} = 2\pi f L_2 = 2\pi \times 50 \times 0.012 = 3.77 \Omega \end{aligned}$$

$$X_{C2} = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 120 \times 10^{-6}} = 26.53 \Omega$$

$$\text{Impedance, } \bar{Z}_1 = R_1 + jX_{L1} = 18 + j15.08 = 23.48 \angle 39.96^\circ$$

$$\text{Impedance, } \bar{Z}_2 = R_2 + jX_{L2} - jX_C = 12 + j3.77 - j26.53 = 12 - j22.76 = 25.73 \angle -62.2^\circ$$

$$\text{Total impedance, } \bar{Z} = \bar{Z}_1 + \bar{Z}_2 = (18 + j15.08) + (12 - j22.76) = 30 - j7.68 = 30.97 \angle -14.36^\circ$$

Current drawn, I :

Taking supply voltage as reference vector, $\bar{V} = V \angle 0^\circ = 230 \angle 0^\circ$.

$$\text{Current, } \bar{I} = \frac{\bar{V}}{Z} = \frac{230 \angle 0^\circ}{30.97 \angle -14.36^\circ} = 7.43 \angle 14.36^\circ \text{ A. (Ans.)}$$

Voltages V_1 and V_2 :

$$\begin{aligned}\text{Voltage, } \bar{V}_1 &= \bar{I}Z_1 = 7.43 \angle 14.36^\circ \times 23.48 \angle 39.96^\circ \\ &= 7.43 \times 23.48 \angle (14.36^\circ + 39.96^\circ) \\ &= 174.46 \angle 54.32^\circ \text{ V. (Ans.)}\end{aligned}$$

$$\begin{aligned}\text{Voltage } \bar{V}_2 &= \bar{I}Z_2 = 7.43 \angle 14.36^\circ \times 25.73 \angle -62.2^\circ \\ &= 7.43 \times 25.73 \angle (14.36^\circ - 62.2^\circ) \\ &= 191.2 \angle -47.84^\circ \text{ (Ans.)}\end{aligned}$$

Phase angle between supply voltage and current i.e., V and I , $\phi = 14.36^\circ$ (lead)

Power factor, cos ϕ :

$$\begin{aligned}\cos \phi &= \cos (14.36^\circ) \\ &= 0.9687 \text{ (leading). (Ans.)}\end{aligned}$$

$$\begin{aligned}[\bar{V} &= \bar{V}_1 + \bar{V}_2 = 174.46 \angle 54.32^\circ \\ &\quad + 191.2 \angle -47.84^\circ = 230 \angle 0^\circ \text{ (check)}]\end{aligned}$$

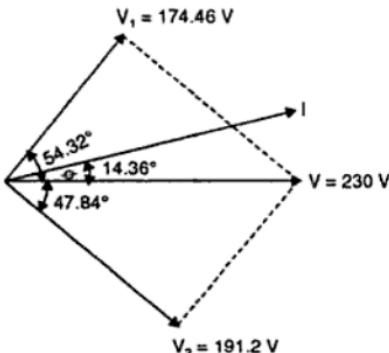


Fig. 53

Resonance, Q-Factor and Bandwidth

Example 36. A circuit consisting of a coil having an inductance of 0.25 H and a resistance of 3Ω is arranged in series with a capacitor of capacitance $20 \mu\text{F}$. Calculate at what frequency resonance will take place and current flow if an alternating voltage of 40 V at the resonant frequency is applied to the circuit. Find also the voltage across the capacitor.

$$\begin{aligned}\text{Solution. Resonant frequency, } f_r &= \frac{1}{2\pi\sqrt{LC}} \text{ [L in henry, C in farad]} \\ &= \frac{1}{2\pi\sqrt{0.25 \times 20 \times 10^{-6}}} = 71.2 \text{ Hz. (Ans.)}\end{aligned}$$

$$\text{At the resonant frequency, } I_r \text{ (or } I_{max}) = \frac{V}{R} = \frac{40}{3} = 13.33 \text{ A. (Ans.)}$$

$$\text{Voltage across the capacitor, } V_c = IX_c$$

$$\begin{aligned}&= \frac{13.33}{2\pi f C} \text{ (where C is in farad)} \\ &= \frac{13.33}{2\pi \times 71.2 \times 20 \times 10^{-6}} = 1489.8 \text{ V. (Ans.)}\end{aligned}$$

Example 37. A coil of inductance 0.64 H and resistance 40Ω is connected in series with a capacitor of capacitance $12 \mu\text{F}$.

Estimate :

- (i) The frequency at which resonance will occur.
- (ii) The voltage across the coil and capacitor, respectively and also the supply voltage when a current of 1.5 A at the resonant frequency is flowing.
- (iii) The three voltages in (ii) with a current of 1.5 A flowing at a frequency of 50 Hz .

$$\begin{aligned}\text{Solution. (i)} \quad f_r &= \frac{1}{2\pi\sqrt{LC}} \text{ [L is in henry, C is in farad]} \\ &= \frac{1}{2\pi\sqrt{0.64 \times 12 \times 10^{-6}}} = 57.4 \text{ Hz. (Ans.)}\end{aligned}$$

$$\begin{aligned}\text{(ii) At resonance the supply voltage } &= IR \\ &= 1.5 \times 40 = 60 \text{ V. (Ans.)}\end{aligned}$$

Voltage across the coil $= I\sqrt{R^2 + X_L^2}$
 $= 1.5 \sqrt{40^2 + (2\pi \times 57.4 \times 0.64)^2} = 351.4 \text{ V. (Ans.)}$

Voltage across the capacitor $= IX_C$
 $= I \times \frac{1}{2\pi f C}$ [C in μF]
 $= \frac{1.5}{2\pi \times 57.4 \times 12 \times 10^{-6}} = 346.6 \text{ V. (Ans.)}$

(iii) At 50 Hz :

Voltage across the coil $= I\sqrt{R^2 + X_L^2}$
 $= 1.5 \sqrt{40^2 + (2\pi \times 50 \times 0.64)^2} = 307.5 \text{ V. (Ans.)}$

Voltage across the capacitor $= IX_C$
 $= \frac{1.5}{2\pi \times 50 \times 12 \times 10^{-6}} = 398 \text{ V. (Ans.)}$

Voltage across the entire circuit,

$$\begin{aligned} V &= I\sqrt{R^2 + (X_L - X_C)^2} \\ &= 1.5 \sqrt{(40)^2 + \left\{ (2\pi \times 50 \times 0.64) - \left(\frac{1}{2\pi \times 50 \times 12 \times 10^{-6}} \right) \right\}^2} \\ &= 1.5 \sqrt{(40)^2 + (-64.2)^2} = 113.5 \text{ V. (Ans.)} \end{aligned}$$

Example 38. A coil having an inductance of 50 mH and resistance 10 Ω is connected in series with a 25 μF capacitor across a 200 V.A.C. supply. Calculate :

(i) Resonance frequency of the circuit ;

(ii) Current flowing at resonance ;

(iii) Value of Q by using different data.

(Bombay University)

Solution. (i) $f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{50 \times 10^{-3} \times 25 \times 10^{-6}}} = 142.3 \text{ Hz. (Ans.)}$

(ii) $I_{max} = \frac{V}{R} = \frac{200}{10} = 20 \text{ A. (Ans.)}$

(iii) $Q = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{10} \sqrt{\frac{50 \times 10^{-3}}{25 \times 10^{-6}}} = 4.47. \text{ (Ans.)}$

Example 39. A series R-L-C series circuit consists of $R = 800 \Omega$, $L = 80 \text{ mH}$ and $C = 8 \text{ pico-farad}$. The applied voltage across the circuit is 100 V. Determine :

(i) Resonant frequency of the circuit.

(ii) Q-factor of the circuit at the resonant frequency.

(iii) Bandwidth of the resonant circuit.

(iv) Frequencies at which the half power points occur.

(v) Bandwidth of the circuit.

(Delhi University)

Solution. Given : $R = 800 \Omega$; $L = 80 \text{ mH} = 0.08 \text{ H}$; $C = 8 \times 10^{-12} \text{ F}$; $V = 100 \text{ volts.}$

(i) Resonant frequency of the circuit, f_r :

$$f_r = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.08 \times 8 \times 10^{-12}}} = 198.94 \text{ kHz. (Ans.)}$$

(ii) Q-factor at the resonant frequency :

$$(Q\text{-factor})_{\text{resonant frequency}} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{800} \sqrt{\frac{0.08}{8 \times 10^{-12}}} = 125. \quad (\text{Ans.})$$

(iii) Bandwidth of the resonant circuit ; B_{hp} ;

$$B_{hp} = \frac{R}{2\pi L} = \frac{800}{2\pi \times 0.08} = 1591.5 \text{ Hz.} \quad (\text{Ans.})$$

Also, $B_{hp} = \frac{f_r}{Q} = \frac{198.94 \text{ kHz}}{125} = 1.5915 \text{ kHz} = 1591.5 \text{ Hz} \quad \dots \text{as above}$

(iv) Frequencies at which the half power points occur, ω_1, ω_2 :

$$f_1 = f_r - \frac{R}{4\pi L} = 198.94 \text{ (kHz)} - \frac{800}{4\pi \times 0.08} \times \frac{1}{1000} \text{ (kHz)} = 198.14 \text{ kHz.} \quad (\text{Ans.})$$

$$f_2 = f_r + \frac{R}{4\pi L} = 198.94 + \frac{800}{4\pi \times 0.08} \times \frac{1}{1000} \text{ (kHz)} = 199.74 \text{ kHz.} \quad (\text{Ans.})$$

(v) Bandwidth of the resonant circuit :

$$\text{Bandwidth} = f_2 - f_1 = 199.74 - 198.14 = 1.6 \text{ kHz.} \quad (\text{Ans.})$$

Example 40. A series R-L-C circuit consists of $R = 20 \Omega$, $L = 20 \text{ mH}$ and $C = 0.5 \mu\text{F}$. If the circuit is connected to a 20 V variable frequency supply calculate the following :

(i) Resonant frequency f_r .

(ii) Resonance circuit Q-factor using L/C ratio.

(iii) Half-power bandwidth, using f_r and Q-factor.

(iv) Half-power bandwidth using the general formula for any bandwidth.

(v) Half-power bandwidth using the given component values.

(vi) Maximum power dissipated at f_r .

(Delhi University)

Solution. Given : $R = 20 \Omega$; $L = 20 \text{ mH} = 0.02 \text{ H}$; $C = 0.5 \times 10^{-6} \text{ F}$; $V = 20 \text{ volts}$.

$$(i) \text{Resonant frequency, } f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{2\pi\sqrt{0.02 \times 0.5 \times 10^{-6}}} = 1591 \text{ Hz.} \quad (\text{Ans.})$$

$$(ii) \text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{20} \sqrt{\frac{0.02}{0.5 \times 10^{-6}}} = 10. \quad (\text{Ans.})$$

$$(iii) \text{Half-power bandwidth (using } \frac{L}{C} \text{ ratio), } B_{hp} = \frac{f_r}{\text{Q-factor}} = \frac{1591}{10} = 159.1 \text{ Hz.} \quad (\text{Ans.})$$

(iv) Half-power bandwidth (using the general formula),

$$B_{hp} = \frac{f_r Q}{(Q)_{\text{resonance}}} = \frac{1591 \times \tan 45^\circ}{10} = 159.1 \text{ Hz.} \quad (\text{Ans.})$$

(\because At half power points, $Q = \tan \theta = \tan 45^\circ = 1$)

(v) Half-power bandwidth (using component values),

$$B_{hp} = \frac{R}{2\pi L} = \frac{20}{2\pi \times 0.02} = 1591.5. \quad (\text{Ans.})$$

(vi) Maximum power dissipated at f_r ,

$$P_r = I_r^2 R = \left(\frac{V}{R}\right)^2 R = \frac{V^2}{R} = \frac{(20)^2}{20} = 20 \text{ W.} \quad (\text{Ans.})$$

4.6. A.C. Parallel Circuits

4.6.1. Introduction

Now-a-days, owing to multiple system of transmission and distribution, we come across parallel circuits (*i.e.*, impedances joined in parallel) more often. Practically all lighting and power circuits are constant voltage circuits with the loads connected in parallel. In a parallel A.C. circuit (like parallel D.C. circuit) the *voltage is the same across each branch*.


4.6.2. Methods for solving A.C. parallel circuits

The following *three* methods are available to solve such circuits :


1. Phasor or vector method
2. Admittance method
3. Vector algebra (symbolic method or *j*-method)

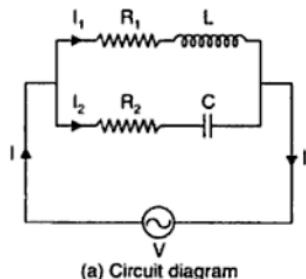1. Vector or phasor method :

Consider a parallel circuit consisting of two branches of impedances $Z_1(R_1, L)$ and $Z_2(R_2, C)$ respectively, and connected in parallel across an alternating voltage V volts (r.m.s.), as shown in Fig. 54 (a). Since the two branches are connected in parallel therefore, the voltage across each branch is the same and equal to supply voltage V but currents through them will be different.



(a) Circuit diagram

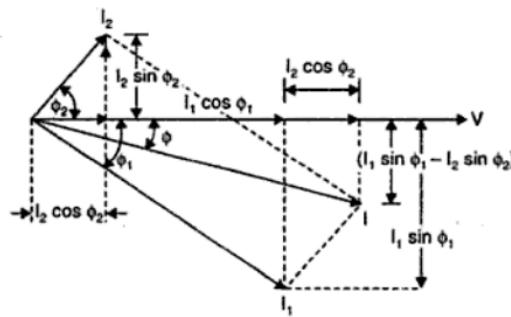

(b) Phasor diagram

Fig. 54. Single-phase parallel circuit—Phasor method.

Branch-1 Impedance, $Z_1 = \sqrt{R_1^2 + X_L^2}$

Current, $I_1 = \frac{V}{Z_1}$;

Power factor, $\cos \phi_1 = \frac{R_1}{Z_1}$ or $\phi_1 = \cos^{-1} \left(\frac{R_1}{Z_1} \right)$;

Current, I_1 lags behind the applied voltage by ϕ_1 .

Branch-2 Impedance, $Z_2 = \sqrt{R_2^2 + X_C^2}$;

Current, $I_2 = \frac{V}{Z_2}$;

Power factor, $\cos \phi_2 = \frac{R_2}{Z_2}$ or $\phi_2 = \cos^{-1} \left(\frac{R_2}{Z_2} \right)$

Current I_2 leads V by ϕ_2 [Fig. 54 (b)]

Resultant current I , which is phasor sum of I_1 and I_2 , can be determined either by using parallelogram law of phasors, as shown in Fig. 54 (b) or by resolving branch currents I_1 and I_2 along X-axis and Y-axis and then determining the resultant of these components analytically.

Component of resultant current I along X-axis

$$= \text{Sum of components of branch currents } I_1 \text{ and } I_2 \text{ along X-axis}$$

or

$$I \cos \phi = I_1 \cos \phi_1 + I_2 \cos \phi_2$$

Similarly, component of resultant current I along Y-axis

$$= \text{Sum of components of branch currents } I_1 \text{ and } I_2 \text{ along Y-axis}$$

or

$$I \sin \phi = -I_1 \sin \phi_1 + I_2 \sin \phi_2$$

$$\therefore I = \sqrt{(I_1 \cos \phi_1 + I_2 \cos \phi_2)^2 + (I_2 \sin \phi_2 - I_1 \sin \phi_1)^2} \quad \dots(9)$$

and

$$\tan \phi = \frac{I_2 \sin \phi_2 - I_1 \sin \phi_1}{I_1 \cos \phi_1 + I_2 \cos \phi_2} = \frac{\text{Y-component}}{\text{X-component}} \quad \dots[9(a)]$$

If $\tan \phi$ is +ve, then current I will lead the applied voltage V , if ϕ is -ve current I will lag behind the applied voltage V .

Power factor of the whole circuit is given by,

$$\cos \phi = \frac{I_1 \cos \phi_1 + I_2 \cos \phi_2}{I} = \frac{\text{X-component}}{I} \quad \dots[9(b)]$$

2. Admittance method :

Admittance (denoted by symbol Y) of a circuit is defined as the reciprocal of its impedance.

$$\therefore Y = \frac{1}{Z} = \frac{I}{V} \quad \text{or} \quad Y = \frac{\text{r.m.s. amperes}}{\text{r.m.s. volts}}$$

The unit of admittance is siemens (S). The old unit was mho (Ω).

As the impedance Z of a circuit has two components R and X (See Fig. 55), similarly, shown in Fig. 56, admittance Y also has two components G (conductance-X-component) and B (susceptance-Y-component).

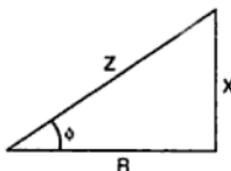


Fig. 55

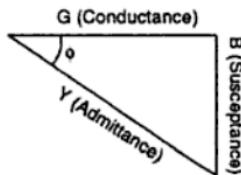


Fig. 56

Obviously,

$$G = Y \cos \phi = \frac{1}{Z} \cdot \frac{R}{Z} = \frac{R}{Z^2} = \frac{R}{R^2 + X^2}$$

Similarly,

$$B = Y \sin \phi = \frac{1}{Z} \cdot \frac{X}{Z} = \frac{X}{Z^2} = \frac{X}{R^2 + X^2}$$

$$\therefore \text{Admittance, } Y = \sqrt{G^2 + B^2} \text{ just as } Z = \sqrt{R^2 + X^2}$$

The units of G , B and Y are in Siemens. Here, we shall consider capacitive susceptance as +ve and inductive capacitance as -ve.

Application of admittance method in solution of single-phase parallel circuits :

Refer Fig. 57. Determine conductance and susceptance of individual branches from the relations

$$G = \frac{R}{Z^2} \text{ and } B = \frac{X}{Z^2}$$

Taking B as +ve if X is capacitive and as -ve if X is inductive. Let the conductances of the three branches of circuit shown in Fig. 57 be G_1, G_2 and G_3 respectively and susceptances be B_1, B_2 and B_3 respectively. Total conductance is found by merely adding the conductances of three branches. Similarly, total susceptance is found by algebraically adding the individual susceptances of different branches.

$$\therefore \text{Total conductance, } G = G_1 + G_2 + G_3$$

$$\text{and, total susceptance, } B = B_1 + B_2 + B_3$$

$$\therefore \text{Total admittance } Y = \sqrt{G^2 + B^2} \quad \dots(10)$$

$$\text{Total current, } I = VY \quad \dots(11)$$

$$\text{Power factor, } \cos \phi = \frac{G}{Y} \quad \dots(12)$$

3. Complex or Phasor algebra :

Consider the parallel circuit shown in Fig. 58 in which two impedances Z_1 and Z_2 , being in parallel, have the same potential difference across them

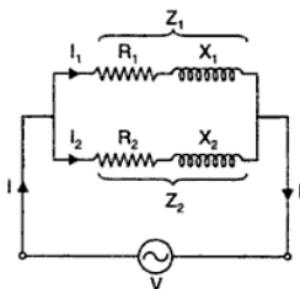


Fig. 58

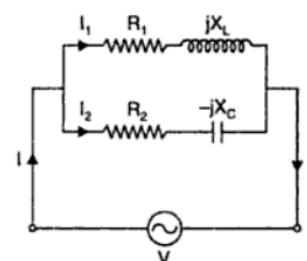


Fig. 59

Now,

$$\bar{I}_1 = \frac{\bar{V}}{Z_1} \text{ and } \bar{I}_2 = \frac{\bar{V}}{Z_2}$$

and current

$$\begin{aligned} \bar{I} &= \bar{I}_1 + \bar{I}_2 = \frac{\bar{V}}{Z_1} + \frac{\bar{V}}{Z_2} \\ &= \bar{V} \left(\frac{1}{Z_1} + \frac{1}{Z_2} \right) = \bar{V}(\bar{Y}_1 + \bar{Y}_2) = \bar{V}\bar{Y} \end{aligned} \quad \dots(13)$$

where \bar{Y} (= total admittance) = $\bar{Y}_1 + \bar{Y}_2$

It may be noted that the admittances are added in parallel branches, whereas impedances are added in series.

It is most important to remember that admittances and impedances being complex quantities must be added in complex form.

Let us now consider the two parallel branches shown in Fig. 59, we have

$$\begin{aligned}\bar{Y}_1 &= \frac{1}{Z_1} = \frac{1}{R_1 + jX_L} = \frac{R_1 - jX_L}{(R_1 + jX_L)(R_1 - jX_L)} \\ &= \frac{R_1 - jX_L}{R_1^2 + X_L^2} = \frac{R_1}{R_1^2 + X_L^2} - j \frac{X_L}{R_1^2 + X_L^2} = G_1 - jB_1\end{aligned}$$

where $G_1 = \frac{R_1}{R_1^2 + X_L^2}$... Conductance of upper branch,

$B_1 = -\frac{X_L}{R_1^2 + X_L^2}$... Susceptance of upper branch.

Similarly, $\bar{Y}_2 = \frac{1}{Z_2} = \frac{1}{R_2 - jX_C} = \frac{(R_2 + jX_C)}{(R_2 - jX_C)(R_2 + jX_C)}$

$$= \frac{R_2 + jX_C}{R_2^2 + X_C^2} = \frac{R_2}{R_2^2 + X_C^2} + j \frac{X_C}{R_2^2 + X_C^2} = G_2 + jB_2$$

Total admittance $\bar{Y} = \bar{Y}_1 + \bar{Y}_2 = (G - jB_1) + (G_2 + jB_2) = (G_1 + G_2) - j(B_1 - B_2) = G - jB$

$$\bar{Y} = \sqrt{(G_1 + G_2)^2 + (B_1 - B_2)^2} \quad \dots(15)$$

and $\phi = \tan^{-1} \left(\frac{B_1 - B_2}{G_1 + G_2} \right) \quad \dots(16)$

For admittance the polar form is :

$$\bar{Y} = Y \angle \phi^\circ, \text{ where } \phi \text{ is as given above}$$

$$Y = \sqrt{G^2 + B^2} \angle \tan^{-1} \left(\frac{B}{G} \right)$$

Total current $\bar{I} = \bar{V} \bar{Y} ; I_1 = \bar{V} \bar{Y}_1 \text{ and } I_2 = \bar{V} \bar{Y}_2$

If $\bar{V} = V \angle 0^\circ$ and $\bar{Y} = Y \angle \phi$ then $\bar{I} = \bar{V} \bar{Y} = V \angle 0^\circ \times Y \angle \phi = VY \angle \phi$

In general, i.e., $\bar{V} = V \angle \alpha$ and $\bar{Y} = Y \angle \beta$, then

$$\bar{I} = \bar{V} \bar{Y} = V \angle \alpha \times Y \angle \beta = VY \angle (\alpha + \beta) \quad \dots(17)$$

Thus, it is worth noting that when vector algebra is multiplied by admittance either in complex (rectangular) or polar form, the result is vector current in its proper phase relationship with respect to the voltage, irrespective of the axis to which the voltage may have been referred to.

Example 41. A resistance of 60Ω , an inductance of $0.18 H$ and a capacitance of $120 \mu F$ are connected in parallel across a $100 V$, $50 Hz$ supply. Calculate :

(i) Current in each path.

(ii) Resultant current.

(iii) Phase angle between the resultant current and the supply voltage.

(iv) Power factor of the circuit.

Solution. Given : $R = 60 \Omega$; $L = 0.18 \text{ H}$; $C = 120 \mu\text{F} = 120 \times 10^{-6} \text{ F}$, $V = 100 \text{ volts}, 50 \text{ Hz}$.

∴ Inductance reactance, $X_L = 2\pi fL = 2\pi \times 50 \times 0.18 = 56.55 \Omega$, and

$$\text{capacitance reactance, } X_C = \frac{1}{2\pi fC} = \frac{1}{2\pi \times 50 \times 120 \times 10^{-6}} = 26.53 \Omega$$

(i) Current in each path :

Current through reactance,

$$I_1 = \frac{V}{R} = \frac{100}{60} = 1.67 \text{ A in phase with voltage V. (Ans.)}$$

Current through inductance,

$$I_2 = \frac{V}{X_L} = \frac{100}{56.55} = 1.77 \text{ A lagging behind voltage V by } 90^\circ. \text{ (Ans.)}$$

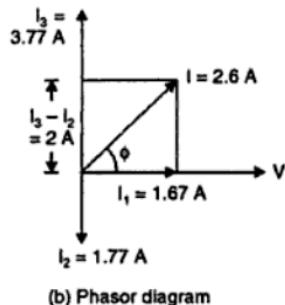
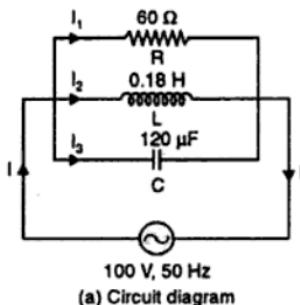


Fig. 60

Current through capacitance,

$$I_3 = \frac{V}{X_C} = \frac{100}{26.53} = 3.77 \text{ A leading the voltage V by } 90^\circ. \text{ (Ans.)}$$

The circuit and phasor diagrams are shown in Fig. 60 (a) and (b) respectively.

(ii) Resultant current, I :

$$\text{Resultant current, } I = \sqrt{(I_1)^2 + (I_3 - I_2)^2} = \sqrt{(1.67)^2 + (3.77 - 1.77)^2} = 6 \text{ A. (Ans.)}$$

(iii) Phase angle between the resultant current and the supply voltage, ϕ :


$$\phi = \tan^{-1} \left(\frac{I_3 - I_2}{I_1} \right) = \tan^{-1} \left(\frac{2}{1.67} \right) = 50.14^\circ \text{ (lead). (Ans.)}$$

(iv) Power factor of the circuit, $\cos \phi$:


$$\cos \phi = \cos 50.14^\circ = 0.641 \text{ (lead). (Ans.)}$$

Example 42. Determine the r.m.s. value of current in each branch and total current of the circuit shown in Fig. 61. Draw the phasor diagram. (PTU, Jan. 2000)

Solution. Refer Fig. 61 (a).

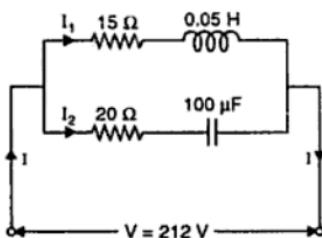

(a) Parallel circuit

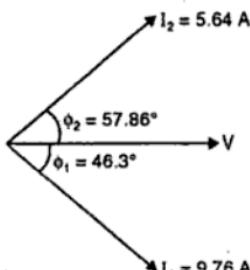

(b) Phasor diagram

Fig. 61

Branch No. 1 :

$$R_1 = 15 \Omega, X_1 = 2\pi f L = 2\pi \times 50 \times 0.05 = 15.7 \Omega$$

$$Z_1 = \sqrt{R_1^2 + X_1^2} = \sqrt{15^2 + 15.7^2} = 21.71 \Omega$$

$$I_1 = \frac{V}{Z_1} = \frac{212}{21.71} = 9.76 \text{ A}$$

$$\cos \phi_1 = \frac{R_1}{Z_1} = \frac{15}{21.71} = 0.691 \quad [\text{or } \phi_1 = \cos^{-1}(0.691) = 46.3^\circ \text{ (lagging)}]$$

$$\sin \phi_1 = \sin(46.3^\circ) = 0.723$$

Branch No. 2 :

$$R_2 = 20 \Omega, X_2 = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} = 31.83 \Omega$$

$$Z_2 = \sqrt{R_2^2 + X_2^2} = \sqrt{20^2 + 31.83^2} = 37.59 \Omega$$

$$I_2 = \frac{V}{Z_2} = \frac{212}{37.59} = 5.64 \text{ A}$$

$$\cos \phi_2 = \frac{R_2}{Z_2} = \frac{20}{37.59} = 0.532 \quad [\text{or } \phi_2 = \cos^{-1}(0.532) = 57.86^\circ \text{ (leading)}]$$

$$\sin \phi_2 = \sin(57.86^\circ) = 0.847$$

The phasor diagram is shown in Fig. 60 (b)

X-components of I_1 and I_2 are $I_1 \cos \phi_1 + I_2 \cos \phi_2$

$$= 9.76 \times 0.691 + 5.64 \times 0.532 = 9.74 \text{ A}$$

Y-components of I_1 and I_2 are $-I_1 \sin \phi_1 + I_2 \sin \phi_2$

$$= -9.76 \times 0.723 + 5.64 \times 0.847 = -2.28 \text{ A}$$

Total current, $I = \sqrt{(9.74)^2 + (2.28)^2} = 10 \text{ A. (Ans.)}$

Example 43. The currents in each branch of a two-branched parallel circuit are given by the expressions $i_A = 7.07 \sin(314t - \pi/4)$ and $i_B = 21.2 \sin(314t + \pi/3)$. The supply voltage is given by the expression $v = 354 \sin 314t$. Derive a similar expression for the supply current and calculate the ohmic value of the components, assuming two pure components in each branch. State whether the reactive components are inductive or capacitive.

(Elect. Engg. Calcutta University)

Solution. From the given expressions of currents, we find that :

- i_A lags the voltage by $\pi/4$ radian or 45° and i_B leads it by $\pi/3$ radian or 60° . Hence branch A consists of a resistance in series with a pure inductive reactance. Branch B consists of a resistance in series with a pure capacitive reactance as shown in Fig. 62

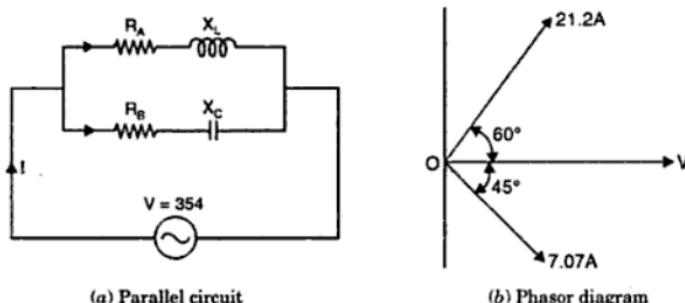


Fig. 62

- Maximum value of current in branch A is 7.07 A and in branch B is 21.2 A.

The resultant current can be found as follows :

As seen from the vector diagram [Fig. 62 (b)],

$$X\text{-component} = 21.2 \cos 60^\circ + 7.07 \cos 45^\circ = 15.6 \text{ A}$$

$$Y\text{-component} = 21.2 \sin 60^\circ - 7.07 \sin 45^\circ = 13.36 \text{ A}$$

Maximum value of the resultant current

$$= \sqrt{(15.6)^2 + (13.36)^2} = 20.54 \text{ A}$$

$$\phi = \tan^{-1}(13.36/15.6) = 40.6^\circ \text{ (lead)}$$

Hence the expression for the supply current is :

$$i = 20.54 \sin(314t + 40.6^\circ) \text{ (Ans.)}$$

$$Z_A = \frac{354}{7.07} = 50 \Omega; \cos \phi_A = \cos 45^\circ = 0.707, \sin \phi_A = \sin 45^\circ = 0.707$$

$$R_A = Z_A \cos \phi_A = 50 \times 0.707 = 35.4 \Omega$$

$$X_L = Z_A \sin \phi_A = 50 \times 0.707 = 35.4 \Omega.$$

$$Z_B = \frac{354}{21.2} = 16.7 \Omega. \text{ (Ans.)}$$


$$R_B = Z_B \cos 60^\circ = 16.7 \times \cos 60^\circ = 8.35 \Omega$$

$$X_B = Z_B \sin 60^\circ = 16.7 \times \sin 60^\circ = 14.46 \Omega. \text{ (Ans.)}$$

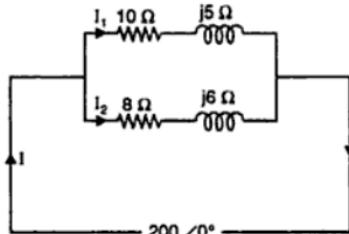
Example 44. Two impedances given by $Z_1 = (10 + j5)$ and $Z_2 = (8 + j6)$ are joined in parallel and connected across a voltage of $v = 200 + j0$. Calculate the circuit current, its phase and the branch currents. Draw the phasor diagram. (M.S. University Baroda)

Solution. Refer Fig. 63 (a).

$$\begin{aligned} \text{Branch A, } Y_1 &= \frac{1}{Z_1} = \frac{1}{(10 + j5)} \\ &= \frac{1}{(10 + j5)} \times \frac{10 - j5}{10 - j5} = \frac{10 - j5}{100 + 25} = \frac{10 - j5}{125} \\ &= (0.08 - j0.04) \text{ siemens} \end{aligned}$$



(a) Parallel circuit

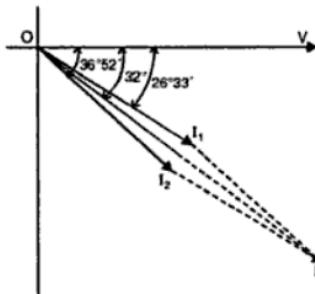

(b) Phasor diagram (not to scale)

Fig. 63

Branch B,

$$\begin{aligned} Y_2 &= \frac{1}{Z_2} = \frac{1}{(8 + j6)} \\ &= \frac{1}{(8 + j6)} \times \frac{(8 - j6)}{(8 - j6)} = \frac{8 - j6}{64 + 36} = \frac{8 - j6}{100} \\ &= (0.08 - j0.06) \text{ siemens} \\ Y &= Y_1 + Y_2 = (0.08 - j0.04) + (0.08 - j0.06) \\ &= (0.16 - j0.1) \text{ siemens} \end{aligned}$$

Alternatively :

$$\begin{aligned} \frac{1}{Z} &= \frac{1}{Z_1} + \frac{1}{Z_2} = \frac{Z_1 + Z_2}{Z_1 Z_2} \\ \therefore Y &= \frac{Z_1 + Z_2}{Z_1 Z_2} = \frac{(10 + j5) + (8 + j6)}{(10 + j5)(8 + j6)} = \frac{(18 + j11)}{50 + j100} \end{aligned}$$

Rationalising the above expression, we get

$$\begin{aligned} Y &= \frac{(18 + j11)(50 - j100)}{(50 + j100)(50 - j100)} = \frac{2000 - j1250}{12500} \\ &= 0.16 - j0.1 \text{ (same as before)} \end{aligned}$$

Now

$$V = 200\angle 0^\circ$$

 \therefore

$$I = VY = (200 + j0)(0.16 - j0.1)$$

$$= 32 - j20 = 37.74 \angle -32^\circ \dots \text{polar form. (Ans.)}$$

It lags behind the applied voltage by 32° .

Power factor

$$= \cos 32^\circ = 0.848. \text{ (Ans.)}$$

$$I_1 = VY_1 = (200 + j0)(0.08 - j0.04)$$

$$= 16 - j8 = 17.89 \angle -26^\circ 33'. \text{ (Ans.)}$$

It lags behind the applied voltage by $26^\circ 33'$.

$$I_2 = VY_2 = (200 + j0)(0.08 - j0.06)$$

$$= 16 - j12 = 20 \angle -36^\circ 52'$$

It lags behind the applied voltage by $36^\circ 52'$.

The phasor diagram is shown in Fig. 63 (b).

Example 45. Fig. 64 shows a parallel circuit in which the values of the parameters are as given below :

$R_1 = 70 \Omega$ (non-inductive) ; Coil : $R_C = 30 \Omega$, $L_C = 0.5 \text{ H}$; $R_2 = 100 \Omega$; $X_C = 157 \Omega$ (at 50 Hz).

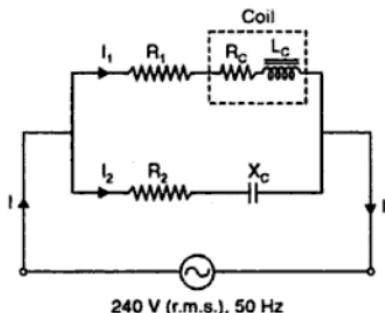


Fig. 64

- Determine the branch currents and the total current.
- Draw the phasor diagram indicating the currents and voltages across coil and condenser.
- If the A.C. source is replaced by an equivalent D.C. source, what current would be drawn by the circuit ?

Solution. Given : $R_1 = 70 \Omega$; $R_C = 30 \Omega$, $L_C = 0.5 \text{ H}$; $R_2 = 100 \Omega$; $X_C = 157 \Omega$.

Applied voltage = 240 V (r.m.s.), 50 Hz

(i) The branch currents (I_1 , I_2) and the total current (I) :

$$\text{Resistance of the inductive branch} = R_1 + R_C = 70 + 30 = 100 \Omega$$

$$\text{Reactance of the inductive branch} = 2\pi f L_C = 2\pi \times 50 \times 0.5 = 157 \Omega$$

Conductance of inductive branch,

$$G_1 = \frac{R_1 + R_C}{(R_1 + R_C)^2 + (2\pi f L_C)^2} = \frac{100}{(100)^2 + (157)^2} = 0.00288 \text{ S (siemens)}$$

Susceptance of inductive branch,

$$B_1 = \frac{2\pi f L_C}{(R_1 + R_C)^2 + (2\pi f L_C)^2}$$

$$= \frac{157}{(100)^2 + (157)^2} = -0.00453 \text{ S (Being inductive)}$$

Conductance of capacitive branch,

$$G_2 = \frac{R_2}{R_2^2 + X_C^2} = \frac{100}{(100)^2 + (157)^2} = 0.00288 \text{ S}$$

Susceptance of capacitive branch,

$$B_2 = \frac{X_C}{R_2^2 + X_C^2} = \frac{157}{(100)^2 + (157)^2} = 0.00453 \text{ S (Being capacitive)}$$

Total conductance of the circuit,

$$G = G_1 + G_2 = 0.00288 + 0.00288 = 0.00576 \text{ S}$$

Total susceptance of the circuit,

$$B = B_1 + B_2 = -0.00453 + 0.00453 = 0$$

Total admittance of the circuit,

$$Y = \sqrt{G^2 + B^2} = \sqrt{(0.00576)^2 + 0^2} = 0.00576 \text{ S}$$

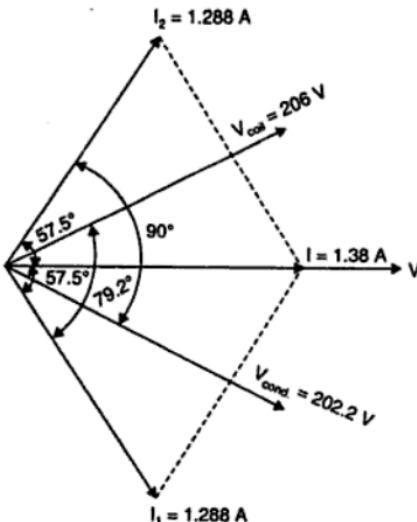


Fig. 65. Phasor diagram.

$$\begin{aligned}\text{Current in inductive branch, } I_1 &= V \times Y_1 = V \sqrt{G_1^2 + B_1^2} \\ &= 240 \sqrt{(0.00288)^2 + (-0.00453)^2} = 1.288 \text{ A. (Ans.)}\end{aligned}$$

$$\text{Phase angle, } \phi_1 = \tan^{-1} \left(\frac{B_1}{G_1} \right) = \tan^{-1} \left(\frac{-0.00453}{0.00288} \right) = -57.5^\circ. \quad (\text{Ans.})$$

$$\begin{aligned}\text{Current in capacitive branch, } I_2 &= V \times Y_2 = V \sqrt{G_2^2 + B_2^2} \\ &= 240 \sqrt{(0.00288)^2 + (0.00453)^2} = 1.288 \text{ A. (Ans.)}\end{aligned}$$

$$\text{Phase angle, } \phi_2 = \tan^{-1} \left(\frac{B_2}{G_2} \right) = \tan^{-1} \left(\frac{0.00453}{0.00288} \right) = 57.5^\circ. \quad (\text{Ans.})$$

$$\text{Total current, } I = V \times Y = 240 \times 0.00576 = 1.38 \text{ A. (Ans.)}$$

$$\text{Phase angle, } \phi = \tan^{-1} \left(\frac{B}{G} \right) = \tan^{-1} \left(\frac{0}{0.00576} \right) = 0^\circ$$

$$\text{Voltage across condenser} = I_2 X_C = 1.288 \times 157 = 202.2 \text{ V lagging behind } I_2 \text{ by } 90^\circ. \quad (\text{Ans.})$$

$$\text{Voltage across coil} = I_1 \times \sqrt{(R_C)^2 + (2\pi f L_C)^2} = 1.288 \sqrt{(30)^2 + (157)^2} = 206 \text{ V}$$

$$\text{Phase angle with current } I_1 = \tan^{-1} \left(\frac{157}{30} \right) = 79.2^\circ. \quad (\text{Ans.})$$

(ii) Phasor diagram :

The phasor diagram indicating the currents and voltages across coil and condenser is shown in Fig. 65.

(iii) Current drawn by the circuit when D.C. source is used :

When energised by equivalent D.C. source (i.e., 240 V D.C.), the capacitive branch will be open and current drawn by the circuit

= Current drawn by inductive branch

$$= \frac{V}{R_L + R_C} = \frac{240}{70 + 30} = 2.4 \text{ A. (Ans.)}$$

Example 46. Fig. 66 shows two impedances $(18 + j24)$ and $(15 - j30)$ Ω connected in parallel; across the combination is applied a voltage of $200\angle 53^\circ 8'$. Determine :

(i) kVA, kVAR and kW in each branch.

(ii) The power factor of the whole circuit.

Solution. Refer Fig. 66

$$\begin{aligned}\bar{Y}_1 &= \frac{1}{18 + j24} = \frac{18 - j24}{(18 + j24)(18 - j24)} \\ &= \frac{18 - j24}{900} = (0.02 - j0.0266) \text{ S}\end{aligned}$$

$$\begin{aligned}\bar{Y}_2 &= \frac{1}{15 - j30} = \frac{15 + j30}{(15 + j30)(15 - j30)} = \frac{15 + j30}{1125} \\ &= (0.0133 + j0.0266) \text{ S}\end{aligned}$$

$$\text{Now, } V = 200\angle 53^\circ 8' = 200(\cos 53^\circ 8' + j \sin 53^\circ 8') \\ = 200(0.6 + j0.8) = (120 + j160) \text{ volts}$$

$$\begin{aligned}\bar{I}_1 &= \bar{V} \bar{Y}_1 = (120 + j160)(0.02 - j0.0266) \\ &= 2.4 + j3.2 - j3.2 + 4.26 = (6.66 + j0)\end{aligned}$$

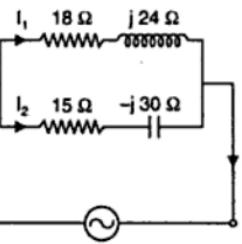


Fig. 66

... (along the reference axis)

$$\therefore I_1 = \bar{V} \bar{Y}_1 = (120 + j160)(0.0133 + j0.0266)$$

$$= 1.6 + j3.2 + j2.13 - 4.26 = -2.66 + j5.33 \text{ (leading)}$$

(i) kVA, kVAR and kW in each branch :

Power calculations can be calculated by the method of conjugates.

Branch 1 (Inductive branch)

The current conjugate of $(6.66 + j0)$ is $(6.66 - j0)$

$$\therefore \bar{V} \bar{I}_1 = (120 + j160)(6.66 - j0) = 800 + j1066 \quad \therefore \text{kW} = \frac{800}{1000} = 0.8. \text{ (Ans.)}$$

$$\therefore \text{kVAR} = \frac{1066}{1000} = 1.066. \text{ (Ans.)}$$

The fact that it is positive merely shows that reactive VA (volt-amps) are due to lagging current

$$\text{kVA} = \sqrt{(\text{kW})^2 + (\text{kVAR})^2} = \sqrt{(0.8)^2 + (1.066)^2} = 1.33. \text{ (Ans.)}$$

Branch 2 (Capacitive branch) :

The current conjugate of $(-2.66 + j5.33)$ is $(-2.66 - j5.33)$

$$\therefore \bar{V} \bar{I}_2 = (120 + j160)(-2.66 - j5.33) = 533.6 - j1065.2$$

$$\therefore \text{kW} = \frac{533.6}{1000} = 0.5336. \text{ (Ans.)} ; \text{ kVAR} = \frac{-1065.2}{1000} = -1.065. \text{ (Ans.)}$$

The negative sign merely indicates the reactive volt-amps are due to leading current.

$$\therefore \text{kVA} = \sqrt{(0.5336)^2 + (-1.065)^2} = 1.191. \quad (\text{Ans.})$$

(ii) The power factor of the whole circuit, $\cos \phi$:

$$\bar{Y} = \bar{Y}_1 + \bar{Y}_2 = (0.02 - j0.0266) + (0.0133 + j0.0266) = 0.0333 + j0$$

$$\bar{I} = \bar{V} \bar{Y} = (120 + j160)(0.0333 + j0) = 4 - j5.33 = 6.66 \angle 53^\circ 8'$$

or

$$\bar{I} = \bar{I}_1 + \bar{I}_2 = (6.66 + j0) + (-2.66 + j5.33) = 4 - j5.33 \quad (\text{Same as above})$$

Power factor of the circuit, $\cos \phi = \cos 0^\circ = 1$. (Ans.)

(\because Current is in phase with voltage)

Example 47. For the circuit of Fig. 67, calculate the current supplied by the voltage source and the voltage across the current source. (PTU June 2000; May 2001)

Solution. Refer Figs. 67 and 68.

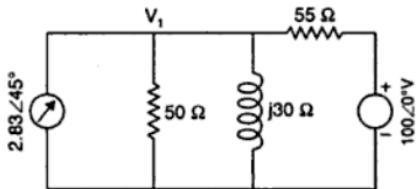


Fig. 67

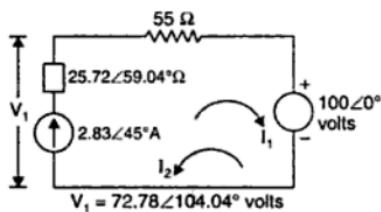


Fig. 68

Let the impedance of the current source be Z_i , then

$$\frac{1}{Z_i} = \frac{1}{50\angle 0^\circ} + \frac{1}{30\angle 90^\circ} = \frac{30\angle 90^\circ + 50\angle 0^\circ}{1500\angle 90^\circ} = \frac{50 + j30}{1500\angle 90^\circ} = \frac{58.31\angle 30.96^\circ}{1500\angle 90^\circ}$$

$$Z_i = \frac{1500\angle 90^\circ}{58.31\angle 30.96^\circ} = 25.72 \angle 59.04^\circ = (13.23 + j22.05) \Omega$$

Voltage across current source,

$$V_1 = IZ_i = 2.83 \angle 45^\circ \times 25.72 \angle 59.04^\circ = 72.78 \angle 104.04^\circ \text{ volts. (Ans.)}$$

Current supplied by one source,

$$\begin{aligned} I_1 &= \frac{V_1}{Z_i + R} = \frac{72.78\angle 104.04^\circ}{13.23 + j22.05 + 55} = \frac{72.78\angle 104.04^\circ}{68.25 + j22.05} \\ &= \frac{72.78\angle 104.04^\circ}{71.72\angle 17.91^\circ} = 1.015 \angle 86.13^\circ = (0.0685 + j1.01) \text{ A} \end{aligned}$$

Current supplied by the other source,

$$I_2 = \frac{V_2}{Z_i + R} = \frac{100\angle 0^\circ}{71.72\angle 17.91^\circ} = 1.394 \angle (-17.91^\circ) = 1.326 - j0.428$$

Current supplied by the voltage source,

$$\begin{aligned} I &= I_2 - I_1 = 1.326 - j0.428 - 0.0685 - j1.01 = 1.2575 - j1.438 \\ &= 1.91 \angle -48.83 \text{ amp. (Ans.)} \end{aligned}$$

4.6.3. Series-Parallel Circuits

Series-parallel circuits may be solved by the following methods :

1. Admittance method.
2. Symbolic method.

1. Admittance method :

In series-parallel circuits, the parallel circuit is first reduced to an equivalent series circuit and then combined with the rest of the circuit as usual.

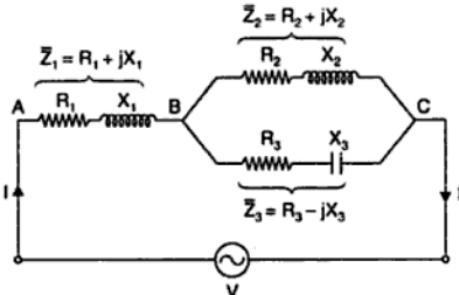


Fig. 69. Series-parallel circuit.

For a parallel circuit,

$$\text{Equivalent series resistance, } R_{eq} = Z \cos \phi = \frac{1}{Y} \cdot \frac{G}{Y} = \frac{G}{Y^2}$$

$$\text{Equivalent series reactance, } X_{eq} = Z \sin \phi = \frac{1}{Y} \cdot \frac{B}{Y} = \frac{B}{Y^2}$$

2. Symbolic method :

Refer series-parallel circuit shown in Fig. 69. First calculate the equivalent impedance of parallel branches and then add it to the series impedance to get the total impedance of the circuit. Then current flowing through the circuit is found as follows :

$$\bar{Y}_2 = \frac{1}{R_2 + jX_2} \quad \text{and} \quad \bar{Y}_3 = \frac{1}{R_3 - jX_3}$$

$$\therefore \bar{Y}_{23} = \frac{1}{R_2 + jX_2} + \frac{1}{R_3 - jX_3}$$

$$\therefore \bar{Z}_{23} = \frac{1}{\bar{Y}_{23}} ; \bar{Z}_1 = R_1 + jX_1$$

$$\bar{Z} = \bar{Z}_{23} + \bar{Z}_1$$

$$\therefore \bar{I} = \frac{\bar{V}}{\bar{Z}}$$

Example 48. For the circuit shown in Fig. 70 calculate :

- (i) Currents I_A , I_B and I_C .
 - (ii) Total power factor for the whole circuit.
- Draw the complete phasor diagram.

Solution. Refer Fig. 70.

Given : $\bar{Z}_A = 2 + j1.5 = 2.5\angle 36.9^\circ$; $\bar{Z}_B = 5 - j3.5 = 6.1\angle -35^\circ$, $\bar{Z}_C = 3 + j2.5 = 3.9\angle 39.8^\circ$

(i) Currents I_A , I_B and I_C :

$$\begin{aligned}\frac{1}{\bar{Z}_{AB}} &= \frac{1}{\bar{Z}_A} + \frac{1}{\bar{Z}_B} \quad \text{or} \quad \bar{Z}_{AB} = \frac{\bar{Z}_A \bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} = \frac{2.5\angle 36.9^\circ \times 6.1\angle -35^\circ}{(2 + j1.5) + (5 - j3.5)} \\ &= \frac{15.25\angle 1.9^\circ}{7 - j2} = \frac{15.25\angle 1.9^\circ}{7.28\angle -16^\circ} = 2.095\angle 17.9^\circ = 2 + j0.65\end{aligned}$$

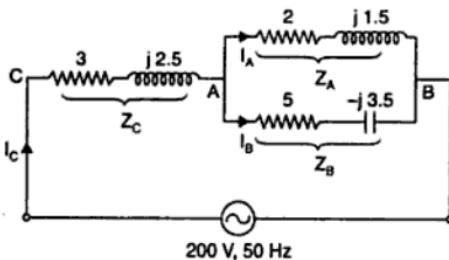


Fig. 70. Circuit diagram.

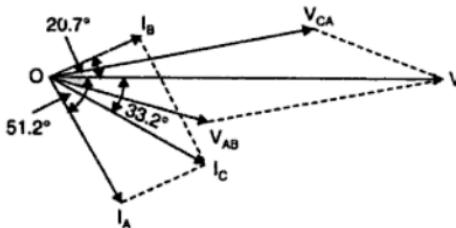


Fig. 71. Phasor diagram.

$$\bar{Z} = \bar{Z}_C + \bar{Z}_{AB} = (3 + j2.5) + (2 + j0.65) = 5 + j3.15 = 5.9\angle 32.2^\circ$$

Let

$$\bar{V} = 200\angle 0^\circ,$$

Then,

$$\bar{I}_C = \frac{\bar{V}}{\bar{Z}} = \frac{200\angle 0^\circ}{5.9\angle 32.2^\circ} = 33.9\angle -32.2^\circ. \quad (\text{Ans.})$$

$$\bar{I}_A = \bar{I}_C \times \frac{\bar{Z}_B}{\bar{Z}_A + \bar{Z}_B} = 33.9\angle -32.2^\circ \times \frac{6.1\angle -35^\circ}{7.28\angle -16^\circ} = 28.4\angle -51.2^\circ. \quad (\text{Ans.})$$

$$\bar{I}_B = \bar{I}_C \times \frac{\bar{Z}_A}{\bar{Z}_A + \bar{Z}_B} = 33.9\angle -32.2^\circ \times \frac{2.5\angle 36.9^\circ}{7.28\angle -16^\circ} = 11.64\angle 20.7^\circ. \quad (\text{Ans.})$$

(ii) Total power factor in the whole circuit :

The phase angle between V and total circuit current I_C is 32.2° .

∴ Power factor for the whole circuit ; $\cos \phi = \cos 32.2^\circ = 0.846$ (lag). (Ans.)

For drawing the phasor diagram of Fig. 71, V_{CA} and V_B have to be calculated.

$$\bar{V}_{CA} = \bar{I}_C \bar{Z}_C = 33.9 \angle -32.2^\circ \times 3.9 \angle 39.8^\circ = 132.2 \angle 7.6^\circ$$

$$\bar{V}_{AB} = \bar{I}_C \bar{Z}_{AB} = 33.9 \angle -32.2^\circ \times 2.095 \angle 17.9^\circ = 71 \angle -14.3^\circ$$

Fig. 71 shows the complete phasor diagram.

Example 49. Determine the current drawn by the following circuit (Fig. 72) when a voltage of 200 V is applied across the same. Draw the phasor diagram.

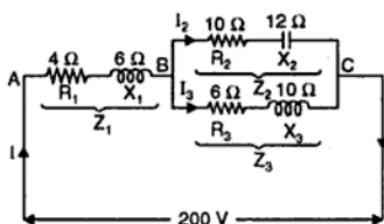


Fig. 72. Series parallel circuit

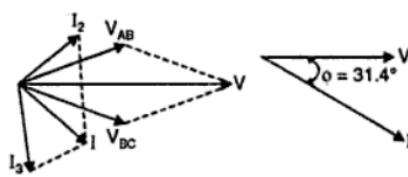


Fig. 73. Phasor diagram

(Elect. Engg. Bangalore University)

Solution. Refer Fig. 72.

$$Z_1 = (4 + j6) = 7.2 \angle 56.3^\circ; Z_2 = (10 - j12) = 15.6 \angle -50.2^\circ$$

$$Z_3 = (6 + j10) = 11.7 \angle 59^\circ$$

$$Z_{BC} = \frac{Z_2 Z_3}{Z_2 + Z_3} = \frac{(10 - j12)(6 + j10)}{(10 - j12) + (6 + j10)} = \frac{(10 - j12)(6 + j10)}{(16 - j2)} = \frac{(180 + j28)}{(16 - j2)}$$

$$= \frac{(180 + j28)(16 + j2)}{(16 - j2)(16 + j2)} = \frac{2824 + j808}{260} = 10.9 + j3.1 = 11.3 \angle 15.9^\circ$$

$$Z = Z_1 + Z_{BC} = (4 + j6) + (10.9 + j3.1) = (14.9 + j9.1) = 17.5 \angle 31.4^\circ$$

$$\text{Assuming } V = 200 \angle 0^\circ; I = \frac{V}{Z} = \frac{200 \angle 0^\circ}{17.5 \angle 31.4^\circ} = 11.4 \angle -31.4^\circ$$

For drawing the phasor diagram, let us find the following quantities :

$$V_{AB} = IZ_1 = 11.4 \angle -31.4^\circ \times 7.2 \angle 56.3^\circ = 82.08 \angle 24.9^\circ$$

$$V_{BC} = IZ_{BC} = 11.4 \angle -31.4^\circ \times 11.3 \angle 15.9^\circ = 128.8 \angle -15.5^\circ$$

$$I_2 = \frac{V_{BC}}{Z_L} = \frac{128.8 \angle -15.5^\circ}{15.6 \angle -50.2^\circ} = 8.26 \angle 34.7^\circ$$

$$I_3 = \frac{V_{BC}}{Z_3} = \frac{128.8 \angle -15.5^\circ}{11.7 \angle 59^\circ} = 11 \angle -74.5^\circ$$

Various currents and voltages are shown in their phase relationship in Fig. 73.

4.6.4. Resonance in parallel circuits

In case of a series circuit consisting of R (resistance), L (inductance) and C (capacitance), resonance takes place when $V_L = V_C$ i.e., when $X_L = X_C$. In other words, resonance takes place when

the power factor of the circuit approaches **unity**. The basic condition for resonance, i.e., power factor of the entire circuit being unity, remains the same for parallel circuits also. Thus, **resonance in a parallel circuit will occur, when the power factor of the entire circuit becomes unity.**

A parallel circuit consisting of an inductive coil in parallel with a capacitor is shown in Fig. 74 (a). The phasor diagram of this circuit with applied voltage as the reference phasor is shown in Fig. 74 (b). The current drawn by the inductive branch lags the applied voltage by an angle ϕ_L . The current drawn by the capacitive branch leads the applied voltage by 90° .

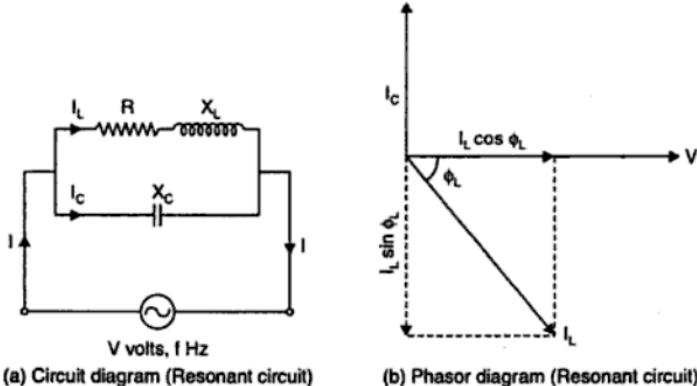


Fig. 74. Resonance in a parallel circuit.

The power factor of the current becomes unity when the total current drawn by the entire circuit is in phase with the applied voltage. This will happen only when the current drawn by the capacitive branch I_C equals the active component of the current of the inductive branch I_L [Fig. 74 (b)].

Hence for **resonance** in parallel circuit.

$$I_C = I_L \sin \phi_L \quad \dots(18)$$

$$\text{Now, } I_L = \frac{V}{Z} ; \sin \phi_L = \frac{X_L}{Z} \text{ and } I_C = \frac{V}{X_C}$$

Hence, condition for resonance becomes

$$\frac{V}{X_C} = \frac{V}{Z} \times \frac{X_L}{Z} \quad \text{or} \quad Z^2 = X_L \times X_C$$

$$\text{Now, } X_L = \omega L, \quad X_C = \frac{1}{\omega C}$$

$$\therefore Z^2 = \frac{\omega L}{\omega C} = \frac{L}{C} \quad \dots(19)$$

$$\text{or} \quad R^2 + X_L^2 = R^2 + (2\pi f_r L)^2 = \frac{L}{C}$$

$$\text{or} \quad (2\pi f_r L)^2 = \frac{L}{C} - R^2 \quad \text{or} \quad 2\pi f_r = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

$$\text{or} \quad f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \dots(20)$$

This is the resonant frequency and is given in Hz if R is in ohm, L is in henry and C in farad.
If R is negligible, then

$$f_r = \frac{1}{2\pi\sqrt{LC}} \quad \text{...same as for series resonance.}$$

Current at resonance

Refer Fig. 74 (b). Since wattless component is zero, the circuit current is given as :

$$I = I_L \cos \phi_L = \frac{V}{Z} \times \frac{R}{Z} = \frac{VR}{Z^2}$$

Putting the value of $Z^2 = \frac{L}{C}$ from eqn. (19), we get

$$I = \frac{VR}{L/C} = \frac{V}{L/C R} \quad \dots(21)$$

Thus, the impedance offered by a resonant parallel circuit = $\frac{L}{CR}$.

This impedance is purely resistive and generally termed as *equivalent* or *dynamic impedance* of the circuit. As the resultant current drawn by a resonant parallel circuit is minimum, the circuit is normally called **rejector** circuit. Such a type of circuit is quite useful in *radio work*.

The phenomenon of resonance in *parallel circuits* is normally termed as "**current resonance**" whereas it is termed "**voltage resonance**" in *series circuit*.

Resonance characteristics :

Fig. 75 shows the characteristics of the parallel circuit consisting of an inductance L and capacitance C in parallel plotted against frequency, the voltage applied being constant.

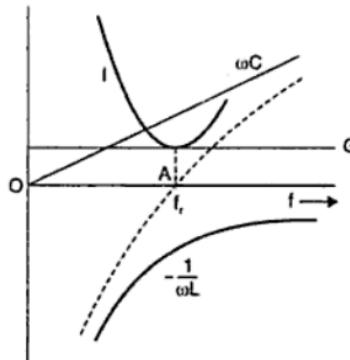


Fig. 75. Resonance characteristics.

$$\text{Inductive susceptance, } b = -\frac{1}{X_L} = -\frac{1}{\omega L} = -\frac{1}{2\pi f L}$$

Thus inductive susceptance is *inversely proportional* to the frequency and is represented by rectangular hyperbola in the fourth quadrant (because it is assumed -ve).

$$\text{Capacitive susceptance, } b = \frac{1}{X_C} \omega C = 2\pi f C$$

Thus capacitive susceptance is *directly proportional* to the frequency and is represented by a straight line passing through the origin.

Net susceptance, B is the difference of the two susceptances and is represented by the dotted hyperbola. The net susceptance is zero at point A, hence *admittance is minimum* and is equal to G . Thus, at point A, *line current is minimum*. The frequency at which the total current becomes minimum is the resonant frequency f_r .

Evidently, below the resonant frequency, the inductive susceptance predominates, thus making the circuit current to be lagging, whereas beyond f_r , capacitive susceptance predominates and the current leads the applied voltage. At resonant frequency f_r , the current is in phase with the applied voltage.

Hence at *parallel resonance* it is seen that :

1. The admittance of the circuit is *minimum* and is *equal to the conductance of the circuit*.

2. The *current drawn is minimum*.

3. The phase angle between the current and voltage is zero, the *power factor is unity*.

4. The resonant frequency is given by $f_r = \frac{1}{2\pi\sqrt{LC}}$ if the *resistance in the inductance and capacitance branches is negligible*.

4.6.5. Comparison of series and parallel resonant circuits

S. No.	Aspects	Series circuit (R-L-C)	Parallel circuit (R-L and C)
1.	<i>Impedance at resonance</i>	Minimum	Maximum
2.	<i>Current at resonance</i>	Maximum = $\frac{V}{R}$	Minimum = $V/(L/CR)$
3.	<i>Effective impedance</i>	R	L/CR
4.	<i>Power factor at resonance</i>	Unity	Unity
5.	<i>Resonant frequency</i>	$\frac{1}{2\pi\sqrt{LC}}$	$\frac{1}{2\pi} \sqrt{\left(\frac{1}{LC} - \frac{R^2}{L^2}\right)}$
6.	<i>It magnifies</i>	Voltage	Current
7.	<i>Magnification is</i>	$\frac{\omega L}{R}$	$\frac{\omega L}{R}$

4.6.6. Q-factor of a parallel circuit

It is defined as the *ratio of the current circulating between its two branches to the line current drawn from the supply or simply, as the current magnification*.

$$\text{Q-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} \quad \dots(22)$$

- It may be noted that in *series circuits*, *Q-factor gives the voltage magnification*, whereas in *parallel circuits* it gives the *current magnification*.

Bandwidth of a parallel resonant circuit :

The bandwidth of a parallel circuit is defined in the same way as that for a series circuit. This circuit also has upper and lower half-power frequencies where power dissipated is half of that at resonant frequency.

The net susceptance B , at bandwidth frequencies, equals conductance. Hence,

$$\text{At } f_2 : \quad B = B_{C2} - B_{L2}$$

$$\text{At } f_1 : \quad B = B_{L1} - B_{C1}$$

$$\text{Hence } Y = \sqrt{G^2 + B^2} = \sqrt{2}G \text{ and } \phi = \tan^{-1} \left(\frac{B}{G} \right) = \tan^{-1} (1) = 45^\circ$$

However, at off-resonant frequencies, $Y > G$ and $B_C \neq B_L$ and phase angle is greater than zero.

Example 50. An inductive circuit of resistance 2 ohms and inductance 0.01 H is connected to a 250 V, 50 Hz supply.

(i) What capacitance placed in parallel will produce resonance?

(ii) Determine also the total current taken from the supply and the currents in the branch circuit. (Kerala University)

Solution. Given : $R = 2 \Omega$; $L = 0.01 \text{ H}$, Supply voltage = 250 V, 50 Hz.

(i) Value of capacitance which will produce resonance, C :

$$\text{Now, } X_L = 2\pi f L = 2\pi \times 50 \times 0.01 = 3.14 \Omega$$

$$Z = \sqrt{R^2 + X_L^2} = \sqrt{2^2 + 3.14^2} = 3.72 \Omega$$

$$\text{We know that, } Z^2 = \frac{L}{C} \quad \text{or} \quad C = \frac{L}{Z^2}$$

$$\therefore C = \frac{0.01}{(3.72)^2} = 722.6 \times 10^{-6} \text{ F} \quad \text{or} \quad 722.6 \mu\text{F. (Ans.)}$$

(ii) Total current and currents in the branch circuits, I, I_L , I_C :

$$I_{R-L} = \frac{V}{Z} = \frac{250}{3.72} = 67.2 \text{ A. (Ans.)}$$

$$\tan \phi_L = \frac{3.14}{2} = 1.57 \quad \text{or} \quad \phi_L = \tan^{-1}(1.57) = 57.5^\circ \quad (\text{Ans.})$$

Hence, current in $R-L$ branch lags the applied voltage by 57.5° .

$$I_C = \frac{V}{X_C} = \frac{V}{1/\omega C} = \omega VC = 2\pi \times 50 \times 250 \times 722.6 \times 10^{-6} = 56.75 \quad (\text{Ans.})$$

This current leads the applied voltage by 90° .

Total current, $I = I_{R-L} \cos \phi = 67.2 \cos 57.5^\circ = 36.1 \text{ A. (Ans.)}$

$$\left[\text{or } I = \frac{V}{L/CR} = \frac{VCR}{L} = \frac{250 \times 722.6 \times 10^{-6} \times 2}{0.01} = 36.1 \text{ A} \right]$$

5. TRANSIENTS

5.1. General Aspects

If a circuit is switched from one condition to another either by a change in the applied voltage or change in a circuit parameter, there exists a transitional period during which the branch currents and voltage drops change from their former values to new ones. After transition period, the circuit becomes steady.

The **transient disturbances** in the electrical circuits are disturbances caused by sudden switching off and on or short circuit of the circuit and sudden change in the applied voltage. The current developed in the circuit due to this disturbance is called the "transient current". The "resultant current" in the circuit is the steady state current with a transient current superimposed. The transient currents are found to be associated with the changes in stored energy in capacitors and inductors. Hence in a purely resistive circuit no transient current is developed since there is no stored energy in a resistor.

Single energy and double energy transients :

- Single energy transient is the transient disturbance where only one form of energy, either electromagnetic or electrostatic is involved e.g., transient disturbance in a circuit consisting of resistor and inductor i.e., $R-L$ circuit or a circuit consisting of resistor and capacitor i.e., $R-C$ circuit.
- Double energy transient is the transient disturbance where both electromagnetic and electrostatic energies are involved e.g., transient disturbance in a circuit consisting of resistor, inductor and capacitor i.e., $R-L-C$ circuit.

5.2. D.C. Transients

(i) R-L transients :

In the R - L circuit shown in Fig. 76

$$i = \frac{V}{R} [1 - e^{-(R/L)t}] \quad \dots(23)$$

The plot of i (exponential rise equation) versus time is shown in Fig. 77.

The time constant (λ) for the above function is the time at which the exponent of e is unity. Thus in this case time constant (λ) is L/R . At one time constant, the value of i will be

$$i = (1 - e^{-1}) = 1 - 0.368 = 0.632$$

At this time current will be 63.2% of its final value.

The voltage across inductance,

$$v_L = L \frac{di}{dt} = V e^{-(R/L)t} \quad \dots(24)$$

and voltage across resistor,

$$v_R = V [1 - e^{-(R/L)t}] \quad \dots(25)$$

The exponential rise of resistor voltage and exponential decay of inductor voltage are shown in Fig. 78.

$$\text{Also, } v_R + v_L = V [1 - e^{-(R/L)t}] + V e^{-(R/L)t} = V$$

Power in the circuit elements is given by

$$P_R = \frac{V^2}{R} [1 - 2e^{-(R/L)t} + e^{-2(R/L)t}] \quad \dots(26)$$

$$P_L = \frac{V^2}{R} [e^{-(R/L)t} - e^{-2(R/L)t}] \quad \dots(27)$$

Total power,

$$P = P_R + P_L = \frac{V^2}{R} [1 - e^{-(R/L)t}] \quad \dots(28)$$

(ii) R-C transients :

In the R - C circuit shown in Fig. 79,

$$i = \frac{V}{R} e^{-t/RC}$$

Transients voltages across R and C are given by

$$v_R = V e^{-t/RC} \quad \dots(29)$$

$$v_C = V (1 - e^{-t/RC}) \quad \dots(30)$$

Also, the power in circuit elements is given by

$$P_R = \frac{V^2}{R} e^{-2t/RC} \quad \dots(31)$$

$$P_L = \frac{V^2}{R} (e^{-t/RC} - e^{-2t/RC}) \quad \dots(32)$$

(iii) R-L-C transients :

For R - L - C circuit shown in Fig. 81 the following integro-differential equation can be written as follows :

$$R_i + L \frac{di}{dt} + \frac{1}{C} \int idt = V \quad \dots(33)$$

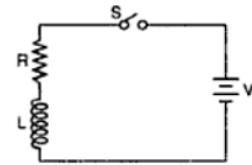


Fig. 76. R - L circuit.

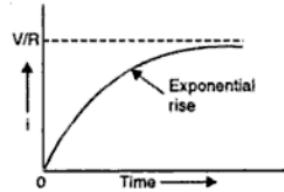


Fig. 77

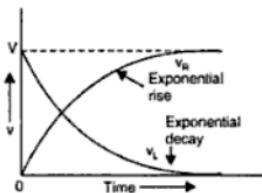


Fig. 78

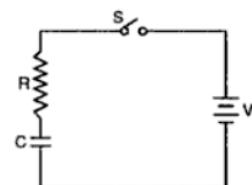


Fig. 79. R - C circuit.

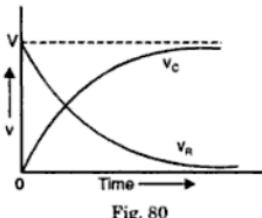


Fig. 80

While solving for i , the following three cases are considered :

$$\text{Case I. } \left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

In this case the current is given by

$$i = C_1 e^{\alpha t} [C_1 (e^{\beta t} + C_2 e^{-\beta t})] \quad \dots(34)$$

$$\text{Case II. } \left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$$

$$\text{Here, } i = e^{\alpha t} (C_1 + C_2 t) \quad \dots(35)$$

$$\text{Case III. } \left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$$

$$\text{Here, } i = e^{\alpha t} (C_1 \cos \beta t + C_2 \sin \beta t) \quad \dots(36)$$

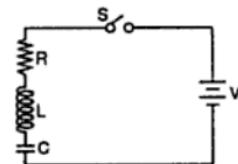


Fig. 81. R-L-C circuit.

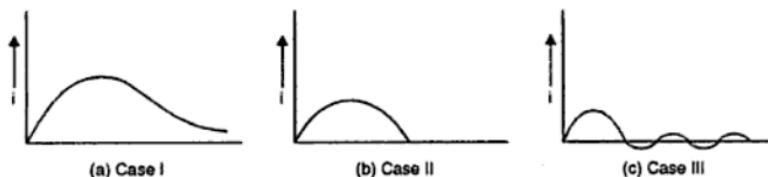


Fig. 82

In all the above cases the current contains the factor $e^{\alpha t}$ and since $\alpha = -R/2L$ the final value is zero, assuming that the complimentary function decays in a relatively short time. Fig. 82 shows the value of i for initial values zero and initial slope positive.


5.3. A.C. Transients

(i) R-L sinusoidal transient : Refer Fig. 83

Here the voltage function could be at any point in the period at the instant of closing the switch and therefore the phase angle ψ can take any values from 0 to 2π rad/sec.

In this case, the current (i) is given by
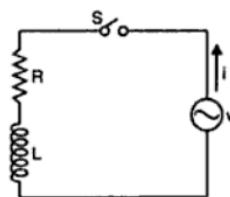
$$i = e^{-(R/L)t} \left[\frac{-V_{max}}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\psi - \tan^{-1} \frac{\omega L}{R} \right) \right] + \frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\omega t + \psi - \tan^{-1} \frac{\omega L}{R} \right) \quad \dots(37)$$



$$v = V_{max} \sin (\omega t + \psi)$$

Fig. 83. R-L circuit.

$$\text{where } \tan^{-1} \left(\frac{\omega L}{R} \right) = \phi.$$

It may be noted that :

- The first part (transient component of current, i_t , of the above equation contains the factor $e^{-(R/L)t}$ which has a value of zero in a relatively short time.

— The second part of the above equation is the steady current (i_s) which lags the applied voltage by $\tan^{-1} \frac{\omega L}{R}$.

$$\text{Here, } \frac{V_{max}}{R^2 + \omega^2 L^2} = I_{max}, \tan^{-1} \left(\frac{\omega L}{R} \right) = \phi$$

(ii) R-C sinusoidal transient :

For R-C circuit shown in Fig. 84 the basic equation is :

$$Ri + \frac{1}{C} \int v dt = V_{max} \sin(\omega t + \psi) \quad \dots(38)$$

Here the current i is given by,

$$i = e^{-t/(RC)} \left[\frac{V_{max}}{R} \sin \psi - \frac{V_{max}}{\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}} \sin \left(\psi + \tan^{-1} \frac{1}{\omega CR} \right) + \frac{V_{max}}{\sqrt{R^2 + \left(\frac{1}{\omega C} \right)^2}} \sin \left(\omega t + \psi + \tan^{-1} \frac{1}{\omega CR} \right) \right] \quad \dots(39)$$

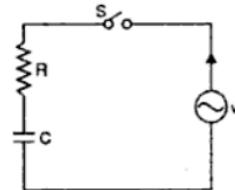


Fig. 84. R-C circuit.

It may be noted that :

—The first part of the above equation is the transient with decay factor $e^{-t/RC}$

—The second part is the steady current which leads the applied voltage by $\tan^{-1} \frac{1}{\omega CR}$.

Example 51. A series circuit has $R = 10 \Omega$ and $L = 0.1 \text{ H}$. A direct voltage of 200 V is suddenly applied to it. Calculate the following :

(i) The voltage drop across the inductance at the instance of switching on and at 0.01 second, and

(ii) The flux linkages at these instants.

(Bombay University)

Solution. Given : $R = 10 \Omega$; $L = 0.1 \text{ H}$; $V = 200$ volts

(i) The voltage drop across the inductance :

(a) *Switching instant.* At the instant of switching on, $i = 0$, so that $iR = 0$ hence all the applied voltage must drop across the inductance only. Therefore, voltage drop across inductance = 200 V. (Ans.)

(b) When $t = 0.01$ second

$$i = \frac{V}{R} [1 - e^{-(R/L)t}] \quad \dots[\text{Eqn. 23}]$$

$$= \frac{200}{10} [1 - e^{-(10/0.1) \times 0.01}] = 20(1 - e^{-1}) = 12.64 \text{ A}$$

and, $iR = 12.64 \times 10 = 126.4 \text{ V}$

∴ The voltage drop across the inductance = $\sqrt{(200)^2 - (126.4)^2} = 155 \text{ V. (Ans.)}$

(ii) The flux linkages :

$$\text{Now, } L = \frac{N\phi}{i} \quad \text{or} \quad N\phi = Li$$

∴ Flux linkages ($N\phi$) = $Li = 0.1 \times 12.64 = 1.264 \text{ Wb-turns. (Ans.)}$

Example 52. A choke has a resistance of 50Ω and inductance of 1.0 H . It is supplied with an A.C. voltage given by $141 \sin 314t$. Find the expression for transient component of the current flowing through the choke after the voltage is suddenly switched on. (Jadavpur University)

Solution. Given : $R = 50 \Omega$; $L = 1.0 \text{ H}$; $e = 141 \sin 314t$

Expression for transient component of the current :

The equation of the transient component of the current is given by :

$$i_t = I_{max} \sin \phi e^{-Rt/L} \quad \dots[\text{Eqn. 37}]$$

Here $I_{max} = \frac{V_{max}}{Z} = \frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} = \frac{141}{\sqrt{(50)^2 + (314)^2 (1.0)^2}} = 0.443 \text{ A}$

and,

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right) = \tan^{-1} \left(\frac{314 \times 1.0}{50} \right) = 80.95^\circ$$

$$\therefore i_t = 0.443 \sin 80.95^\circ e^{-(50/1.0)t} = 0.437 e^{-50t}. \quad (\text{Ans.})$$

Example 53. A series circuit has $R = 10 \Omega$ and $L = 0.1 \text{ H}$. A 50 Hz sinusoidal voltage of maximum value of 400 V is applied across this circuit. Find an expression for the value of current at any instant after the voltage is applied, assuming that the voltage is zero at the instant of application. Calculate its value 0.02 second after switching on. (Punjab University)

Solution. Given : $R = 10 \Omega$; $L = 0.1 \text{ H}$; $f = 50 \text{ Hz}$; $V_{max} = 400 \text{ V}$; $t = 0.02 \text{ s}$.

The current consists of transient component and steady-state component. The equation of the resultant current is given by :

$$i = e^{-(R/L)t} \left[-\frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\psi - \tan^{-1} \frac{\omega L}{R} \right) \right] \quad (\text{Transient current})$$

$$+ \frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\omega t + \psi - \tan^{-1} \frac{\omega L}{R} \right) \quad \dots[\text{Eqn. 37}]$$

(Steady-state current)

where $\frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} = I_{max}, \tan^{-1} \left(\frac{\omega L}{R} \right) = \phi$

Here, $\psi = 0$ as per given condition, then

$$i = e^{-(R/L)t} \left[-\frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(-\tan^{-1} \frac{\omega L}{R} \right) \right]$$

$$+ \frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} \sin \left(\omega t - \tan^{-1} \frac{\omega L}{R} \right) \quad \dots(i)$$

Now, $\frac{V_{max}}{\sqrt{R^2 + \omega^2 L^2}} = I_{max} = \frac{400}{\sqrt{10^2 + (314)^2 (0.1)^2}} = 12.14 \text{ A}$

$$\tan^{-1} \frac{\omega L}{R} = \phi = \tan^{-1} \left(\frac{314 \times 0.1}{10} \right) = 72.3^\circ = 1.262 \text{ rad.}$$

Substituting the value in eqn. (i), we get

$$i = e^{-(10/0.1) \times 0.02} [-12.14 \sin (-72.3^\circ)] + 12.14 \sin (314 \times 0.02 - 1.262)$$

$$= e^{-2} [12.14 \sin (72.3^\circ)] + 12.14 \sin (5.018)$$

(rad)

$$= 0.1353 (12.14 \times 0.9527) + 12.14 \sin (287.5^\circ)$$

(deg)

$$= 1.56 - 11.58 = -10.02 \text{ A.} \quad (\text{Ans.})$$

Example 54. In a simple saw-tooth generator circuit with the thyratrons switches on at 150 V and switches off at 10 V. If this circuit is supplied with 250 V D.C. source; find the time period of saw-tooth wave. The resistance and capacitance have the values of 10 k Ω and 1 μF respectively.

(Jadavpur University)

Solution. Given : $R = 10 \text{ k}\Omega$; $\mu = 1 \mu\text{F} = 1 \times 10^{-6} \text{ F}$; Circuit voltage = 250 V; Switching on voltage = 150 V; Switching off voltage = 10 V.

Time period of saw-tooth wave : Refer Fig. 84

Let, V = Applied voltage

v_{C1} = Switching-off voltage of thyratron = 10 V

v_{C2} = Switching-on voltage of thyratron = 150 V

Now, $v = V(1 - e^{-t/RC})$

...[Eqn. 30]

$$\therefore v_{C1} = V(1 - e^{-t_1/RC}) \quad \dots(i)$$

$$v_{C2} = V[1 - e^{-(t_1 + T)/RC}] \quad \dots(ii)$$

where, T is the time period of the saw-tooth wave.

Eqns. (i) and (ii) can be written as :

$$V - v_{C1} = e^{-t_1/RC} \quad \dots(iii)$$

$$V - v_{C2} = e^{-(t_1 + T)/RC} \quad \dots(iv)$$

Dividing (i) by (ii), we get

$$\frac{V - v_{C1}}{V - v_{C2}} = \frac{e^{-t_1/RC}}{e^{-(t_1 + T)/RC}} = e^{[-t_1/RC - (-t_1 + T)/RC]} = e^{T/RC}$$

$$\text{or } T/RC = \ln \left(\frac{V - v_{C1}}{V - v_{C2}} \right) \text{ or } T = \ln \left(\frac{V - v_{C1}}{V - v_{C2}} \right) \times RC$$

Here, $v_{C1} = 10 \text{ V}$; $v_{C2} = 150 \text{ V}$

Substituting the values, we get

$$T = \ln \left(\frac{250 - 10}{250 - 150} \right) \times 10 \times 10^3 \times 1 \times 10^{-6} = 0.00875 \text{ s. (Ans.)}$$

HIGHLIGHTS

- Modern alternators produce an e.m.f. which is for all practical purposes sinusoidal (i.e. a sine curve), the equation between the e.m.f. and time being

$$e = E_{\max} \sin \omega t$$

where e = instantaneous voltage; E_{\max} = maximum voltage;

ω = angle through which the armature has turned from neutral.

- The r.m.s. value of an alternating current is given by that steady (D.C.) current which when flowing through a given circuit produces the same heat as is produced by the alternating current when flowing through the same circuit for the same time.

$$I_{\text{rms}} = 0.707 I_{\max}$$

- The average or mean value of an alternating current is expressed by that steady current which transfers across any circuit the same charge as is transferred by that alternating current during the same time.

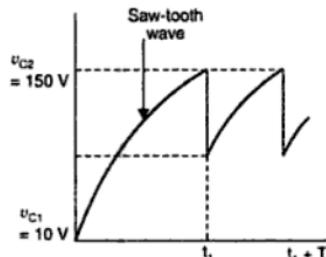


Fig. 84

$$I_{\text{eff}} = 0.637 I_{\text{max}}$$

Form factor is the ratio of r.m.s. value to average value of the wave form.

Peak factor is the ratio of maximum value to the r.m.s. value of the wave form.

4. The frequency (series circuit) of the voltage which gives the maximum value of the current in the circuit is called *resonant frequency* (f_r) and the circuit is said to be *resonant*.

$$f_r = \frac{1}{2\pi \sqrt{IC}}.$$

5. Q-factor of a series circuit is defined as equal to the voltage magnification in the circuit at resonance.

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}.$$

6. *Q-factor* of a parallel circuit is defined as the ratio of the current circulating between its two branches to the line current drawn from the supply or simply, as the current magnification.

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}}.$$

OBJECTIVE TYPE QUESTIONS

Choose the Correct Answer:

ANSWERS

- | | | | | | |
|---------|---------|---------|---------|---------|----------|
| 1. (a) | 2. (c) | 3. (b) | 4. (b) | 5. (d) | 6. (d') |
| 7. (b) | 8. (a) | 9. (a) | 10. (c) | 11. (b) | 12. (b) |
| 13. (b) | 14. (b) | 15. (b) | 16. (c) | 17. (a) | 18. (a) |
| 19. (b) | 20. (c) | 21. (c) | 22. (a) | 23. (c) | 24. (b) |
| 25. (a) | 26. (c) | 27. (d) | 28. (d) | 29. (c) | 30. (b) |
| 31. (d) | 32. (a) | 33. (c) | 34. (c) | 35. (a) | 36. (b) |
| 37. (e) | 38. (a) | 39. (e) | 40. (b) | 41. (e) | 42. (d') |
| 43. (d) | 44. (c) | 45. (c) | 46. (e) | 47. (c) | 48. (a) |
| 49. (a) | 50. (c) | 51. (d) | 52. (e) | 53. (d) | 54. (c) |
| 55. (c) | | | | | |

THEORETICAL QUESTIONS

1. Define the following terms :
Circuit, Electrical network, Active network, Node and Branch.
 2. What are the limitations of ohm's law ?
 3. State and explain Kirchhoff's laws.
 4. Discuss briefly application of Kirchhoff's laws.

5. Explain the nodal voltage method for solving networks. How are the nodal equations written ?
6. Explain Cramer's rule used for solving equations by determinants.
7. State and explain Superposition theorem.
8. State Norton's theorem. List the steps for finding the current in a branch of a network with the help of this theorem.
9. State Thevenin's theorem.
10. State the maximum power transfer theorem and explain its importance.
11. Define the following terms as applied to an alternating current :
Cycle, frequency, time period, amplitude.
12. What do you mean by the term "Phase difference" ?
13. Explain the following terms relating alternating current :

(i) R.M.S. value	(ii) Average value
(iii) Form factor	(iv) Peak factor.
14. Explain briefly the following as applied to A.C. series and parallel circuits :

(i) Resonance frequency	(ii) Q-factor.
-------------------------	----------------
15. What do you mean by transient disturbances ?
16. Define single energy and double energy transients.

UNSOLVED EXAMPLES

1. An alternating current of frequency 60 Hz has a maximum value of 120 A. Write down the equation for its instantaneous value. Reckoning time from the instant the current is zero and is becoming positive, find :
 - (i) The instantaneous value after $\frac{1}{360}$ second ;
 - (ii) The time taken to reach 96 A for the first time. [Ans. 103.9 A, 0.00245 second]
2. An alternating current of frequency 50 Hz has a maximum value of 100 A. Calculate :
 - (i) Its value 1/600 second after the instant the current is zero and its value decreasing thereafter wards.
 - (ii) How many seconds after the instant the current is zero (increasing thereafter wards) will the current attain the value of 86.6 A ? [Ans. - 50 A, 1/300 s]
3. Calculate the r.m.s. value, the form factor of a periodic voltage having the following values for equal time intervals changing suddenly from one value to the next : 0, 5, 10, 20, 50, 60, 50, 20, 10, 5, 0, 5, 10 V etc. What would be the r.m.s. value of sine wave having the same peak value ? [Ans. 31 V ; 23 V ; 1.35 ; (app.) ; 42.2 V]
4. A sinusoidally varying alternating current has an average value of 127.4 A. When its value is zero, then its rate of change is 62,800 A/s. Find the analytical expression for the sine wave. [Ans. $i = 200 \sin 100 \pi t$]
5. A coil of resistance 10Ω and inductance 0.1 H is connected in series with a $150 \mu\text{F}$ capacitor across a $200 \text{ V}, 50 \text{ Hz}$ supply. Calculate (i) the inductive reactance, (ii) the capacitive reactance, (iii) the impedance (iv) the current, (v) the power factor, (vi) the voltage across the coil and the capacitor respectively. [Ans. (i) 31.4Ω , (ii) 21.2Ω , (iii) 14.3Ω , (iv) 14 A , (v) 0.7 lag (vi) $460 \text{ V}, 297 \text{ V}$]
6. A circuit is made up of 10Ω resistance, 12 mH inductance and $281.5 \mu\text{F}$ capacitance in series. The supply voltage is 100 V (constant). Calculate the value of the current when the supply frequency is (i) 50 Hz and (ii) 150 Hz . [Ans. 8 A leading ; 8 A lagging]
7. A coil having a resistance of 10Ω and an inductance of 0.2 H is connected in series with a capacitor of $50.7 \mu\text{F}$. The circuit is connected across a $100 \text{ V}, 50 \text{ Hz}$ A.C. supply. Calculate (i) the current flowing (ii) the voltage across the capacitor (iii) the voltage across the coil. Draw a vector diagram to scale. [Ans. (i) 10 A (ii) 628 V (iii) 635 V]
8. A coil is in series with a $20 \mu\text{F}$ capacitor across a $230 \text{ V}, 50 \text{ Hz}$ supply. The current taken by the circuit is 8 A and the power consumed is 200 W . Calculate the inductance of the coil if the power factor of the circuit is (i) leading and (ii) lagging.

Sketch a vector diagram for each condition and calculate the coil power factor in each case.

(Ans. 0.415 H : 0.597 H : 0.0238 : 0.0166)

Given that the applied voltage is 200 V.

[Ans. 46 Hz ; 20 A ; 4 kW]

10. A circuit consists of an inductor which has a resistance of $10\ \Omega$ and an inductance of 0.3 H , in series with a capacitor of $30\ \mu\text{F}$ capacitance. Calculate :

 - The impedance of the circuit to currents of 40 Hz ;
 - The resonant frequency ;
 - The peak value of stored energy in joules when the applied voltage is 200 V at the resonant frequency.

(iii) The inductance.

JAN = 420 G 6.26 - E - 150 W

12. A resistance, a capacitor and a variable inductance are connected in series across a 200 V, 50 Hz supply. The maximum current which can be obtained by varying the inductance is 314 mA and the voltage across the capacitor is then 300 V. Calculate the capacitance and the values of the inductance and resistance.

13. A circuit consisting of a coil of resistance 12Ω and inductance 0.15 H in series with a capacitor of $12 \mu\text{F}$ is connected to a variable frequency supply which has a constant voltage of 24 V . Calculate : (i) The resonant frequency, (ii) The current in the circuit at resonance, (iii) The voltage across the capacitor and the coil at resonance. [Ans. (i) 153 Hz , (ii) 2 A , (iii) 224 V]

14. A resistance of $24\ \Omega$, a capacitance of $150\ \mu F$ and an inductance of $0.16\ H$ are connected in series with each other. A supply at $240\ V$, $50\ Hz$ is applied to the ends of the combination. Calculate (i) the current in the circuit (ii) the potential differences across each element of the circuit (iii) the frequency to which the supply would need to be changed so that the current would be at unity power-factor and find the current at this frequency. [Ans. (i) $6.37\ A$ (ii) $V_R = 152.8\ V$, $V_C = 320\ V$, $V_L = 123.3\ V$ (iii) $32\ Hz$; $10\ A$]

15. A coil-A of inductance $80\ mH$ and resistance $120\ \Omega$ is connected to a $230\ V$, $50\ Hz$ single-phase supply. In parallel with it is a $16\ \mu F$ capacitor in series with a $40\ \Omega$ non-inductive resistor B. Determine (i) The power factor of the combined circuit,

16. A choking coil of inductance 0.08 H and resistance 12 ohm. is connected in parallel with a capacitor of

17. A choking coil having a resistance of $20\ \Omega$ and an inductance of 0.07 henry is connected with a capacitor of $60\ \mu F$ capacitance which is in series with a resistor of $50\ \Omega$. Calculate the total current and the phase angle when this arrangement is connected to $220\ V, 50\ Hz$. [Ans. $7.15\ A, 0.943^\circ$ lag]

18. A coil of resistance of 15Ω and inductance 0.05 H is connected in parallel with a non-inductive resistor of 20Ω . Find (i) the current in each branch ; (ii) the total current (iii) the phase angle of resistive arrangement for an applied voltage of 200 V at 50 Hz . [Ans. $9.22 \text{ A} ; 10 \text{ A} ; 22.1^\circ$]

19. A sinusoidal 50 Hz voltage of 200 V (r.m.s.) supplies the following three circuits which are in parallel :
 (i) a coil of inductance 0.03 H and resistance 3 Ω ; (ii) a capacitor of $400 \mu\text{F}$ in series with a resistance of 100 Ω ; (iii) a coil of inductance 0.02 H and resistance 7 Ω in series with a $300 \mu\text{F}$ capacitor. Find the total current supplied and draw a complete vector diagram. [Ans. 29.4 A]

20. In a series-parallel circuit, the two parallel branches A and B are in series with C. The impedances are $Z_A = (10 - j8) \Omega$, $Z_B = (9 - j6) \Omega$ and $Z_C = (100 + j0)$. Find the currents I_A and I_B and the phase difference between them. Draw the phasor diagram. [Ans. $I_A = 12.71 \angle -30^\circ$; $I_B = 15 \angle -35^\circ$; $\phi = 58^\circ$]

Three-Phase A.C. Network

1. Introduction.
2. Advantages of polyphase systems.
3. Generation of three-phase voltages.
4. Phase sequence and numbering of phases.
5. Inter-connection of three phases.
6. Star or Wye (Y) connection.
7. Delta (Δ) or mesh connection.
8. Comparison between star and delta systems.
9. Measurement of power in 3-phase circuit—Three wattmeters method—Two wattmeters method—One wattmeter method.
10. Measurement of reactive volt amperes.
11. Types of energy meters.
12. Power factor improvement.
13. Earthing and Grounding—General Aspects—Objects of earthing—Specifications required for earthing as per I.S.I.—Methods of earthing—Sizes of earth wire and earth plate for domestic and motor installations—Indian electricity rules—Measurement of earth resistance by earth tester—Earthing of a power system—Highlights—Objective Type Questions—Theoretical Questions—Unsolved Examples.

1. INTRODUCTION

- Generation, transmission and heavy-power utilisation of A.C. electric energy almost invariably involve a type of system or circuit called a *polyphase system* or *polyphase circuit*. In such a system, each voltage source consists of a group of voltages having relative magnitudes and phase angles. Thus, a *m-phase system will employ voltage sources which, conventionally, consist of m voltages substantially equal in magnitude and successively displaced by a phase angle of $360^\circ/m$* .
- A *3-phase system will employ voltage sources which, conventionally, consist of three voltages substantially equal in magnitude and displaced by phase angles of 120°* . Because it possesses definite economic and operating advantages, the 3-phase system is by far the most common, and consequently emphasis is placed on 3-phase circuits.

2. ADVANTAGES OF POLYPHASE SYSTEMS

The advantages of polyphase systems over single-phase systems are :

1. A polyphase transmission line requires less conductor material than a single-phase line for transmitting the same amount power at the same voltage.
2. For a given frame size a polyphase machine gives a higher output than a single-phase machine. For example, output of a 3-phase motor is 1.5 times the output of single-phase motor of same size.
3. Polyphase motors have a uniform torque where most of the single-phase motors have a pulsating torque.
4. Polyphase induction motors are self-starting and are more efficient. On the other hand single-phase induction motors are not self-starting and are less efficient.
5. Per unit of output, the polyphase machine is very much cheaper.
6. Power factor of a single-phase motor is lower than that of polyphase motor of the same rating.
7. Rotating field can be set up by passing polyphase current through stationary coils.

8. Parallel operation of polyphase alternators is simple as compared to that of single-phase alternators because of pulsating reaction in single-phase alternator.

It has been found that the above advantages are best realised in the case of three-phase systems. Consequently, the electric power is generated and transmitted in the form of three-phase system.

3. GENERATION OF THREE-PHASE VOLTAGES

- Let us consider an elementary 3-phase 2-pole generator as shown in Fig. 1. On the armature are three coils, ll' , mm' , and nn' whose axes are displaced 120° in space from each other.

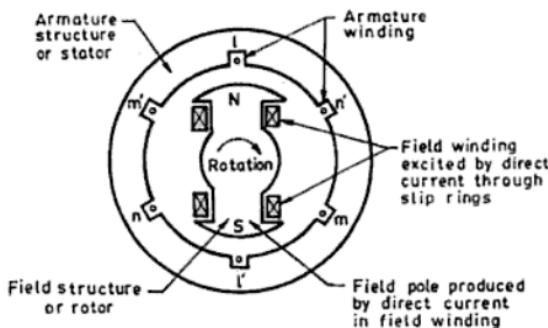


Fig. 1. Elementary 3-phase 2-pole generator.

- When the field is excited and rotated, voltages will be generated in the three phases in accordance with Faraday's law. If the field structure is so designed that the flux is distributed sinusoidally over the poles, the flux linking any phase will vary sinusoidally with time and sinusoidal voltages will be induced in three-phases. These three waves will be displaced 120 electrical degrees (Fig. 2) in time as a result of the phases being displaced

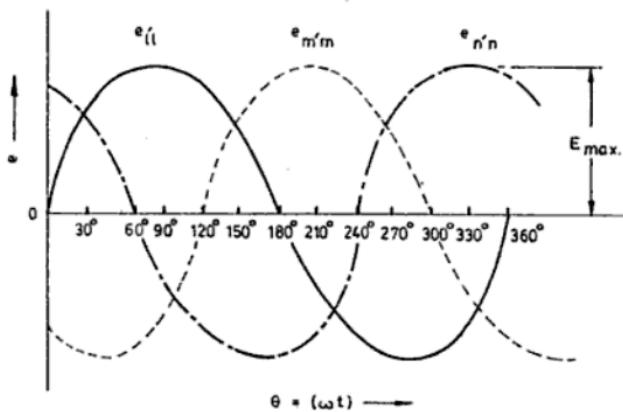


Fig. 2. Voltage waves generated in windings of Fig. 1.

120° in space. The corresponding phasor diagram is shown in Fig. 3. The equations of the instantaneous values of the three voltages (given by Fig. 2) are :

$$e_{l'l} = E_{\max} \sin \omega t$$

$$e_{m'm} = E_{\max} \sin (\omega t - 120^\circ)$$

$$e_{n'n} = E_{\max} \sin (\omega t - 240^\circ)$$

The sum of the above three e.m.f.s. is always zero as shown below :

Resultant instantaneous e.m.f.

$$\begin{aligned} &= e_{l'l} + e_{m'm} + e_{n'n} \\ &= E_{\max} \sin \omega t + E_{\max} \sin (\omega t - 120^\circ) \\ &\quad + E_{\max} \sin (\omega t - 240^\circ) \\ &= E_{\max} [\sin \omega t + (\sin \omega t \cos 120^\circ \\ &\quad - \cos \omega t \sin 120^\circ + \sin \omega t \cos 240^\circ \\ &\quad - \cos \omega t \sin 240^\circ)] \\ &= E_{\max} [\sin \omega t + (-\sin \omega t \cos 60^\circ - \cos \omega t \sin 60^\circ - \sin \omega t \cos 60^\circ + \cos \omega t \sin 60^\circ)] \\ &= E_{\max} (\sin \omega t - 2 \sin \omega t \cos 60^\circ) \\ &= E_{\max} (\sin \omega t - \sin \omega t) = 0. \end{aligned}$$

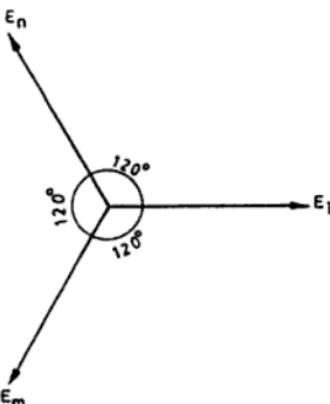


Fig. 3. Phasor diagram of generated voltages.

4. PHASE SEQUENCE AND NUMBERING OF PHASES

- By phase sequence is meant the order in which the three phases attain their peak or maximum.

In the generation of three-phase e.m.f.s. in Fig. 2 clockwise rotation of the field system in Fig. 1 was assumed. This assumption made the e.m.f. of phase 'm' lag behind that of 'l' by 120° and in a similar way, made that of 'n' lag behind that of 'm' by 120° (or that of l by 240°). Hence, the order in which the e.m.f.s. of phases l, m and n attain their maximum value is lm̄n. It is called the *phase order* or phase sequence $l \rightarrow m \rightarrow n$. If now the rotation of field structure of Fig. 1 is reversed i.e. made counter-clockwise, then the order in which three phases would attain their corresponding maximum voltages would also be reversed. The phase sequence would become $l \rightarrow n \rightarrow m$. This means that e.m.f. of phase 'n' would now lag behind that of phase 'l' by 120° instead of 240° as in the previous case.

The phase sequence of the voltages applied to a load, in general, is determined by the order in which the 3-phase lines are connected. The *phase sequence can be reversed by interchanging any pair of lines*. (In the case of an induction motor, reversal of sequence results in the reversed direction of motor rotation).

- The three-phases may be numbered l, m, n or 1, 2, 3 or they may be given three colours (as is customary).

The colours used commercially are *red*, *yellow* (or sometimes *white*) and *blue*. In this case sequence is RYB.

Evidently in any three-phase system, there are two possible sequences, in which three coils or phase voltages may pass through their maximum value i.e. red \rightarrow yellow \rightarrow blue (RYB) or red \rightarrow blue \rightarrow yellow (RBY).

By convention :

RYB taken as *positive*.

RBY taken as *negative*.

5. INTER-CONNECTION OF THREE PHASES

Each coil of three phases has two terminals [one 'start' (S) and another 'finish' (F)] and if individual phase is connected to a separate load circuit, as shown in Fig. 4, we get a non-interlinked 3-phase system. In such a system each circuit will require two conductors, therefore, 6 conductors in all. This makes the whole system *complicated and expensive*. Hence the *three phases are generally interconnected which results in substantial saving of copper*.

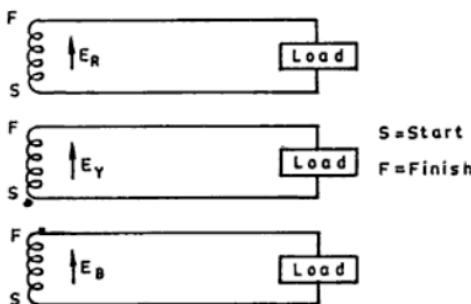


Fig. 4. Non-interlinked 3-phase system.

The general method of inter-connections are :

1. Star or Wye (Y) connection.
2. Mesh or delta (Δ) connection.

6. STAR OR WYE (Y) CONNECTION

- In this method of inter-connection the similar ends either the 'start' or 'finish' are joined together at point N . This common point N [Fig. 5 (a)] is called *star point* or *neutral point*. Ordinarily only three wires are carried to the external circuit giving 3-phase, 3-wire star connected system but sometimes a *fourth-wire*, known as *neutral wire* is carried to the neutral point of the external load circuit giving 3-phase, 4 wire star connected system.
- The *voltage between any line and the neutral point* (i.e. voltage across the phase winding) is called the '**phase voltage**' (E_{ph}) ; while the *voltage available between any pair of terminals* (or outers) is called the '**line voltage**' (E_L).
- In star connection, as is evident in Fig. 5 (a) there are two-phase windings between each pair of terminals, but since their *similar* ends have been joined together, they are in *opposition*. Obviously, the instantaneous value of potential difference between any two terminals is the *arithmetic difference* of the two-phase e.m.f.s. concerned. However, the r.m.s. value of this potential difference is given by the *vector difference* of the two-phase e.m.f.s.
- Fig. 5 (b) shows the vector diagram for phase voltages and currents in a star connection where a *balanced system has been assumed*. [A balanced system is one in which (i) the voltages in all phases are equal in magnitude and differ in phase from one another by

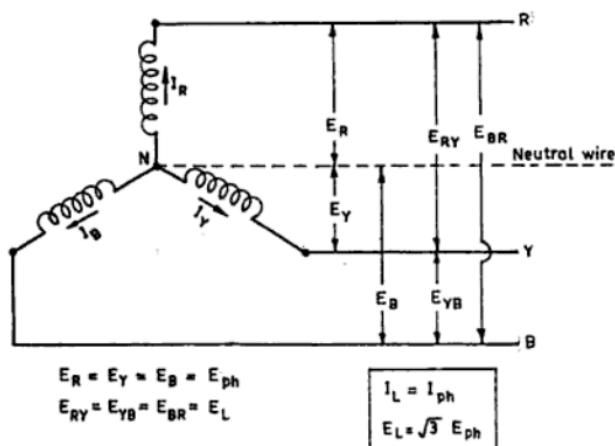


Fig. 5 (a)

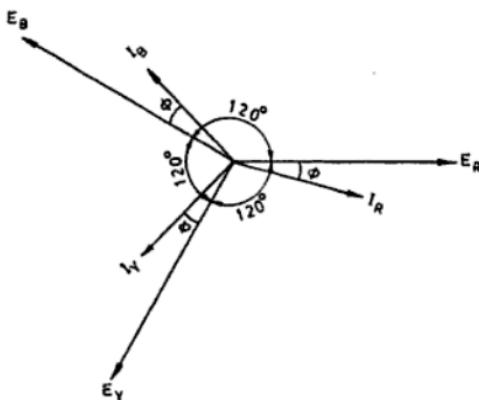


Fig. 5. (b) Star-connected three-phase net work.

equal angles, in this case, the angle $= 360/3 = 120^\circ$, (ii) the currents in the three phases are equal in magnitude and also differ in phase from one another by equal angles. A three-phase balanced load is that in which the loads connected across the three-phases are *identical*. Thus, we have

$$E_R = E_Y = E_B = E_{ph} \text{ (phase e.m.f.)}$$

Line voltage, $E_{RY} (= E_L) = \text{Vector difference of } E_R \text{ and } E_Y$
 $= E_R - E_Y$

Line voltage, $E_{YB} = E_Y - E_B$

Line voltage, $E_{BR} = E_B - E_R$.

(a) Relation Between Line Voltages and Phase Voltages. Refer Fig. 6.

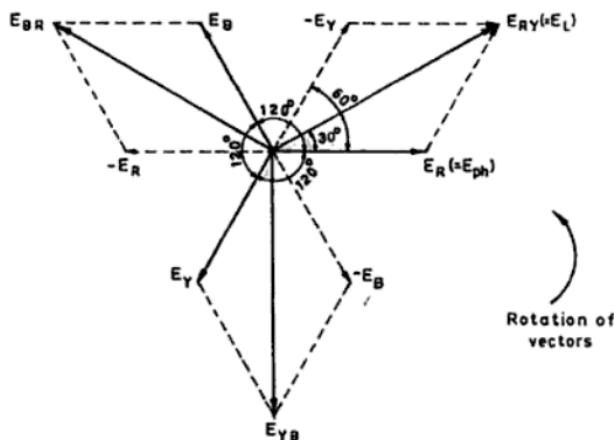


Fig. 6. Vector diagram for star connected network.

The potential difference between outers R any Y is

$$E_{RY} = E_R - E_Y \quad \text{[vector difference]}$$

or

$$E_{RY} = E_R + (-E_Y) \quad \text{[vector sum]}$$

Hence, E_{RY} is found by compounding E_R and E_Y reversed and its value is given by the diagonal of the parallelogram (Fig. 6). Obviously the angle between E_R and E_Y reversed is 60° and the value of

$$E_{RY}(\text{or } E_L) = \sqrt{E_R^2 + E_Y^2 + 2E_R E_Y \cos 60^\circ} = \sqrt{E_{ph}^2 + E_{ph}^2 + 2E_{ph} \times E_{ph} \times \frac{1}{2}} = \sqrt{3} E_{ph}$$

Similarly

$$E_{YB}(= E_L) = E_Y - E_B = \sqrt{3} E_{ph}$$

and

$$E_{BR}(= E_L) = E_B - E_R = \sqrt{3} E_{ph}$$

i.e.

$$E_{RY} = E_{YB} = E_{BR} = E_L = \sqrt{3} E_{ph}$$

Hence,

$$E_L = \sqrt{3} E_{ph}$$

...(1)

(i.e. Line voltage = $\sqrt{3}$ phase voltage).

(b) Relation between Line Currents and Phase Currents. Since in star-connected system each line conductor is connected to separate phase, so the current flowing through the line and phase are same.

Current in outer (or line) $R = I_R$

Current in outer $Y = I_Y$

Current in outer $B = I_B$

Since

 $I_R = I_Y = I_B = \text{say, } I_{ph}$ —the phase current

∴ Line current,

$$I_L = I_{ph}$$

...(2)

(c) Power. If the phase current has a phase difference of ϕ with phase voltage,

Power per phase

$$= E_{ph} I_{ph} \cos \phi$$

Total power (true),

$$P = 3 \times \text{power per phase}$$

$$P = 3 \times E_{ph} I_{ph} \cos \phi$$

...(3)

Now

$$E_{ph} = \frac{E_L}{\sqrt{3}} \quad \text{and} \quad I_{ph} = I_L$$

Hence in terms of line values, the above expression becomes

$$P = 3 \times \frac{E_L}{\sqrt{3}} I_L \cos \phi$$

or

$$P = \sqrt{3} E_L I_L \cos \phi \quad \dots(4)$$

(Apparent power $= \sqrt{3} E_L I_L$).

In a balanced star-connected net work the following points are worthnoting :

- (i) Line voltages are $\sqrt{3}$ times the phase voltages.
- (ii) Line currents are equal to phase currents.
- (iii) Line voltages are 120° apart.
- (iv) Line voltages are 30° ahead of the respective phase voltages.
- (v) The angle between line currents and the corresponding line voltages is $(30^\circ \pm \phi)$ + for lagging currents – ve for leading currents.
- (vi) True power $= \sqrt{3} E_L I_L \cos \phi$, where ϕ is the angle between respective phase current and phase voltage, not between the line current and line voltage.
- (vii) Apparent power $= \sqrt{3} E_L I_L$.
- (viii) In balance system, the potential of the neutral or star point is zero.
 \therefore Potential at neutral (or star) point $= E_{NR} + E_{NY} + E_{NB} = 0$.

Star or Wye Connection

Example 1. A balanced star connected load of $(8 + j6) \Omega/\text{phase}$ is connected to a 3-phase, 230 volts, 50 Hz supply. Find the current, p.f., power, volt ampere and reactive power. Draw the phasor diagram for the above circuit. (PTU, 1999)

Solution. Given : $R = 8 \Omega$; $X_L = 6 \Omega$; $E_L = 230$ volts, $f = 50$ Hz.

The circuit is shown in Fig. 7 (a).

Phase voltage, $E_{ph} = \frac{E_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} = 132.8 \text{ V}$

Impedance, $Z = \sqrt{R^2 + X_L^2} = \sqrt{8^2 + 6^2} = 10 \Omega$

Current, $I_{ph} = I_L = \frac{E_{ph}}{Z} = \frac{132.8}{10} = 13.28 \text{ A. (Ans.)}$

Power factor, $\cos \phi = \frac{R}{Z} = \frac{8}{10} = 0.8. \text{ (Ans.)}$ $(\therefore \phi = \cos^{-1}(0.8) = 36.87^\circ)$

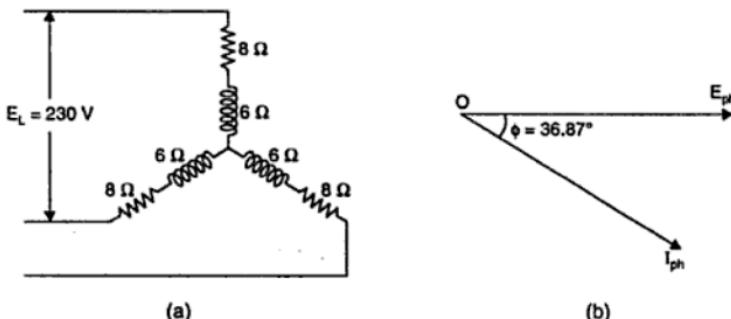


Fig. 7

Power,

$$P = \sqrt{3} E_L J_L \cos \phi \\ = \sqrt{3} \times 230 \times 13.28 \times 0.8 = 4342.3 \text{ W. (Ans.)}$$

Apparent power

$$= \sqrt{3} E_L J_L = \sqrt{3} \times 230 \times 13.28 = 5290.4 \text{ VA. (Ans.)}$$

Reactive power

$$= \sqrt{3} E_L J_L \sin \phi = \sqrt{3} \times 230 \times 13.28 \times \sin(36.87^\circ) \\ = 3174 \text{ VAR. (Ans.)}$$

The phasor diagram is shown in Fig. 7 (b).

Example 2. Three equal impedances each having a resistance of 25Ω and reactance of 40Ω are connected in star to a 400 V , $3\text{-phase}, 50 \text{ Hz}$ system. Calculate :

(i) The line current

(ii) Power factor, and

(iii) Power consumed.

Solution. Resistance per phase, $R_{ph} = 25 \Omega$ Reactance per phase, $X_{ph} = 40 \Omega$ Line voltage, $E_L = 400 \text{ V}$ **Line current, I_L :****Power factor, $\cos \phi$:****Power consumed, P :**

Refer Fig. 8.

Impedance per phase, $Z_{ph} = \sqrt{R_{ph}^2 + X_{ph}^2}$

$$\therefore Z_{ph} = \sqrt{25^2 + 40^2} = 47.17 \Omega$$

Phase voltage, $E_{ph} = \frac{E_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$ Phase current, $I_{ph} = \frac{E_{ph}}{Z_{ph}} = \frac{231}{47.17} = 4.9 \text{ A (app.)}$ **(i) Line current,** $I_L = \text{phase current, } I_{ph}$ \therefore

$$I_L = 4.9 \text{ A. (Ans.)}$$

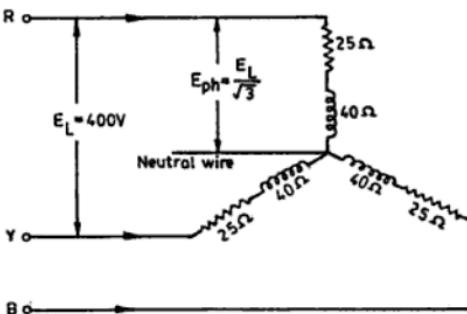


Fig. 8

(ii) Power factor, $\cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{95}{47.17} = 0.53$ (lag). (Ans.)

(iii) Power consumed, $P = \sqrt{3} E_L I_L \cos \phi = \sqrt{3} \times 400 \times 4.9 \times 0.53 = 1800$ W (app.). (Ans.)

[or $P = 3I_{ph}^2 R_{ph} = 3 \times 4.9^2 \times 25 = 1800$ W.]

Example 3. Three identical coils are connected in star to a 400 V (line voltage), 3-phase A.C. supply and each coil takes 300 W. If the power factor is 0.8 (lagging). Calculate :

(i) The line current, (ii) Impedance, and

(iii) Resistance and inductance of each coil.

Solution. Line voltage, $E_L = 400$ V

Power taken by each coil, $P_{ph} = 300$ W

Power factor, $\cos \phi = 0.8$ (lagging)

I_L ; Z ; R_{ph} ; L_{ph} :

Phase voltage, $E_{ph} = \frac{E_L}{\sqrt{3}} = \frac{400}{\sqrt{3}}$ V

Also $P_{ph} = E_{ph} I_{ph} \cos \phi$

$$300 = \frac{400}{\sqrt{3}} \times I_{ph} \times 0.8$$

$$\therefore I_{ph} = \frac{300 \times \sqrt{3}}{400 \times 0.8} = 1.62 \text{ A.}$$

(i) **Line current,** $I_L = \text{phase current, } I_{ph}$

$$I_L = 1.62 \text{ A. (Ans.)}$$

(ii) **Coil impedance,** $Z_{ph} = \frac{400}{I_{ph}}$

$$Z_{ph} = \frac{400}{1.62} = \frac{\sqrt{3}}{1.62} = 142.5 \Omega$$

$$\therefore Z_{ph} = 142.5 \Omega. \text{ (Ans.)}$$

(iii) $R_{ph} = Z_{ph} \cos \phi = 142.5 \times 0.8 = 114 \Omega$

Coil reactance, $X_{ph} = Z_{ph} \sin \phi = 142.5 \times 0.6 = 85.5 \Omega \text{ (Ans.)}$

But

$$X_{ph} = 2\pi f L_{ph}$$

$$\therefore L_{ph} = \frac{X_{ph}}{2\pi f} = \frac{85.5}{2\pi \times 50} = 0.272 \text{ H.}$$

$$\text{Hence, } R_{ph} = 114 \Omega. \text{ (Ans.)}$$

and

$$L_{ph} = 0.272 \text{ H. (Ans.)}$$

Example 4. In a 3-phase, 3-wire system with star-connected load the impedance of each phase is $(3 + j4) \Omega$. If the line voltage is 230 V, calculate :

(i) The line current, and

(ii) The power absorbed by each phase.

Solution. Line voltage, $E_L = 230 \text{ V}$

Resistance per phase, $R_{ph} = 3 \Omega$

Reactance per phase, $X_{ph} = 4 \Omega$

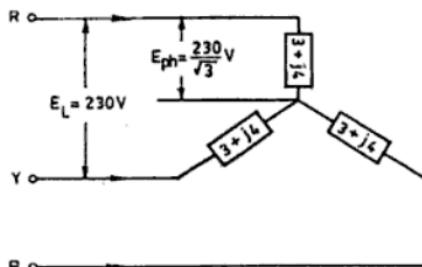


Fig. 9

I_L ; P_{ph} :

Phase voltage, $E_{ph} = \frac{E_L}{\sqrt{3}} = \frac{230}{\sqrt{3}} \text{ V}$

Impedance per phase, $Z_{ph} = \sqrt{R_{ph}^2 + X_{ph}^2} = \sqrt{3^2 + 4^2} = 5 \Omega$

Power factor, $\cos \phi = \frac{R}{Z} = \frac{3}{5} = 0.6$

Phase current, $I_{ph} = \frac{E_{ph}}{Z_{ph}} = \frac{230}{\sqrt{3} \times 5} = 26.56 \text{ A}$

Line current, $I_L = I_{ph} = 26.56 \text{ A. (Ans.)}$

Power absorbed by each phase,

$$P_{ph} = E_{ph} I_{ph} \cos \phi = \frac{230}{\sqrt{3}} \times 26.56 \times 0.6 = 2116 \text{ W (Ans.)}$$

$$[P_{ph} = I_{ph}^2 R_{ph} = 26.56^2 \times 3 = 2116 \text{ W}]$$

Solution by Symbolic Notation. In Fig. 10 E_R , E_Y and E_B are the phase voltages whereas I_R , I_Y and I_B are phase currents.

Taking E_R as the reference vector, we get

$$E_R = \frac{230}{\sqrt{3}} \angle 0^\circ = 133 \angle 0^\circ = 133 + j0 \text{ volt}$$

$$E_Y = 133 \angle -120^\circ = 133 (-0.5 - j0.866) = (-66.5 - j115) \text{ volts}$$

$$E_B = 133 \angle 120^\circ = 133 (-0.5 + j0.866) = (-66.5 + j115) \text{ volts}$$

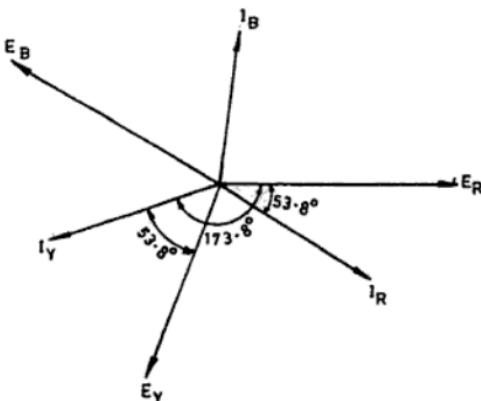


Fig. 10

$$Z = 3 + j4 = 5 \angle 53^\circ 8'$$

$$I_R = \frac{E_R}{Z} = \frac{133 \angle 0^\circ}{5 \angle 53^\circ 8'} = 26.6 \angle -53^\circ 8'$$

This current lags behind the reference voltage (E_R) by $53^\circ 8'$ (Fig. 10).

$$I_Y = \frac{E_Y}{Z} = \frac{133 \angle -120^\circ}{5 \angle 53^\circ 8'} = 26.6 \angle -173^\circ 8'$$

It lags the reference vector i.e., E_R by $173^\circ 8'$ which amounts to lagging behind its phase voltage E_Y by $53^\circ 8'$,

$$I_B = \frac{E_B}{Z} = \frac{133 \angle 120^\circ}{5 \angle 53^\circ 8'} = 26.6 \angle 66^\circ 52'$$

This current leads E_R by $66^\circ 52'$ which is the same as lagging behind its phase voltage by $53^\circ 8'$.

Let us consider R-phase for calculation of power

$$E_R = (133 + j0); I_R = 26.6 (0.6 - j0.8) = (15.96 - j21.28)$$

Using method of conjugates, we get

$$P_{VA} = (133 - j0)(15.96 - j21.28) = 2116 - j2830$$

\therefore Real power absorbed/phase = 2116 W ... (As before)

Example 5. A star-connected, 6000 V, 3-phase alternator is supplying 4000 kW at a power factor of 0.8. Calculate the active and reactive components of the current in each phase.

Solution. Line voltage, $E_L = 6000$ V

Power supplied, $P = 4000$ kW

Power factor, $\cos \phi = 0.8$

Active and reactive components of current :

We know that, $P = \sqrt{3} E_L I_L \cos \phi$

$$4000 \times 1000 = \sqrt{3} \times 6000 \times I_L \times 0.8$$

i.e., $I_L = \frac{4000 \times 1000}{\sqrt{3} \times 6000 \times 0.8} = 481 \text{ A}$

$\therefore I_{ph} = I_L = 481 \text{ A}$

Active component $= I_{ph} \cos \phi = 481 \times 0.8 = 384.8 \text{ A. (Ans.)}$

Reactive component $= I_{ph} \sin \phi = 481 \times 0.6 = 288.6 \text{ A. (Ans.)}$

Example 6. A balanced 3-phase star connected load of 100 kW takes a leading current of 80 A when connected across a 3-phase, 1100 V, 50 Hz supply. Find the circuit constants of the load per phase.

Solution. Given : $P = 100 \text{ kW}$; $I_{ph} (= I_L) = 80 \text{ A}$; $E_L = 1100 \text{ V}$; $f = 50 \text{ Hz}$

Circuit constants of the load per phase, R, C :

As the 3- ϕ load is balanced and star connected, line or phase current,

$$I_L = (I_{ph}) = \frac{P}{\sqrt{3} E_L \cos \phi} = \frac{100 \times 10^3}{\sqrt{3} \times 1100 \times \cos \phi}$$

or

$$\cos \phi = \frac{100 \times 10^3}{\sqrt{3} \times 1100 \times 80} = 0.656$$

Load impedance,

$$Z = \frac{E_{ph}}{I_{ph}} = \frac{(1100/\sqrt{3})}{80} = 7.94 \Omega$$

\therefore

$$R = Z \cos \phi = 7.94 \times 0.656 = 5.2 \Omega. \text{ (Ans.)}$$

Now $X_C = \frac{1}{2\pi f C}$ as the current given is leading current.

\therefore

$$C = \frac{1}{2\pi f X_C}$$

But

$$X_C = Z \sin \phi = 7.94 \times 0.755 = 5.99 \Omega$$

\therefore


$$C = \frac{1}{2\pi \times 50 \times 5.99} F$$

$$= \frac{10^6}{2\pi \times 50 \times 5.99} \mu F = 531.4 \mu F. \text{ (Ans.)}$$


Example 7. A 3-phase, star-connected system with 230 V between each phase and neutral has resistances of 8, 10 and 20 Ω respectively in three phases, calculate :

- (i) The current flowing in each phase, (ii) The neutral current, and
 (iii) The total power absorbed.

Solution. Refer Figs. 11 (a) and (b).

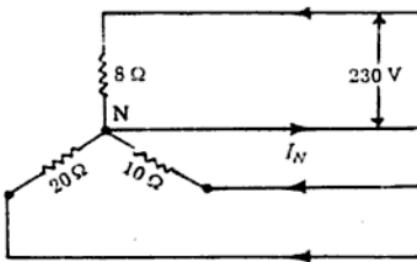

(a)

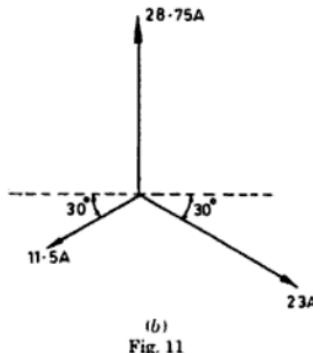

Phase voltage, $E_{ph} = 230 \text{ V}$

$$(i) \text{ Current in } 8 \Omega \text{ resistor} = \frac{230}{8} = 28.75 \text{ A. (Ans.)}$$

$$\text{Current in } 10 \Omega \text{ resistor} = \frac{230}{10} = 23 \text{ A. (Ans.)}$$

$$\text{Current in } 12 \Omega \text{ resistor} = \frac{230}{20} = 11.5 \text{ A. (Ans.)}$$

(ii) The above currents are mutually displaced by 120° . The neutral current I_N is the vector sum of these three currents.

I_N can be found by splitting up these three-phase currents into their X-components and Y-components and then by combining them together.

$$\Sigma \text{X-components} = 23 \cos 30^\circ - 11.5 \cos 30^\circ = 11.5 \cos 30^\circ = 9.96 \text{ A}$$

$$\Sigma \text{Y-components} = 28.75 - 23 \sin 30^\circ - 11.5 \sin 30^\circ = 28.75 - 34.5 \sin 30^\circ = 11.5 \text{ A}$$

$$\therefore \text{Neutral current, } I_N = \sqrt{(9.96)^2 + (11.5)^2} = 15.21 \text{ A. (Ans.)}$$

(iii) Total power absorbed,

$$P = 230 (28.75 + 23 + 11.5) = 14547.5 \text{ W. (Ans.)}$$

7. DELTA (Δ) OR MESH CONNECTION

In a delta or mesh connection the *dissimilar* ends of the three-phase windings are joined together i.e. the 'starting' end of one phase is joined to the 'finishing' end of the other phase and so on as shown in Fig. 12. In other words, the three windings are joined in series to form a closed mesh. Three leads are taken out from the junctions as shown and outward directions are taken as positive.


(a) Relation between line voltages and phase voltages :

Since in delta or mesh connected system, only one phase is included between any pair of line outers, therefore potential difference between the line outers, called the *line voltage*, is equal to phase voltage.

i.e., Line voltage, E_L = phase voltage, E_{ph} .

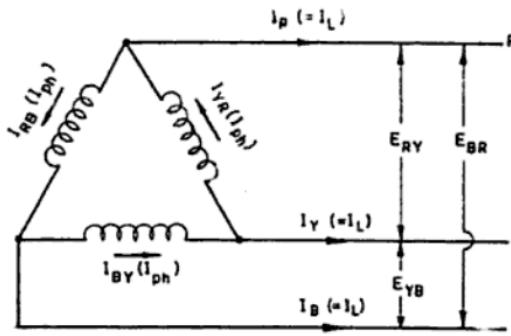(b) Relation between line currents and phase currents :

From Fig. 12 it is obvious that line current is the vector difference of phase currents of two phases concerned.



$$E_{RY} = E_{YB} = E_{BR} = E_{ph} = E_L$$

$$I_R = I_Y = I_B = I_L (\approx \sqrt{3} I_{ph})$$

Fig. 12. Delta or mesh connected diagram.

Thus, line current,

$$I_R = I_{YR} - I_{RB}$$

$$= I_{YR} + (-I_{RB})$$

(Vector difference)
(Vector sum)

Similarly,

$$I_Y = I_{BY} - I_{YR} \quad \text{and} \quad I_B = I_{RB} - I_{BY}$$

Refer Fig. 13. Since phase angle between phase current I_{YR} and $-I_{RB}$ is 60° ,

$$\therefore I_R = \sqrt{I_{YR}^2 + I_{RB}^2 + 2I_{YR}I_{RB} \cos 60^\circ}$$

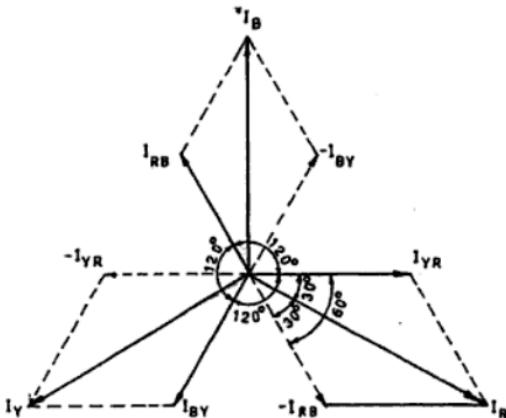


Fig. 13. Vector diagram for delta connected net work.

Assuming the delta connected system or network be balanced, the phase current in each winding is equal and let each be equal to I_{ph} (i.e., $I_{YR} = I_{BY} = I_{RB} = I_{ph}$)

$$\therefore I_R (= I_L) = \sqrt{I_{ph}^2 + I_{ph}^2 + 2I_{ph}I_{ph} \cos 60^\circ} = \sqrt{2I_{ph}^2 + 2I_{ph}^2 \times \frac{1}{2}} = \sqrt{3} I_{ph}$$

Similarly, $I_Y = I_B = \sqrt{3} I_{ph}$

Hence, $I_L = \sqrt{3} I_{ph}$

(i.e., line current = $\sqrt{3}$ phase current)

(c) Power :

Power/phases $= E_{ph} I_{ph} \cos \phi$

Total power (true) $P = 3E_{ph} I_{ph} \cos \phi$

But $E_{ph} = E_L$ and $I_{ph} = \frac{I_L}{\sqrt{3}}$

Hence, in terms of line values, the above expression for power becomes

$$P = 3 \times E_L \times \frac{E_L}{\sqrt{3}} \cos \phi$$

$$P = \sqrt{3} E_L I_L \cos \phi$$

or

where ϕ = the phase power factor angle.

(Apparent power = $\sqrt{3} E_L I_L$)

In case of delta or mesh connected system the following points are worth noting :

(i) Line voltages are equal to phase voltages.

(ii) Line currents are $\sqrt{3}$ times phase currents.

(iii) Line currents are 120° apart.

(iv) Line currents are 30° behind their respective phase currents.

(v) The angle between line currents and corresponding line voltages is $(30^\circ \pm \phi)$ as in the star system.

(vi) True power = $\sqrt{3} E_L I_L \cos \phi$, where ϕ is the phase angle between respective phase current and phase voltage.

(vii) Apparent power = $\sqrt{3} E_L I_L$.

(viii) In balanced system, the resultant e.m.f. in the closed circuit will be zero.

i.e., $E_{RY} + E_{YB} + E_{BR} = 0$.

Hence, there will no circulating current in the mesh if no-load is connected to the lines.

8. COMPARISON BETWEEN STAR AND DELTA SYSTEMS

The comparison between star and delta connected systems is given below :

Star connected system	Delta connected system
<ol style="list-style-type: none"> Similar ends are joined together. Phase voltage = $\frac{1}{\sqrt{3}}$ line voltage $\left(\text{i.e., } E_{ph} = \frac{E_L}{\sqrt{3}} \right)$ Phase current = line current (i.e., $I_{ph} = I_L$). Possible to carry neutral to the load. Provides 3-phase 4-wire arrangement. Can be used for lighting as well as power load. Neutral wire of a star connected alternator can be connected to earth, so relays and protective devices can be provided in the star connected alternators for safety. 	<ol style="list-style-type: none"> Dissimilar ends are joined. Phase voltage = line voltage (i.e., $E_{ph} = E_L$). Phase current = $\frac{1}{\sqrt{3}} \times$ line current $\left(\text{i.e., } I_{ph} = \frac{I_L}{\sqrt{3}} \right)$ Neutral wire not available. Provides 3-phase 3-wire arrangement. Can be used for power loads only. Not possible. <p>Delta connected system is mostly used in transformer for running of small low voltage 3-phase motors and best suited for rotary converters.</p>

Delta or Mesh Connection

Example 8. Three identical coils connected in delta across 400 V, 50 Hz, 3-phase supply take a line current of 15 A at a power factor 0.8 lagging. Calculate :

- The phase current, and
- The impedance, resistance and inductance of each winding.

Solution. Line voltage, $E_L = 400 \text{ V}$

Line current, $I_L = 15 \text{ A}$

Power factor, $\cos \phi = 0.8$ lagging

I_{ph} ; Z_{ph} ; R_{ph} ; L :

Phase voltage, $E_{ph} = E_L = 400 \text{ V}$

$$(i) \text{ Phase current, } I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{15}{\sqrt{3}} = 8.66 \text{ A. (Ans.)}$$

$$(ii) \text{ Impedance of each phase, } Z_{ph} = \frac{E_{ph}}{I_{ph}} = \frac{400}{8.66} = 46.19 \Omega. \text{ (Ans.)}$$

$$\text{Resistance of each phase, } R_{ph} = Z_{ph} \cos \phi = 46.19 \times 0.8 = 36.95 \Omega. \text{ (Ans.)}$$

$$\begin{aligned} \text{Reactance of each phase, } X_{ph} &= Z_{ph} \sin \phi = 46.19 \sqrt{1 - \cos^2 \phi} \\ &= 46.19 \sqrt{1 - (0.8)^2} = 27.71 \Omega \end{aligned}$$

$$\therefore \text{ Inductance, } L = \frac{X_{ph}}{2\pi f} = \frac{27.71}{2\pi \times 50} = 0.088 \text{ H. (Ans.)}$$

Example 9. A 220 V, 3-phase voltage is applied to a balanced delta-connected 3-phase load of phase impedance $(6 + j8)$.

- Find the phasor current in each line.

- What is the power consumed per phase?

- What is the phasor sum of the three line currents? What does it have this value?

Solution. Refer Fig. 14.

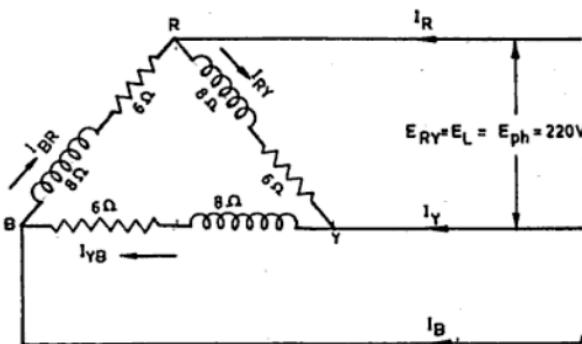


Fig. 14

Resistance per phase,

$$R_{ph} = 6 \Omega$$

Reactance per phase,

$$X_{ph} = 8 \Omega$$

$$E_L = E_{ph} = 220 \text{ V}$$

Impedance per phase, $Z_{ph} = \sqrt{R_{ph}^2 + X_{ph}^2} = \sqrt{6^2 + 8^2} = 10 \Omega$

(i) Phase current, $I_{ph} = \frac{E_{ph}}{Z_{ph}} = \frac{220}{10} = 22 \text{ A}$

∴ Line current, $I_L = \sqrt{3} \times 22 = 38.1 \text{ A. (Ans.)}$

(ii) Power consumed per phase,

$$P_{ph} = I_{ph}^2 \times R_{ph} = 22^2 \times 6 = 2904 \text{ W. (Ans.)}$$

(iii) Phasor sum would be zero because the three currents are equal in magnitudes and have a mutual phase difference of 120° .

Solution by Symbolic Notation. Let E_{RY} is taken as a reference vector (Fig. 15).

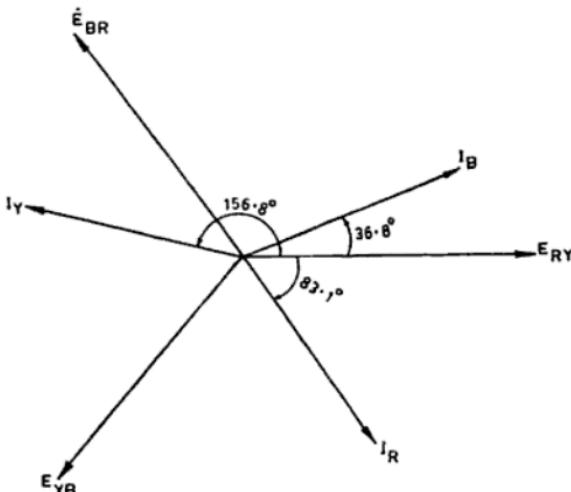


Fig. 15

$$E_{RY} = 220 \angle 0^\circ, E_{YB} = 220 \angle -120^\circ$$

$$E_{BR} = 220 \angle 120^\circ, Z = 6 + j8 = 10 \angle 53^\circ 8'$$

$$I_{RY} = \frac{E_{RY}}{Z} = \frac{220 \angle 0^\circ}{10 \angle 53^\circ 8'} = 22 \angle -53^\circ 8' = (13.22 - j17.6) \text{ A}$$

$$I_{YB} = \frac{E_{YB}}{Z} = \frac{220 \angle -120^\circ}{10 \angle 53^\circ 8'} = 22 \angle -173^\circ 8' = (-21.84 - j2.63)$$

$$I_{BR} = \frac{E_{BR}}{Z} = \frac{220 \angle 120^\circ}{10 \angle 53^\circ 8'} = 22 \angle 66^\circ 52' = (8.64 + j20.23)$$

(i) Current in each line :

$$I_R = I_{RY} - I_{BR} = (13.22 - j17.6) - (8.64 + j20.23) = 4.58 - j37.83 = 38.1 \angle 83.1^\circ. \text{ (Ans.)}$$

$$I_Y = I_{YB} - I_{RY} = (-21.84 - j2.63) - (13.22 - j17.6)$$

$$= -21.84 - j2.63 - 13.22 + j17.60 = -35.06 + j14.97 = 38.12 \angle 156.8^\circ. \text{ (Ans.)}$$

$$I_B = I_{BR} - I_{YB} = (8.64 + j20.23) - (-21.84 + j2.63) = 8.64 + j20.23 + 21.84 + j2.63 \\ = 30.48 + j22.86 = 38.1 \angle 36.8^\circ. \text{ (Ans.)}$$

(ii) Power consumed per phase :

Using conjugate of voltage, we get for *R*-phase

$$P_{VA} = E_{RY} \cdot I_{RY} = (220 - j0)(13.22 - j17.6) = (2908.4 - j3872) \text{ volt ampere}$$

True power per phase = 2.908 kW. (Ans.)

(iii) Phase sum of the three line currents

$$\begin{aligned} &= I_R + I_Y + I_B \\ &= (4.58 - j37.83) + (-35.06 + j14.96) + (30.48 + j22.86) = 0 \end{aligned}$$

Hence, the phasor sum of three line currents drawn by a 'balanced load' is zero. (Ans.)

Example 10. A delta-connected balanced 3-phase load is supplied from a 3-phase, 400 V supply. The line current is 30 A and the power taken by the load is 12 kW. Find :

(i) Impedance in each branch ; and

(ii) The line current, power factor and power consumed if the same load is connected in star.

Solution. Delta-connection :

$$E_{ph} = E_L = 400 \text{ V}$$

$$I_L = 30 \text{ A}$$

$$\therefore I_{ph} = \frac{I_L}{\sqrt{3}} = \frac{30}{\sqrt{3}} = 17.32 \text{ A.}$$

(i) Impedance per phase

$$Z_{ph} = \frac{E_{ph}}{I_{ph}} = \frac{400}{17.32} = 23.09 \Omega. \text{ (Ans.)}$$

Now

$$P = \sqrt{3} E_L I_L \cos \phi$$

$$12000 = \sqrt{3} \times 400 \times 30 \times \cos \phi.$$

$$\text{or } \cos \phi \text{ (power factor)} = \frac{12000}{\sqrt{3} \times 400 \times 30} = 0.577$$

(ii) Star-connection

$$E_{ph} = \frac{E_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$$

$$I_L = I_{ph} = \frac{E_{ph}}{Z_{ph}} = \frac{231}{23.09} = 10 \text{ A. (Ans.)}$$

Power factor, $\cos \phi = 0.577$ (since impedance is same)

Power consumed $= \sqrt{3} E_L I_L \cos \phi = \sqrt{3} \times 400 \times 10 \times 0.577 = 3997.6 \text{ W. (Ans.)}$

Example 11. Three 50 Ω non-inductive resistances are connected in (i) star, (ii) delta across a 400 V, 50 Hz., 3-phase mains. Calculate the power taken from the supply system in each case. In the event of one of the three resistances getting opened, what would be the value of the total power taken from the mains in each of the two cases.

Solution. Star connection :

$$\text{Phase voltage, } E_{ph} = \frac{E_L}{\sqrt{3}} = \frac{400}{\sqrt{3}} = 231 \text{ V}$$

$$\text{Phase current, } I_{ph} = \frac{E_{ph}}{R_{ph}} = \frac{231}{50} = 4.62 \text{ A}$$

$$\text{Power consumed, } P = 3I_{ph}^2 R_{ph} = 3 \times 4.62^2 \times 50 = 3200 \text{ W. (Ans.)}$$

$$[\text{or } P = \sqrt{3} E_L I_L \cos \phi = \sqrt{3} \times 400 \times 4.62 \times 1 = 3200 \text{ W}]$$

Delta connection :

Phase voltage, $E_{ph} = E_L = 400 \text{ V}$

$$\text{Phase current, } I_{ph} = \frac{E_{ph}}{R_{ph}} = \frac{400}{50} = 8 \text{ A}$$

$$\text{Power consumed, } P = 3I_{ph}^2 R_{ph} = 3 \times 8^2 \times 50 = 9600 \text{ W. (Ans.)}$$

When one of the resistances is disconnected :

(i) **Star connection.** Refer Fig. 16.

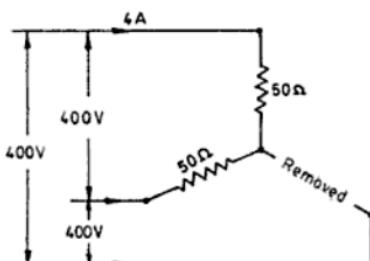


Fig. 16

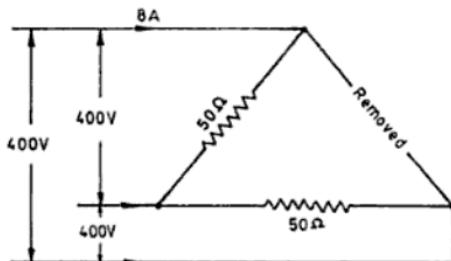


Fig. 17

When one of the resistances is disconnected, the circuit is no longer 3-phase but converted into single-phase circuit, having two resistances each of 50 ohm connected in series across supply of 400 V.

$$\text{Hence line current, } I_L = \frac{E_L}{2R_{ph}} = \frac{400}{2 \times 50} = 4 \text{ A}$$

$$\text{Power consumed, } P = 4^2 (50 + 50) = 1600 \text{ W. (Ans.)}$$

$$[\text{or } P = VI \cos \phi = 400 \times 4 \times 1 = 1600 \text{ W.}]$$

(ii) **Delta connection.** Refer Fig. 17.

Potential difference across each resistance, $E_{ph} = 400 \text{ V}$

$$\text{Current in each resistance} = \frac{400}{50} = 8 \text{ A}$$

$$\text{Power consumed in both resistances} = 2 \times 8^2 \times 50 = 6400 \text{ W. (Ans.)}$$

$$[\text{or } P = 2 \times E_{ph} I_{ph} \cos \phi = 2 \times 400 \times 8 \times 1 = 6400 \text{ W.}]$$

Example 12. The secondary of a 3-phase star-connected transformer, which has a phase voltage of 230 V feeds a 3-phase delta connected load; each phase of which has a resistance of 30 Ω and an inductive reactance of 40 Ω . Draw the circuit diagram of the system and calculate :

- (i) The voltage across each phase of load,
- (ii) The current in each phase of load,
- (iii) The current in the transformer secondary windings, and
- (iv) The total power taken from the supply and its power factor.

Solution. Refer Fig. 18.

$$\text{Resistance per phase, } R_{ph} = 20 \Omega$$

$$\text{Reactance per phase, } X_{ph} = 40 \Omega$$

Phase voltage across transformer secondary,

$$E_{ph} = 230 \text{ V}$$

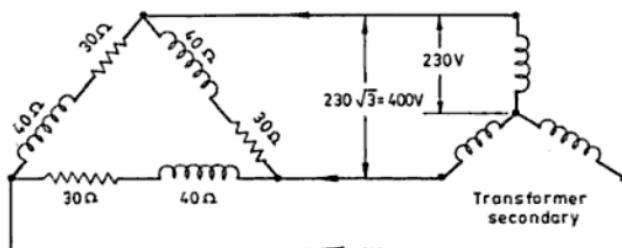


Fig. 18

Line voltage across delta connected load = line voltage across transformer secondary
 $= \sqrt{3} \times 230 = 400$ V (app.)

(i) Voltage across each phase of the load,

$$E_{ph} = E_L = 400 \text{ V. (Ans.)}$$

(ii) Current in each phase of the load,

$$I_{ph} = \frac{E_{ph}}{Z_{ph}} = \frac{400}{\sqrt{R_{ph}^2 + X_{ph}^2}} = \frac{400}{\sqrt{30^2 + 40^2}} = \frac{400}{50} = 8 \text{ A. (Ans.)}$$

(iii) Current in the transformer secondary

$$= \text{line current of load} = \sqrt{3} \times I_{ph} = \sqrt{3} \times 8 = 13.86 \text{ A. (Ans.)}$$

(iv) Power factor, $\cos \phi = \frac{R_{ph}}{Z_{ph}} = \frac{30}{50} = 0.6.$ (Ans.)

Total power consumed, $P = \sqrt{3} E_L I_L \cos \phi = \sqrt{3} \times 400 \times 13.86 \times 0.6 = 5761.5 \text{ W. (Ans.)}$

9. MEASUREMENT OF POWER IN 3-PHASE CIRCUIT

- The power in 3-phase load can be measured by using the following methods :
 1. Three wattmeters method.
 2. Two wattmeters method.
 3. One wattmeter method.
- A wattmeter consists of two coils : Refer Fig. 19.
 1. *Current coil—possesses a low resistance.*
 2. *Pressure or potential coil—possesses a high resistance.*

The 'current coil' is connected in series with the line carrying the current and the 'pressure coil' is connected across the two points whose potential difference is to be measured. A wattmeter shows a reading which is proportional to the product of the current through its current coil, the potential difference across its pressure coil and cosine of the angle between this voltage and current.

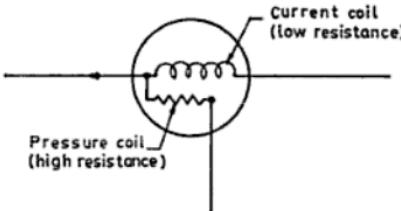


Fig. 19. Connections of a wattmeter.

9.1. Three-wattmeters Method. Figs. 20 and 21 show the connection diagram for star-connected and delta-connected loads respectively. As indicated in the figures three wattmeters are connected in each of the three phases of the load whether star or delta connected. The current coil of each wattmeter carries the current of one phase only and the pressure coil measures the

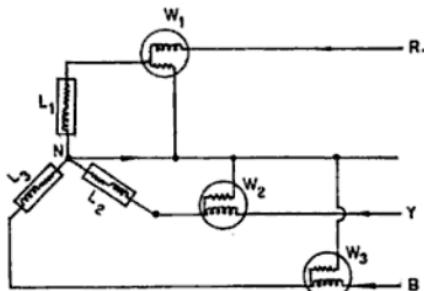


Fig. 20. Star-connected load.

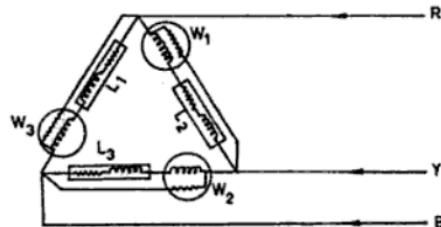


Fig. 21. Delta-connected load.

phase-voltage of the phase. Hence, each wattmeter measures the power in a single phase. The total power in the load is given by the algebraic sum of the readings of the three wattmeters.

While using this method following difficulty is met with :

- In case of star-connected load it is not always possible to get at neutral point which is required for connections (Fig. 20).
- In case of delta-connected load, under ordinary conditions it is not generally feasible to break into the phases of the load.

To measure power it is not necessary to use three wattmeters, two wattmeters can be used for the purpose as explained in the Article 9.2.

9.2. Two-wattmeters Method. Balanced or unbalanced load, Figs. 22 and 23 show connection diagrams for star-connected and delta-connected loads respectively. In this method the current coils of the two wattmeters are inserted in *any two lines* and the pressure (or potential) coil of each joined to the *third line*.

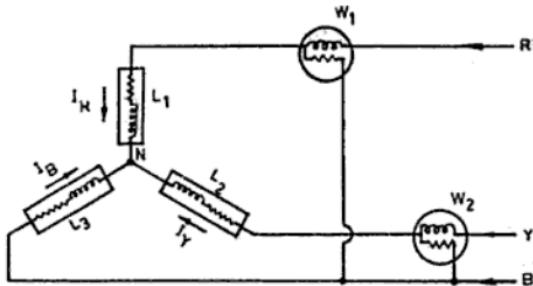


Fig. 22. Star-connected load.

It can be proved that the sum of the instantaneous powers indicated by W_1 and W_2 gives the instantaneous power absorbed by the three loads L_1 , L_2 and L_3 . Let us consider a star-connected load (although it can be equally applied to a delta-connected load which can always be replaced by an equivalent star-connected load).

Keeping in mind that it is important to take the direction of the voltage through the circuit as the same as that taken for the current when establishing the readings of the two wattmeters.

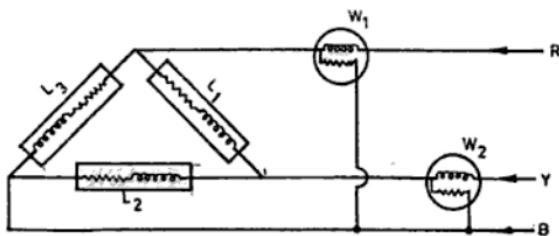


Fig. 23. Delta-connected load.

Instantaneous current through $W_1 = i_R$

Instantaneous potential difference across $W_1 = e_{RB} = e_R - e_B$

Instantaneous power read by $W_1 = i_R(e_R - e_B)$

Instantaneous current through $W_2 = i_Y$

Instantaneous potential difference across $W_2 = e_{YB} = e_Y - e_B$

Instantaneous power read by $W_2 = i_Y(e_Y - e_B)$

$$\therefore W_1 + W_2 = i_R(e_R - e_B) + i_Y(e_Y - e_B) = i_Re_R + i_Ye_Y - e_B(i_R + i_Y)$$

Now according to Kirchhoff's point law

$$i_R + i_Y + i_B = 0$$

$$\therefore i_R + i_Y = -i_B$$

$$\therefore W_1 + W_2 = i_Re_R + i_Ye_Y + i_Be_B = p_1 + p_2 + p_3$$

where p_1 = power absorbed by load L_1 , p_2 = power absorbed by load L_2 , and

p_3 = power absorbed by load L_3 .

$$\therefore W_1 + W_2 = \text{total power absorbed.}$$

This proof is true whether the load is *balanced* or *unbalanced*.

In case the load is star-connected, then it should have no neutral connection (*i.e.*, 3-phase, 3-wire connected) and if it has a neutral connection (*i.e.*, 3-phase, 4-wire connected) that it should be exactly balanced so that in each case there is no neutral current i_N otherwise Kirchhoff's point law will give $i_R + i_Y + i_B + i_N = 0$.

In the above derivation we have considered the *instantaneous* readings. In fact the moving system wattmeter, due to its inertia, cannot quickly follow the variations taking place in cycle, hence it indicates the *average power*.

$$\begin{aligned} \therefore \text{Total power} &= W_1 + W_2 \\ &= \frac{1}{T} \int_0^T i_Re_{RB} dt + \frac{1}{T} \int_0^T i_Ye_{YB} dt. \end{aligned} \quad \dots(7)$$

Two-wattmeter Method—Balanced load. The total power consumed by a *balanced load* can be found by using two wattmeters (Figs. 22 and 21). When load is assumed inductive in Fig. 20, the vector diagram for such a balanced star-connected load is shown in Fig. 24.

Let us consider the problem in terms of r.m.s. values (instead of instantaneous values).

Let E_R, E_Y, E_B = r.m.s. values of the three phase voltages,

and I_R, I_Y, I_B = r.m.s. values of the currents.

Since these voltages and currents are assumed sinusoidal, they can be represented by vectors, the currents lagging behind their respective phase voltages by 90° .

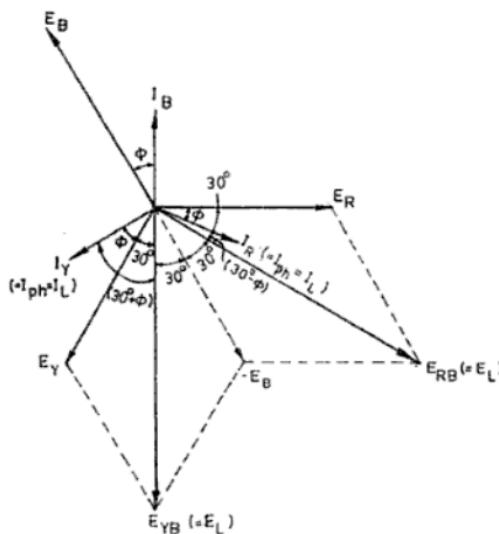


Fig. 24. Vector diagram—two wattmeters method.

Refer Fig. 24.

Current through wattmeter $W_1 = I_R$

Potential difference across pressure coil of wattmeter

$$W_1 = E_{RB} = E_R - E_B \quad (\text{Vectorially})$$

The value of E_{RB} is found by compounding E_R and E_B reversed as shown in Fig. 24. It may be observed that phase difference between E_{RB} and I_R = $(30^\circ - \phi)$.

∴ Reading of wattmeter $W_1 = E_{RB}I_R \cos (30^\circ - \phi)$... (8)

Similarly, current through wattmeter $W_2 = I_Y$

Potential difference across pressure coil of wattmeter

$$W_2 = E_{YB} = E_Y - E_B \quad (\text{Vectorially})$$

The value of E_{YB} is found by compounding E_Y and E_B reversed as shown in Fig. 24. The phase difference between E_{YB} and I_Y = $(30^\circ + \phi)$.

∴ Reading of wattmeter $W_2 = E_{YB}I_Y \cos (30^\circ + \phi)$... (9)

Since the load is balanced, $E_{RB} = E_{YB} = E_L$ (Line voltage)

and $I_R = I_Y = I_L$ (Line current)

∴ $W_1 = E_L I_L \cos (30^\circ - \phi)$

$$W_2 = E_L I_L \cos (30^\circ + \phi)$$

∴ Total power,

$$\begin{aligned} P &= W_1 + W_2 \\ &= E_L I_L \cos (30^\circ - \phi) + E_L I_L \cos (30^\circ + \phi) \\ &= E_L I_L [\cos (30^\circ - \phi) + \cos (30^\circ + \phi)] \end{aligned}$$

$$\begin{aligned}
 &= E_L I_L [\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi + \cos 30^\circ \cos \phi - \sin 30^\circ \sin \phi] \\
 &= E_L I_L (2 \cos 30^\circ \cos \phi) = E_L I_L \times 2 \times \frac{\sqrt{3}}{2} \cos \phi = \sqrt{3} E_L I_L \cos \phi
 \end{aligned}$$

$$P = \sqrt{3} E_L I_L \cos \phi$$

i.e.,

Hence the sum of the readings of the two wattmeters give the total power consumption in the 3-phase load.

It is worth noting that in the above case the phase sequence of RYB has been assumed, the readings of the two wattmeters will change if the phase sequence is reversed.

Variations in wattmeter readings. As shown above that for a lagging power factor

$$W_1 = E_L I_L \cos (30^\circ - \phi)$$

and

$$W_2 = E_L I_L \cos (30^\circ + \phi)$$

From above it is evident that individual readings of the wattmeters not only depend on the load but also upon its power factor. Let us take up the following cases :

(i) When $\phi = 0$

i.e., power factor is unity (i.e., load is resistive)

$$\text{Then } W_1 = W_2 = E_L I_L \cos 30^\circ$$

The reading of each wattmeter will be equal and opposite (i.e., up-scale reading).

(ii) When $\phi = 60^\circ$

i.e., power factor = 0.5 (lagging)

$$\text{Then } W_2 = E_L I_L \cos (30^\circ + 60^\circ) = 0$$

Hence, the power is measured by W_1 above.

(iii) When $90^\circ > \phi > 60^\circ$

i.e., $0.5 > \text{p.f.} > 0$

Then W_1 is still positive but reading of W_2 is reversed. For a leading p.f., conditions are just the opposite of this. In that case, W_1 will read negative because the phase angle between the current and voltage is more than 90° . For getting the total power, the reading of W_2 is to be subtracted from that of W_1 . Under this condition, W_2 will read 'down scale' i.e., backwards. Hence, to obtain a reading on W_2 , it is necessary to reverse either its pressure coil or current coil, usually the former.

All readings taken after reversal of pressure coil are to be taken as negative.

(iv) When $\phi = 90^\circ$

(i.e., p.f. = 0 i.e., pure inductive or capacitive load)

$$\text{Then } W_1 = E_L I_L \cos (30^\circ - 90^\circ) = E_L I_L \sin 30^\circ$$

and $W_2 = E_L I_L \cos (30^\circ + 90^\circ) = -E_L I_L \sin 30^\circ$

These two readings are equal in magnitude but opposite in sign

$$\therefore W_1 + W_2 = 0.$$

So far we have considered lagging angles (taken as positive). Now let us discuss how the readings of wattmeters change when the power factor is leading one.

— For $\phi = +60^\circ$ (lag) : $W_2 = 0$

— For $\phi = -60^\circ$ (lead) : $W_1 = 0$

Thus we find that for angles of lead the readings of the two wattmeters are interchanged.

Hence, when the power is *leading*:

$$W_1 = E_L I_L \cos (30^\circ + \phi)$$

$$W_2 = E_L I_L \cos (30^\circ - \phi).$$

Power Factor—When the load is 'balanced'. When load is balanced with a *lagging power factor* and the voltage and currents are sinusoidal:

$$W_1 + W_2 = E_L I_L \cos (30^\circ - \phi) + E_L I_L \cos (30^\circ + \phi) = \sqrt{3} E_L I_L \cos \phi \quad \dots(10)$$

Similarly,

$$\begin{aligned} W_1 - W_2 &= E_L I_L \cos (30^\circ - \phi) - E_L I_L \cos (30^\circ + \phi) \\ &= E_L I_L (2 \sin \phi \sin 30^\circ) = E_L I_L \sin \phi \end{aligned} \quad \dots(11)$$

Dividing (11) by (10), we get

$$\tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{(W_1 + W_2)} \quad \dots(12)$$

For a *leading power*, this expression becomes

$$\tan \phi = -\frac{\sqrt{3}(W_1 - W_2)}{(W_1 + W_2)} \quad \dots(13)$$

After finding $\tan \phi$, hence ϕ , the value of power factor $\cos \phi$ can be found (from trigonometrical tables).

One important point which must be kept in mind is that if W_2 reading has been taken after reversing the pressure coil i.e., if W_2 is *negative*, then the eqn. (12) becomes

$$\tan \phi = \sqrt{3} \frac{W_1 - (-W_2)}{W_1 + (-W_2)}$$

$$\text{or } \tan \phi = \sqrt{3} \frac{W_1 + W_2}{W_1 - W_2} \quad \dots(14)$$

The power factor may also be expressed in terms of ratio of the readings of the two wattmeters.

$$\text{Let } \frac{\text{Smaller reading}}{\text{Larger reading}} = \frac{W_2}{W_1} = \alpha$$

Then from eqn. (12) above, we have

$$\tan \phi = \frac{\sqrt{3} \left[1 - \left(\frac{W_2}{W_1} \right) \right]}{\left[1 + \left(\frac{W_2}{W_1} \right) \right]} = \frac{\sqrt{3} (1 - \alpha)}{(1 + \alpha)}$$

We know that,

$$\sec^2 \phi = 1 + \tan^2 \phi$$

$$\text{or } \frac{1}{\cos^2 \phi} = 1 + \tan^2 \phi \quad \text{or} \quad \cos^2 \phi = \frac{1}{1 + \tan^2 \phi}$$

$$\cos \phi = \frac{1}{\sqrt{1 + \tan^2 \phi}} = \frac{1}{\sqrt{1 + \left[\frac{\sqrt{3} (1 - \alpha)}{1 + \alpha} \right]^2}}$$

$$\text{or } = \frac{1}{\sqrt{1 + 3 \left(\frac{1 - \alpha}{1 + \alpha} \right)^2}} = \frac{1 + \alpha}{\sqrt{(1 + \alpha)^2 + 3 (1 - \alpha)^2}}$$

$$\begin{aligned}
 &= \frac{1+\alpha}{\sqrt{1+\alpha^2+2\alpha+3(1+\alpha^2-2\alpha)}} = \frac{1+\alpha}{\sqrt{4+4\alpha^2-4\alpha}} \\
 &= \frac{1+\alpha}{2\sqrt{1-\alpha+\alpha^2}} \\
 \text{i.e., } \cos \phi &= \frac{1+\alpha}{2\sqrt{1-\alpha+\alpha^2}} \quad \dots(15)
 \end{aligned}$$

If a curve is plotted between α and $\cos \phi$, then the curve obtained will be as shown in Fig. 25, this curve is called **watt-ratio curve**.

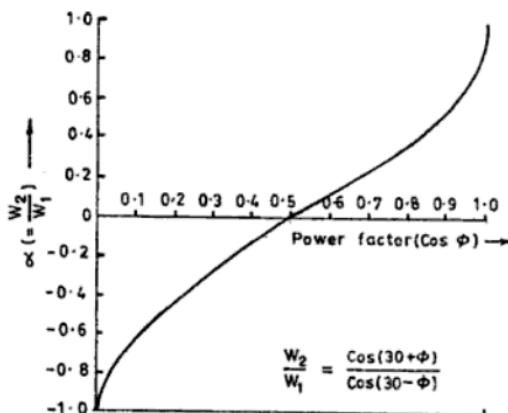


Fig. 25. Watt-ratio curve.

Reactive volt amperes (with two watt-meters)

$$\text{We know that } \tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2}$$

As the tangent of the angle of lag between phase current and phase voltage of a circuit is always equal to the ratio of reactive power to the true power (Fig. 26). Hence, in case of a balanced load, the reactive power is given by $\sqrt{3}$ times the difference of the readings of the two wattmeters used to measure the power of a 3-phase circuit by two wattmeter method.

Mathematical proof is as follows :

$$\begin{aligned}
 \sqrt{3}(W_1 - W_2) &= \sqrt{3} [(E_L I_L \cos(30^\circ - \phi) - E_L I_L \cos(30^\circ + \phi))] \\
 &= \sqrt{3} E_L I_L [(\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi) - (\cos 30^\circ \cos \phi - \sin 30^\circ \sin \phi)] \\
 &= \sqrt{3} E_L I_L [\cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi - \cos 30^\circ \cos \phi + \sin 30^\circ \sin \phi]
 \end{aligned}$$

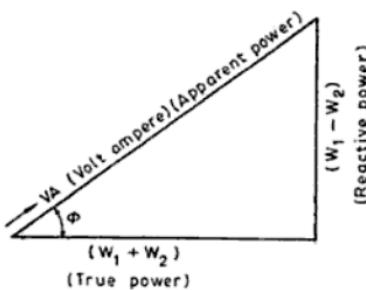


Fig. 26

$$= \sqrt{3} E_L I_L (2 \sin 30^\circ \sin \phi) = \sqrt{3} E_L I_L \sin \phi$$

i.e., $\sqrt{3} (W_1 - W_2) = \sqrt{3} E_L I_L \sin \phi.$

9.3. One-wattmeter method. In this method the current coil is connected in any one line and the pressure coil is connected alternately between this and the other two lines as shown in Fig. 27. The two readings so obtained, for a balanced load, correspond to those obtained by normal two wattmeter method.

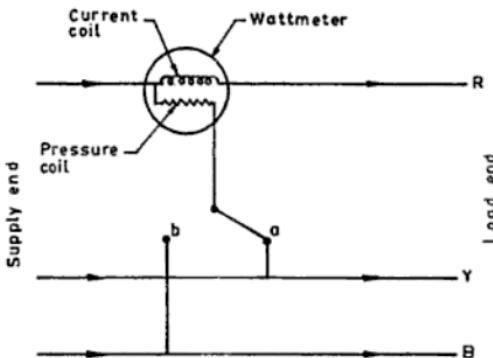


Fig. 27. One wattmeter method.

This method is not of as much universal application as the two wattmeter method because it is restricted to *fairly balanced loads only*. However, it may be conveniently applied, for instance, when it is desired to find the power input to a factory motor *in order to check the load upon the motor*.

10. MEASUREMENT OF REACTIVE VOLT AMPERES

In order to measure reactive power in a single phase circuit a *compensated wattmeter* is used. In this wattmeter the voltage applied to the pressure coil is *90° out of phase with the actual voltage* and hence it will read $VI \cos(90^\circ - \phi)$ i.e., $VI \sin \phi$, reactive power.

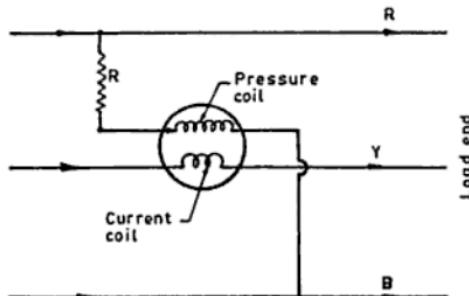


Fig. 28. Measurement of reactive volt-amperes.

In balanced three-phase circuit the reactive power can be determined by using one wattmeter. The necessary connections are shown in Fig. 28. The current coil is inserted in one line and the pressure coil is connected across the other two lines.

The current following through the current coil of the wattmeter

$$= I_Y = I_{ph} \text{ (say)}$$

The potential difference across the potential coil of wattmeter,

$$E = E_R - E_B$$

$$= \sqrt{3} E_{ph} \text{ leading vector } E_Y \text{ by } 90^\circ$$

$$= \sqrt{3} E_{ph} \text{ leading the vector of current } I_Y \text{ by } (90^\circ + \phi)$$

\therefore Reading of the wattmeter (Fig. 29)

$$= \sqrt{3} E_{ph} I_{ph} \cos (90^\circ + \phi)$$

$$= -\sqrt{3} E_{ph} I_{ph} \sin \phi = -W_r$$

Total reactive power of the circuit,

$$= 3 E_{ph} I_{ph} \sin \phi = -\sqrt{3} W_r$$

Reactive power (as earlier started) can also be determined from two wattmeter readings connected for measurement of power.

$$W_1 - W_2 = E_L I_L \cos (30^\circ - \phi) - E_L I_L \cos (30^\circ + \phi)$$

or

$$W_1 - W_2 = E_L I_L \times 2 \sin 30^\circ \sin \phi$$

or

$$E_L I_L \sin \phi = W_1 - W_2$$

Reactive power of load circuit.

$$W_r = \sqrt{3} E_L I_L \sin \phi = \sqrt{3} (W_1 - W_2).$$

Power Measurement in 3-phase Circuits

Example 13. The power input to a 3-phase induction motor is read by two wattmeters. The readings are 920 W and 300 W. Calculate the power factor of the motor.

Solution. Reading of wattmeter, $W_1 = 920$ W

Reading of wattmeter, $W_2 = 300$ W

Power factor of the motor, $\cos \phi$:

$$\text{Using the relation, } \tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} = \frac{\sqrt{3} (920 - 300)}{(920 + 300)} = \frac{\sqrt{3} \times 620}{1220} = 0.88$$

$$\therefore \phi = \tan^{-1} 0.88 = 41.35^\circ$$

Power factor of the motor,

$$\cos \phi = \cos 41.35^\circ = 0.75 \text{ (lag). (Ans.)}$$

Example 14. While performing a load test on a 3-phase wound-rotor induction motor by two wattmeters method, the readings obtained on two wattmeters were + 14.2 kW and - 6.1 kW and the line voltage was 440 V. Calculate :

(i) True power drawn by the motor

(ii) Power factor, and

(iii) Line current.

Solution. Reading of wattmeter, $W_1 = 14.2$ kW

Reading of wattmeter, $W_2 = -6.1$ kW

Line voltage, $E_L = 440$ V

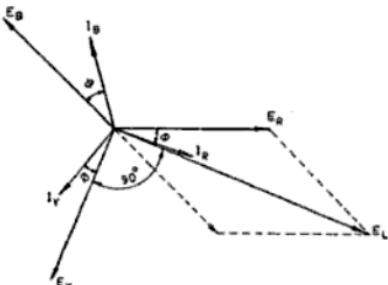


Fig. 29

(i) True power drawn by the motor

$$= 14.2 - 6.1 = 8.1 \text{ kW. (Ans.)}$$

$$(ii) \tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} = \frac{\sqrt{3} [14.2 - (-6.1)]}{[14.2 + (-6.1)]} = \frac{\sqrt{3} \times 20.3}{8.1} = 4.34$$

$$\therefore \phi = \tan^{-1} 4.34 = 77^\circ$$

∴ Power factor, $\cos \phi = \cos 77^\circ = 0.2249$ (lag). (Ans.)

(iii) Line current, I_L :

Using the relation, $P = \sqrt{3} E_L I_L \cos \phi$

$$8.1 \times 1000 = \sqrt{3} \times 440 \times I_L \times 0.2249$$

$$\therefore I_L = \frac{8.1 \times 1000}{\sqrt{3} \times 440 \times 0.2249} = 47.26 \text{ A}$$

Hence, line current = 47.26 A. (Ans.)

Example 15. A 3-phase, 440 V motor load has a power factor of 0.6. Two wattmeters connected to measure the power show the input to be 25 kW. Find the reading on each instrument.

Solution. Input power = 25 kW

Line voltage, $E_L = 440 \text{ V}$

Power factor of the motor load, $\cos \phi = 0.6$

W_1 ; W_2 :

$$\text{Using the relation: } \tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} \quad \dots(i)$$

$$\text{Now, } \cos \phi = 0.6, \therefore \phi = 53.13^\circ$$

$$\therefore \tan \phi = \tan 53.13^\circ = 1.333$$

$$\text{Also } W_1 + W_2 = 25 \text{ kW} \quad (\text{given}) \quad \dots(ii)$$

Substituting these values in (i), we get

$$1.333 = \frac{\sqrt{3} (W_1 - W_2)}{25}$$

$$\therefore W_1 - W_2 = \frac{1.333 \times 25}{\sqrt{3}} = 19.24 \text{ kW} \quad \dots(iii)$$

From (ii) and (iii), we get $W_1 = 22.12 \text{ kW}$

$$W_2 = 2.88 \text{ kW. (Ans.)}$$

and

Example 16. In a 3-phase circuit two wattmeters used to measure power indicate 1200 W and 600 W respectively. Find the power factor of the circuit:

(i) When both wattmeter readings are positive.

(ii) When the latter is obtained by reversing the current coil connections.

Solution. (i) When both wattmeter readings are positive :

Reading of wattmeter, $W_1 = 1200 \text{ W}$

Reading of wattmeter, $W_2 = 600 \text{ W}$

$$\text{We know that, } \tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} = \frac{\sqrt{3} (1200 - 600)}{(1200 + 600)} = 0.577$$

$$\phi = \tan^{-1} 0.577 = 30^\circ$$

Power factor, $\cos \phi = \cos 30^\circ = 0.866$ (lag). (Ans.)

(ii) When the reading of wattmeter W_2 is obtained by reversing the coil connection :

Reading of wattmeter, $W_1 = 1200 \text{ W}$

Reading of wattmeter, $W_2 = -600 \text{ W}$

$$\text{We know that, } \tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)} = \frac{\sqrt{3} [1200 - (-600)]}{[1200 + (-600)]} = \frac{\sqrt{3} \times 1800}{600} = 5.196$$

or

$$\phi = \tan^{-1} 5.196 = 79.1^\circ$$

Hence, power factor $= \cos \phi = \cos 79.1^\circ = 0.1889$. (Ans.)

Example 17. In order to measure the power input and the power factor of an over-excited synchronous motor two wattmeters are used. If the meters indicate (-3.5 kW) and ($+8.0 \text{ kW}$) respectively. Calculate :

(i) Power factor of the motor.

(ii) Power input to the motor.

Solution. (i) Since an over-excited synchronous motor runs with a leading power factor, we should use the relation,

$$\tan \phi = - \frac{\sqrt{3} (W_1 - W_2)}{(W_1 + W_2)}$$

Moreover it is W_1 that gives negative reading and not W_2 . Hence $W_1 = -3.5 \text{ kW}$.

$$\therefore \tan \phi = - \frac{\sqrt{3} (-3.5 - 8)}{(-3.5 + 8)} = - \frac{\sqrt{3} \times 11.5}{5.5} = 3.62$$

$$\therefore \phi = \tan^{-1} 3.62 = 74.6^\circ (\text{lead})$$

(ii) Power factor, $\cos \phi = \cos 74.6^\circ = 0.2655$ (lead). (Ans.)

(ii) Power input $= W_1 + W_2 = -3.5 + 8 = 4.5 \text{ W}$. (Ans.)

Example 18. Two wattmeters are used to measure power input to a $1.5 \text{ kV}, 50 \text{ Hz}, 3\text{-phase}$ motor running on full-load at an efficiency of 85 per cent. Their readings are 250 kW and 80 kW respectively. Calculate :

(i) Input, (ii) Power factor,

(iii) Line current, and (iv) Output.

Solution. Since the motor is running at full-load, its power factor must be greater than 0.5.

Hence W_2 reading is positive

$$\therefore \begin{aligned} \text{(i) Input} \quad W_1 &= +250 \text{ kW} \quad \text{and} \quad W_2 = +80 \text{ kW} \\ &= W_1 + W_2 = 250 + 80 = 330 \text{ kW}. \quad (\text{Ans.}) \end{aligned}$$

$$\text{(ii)} \quad \tan \phi = \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} = \frac{\sqrt{3} (250 - 80)}{(250 + 80)} = 0.892$$

$$\therefore \phi = \tan^{-1} 0.892 = 41.74^\circ$$

and power factor $= \cos \phi = \cos 41.74^\circ = 0.746$ (lag). (Ans.)

(iii) Power, $P = \sqrt{3} E_L I_L \cos \phi$

$$\therefore I_L = \frac{P}{\sqrt{3} E_L \cos \phi} = \frac{330 \times 1000}{\sqrt{3} \times 1.5 \times 1000 \times 0.746} = 170.27$$

Hence, line current = 170.27 A . (Ans.)

(iv) Output = input \times efficiency = $330 \times 0.85 = 280.5 \text{ kW}$. (Ans.)

Example 19. Two wattmeters are used to measure power input to a synchronous motor. Each of them indicates 60 kW . If the power factor be changed to 0.866 leading, determine the readings of the two wattmeters, the total input power remaining the same. Draw the vector diagram for the second condition of the load.

Solution. Reading of wattmeter, $W_1 = 60 \text{ kW}$

Reading of wattmeter, $W_2 = 60 \text{ kW}$.

First case. In the first case, both wattmeters read equal and positive. Hence, motor must be running at unity power factor.

Second case. Power factor is 0.866 leading.

In this case : $W_1 = E_L I_L \cos(30^\circ + \phi)$
 $W_2 = E_L I_L \cos(30^\circ - \phi)$

$$\therefore W_1 + W_2 = \sqrt{3} E_L I_L \cos \phi$$

$$W_1 - W_2 = -E_L I_L \sin \phi$$

$$\therefore \tan \phi = -\frac{\sqrt{3}(W_1 - W_2)}{(W_1 + W_2)}$$

Since $\cos \phi = 0.866$ (given)

$$\therefore \phi = \cos^{-1} 0.866 = 30^\circ$$

and

$$\tan \phi = \tan 30^\circ = \frac{1}{\sqrt{3}}$$

$$\therefore \frac{1}{\sqrt{3}} = -\frac{\sqrt{3}(W_1 - W_2)}{120}$$

$$[\because W_1 + W_2 = 120 \text{ kW (given)}]$$

$$\therefore W_1 - W_2 = -\frac{120}{3} = -40 \quad \dots(i)$$

But $W_1 + W_2 = 120 \quad \dots(ii)$

From (i) and (ii), we get $W_1 = 40 \text{ kW}$, $W_2 = 80 \text{ kW}$. (Ans.)

For connection diagram, please refer to Fig. 23. The vector or phasor diagram is shown in Fig. 30.

Example 20. Two wattmeters connected to read the total power in a 3-phase system supplying a balanced load read 10.5 kW and -2.5 kW respectively. Calculate the total power and power factor.

Also, explain the significance of (i) equal wattmeter readings and (ii) a zero reading on one wattmeter.

Solution. Given : $W_1 = 10.5 \text{ kW}$; $W_2 = -2.5 \text{ kW}$.

For two wattmeter method,

$$\text{total power} = W_1 + W_2 = 10.5 + (-2.5) = 8.0 \text{ kW. (Ans.)}$$

We know that, $\tan \phi = \frac{\sqrt{3}(W_1 - W_2)}{W_1 + W_2} = \frac{\sqrt{3}[10.5 - (-2.5)]}{[10.5 + (-2.5)]} = 2.8145$

or

$$\phi = 70.44^\circ$$

i.e. Power factor, $\cos \phi = \cos 70.44^\circ = 0.335$. (Ans.)

(i) For readings of the two wattmeters to be equal,

$$W_1 = W_2$$

or $\sqrt{3} E_L I_L \cos(30^\circ - \phi) = \sqrt{3} E_L I_L \cos(30^\circ + \phi)$

or $\cos(30^\circ - \phi) = \cos(30^\circ + \phi)$

$$\therefore \phi = 0^\circ \text{ or } \cos \phi = 1$$

i.e., for unity power factor, the readings of two wattmeters are equal. (Ans.)

(ii) As readings of wattmeters are

$$W_1 = \sqrt{3} E_L I_L \cos(30^\circ - \phi), \text{ and}$$

$$W_2 = \sqrt{3} E_L I_L \cos(30^\circ + \phi).$$

for reading of one of the wattmeters to be zero ϕ must be 60° , which makes $W_2 = \sqrt{3} E_L I_L \cos 90^\circ = 0$. (Ans.)

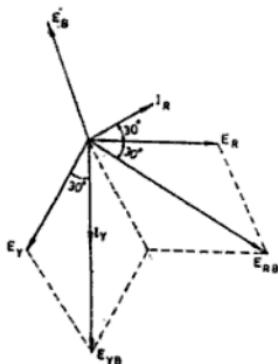


Fig. 30

11. TYPES OF ENERGY METERS

Energy meters are generally of the following three types :

1. Electrolytic meters
2. Motor meters
3. Clock meters.

Here only motor meters will be discussed.

11.1. Motor Meters. The motor meters can be used in D.C. as well as in A.C. circuits. In principle the motor meter is a small motor of D.C. or A.C. type whose *instantaneous speed of rotation is proportional to the circuit current in case of an ampere-hour meter and to the power of the circuit in case of a watt-hour meter*.

The following are the essential parts of the motor meters :

1. **An operating torque system.** It produces a torque and causes the moving system to rotate continuously.

2. **A braking device.** It is usually a permanent magnet, known as *brake magnet*. This brake magnet induces current in some part of the moving system which in turn produces the braking torque. Thus the braking torque is *proportional to the induced currents* whereas the induced currents are *proportional to the speed of the moving system* (and hence the *braking torque is proportional to the speed of the moving system (disc)*). When the braking torque is equal to the driving torque the moving system attains a steady speed.

3. **Revolution registering device.** This device is obtained by having a worm cut on the spindle of the instrument. The worm engages with a pinion and thus drives the train of wheels and registers ampere-hours and watt-hours directly.

Types of motor meters. The various types of motor meters are :

- (i) Mercury motor meters
 - (ii) Commutator motor meters
 - (iii) Induction motor/energy meters.
- *Mercury motor meters and commutator meters are used on D.C. circuits*
- *Induction meters are used on A.C. circuit.*

11.2. Motor-driven Meter—Watt-hour Meter

The motor-driven meter shown in Fig. 31 can be used on direct or alternating current. It contains a small motor and an aluminium retarding disc. *The field winding is connected in series with the load, and the field strength is proportional to the load current.*

The armature is connected across the source, and the *current in the armature is proportional to the source or line voltage*. The torque produced in the armature is *proportional to the power consumed by the load*.

The armature shaft drives a series of counters that are calibrated in watt-hours. The power that is used can be read directly from the dials.

The aluminium disc attached to the armature is used to control the armature speed. The disc turns in a magnetic field produced by the permanent magnets, and the retarding force increases as the rotation increases and stops when the disc stops. The retarding force is produced by the aluminium conductor cutting through the lines of force of the permanent magnets. This is a form of magnetic damping.

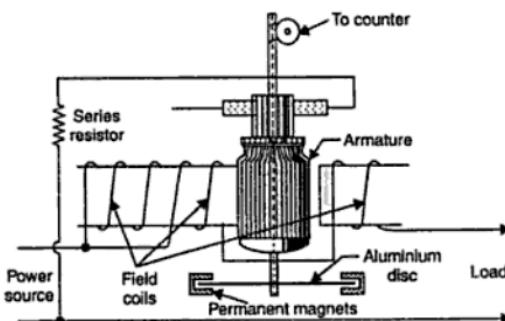


Fig. 31. Motor-driven meter (watt-hour meter) designed to operate on direct or alternating current.

The meter must overcome the friction of the bearings and indicators at *very light loads*. A portion of the field is produced by the armature current (coil in series with the armature winding). This coil is (called as compensating coil) wound to aid the field and is adjusted to the point where it just overcomes the meter friction.

11.3. Induction Type Watt-hour Meter. This is the *most commonly used meter on A.C. circuits* for measurement of energy.

Advantages :

- (i) Simple in operation
- (ii) High torque/weight ratio
- (iii) Cheap in cost
- (iv) Correct registration even at very low power factor
- (v) Unaffected by temperature variations
- (vi) More accurate than commutator type energy meter on light loads (owing to absence of a commutator with its accompanying friction).

11.4. Induction Type Single Phase Energy Meters

These are, by far, the most common form of A.C. meters met with in every-day *domestic and industrial installations*. These meters measure electric energy in kWh.

The principle of these meters is practically the same as that of induction watt meters. Instead of the control spring and the pointer of the watt-meter, the watt-hour meter, (energy meter) employs a *brake magnet and a counter attached to the spindle*. Just like other watt-hour meters, the eddy currents induced in the aluminium disc by the brake magnet due to the revolution of the disc, are utilised to control the continuously rotating disc.

Construction. The construction of a typical meter of this type is shown in Fig. 32. The brake-magnet and recording wheel-train being omitted for clearances. It consists of the following :

- (i) Series magnet M_1
- (ii) Shunt magnet M_2
- (iii) Brake magnet
- (iv) A rotating disc.

The *series electro-magnet M_1* consists of a number of U-shaped iron laminations assembled together to form a core, wound with a few turns of a heavy gauge wire. This wound coil is known as

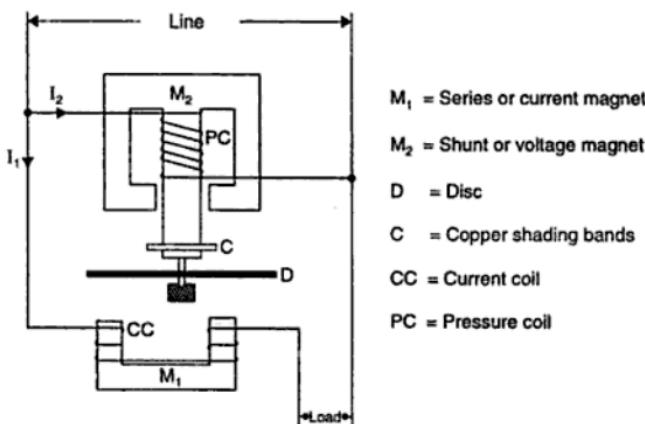


Fig. 32. Induction type single phase energy meter.

current coil and is connected in one of the lines and in series with the load to be metered. The series electromagnet is energized and sets up a magnetic field cutting through the rotating disc, when load current flows through the current coil C.C. The rotating disc is an aluminum disc mounted on a vertical spindle and supported on a sapphire cup contained in a bottom screw. The bottom pivot, which is usually removable, is of hardened steel, and the end, which is hemispherical in shape, rests in the sapphire cup. The top pivot (not shown) merely serves to maintain the spindle in a vertical position under working condition and does not support any weight or exert any appreciable thrust in any direction.

The *shunt magnet* M_2 consists of a number of M shaped iron laminations assembled together to form a core. A core having *large number of turns of fine wire* is fitted on the middle limb of the shunt magnet, this coil is known as *pressure coil P.C.* and is connected across the supply mains.

The *brake magnet* consists of *C* shaped piece of alloy steel bent round to form a complete magnetic circuit, with the exception of a narrow gap between the poles. This magnet is mounted so that the disc revolves in the air gap between the polar extremities. The movement of the rotating disc through the magnetic field crossing the air gap *sets up eddy currents in the disc which react with the field and exerts a braking effect*. The speed of the rotating disc may be adjusted by changing the position of the brake magnet or by diverting some of the flux there from.

Working. The shunt electromagnet produces a magnetic field which is of pulsating character ; it cuts through the rotating disc and induces eddy currents there in, but normally *does not in itself produce any driving force*. Similarly series electromagnet induces eddy currents in the rotating disc, but *does not in itself produce any driving force*. In order to obtain driving force in this type of meter, *phase displacement of 90° between the magnetic field set up by shunt electromagnet and applied voltage V is achieved by adjustment of copper shading band C* (also known as power factor compensator or compensating loop). *The reaction between these magnetic fields and eddy currents set up a driving torque in the disc.*

Sources of Errors. The various sources of errors in an induction-type energy meter are given below :

(i) *Incorrect magnitude of the fluxes.* These may arise from abnormal voltages and load currents.

(ii) *Incorrect phase relation of fluxes.* These may arise from defective lagging, abnormal frequencies, changes in the iron losses etc.

(iii) *Unsymmetrical magnetic structure.* The disc may go on rotating while no current is being drawn but pressure coils alone are excited.

(iv) *Changes in the resistance of the disc.* It may occur due to changes in temperature.

(v) *Changes in the strength of the drag magnets.* It may be due to temperature or ageing.

(vi) Phase-angle errors due to lowering of power factor.

(vii) Abnormal friction of moving parts.

(viii) Badly distorted waveform.

(ix) Changes in the retarding torque due to the disc moving through the field of the current coils.

Example 21. A 5 A, 230 V meter on full load unity power factor test makes 60 revolutions in 360 seconds. If the normal disc speed is 520 revolutions per kWh, what is the percentage error?

Sol. Energy consumed in 360 seconds

$$\begin{aligned} &= \frac{VI \cos \phi \times t}{3600 \times 1000} \text{ kWh} \\ &= \frac{230 \times 5 \times 1 \times 360}{3600 \times 1000} = 0.115 \text{ kWh} \end{aligned}$$

where, t is in seconds.

Energy recorded by the meter

$$\begin{aligned} &= \frac{60}{520} = 0.11538 \text{ kWh} \\ \therefore \% \text{ age error} &= \frac{0.11538 - 0.115}{0.115} \times 100 = 0.33\% \text{ (fast). (Ans.)} \end{aligned}$$

Example 22. The constant of a 230 V, 50 Hz, single phase energy meter is 185 revolutions per kWh. The meter takes 190 seconds for 10 revolutions while supplying a non-inductive load of 4.5 A at normal voltage. What is the percentage error of the instrument?

Sol. Energy consumed in 190 seconds

$$\begin{aligned} &= \frac{VI \cos \phi}{1000} \times t = \frac{230 \times 4.5 \times 1}{1000} \times \frac{190}{3600} = 0.0546 \text{ kWh} \\ &\quad [\cos \phi = 1, \text{ since load supplied is non-inductive}] \end{aligned}$$

Energy registered by the meter = $\frac{10}{185} = 0.054 \text{ kWh}$

$$\therefore \% \text{ age error} = \frac{0.054 - 0.0546}{0.054} = 0.06\% \text{ (slow). (Ans.)}$$

Example 23. The name plate of a meter reads "1 kWh = 15000 revolutions". In a check up, the meter completed 150 revolutions during 45 seconds. Calculate the power in the circuit.

Sol. Power metered in 150 revolutions

$$= 1 \times 150/15000 = 0.01 \text{ kWh}$$

If P kilowatt is the power in the circuit, then energy consumed in 45 seconds

$$= \frac{P \times 45}{3600} \text{ kWh} = 0.0125 P \text{ kWh}$$

Equating the two amounts of energy, we have

$$0.0125 P = 0.01$$

$$\therefore P = 0.8 \text{ kW} = 800 \text{ W. (Ans.)}$$

Example 24. A 230 V ampere-hour type meter is connected to a 230 V D.C. supply. If the meter completes 225 revolutions in 10 minutes when carrying 14 A, calculate : (i) The kWh registered by the meter, and (ii) The percentage error of the meter above or below the original calibration.

The timing constant of the meter is 40 A-s/revolution.

Sol. During 225 revolutions the meter would register 40×225 A-s or coulombs. since time taken is 10 minutes or 600 seconds it corresponds to a current of $\frac{40 \times 225}{600} = 15$ A.

$$(i) \text{Energy recorded by the meter} = \frac{VI t}{1000} \text{ kWh}$$

where t is in hour

$$= \frac{230 \times 15}{1000} \times \frac{10}{60} = 0.575 \text{ kWh.}$$

$$(ii) \text{Actual energy consumed} = \frac{230 \times 14}{1000} \times \frac{10}{60} = 0.5367 \text{ kWh}$$

$$\text{Percentage error} = \frac{0.575 - 0.5367}{0.575} \times 100 = 6.66\%. \quad (\text{Ans.})$$

12. POWER FACTOR IMPROVEMENT

The power factors of different loads are as follows :

Type of load	Power factor (range)
Heating and lighting	0.95 to unity
Motor loads	0.5 to 0.9
Single-phase motors	as low as 0.4
Electric welding units	0.2 to 0.3

The power factor is given by :

$$\cos \phi = \frac{kW}{kVA} \quad \text{or} \quad kVA = \frac{kW}{\cos \phi}$$

In case of single-phase supply,

$$kVA = \frac{VI}{1000} \quad \text{or} \quad I = \frac{1000 \text{ kVA}}{V}$$

$$I \propto kVA$$

In case of three-phase supply,

$$kVA = \frac{\sqrt{3} E_L I_L}{1000} \quad \text{or} \quad I_L = \frac{1000 \text{ kVA}}{\sqrt{3} E_L}$$

$$I_L \propto kVA$$

In each case, the kVA is directly proportional to current.

The higher current due to poor power factor affects the system and lead to the following undesirable results :

1. Rating of alternators and transformers are proportional to their output current hence inversely proportional to power factor, therefore large generators and transformers are required to deliver same load but at a low power factor.

2. When a load having a low lagging power is switched on, there is a large voltage drop in the supply voltage because of the increased voltage drop in the supply lines and transformers. This drop in voltage adversely affects the starting torque of motors and necessitates expensive voltage stabilizing equipment for keeping the consumer's voltage fluctuations within the statutory limits.

3. The cross-sectional area of the bus-bar, and the contact surface of switch gear is required to be enlarged for the same power to be delivered but at a low power factor.

4. To transmit same power at low power factor, more current will have to be carried by the transmission line or the distributor or cable. If the current density in the line is to be kept constant the size of the conductor will have to be increased. Thus more copper is required to deliver the same load but at a low power factor.

5. Copper losses are proportional to the square of the current hence inversely proportional to the square of the power factor i.e., more copper losses at low power factor and hence poor efficiency.

Thus, we find that the capital cost of transformers, alternators, distributors, transmission lines etc. increase with the low power factor.

Causes of Low Power Factor :

(i) All A.C. motors (except overexcited synchronous motors and certain types of commutators motors) and transformers operate at lagging power factor.

(ii) Due to typical characteristic of the arc, arc lamps operate at low power factor.

(iii) When there is increase in supply voltage, which usually occurs during low load periods (such as lunch hours, night hours etc.) the magnetizing current of inductive reactances increases and power factor of the electrical plant as a whole decreases.

(iv) Arc and induction furnaces etc. operate at a very low lagging power factor.

(v) Due to improper maintenance and repairs of motors the power factor at which motors operate fall.

Methods of Improving Power Factor. The power factor may improve by using the following methods :

1. Use of high power factor motors.
2. Use of induction motors with phase advancers.
3. Use of static capacitors.
4. Use of capacitance boosters.
5. Use of synchronous condensers.

Example 25. A 40-MVA, 11 kV 3-phase alternator supplies full-load at a lagging power factor of 0.6. Find the percentage increase in earning capacity if the power factor is increased to 0.9.

Solution. Rating of the alternator = 40 MVA

Supply voltage = 11 kV

Initial power factor = 0.6 (lagging)

Final power factor after increase = 0.9 (lagging)

Percentage increase in earning capacity :

The earning capacity is proportional to the power (in MW or kW) supplied by the alternator.

MW supplied at 0.6 lagging = $40 \times 0.6 = 24$

MW supplied at 0.9 lagging = $40 \times 0.9 = 36$

Increase in MW = $36 - 24 = 12$

The increase in earning capacity is proportional to 12.

$$\therefore \text{Percentage increase in earning capacity} = \frac{12}{24} \times 100 = 50\%. \quad (\text{Ans.})$$

Example 26. A 3-phase, 40 kW, 440 V, 50 Hz induction motor operates on full-load with an efficiency of 90 per cent and at a power factor of 0.8 lagging. Calculate the total kVA rating of capacitors required to raise the full-load power factor to 0.9 lagging. What will be capacitance per phase if the capacitances are :

(i) Delta connected

(ii) Star-connected.

Solution. Motor output = 40 kW

Supply voltage = 440 V

Efficiency of motor = 90%

$$\text{Motor power input, } P = \frac{\text{output}}{\text{efficiency}} = \frac{40}{0.9} = 44.44 \text{ kW}$$

Power factor 0.8 (lagging)

$$\cos \phi_1 = 0.8$$

$$\therefore \phi_1 = \cos^{-1} 0.8 = 36.9^\circ$$

$$\tan \phi_1 = 0.75$$

$$\text{Motor kVAR}_1 = P \tan \phi_1 = 44.44 \times 0.75 = 33.33$$

Power factor 0.9 (lagging)

$$\text{Motor power input} = 44.44 \text{ kW}$$

[As before]

[Power is same as before since the capacitors are loss free i.e., they do not absorb any power]

$$\cos \phi_2 = 0.9$$

$$\therefore \phi_2 = 25.8^\circ$$

$$\tan \phi_2 = 0.484$$

$$\therefore \text{Motor kVAR}_2 = P \tan \phi_2 = 44.44 \times 0.484 = 21.5.$$

The difference in values of kVAR is due to the capacitors which supply leading kVAR to partially neutralize the lagging kVAR of the machine.

∴ Leading kVAR supplied by capacitors is

$$= \text{kVAR}_1 - \text{kVAR}_2 = 33.33 - 21.5$$

$$= 11.83 \dots \text{MQ or NT.}$$

Since capacitors are loss-free, their kVAR is same as kVA

∴ Total kVA rating of capacitors = 11.83 (Ans.)

$$\text{kVAR/capacitor} = \frac{11.83}{3} = 3.943$$

$$\therefore \text{VAR/capacitor} = 3943.$$

(i) Delta connection. In delta-connection, voltage across each capacitor is 440 V.

$$\text{Current drawn by each capacitor, } I_C = \frac{3943}{440} = 8.96 \text{ A}$$

$$\text{Now, } I_C = \frac{V}{X_C} = \frac{V}{\frac{1}{2\pi f C}} = 2\pi f C V$$

$$\therefore C = \frac{I_C}{2\pi f V} = \frac{6.96}{2\pi \times 50 \times 440} = 50.35 \times 10^{-6} \text{ F} = 50.35 \mu\text{F}$$

Hence, capacitance of each capacitor = 50.35 μF . (Ans.)

(ii) Star-connection. In star-connection, voltage across each capacitor

$$= \frac{440}{\sqrt{3}} = 254 \text{ V}$$

$$\text{Current drawn by each capacitor, } I_C = \frac{3943}{254} = 15.52 \text{ A}$$

$$\text{Now, } I_C = \frac{V}{X_C} = \frac{V}{\frac{1}{2\pi f C}} = 2\pi f C V$$

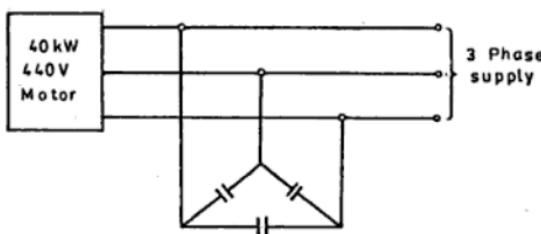


Fig. 33

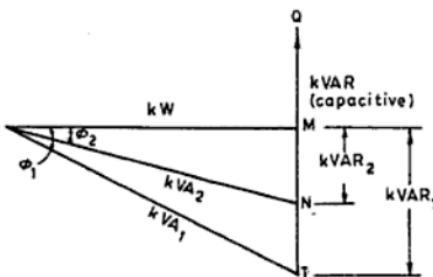


Fig. 34

$$C = \frac{I_C}{2\pi f V} = \frac{15.52}{2\pi \times 50 \times 440} = 112.3 \times 10^{-6} F = 112.3 \mu F$$

Hence, capacitance of each capacitor = $112.3 \mu F$. (Ans.)

13. EARTHING AND GROUNDING

13.1. General Aspects

- The process of connecting the neutral point of a supply system on the non-concurrent carrying parts of electrical apparatus to the general mass of earth in such a manner that at all times an immediate discharge of electrical energy takes place without danger is called earthing.

Or

Eartthing means connecting earth-terminals to electrodes installed solidly in the mass of earth.

Or

A wire coming from the ground 2.5 to 3 metres deep from an electrode (plate or so) is called earthing.

- The earth's potential is always taken as zero for all practical purposes. The electrical appliances or machines when connected with earth attain zero potential and are said to be earthed.
- Good earthing is that earthing which gives very low resistance to the flow of heavy current (short-circuit current) of a circuit.
- Double earth is used to give minimum resistance to the flow of whole current of the apparatus in case short circuit to leakage or any other such fault occurs. Second reason is, if one earth is out of order, second will do the work.

- The earth resistance for copper wire is 1Ω and for G.I. wire it should not be more than 3Ω .
- *The earth resistance should be kept as low as possible.*

13.2. Objects of Earthing

Earthing is carried out to achieve the following *objectives* :

1. To save human life from danger or shock or death by blowing fuse of any apparatus which becomes leaky.
2. To protect all machines fed from overhead lines from lightning arrestors.
3. To protect large buildings from atmospheric lightning.
4. To maintain the line voltage constant (since neutral of every alternator, transformer is earthed).

13.3. Specifications Required for Earthing as per I.S.I.

Following are *recommended specifications as per I.S.I.* for providing *good earthing* :

1. The earthing electrode should be situated at a place atleast $1\frac{1}{2}$ metres away from the building (outside) whose installation system is being earthed.
2. The earth wire should be of same material as that of earth electrode used.
3. The minimum sectional area of earth lead wire should not be less than 0.02 sq. inch (No. 8 S.W.G.) and not more than 0.1 sq. inch.
4. The size of earth conductor as a general rule should not be less than half of the section of the line conductor.
5. The earth wire should be taken through G.I. pipe of 12 mm dia. for at least 32 cm length above and below ground surface to the earth electrode to safeguard against mechanical wear and tear.
6. Loose earth and coal salt mixture should be filled around the earth electrode for effective earthing (see plate earthing and pipe earthing figures for more specifications).
7. The earth wire connected to the earth electrode shall not be necessarily run along the whole wiring system. All the earth wire run along the sub-circuits should be terminated and hooked firmly at the main board and from where the main earth wires should be run to the earth electrode. The loop earth wires should be of 14 S.W.G. copper wire.
8. All the joints in the earth wire should be firmly done with nuts and bolts of the same material as of earth wire.

13.4. Methods of Earthing

The various methods of earthing are :

1. Strip or wire earthing.
2. Earthing through water mains.
3. Rod earthing.
4. Pipe earthing.
5. Plate earthing.

1. Strip earthing :

- In this system of earthing a copper wire of 5 S.W.G. or strip of cross-section *not-less than* $25\text{ mm} \times 1.6\text{ mm}$ is used.
- The length of the buried conductor shall be *sufficient* to give the required earth resistance, but shall *not be less than* 15 m.
- If conditions demand the use of more than one strip, they shall be laid either in parallel trenches or in radial trenches.
- This type of earthing is employed for *rocky soil earth bed where excavation work is difficult.*

2. Earthing through water mains :

- This system of earthing makes use of a stranded copper lead rounded on the pipe with the help of a steel binding wire and an earthing clip.
- The copper lead is soldered to make it solid.
- It should be ensured, before making connection to the water main, that G.I. pipe is used throughout.

3. Rod earthing :

- This system of earthing is *very cheap* as no excavation work is needed.
- Here 12.5 mm diameter solid rods of copper, 16 mm diameter solid rods of galvanised iron or steel or hollow section—25 mm G.I. pipes of length not less than 2.5 metres are driven vertically into the earth manually or pneumatically.
- Rod earthing is suitable for *sandy areas*.

4. Pipe earthing :

Pipe earthing with full specifications as per Indian Standard is described below. Refer Fig. 35.

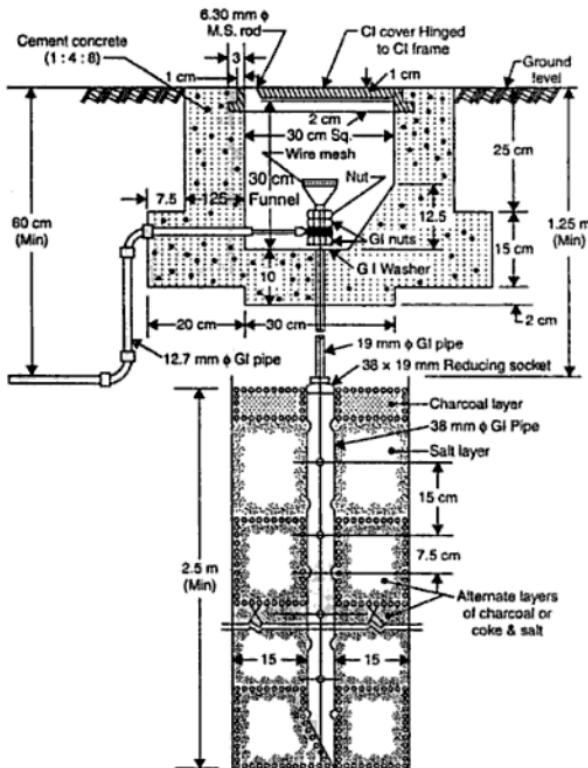



Fig. 35. Pipe earthing.

- In this system of earthing a G.I. pipe of 38 mm dia. and 2 metres length is embedded vertically in ground to work as earth electrode but the depth depends upon the soil conditions ; there is no hard and fast rule for this.
- The earth wires are fastened to the top section of the pipe with nut bolts.
- The pit area around G.I. pipes is filled with *salt and coal mixture* for *improving the soil condition and efficiency of the earthing system*.

The contact surface area of G.I. pipe with soil is more in comparison to the *plate* because of its circular section and hence can *take up heavy leakage current for the same electrode size*. The earth wire connection with the G.I. pipe being above the ground level can be checked for carrying out continuity test as and when desired (while in plate earthing it is difficult).

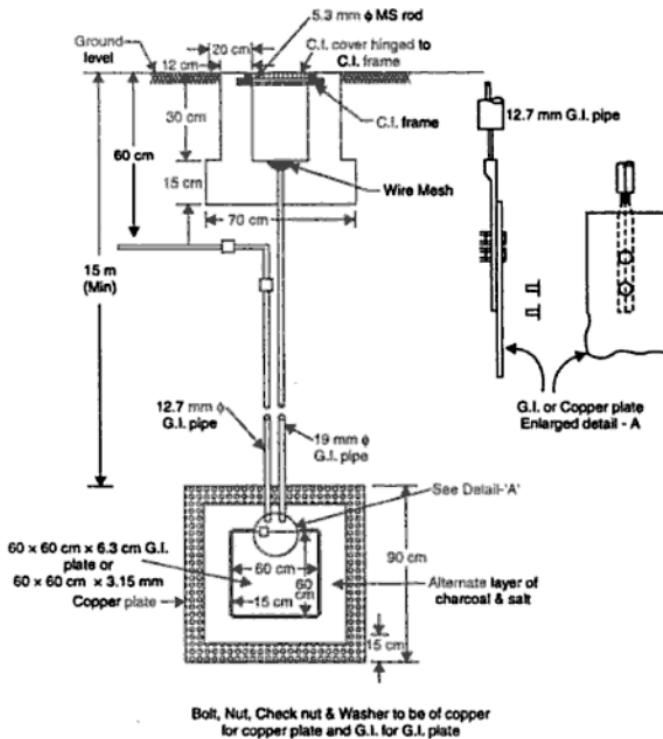5. Plate earthing :

- In plate earthing, the looping earth wire is bolted effectively with the earth plate made up of copper size $60 \text{ cm} \times 60 \text{ cm} \times 3.18 \text{ mm}$ ($2' \times 2' \times 1/4''$) and embedded 3 metres in ground. Copper plates are found to be most effective earth electrodes and are not affected by the soil moisture, i.e., these do not get rusted. But on account of its high material cost, galvanized iron plates are preferred and usually used for normal work.
- In case the soil resistivity is high, the plate should be placed vertically in ground at a higher depth. A line diagram showing the plate earthing system is shown in Fig. 36.



The plate is kept with its face vertical and is so arranged that it is embedded in an alternate layer of coke and salt for a minimum thickness of about 15 cm. The coke salt decreases the earth resistance. It should be remembered that the nuts and bolts must be of copper for copper plate and should be of G.I. for G.I. plates. Usually, the earth wire is drawn through a G.I. pipe fitted with a tunnel on the top through which salty water is poured in the pit of earth plate from time to time in summer season when the moisture of the soil will decrease to a larger extent which will increase the earth resistance.

- The conductivity, i.e., earthing efficiency, increases with the increase of plate area and depth of embedding. Its only *disadvantage is that discontinuity of earth wire and plate below the earth cannot be observed physically; hence is misleading and sometimes results in heavy loss in case of any fault.*

13.5. Sizes of Earth Wire and Earth Plate for Domestic and Motor Installations

- For *house-hold wiring or installation*, a 14SWG hand drawn bare copper conductor is employed as earth wire.
- For *power installations*, the size of the earth wire is decided on the basis of rating of motors installed. The size of the earth wire, for different ratings of motors, can be selected from the following table :

S. No.	Capacity of apparatus	Size of earth wire in SWG		Size of earth electrode	
		Copper	G.I.	Copper	G.I.
1.	Up 10 H.P.	No 8	No 8	60 cm × 60 cm × 3 mm	60 cm × 60 cm × 6 mm
2.	Above 10 H.P. and upto 15 H.P.	No 8	No 6	-do-	-do-
3.	Above 15 H.P. and upto 30 H.P.	No 6	No 2	-do-	90 cm × 90 cm × 6 mm
4.	Above 30 H.P. and upto 50 H.P.	No 4	—	90 cm × 90 cm × 6 mm	—
5.	Above 50 H.P. and upto 100 H.P.	No 2 or strip 13 mm × 2.5 mm	—	-do-	—
6.	Above 100 H.P.	Strip 25 mm × 2.5 mm	--	-do-	—

13.6. Indian Electricity Rules

A few important/relevant Indian Electricity Rules are mentioned below :

- **Rule 33 Earthed terminal or consumer's premises :**
 1. The supplier shall provide and maintain on the consumer's premises for the consumer's use a suitable earthed terminal in an accessible position at or near the point of commencement of supply as defined under rule 58.
Provided that in the case of medium, high or extra high voltage installation, the consumer shall, in addition to the afore-mentioned earthing arrangement, provide his own earthing system with an independent electrode,
Provided further that the supplier may not provide any earthed terminal in the case of installations already connected to his system on or before the date to be specified by the State Government in this behalf if he is satisfied that the consumer's earthing arrangement is efficient.

2. The consumer shall take all reasonable precautions to prevent mechanical damage to the earthed terminal and its lead belonging to the supplier.
3. The supplier may recover from the consumer the cost of installation of such earthed terminal on the basis laid down in the sub-rule (2) of rule 82.

- **Rule 46. Periodical inspection and testing of consumer's installation :**

1. (a) Where an installation is already connected to supply system of the supplier, every such installation shall be periodically inspected and tested at intervals not exceeding five years either by the Inspector or by the supplier as may be directed by the State Government in this behalf or in the case of installations in mines, oil-fields and railways by the Central Government.
 (b) Where the supplier is directed by the Central or the State Government, as the case may be, to inspect and test the installation, he shall report on the condition of the installation to the consumer concerned in a form approved by the Inspector and shall submit a copy of such report to the Inspector.
2. (a) The fees for such inspection and test shall be determined by the Central or the State Government, as the case may be, in the case of each class of consumers and shall be payable by the consumer in advance.
 (b) In the event of the failure of any consumer to pay the fees on or before the date specified in the fee-notice, supply to the installation of such consumer shall be liable to be disconnected under the direction of Inspector. Such disconnection, however, shall not be made by the supplier without giving to the consumer even clear day's notice in writing of his intention so to do.
3. Notwithstanding the provisions of this rule, the consumer shall at all times be solely responsible for the maintenance of his installation in such condition as to be free from danger.

- **Rule 47. Testing of consumer's installation :**

1. Upon receipt of an application for a new or additional supply of energy and before connecting the supply or reconnecting the same after a period of six months, the supplier shall inspect and test the applicant's installation.
 The supplier shall maintain a record of test results obtained at each supply point to a consumer, in a form to be approved by the inspector.
2. If as a result of such inspection and test, the supplier is satisfied that the installation is likely to constitute danger, he shall serve on the applicant a notice in writing requiring him to make such modifications as are necessary to render the installation safe. The supplier may refuse to connect or reconnect the supply until the required modifications have been completed and he has been notified by the applicant.

- **Rule 61. Connection with earth :**

1. The following provisions shall apply to the connection with earth of systems at low voltage in cases where the voltage normally exceeds 125 volts and of systems at medium voltage.
 - (a) The neutral conductor of a three-phase four-wire system and the middle conductor of a two-phase three-wire system shall be earthed by not less than two separate and distinct connections with earth both at the generating station and at the sub-station. It may also be earthed at one or more points along the distribution system or service line in addition to any connection with earth which may be at the consumer's premises.
 - (b) In case of a system comprising electric supply lines having concentric cables, the external conductor of such cable shall be earthed by two separate and distinct connections with earth.

- (c) The connection with earth may include a link by means of which the connection may be temporarily interrupted for the purpose of testing or for locating a fault.
 - (d)
 - (i) In a direct current three-wire system the middle conductor shall be earthed at the generating station only, and the current from the middle conductor to earth shall be continuously recorded by means of a recording ammeter, and if at any time the current exceeds one-thousandth part of the maximum supply current, immediate steps shall be taken to improve the insulation of the system.
 - (ii) Where the middle conductor is earthed by means of a service-breaker with a resistance connected in parallel the resistance shall not exceed 10 ohms and on the opening of the circuit-breaker immediate steps shall be taken to improve the insulation of the system and the circuit-breaker shall be reclosed as soon as possible.
 - (iii) The resistance shall be used only as a protection for the ammeter in the case of earths on the system and until such earths are removed, immediate steps shall be taken to locate and remove the earth.
 - (e) In the case of an alternating system, there shall not be inserted in the connection, with earth any impedance (other than that required solely for the operation of switch-gear or instruments), cut-out or circuit-breaker, and the result of any test made to ascertain whether current (if any) passing through the connection with earth is normal, shall be duly recorded by the supplier.
 - (f) No person shall make connection with earth by the aid of, nor shall he kept it contact with, any water main not belonging to him except with the consent of the owner thereof and of the Inspector.
 - (g) Alternating current systems which are connected with earth as aforesaid may be electrically interconnected.
Provided that each connection with earth is bounded to the metal sheathing and metallic armouring (if any) of the electric supply lines concerned.
2. The frame of every generator, stationary motor, and so far as is practicable, portable motor, and the metallic parts (not intended as conductors) of all transformers and any other apparatus used for regulating or controlling energy and all medium voltage energy consuming apparatus shall be earthed by the owner by two separate and distinct connections with earth.
3. All metal casings or metallic coverings containing or protecting any electric supply line or apparatus shall be connected with earth and shall be so joined and connected across all junction boxes and other openings as to make good mechanical and electrical connection throughout their whole length :
Provided that where the supply is at low voltage, the sub-rule shall not apply to the isolated wall tubes or to brackets, switches, fans regulator covers or other fittings (other than portable hand lamps and portable and transportable apparatus) unless provided with earth terminal.
- This sub-rule shall come into force immediately in the case of new installations and in case of existing installation ; the provision of this sub-rule shall be complied with before the expiry of a period of two years from the commencement of those rules.
4. All earthing systems shall, before electric supply lines or apparatus are energised, be tested for electrical resistance to ensure efficient earthing.
5. All earthing systems belonging to the supplier shall, in addition, be tested for resistance on dry day during the dry season not less than once every two years.

6. A record of every earth test made and the result thereof shall be kept by the supplier for a period of not less than two years after the day of testing and shall be available to the Inspector when required.

- **Rule 67. Connection with earth :**

1. The following provisions shall apply to the connection with earth of three-phase systems for use at high or extra-high voltages :

In the case of star-connected systems with earthed neutrals or delta connected systems with earthed artificial neutral point :

- (a) the neutral point shall be earthed by not less than two separate and distinct connections with earth each having its own electrode at the generating station and at the sub-station and may be earthed at any other point, provided that no interference of any description is caused by such earthing ;
- (b) in the event of an appreciable harmonic current flowing in the neutral connections so as to cause interference with communication circuits, the generator or transformer neutral shall be earthed through a suitable impedance.

2. Single-phase or extra-high voltage systems shall be earthed in a manner approved by the Inspector.

3. In the case of a system comprising electric supply lines having concentric cables, the external conductor shall be the one to be connected with earth.

4. Where a supplier proposes to connect with earth an existing system for use at high or extra-high voltage which has not either been so connected with earth, he shall give not less than fourteen days notice in writing together with particulars to the telegraph authority of the proposed connection with earth.

5. Where the earthing lead and earth connection are used only in connecting earthing guards erected under high or extra-high voltage overhead lines where they cross a telecommunication line or a railways line, and where such lines are equipped with earth leakage relays of a type and setting approved by the Inspector, the resistance shall not exceed 25 ohms.

6. In so far as the provisions of rule 61 are consistent with the provisions of this rule, all connections with earth shall also comply with the provisions of that rule.

13.7. Measurement of Earth Resistance by Earth Tester

The earth resistance can be measured with the help of *Earth tester* or a *Megger Earth Tester*.

The Megger Earth Tester (Fig. 37) is essentially a *direct reading ohmmeter* and a *hand driven generator* which supplies the testing current.

Construction :

- The ohmmeter consists of two coils (current coil and potential coil) mounted at a fixed angle to each other on a common axle. The current coil carries current proportional to the current flowing in the test circuit, while the potential coil carries current proportional to the potential across the resistance under test. Thus the potential coil acts as a voltmeter while current coil acts as an ammeter. Since the deflection of the needle is proportional to the ratio of the current in the two coils, it gives *resistance directly*.
- The hand operated generator produces the direct current, but to eliminate the effect of electrolytic *e.m.f.*, it is necessary to pass alternating current through the soil, so to change the D.C. into an alternating supply a rotary current reverser is mounted on the same shaft of the generator. The alternating current in the soil will produce an alternating drop in the soil but the potential to be applied across the moving coil must be direct because the ohmmeter is a moving coil instrument working on D.C. alone, so for changing the

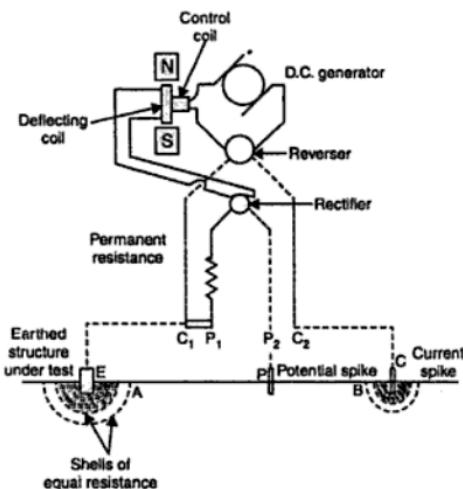


Fig. 37. Megger Tester circuit containing direct current shown by full lines ; circuit containing A.C. current shown by dotted lines.

alternating drop into the direct drop a synchronous rotary rectifier is also attached as shown in Fig. 37. Although the instrument is immune to stray currents, yet while taking readings sometimes it will be observed that the needle vibrates ; this happens only at the instant when the stray alternating current has the same frequency as the frequency generated. For such occasions either *increase the speed of the generator a little or lower its speed.*

Working :

- For measurement of earth resistance two spikes acting as current and potential electrodes are driven into the ground at a suitable distance (C_2 at a distance of about 25 m from earth electrode under test). P_1 and C_1 terminals of the meter are shorted and are connected to the earth electrode under test.
- First spike P_2 is fixed between the spike C_2 and the earth electrode and the resistance is determined ; then this spike taken 3 to 4 m near to the earth electrode and then for the same distance near to electrode C_2 and the two readings are again noted. The average of these three readings is the required earth resistance.

13.8. Earthing of a Power System

Earthing of neutrals of all industrial power systems is always preferable. Earthing is necessary as it offers many *advantages* given below :

1. Persistent arcing grounds is eliminated.
2. Over-voltage due to restriking is minimized.
3. The ground faults can be located and isolated fastly.
4. Steady state voltage stress to earth is reduced.
5. Sensitive protective apparatus can be used.
6. The maintenance expenditure is reduced.
7. Better safety is ensured.

8. Service reliability is improved.
9. Earthing provides improved lighting protection.

The earthing of systems should be done at the neutral of the supply transformers and generators. If the supply transformers and generators are delta connected, separate earthing transformers may be used.

HIGHLIGHTS

1. In a star-connected system, $E_{ph} = \frac{E_L}{\sqrt{3}}$

$$I_{ph} = I_L$$

$$P = \sqrt{3} E_L I_L \cos \phi.$$

2. In a delta-connected system,

$$E_{ph} = E_L$$

$$I_{ph} = \frac{I_L}{\sqrt{3}}$$

$$P = \sqrt{3} E_L I_L \cos \phi.$$

3. Two-wattmeter method is generally used to measure 3-phase power. In this method, the current coils of the two wattmeters are connected in any two lines and their potential coils to the remaining third line. The sum of the two wattmeters readings gives the total power in the circuit. If the load is balanced, then its power factor can also be calculated from these two readings. The readings of the two wattmeters are :

$$(i) \quad \begin{aligned} W_1 &= E_L I_L \cos (30^\circ - \phi) \\ W_2 &= E_L I_L \cos (30^\circ + \phi) \\ \tan \phi &= \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} \end{aligned}$$

Lagging power factor

$$(ii) \quad \begin{aligned} W_1 &= E_L I_L \cos (30^\circ + \phi) \\ W_2 &= E_L I_L \cos (30^\circ - \phi) \\ \tan \phi &= - \frac{\sqrt{3} (W_1 - W_2)}{W_1 + W_2} \end{aligned}$$

Leading power factor

4. In a single-phase as well as in a three-phase system, the kVA is directly proportional to the current I . The disadvantage of a lower power factor is that the current required for a given power is very high, which fact leads to many undesirable results. The power factor may be improved by the following :

- Static capacitors
- Phase advancers
- Synchronous capacitors
- Capacitor boosters
- High power factor motors.

OBJECTIVE TYPE QUESTIONS

Choose the Correct Answer :

1. The power in a 3-phase system is given by $\sqrt{3} V_L I_L \cos \phi$ where ϕ is the phase angle between

(a) line-voltage and line current	(b) phase voltage and phase current
(c) line voltage and phase current	(d) phase voltage and line current.

2. Which of the following statements associated with 3-phase delta connected circuits is *true* ?
 - (a) Line voltage is equal to phase voltage
 - (b) Line current is equal to phase current
 - (c) Line voltage is $\sqrt{3}$ time of phase voltage
 - (d) Line currents are 60° apart.
3. In a 3-phase supply, floating neutral is undesirable because it may result in across the load.
 - (a) unequal line voltages
 - (b) high voltage
 - (c) low voltage.
4. Phase reversal in a 4-wire unbalanced load supplied from a balanced 3-phase supply causes change in
 - (a) the power consumed
 - (b) magnitude of phase currents
 - (c) only the magnitude of the neutral current
 - (d) magnitude as well as phase angle of the neutral current.
5. A 3-phase star connected symmetrical load consumes P watts of power from a balanced supply. If the same load is connected in delta to the same supply, the power consumption will be
 - (a) P
 - (b) $\sqrt{3}P$
 - (c) $3P$
 - (d) not determined from the given data.
6. Three unequal impedances are connected in star to a 3-phase system. The sum of three line currents will be
 - (a) equal to the each line current
 - (b) zero
 - (c) none of these.
7. Three equal impedances are first connected in delta across a 3-φ balanced supply. If the same impedances are connected in star across the same supply
 - (a) phase currents will be one-third
 - (b) line currents will be one-third
 - (c) power consumed will be one-third
 - (d) none of the above.
8. Which of the following is a four wire system ?
 - (a) Delta
 - (b) Star
 - (c) Both delta and star
 - (d) Neither delta nor star.
9. In a 3-phase balanced star-connected load, neutral current is equal to
 - (a) zero
 - (b) I_p
 - (c) I_L
 - (d) unpredictable.
10. Which of the following equations is valid for a 3-phase 4-wire balanced star-connected load ?
 - (a) $I_R + I_Y + I_B = I_N = 0$
 - (b) $I_R + I_Y - I_B = I_N$
 - (c) $I_R - I_Y + I_B = I_N$
 - (d) $\frac{V_B + V_R + V_Y}{Z} = I_N$.
11. Three unequal impedances are connected in delta to a 3-phase, 3-wire system.
 - (a) The voltages across the three phases will be different
 - (b) Both of the phase currents and line currents will be unbalanced
 - (c) Phase currents will be unbalanced but the line currents will be balanced
 - (d) None of the above.
12. The relationship between the line and phase voltages of a delta-connected circuit is given by
 - (a) $V_L = V_p$
 - (b) $V_L = \sqrt{3}V_p$
 - (c) $V_L = \frac{V_p}{\sqrt{2}}$
 - (d) $V_L = \frac{2}{\pi}V_p$.
13. In case of a delta connected load, if one resistor is removed, the power will become
 - (a) zero
 - (b) one-third
 - (c) two-third
 - (d) none of the above.
14. Readings of 1154 and 577 watts are obtained when two wattmeters method was used on a balanced load. The delta connected load impedance for a system of 100 V will be
 - (a) $15 \angle \pm 30^\circ$
 - (b) $15 \angle + 30^\circ$
 - (c) $15 \angle - 30^\circ$
 - (d) $15 \angle + 90^\circ$.

ANSWERS

- | | | | | | |
|----------------|----------------|----------------|----------------|----------------|----------------|
| 1. (b) | 2. (a) | 3. (a) | 4. (d) | 5. (c) | 6. (b) |
| 7. (c) | 8. (b) | 9. (a) | 10. (a) | 11. (b) | 12. (a) |
| 13. (c) | 14. (b) | 15. (d) | 16. (b) | 17. (d) | 18. (d) |
| 19. (a) | 20. (c) | 21. (b) | 22. (b) | 23. (d) | 24. (d) |
| 25. (c) | 26. (c) | 27. (b) | 28. (c) | 29. (c) | 30. (b) |
| 31. (d) | | | | | |

THEORETICAL QUESTIONS

1. State the advantages of A.C. polyphase supply system over single-phase system.
 2. Why is the number of phases in a polyphase system always three rather than any other number ?
 3. Explain clearly what is meant by 'phase sequence' of 3-phase voltages.
 4. What are the two systems in which three-phases can be connected ? What are the advantages and disadvantages of each system ?
 5. What are the advantages of inter-connecting the 3-phases ?
 6. Derive an expression for power in a 3-phase star-connected system in terms of (i) phase values and (ii) line values of voltages and currents.
 7. Derive the numerical relationship between line and phase currents for a balanced 3-phase delta-connected load.

8. Deduce an expression for power in a 3-phase balanced load circuit. Show that it is the same irrespective of the load being connected in star or delta.
9. Compare the star and delta connections in a 3-phase system.
10. Enumerate various methods for 3-phase power measurement, and describe in detail two-wattmeter method for 3-phase power measurement.
11. Prove that the power in a balanced 3-phase circuit can be deduced from the readings of two-wattmeters. Draw the relevant connection diagram and vector diagram.
12. Discuss two-wattmeter method for power measurement in 3-phase system and obtain a relation for the power factor.
13. Derive an expression for star-connected impedances equivalent to three delta-connected impedances.
14. What is earthing?
15. Why double earthing is provided for power equipment?
16. What are the specifications required for earthing as per I.S.I.?
17. How is earth resistance measured with the help of an earth tester? Explain with the help of a neat sketch.

UNSOLVED EXAMPLES

Star/Delta Connections

1. Three equal impedances each having a resistance of $20\ \Omega$ and reactance of $15\ \Omega$ are connected in star to a 400 V, 3-phase, 50 Hz system. Calculate :
 - (i) The line current,
 - (ii) The power factor, and
 - (iii) The power consumed.

[Ans. 9.24 A ; 0.8 (lag) ; 5120 W]
2. Three equal impedances are star-connected to a 3-phase, 50 Hz supply. If the resistance and reactance of each branch are $25\ \Omega$ and $38\ \Omega$ respectively, calculate :
 - (i) The line current, and
 - (ii) The power consumed.

[Ans. 5.28 A ; 2086 W]
3. Three resistances of $20\ \Omega$ each are connected in star across the 400 V, 3-phase A.C. supply. Calculate :
 - (i) The line and phase currents,
 - (ii) Phase voltages, and
 - (iii) Total power taken.

[Ans. (i) 11.55 A ; (ii) 231 V ; (iii) 8.0 kW]
4. A star-connected, 3-phase load consists of three similar impedances. When the load is connected to a 3-phase, 500 V, 50 Hz supply, the line current is 28.85 A and the power factor is 0.8 lagging, calculate :
 - (i) The total power taken by the load, and
 - (ii) The resistance of each phase of the load.

[Ans. 20 kW ; 8 Ω]
5. Three non-inductive resistances each of $50\ \Omega$ are connected in star across 400 V, 3-phase A.C. supply. Calculate the current through each. Calculate the current if they were connected in delta across the same supply.

[Ans. 4.62 A ; 8 A]
6. Three identical coils are connected in star to a 200 V (line voltage), 3-phase, A.C. supply and each coil takes 200 W. The power factor is 0.8 (lagging), calculate :
 - (i) The line current,
 - (ii) Impedance, and
 - (iii) Resistance and inductance of each coil.

[Ans. 2.165 A ; $53.334\ \Omega$, $42.662\ \Omega$, 0.102 H]
7. In a three-phase, 3-wire system with star-connected load the impedance of each phase is $(6+j8)\ \Omega$. If the line voltage is 230 V, calculate :
 - (i) The line current, and
 - (ii) The power absorbed by each phase.

[Ans. 13.3 A ; 1067 W]
8. A balanced star-connected load of $(8+j6)\ \Omega$ per phase is connected to 3-phase, 230 V supply. Find :
 - (i) Line current,
 - (ii) Power factor,
 - (iii) Power,
 - (iv) Reactive volt-amperes, and
 - (v) Total volt-amperes.

[Ans. 13.28 A ; 0.8 (lag) ; 4.232 W ; 3174 ; 5290]

9. A star-connected, 5000 V, 3-phase alternator is supplying 3,000 kW at power factor of 0.8. Calculate the active and reactive components of the current in each phase. [Ans. 346.2 A ; 260 A]
10. In a 3-phase, 4-wire system, two phases have currents of 10 A and 6 A in lagging power factors of 0.8 and 0.6 respectively, while the third phase is open-circuited. Calculate the current in the neutral and sketch the vector diagram. [Ans. 7 $\angle -73^\circ 24'$]
11. In a star-connected load each phase consists of a resistance of $100\ \Omega$ in parallel with a capacitor of capacitance $31.8\ \mu F$. When it is connected to a 416 V, 3-phase, 50 Hz supply, calculate :
 (i) The line current, (ii) The power factor,
 (iii) The power absorbed, and (iv) The total kVA. [Ans. 3.39 A ; 0.707 (leading) ; 1.728 kW ; 2.443 kVA]
12. Three identical coils connected in delta across 400 V, 50 Hz, 3-phase supply takes a line current of 17.32 A at power factor 0.5 lagging. Determine :
 (i) The current in each phase, and
 (ii) Resistance, inductance and impedance of each phase winding. [Ans. 10 A ; $20\ \Omega$; $0.11\ H$, $40\ \Omega$]
13. A 220 V, 3-phase voltage is applied to a balanced delta-connected 3-phase load of phase impedance $(15 + j20)\ \Omega$. Find :
 (i) The phasor current in each line. (ii) What is the power consumed per phase ?
 (iii) What is the phasor sum of the three line currents ? Why does it have this value ? [Ans. 15.24 A ; 1161.6 W ; zero]
14. Calculate (i) line current and (ii) the total power absorbed when three coils each having a resistance of $10\ \Omega$ and reactance of $7\ \Omega$ are connected (a) in star and (b) in delta across a 400 V, 3-phase supply. [Ans. 18.93 A, 10750 W ; 56.7 A, 32250 W]
15. A delta-connected balanced 3-phase load is supplied from a 3-phase 400 V supply. The line current is 20 A and power taken by the load is 10000 W. Find :
 (i) Impedance in each branch ; and
 (ii) The line current, power factor and power consumed if the same load is connected in star. [Ans. $34.6\ \Omega$, $20/3\ A$, 0.7217 , $3330\ W$]
16. A balanced 3-phase load consists of resistances of $4\ \Omega$ each. Determine the total power when the resistances connected to 400 V supply are :
 (i) Star connected (ii) Delta connected. [Ans. 40 kW ; 120 kW]
17. Three non-inductive resistances, each of $100\ \Omega$ are connected in star across 400 V supply. Calculate the current through each. What would be the current through each if they are connected in delta across the same supply. [Ans. $2.31\ A$; $4\ A$]
18. Three $100\ \Omega$ non-inductive resistances are connected in (i) star (ii) delta across a 400 V, 50 Hz, 3-phase mains. Calculate the power taken from the supply system in each case. In the event of one of the three resistances opened, what would be the value of the total power taken from the mains in each of the two cases. [Ans. 1600 W ; 4800 W]
19. A 3-phase delta connected load ; each phase of which has an inductive reactance of $40\ \Omega$ and a resistance of $25\ \Omega$, is fed from the secondary of a 3-phase star-connected transformer, which has phase voltage of 240 V. Draw the circuit diagram of the system and calculate :
 (i) The current in each phase of the load, (ii) The voltage across each phase of the load,
 (iii) The current in the transformer secondary windings, and
 (iv) The total power taken from the supply and its power factor. [Ans. $8.6\ A$; $415.7\ V$; $15.3\ A$; $5820\ W$]
20. Three similar resistors are connected in star across 400 V, 3-phase supply. The line current is 5 A. Calculate the value of each resistor. To what value line voltage be changed to obtain the same current with the resistors connected in delta ? [Ans. $46.2\ \Omega$; $133.3\ V$]
21. A 3-phase, star-connected system with 230 V between each phase and neutral has a resistance of 4, 5 and $6\ \Omega$ respectively in three phases. Calculate :
 (i) The current flowing in each phase, (ii) The neutral current, and
 (iii) The total power absorbed. [Ans. $57.5\ A$, $46\ A$, $38.3\ A$; $16.71\ A$; $32610\ W$]

22. In a 3-phase, 4 wire system there is a balanced 3-phase motor load taking 20 kW at a power factor of 0.8 lagging while lamps connected between phase conductors and the neutral are taking 5, 4 and 10 kW respectively. Voltage between line conductors is 430 V. Calculate the current in each conductor and in the neutral wire of the feeder supplying these loads. [Ans. 51.2 A ; 47.5 A ; 80 A ; 22.4 A]

Power Measurement in 3-phase Circuits

23. The power input to a 3-phase induction motor is read by two wattmeters. The readings are 860 W and 240 W. What is the power factor of the motor ? [Ans. 0.7155 (lag)]
24. While performing a load test on a 3-phase wound rotor induction motor by two wattmeters method, the readings obtained on two wattmeters were + 12.5 kW and - 4.8 kW and the line voltage was 440 V. Calculate :
 (i) Power drawn by the motor, (ii) Power factor, and [Ans. 7.7 kW ; 0.2334 ; 43.3 A]
 (iii) Line current.
25. The input power to a 3-phase delta-connected motor was measured by two wattmeters method. The readings were 20.8 kW and - 6.8 kW and the line voltage was 400 V. Calculate :
 (i) Input power, (ii) Power factor, and [Ans. 14 kW ; 0.281 ; 72 A]
 (iii) Line current.
26. A 3-phase, 500 V motor load has a power factor of 0.4. Two wattmeters connected to measure the power show the input to be 30 kW. Find the reading on each instrument. [Ans. 35 kW ; - 5 kW]
27. The power in a 3-phase circuit is measured by two wattmeters. If the total power is 100 kW and power factor is 0.66 leading, what will be the reading of each wattmeter ? For what power factor will one of the wattmeters read zero ? [Ans. 17.15 kW ; 82.85 kW ; p.f. = 0.5]
28. Two wattmeters used to measure the power input in a 3-phase circuit indicate 1000 W and 500 W respectively. Find the power factor of the circuit
 (i) when both wattmeter readings are positive ; and
 (ii) when the latter is obtained by reversing the current coil connections. [Ans. 0.866 (lag) ; 0.1889 (lag)]
29. Two wattmeters connected to read the total power in a 3-phase system supplying a balanced load read 10.5 kW and - 2.5 kW respectively. Calculate the total power and the power factor. Draw suitable phasor diagram, explain the significance of
 (i) equal wattmeter readings ; and (ii) a zero reading on one wattmeter. [Ans. 8 kW ; 0.3348 (lag) (i) unity p.f., (ii) 0.5 p.f.]
30. The power input to a 1000 V, 3-phase induction motor running on full-load is measured by two wattmeters which indicate 300 kW and 100 kW respectively. Determine :
 (i) Input, (ii) Line current.
 (iii) Power factor, and (iv) Output if the efficiency of the motor is 92%. [Ans. 400 kW ; 303.5 A ; 0.756 (lag) ; 368 kW]
31. Two wattmeters are used for measuring the power input and the power factor of an over-excited synchronous motor. If the readings of the meters are - 2.0 kW and + 7.0 kW respectively, calculate the input and power factor of the motor. [Ans. 5 kW ; 0.3057 (leading)]
32. The power input to a 2-kV, 50 Hz, 3-phase motor running on full-load at an efficiency of 90 per cent is measured by two wattmeters which indicate 300 kW and 100 kW respectively. Calculate :
 (i) Input, (ii) Power factor.
 (iii) Line current, and (iv) Output. [Ans. 400 kW ; 0.756 (lag) ; 153 A ; 360 kW]
33. In a balanced three-phase system power is measured by two-wattmeters method and the ratio of the two wattmeter readings is 2 : 1. Find the power factor of the system. [Ans. 0.866 (lag)]
34. The power input of a synchronous motor is measured by two wattmeters both of which indicate 50 kW. If the power factor of the motor be changed to 0.866 leading, determine the readings of the two wattmeters, the total input power remaining the same. Draw the vector diagram for the second condition of load. [Ans. 33.33 kW ; 66.67 kW]

35. Each phase of a 3-phase delta-connected load consists of an impedance $Z = 20 \angle 60^\circ \Omega$. The line voltage is 440 V at 50 Hz. Calculate the power consumed by each phase impedance and the total power. What will be the readings of the two wattmeters connected? [Ans. 4840 W ; 14520 W ; 14520 W, zero]
36. A 3-phase 3-wire, 415 V supplies a balanced load of 20 A at power factor 0.8 lagging. Two wattmeters are used to measure power. Calculate :
 (i) Power, (ii) Reading of wattmeter No 1, and
 (iii) Reading of wattmeter No. 2. [Ans. 11.5 kW ; 8240 W ; 3260 W]
37. A balanced load is supplied from a 3-phase, 400 V, 3-wire system whose power is measured by two wattmeters. If the total power supplied is 26 kW at 0.75 power factor lagging, find the readings of each of the two wattmeters. [Ans. 19.62 kW ; 6.38 kW]
38. A 3-phase 4-wire, star-connected system supplies only non-inductive load. The current in line R is 8 A, the current in line Y is 10 A and the current in line B is 6 A. The voltage from each line to neutral is 120 V. Find :
 (i) Wattage shown by each of the three wattmeters, and
 (ii) Power taken by the lighting load. [Ans. 960 W, 1200 W, 720 W ; 2880 W]
39. Three identical coils, each having a resistance of 20Ω and reactance of 20Ω are connected in (i) star ; and (ii) delta across 440 V, 3-phase supply. Calculate for each method of connection the line current and reading on each of the two wattmeters connected to measure power.
 [Ans. 8.98 A ; 3817.5 W, 1022.5 W ; 26.95 A ; 12452.5 W ; 3067.5 W]
40. A balanced star-connected load, each having a resistance of 10Ω and inductive reactance of 30Ω is connected to a 400 V, 50 Hz supply. The phase sequence is RYB. Two wattmeters connected to read total power have their current coils connected in the red and blue lines respectively. Calculate the reading of each wattmeter. Draw the circuit and vector diagrams. [Ans. $W_1 = -585$ W ; $W_2 = 2185$ W]



Transformers

1. General aspects 2. Basic definitions 3. Working principle of a transformer 4. Transformer ratings 5. Kinds of transformers 6. Transformer construction 7. Transformer windings, terminals, tappings and bushings 8. Transformer cooling 9. Single phase transformer : Elementary theory of an ideal transformer, E.m.f. equation of a transformer—Voltage transformation ratio—Transformer with losses but no magnetic leakage—Resistance and magnetic leakage—Transformer with resistance and leakage reactance—Equivalent resistance and reactance—Total voltage drop in a transformer—Equivalent circuit—Transformer tests—Regulation of a transformer—Percentage resistance and reactance—Transformer losses—Transformer efficiency—All-day efficiency—Transformer noise—Auto-transformer—Polarity of transformers 10. Three-phase transformer : Three-phase transformer connections, Three-phase transformer construction, Parallel operation of three-phase transformers—Highlights—Objective type questions—Theoretical questions—Unsolved Examples.

1. GENERAL ASPECTS

Although the transformer is not classified as an electric machine, the principles of its operation are fundamental for the induction motor and synchronous machines. Since A.C. electric machines are normally built for low frequencies only the low-frequency power transformer will be considered in this text.

Function. *The function of a transformer, as the name implies, is to transform alternating current energy from one voltage into another voltage. The transformer has no rotating parts, hence it is often called a static transformer.*

When energy is transformed into a higher voltage the transformer is called a *step-up transformer* but when the case is otherwise it is called a *step-down transformer*. Most power transformers operate at constant voltage, i.e. if the power varies the current varies while the voltage remains fairly constant.

Applications. A transformer performs many important functions in prominent areas of electrical engineering.

- In *electrical power engineering* the transformer makes it possible to convert electric power from a generated voltage of about 11 kV (as determined by generator design limitations) to higher values of 132 kV, 220 kV, 400 kV, 500 kV and 765 kV thus permitting transmission of huge amounts of power along long distances to appropriate distribution points at tremendous savings in the cost of transmission lines as well as in power losses.
- At *distribution points* transformers are used to reduce these high voltages to a safe level of 400/230 volts for use in homes, offices etc.
- In *electric communication circuits* transformers are used for a variety of purposes e.g., as an impedance transformation device to allow maximum transfer of power from the input circuit to the output device.

- In *radio and television circuits* input transformers, interstage transformers and output transformers are widely used.
- Transformers are also used in *telephone circuits, instrumentation circuits and control circuits*.

2. BASIC DEFINITIONS

- A *transformer* is a *static electromagnetic device designed for the transformation of the (primary) alternating current system into another (secondary) one of the same frequency with other characteristics, in particular, other voltage and current*.
- As a rule a transformer consists of a core assembled of sheet transformer steel and two or several windings coupled *electromagnetically*, and in the case of *autotransformer*, also *electrically*.
- A transformer with two windings is called *double-wound transformer*; a transformer with three or more windings is termed a *triple wound* or *multi-winding* one.
- According to the kind of current, transformers are distinguished as single-phase, three-phase and poly-phase ones. A *poly-phase transformer winding is a group of all phase windings of the same voltage*, connected to each other in a definite way.
- **Primary and secondary windings.** The transformer winding to which the energy of the alternating current is delivered is called the *primary winding*; the other winding from which energy is received is called the *secondary winding*.
- In accordance with the names of the windings, all quantities pertaining to the primary winding as, for example, power, current, resistance etc., are also primary, and those pertaining to the secondary winding secondary.
- **h.v. and l.v. windings.** The winding connected to the circuit with the higher voltage is called the *high-voltage winding* (h.v.), the winding connected to the circuit with the lower voltage is called the *low-voltage winding*. (l.v.). If the secondary voltage is *less* than the primary one, the transformer is called a *step-down transformer* and if *more-a step-up transformer*.
- **A tapped transformer** is one whose windings are fitted with special taps for changing its voltage or current ratio.
- **Oil and dry transformers.** To avoid the detrimental effect of the air on the winding insulation and improve the cooling conditions of the transformer its core together with the windings assembled on it is immersed in a tank filled with transformer oil. Such transformers are called **oil transformers**. Transformers not immersed in oil are called **dry transformers**.

3. WORKING PRINCIPLE OF A TRANSFORMER

A transformer operates on the principle of *mutual inductance*, between two (and sometimes more) inductively coupled coils. It consists of two windings in close proximity as shown in Fig. 1. *The two windings are coupled by magnetic induction.* (There is no conductive connection between the windings). One of the windings called *primary* is energised by a sinusoidal voltage. The second winding, called *secondary* feeds the load. The alternating current in the primary winding sets up an alternating flux (ϕ) in the core. The secondary winding is linked by most of this flux and e.m.f.s are induced in the two windings. The e.m.f. induced in the secondary winding drives a current through the load connected to the winding. Energy is transferred from the primary circuit to the secondary circuit through the medium of the magnetic field.

In brief, a transformer is a device that :

- transfers electric power from one circuit to another ;*
- it does so without change of frequency ; and*
- it accomplishes this by electromagnetic induction (or mutual inductance).*

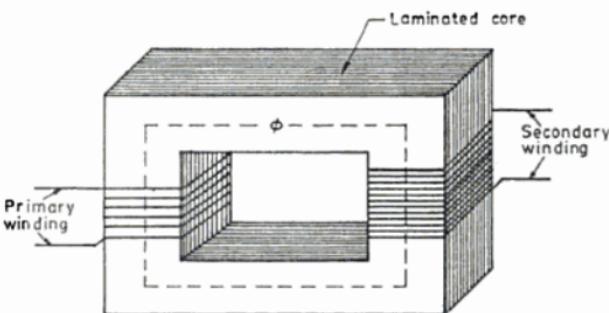


Fig. 1. Two winding transformer.

4. TRANSFORMER RATINGS

The rated quantities of a transformer, its power, voltage, frequency, etc. are given in Manufacturer's name plate, which should always be arranged so as to be accessible. But the term 'rated' can also be applied to quantities not indicated on the name plate, but relating to the rated duty, as for example, the rated efficiency, rated temperature conditions of the cooling medium, etc. :

- *The rated duty* of a transformer is determined by the quantities given in the name plate.
- *The rated power* of the transformer is the power at the secondary terminals, indicated in the name plate and expressed in kVA.
- *The rated primary voltage* is the voltage indicated in the transformer name plate ; if the primary is provided with taps, the rated tapped voltage is specially noted.
- *The rated secondary voltage* is the voltage across the transformer *secondary terminals at no-load* and with the rated voltage across the primary terminals ; if the secondary winding has taps, then their rated voltage is specially indicated.
- *The rated currents* of the transformer, primary and secondary, are the currents indicated in the name plate of the transformer and calculated by using the corresponding rated values of power and voltage.

5. KINDS OF TRANSFORMERS

The following kinds of transformers are the most important ones :

1. **Power transformers.** *For the transmission and distribution of electric power.*
 2. **Auto-transformers.** *For converting voltages within relatively small limits to connect power systems of different voltages, to start A.C. motors etc.*
 3. **Transformer for feed installations with static convertors.** (Mercury arc rectifiers, ignitrons, semi-conductor valves, etc.) *When converting A.C. into D.C. (rectifying) and converting D.C. into A.C. (inverting).*
 4. **Testing transformers.** *For conducting tests at high and ultra-high voltages.*
 5. **Power transformers for special applications.** Furnace, welding etc.
 6. **Radio-transformers.** *It is used in radio engineering etc.*
- Note.** *Distribution transformers* should be designed to have maximum efficiency at a load much *lower than full-load* (about 50 per cent).
- Power transformers* should be designed to have maximum efficiency *at or near full-load*.

6. TRANSFORMER CONSTRUCTION

All transformers have the following essential elements :

1. Two or more **electrical windings** insulated from each other and from the core (except in auto-transformers).

2. A **core**, which in case of a single-phase distribution transformers usually comprises *cold-rolled silicon-steel strip* instead of an assembly of punched silicon-steel laminations such as are used in the larger power-transformer cores. The *flux path in the assembled core is parallel to the directions of steel's grain or 'orientation'*. This results in a *reduction in core losses* for a given flux density and frequency, or it permits the use of *higher core densities and reduced size of transformers for given core losses*.

Other necessary parts are :

- A *suitable container* for the assembled core and windings.
- A *suitable medium* for insulating the core and its windings from each other and from the container.
- Suitable *bushings* for insulating and bringing the terminals of the windings out of the case.

The two basic types of transformer construction are :

1. *The core type*.
2. *The shell type*.

The above two types differ in their relative arrangements of copper conductors and the iron cores. In the '*core type*', the *copper virtually surrounds the iron core*, while in the '*shell type*', the *iron surrounds the copper winding*.

6.1. Core Type Transformer. The completed magnetic circuit of the core-type transformer is in the shape of the hollow rectangle, exactly as shown in Fig. 2 in which I_0 is the no-load current and ϕ is the flux produced by it. N_1 and N_2 are the number of turns on the primary and secondary sides respectively.

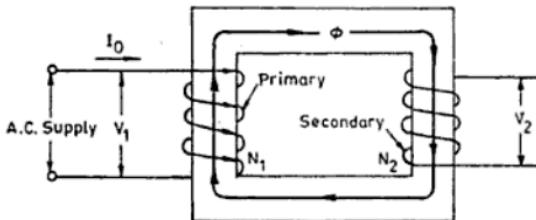


Fig. 2. Magnetic circuit of a core-type transformer.

The core is made up of *silicon-steel laminations* which are, either rectangular or L-shaped. With the coils wound on two legs the appearance is that of Fig. 3. If the two coils shown were the respective high and low-side coils as in Fig. 3, the *leakage reactance would be much too great*. In order to provide maximum *linkage* between windings, the group on *each leg is made up of both high-tension and low-tension coils*. This may be seen in Fig. 4, where a cross-sectional cut is taken across the legs of the core. By placing the high-voltage winding around the low-voltage winding, only one layer of high-voltage insulation is required, that between the two coils. If the high-voltage coils were adjacent to the core, an additional high-voltage insulation layer would be necessary between the coils and the iron core.

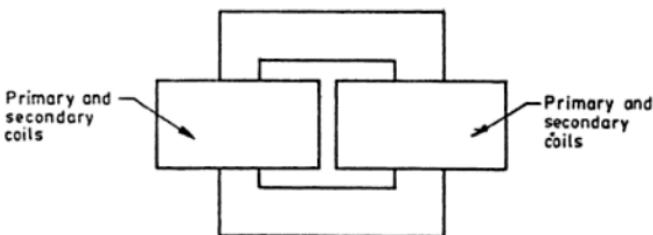


Fig. 3. Core-type transformer.

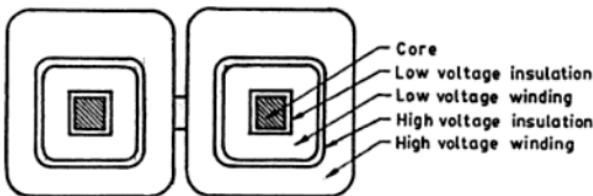


Fig. 4. Cross-section of a core-type transformer.

Fig. 5 shows the coils and laminations of a core-type transformer with a cruciform core and circular coils.

- Fig. 6 shows the different types of cores used in core type transformers.

Rectangular cores [Fig. 6 (a)] with rectangular cylindrical coils can be used for small size core-type transformers. For large size transformers it becomes wasteful to use rectangular cylindrical coils and so circular cylindrical coils are preferred. For such purposes, 'square cores' may be used as shown in Fig. 6 (b) where circles represent the tubular former carrying the coils. Evidently a considerable amount of useful space is still wasted. A common improvement on the square core is to employ a 'cruciform core' [Fig. 6 (c)] which demands, atleast, two sizes of core strips. For very large transformers, further core stepping is done as in Fig. 6 (d) where atleast three sizes of core plates are necessary. Core stepping not only gives high space factor but also results in reduced length of the mean turn and the consequent I^2R loss. Three stepped core is the most commonly used although more steps may be used for very large transformers as shown in Fig. [6 (e)].

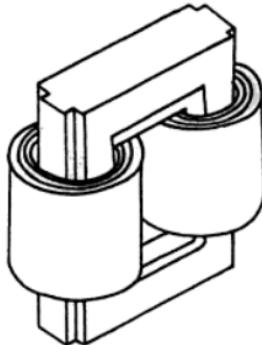


Fig. 5. Coils and laminations of a core-type transformer.

6.2. Shell Type Transformer. In the shell-type construction the iron almost entirely surrounds the copper (Fig. 7). The core is made up of E-shaped or F-shaped laminations which are stacked to give a rectangular figure eight. All the windings are placed on the centre leg, and in order to reduce leakage, each high-side coil is adjacent to a low-side coil. The coils actually occupy the entire space of both windows, are flat or pancake in shape, and are usually constructed of strip copper. Again, to reduce the amount of high-voltage insulation required, the low-voltage coils are placed adjacent to the iron core.

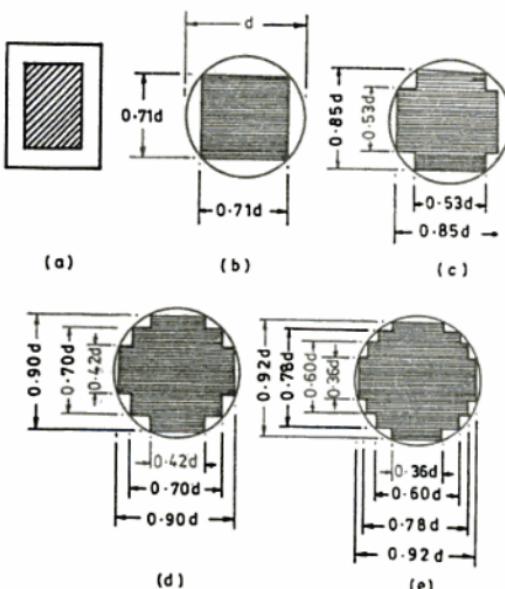


Fig. 6. Various types of cores.

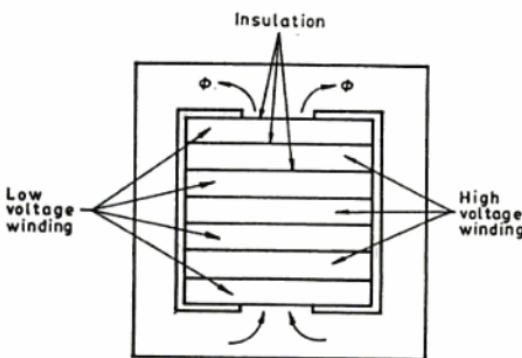


Fig. 7. Shell-type transformer.

Fig. 8 shows the coils and laminations of a typical shell-type transformer.

Choice of Core- or Shell Type Construction. In general, the core-type has a longer mean length of core and a shorter mean length of coil turn. The core type also has a smaller cross-section of iron and so will need a greater number of turns of wire, since, in general, not as high a flux may be reached in the core. However, *core type is better adopted for some high-voltage service since there is more room for insulation. The shell type has better provision for mechanically supporting and*

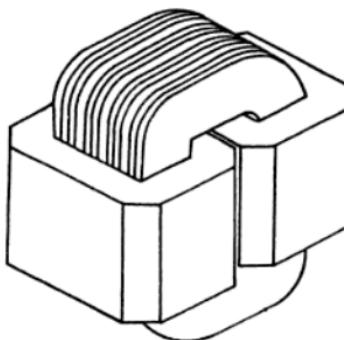


Fig. 8. Coils and laminations of a shell-type transformer.

bracing the coils. This allows better resistance to the very high mechanical forces that develop during a high-current short circuit.

The choice of core- or shell type construction is usually one of cost, for similar characteristics can be obtained with both types.

Both core and shell forms are used, and selection is based upon many factors such as voltage rating, kVA rating, weight, insulation stress, mechanical stress, and heat distribution.

6.3. Spiral Core Transformer. The typical spiral core is shown in Fig. 9. The core is assembled either of a continuous strip of transformer steel wound in the form of a circular or elliptical cylinder or of a group of short strips assembled to produce the same elliptical-shaped core. By using this construction the core flux always follows along the grain of the iron. Cold-rolled steel of high silicon content enables the designer to use higher operating flux densities with lower loss per kg. *The higher flux density reduces the weight per kVA.*

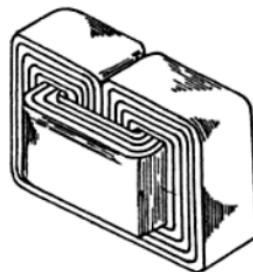


Fig. 9. Spiral-core transformer.

7. TRANSFORMER WINDINGS, TERMINALS, TAPPINGS AND BUSHINGS

7.1. Transformer Windings. The most important requirements of transformer windings are :

1. The winding should be *economical both as regards initial cost*, with a view to the market availability of copper, and the efficiency of the transformer in service.
2. The heating conditions of the windings should *meet standard requirements*, since departure from these requirements towards allowing higher temperature will drastically shorten the service life of the transformer.
3. The winding should be *mechanically stable* in respect to the forces appearing when sudden short circuit of the transformer occur.
4. The winding should have the *necessary electrical strength in respect to over voltages*.

The different types of windings are classified and briefly discussed below :

1. Concentric windings :

(i) Cross-over

(ii) Helical

(iii) Disc.

2. Sandwich windings

1. Concentric windings. Refer Fig. 10. These windings are used for core type transformers. Each limb is wound with a group of coils consisting of both primary and secondary turns which may be concentric cylinders. The l.v. winding is placed next to the core and h.v. winding on the outside. But the two windings can be sub-divided, and interlaced with high tension and low tension section alternately to reduce leakage reactance. These windings can be further divided as follows :

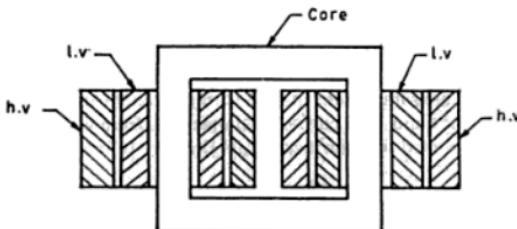


Fig. 10. Concentric coils.

(i) Cross-over windings. Cross-over windings are used for currents up to 20 A and so they are suitable for h.v. winding of small transformers. The conductors are either cotton covered round wires or strips insulated with paper. Cross-over coils are wound over formers and each coil consists of a number of layers with a number of turns per layer. The complete winding consists of a number of coils connected in series. Two ends of each coil are brought out, one from inside and one from outside. The inside end of a coil is connected to the outside end of the adjacent coil.

(ii) Helical winding. A helical winding consists of rectangular strips wound in the form of a helix. The strips are wound in parallel radially and each turn occupies the total radial depth of winding.

Helical coils are well suited for l.v. windings of large transformers. They can also be used for h.v. windings by putting extra insulation between layers in addition to insulation of conductors.

(iii) Continuous disc winding. This type of winding consists of a number of flat strips wound spirally from inside (radially) outwards. The conductor is used in such lengths as are sufficient for complete winding or section of winding between tappings. The conductor can either be a single strip or a number of strips in parallel, wound on the flat. This gives a robust construction for each disc. The discs are wound on insulating cylinders spaced from it by strips along the length of cylinder. The discs are separated from each other with press board sectors attached to the vertical strips. The vertical and horizontal spacers provide ducts for free circulation of oil which is in contact with every turn.

2. Sandwich coils. Sandwich coils (Fig. 11) are employed in transformers of shell type. Both high and low voltage windings are split into a number of sections. Each high voltage section lies between the low voltage sections.

The advantage of sandwich coils is that their leakage can be easily controlled and so any desired value of leakage reactance can be had by the division of windings.

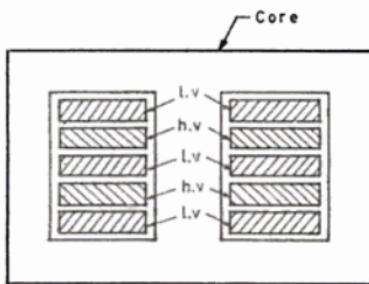


Fig. 11. Sandwich coils.

7.2. Terminals and Leads. The connection to the windings are of insulated copper rods or bars. The shape and size of leads is important in high voltage transformers owing to dielectric stress and corona which are caused at bends and corners. Connections from windings are directly taken to the busbars in the case of air-cooled transformers while they are taken to insulated bushings in the case of oil-cooled transformers.

7.3. Tappings. In a supply network the voltage can be controlled by changing the transformation ratio. This can be done by tapping the winding in order to alter the number of turns. The change in number of turns may be effected when the transformer is out of circuit (known as off load tap changing) or when on load (known as on load tap changing). *The tappings are provided on the high voltage winding because a fine voltage variation is obtained owing to large number of turns. It is difficult to obtain voltage variation within close percentage limits in low voltage winding as there are few turns and voltage per turn is a large percentage of the total voltage.*

In transformers, the tappings can be provided at :

- (i) phase ends ; and
- (ii) neutral point or in the middle of the windings.

- The advantage of providing tappings at *phase ends* is that the number of bushing insulators is reduced, this is important where the cover space is limited. Some transformers have reinforced insulation at the phase ends. It is essential that in such cases either the tapping should not be provided at end turns or the reinforcement should be carried beyond the lower tap.
- When the tappings are made at the *neutral point* the insulation between various parts is small. *This arrangement is economical especially in the case of high voltage transformers.*

7.4. Bushings. The bushings are employed for insulating and bringing out terminals of the winding from the container to the external circuit. For low-voltage transformers this is accomplished by employing *bushings of porcelain around the conductor at the point of entry*. For high voltages it is necessary to employ bushings of larger sizes. In modern transformers the problem is met by using *large porcelain or composition bushings for voltages as high as 33 kV, above that oil filled or condenser type bushings are used.*

8. TRANSFORMER COOLING

8.1. Cooling Methods. The transformers get heated due to iron and copper losses occurring in them. It is necessary to dissipate this heat so that the temperature of the windings is kept below the value at which the insulation begins to deteriorate. *The cooling of transformers is more difficult than that of rotating machines because the rotating machines create a turbulent air flow which assists in removing the heat generated due to losses.* Luckily the losses in transformers are comparatively

small. Nevertheless the elaborate cooling arrangements have been devised to deal with the whole range of sizes.

As far as cooling methods are concerned, the transformers are of following two types :

1. Dry type.

2. Oil immersed type.

Dry Type Transformers. Small transformers upto 25 kVA size are of the dry type and have the following cooling arrangements :

(i) **Air natural.** In this method the natural circulation of surrounding air is utilized to carry away the heat generated by losses. A sheet metal enclosure protects the winding from mechanical injury.

(ii) **Air blast.** Here the transformer is cooled by a continuous blast of cool air forced through the core and windings (Fig. 12). The blast is produced by a fan. The air supply must be filtered to prevent accumulation of dust in ventilating ducts.

Oil Immersed Transformers. In general most transformers are of oil immersed types. The *oil provides better insulation than air and it is a better conductor of heat than air*. Mineral oil is used for this purpose.

Oil immersed transformers are classified as follows :

(i) **Oil immersed self-cooled transformers.** The transformer is immersed in oil and heat generated in cores and windings is passed to oil by conduction. Oil in contact with heated parts rises and its place is taken by cool oil from the bottom. The natural oil transfers its heat to the tank walls from where heat is taken away by the ambient air. The oil gets cooler and falls to the bottom from where it is dissipated into the surroundings. The tank surface is the best dissipator of heat but a plain tank will have to be excessively large, if used without any auxiliary means for high rating transformers. As both space and oil are costly, these auxiliary means should not increase the cubic capacity of the tank. The heat dissipating capacity can be increased by providing (i) corrugations, (ii) fins, (iii) tubes (Fig. 13) and (iv) radiator tanks.

The advantages of 'oil natural' cooling is that it does not clog the ducts and the windings are free from effects of moisture.

(ii) **Oil immersed forced air-cooled transformers.** In this type of cooling, air is directed over the outer surfaces of the tank of the transformer immersed in oil.

(iii) **Oil immersed water-cooled transformers.** Heat is extracted from the oil by means of a stream of water pumped through a metallic coil immersed in the oil just below the top of the tank. The heated water is in turn cooled in a spray pond or a cooling tower.

(iv) **Oil immersed forced oil cooled transformers.** In such transformers heat is extracted from the oil by pumping the oil itself upward through the winding and then back by way of external radiators which themselves be cooled by fans. The *extra cost of oil pumping equipment must of*

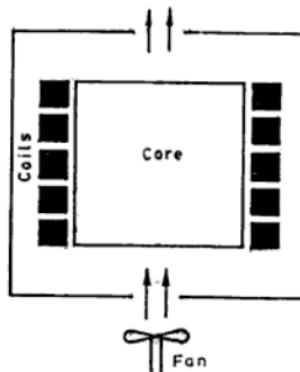


Fig. 12

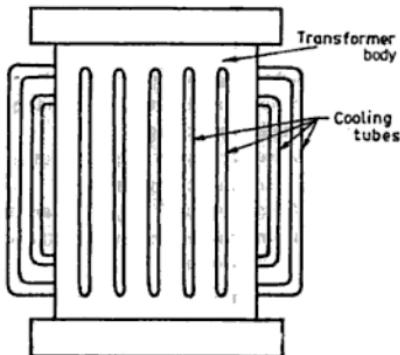


Fig. 13. Transformer with cooling tubes.

course be economically justified but it has incidentally the advantage of reducing the temperature difference between the top and bottom of enclosing tank.

Fig. 14 shows the cooling of transformers having capacities from 10000 kVA and higher. In such cases air blast cooling of radiator is used.

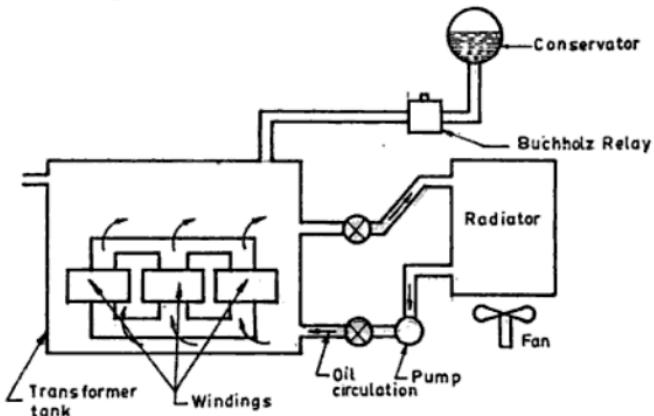


Fig. 14. Air blast cooling of radiator.

8.2. Transformer Oil. It is a mineral oil obtained by refining crude petroleum. It serves the following purposes :

- (i) Provides additional insulation.
- (ii) Carries away the heat generated in the core and coils.
- (iii) Protects the paper from dirt and moisture.

The transformer oil should possess the following properties :

1. High dielectric strength.
2. Low viscosity to provide good heat transfer.
3. Good resistance to emulsion.
4. Free from inorganic acid, alkali and corrosive sulphur.
5. Free from sludging under normal operating conditions.
6. High flash/fire point.

8.3. Conservator and Breather

Conservator. The oil should not be allowed to come in contact with atmospheric air as it may take up moisture which may spoil its insulating properties. Also air may cause acidity and sludging of oil. To prevent this, many transformers are provided with conservators. The function of a conservator (Fig. 14) is to take up contraction and expansion of oil without allowing it to come in contact with outside air. The conservator consists of an air tight metal-drum fixed above the level of the top of the tank and connected with it by a pipe. The main tank is completely filled with oil when cold. The conservator is partially filled with oil. So the oil surface in contact with air is greatly reduced. The sludge thus formed remains in the conservator itself and does not go to the main tank.

Breather. When the temperature changes, the oil expands or contracts and there is a displacement of air. When the transformer cools, the oil level goes down, and air is drawn in. This is known as *breathing*. The air, coming in, is passed through an apparatus called *breather* for the

purpose of extracting moisture. The breather consists of a small vessel which contains a drying agent like silica gel crystal impregnated with cobalt crystal.

Note. Sludging means the slow formation of solid hydrocarbons due to heating and oxidation. The sludge deposit itself on the windings and cooling ducts producing overheating. This makes transformer still hotter producing more sludge. This process may continue till the transformer becomes unusable due to overheating. So the contact of oil with air should be avoided as the air contains oxygen.

9. SINGLE PHASE TRANSFORMER

9.1. Elementary Theory of an Ideal Transformer. The basic theory of a transformer is not difficult to understand. To simplify matters as much as possible, let us first consider an *ideal transformer*, that is, one in which the resistance of the windings is negligible and the core has no losses.

Let the secondary be open (Fig. 15), and let a sine wave of potential difference v_1 (Fig. 16) be impressed upon the primary. The impressed potential difference causes an alternating current to

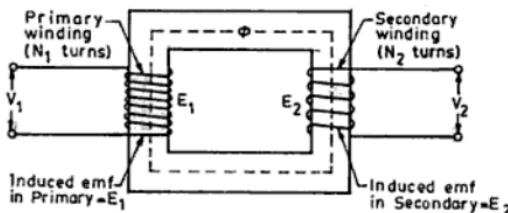


Fig. 15. Elementary diagram of an ideal transformer with an open secondary winding.

flow in the primary winding. Since the primary resistance is negligible and there are no losses in the core, the effective resistance is zero and the circuit is purely reactive. Hence the current wave i_m lags the impressed voltage wave v_1 by 90° time degrees, as shown in Fig. 17. The reactance of circuit is very high and the magnetizing current is very small. This current in the N_1 turns of the primary magnetizes the core and produces a flux ϕ that is at all times proportional to the current (if the permeability of the circuit is assumed to be constant), and therefore in time phase with the current. The flux, by its rate of change, induces in the primary winding E_1 which at every instant of time is equal in value and opposite in direction to V_1 . It is called *counter e.m.f.* of the primary. The value which the primary current attains must be such that the flux which it produces in the core is of sufficient value to induce in the primary the required counter e.m.f.

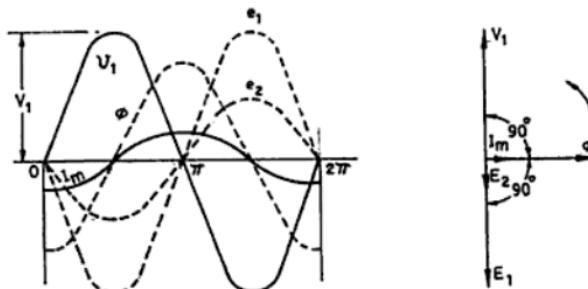


Fig. 16, 17. Current, voltage and flux curves of an ideal (no loss) transformer.

Since the flux also threads (or links) the secondary winding a voltage e_2 is induced in the secondary. This voltage is likewise proportional to the rate of change of flux and so is in time phase with e_1 , but it may have any value depending upon the number of turns N_2 in the secondary.

9.2. E.M.F. Equation of a Transformer

Let N_1 = number of turns in primary,

N_2 = number of turns in secondary,

ϕ_m = maximum flux in the core, Wb.

$= B_m \times A$, [where B_m is the maximum flux density in the core and A is the core area], and

f = frequency of a.c. input, Hz.

Refer Fig. 18. Since the flux increases from its zero value to maximum value ϕ_m in one quarter of the cycle i.e. in $\frac{T}{4}$ or $\frac{1}{4f}$ second (T being time-period of the cycle),

∴ Average rate of change of flux

$$= \frac{\phi_m}{\frac{1}{4}} = 4f\phi_{\max} \text{ Wb/s or volt}$$

If flux ϕ varies sinusoidally, then r.m.s. (root mean square) value of induced e.m.f. is obtained by multiplying the average value with form factor.

But, form factor $= \frac{\text{r.m.s. value}}{\text{average value}} = 1.11$

∴ r.m.s. value of e.m.f./turn

$$= 1.11 \times 4f\phi_{\max} = 4.44f\phi_{\max} \text{ volt}$$

Now, r.m.s. value of induced e.m.f. in the whole of primary winding,

$$E_1 = 4.44f\phi_{\max} N_1 \quad \dots(1)$$

Similarly r.m.s. value of induced e.m.f. in secondary is,

$$E_2 = 4.44f\phi_{\max} N_2 \quad \dots(2)$$

In an ideal transformer on no-load $V_1 = E_1$ and $V_2 = E_2$ (Fig. 15).

9.3. Voltage Transformation Ratio (K). The transformation ratio is defined as the ratio of the secondary voltage to primary voltage. It is denoted by the letter K .

$$\text{From eqns. (1) and (2), } \frac{E_2}{E_1} = \frac{N_2}{N_1} = K$$

- If $N_2 > N_1$ i.e. $K > 1$, then transformer is called step-up transformer.

- If $N_2 < N_1$ i.e. $K < 1$, then transformer is called step-down transformer.

Again for an ideal transformer

Input (VA) = Output (VA)

$$V_1 I_1 = V_2 I_2 \text{ or } E_1 I_1 = E_2 I_2$$

$$\frac{I_2}{I_1} = \frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{1}{K} \quad \dots(4)$$

i.e., Primary and secondary currents are inversely proportional to their respective turns.

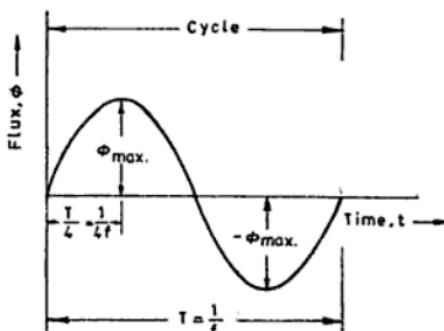


Fig. 18

Example 1. A 40 kVA, single phase transformer has 400 turns on the primary and 100 turns on the secondary. The primary is connected to 2000 V, 50 Hz supply. Determine :

- The secondary voltage on open circuit.
- The current flowing through the two windings on full-load.
- The maximum value of flux.

Solution. Rating = 40 kVA

Primary turns, $N_1 = 400$

Secondary turns, $N_2 = 100$

Primary induced voltage, $E_1 = V_1 = 2000 \text{ V}$

(i) Secondary voltage on open circuit V_2 :

Using the relation,

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$E_2 = E_1 \times \frac{N_2}{N_1}$$

$$\therefore E_2 = V_2 = 2000 \times \frac{100}{400} = 500 \text{ V}$$

Hence, $V_2 = 500 \text{ V. (Ans.)}$

(ii) Primary current, I_1 :

Secondary current, I_2 :

Primary full-load current, $I_1 = \frac{\text{kVA} \times 1000}{V_1} = \frac{40 \times 1000}{2000} = 20 \text{ A. (Ans.)}$

Secondary full-current, $I_2 = \frac{\text{kVA} \times 1000}{V_2} = \frac{40 \times 1000}{500} = 80 \text{ A (Ans.)}$

(iii) Maximum value of flux, ϕ_{\max} :

Using e.m.f. equation, $E_1 = 4.44f\phi_{\max} N_1$

$$\therefore 2000 = 4.44 \times 50 \times \phi_{\max} \times 400$$

$$\therefore \phi_{\max} = \frac{2000}{4.44 \times 50 \times 400} = 0.0225 \text{ Wb.}$$

Hence, $\phi_{\max} = 0.0225 \text{ Wb. (Ans.)}$

Example 2. The no-load ratio required in a single-phase 50 Hz transformer is 6600/600 V. If the maximum value of flux in the core is to be about 0.08 Wb, find the number of turns in each winding.

Solution. Primary, $E_1 = V_1 = 6600 \text{ V}$

Secondary, $E_2 = V_2 = 600 \text{ V}$

Maximum value of flux $\phi_{\max} = 0.08 \text{ Wb.}$

Primary turns, N_1 :

Secondary turns, N_2 :

Using the relation,

$$E_1 = 4.44f\phi_{\max} N_1$$

$$6600 = 4.44 \times 50 \times 0.08 \times N_1$$

$$\therefore N_1 = \frac{6600}{4.44 \times 50 \times 0.08} \approx 372$$

Hence, $N_1 = 372. \text{ (Ans.)}$

Also

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

∴

$$N_2 = \frac{E_2 N_1}{E_1} = \frac{600 \times 372}{6600} = 34$$

Hence,

$$N_2 = 34. \text{ (Ans.)}$$

Example 3. A single-phase transformer is connected to a 230 V, 50 Hz supply. The net cross-sectional area of the core is 60 cm^2 . The number of turns in the primary is 500 and in the secondary 100. Determine :

- (i) Transformation ratio.
- (ii) E.m.f. induced in secondary winding.
- (iii) Maximum value of flux density in the core.

Solution. Primary turns,

$$N_1 = 500$$

Secondary turns,

$$N_2 = 100$$

Primary,

$$E_1 = V_1 = 230 \text{ V}$$

Core area,

$$a = 60 \text{ cm}^2 = 60 \times 10^{-4} \text{ m}^2$$

(i) Transformation ratio, K :

$$K = \frac{N_2}{N_1} = \frac{100}{500} = 0.2$$

Hence,

$$K = 0.2. \text{ (Ans.)}$$

(ii) Maximum value of flux density, B_{\max} :

Using the e.m.f. equation,

$$E_1 = 4.44 f \phi_{\max} N_1$$

∴

$$230 = 4.44 \times 50 \times \phi_{\max} \times 500$$

or

$$\phi_{\max} = \frac{230}{4.44 \times 50 \times 500} = 0.00207 \text{ Wb}$$

Now,

$$B_{\max} = \frac{\phi_{\max}}{A} = \frac{0.00207}{60 \times 10^{-4}} = 0.345 \text{ T}$$

[where T stands for tesla (Wb/m^2)]

Hence,

$$B_{\max} = 0.345 \text{ T. (Ans.)}$$

- (iii) E.m.f. induced in the secondary winding, E_2 :

Using the relation,

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\frac{E_2}{230} = \frac{100}{500}$$

∴

$$E_2 = 46 \text{ V. (Ans.)}$$

Example 4. 3300/300 V single-phase 300 kVA transformer has 1100 primary turns. Find :

- (i) Transformation ratio.
- (ii) Secondary turns.
- (iii) Voltage/turn.
- (iv) Secondary current when it supplies a load of 200 kW at 0.8 power factor lagging.

Solution. Primary,

$$E_1 = 3300 \text{ V}$$

$$N_1 = 1100$$

Secondary,

$$E_2 = 300 \text{ V}$$

Rating of the transformer

$$= 300 \text{ kVA}$$

Output

$$= 200 \text{ kW}$$

(i) Transformation ratio, $K = ?$

$$K = \frac{N_2}{N_1} = \frac{E_2}{E_1} = \frac{300}{3300} = \frac{1}{11}$$

Hence,

$$K = \frac{1}{11}. \quad (\text{Ans.})$$

(ii) Secondary turns, $N_2 = ?$

Using the relation,

$$\frac{E_2}{E_1} = \frac{N_2}{N_1}$$

$$\therefore N_2 = \frac{E_2 N_1}{E_1} = \frac{300 \times 1100}{3300} = 100$$

Hence,

$$N_2 = 100. \quad (\text{Ans.})$$

(iii) Voltage/turn = ?

Voltage/turn

$$\frac{E_1}{N_1} = \frac{3300}{1100} = 3 \text{ V.} \quad (\text{Ans.})$$

(iv) Secondary current,

$$I_2 = \frac{\text{Output}}{V_2 \cos \phi} = \frac{200 \times 1000}{300 \times 0.8} = 833.33 \text{ A}$$

Hence,

$$I_2 = 833.33 \text{ A.} \quad (\text{Ans.})$$

Example 5. The voltage per turn of a single-phase transformer is 1.1 V. When the primary winding is connected to a 220 V, 50 Hz A.C. supply, the secondary voltage is found to be 550 V. Find :

(i) Primary and secondary turns.

(ii) Core area if the maximum flux density is 1.1 T.

Solution. Voltage per turn = 1.1 V

Primary, $E_1 = 220 \text{ V}$

Secondary, $E_2 = 550 \text{ V}$

Max. flux density, $B_{\max} = 1.1 \text{ T}$

$$(i) \text{Primary turns, } N_1 = \frac{E_1}{1.1} = \frac{220}{1.1} = 200. \quad (\text{Ans.})$$

$$\text{Secondary turns, } N_2 = \frac{E_2}{1.1} = \frac{550}{1.1} = 500. \quad (\text{Ans.})$$

(ii) Core area A :

Using the relation, $E_1 = 4.44 f \Phi_{\max} N_1$

$$220 = 4.44 \times 50 \times \Phi_{\max} \times 200$$

$$\therefore \Phi_{\max} = \frac{220}{4.44 \times 50 \times 200} = 0.004955 \text{ Wb}$$

$$\text{Core area, } A = \frac{\Phi_{\max}}{B_{\max}} = \frac{0.004955}{1.1} = 0.004504 \text{ m}^2 = 45.04 \text{ cm}^2. \quad (\text{Ans.})$$

Example 6. The core of 1000 kVA, 11000/550 V, 50 Hz, single-phase transformer has a cross-section of 20 cm × 20 cm. If the maximum core density is not to exceed 1.3 tesla, calculate :

(i) The number of h.v. and l.v. turns per phase.

(ii) The e.m.f. per turns.

Assume a stacking factor of 0.9.

Solution. Given : $A = 20 \text{ cm} \times 20 \text{ cm} = 400 \times 10^{-4} \text{ m}^2$; $B_{\max} = 1.3 \text{ Wb/m}^2$, $f = 50 \text{ Hz}$;
 $E_1 = 11000 \text{ V}$; $E_2 = 550 \text{ V}$; Stacking factor = 0.9

(i) Number of turns N_1 (h.v.) ; N_2 (l.v.) :

We know that, Flux = flux density \times area of cross-section \times stacking factor

$$\therefore \quad \phi_{max} = 1.3 \times 400 \times 10^{-4} \times 0.9 = 0.0468 \text{ Wb}$$

$$E_1 = 4.44 f \phi_{max} N_1$$

$$\text{or} \quad 11000 = 4.44 \times 50 \times 0.0468 \times N_1$$

$$\therefore \quad N_1 = \frac{11000}{4.44 \times 50 \times 0.0468} = 1058.75 \approx 1059. \text{ (Ans.)}$$

$$\text{and} \quad N_2 = \frac{E_2}{E_1} \times N_1 = \frac{550}{11000} \times 1059 = 52.95 \approx 53. \text{ (Ans.)}$$

(ii) The e.m.f. per turn :

$$\text{E.M.F. per turn} \quad = \frac{E_1}{N_1} = \frac{11000}{1059} = 10.387 \text{ V. (Ans.)}$$

9.4. Transformer with Losses but no Magnetic Leakage. We shall consider the following two cases :

1. When transformer is on no-load.
2. When transformer is on load.

9.4.1. Transformer on no-load. A transformer is said to be on *no-load* if its secondary side is open and primary is connected to a sinusoidal alternating voltage V_1 . The alternating applied voltage will cause *flow of alternating current in the primary winding which will create alternating flux*. This primary input current (I_0) under no-load conditions supply :

(i) *Iron losses in the core (i.e. hysteresis loss and eddy current loss).*

(ii) *A very small amount of copper losses in primary* (there being no copper loss in the secondary as it is open).

Thus I_0 is not at 90° behind V_1 , but lags it by an angle $\phi_0 < 90^\circ$.

No-load power input, $P_0 = V_1 I_0 \cos \phi_0$

where $\cos \phi_0$ = primary power factor under no-load conditions.

As is evident from Fig. 19, primary current I_0 has the following two components :

(i) *Active or working or iron loss component I_w* . This component is in phase with V_1 and mainly supplies the iron loss plus small quantity of primary copper loss.

$$I_w = I_0 \cos \phi_0 \quad \dots(i)$$

(ii) *Magnetising component I_m* . This component is in quadrature with V_1 and its function is to sustain the alternating flux in the core. It is wattless.

$$I_m = I_0 \sin \phi_0 \quad \dots(ii)$$

$$\text{Also} \quad I_0 = \sqrt{I_w^2 + I_m^2} \quad \dots(iii)$$

The following points are worth noting :

- The no-load primary current I_0 is very small as compared to the full-load primary current.
- As I_0 is very small, the no-load primary copper loss is negligibly small which means that *no-load primary input is practically equal to the iron loss in the transformer.*

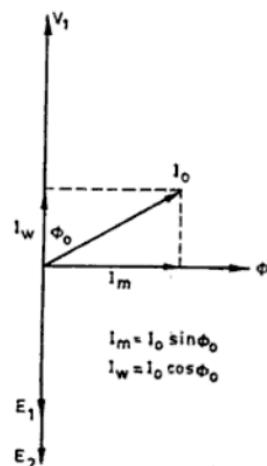


Fig. 19. No-load vector diagram.

- Since, it is primarily the core loss which is responsible for shift in the current vector, angle ϕ_0 is known as **hysteresis angle of advance**.

Example 7. A 3300/300 V single-phase transformer gives 0.6 A and 60 W as ammeter and wattmeter readings when supply is given to the low voltage winding and high voltage winding is kept open, find :

- Power factor of no-load current.
- Magnetising component.
- Iron loss component.

Solution. No-load losses, $P_0 = 60$ W

No-load current, $I_0 = 0.6$ A

$$(i) \quad P_0 = VI_0 \cos \phi_0$$

$$\therefore \quad 60 = 300 \times 0.6 \times \cos \phi_0$$

$$\text{or} \quad \cos \phi_0 = \frac{60}{300 \times 0.6} = 0.33 \text{ (lagging)}$$

Hence, power factor of no-load current = 0.33. (Ans.)

$$(ii) \text{ Magnetising component, } I_m = I_0 \sin \phi_0 = 0.6 \sqrt{1 - \cos^2 \phi_0} = 0.6 \sqrt{1 - (0.33)^2} = 0.566 \text{ A}$$

$$\therefore \quad I_m = 0.566 \text{ A. (Ans.)}$$

$$(iii) \text{ Iron loss component, } I_w = I_0 \cos \phi_0 = 0.6 \times 0.33 = 0.198 \text{ A. (Ans.)}$$

$$\text{[or} \quad I_w = \sqrt{I_0^2 - I_m^2} = \sqrt{(0.6)^2 - (0.566)^2} = 0.198 \text{ A].}$$

Example 8. Find (i) active and reactive components of no-load current ; and (ii) no-load current of a 440/220 V single-phase transformer if the power input on no-load to the high voltage winding is 80 W and power factor of no-load current is 0.3 lagging.

Solution. Primary, $E_1 = 440$ V

Secondary, $E_2 = 220$ V

Power factor, $\cos \phi_0 = 0.3$ (lagging)

No-load losses, $P_0 = 80$ W

(i) **Active component** (or wattful component),

$$I_w = (I_0 \cos \phi_0) = \frac{P_0}{V_1} = \frac{80}{440} = 0.182 \text{ A. (Ans.)}$$

$$\cos \phi_0 = 0.3 ; \phi_0 = \cos^{-1}(0.3) = 72.54^\circ$$

$$\therefore \quad \tan \phi_0 = 3.18$$

Reactive component (or magnetising components)

$$I_m = I_w \tan \phi_0 = 0.182 \times 3.18 = 0.578 \text{ A. (Ans.)}$$

$$(ii) \quad I_w = I_0 \cos \phi_0$$

$$\therefore \quad I_0 = \frac{I_w}{\cos \phi_0} = \frac{0.182}{0.3} = 0.606. \text{ (Ans.)}$$

$$\text{or} \quad |I_0| = \sqrt{I_w^2 + I_m^2} = \sqrt{(0.182)^2 + (0.578)^2} = 0.606 \text{ A.}$$

Example 9. A 3300/220 V, 30 kVA, single-phase transformer takes a no-load current of 1.5 A when the low voltage winding is kept open. The iron loss component is equal to 0.4 A find :

(i) No-load input power.

(ii) Magnetising component and power factor of no-load current.

Solution. Rating of transformer = 30 kVA

Primary,	$E_1 = 3300 \text{ V}$
Secondary,	$E_2 = 220 \text{ V}$
No-load current,	$I_0 = 1.5 \text{ A}$
Iron loss component,	$I_m = 0.4 \text{ A}$

(i) No-load input power,

$$P_0 = V_1 I_0 \cos \phi_0 = V_1 I_w \quad (\because I_w = I_0 \cos \phi_0)$$

$$= 3300 \times 0.4 = 1320 \text{ W. (Ans.)}$$

(ii) Magnetising component,

$$I_m = \sqrt{I_0^2 - I_w^2} = \sqrt{1.5^2 - 0.4^2} = 1.44 \text{ A. (Ans.)}$$

No-load power factor,

$$\cos \phi_0 = \frac{I_w}{I_0} = \frac{0.4}{1.5} = 0.267. \text{ (Ans.)}$$

9.4.2. Transformer on load. The transformer is said to be loaded when the secondary circuit of a transformer is completed through an impedance or load. The magnitude and phase of secondary current I_2 with respect to secondary terminal voltage will depend upon the characteristic of load, i.e. current I_2 will be in phase, lag behind and lead the terminal voltage V_2 respectively when the load is purely resistive, inductive and capacitive.

The secondary current I_2 sets up its own ampere-turns ($= N_2 I_2$) and creates its own flux ϕ_2 opposing the main flux ϕ_0 created by no-load current I_0 . The opposing secondary flux ϕ_2 weakens the primary flux ϕ_0 momentarily hence primary counter or back e.m.f. E_1 tends to be reduced. V_1 gains the upper hand over E_1 momentarily and hence causes more current to flow in primary. Let this additional primary current be I_2' . It is known as *load component of primary current*. The additional primary m.m.f. $N_1 I_2'$ sets up its own flux ϕ_2' which is in opposition to ϕ_2 (but is in the same direction as ϕ_0) and is equal to it in magnitude. Hence they cancel each other. Thus we find that the magnetic effects of secondary current I_2 are immediately neutralised by the additional primary current I_2' which is brought into existence exactly at the same instant as I_2 .

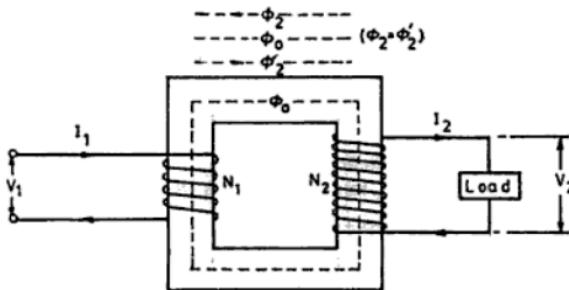


Fig. 20. An ideal transformer on load.

From above discussion it can be concluded that :

- Whatever be the load conditions, the net flux passing through the core is approximately the same as at no-load.
- Since the core flux remains constant at all loads, the core loss almost remains constant under different loading conditions.

Since

$$\phi_2 = \phi_2'$$

∴

$$N_2 I_2 = N_1 I_2'$$


i.e.,

$$I_2' = \frac{N_2}{N_1} \times I_2 = K I_2$$

$$\left(\because \frac{N_2}{N_1} = K \right)$$

The total primary current is the vector sum of I_0 and I_2' ; the current I_2' is in *antiphase* with I_2 and K times in magnitude.

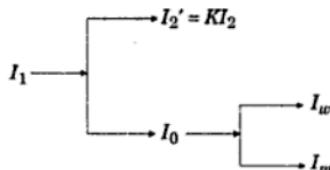The components of primary current can be shown as below :



The vector diagrams for transformer on non-inductive, inductive and capacitive loads are shown in Fig. 21 (a, b, c).

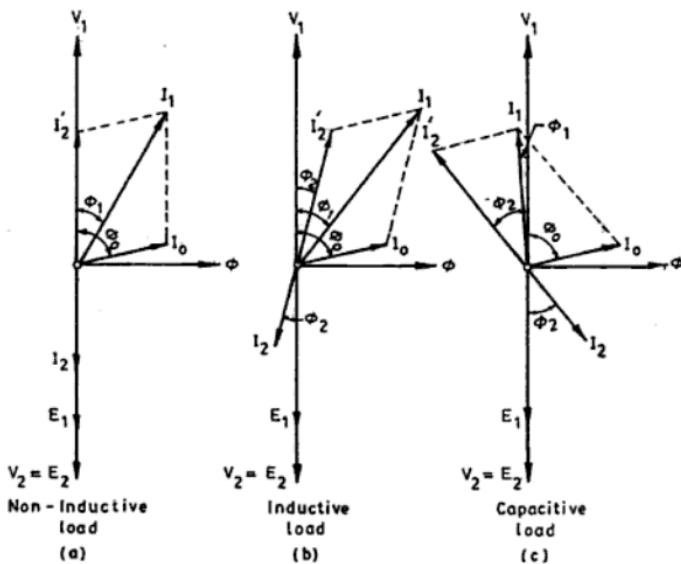


Fig. 21

9.5. Resistance and Magnetic Leakage. In an ideal transformer it is assumed that windings have got no resistance and there is no leakage flux. But in actual practice it is not possible to have an ideal transformer.

Resistance. In an actual transformer the primary as well secondary winding possess some resistance due to which some voltage drop takes place in them.

Magnetic leakage. Magnetic flux cannot be confined into a desired path. The greater portion of the flux (*i.e.*, the mutual flux) remains confined to the core and links both the windings but a small portion, called the *leakage flux*, completes its path through the air surrounding the coils. As shown in Fig. 22 each of the winding is associated with a leakage flux. Since the path of the leakage flux is

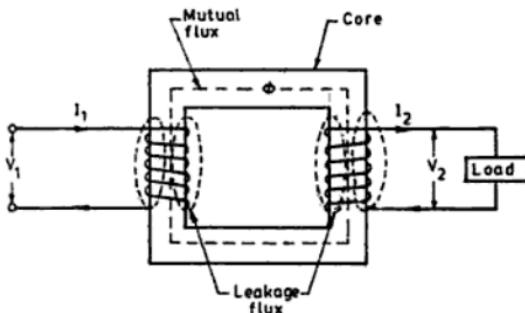


Fig. 22. Magnetic flux in a transformer.

largely in air the leakage flux and the voltage induced by it vary *linearly with the current*. The primary leakage flux varies linearly with the primary current and the secondary leakage flux varies linearly with the secondary current. The effect of primary leakage may be simulated by assigning to the primary a leakage inductance (equal to primary leakage flux per ampere of primary current). The reactance corresponding to this primary leakage inductance (*i.e.* $2\pi f \times$ primary leakage inductance) is known as primary leakage reactance X_1 . Similarly the effect of secondary leakage flux may be simulated by a secondary leakage inductance and the corresponding leakage reactance X_2 .

The terminal voltage V_1 applied to the primary must have a component $jI_1 X_1$ to balance the primary leakage e.m.f. Similarly V_2 *i.e.* the output voltage from secondary will be less than the induced e.m.f. E_2 by a component $jI_2 X_2$ to account for the secondary leakage flux.

A transformer with winding resistance and magnetic leakage is equivalent to an ideal transformer (having no resistance and leakage resistance) having resistive and inductive coils connected in series with each winding as shown in Fig. 23.

9.6. Transformer with Resistance and Leakage Reactance. Let us consider transformer (Fig. 23) having primary and secondary windings of resistances R_1 and R_2 and reactances X_1 and X_2 respectively.

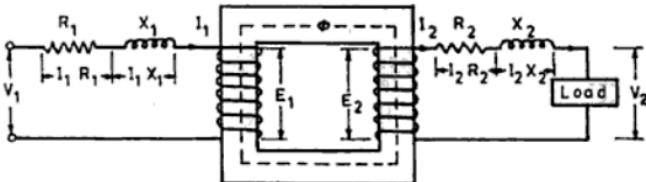


Fig. 23. An equivalent diagram of an actual transformer.

$$\text{Impedance of primary winding, } Z_1 = R_1 + jX_1$$

$$\text{Impedance of secondary winding, } Z_2 = R_2 + jX_2$$

The vector diagrams for different kinds of loads for such a transformer are shown in Fig. 24 (a, b, c). In these diagrams, vectors for resistive drops are drawn parallel to current vectors whereas reactive drops are drawn perpendicular to the current vectors. The angle ϕ_1 between V_1 and I_1 gives the power factor angle of the transformer.

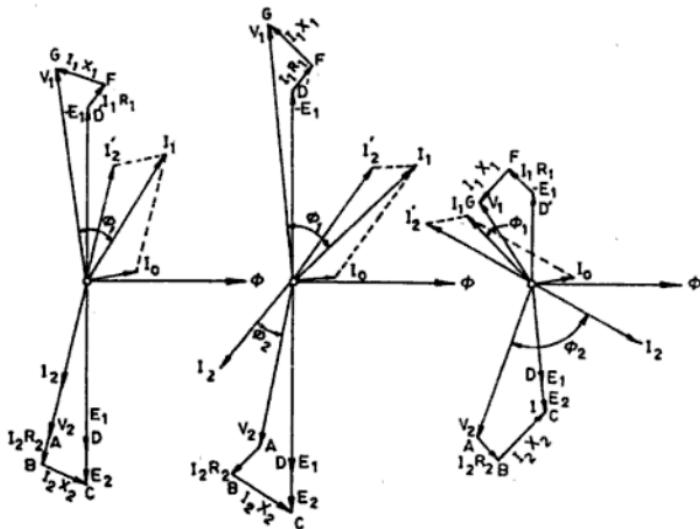


Fig. 24. (a) Unity p.f., (b) lagging p.f. and (c) leading p.f.

9.7. Equivalent Resistance and Reactance

Equivalent Resistance. In Fig. 25 is shown a transformer whose primary and secondary windings have resistances of R_1 and R_2 respectively (shown external to the windings). The resistances of the two windings can be transferred to any one of the two windings. If both the resistances are concentrated in one winding the calculations become simple since then we can work in one winding only.

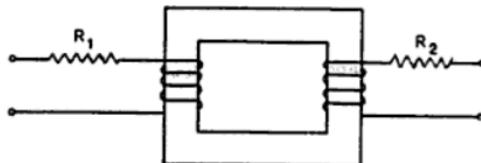


Fig. 25

We shall now prove that a resistance of R_2 in secondary is equivalent to $\frac{R_2}{K^2}$ in primary and its value will be denoted by R'_2 , — the equivalent secondary resistance referred to primary.

In the secondary, copper loss is $I_2^2 R_2$. This loss is supplied by primary which takes a current of I_1 . Hence, if R'_2 is the equivalent resistance referred to primary which would have caused the same loss as R_2 in secondary, then

$$I_1^2 R'_2 = I_2^2 R_2 \quad \text{or} \quad R'_2 = \left(\frac{I_2}{I_1} \right)^2 R_2$$

If no-load current I_0 is neglected,

then,

$$\frac{I_2}{I_1} = \frac{1}{K}$$

Hence,

$$R'_2 = \frac{R_2}{K^2}$$

Similarly, equivalent primary resistance as referred to secondary is

$$R'_1 = K^2 R_1$$

In Fig. 26, secondary resistance has been transferred to primary side (leaving secondary circuit resistanceless).

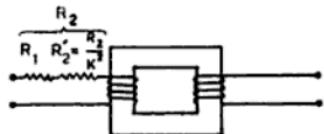


Fig. 26

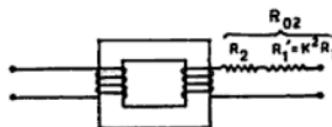


Fig. 27

The resistance $R_1 + R'_2 = R_1 + \frac{R_2}{K^2}$ is known as the *equivalent or effective resistance of the transformer as referred to the primary* and may be designated as R_{01} .

$$\text{Thus} \quad R_{01} = R_1 + R'_2 = R_1 + \frac{R_2}{K^2} \quad \dots(6)$$

Similarly, the equivalent resistance of the transformer as referred to the secondary (Fig. 27) is

$$R_{02} = R_2 + R'_1 = R_2 + K^2 R_1 \quad \dots(7)$$

The following points are worth remembering :

- (i) When shifting resistance to the secondary, multiply it by K^2 .
- (ii) When shifting resistance to the primary, divide by K^2 .

Leakage reactance. Leakage reactance can also be transferred from one winding to the other in the same way as resistance (Fig. 28 and Fig. 29).

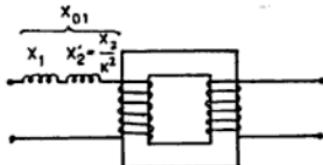


Fig. 28

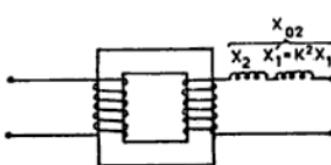


Fig. 29

$$X_2' = \frac{X_2}{K^2} \quad \text{and} \quad X_1' = K^2 X_1$$

and

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} \quad \dots(8)$$

$$X_{02} = X_2 + X_1' = X_2 + K^2 X_1 \quad \dots(9)$$

Total impedance. It is obvious that total impedance of the transformer as referred to primary is given by

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} \quad (\text{Fig. 30}) \quad \dots(10)$$

and

$$Z_{02} = \sqrt{R_0^2 + X_{02}^2} \quad (\text{Fig. 31}) \quad \dots(11)$$

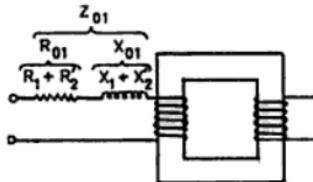


Fig. 30

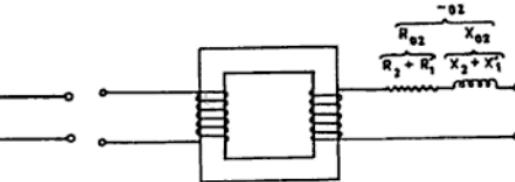


Fig. 31

9.8. Total Voltage Drop in a Transformer

(i) **Approximate voltage drop.** When there is no-load on the transformer, then,

$$V_1 = E_1 \text{ (approximately).}$$

and

$$E_2 = KE_1 = KV_1$$

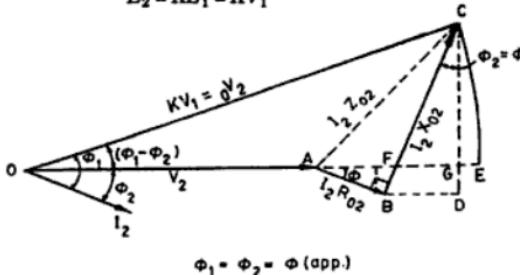


Fig. 32. Lagging power factor.

Also

$$E_2 = _0 V_2, \text{ where } _0 V_2 \text{ is secondary terminal voltage on no-load}$$

or

$$E_2 = _0 V_2 = KV_1$$

$$V_2 = \text{secondary voltage on load.}$$

Refer Fig. 32. The procedure of finding the approximate voltage drop of the transformer as referred to secondary is given below :

- Taking O as centre, radius OC draw an arc cutting OA produced at E . The total voltage drop $I_1 Z_{02} = AC = AE$ which is approximately equal to AG .
- From B draw BF perpendicular on OA produced. Draw CG perpendicular to OE and draw BD parallel to OE .

$$\begin{aligned}\text{Approximate voltage drop } &= AG = AF + FG = AF + BD \\ &= I_2 R_{02} \cos \phi + I_2 X_{02} \sin \phi\end{aligned}$$

$$[\because FG = BD]$$

This is the value of approximate voltage drop for a *lagging power factor*. Figs. 33 and 34 refer to *unity* and *leading power factor* respectively.

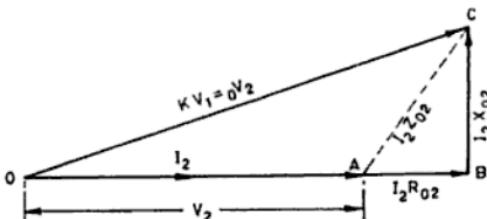


Fig. 33. Unity power factor.

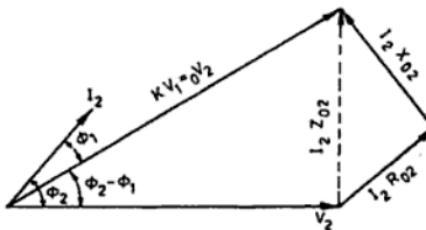


Fig. 34. Leading power factor.

- The approximate voltage drop for a *leading power factor* becomes : $(I_2 R_{02} \cos \phi - I_2 X_{02} \sin \phi)$
- The approximate voltage drop for a transformer *in general* is given by : $(I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi)$... (12)
- The voltage drop as *referred to primary* is given by : $(I_1 R_{01} \cos \phi \pm I_1 X_{01} \sin \phi)$
- Percentage voltage drop in secondary*

$$= \left(\frac{I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi}{V_2} \right) \times 100 \quad \dots (13)$$

(ii) **Exact voltage drop.** When we refer to Fig. 32 we find that exact drop is AE and not AG . If quantity GE is added to AG the exact value of voltage drop will be obtained.

From right angled triangle OCG , we get

$$\begin{aligned}CG^2 &= OC^2 - OG^2 = (OC + OG)(OC - OG) \\ &= (OC + OG)(OE - OG) = GE \times 2OC\end{aligned}$$

$$GE = \frac{CG^2}{2OC}$$

Now

$$CG = I_2 X_{02} \cos \phi - I_2 R_{02} \sin \phi$$

$$GE = \frac{(I_2 X_{02} \cos \phi - I_2 R_{02} \sin \phi)^2}{2V_2}$$

∴ The exact voltage drop for a lagging power factor is

$$= AG + GE$$

$$= (I_2 R_{02} \cos \phi + I_2 X_{02} \sin \phi) + \frac{(I_2 X_{02} \cos \phi - I_2 R_{02} \sin \phi)^2}{2_0 V_2} \quad \dots(14)$$

For a leading power, the expression becomes

$$= (I_2 R_{02} \cos \phi - I_2 X_{02} \sin \phi) + \frac{(I_2 X_{02} \cos \phi + I_2 R_{02} \sin \phi)^2}{2_0 V_2} \quad \dots(15)$$

In general, the exact voltage drop is

$$= (I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi) + \frac{(I_2 X_{02} \cos \phi \mp I_2 R_{02} \sin \phi)^2}{2_0 V_2}$$

Percentage drop is

$$= \frac{(I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi) \times 100}{V_2} + \frac{(I_2 X_{02} \cos \phi \mp I_2 R_{02} \sin \phi)^2 \times 100}{2_0 V_2^2} \quad \dots(16)$$

[Upper signs ... for lagging power factor
Lower signs ... for leading power factor]

9.9. Equivalent Circuit. In transformers, the problems concerning voltages and currents can be solved by the use of phasor diagrams. However, it is more convenient to represent the transformer by an equivalent circuit. If an equivalent circuit is available the computations can be done by the direct application of circuit theory. An equivalent circuit is merely a circuit interpretation of the equations which describe the behaviour of the device.

The transformer windings, in the equivalent circuit, are shown as ideal. The resistance and leakage reactance of the primary and secondary are shown separately in the primary and secondary circuits. The effect of magnetising current is represented by X_0 connected in parallel across the winding. The effect of core loss is represented by a non-inductive resistance R_0 as shown in Fig. 35.

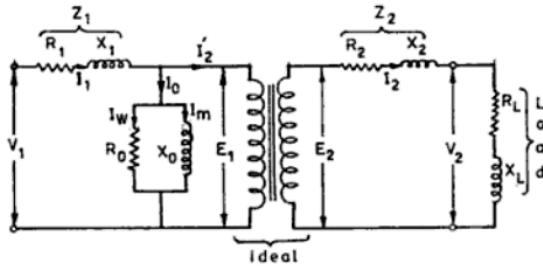


Fig. 35. Equivalent circuit of a transformer.

The equivalent circuit can be simplified by transferring the secondary resistances and reactances to the primary side in such a way that the ratio of E_2 to E_1 is not affected in magnitude or phase. Let R'_2 be the resistance which must be placed in the primary circuit to produce the same drop as produced by R_2 in the secondary. Then R'_2 causes a voltage drop in primary equal to $I_2 R'_2$.

The ratio of $I_2 R'_2$ and $I_2 R_2$ must be the same as the turn ratio $\frac{N_1}{N_2}$.

$$\text{Thus } \frac{I_2' R_2'}{I_2 R_2} = \frac{N_1}{N_2} = \frac{1}{K} \quad \text{or} \quad R_2' = R_2 \times \frac{I_2}{I_2'} \times \frac{1}{K}$$

$$\text{But } \frac{I_2}{I_2'} = \frac{N_1}{N_2} = \frac{1}{K}$$

$$\therefore R_2' = \frac{R_2}{K^2}$$

$$\text{Similarly } X_2' = \frac{X_2}{K^2}.$$

The load resistance and reactance can be transferred to the primary side in the same way. When all the secondary impedances have been transferred to the primary side, the winding need not be shown in the equivalent circuit. The exact equivalent circuit of the transformer with all impedances transferred to the primary side is shown in Fig. 36.

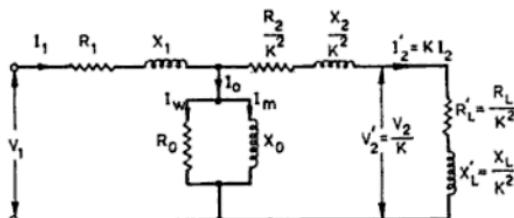


Fig. 36. Equivalent circuit with secondary impedances transferred to primary.

Just as the secondary impedances have been transferred to the primary it is possible to transfer the primary winding resistance and reactance to the secondary side. The primary resistance R_1 and leakage reactance X_1 when transferred to secondary are denoted by R_1' and X_1' and are given by

$$R_1' = K^2 R_1$$

$$X_1' = K^2 X_1.$$

Approximate equivalent circuit. It is seen that E_1 differs from V_1 by a very small amount. Moreover, the no-load current I_0 is only a small fraction of full-load primary current so that I_2' is practically equal to I_1 . Consequently the equivalent circuit can be simplified by transferring the parallel branch consisting of R_0 and X_0 to the extreme left position of the circuit as shown in Fig. 37. This circuit is known as *approximate equivalent circuit*. Analysis with the approximate equivalent circuit gives almost the same results as the analysis with the exact equivalent circuit. However, the analysis

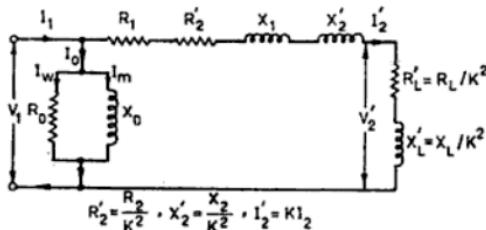


Fig. 37. Approximate equivalent circuit of transformer.

with the approximate equivalent circuit is simple because the resistances R_1 and R_2' and leakage reactances X_1 and X_2' can be combined.

9.10. Transformer Tests. The performance of a transformer can be calculated on the basis of its equivalent circuit which contains the following four main parameters :

- Equivalent resistance R_{01} as referred to primary (or secondary R_{02}).
- Equivalent leakage resistance X_{01} as referred to primary (or secondary X_{02}).
- Core loss conductance G_0 (or resistance R_0).
- Magnetising susceptance B_0 (or reactance X_0).

These parameters or constants can be determined by the following two tests :

- Open-circuit or no-load test.
- Short-circuit or impedance test.

The above two tests are convenient to perform and very economical because they furnish the required information without actually loading the transformer.

9.10.1. Open-circuit or no-load test (O.C. Test). An open-circuit or no-load test is conducted to find :

- No-load loss or core loss.
- No-load current I_0 which is helpful in finding R_0 and X_0 .

The connections for this test are made as shown in Fig. 38. One winding of the transformer (usually high voltage winding) is left open and the other is connected to its supply of normal voltage and frequency. Ammeter A and wattmeter W are connected to measure no-load current (I_0) and no-load input power (P_0) respectively.

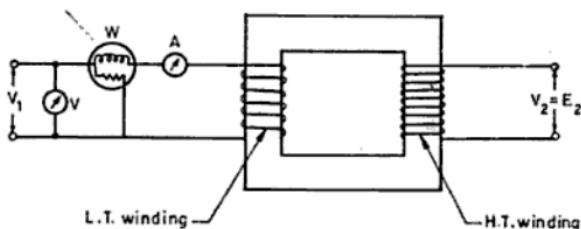


Fig. 38. Circuit diagram for open-circuit test.

As the primary no-load current I_0 (as measured by ammeter) is small (usually 3 to 10% of rated load current) copper loss is negligibly small in primary (L.T. winding) and nil in secondary winding (it being open). Hence the wattmeter reading represents practically the core-loss under no-load conditions (and this loss is same for all loads).

From the data available from this test R_0 , X_0 , $\cos \phi_0$ (no-load power factor), I_w and I_m can be calculated as follows :

$$\begin{aligned} \text{Now, Iron loss} &= P_i = \text{input power on no-load} \\ &= P_0 \text{ watts (say)} \end{aligned}$$

$$\text{No-load current} = I_0$$

$$\text{Applied primary voltage} = V_1$$

$$\text{Also } P_0 = V_1 I_0 \cos \phi_0 \quad (\text{where } \cos \phi_0 = \text{no-load power factor})$$

$$\therefore \cos \phi_0 = \frac{P_0}{V_1 I_0} \quad \dots(17)$$

or $\phi_0 = \cos^{-1} \frac{P_0}{V_1 I_0}$

No-load current *wattful component*,

$$I_w = I_0 \cos \phi_0 = \frac{P_0}{V_1} \quad \dots(18)$$

No-load current *magnetising component*,

$$I_m = \sqrt{I_0^2 - I_w^2} \quad \dots(19)$$

$$\text{The no-load resistance, } R_0 = \frac{V_1}{I_w} = \frac{V_1^2}{P_0} \quad \dots(20)$$

$$\text{The no-load reactance, } X_0 = \frac{V_1}{I_m} = \frac{V_1}{\sqrt{I_0^2 - I_w^2}} \quad \dots(21)$$

The no-load vector diagram is shown in Fig. 19.

Since the current is practically all-exciting current when a transformer is on no-load (*i.e.* $I_0 = I_m$) and the voltage drop in primary leakage impedance is small, hence the exciting admittance Y_0 of the transformer is given by

$$I_0 = V_1 Y_0 \quad \text{or} \quad Y_0 = \frac{V_1}{I_0} \quad \dots(22)$$

$$\text{The exciting conductance } G_0 = \frac{P_0}{V_1^2} \quad \dots(23)$$

$$\text{The exciting susceptance } B_0 = \sqrt{Y_0^2 - G_0^2} \quad \dots(24)$$

Separation of core losses. The core loss is made up of the following two parts :

(i) Eddy current loss.

(ii) Hysteresis loss.

Eddy current loss, $P_e = AB^2 \max f^2$, where A is constant.

Hysteresis loss, $P_h = BB^{1.6} \max f$, where B is constant.

Total loss $= P_e + P_h = AB^2 \max f^2 + BB^{1.6} \max f$.

The values of constants A and B can be found out by conducting two experiments using two different frequencies but the same maximum flux density ; thereafter eddy current and hysteresis loss can be found separately.

9.10.2. Short-circuit or impedance test (S.C. Test). This test is conducted to determine the following :

(i) Full-load copper loss.

(ii) Equivalent resistance and reactance referred to metering side.

In this test (Fig. 39) the terminals of the secondary winding (*usually low voltage winding*) are short-circuited by a thick conductor or through an ammeter which may serve the additional purpose of indicating rated load current. A low voltage, usually 5 to 10% of normal primary voltage, at correct frequency is applied to the primary and is continuously increased till full-load currents flow in the primary as well as secondary windings (as indicated by the respective ammeters).

Since applied voltage is very low so flux linking with the core is very small and therefore, iron losses are so small that these can be neglected, the reading of the wattmeter gives total copper losses at full-load.

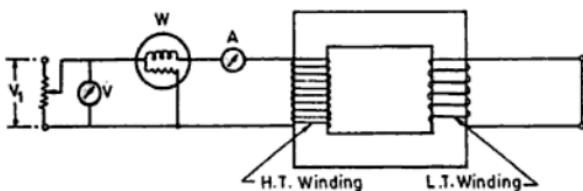


Fig. 39. Short-circuit test.

The equivalent circuit of the transformer under short-circuit condition is shown in Fig. 40.

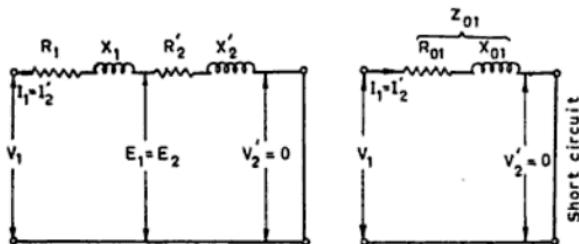


Fig. 40. Equivalent circuit of transformer under short-circuit condition.

Let

$$V_{SC} = \text{voltage required to circulate rated load currents}$$

I_1 = reading of the ammeter on the primary side

Z_{01} = total impedance as referred to primary side

R_{01} = total resistance as referred to primary side

X_{01} = total reactance as referred to primary side.

Then, equivalent impedance as referred to primary side,

$$Z_{01} = \frac{V_{SC}}{I_1} \quad \dots(25)$$

Also

$$P = I_1^2 R_{01}$$

∴

$$R_{01} = \frac{P}{I_1^2} \quad \dots(26)$$

and

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} \quad \dots(27)$$

9.11. Regulation of a Transformer

- Due to the resistances of the windings and leakage reactances voltage drop takes place in a transformer. Accordingly the output voltage under load conditions is different from the output voltage under no-load conditions. **Voltage regulation** is defined as :

"The change in secondary voltage when rated load at a specified power is removed".

It is specified as a percentage of the rated secondary voltage.

Thus, if $0V_2$ = secondary terminal voltage at no-load

$$= E_2 = KE_1 = KV_1 \text{ because at no-load the impedance drop is negligible}$$

V_2 = secondary terminal voltage on full-load

$$\text{Then, \% regulation (down)} = \frac{0V_2 - V_2}{0V_2} \times 100 \quad \dots(28)$$

$$\% \text{ regulation (up)} = \frac{\left| V_2 - V_2' \right|}{V_2} \times 100 \quad \dots(29)$$

For calculating the regulation it is convenient to refer the total resistance and reactance to the secondary side.

- Refer Fig. 32.

$$\% \text{ regulation} = \left(\frac{I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi}{V_2} \right) \times 100 \quad (\text{app.}) \quad \dots(30)$$

[+ sign for lagging power factor
- sign for leading power factor]

The less this value, the better the transformer, because a good transformer should keep its secondary terminal voltage as constant as possible under all conditions of load.

The regulation may also be expressed in terms of primary values as follows :

$$\begin{aligned} \% \text{ regulation} &= \frac{V_1 - V_2'}{V_1} \times 100 && (\text{neglecting angle between } V_1 \text{ and } V_2') \\ &= \left(\frac{I_1 R_{01} \cos \phi \pm I_1 X_{01} \sin \phi}{V_1} \right) \times 100 \end{aligned} \quad \dots(31)$$

- In the above definitions of regulation, primary voltage was supposed to be kept constant and changes in secondary terminal were considered. But as the transformer is loaded, the secondary terminal voltage falls (for lagging power factor); hence to keep the circuit voltage constant, the primary voltage must be increased. The rise in primary voltage required to maintain rated output voltage from no-load to full-load at a given power factor expressed as percentage of rated primary voltage gives the regulation of the transformer.

If the primary voltage has to be raised from its rated value V_1 to V_1' , then

$$\% \text{ regulation} = \frac{V_1' - V}{V_1} \times 100 \quad \dots[31(a)]$$

9.12. Percentage Resistance and Reactance

- Invariably the equivalent resistance and reactance of a transformer are expressed in percent.

Percentage resistance is the resistance drop in volts at rated current and frequency as a percentage of the rated voltage i.e.,

$$\text{Percent } R = \frac{IR}{V} \times 100 \quad \dots(i)$$

Percentage reactance is the reactance drop in volts at rated current and frequency expressed as a percentage of the rated voltage i.e.,

$$\text{Percent } X = \frac{IX}{V} \times 100 \quad \dots(ii)$$

and

$$\text{Percent } Z = \frac{IZ}{V} \times 100 \quad \dots(iii)$$

The important advantage of expressing resistance and reactance of a transformer in percentage is that the percentage resistance and percentage reactance have same values whether determined referred to primary or secondary whereas when expressed in ohms they have different values when referred to primary and secondary.

Further, percent reactances and impedances are convenient for computing the current that will flow in a transformer when the secondary is accidentally shorted. When the secondary is shorted,

$I_1 = \frac{E_1}{Z_0}$ or $E_1 = I_1 Z_0$ i.e., when secondary is shorted, $I_1 Z_0$ is 100 percent of E_1 . Therefore, the short-circuit current is given by the equation,

$$\text{Short circuit current } I_{SC} = \frac{100}{\text{Percent impedance}} \times \text{full load rated current} \quad \dots(iv)$$

Unless the transformer is quite small, equivalent resistance is negligible and percent reactance may be substituted for percent impedance in the above equation (iv).

- Another method of designating the resistances and reactances is by the per unit values. The per unit values are equal to the percentage values divided by 100.

$$\therefore \text{Per unit } R = \frac{IR}{V} \quad \dots(v)$$

$$\text{and} \quad \text{Per unit } X = \frac{IX}{V} \quad \dots(vi)$$

9.13. Transformer Losses. The losses in a transformer are classified as follows :

1. Iron losses (or core losses).

2. Copper losses.

1. **Iron or core losses.** It includes *hysteresis loss* and *eddy current loss*.

(i) **Hysteresis loss.** Since the flux in a transformer core is alternating, power is required for the continuous reversals of the elementary magnets of which the iron is composed. This loss is known as *hysteresis loss*.

$$\text{Hysteresis loss} = K_h B_{\max}^{1.6} \quad \dots(32)$$

where f is the frequency in Hz, B_{\max} is the maximum flux density in core and K_h is a constant.

(ii) **Eddy current loss.** This is due to the flow of eddy currents in the core. Thin laminations, insulated from each other, reduce the eddy current loss to small proportion.

$$\text{Eddy current loss} = K_e f^2 B_{\max}^2 \quad \dots(33)$$

where K_e is a constant.

Iron or core loss is found from open circuit test. The input of the transformer when on no-load measures the core loss.

2. **Copper losses.** These losses are due to the ohmic resistance of the transformer windings.

$$\text{Total copper loss} = I_1^2 R_1 + I_2^2 R_2 = I_1^2 R_{01} = I_2^2 R_{02}$$

These losses, as is evident, are proportional to square of the current (or kVA)².

The value of copper losses is found from the *short-circuit test*.

9.14. Transformer Efficiency. The efficiency of a transformer at a particular load and power factor is defined as the ratio of power output to power input.

$$\therefore \text{Efficiency} = \frac{\text{output}}{\text{input}} = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{\text{output}}{\text{output} + \text{cu loss} + \text{iron loss}} \quad \dots(34)$$

$$\text{or} \quad \text{Efficiency} = \frac{\text{input} - \text{losses}}{\text{input}} = 1 - \frac{\text{losses}}{\text{input}} \quad \dots(35)$$

It may be noted that efficiency is based on power output in watts and not in volt-amperes, although losses are proportional to volt-amperes. Hence at any volt-ampere load, the efficiency depends on power factor, being *maximum at unity power factor*.

Efficiency can be calculated by determining core losses from open-circuit test and copper losses from short-circuit test.

Condition for maximum efficiency :

$$\text{Iron losses, } P_i = \text{hysteresis loss + eddy current loss} \\ = P_h + P_e$$

$$\text{Copper losses, } P_c = I_1^2 R_{01} \text{ or } I_2^2 R_{02}$$

Considering primary side :

$$\text{Input to primary } = V_1 I_1 \cos \phi_1$$

$$\text{Efficiency, } \eta = \frac{V_1 I_1 \cos \phi_1 - \text{losses}}{V_1 I_1 \cos \phi_1} = \frac{V_1 I_1 \cos \phi_1 - I_1^2 R_{01} - P_i}{V_1 I_1 \cos \phi_1} \\ = 1 - \frac{I_1 R_{01}}{V_1 \cos \phi_1} - \frac{P_i}{V_1 I_1 \cos \phi_1}$$

Differentiating both sides w.r.t. I_1 , we get

$$\frac{d\eta}{dI_1} = 0 - \frac{R_{01}}{V_1 \cos \phi_1} + \frac{P_i}{V_1 I_1^2 \cos \phi_1}$$

For η to be maximum,

$$\frac{d\eta}{dI_1} = 0. \text{ Hence the above equation reduces to}$$

$$\frac{R_{01}}{V_1 \cos \phi_1} = \frac{P_i}{V_1 I_1^2 \cos \phi_1}$$

$$P_i = I_1^2 R_{01} \text{ or } I_2^2 R_{02}$$

$$\text{or} \quad \text{Copper losses} = \text{Iron losses} \quad \dots(36)$$

The output current corresponding to maximum efficiency is

$$I_2 = \sqrt{\frac{P_i}{R_{02}}} \quad \dots(37)$$

By proper design it is possible to make the maximum efficiency occur at any desired load.

Variation of efficiency with power factor. We know that transformers efficiency,

$$\eta = \frac{\text{output}}{\text{input}} = \frac{\text{input} - \text{losses}}{\text{input}} \\ = 1 - \frac{\text{losses}}{\text{input}} = 1 - \frac{\text{losses}}{(V_2 I_2 \cos \phi + \text{losses})}$$

Let,

$$\frac{\text{losses}}{V_2 I_2} = \beta$$

$$\therefore \eta = 1 - \left(\frac{\text{losses}/V_2 I_2}{\cos \phi + \text{losses}/V_2 I_2} \right) \quad \text{or} \quad = 1 - \frac{\beta}{(\cos \phi + \beta)}$$

$$\text{or} \quad \eta = 1 - \frac{(\beta/\cos \phi)}{1 + (\beta/\cos \phi)} \quad \dots(38)$$

The variations of efficiency with power factor at different loadings on a typical transformer are shown in Fig. 41.

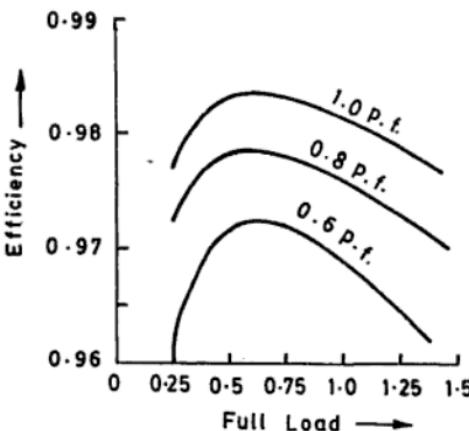


Fig. 41. Variations of efficiency with power factor at different loadings.

Transformer on Load

Example 10. A 230 V/115 V single-phase transformer takes a no-load current of 2 A at a power factor of 0.2 lagging with low voltage winding kept open. If the low voltage winding is now loaded to take a current of 15 A at 0.8 power factor lagging find the current taken by high voltage winding.

Solution. Primary, $E_1 = V_1 = 230$ V

Secondary, $E_2 = V_2 = 115$ V

No-load current $I_0 = 2$ A

No-load power factor, $\cos \phi_0 = 0.2$ or $\phi_0 = 78.46^\circ$ or $78^\circ 29'$

Load power factor, $\cos \phi_2 = 0.8$ or $\phi_2 = 36.9^\circ$ or $36^\circ 54'$

Current taken by h.v. winding, I_1 :

Now, transformation ratio,

$$K = \frac{V_2}{V_1} = \frac{E_2}{E_1} = \frac{115}{230} = \frac{1}{2}$$

\therefore Secondary current referred to primary,

$$I_2' = K I_2 = \frac{1}{2} \times 15 = 7.5 \text{ A}$$

Phase angle, between I_0 and I_2'

$$= 78.46^\circ - 36.9^\circ = 41.56^\circ \text{ or } 41^\circ 34'$$

Using parallelogram law of forces (Fig. 42), we get

$$\begin{aligned} I_1 &= \sqrt{2^2 + 7.5^2 + 2 \times 2 \times 7.5 \times \cos 41.56^\circ} \\ &= 9.09 \text{ A} \end{aligned}$$

Hence, current taken by h.v. winding,

$$I_1 = 9.09 \text{ A. (Ans.)}$$

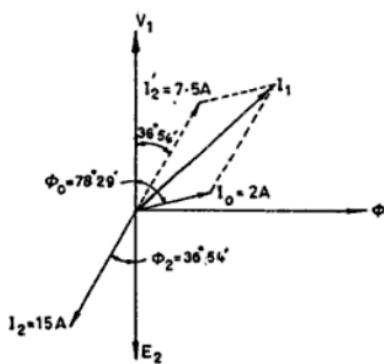


Fig. 42

Example 11. The number of turns on the primary and secondary windings of a transformer are 1000 and 200 respectively. When the load current on the secondary is 100 A at 0.8 power factor lagging, the primary current is 30 A at 0.707 power factor lagging. Determine the no-load current of the transformer and its phase with respect to the voltage.

Solution. Primary turns, $N_1 = 1000$

Secondary turns, $N_2 = 200$

Secondary current, $I_2 = 100 \text{ A}$

Power factor, $\cos \phi_2 = 0.8 \text{ or } \phi_2 = 36.9^\circ \text{ or } 36^\circ 54'$

Primary current, $I_1 = 30 \text{ A}$

Power factor, $\cos \phi_1 = 0.707 \text{ or } \phi_1 = 45^\circ$

No-load current, $I_0, \phi_0 :$

$$\text{Transformation ratio, } K = \frac{200}{1000} = \frac{1}{5}$$

Secondary current referred to primary,

$$I_2' = K I_2 = \frac{1}{5} \times 100 = 20 \text{ A}$$

Refer Fig. 43. I_1 is the vector sum of I_0 and I_2' . Let I_0 lag behind V_1 by an angle ϕ_0 .

Resolving currents into their X-and Y-components, we get

$$I_0 \cos \phi_0 + 20 \cos 36.9^\circ = 30 \cos 45^\circ$$

$$\therefore I_0 \cos \phi_0 = 30 \cos 45^\circ - 20 \cos 36.9^\circ \\ = 21.21 - 16 = 5.21 \text{ A} \quad \dots(i)$$

$$I_0 \sin \phi_0 + 20 \sin 36.9^\circ = 30 \sin 45^\circ$$

$$\therefore I_0 \sin \phi_0 = 30 \sin 45^\circ - 20 \sin 36.9^\circ \\ = 21.21 - 12 = 9.21 \text{ A} \quad \dots(ii)$$

From (i) and (ii), we get

$$\tan \phi_0 = \frac{9.21}{5.21} = 1.767$$

$$\therefore \phi_0 = 60.5^\circ$$

Putting the value of ϕ_0 in (i), we get

$$I_0 \cos 60.5^\circ = 5.21$$

$$\therefore I_0 = \frac{5.21}{\cos 60.5^\circ} = 10.58 \text{ A}$$

Hence, **no-load current = 10.58 A**

and

$$\phi_0 = 60.5^\circ. \text{ (Ans.)}$$

Example 12. A 30 kVA, 2000/200 V, single-phase, 50 Hz transformer has a primary resistance of 3.5Ω and reactance of 4.5Ω . The secondary resistance and reactance are 0.015Ω and 0.02Ω respectively. Find :

(i) Equivalent resistance, reactance and impedance referred to primary.

(ii) Equivalent resistance, reactance and impedance referred to secondary.

(iii) Total copper loss of the transformer.

Solution. Primary resistance, $R_1 = 3.5 \Omega$

Primary reactance, $X_1 = 4.5 \Omega$

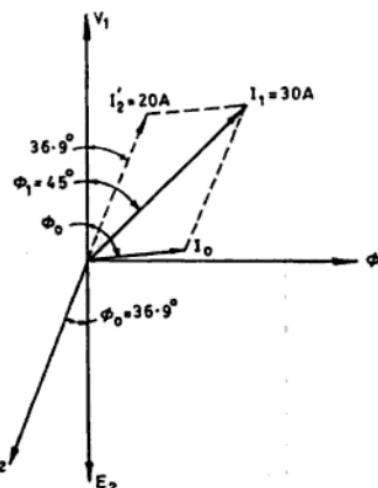


Fig. 43

$$\text{Secondary resistance, } R_2 = 0.015 \Omega$$

$$\text{Transformation ratio, } K = \frac{200}{2000} = \frac{1}{10}$$

(i) Equivalent resistance referred to primary,

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} = 3.5 + \frac{0.015}{\left(\frac{1}{10}\right)^2} = 5.0 \Omega \quad (\text{Ans.})$$

Equivalent reactance referred to primary,

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} = 4.5 + \frac{0.02}{\left(\frac{1}{10}\right)^2} = 6.5 \Omega. \quad (\text{Ans.})$$

Equivalent impedance referred to primary,

$$Z_{01} = \sqrt{(R_{01})^2 + (X_{01})^2} = \sqrt{(5)^2 + (6.5)^2} = 8.2 \Omega. \quad (\text{Ans.})$$

(ii) Equivalent resistance referred to secondary,

$$R_{02} = R_2 + R_1' = R_2 + K^2 R_1 \\ = 0.015 + \left(\frac{1}{10} \right)^2 \times 3.5 = 0.05 \Omega. \quad (\text{Ans.})$$

Equivalent reactance referred to secondary.

$$X_{02} = X_2 + X_1' = X_2 + K^2 X_1 = 0.02 + \left(\frac{1}{10}\right)^2 \times 4.5 = 0.065 \Omega. \quad (\text{Ans.})$$

Equivalent impedance referred to secondary,

$$Z_{02} = \sqrt{(R_{02})^2 + (X_{02})^2} = \sqrt{(0.05)^2 + (0.065)^2} = 0.082 \Omega. \quad (\text{Ans.})$$

(iii) Total copper loss :

$$\text{Secondary current} = \frac{30 \times 1000}{200} = 150 \text{ A}$$

$$\text{Total copper loss} = I_2^2 R_{02} = 150^2 \times 0.05 = 1125 \text{ W. (Ans.)}$$

Example 13. A single-phase transformer has the following data :

Turn ratio $20 : 1$; $R_1 = 20 \Omega$, $X_1 = 80 \Omega$; $R_2 = 0.04 \Omega$; $X_2 = 0.2 \Omega$. No-load current = $1.2 A$ leading the flux by 30° .

The secondary delivers 180 A at a terminal voltage of 400 V and at a power factor of 0.8 lagging. Determine by the aid of a vector diagram :

- (i) The primary applied voltage. (ii) The primary power factor.
 (iii) The efficiency.

Solution. Refer Fig. 44 :

(i) Primary applied voltage, V_1 :

Taking V_2 as the reference vector

$$V_2 = 400 \angle 0^\circ = 400 + j0$$

$$I_2 = 180(0.8 - j0.6) = 144 - j108$$

$$Z_0 = (0.04 \pm i0.2)$$

$$E_2 = V_2 + I_2 Z_2 = (400 + j0) + (144 - j108) \times (0.04 + j0.2)$$

$$E_2 = V_2 + jZ_2 = (400 + j0) + (144 - j188) \times (0.54 + j0.2) \\ = 400 + (5.76 + j28.8 - j4.32 + j1.6) = (427.36 + j24.48) = 428.1 \angle 3.28^\circ$$

Obviously,

$$\beta = 3.28^\circ$$

$$E_1 = \frac{E_2}{K} = 20E_2 = 20(427.36 + j24.48) = 8547 + j490$$

$$\therefore -E_1 = -8547 - j490 = 8561 \angle 183.28^\circ$$

Secondary current referred to primary,

$$I_2' = -KI_2 = \frac{(-144 + j108)}{20} = -7.2 + j5.4$$

As seen from Fig. 44, I_0 leads V_2 by an angle

$$3.28^\circ + 90^\circ + 30^\circ = 123.28^\circ$$

$$\therefore I_0 = 1.2 \angle 123.28^\circ = 1.2(\cos 123.28^\circ + j \sin 123.28^\circ)$$

$$= 1.2(-0.548 + j0.836) = -0.657 + j1.003.$$

Primary current,

$$I_1 = -I_2' + I_0 = (-7.2 + j5.4) + (-0.657 + j1.003)$$

$$= -7.857 + j6.403 = 10.14 \angle 140.8^\circ$$

$$V_1 = -E_1 + I_1 Z_1 = (-8547 - j490)$$

$$+ (-7.857 + j6.403)(20 + j80)$$

$$= -8547 - j490 + (-157.14 - j628.56 + j128.06)$$

$$- 512.24)$$

$$= -9216.38 - j990.5 = 9269 \angle 186.13^\circ. \text{ (Ans.)}$$

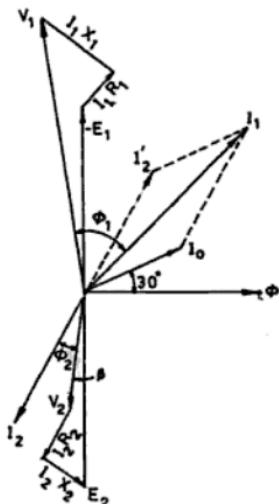


Fig. 44

(ii) Primary power factor, $\cos \phi_1$:

Phase angle between V_1 and I_1 ,

$$\phi_1 = 186.13^\circ - 140.8^\circ = 45.33^\circ$$

$$\therefore \text{Primary power factor} = \cos 45.33^\circ = 0.703 \text{ (lag). (Ans.)}$$

(iii) Efficiency :

No-load primary input power

$$= V_1 I_1 \cos \phi_0 = 9269 \times 1.2 \times \cos 60^\circ = 5561.4 \text{ W}$$

$$R_{02} = R_2 + K^2 R_1 = 0.04 + \left(\frac{1}{20} \right)^2 \times 20 = 0.09 \Omega$$

Total copper losses as referred to secondary

$$= I_2'^2 R_{02} = (180)^2 \times 0.09 = 2916 \text{ W}$$

$$\text{Output} = V_2 I_2 \cos \phi_2 = 400 \times 180 \times 0.8 = 57600 \text{ W}$$

$$\text{Total losses} = 5561.4 + 2916 = 8477.4 \text{ W}$$

$$\text{Input} = \text{Output} + \text{Losses} = 57600 + 8477.4 = 66077.4 \text{ W}$$

$$\therefore \text{Efficiency, } \eta = \frac{\text{output}}{\text{input}} = \frac{57600}{66077.4} = 0.872 \text{ or } 87.2\%. \text{ (Ans.)}$$

Example 14. The high voltage and low voltage windings of a 2200/220 V single-phase 50 Hz transformer has resistances of 4.8Ω and 0.04Ω and reactances 2Ω and 0.018Ω respectively. The low voltage winding is connected to a load having an impedance of $(6 + j4) \Omega$. Determine :

- (i) Current in l.v. winding,
- (ii) Current in h.v. winding,
- (iii) Load voltage, and
- (iv) Power consumed by the load.

Solution. Primary resistance, $R_1 = 4.8 \Omega$
 Primary reactance, $X_1 = 2 \Omega$
 Secondary resistance, $R_2 = 0.04 \Omega$
 Secondary reactance, $X_2 = 0.018 \Omega$
 Impedance of load, $Z_L = (6 + j4)$

$$\text{Transformation ratio, } K = \frac{E_2}{E_1} = \frac{220}{2200} = \frac{1}{10}$$

Equivalent resistance referred to l.v. side,

$$R_{02} = R_2 + K^2 R_1 = 0.04 + \left(\frac{1}{10} \right)^2 \times 4.8 = 0.088 \Omega$$

Equivalent reactance referred to l.v. side,

$$X_{02} = X_2 + K^2 X_1 = 0.018 + \left(\frac{1}{10} \right)^2 \times 2 = 0.038 \Omega$$

Equivalent impedance referred to l.v. side,

$$Z_{02} = R_{02} + jX_{02} = (0.088 + j0.038) \Omega$$

(i) Current in l.v. winding,

$$\begin{aligned} I_2 &= \frac{220}{Z_{02} + Z_L} = \frac{220}{(0.088 + j0.038) + (6 + j4)} \\ &= \frac{220}{6.088 + j4.038} = \frac{220}{\sqrt{(6.088)^2 + (4.038)^2}} = 30.11 \text{ A. (Ans.)} \end{aligned}$$

(ii) Current in h.v. winding,

$$I_1 = I_2' = K I_2 = \frac{1}{10} \times 30.11 = 3.011 \text{ A. (Ans.)}$$

$$(iii) \text{ Load voltage, } V_2 = I_2 Z_L = 30.11(6 + j4) = 30.11 \times \sqrt{(6)^2 + (4)^2} = 217.12 \text{ V. (Ans.)}$$

(iv) Power consumed by the load,

$$= I^2 R_L = 30.11^2 \times 6 = 5439.6 \text{ W. (Ans.)}$$

Example 15. A single-phase transformer has $Z_1 = 1.4 + j5.2 \Omega$ and $Z_2 = 0.0117 + j0.0465 \Omega$. The input voltage is 6600 V and the turn ratio is 10.6 : 1. The secondary feeds a load which draws 300 A at 0.8 power factor lagging. Find the secondary terminal voltage and the kW output. Neglect no-load current I_0 .

Solution. Impedance $Z_1 = 1.4 + j5.2 \Omega$
 Impedance $Z_2 = 0.0117 + j0.0465 \Omega$
 Input voltage $V_1 = 6600 \text{ V}$
 Turn ratio, $K = 10.6 : 1$
 Secondary load current, $I_2 = 300 \text{ A}$
 Power factor, $\cos \phi_2 = 0.8$

Secondary terminal voltage, V_2 :

kW output :

Let the secondary terminal voltage = $V_2 \angle 0^\circ$

$$I_2 = 300 \angle -36.87^\circ \text{ A}$$

$$\begin{aligned} E_2 &= V_2 \angle 0^\circ + I_2 Z_2 \\ &= V_2 \angle 0^\circ + (300 \angle -36.87^\circ)(0.0117 + j0.0465) = V_2 \angle 0^\circ + 14.4 \angle 39^\circ \end{aligned}$$

$$E_1 = 10.6E_2 = 10.6V_2 \angle 0^\circ + 152.64 \angle 39^\circ$$

$$I_1 = \frac{300}{10.6} \angle -36.87^\circ = 28.3 \angle -36.87^\circ$$

$$\begin{aligned} V_1 &= E_1 + I_1 Z_1 \\ &= 10.6V_2 \angle 0^\circ + 152.64 \angle 39^\circ + (28.3 \angle -36.87^\circ)(1.4 + j5.2) \\ &= 10.6V_2 + 152.64 \angle 39^\circ + 152.4 \angle 38^\circ \\ &= 10.6V_2 + 118.62 + j96.06 + 120 + j93.83 \\ &= 10.6V_2 + 238.62 + j189.89 \end{aligned}$$

Since $|V_1| = 6600 \text{ V}$

$$\therefore (10.6V_2 + 238.62)^2 + (189.89)^2 = 6600^2$$

$$V_2 = 600 \text{ V}$$

or

Hence, secondary terminal voltage = 600 V. (Ans.)

Output :

$$\text{Output} = V_2 I_2 \cos \phi_2 = 600 \times 300 \times 0.8 = 144000 \text{ W or } 144 \text{ kW. (Ans.)}$$

Example 16. The full-load copper loss on h.v. side of 100 kVA, 11000/317 V 1-phase transformer is 0.62 kW and on the l.v. side is 0.48 kW.

(i) Calculate R_1 , R_2 and R_2' in ohms :

(ii) The total reactance is 4 percent, find X_1 , X_2 and X_2' in ohms if the reactance is divided in the same proportion as resistance.

Solution. Given : Rated kVA = 100 ; $V_1 = 11000 \text{ V}$; $V_2 = 317 \text{ V}$; loss on h.v. side = 0.62 kW ; loss of l.v. side = 0.48 kW ; total reactance = 4%.

(i) R_1 , R_2 and R_2' :

$$\text{h.v. side full-load current, } I_1 = \frac{\text{rated kVA} \times 1000}{V_1} = \frac{100 \times 1000}{11000} = 9.09 \text{ A}$$

$$\text{l.v. side full-load current, } I_2 = \frac{\text{rated kVA} \times 1000}{V_2} = \frac{100 \times 1000}{317} = 315.46 \text{ A}$$

$$\begin{aligned} \text{Primary winding resistance, } R_1 &= \frac{\text{full-load copper loss in primary winding}}{I_1^2} \\ &= \frac{0.62 \times 1000}{(9.09)^2} = 7.5 \Omega. \text{ (Ans.)} \end{aligned}$$

$$\begin{aligned} \text{Secondary winding resistance, } R_2 &= \frac{\text{full-load copper loss in secondary winding}}{I_2^2} \\ &= \frac{0.48 \times 1000}{(315.46)^2} = 0.00482 \Omega. \text{ (Ans.)} \end{aligned}$$

$$\text{Transformation ratio, } K = \frac{V_2}{V_1} = \frac{317}{11000} = 0.02882$$

Secondary resistance referred to primary,

$$R_2' = \frac{R_2}{K^2} = \frac{0.00482}{(0.02882)^2} = 5.8 \Omega. \text{ (Ans.)}$$

(ii) X_1 , X_2 and X_2' :

$$\text{Percentage reactance referred to h.v. side} = \frac{I_1 X_{01}}{V_1} \times 100 = 4$$

or transformer total reactance referred to primary,

$$X_{01} = \frac{4 \times V_1}{100 I_1} = \frac{4 \times 11000}{100 \times 9.09} = 48.4 \Omega.$$

Now,

$$\frac{R_1}{R_2'} = \frac{X_1}{X_2'} \quad \dots(\text{Given})$$

or

$$\frac{R_1 + R_2'}{R_2'} = \frac{X_1 + X_2'}{X_2'}$$

or

$$\frac{7.5 + 5.8}{5.8} = \frac{48.4}{X_2'}$$

or $X_2' = \frac{48.4 \times 5.8}{(7.5 + 5.8)} = 21.1 \Omega. \quad (\text{Ans.})$

Primary winding reactance, $X_1 = X_{01} - X_2' = 48.4 - 21.1 = 27.3 \Omega. \quad (\text{Ans.})$

Secondary winding reactance, $X_2 = K^2 X_2' = \left(\frac{377}{11000} \right)^2 \times 21.1 = 0.0175 \Omega. \quad (\text{Ans.})$

Hysteresis and Eddy Current Losses

Example 17. A 230 V, 2.5 kVA single-phase transformer has an iron loss of 100 W at 40-Hz and 70 W at 30-Hz. Find the hysteresis and eddy current losses at 50-Hz.

Solution. Iron loss at 40-Hz = 110 W

Iron loss at 30-Hz = 75 W

Hysteresis and eddy current loss at 50-Hz :

We know that hysteresis loss,

$$P_h \propto f = Af$$

Eddy current loss, $P_e \propto f^2 = Bf^2$

Iron loss, $P_i = P_h + P_e = Af + Bf^2$

At 40-Hz :

$$100 = 40A + (40)^2 B$$

i.e., $40A + 1600B = 100$

or $A + 40B = 2.5$

...(i)

At 30-Hz :

$$70 = 30A + (30)^2 B$$

i.e., $30A + 900B = 70$

or $3A + 90B = 7$

...(ii)

Solving (i) and (ii), we get $A = \frac{11}{6}$, $B = \frac{1}{60}$.

Hysteresis loss at 50-Hz

$$= Af = \frac{11}{6} \times 50 = 91.67 \text{ W.} \quad (\text{Ans.})$$

Eddy current loss at 50-Hz

$$= Bf^2 = \frac{1}{60} \times 50^2 = 41.67 \text{ W.} \quad (\text{Ans.})$$

Example 18. When a transformer is supplied at 400 V, 50-Hz the hysteresis loss is found to be 310 W and eddy current loss is found to be 260 W. Determine the hysteresis loss and eddy current loss when the transformer is supplied at 800 V, 100-Hz.

Solution. Hysteresis loss at 400 V, 50 Hz = 310 W

Eddy current loss at 400 V, 50-Hz = 260 W

We know that,

$$\text{Induced e.m.f.} \quad E = 4.44f\Phi_{\max}N = 4.44(B_{\max}A)/N$$

$$\text{i.e.} \quad E \propto B_{\max}f$$

$$\text{or} \quad B_{\max} \propto \frac{E}{f} = a \frac{E}{f} \quad [a = \text{constant}]$$

$$\text{In the IInd case, } B_{\max_1} = a \cdot \frac{E_1}{f_1} = a \cdot \frac{400}{50} = 8a.$$

$$\text{In the IIInd case, } B_{\max_2} = a \cdot \frac{E_2}{f_2} = a \cdot \frac{800}{100} = 8a$$

$$\text{Hence, } B_{\max_1} = B_{\max_2}$$

[∴ Core area A, and number of turns N remain the same]

$$\text{Hence, } P_h = Af^2 \quad \text{and} \quad P_e = Bf^2$$

$$P_{h1} = 310 \text{ W at } f_1 = 50\text{-Hz}$$

$$\therefore A = \frac{310}{50} = 6.2$$

Hysteresis loss at 100-Hz

$$= Af_2 = 6.2 \times 100 = 620 \text{ W. (Ans.)}$$

$$P_{e1} = 260 \text{ W at } f_1 = 50\text{-Hz}$$

$$\therefore B = \frac{260}{50^2} = 0.104$$

Eddy current loss at 100-Hz

$$= Bf_2^2 = 0.104 \times 100^2 = 1040 \text{ W. (Ans.)}$$

Transformer Tests (O.C. and S.C.) and Equivalent Circuit

Example 19. A 50-Hz, single-phase transformer has a turn ratio of 5. The resistances are 0.8Ω , 0.02Ω and reactances are 4Ω and 0.12Ω for high-voltage and low-voltage windings respectively. Find :

(i) The voltage to be applied to the h.v. side to obtain full-load current of 180 A in the l.v. winding on short-circuit.

(ii) The power factor on short-circuit.

Draw the equivalent circuit and vector diagram.

$$\text{Solution. Turn ratio, } \frac{N_1}{N_2} = 5, K = \frac{1}{5}$$

$$\text{Primary resistance, } R_1 = 0.8 \Omega$$

$$\text{Primary reactance, } X_1 = 4 \Omega$$

$$\text{Secondary resistance, } R_2 = 0.02 \Omega$$

$$\text{Secondary reactance, } X_2 = 0.12 \Omega$$

Total resistance referred to primary,

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} = 0.8 + 0.02 \times (5)^2 = 0.8 + 0.5 = 1.3 \Omega$$

Total reactance referred to secondary,

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} = 4 + 0.12(5)^2 = 4 + 3 = 7 \Omega$$

Total impedance referred to primary,

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = \sqrt{(1.3)^2 + (7)^2} = 7.12 \text{ ohm}$$

Also

$$I_1 = K I_2 = \frac{1}{5} \times 180 = 36 \text{ A}$$

(i) Voltage to be applied on h.v. side to obtain full-load current I_1 ,

$$V_{SC} = I_1 Z_{01} = 36 \times 7.12 = 256.3 \text{ V. (Ans.)}$$

(ii) The power factor on short-circuit,

$$\cos \phi_0 = \frac{R_{01}}{Z_{01}} = \frac{1.3}{7.12} = 0.1825. \text{ (Ans.)}$$

Equivalent circuit and vector diagram are shown in Figs. 45, 46 and 47.

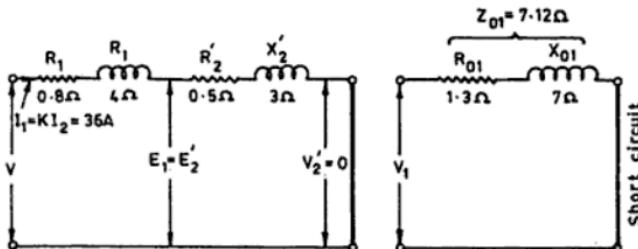


Fig. 45

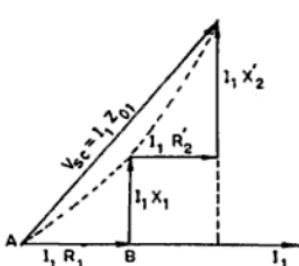


Fig. 46

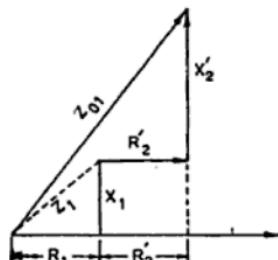


Fig. 47

Example 20. A 12 kVA 4000/400 V transformer has primary and secondary winding resistances of 13 Ω and 0.15 Ω and leakage reactances of 20 Ω and 0.25 Ω respectively. The magnetising reactance is 6000 Ω and the resistance representing core loss is 12000 Ω. Determine :

- (i) Equivalent resistance and reactance as referred to primary.
- (ii) Input current with secondary terminals open circuited.
- (iii) Input current when the secondary load current is 30 A at 0.8 power factor lagging.

Solution. Transformation ratio, $K = \frac{400}{4000} = \frac{1}{10}$

Primary resistance,	$R_1 = 13 \Omega$
Primary reactance,	$X_1 = 20 \Omega$
Secondary resistance,	$R_2 = 0.15 \Omega$
Secondary reactance,	$X_2 = 0.25 \Omega$
Magnetising reactance,	$X_0 = 6000 \Omega$
Resistance representing the core loss, $R_0 = 12000 \Omega$	

(i) Equivalent resistance referred to primary,

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2}$$

$$= 13 + \frac{0.15}{\left(\frac{1}{10}\right)^2} = 13 + 15 = 28 \Omega. \quad (\text{Ans.})$$

Equivalent reactance referred to primary,

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2}$$

$$= 20 + \frac{0.25}{\left(\frac{1}{10}\right)^2} = 20 + 25 = 45 \Omega. \quad (\text{Ans.})$$

(ii) Input current with secondary terminals open-circuited (or input current at no-load) :

$$\text{Magnetising component, } I_m = \frac{4000}{6000} = 0.667 \text{ A}$$

$$\text{Wattful component, } I_w = \frac{4000}{12000} = 0.333 \text{ A}$$

Hence input current at no-load,

$$I_0 = 0.333 - j0.667 = 0.745 \angle -63.5^\circ \text{ A.} \quad (\text{Ans.})$$

(iii) Input current I_1 :

$$\text{Secondary output current, } I_2 = 30 \text{ A}$$

(given)

$$\text{Power factor, } \cos \phi_2 = 0.8 \text{ (lagging)}$$

i.e.,

$$I_2 = 30 \angle -36.9^\circ$$

Secondary current referred to primary,

$$I_2' = K I_2 = \frac{30}{10} \angle -36.9^\circ = 3 \angle -36.9^\circ = 2.4 - j1.8$$

$$\therefore \text{Input current, } I_1 = I_2' + I_0 = (2.4 - j1.8) + (0.333 - j0.667)$$

$$= 2.733 - j2.467 = 3.68 \angle -42.07^\circ \text{ A.} \quad (\text{Ans.})$$

Example 21. Obtain the approximate equivalent circuit of a given 200/2000 V single-phase 30 kVA transformer having the following test results :

O.C. test : 200 V, 6.2 A, 360 W on l.v. side

S.C. test : 75 V, 18 A, 600 W on h.v. side.

Solution. O.C. test (l.v. side)Primary voltage, $V_1 = 200 \text{ V}$ No-load current, $I_0 = 6.2 \text{ A}$ No-load loss, $P_0 = 360 \text{ W}$ Now, $P_0 = V_1 I_0 \cos \phi_0$

$$360 = 200 \times 6.2 \times \cos \phi_0$$

$$\therefore \cos \phi_0 = \frac{360}{200 \times 6.2} = 0.29$$

$$\sin \phi_0 = 0.957$$

Wattful component of no-load current,

$$I_w = I_0 \cos \phi_0 = 6.2 \times 0.29 = 1.8 \text{ A.}$$

Resistance representing the core loss,

$$R_0 = \frac{V_1}{I_w} = \frac{200}{1.8} = 111.11 \Omega. \quad (\text{Ans.})$$

Magnetising component of no-load current,

$$I_m = I_0 \sin \phi_0 = 6.2 \times 0.95 = 5.93 \text{ A}$$

$$\text{Magnetising reactance, } X_0 = \frac{V_1}{I_m} = \frac{200}{5.93} = 33.7 \Omega. \quad (\text{Ans.})$$

S.C. test (h.v. side) :Short-circuit voltage, $V_{SC} = 75 \text{ V}$ Short-circuit current, $I_{SC} = 18 \text{ A}$ Losses, $P_{SC} = 600 \text{ W}$

Impedance of transformer referred to h.v. side,

$$Z_{02} = \frac{V_{SC}}{I_{SC}} = \frac{75}{18} = 4.167 \Omega$$

$$P_{SC} = I_{SC}^2 \times R_{02}$$

$$600 = 18^2 \times R_{02}$$

$$\therefore R_{02} = \frac{600}{18^2} = 1.85 \Omega$$

$$\text{Transformation ratio, } K = \frac{2000}{200} = 10$$

Referred to 200 V side :

$$Z_{01} = \frac{Z_{02}}{K^2} = \frac{4.167}{(10)^2} = 0.04167 \Omega$$

$$R_{01} = \frac{R_{02}}{K^2} = \frac{1.85}{(10)^2} = 0.0185 \Omega$$

$$\therefore Z_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{(0.04167)^2 - (0.0185)^2} = 0.0373 \Omega. \quad (\text{Ans.})$$

Approximate equivalent circuit is shown in Fig. 48.

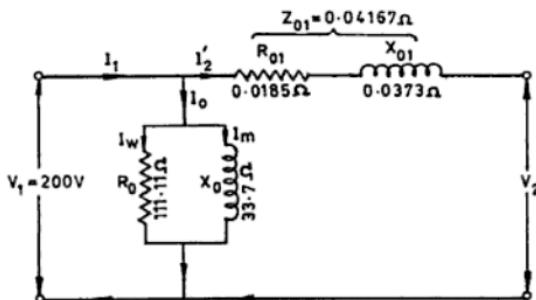


Fig. 48

Example 22. The following readings were obtained on O.C. and S.C. tests on a 200/400 V, 50 Hz, single-phase transformer.

O.C. test (l.v. side) : 200 V, 0.6 A, 60 W

S.C. test (h.v. side) : 15 V, 9 A, 80 W

Calculate the secondary voltage when delivering 4 kW at 0.8 power factor lagging, the primary voltage being 200 V.

Solution. O.C. test—l.v. side (*Instruments in the primary side and secondary open*)

$$\text{Primary voltage, } V_1 = 200 \text{ V}$$

$$\text{No-load current, } I_0 = 0.6 \text{ A}$$

$$\text{No-load loss, } P_0 = 60 \text{ W}$$

$$\begin{aligned} \text{Now, } P_0 &= V_1 I_0 \cos \phi_0 \\ 60 &= 200 \times 0.6 \times \cos \phi_0 \end{aligned}$$

$$\therefore \cos \phi_0 = \frac{60}{200 \times 0.6} = 0.5$$

$$\sin \phi_0 = 0.866$$

Wattful component of no-load current

$$I_w = I_0 \cos \phi_0 = 0.6 \times 0.5 = 0.3 \text{ A}$$

Magnetising component of no-load current,

$$I_m = I_0 \sin \phi_0 = 0.6 \times 0.866 = 0.52 \text{ A}$$

∴ Resistance representing the core loss,

$$R_0 = \frac{V_1}{I_w} = \frac{200}{0.3} = 666.67 \Omega. \quad (\text{Ans.})$$

$$\text{Magnetising reactance, } X_0 = \frac{V_1}{I_m} = \frac{200}{0.52} = 384.6 \Omega. \quad (\text{Ans.})$$

S.C. test—h.v. side (*Instruments in the secondary side and primary short-circuited*)

$$\text{Short circuit voltage, } V_{SC} = 15 \text{ V}$$

$$\text{Short circuit current, } I_{SC} = 9 \text{ A}$$

$$\text{Losses, } P_{SC} = 80 \text{ W}$$

Impedance of transformer referred to secondary,

$$Z_{02} = \frac{V_{SC}}{I_{SC}} = \frac{15}{9} = 1.667 \Omega$$

Also,

$$P_{SC} = I_{SC}^2 \times R_{02}$$

$$80 = 9^2 \times R_{02}$$

$$\therefore R_{02} = \frac{80}{81} = 0.987 \Omega \text{ (Ans.)}$$

Referred to 200 V side :

$$\text{Transformation ratio, } K = \frac{400}{200} = 2$$

$$Z_{01} = \frac{Z_{02}}{K^2} = \frac{1.667}{2^2} = 0.417 \Omega$$

$$R_{01} = \frac{R_{02}}{2^2} = \frac{0.987}{4} = 0.247 \Omega$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{(0.417)^2 - (0.247)^2} = 0.336 \Omega$$

$$\text{Output, } kVA = \frac{4}{0.8} = 5 \text{ kVA}$$

$$\text{Output current, } I_2 = \frac{5 \times 1000}{400} = 12.5 \text{ A. (Ans.)}$$

This value of I_2 is approximate because V_2 (which is to be calculated as yet) has been taken equal to 400 V (which in fact is equal to E_2 or $0V_2$)

Now,

$$Z_{02} = 1.667 \Omega$$

$$R_{02} = 0.987 \Omega$$

$$\therefore X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{1.667^2 - 0.987^2} = 1.343 \Omega$$

Total drop as referred to secondary

$$\begin{aligned} &= I_2 (R_{02} \cos \phi_2 + X_{02} \sin \phi_2) \\ &= 12.5(0.987 \times 0.8 + 1.343 \times 0.6) = 19.94 \text{ V} \end{aligned}$$

$$\therefore V_2 = 400 - 19.94 = 380 \text{ V}$$

Hence, secondary voltage = 380 V. (Ans.)

Approximate equivalent circuit is shown in Fig. 49.

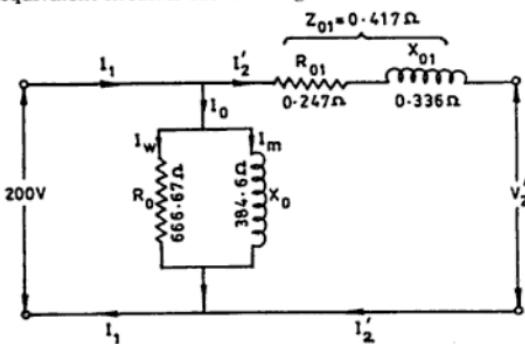


Fig. 49

Example 23. A 4 kVA, 400/200 V, 50-Hz single-phase transformer has the following test data :

O.C. test (l.v. side) 200 V, 1 A, 64 W

S.C. test (h.v. side) 15 V, 10 A, 80 W

Determine :

(i) Equivalent circuit referred to l.v. side, and

(ii) Secondary load voltage on full-load at 0.8 power factor lagging.

Solution. (i) O.C. test—l.v. side :

Voltage, $V_0 = 200 \text{ V}$

No-load current, $I_0 = 1 \text{ A}$

No-load loss, $P_0 = 64 \text{ W}$

Now, $P_0 = V_0 I_0 \cos \phi_0$

$$64 = 200 \times 1 \times \cos \phi_0$$

$$\therefore \cos \phi_0 = 0.32$$

$$\sin \phi_0 = 0.9474$$

Wattful component of no-load current,

$$I_w = I_0 \cos \phi_0 = 1 \times 0.32 = 0.32 \text{ A}$$

Magnetising component of no-load current,

$$I_m = I_0 \sin \phi_0 = 1 \times 0.9474 = 0.9474 \text{ A}$$

∴ Resistance representing the core loss,

$$R_0 = \frac{V_0}{I_w} = \frac{200}{0.32} = 625 \Omega. \quad (\text{Ans.})$$

$$\text{Magnetising reactance, } X_0 = \frac{V_0}{I_m} = \frac{200}{0.9474} = 211.1 \Omega. \quad (\text{Ans.})$$

S.C. test—h.v. side :

Short-circuit voltage, $V_{SC} = 15 \text{ V}$

Short-circuit current, $I_{SC} = 10 \text{ A}$

Losses, $P_{SC} = 80 \text{ W}$

Impedance of the circuit referred to h.v. side,

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{15}{10} = 1.5 \Omega. \quad (\text{Ans.})$$

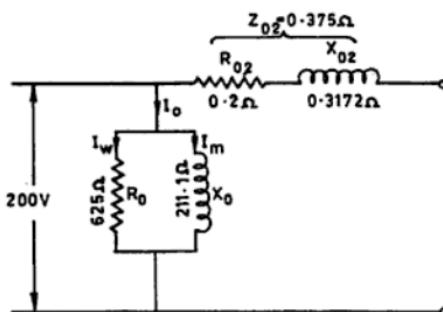


Fig. 50

Also $P_{SC} = I_{SC}^2 \times R_{01}$
 $\therefore 80 = 10^2 \times R_{01}$
 $\therefore R_{01} = \frac{80}{100} = 0.8 \Omega. \text{ (Ans.)}$

Referred to l.v. side :

Transformation ratio, $K = \frac{200}{400} = \frac{1}{2}$
 $Z_{02} = K^2 Z_{01} = (\frac{1}{2})^2 \times 1.5 = 0.375 \Omega. \text{ (Ans.)}$
 $R_{02} = K^2 R_{01} = (\frac{1}{2})^2 \times 0.8 = 0.2 \Omega. \text{ (Ans.)}$
 $\therefore X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{(0.375)^2 - (0.2)^2} = 0.3172 \Omega. \text{ (Ans.)}$

The approximate equivalent circuit is shown in Fig. 52.

(ii) Secondary load voltage, V_2 :

Secondary full-load current, $I_2 = \frac{4 \times 1000}{200} = 20 \text{ A}$

$$\cos \phi_2 = 0.8$$

$$\sin \phi_2 = 0.6$$

$\therefore I_2 = 20(0.8 - j0.6) = (16 - j12)$

$$Z_{02} = R_{02} + jX_{02} = 0.2 + j0.3172$$

Secondary load voltage, $V_2 = 200 - I_2 Z_{02} = 200 - (16 - j12)(0.2 + j0.3712)$
 $= 200 - (3.2 + j5.075 - j2.4 + 3.806)$
 $= 200 - (7 + j2.675) = 193 - j2.675 = 193 \text{ V. (Ans.)}$

Example 24. A single-phase step-down transformer has a turn ratio of 3. The resistance and reactance of the primary winding are 1.2Ω and 6Ω and those of the secondary winding are 0.05Ω and 0.03Ω respectively. If the h.v. winding is supplied at $230 \text{ V}, 50\text{-Hz}$ with l.v. winding short circuited, find :

- (i) Current in the l.v. winding, (ii) Copper loss in the transformer, and
 (iii) Power factor.

Solution. Turn ratio $= 3$, i.e., $K = \frac{1}{3}$

Resistance of primary, $R_1 = 1.2 \Omega$

Reactance of primary, $X_1 = 6 \Omega$

Resistance of secondary, $R_2 = 0.05 \Omega$

Reactance of secondary, $X_2 = 0.3 \Omega$

Referred to h.v. side

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} = 1.2 + 0.05 \times (3)^2 = 1.65 \Omega$$

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} = 6 + 0.3 \times (3)^2 = 8.7 \Omega$$

$$Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = \sqrt{(1.65)^2 + (8.7)^2} = 8.855 \Omega$$

Current in h.v. winding when l.v. winding is short-circuited,

$$I_{SC} = \frac{V_{SC}}{Z_{01}} = \frac{230}{8.855} = 25.97 \text{ A}$$

Neglecting I_0 , $I_1 = I_2' = 25.97 \text{ A}$

(i) Current in the l.v. winding,

$$I_2 = \frac{I_2'}{K} = \frac{25.97}{\left(\frac{1}{3}\right)} = 77.91 \text{ A. (Ans.)}$$

$$(ii) \text{Total copper loss} = I_1^2 R_{01} = (25.97)^2 \times 1.65 = 1112.8 \text{ W. (Ans.)}$$

(iii) Primary power factor :

Power input on short-circuit,

$$P_{SC} = V_{SC} I_{SC} \cdot \cos \phi_{SC}$$

$$1112.8 = 230 \times 25.97 \times \cos \phi_{SC}$$

$$\therefore \cos \phi_{SC} = \frac{1112.8}{230 \times 25.97} = 0.1863. \text{ (Ans.)}$$

Example 25. A single-phase, 3 kVA, 230/115 V, 50-Hz transformer has the following constants :

Resistance : Primary 0.3 Ω, secondary 0.09 Ω

Reactance : Primary 0.4 Ω, secondary 0.1 Ω

Resistance of equivalent exciting circuit referred to primary, $R_0 = 600 \Omega$.

Reactance of equivalent exciting circuit-referred to primary, $X_0 = 200 \Omega$.

What would be the readings of the instruments when the transformer is connected for (i) O.C. test, (ii) S.C. test. In both tests supply is given to h.v. side.

Solution. Primary resistance, $R_1 = 0.3 \Omega$

Primary reactance, $X_1 = 0.4 \Omega$

Secondary resistance, $R_2 = 0.09 \Omega$

Secondary reactance, $X_2 = 0.1 \Omega$

$R_0 = 600 \Omega$

$X_0 = 200 \Omega$

(i) O.C. test :

Wattful component of no-load current,

$$I_w = \frac{V_1}{R_0} = \frac{230}{600} = 0.383 \text{ A}$$

Magnetising component of no-load current,

$$I_m = \frac{V_1}{X_0} = \frac{230}{200} = 1.15 \text{ A}$$

$$\therefore \text{No-load current, } I_0 = \sqrt{I_w^2 + I_m^2} = \sqrt{(0.383)^2 + (1.15)^2} = 1.212 \text{ A}$$

Input on no-load to h.v. winding

$$= V_1 I_w = 230 \times 0.383 = 88.09 \text{ W}$$

Hence, the readings of the instruments are :

Voltmeter reading = 230 V. (Ans.)

Ammeter reading = 1.212 A. (Ans.)

Wattmeter reading = 88.09 W. (Ans.)

(ii) S.C. test :

$$\text{Transformation ratio, } K = \frac{115}{230} = \frac{1}{2}$$

$$\text{Referred to h.v. side, } R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} = 0.3 + \frac{0.09}{(\frac{1}{2})^2} = 0.66 \Omega$$

$$X_{01} = X_1 + X_2' = X_1 + \frac{X_2}{K^2} = 0.4 + \frac{0.1}{(\frac{1}{2})^2} = 0.8 \Omega$$

$$\therefore Z_{01} = \sqrt{R_{01}^2 + X_{01}^2} = \sqrt{(0.66)^2 + (0.8)^2} = 1.037 \Omega$$

Full-load current in the h.v. winding

$$I_1 = \frac{3 \times 1000}{230} = 13.04 \text{ A}$$

Voltage to be applied to h.v. winding on short-circuiting l.v. winding to pass full-load current of 13.04 A through h.v. winding.

$$V_{SC} = I_1 Z_{01} = 13.04 \times 1.037 = 13.52 \text{ V}$$

Power supplied to h.v. winding on short-circuit

$$= I_1^2 \cdot R_{01} = (13.04)^2 \times 0.66 = 112.2 \text{ W}$$

Hence, the readings of the instruments are :

Voltmeter reading = 13.52 V. (Ans.)

Ammeter reading = 13.04 A. (Ans.)

Wattmeter reading = 112.2 W. (Ans.)

Regulation and Efficiency of a Transformer

Example 26. A 4kVA 220/440 V, 50 Hz, single-phase transformer gave the following test figures. No load test performed on 220 V side keeping 440 V side open : 220 V, 0.7 A, 60 W. Short circuit test performed short circuiting the 440 V side through an ammeter : 9V, 6A, 21.6W calculate.

(a) The magnetising current and the component corresponding to iron loss at normal voltage and frequency.

(b) The efficiency at full-load at unity power factor and the corresponding secondary terminal voltage.

(c) Draw the phasor diagram corresponding to the full load operation. (PTU, May, 2000)

Solution. Open circuit test on 220 V (l.v.) side : $V_1 = 220 \text{ V}$; $P_0 = 60 \text{ W}$; $I_0 = 0.7 \text{ A}$

Short circuit test on 440 V (h.v.) side : $V_{SC} = 9 \text{ V}$; $I_{SC} = 6 \text{ A}$; $P_{SC} = 21.6 \text{ W}$

(a) $P_0 = V_1 I_0 \cos \phi_0$ or $60 = 220 \times 0.7 \times \cos \phi_0$

or $\cos \phi_0 = 0.3896$, and $\sin \phi_0 = 0.921$

∴ Iron loss component of current, $I_w = I_0 \cos \phi_0 = 0.7 \times 0.3896 = 0.273 \text{ A}$. (Ans.)

Magnetising component of current, $I_m = I_0 \sin \phi_0 = 0.7 \times 0.921 = 0.6447 \text{ A}$. (Ans.)

(b) Full-load secondary current, $I_2 = \frac{4 \times 1000}{440} = 9.1 \text{ A}$

Full-load primary current, $I_1 = \frac{4 \times 1000}{220} = 18.2 \text{ A}$

Full-load copper losses, $P_c = \left(\frac{I_1}{I_{sc}} \right)^2 \times P_{SC} = \left(\frac{18.2}{6} \right)^2 \times 21.6 = 198.7 \text{ W}$

∴ Full-load efficiency at unity power factor,

$$\eta = \frac{4 \times 1000 \times 1}{4 \times 1000 \times 1 + 60 + 198.7} \times 100 = 93.92\%. \text{ (Ans.)}$$

From short circuit test, we have

$$Z_{01} = \frac{V_{SC}}{I_{sc}} = \frac{9}{6} = 1.5 \Omega$$

$$R_{01} = \frac{P_{SC}}{I_{sc}^2} = \frac{21.6}{6^2} = 0.6 \Omega$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{1.5^2 - 0.6^2} = 1.375 \Omega$$

Now, $R_{02} = K^2 R_{01} = (2)^2 \times 0.6 = 2.4 \Omega$ $\left(\because K = \frac{440}{220} = 2 \right)$

$$X_{02} = K^2 X_{01} = 2^2 \times 1.375 = 5.5 \Omega$$

Since $\cos \phi_2 = 1 \quad \therefore \sin \phi_2 = \sin^{-1} (\cos^{-1} 1) = 0$

$$V_2^2 = (V_2 + I_2 R_{02})^2 + (I_2 X_{02})^2$$

$$(440)^2 = (V_2 + 9.1 \times 2.4)^2 + (9.1 \times 5.5)^2$$

or $(V_2 + 21.84)^2 = (440)^2 - (9.1 \times 5.5)^2 = 191095$

or $V_2 = (\sqrt{191095} - 21.84) = 415.3 \text{ V. (Ans.)}$

(c) The phasor diagram of transformer corresponding to full-load operation is shown in Fig. 51.

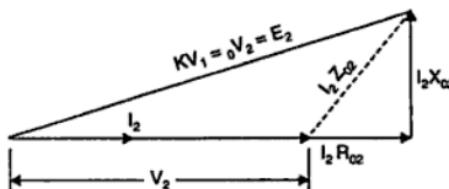


Fig. 51

Example 27. The parameters of the equivalent circuit of a 100 kVA, 2000 / 200 volt single-phase transformer are as follows :

Primary resistance = 0.2 ohms ;

Secondary resistance = 2 milli ohms.

Primary leakage reactance = 0.45 ohms ;

Secondary leakage reactance = 4.5 milli ohms.

Core loss resistance = 10 kilo ohms ;

Magnetizing reactance = 1.55 kilo ohms.

Using the circuit referred to primary, determine the :

(i) Voltage regulation.

(ii) Efficiency of the transformer operating at rated load with 0.8 lagging power factor.

(PTU, June and Dec. 2000)

Solution. Given : Rating = 100 kVA ; $R_1 = 0.2 \Omega$; $R_2 = 0.002 \Omega$;

$$X_1 = 0.45 \Omega ; X_2 = 0.0045 \Omega ; R_0 = 10000 \Omega ; X_0 = 1550 \Omega.$$

(i) Voltage regulation :

$$\text{Transformation ratio, } K = \frac{200}{2000} = 0.1$$

$$R_{01} = R_1 + R'_2 = R_1 + \frac{R_2}{K^2} = 0.2 + \frac{0.002}{0.1^2} = 0.4 \Omega$$

$$X_{01} = X_1 + X'_2 = X_1 + \frac{X_2}{K^2} = 0.45 + \frac{0.0045}{0.1^2} = 0.9 \Omega$$

$$\text{Primary full-load current, } I_1 = \frac{100 \times 1000}{2000} = 50 \text{ A,}$$

$$\cos \phi = 0.8, \sin \phi = \sin [\cos^{-1}(0.8)] = 0.6$$

Refer Fig. 52.

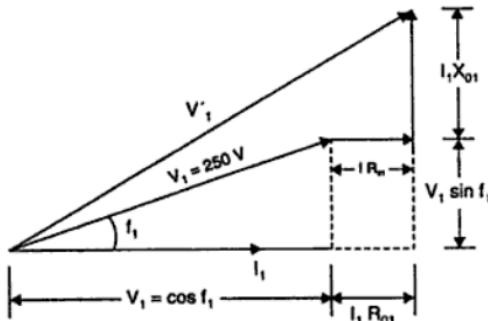


Fig. 52

$$\begin{aligned} \text{Applied voltage, } V_1 &= \sqrt{(V_1 \cos \phi + I_1 R_{01})^2 + (V_1 \sin \phi + I_1 X_{01})^2} \\ &= \sqrt{(2000 \times 0.8 + 50 \times 0.4)^2 + (2000 \times 0.6 + 50 \times 0.9)^2} = 2043 \text{ V} \\ \therefore \% \text{ voltage regulation} &= \frac{V_1 - V_1}{V_1} \times 100 = \frac{2043 - 2000}{2000} \times 100 = 2.15\%. \text{ (Ans.)} \end{aligned}$$

(ii) Efficiency of the transformer, η :

$$\text{Working component of no-load current, } I_w = \frac{V}{R_0} = \frac{2000}{10000} = 0.2 \text{ A}$$

$$\text{Iron loss} = V_1 I_0 \cos \phi_0 = V_1 I_w = 2000 \times 0.2 = 400 \text{ W}$$

$$\text{Full-load copper losses, } P_c = I_1^2 R_{01} = (50)^2 \times 0.4 = 1000 \text{ W}$$

Efficiency of the transformer at 0.8 p.f.,

$$\begin{aligned} \% \eta &= \frac{kVA \times 1000 \times \cos \phi}{(kVA \times 1000 \times \cos \phi) + P_i + P_c} \times 100 \\ &= \frac{(100 \times 1000 \times 0.8)}{(100 \times 1000 \times 0.8 + 400 + 1000)} \times 100 \\ &= 98.28\%. \text{ (Ans.)} \end{aligned}$$

Example 28. In a 25 kVA, 2000/200 V transformer, the constant and variable losses are 350 W and 400 W respectively. Calculate the efficiency on u.p.f. at

(i) Full load, and

(ii) Half full load.

[PTU, 1999]

Solution. Rating of transformer = 25 kVA

Constant or iron losses, $P_i = 350 \text{ W or } 0.35 \text{ kW}$

Variable or copper losses, $P_c = 400 \text{ W or } 0.4 \text{ kW}$

Power factor, $\cos \phi = 1$

Efficiency, η :

(i) At full load :

$$\begin{aligned}\eta &= \frac{\text{output}}{\text{output} + \text{losses}} = \frac{kVA \cos \phi}{kVA \cos \phi + P_i + P_c} \\ &= \frac{25 \times 1}{25 \times 1 + 0.35 + 0.4} = 0.9708 \text{ or } 97.08\%. \text{ (Ans.)}\end{aligned}$$

(ii) At half full load :

$$\begin{aligned}\eta &= \frac{(0.5 \times 25) \times 1}{(0.5 \times 25 \times 1) + 0.35 + \left[\left(\frac{1}{2} \right)^2 \times 0.4 \right]} \\ &= 0.9653 \text{ or } 96.53\%. \text{ (Ans.)}\end{aligned}$$

Example 29. The following readings were obtained from O.C. and S.C. tests on 8 kVA 400/120 V, 50-Hz transformer.

O.C. test (l.v. side) : 120 V; 4 A; 75 W.

S.C. test (h.v. side) : 9.5 V; 20 A; 110 W.

Calculate :

- (i) The equivalent circuit (approximate) constants,
- (ii) Voltage regulation and efficiency for 0.8 lagging power factor load, and
- (iii) The efficiency at half full-load and 0.8 power factor load.

Solution. (i) Transformation ratio, $K = \frac{120}{400} = \frac{3}{10}$

O.C. test :

It is seen from the O.C. test, that primary open, the secondary draws a no-load current of 4 A.

Since $K = \frac{3}{10}$, the corresponding no-load current $I_0 = 4 \times \frac{3}{10} = 1.2 \text{ A}$.

Also

$$P_0 = V_1 I_0 \cos \phi_0$$

∴

$$75 = 400 \times 1.2 \times \cos \phi_0$$

i.e.,

$$\cos \phi_0 = \frac{75}{400 \times 1.2} = 0.156$$

and

$$\sin \phi_0 = 0.987$$

Now, wattful component of no-load current, I_{0w} ,

$$I_{0w} = I_0 \cos \phi_0 = 1.2 \times 0.156 = 0.187 \text{ A}$$

and magnetising component of no-load current I_m ,

$$I_m = I_0 \sin \phi_0 = 1.2 \times 0.987 = 1.184 \text{ A}$$

∴ Resistance representing the core loss,

$$R_0 = \frac{V_1}{I_{0w}} = \frac{400}{0.187} = 2139 \Omega. \text{ (Ans.)}$$

$$\text{Magnetising reactance, } X_0 = \frac{V_1}{I_m} = \frac{400}{1.184} = 337.8 \Omega. \text{ (Ans.)}$$

S.C. test :

During S.C. test the instruments have been placed in primary.

Here,

$$V_{SC} = 9.5 \text{ V}$$

$$I_{SC} = 20 \text{ A}$$

$$P_{SC} = 110 \text{ W}$$

Now,

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{9.5}{20} = 0.475 \Omega. \quad (\text{Ans.})$$

$$R_{01} = \frac{P_{SC}}{I_{SC}^2} = \frac{110}{(20)^2} = 0.25 \Omega. \quad (\text{Ans.})$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{(0.475)^2 - (0.25)^2} = 0.404 \Omega. \quad (\text{Ans.})$$

The equivalent circuit is shown in Fig. 53.

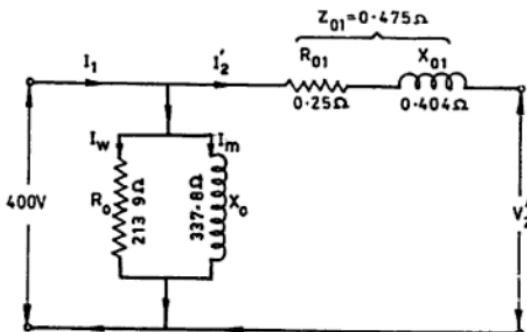


Fig. 53

(ii) Total approximate voltage drop as referred to primary is

$$= I_1 (R_{01} \cos \phi + X_{01} \sin \phi)$$

$$\text{Now, full-load, } I_1 = \frac{8 \times 1000}{400} = 20 \text{ A}$$

$$\therefore \text{Voltage drop} = 20 (0.25 \times 0.8 + 0.404 \times 0.6) = 8.85 \text{ V}$$

$$\% \text{ Voltage regulation} = \frac{8.85}{400} \times 100 = 2.21\%. \quad (\text{Ans.})$$

$$\text{Iron loss, } P_i = 75 \text{ W}$$

$$\text{Copper loss, } P_c = 110 \text{ W}$$

$$\text{Full-load losses} = P_i + P_c = 75 + 110 = 185 \text{ W}$$

$$\therefore \text{Full-load output} = 8 \times 1000 \times 0.8 = 6400 \text{ W}$$

$$\therefore \text{Full-load efficiency, } \eta = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{6400}{6400 + 185} = 0.972 \text{ or } 97.2\%. \quad (\text{Ans.})$$

(iii) Half full-load :

$$\text{Iron loss, } P_i = 75 \text{ W}$$

$$\text{Copper loss, } P_c = \left(\frac{1}{2}\right)^2 \times 110 = 27.5 \text{ W}$$

$$\text{Total losses} = P_i + P_c = 75 + 27.5 = 102.5 \text{ W}$$

$$\text{Output at half full-load} = \frac{1}{2} \times 8 \times 1000 \times 0.8 = 3200 \text{ W}$$

$$\therefore \text{Efficiency} = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{3200}{3200 + 102.5} = 0.969 \text{ or } 96.9\%. \quad (\text{Ans.})$$

Example 30. Consider a 20 kVA, 2200/220 V, 50 Hz transformer. The OC/SC test results are as follows :

O.C. Test : 220 V, 4.2 A, 148 W (l.v. side)

S.C. Test : 86 V, 10.5 A, 360 W (h.v. side)

(i) Determine the regulation at 0.8 p.f. lagging at full load.

(ii) What is the p.f. on short-circuit ?

(Nagpur University, 1998)

Solution. Given :

S.C. Test :

$$V_{SC} = 86 \text{ V}, I_{SC} = 10.5 \text{ A}, P_C = 360 \text{ W}$$

$$(i) \text{Regulation : Equivalent impedance referred to primary, } Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{86}{10.5} = 8.19 \Omega$$

\therefore Short-circuit test has been conducted on the h.v. (primary) side

$$\text{Equivalent resistance referred to primary, } R_{01} = \frac{P_{SC}}{I_{SC}^2} = \frac{360}{(10.5)^2} = 3.27 \Omega$$

$$\text{Equivalent reactance referred to primary, } X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{8.19^2 - 3.27^2} = 7.51 \Omega$$

$$\text{Full load primary current, } I_1 = \frac{20 \times 1000}{2200} = 9.09 \text{ A}$$

$$\begin{aligned} \text{Percentage regulation} &= \frac{I_1 (R_{01} \cos \phi + X_{01} \sin \phi)}{V_1} \times 100 \\ &= \frac{9.09(3.27 \times 0.8 + 7.51 \times 0.6)}{2200} \times 100 = 2.94\%. \quad (\text{Ans.}) \end{aligned}$$

(ii) P.f. on short-circuit, $\cos \phi_{SC}$:

$$\therefore \cos \phi_{SC} = \frac{R_{01}}{Z_{01}} = \frac{3.27}{8.19} = 0.399 \text{ (lag).} \quad (\text{Ans.})$$

Example 31. High voltage side short circuit test data for 20 kVA, 2300/230 V transformer are :

Power = 250 watts ; Current = 8.7 A ; Voltage = 50 V.

Calculate equivalent impedance, resistance, reactance referred to h.v. side. Find the transformer regulation at 0.7 lagging power factor.

Solution. Given : h.v. side : $P_{SC} = 250 \text{ W}$; $I_{SC} = 8.7 \text{ A}$; $V_{SC} = 50 \text{ V}$; $\cos \phi = 0.7$.

From S.C. test with measurements performed on h.v. side the various parameters referred to h.v. side are :

$$R_{01} = \frac{P_{SC}}{I_{SC}^2} = \frac{250}{8.7^2} = 3.303 \Omega$$

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{50}{8.7} = 5.747 \Omega$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{5.747^2 - 3.303^2} = 4.703 \Omega$$

$$\text{We know that, \% Regulation} = \frac{I_1 R_{01} \cos \phi + I_1 X_{01} \sin \phi}{V_1} \times 100$$

where $I_1 = \frac{20 \times 10^3}{2300} = 8.696 \text{ A}$ (rated current); and

$\cos \phi = 0.7$ (given) and hence $\sin \phi = \sin(\cos^{-1} 0.7) = 0.714$.

$$\therefore \% \text{ Regulation} = \frac{8.696 \times 3.303 \times 0.7 + 8.696 \times 4.703 \times 0.714}{2300} \times 100 = 2.14\%. \quad (\text{Ans.})$$

Example 32. A 10 kVA, 2300/230 V, 50 Hz, distribution transformer has h.v. winding resistance 3.96Ω and leakage resistance of 15.8Ω . The l.v. winding has corresponding value of 0.0396Ω and 0.158Ω respectively. The transformer has a core loss of 58 W under normal operating conditions. Find :

(i) Load terminal voltage when transformer delivers rated current at 0.8 p.f. lagging to a load on l.v. side, with h.v. side voltage held at rated value and compute efficiency at this load.

(ii) The h.v. side voltage necessary to maintain rated voltage at load terminals when the transformer is loaded as above. Is efficiency same as in (i)? (AMIE Summer, 1999)

Solution. Given : $R_1 = 3.96 \Omega$; $X_1 = 15.8 \Omega$; $R_2 = 0.0396 \Omega$; $X_2 = 0.158 \Omega$;
 $P_i = 58 \text{ W}$; p.f. = 0.8 lagging

(i) **Load terminal voltage :**

$$\text{Rated secondary current, } I_2 = \frac{10 \times 10^3}{230} = 43.48 \text{ A}$$

$$R_{02} = R_2 + K^2 R_1 = 0.0396 + \left(\frac{230}{2300} \right)^2 \times 3.96 = 0.0792 \Omega$$

$$X_{02} = X_2 + K^2 X_1 = 0.158 + \left(\frac{230}{2300} \right)^2 \times 15.8 = 0.316 \Omega$$

$$\therefore \text{Voltage drop on load side} = I_2 (R_{02} \cos \phi + X_{02} \sin \phi)$$

$$= 43.48 (0.0792 \times 0.8 + 0.316 \times 0.6) = 11 \text{ V}$$

$$\therefore \text{Load terminal voltage} = 230 - 11 = 219 \text{ V.} \quad (\text{Ans.})$$

$$\text{Copper loss (P}_C) = I_2^2 R_{02} = 43.48^2 \times 0.0792 = 149.73 \text{ W}$$

$$\begin{aligned} \eta &= \frac{\text{Output}}{\text{Output} + \text{Core loss (P}_i) + \text{Copper loss (P}_C)} \\ &= \frac{10 \times 10^3 \times 0.8}{(10 \times 10^3 \times 0.8) + 58 + 149.73} = 0.9747 \text{ or } 97.47\%. \quad (\text{Ans.}) \end{aligned}$$

(ii) To maintain rated voltage at load terminals of 230 V, the O.C. voltage required at secondary terminals would be $230 + 11 = 241$ V. Hence primary induced voltage required

$$= 241 \times \frac{2300}{230} = 2410 \text{ V.} \quad (\text{Ans.})$$

Example 33. The following test results were obtained for a 1000/100 V, 100 kVA single-phase transformer :

O.C. test :

Primary volts = 1000, secondary volts = 100, watts in primary = 950.

S.C. test :

Primary volts for full-load current = 20, watts in primary = 1000.

Determine the regulation and efficiency of the transformer at full-load and at 0.8 power factor lagging.

(i) **Unity power factor, $\cos \phi_2 = 1$:**

$$\begin{aligned}\text{Voltage drop} &= I_2 R_{02} \cos \phi_2 + I_2 X_{02} \sin \phi_2 = 120 \times 0.02648 \times 1 + 0 = 3.177 \text{ V} \\ \text{\% regulation} &= \frac{3.177}{250} \times 100 = 1.27\%. \quad (\text{Ans.})\end{aligned}$$

(ii) **0.8 power factor (lagging) :**

$$\begin{aligned}\text{Voltage drop} &= I_2 R_{02} \cos \phi_2 + I_2 X_{02} \sin \phi_2 \\ &= 120 \times 0.02648 \times 0.8 + 120 \times 0.04304 \times 0.6 = 5.64 \text{ V} \\ \text{\% regulation} &= \frac{5.64}{250} \times 100 = 2.256\%. \quad (\text{Ans.})\end{aligned}$$

(iii) **0.8 power factor (leading) :**

$$\begin{aligned}\text{Voltage drop} &= I_2 R_{02} \cos \phi_2 - I_2 X_{02} \sin \phi_2 \\ &= 120 \times 0.02648 \times 0.8 - 120 \times 0.04304 \times 0.6 = -0.557 \text{ V} \\ \text{\% regulation} &= -\frac{0.557}{250} \times 100 = -0.223\%. \quad (\text{Ans.})\end{aligned}$$

Example 35. Short-circuit test is conducted on a 5 kVA, 400 V/100 V single phase transformer with 100 V winding shorted. The input voltage at full load current is 40 V. The wattmeter, on the input reads 250 W. Find the power factor for which regulation at full load is zero. (GATE, 1994)

Solution. Given : Rating of transformer : 5 kVA, 400 V/100 V

Input power, on short-circuit, $P_{SC} = 250 \text{ W}$

The input voltage at full load current, $V_{SC} = 40 \text{ V}$

Power factor for which regulation at full load is zero :

$$\text{Input current } I_{SC} = \text{full load current, } I_1 = \frac{5 \times 1000}{400} = 12.5 \text{ A}$$

$$\text{Equivalent resistance as referred to primary, } R_{01} = \frac{P_{SC}}{I_{SC}^2} = \frac{250}{(12.5)^2} = 1.6 \Omega$$

$$\text{Equivalent impedance referred to primary, } Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{40}{12.5} = 3.2 \Omega$$

$$\text{Equivalent reactance referred to primary, } X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{3.2^2 - 1.6^2} = 2.77 \Omega$$

Regulation will be zero when phase angle,

$$\phi = \tan^{-1} \frac{R_{02}}{X_{02}} = \tan^{-1} \frac{R_{01}}{X_{01}} = \tan^{-1} \left(\frac{1.6}{2.77} \right) = 30^\circ$$

or **power factor** $= \cos \phi = \cos (30^\circ) = 0.866. \quad (\text{Ans.})$

Example 36. A 50 MVA, 76.2 V/33 kV, 1-phase, 50 Hz, two-winding transformer with tap changer has percentage impedance of $0.5 + j7.0$. What tapping must be used to maintain rated voltage at the secondary on

(i) *full load at 0.8 lagging power factor, and*

(ii) *40 MVA load at 0.6 lagging power factor.*

Assume that the tap changer is provided on the h.v. side.

Solution. Given : Rated MVA = 50 ; $f = 50 \text{ Hz}$; $E_1 = 76.2 \text{ V}$; $E_2 = 33 \text{ kV}$; percentage impedance = $0.5 + j7.0$.

$$\begin{aligned}
 \text{(i) Percentage regulation} &= \frac{I_2 R_{02} \cos \phi + I_2 X_{02} \sin \phi}{E_2} \times 100 \\
 &= \frac{I_2 R_{02}}{E_2} \times 100 \cos \phi + \frac{I_2 X_{02}}{E_2} \times 100 \sin \phi \\
 &= \% R \cos \phi + \% X \sin \phi \\
 &= 0.5 \times 0.8 + 7 \times 0.6 = 4.6\%
 \end{aligned}$$

i.e., voltage to be raised for maintaining rated voltage = 4.6%

So tap setting required on h.v. side = - 4.6% or 4.6% down. (Ans.)

(ii) At load of 40 MVA i.e. 80% of full load or 0.8 times full load,

$$\begin{aligned}
 \text{voltage regulation} &= 0.8 (\% R \cos \phi + \% X \sin \phi) \\
 &= 0.8(0.5 \times 0.6 + 7 \times 0.8) = 4.72\%
 \end{aligned}$$

Tap setting required on h.v. side = 4.72% down. (Ans.)

Note. If the tap changer is on the primary side, tap setting will be down and if it is to be provided on secondary side, tap setting will be up for raising the secondary voltage on load.

Example 37. The percentage resistance and reactance of a transformer are 2% and 4% respectively. Find the approximate regulation on full-load at :

- (i) Unity power factor,
- (ii) 0.8 power factor lagging, and
- (iii) 0.8 power factor leading.

Solution. Percentage resistance = 2%

Percentage reactance = 4%

Approximate % regulation = % resistance \times cos ϕ \pm % reactance \times sin ϕ

(i) **Unity power factor :**

$$\begin{aligned}
 \text{Approximate \% regulation} &= \% \text{ resistance} \cos \phi && (\because \sin \phi = 0) \\
 &= 2 \times 1 = 2\%. \quad (\text{Ans.})
 \end{aligned}$$

(ii) **0.8 power factor lagging :**

$$\begin{aligned}
 \text{Approximate \% regulation} &= \% \text{ resistance} \cos \phi + \% \text{ reactance} \times \sin \phi \\
 &= 2 \times 0.8 + 4 \times 0.6 = 1.6 + 2.4 = 4\%. \quad (\text{Ans.})
 \end{aligned}$$

(iii) **0.8 power factor leading :**

$$\begin{aligned}
 \text{Approximate \% regulation} &= \% \text{ resistance} \cos \phi - \% \text{ reactance} \times \sin \phi \\
 &= 2 \times 0.8 - 4 \times 0.6 = 1.6 - 2.4 = - 0.8\%. \quad (\text{Ans.})
 \end{aligned}$$

Example 38. A single-phase 80 kVA, 2000/200 V, 50-Hz transformer has impedance drop of 8% and resistance drop of 4% :

(i) Find the regulation at full-load 0.8 power factor lagging.

(ii) At what power factor is the regulation zero.

Solution. Impedance drop = 8%

Resistance drop = 4%

$$\text{i.e., } \frac{I_2 Z_{02}}{V_2} = \frac{8}{100} \quad \text{or} \quad I_2 Z_{02} = \frac{200 \times 8}{100} = 16 \text{ V}$$

$$\text{and } \frac{I_2 R_{02}}{V_2} = \frac{4}{100} \quad \text{or} \quad I_2 R_{02} = \frac{200 \times 4}{100} = 8 \text{ V}$$

$$\therefore I_2 X_{02} = \sqrt{(I_2 Z_{02})^2 - (I_2 R_{02})^2} = \sqrt{16^2 - 8^2} = 13.86 \text{ V.}$$

$$(i) \% \text{ regulation} = \frac{I_2 R_{02} \cos \phi_2 + I_2 X_{02} \sin \phi_2}{V_2}$$

$$= \frac{8 \times 0.8 + 13.86 \times 0.6}{200} = \frac{6.4 + 8.316}{200} = 7.36\%. \quad (\text{Ans.})$$

(ii) Regulation can be zero only when the power factor is leading. Then

$$\frac{I_2 R_{02} \cos \phi_2 - I_2 X_{02} \sin \phi_2}{V_2} = 0$$

or $I_2 R_{02} \cos \phi_2 - I_2 X_{02} \sin \phi_2 = 0$

or $I_2 R_{02} \cos \phi_2 = I_2 X_{02} \sin \phi_2$

or $\tan \phi_2 = \frac{I_2 R_{02}}{I_2 X_{02}} = \frac{8}{13.86} = 0.577 \quad \text{or} \quad \phi_2 = 30^\circ$

\therefore Power factor $= \cos \phi_2 = 0.866$ leading. (Ans.)

Example 39. The high voltage of a single-phase 200 kVA 4400/220 V transformer takes a current of 35 A and power of 1250 W at 80 V when the low voltage winding is short-circuited. Determine :

(i) The voltage to be applied to the high voltage winding on full-load at 0.8 power factor lagging if the full-load secondary terminal voltage is to be kept at 220 V.

(ii) % regulation.

Solution. (i) Transformation ratio, $K = \frac{220}{4400} = \frac{1}{20}$

Voltage applied to h.v. winding in S.C. test

$$V_{SC} = 80 \text{ V}$$

and

$$I_{SC} = 35 \text{ A}$$

$$P_{SC} = 1250 \text{ W}$$

Referred to h.v. side,

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{80}{35} = 2.28 \Omega$$

$$R_{01} = \frac{P_{SC}}{I_{SC}^2} = \frac{1250}{35^2} = 1.02 \Omega$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{2.28^2 - 1.02^2} = 2.04 \Omega$$

Full-load current in h.v. winding,

$$I_1 = \frac{200 \times 1000}{4400} = 45.45 \text{ A}$$

Voltage drop in resistance $= I_1 R_{01} = 45.45 \times 1.02 = 46.36 \text{ V}$

Voltage drop in reactance $= I_1 X_{01} = 45.45 \times 2.04 = 92.72 \text{ V}$

Full-load secondary voltage referred to primary,

$$V_2' = \frac{V_2}{K} = \frac{220}{\frac{1}{20}} = 4400 \text{ V}$$

To get full-load secondary voltage equal to 220 V, supply voltage V_1 must be equal to the vector sum of 4400 V, $I_1 R_{01}$ and $I_1 X_{01}$.

From Fig. 54,

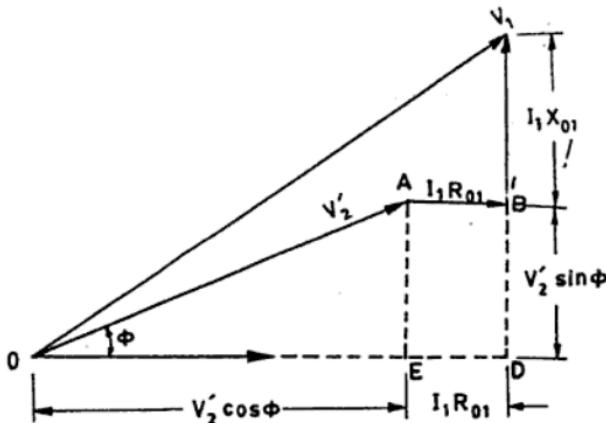


Fig. 54

$$\begin{aligned}OC^2 &= OD^2 + CD^2 = (OE + ED)^2 + (BD + BC)^2 \\V_1^2 &= (V_2' \cos \phi + I_1 R_{01})^2 + (V_2' \sin \phi + I_1 X_{01})^2 \\&= (4400 \times 0.8 + 46.36)^2 + (4400 \times 0.6 + 92.72)^2 \\V_1 &= 4493 \text{ V}\end{aligned}$$

or

Voltage to be applied to h.v. winding to get a full-load secondary voltage of 220 V
= 4493 V. (Ans.)

$$(ii) \% \text{ regulation} = \frac{V_1 - V_2'}{V_1} \times 100 = \frac{4493 - 4400}{4493} \times 100 = 2.07\%. \text{ (Ans.)}$$

Example 40. The high voltage and low voltage windings of a 50 kVA, 4400/220 V, 50-Hz transformer have resistances of 2.2Ω and 0.005Ω respectively. The full-load current is obtained when 160 V is applied to h.v. winding with l.v. winding short-circuited. Find :

- (i) The equivalent resistance and reactance of the transformer referred to h.v. side, and
- (ii) Reactance of each winding.

Assume that the ratio of resistance to reactance is the same for each winding and the full-load efficiency of transformer is 0.98.

$$\text{Solution. (i) Transformation ratio, } K = \frac{220}{4400} = \frac{1}{20}$$

$$\text{Primary resistance, } R_1 = 22 \Omega$$

$$\text{Secondary resistance, } R_2 = 0.005 \Omega$$

$$\text{Full-load output} = 50 \text{ kVA} = 50 \times 10^3 \text{ VA}$$

$$\text{Full-load input} = \frac{\text{output}}{\text{efficiency}} = \frac{50 \times 10^3}{0.98} \text{ VA}$$

$$\text{Full-load input current, } I_1 = \frac{\text{input in VA}}{\text{supply voltage}} = \frac{50 \times 10^3}{0.98 \times 4400} = 11.6 \text{ A}$$

Impedance referred to h.v. side

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{160}{11.6} = 13.8 \Omega$$

Total resistance referred to h.v. side,

$$R_{01} = R_1 + R_2' = R_1 + \frac{R_2}{K^2} = 2.2 + \frac{0.005}{\left(\frac{1}{20}\right)^2} = 2.2 + 2 = 4.2 \Omega. \quad (\text{Ans.})$$

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{(13.8)^2 - (4.2)^2} = 13.15 \Omega. \quad (\text{Ans.})$$

(ii) Since the ratio of resistance to reactance remains same (given),

$$\therefore \frac{R_1}{X_1} = \frac{R_2}{X_2} = \frac{R_2'}{X_2'}$$

$$\text{i.e., } \frac{R_1}{R_2'} = \frac{X_1}{X_2'}$$

$$\text{or } \frac{R_1 + R_2'}{R_2'} = \frac{X_1 + X_2'}{X_2'} \quad \text{or} \quad \frac{R_{01}}{R_2'} = \frac{X_{01}}{X_2'}$$

$$\text{or } X_2' = \frac{R_2' X_{01}}{R_{01}} = \frac{2 \times 13.15}{4.2} = 6.26 \Omega$$

Reactance of primary winding,

$$X_1 = X_{02} - X_2' = 13.15 - 6.26 = 6.85 \Omega. \quad (\text{Ans.})$$

Reactance of secondary winding,

$$X_2 = K^2 X_2' = \left(\frac{1}{20}\right)^2 \times 6.26 = 0.01565 \Omega. \quad (\text{Ans.})$$

Example 41. The following test results were obtained in a 250/500 V transformer :

O.C. test (l.v. side) : 250 V, 1 A, 80 W.

S.C. test (l.v. winding short-circuited) : 20 V, 12 A, 100 W.

Determine :

(i) The circuit constants.

(ii) The applied voltage and efficiency when the output is 10 A at 500 V and 0.8 power factor lagging.

Solution. Transformation ratio, $K = \frac{500}{250} = 2$

(i) Circuit constants :

O.C. test (l.v. side)

Voltage, $V_1 = 250 \text{ V}$

No-load current, $I_0 = 1 \text{ A}$

No-load loss, $P_0 = 80 \text{ W}$

Also, $P_0 = V_1 I_0 \cos \phi_0$

$$80 = 250 \times 1 \times \cos \phi_0$$

$$\cos \phi_0 = \frac{80}{250} = 0.32$$

Wattful component of no-load current I_0 ,

$$I_w = I_0 \cos \phi_0 = 1 \times 0.32 = 0.32 \text{ A}$$

Magnetising component of no-load current, I_0 ,

$$I_m = \sqrt{I_0^2 - I_w^2} = \sqrt{1^2 - 0.32^2} = 0.95 \text{ A}$$

Now, resistance representing the core loss,

$$R_0 = \frac{V_1}{I_w} = \frac{250}{0.32} = 781.25 \Omega. \quad (\text{Ans.})$$

$$\text{Magnetising reactance, } X_0 = \frac{V_1}{I_m} = \frac{250}{0.95} = 263.16 \Omega. \quad (\text{Ans.})$$

S.C. test (L.v. winding short-circuited)

$$\text{Short-circuit voltage, } V_{SC} = 20 \text{ V}$$

$$\text{Short-circuit current, } I_{SC} = 12 \text{ A}$$

$$\text{Losses, } P_{SC} = 100 \text{ W}$$

As the primary is short-circuited all values refer to secondary winding.

$$\therefore R_{02} = \frac{P_{SC}}{I_{SC}^2} = \frac{100}{(12)^2} = 0.694 \Omega$$

$$Z_{02} = \frac{V_{SC}}{I_{SC}} = \frac{20}{12} = 1.677 \Omega$$

$$\text{and } X_{02} = \sqrt{Z_{02}^2 - R_{02}^2} = \sqrt{(1.667)^2 - (0.694)^2} = 1.516 \Omega$$

As R_0 and X_0 refer to primary, let us transfer these values to primary as follows :

$$R_{01} = \frac{R_{02}}{K^2} = \frac{0.694}{(2)^2} = 0.174 \Omega$$

$$X_{01} = \frac{X_{02}}{K^2} = \frac{1.516}{(2)^2} = 0.38 \Omega$$

$$Z_{01} = \frac{Z_{02}}{K^2} = \frac{1.669}{(2)^2} = 0.417 \Omega$$

The equivalent circuit is shown in Fig. 55.

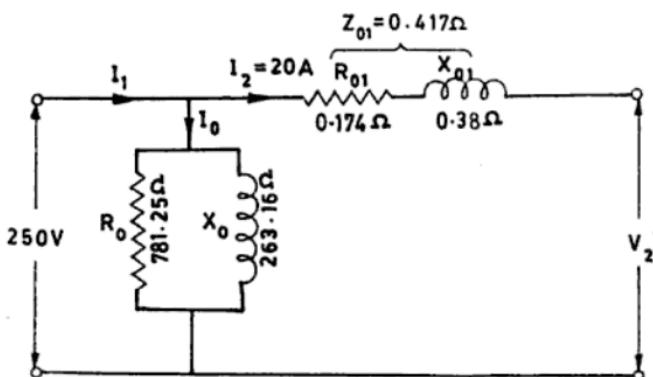


Fig. 55

(ii) Applied voltage, V_1' :

The applied voltage V_1' is the vector sum of V_1 and $I_1 Z_{01}$ (Fig. 56).

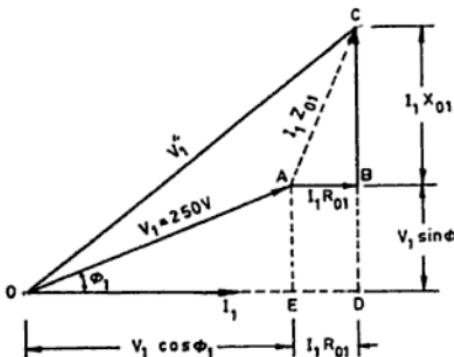


Fig. 56

$$\text{Output current, } I_2 = 10 \text{ A}$$

$$\therefore I_1 = KI_2 = 2 \times 10 = 20 \text{ A}$$

$$\text{Now, } I_1 R_{01} = 20 \times 0.174 = 3.48 \text{ V}$$

$$I_1 X_{01} = 20 \times 0.38 = 7.6 \text{ V}$$

Refer Fig. 56. Neglecting the angle between V_1 and V_1' , we have

$$OC^2 = OD^2 + DC^2$$

$$OC = V_1' = \sqrt{(OE + ED)^2 + (DB + BC)^2}$$

$$= \sqrt{(V_1 \cos \phi_1 + I_1 R_{01})^2 + (V_1 \sin \phi_1 + I_1 X_{01})^2}$$

$$= \sqrt{(250 \times 0.8 + 3.48)^2 + (250 \times 0.6 + 7.6)^2} = 257.4 \text{ V}$$

Hence, applied voltage = 257.4 V. (Ans.)

Efficiency :

$$\text{Iron loss, } P_i = 80 \text{ W}$$

$$\text{Total copper loss, } P_c = I_2^2 R_{02} = 10^2 \times 0.694 = 69.4 \text{ W}$$

$$\text{Total loss, } = P_i + P_c = 80 + 69.4 = 149.4 \text{ W}$$

$$\text{Output } = 500 \times 10 \times 0.8 = 4000 \text{ W}$$

$$\therefore \text{Efficiency, } \eta = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{4000}{4000 + 149.4} = 0.964 \text{ or } 96.4\%. \text{ (Ans.)}$$

Example 42. A 25-kVA, 2200/220 V, 50-Hz distribution transformer is tested for efficiency and regulation as follows :

O.C. test (l.v. side) : 220 V, 4 A, 150 W.

S.C. test (h.v. side) : 90 V, 10 A, 350 W.

Determine :

(i) Core loss,

(ii) Equivalent resistance referred to primary.

- (iii) Equivalent reactance referred to secondary,
- (iv) Equivalent reactance referred to primary,
- (v) Equivalent reactance referred to secondary,
- (vi) Regulation of transformer at 0.8 power factor lagging current, and
- (vii) Efficiency at full-load and half-load at 0.8 power factor lagging current.

Solution. Transformation ratio, $K = \frac{220}{2200} = \frac{1}{10}$

(i) **Core loss :**

Since no-load primary input is practically equal to the core loss, hence, core loss as found from no-load test, is 150 W. (Ans.)

(ii) **From S.C. test :**

$$V_{SC} = 90 \text{ V (short-circuit voltage)}$$

$$I_{SC} = 10 \text{ A (short-circuit current)}$$

$$P_{SC} = 350 \text{ W (copper loss)}$$

∴ **Equivalent resistance referred to primary,**

$$R_{01} = \frac{P_{SC}}{I_{SC}^2} = \frac{350}{(10)^2} = 3.5 \Omega. \quad (\text{Ans.})$$

(iii) **Equivalent resistance referred to secondary,**

$$R_{02} = K^2 R_{01} = \left(\frac{1}{10}\right)^2 \times 3.5 = 0.035 \Omega. \quad (\text{Ans.})$$

(iv) Also $Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{90}{10} = 9 \Omega$

∴ **Equivalent reactance referred to primary,**

$$X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{9^2 - 3.5^2} = 8.29 \Omega. \quad (\text{Ans.})$$

(v) **Equivalent reactance referred to secondary,**

$$X_{02} = K^2 X_{01} = \left(\frac{1}{10}\right)^2 \times 8.29 = 0.0829 \Omega. \quad (\text{Ans.})$$

(vi) **% regulation :**

Let us find the rise in voltage necessary to maintain the output terminal voltage constant from no-load to full-load.

$$\text{Rated primary current} = \frac{25 \times 1000}{2200} = 11.36 \text{ A}$$

Now, using the relation,

$$\begin{aligned} V_1' &= \sqrt{(V_1 \cos \phi + I_1 R_0)^2 + (V_1 \sin \phi + I_1 X_{01})^2} \\ &= \sqrt{(2200 \times 0.8 + 11.36 \times 3.5)^2 + (2200 \times 0.6 + 11.36 \times 8.29)^2} \\ &= 2289 \text{ V (app.)} \\ \therefore \% \text{ regulation} &= \frac{V_1' - V_1}{V_1} \times 100 \quad (\text{Art. 9.11}) \\ &= \frac{2289 - 2200}{2200} \times 100 = 4.045\%. \quad (\text{Ans.}) \end{aligned}$$

We can get the same result by working in the secondary :
Rated secondary current,

$$\begin{aligned} I_2 &= \frac{I_1}{K} = \frac{11.36}{1/10} = 113.6 \text{ A} \\ 0V_2 &= \sqrt{(V_2 \cos \phi + I_2 R_{02})^2 + (V_2 \sin \phi + I_2 X_{02})^2} \\ &= \sqrt{(220 \times 0.8 + 113.6 \times 0.035)^2 + (220 \times 0.6 + 113.6 \times 0.0829)^2} \\ &= 228.9 \text{ V} \\ \therefore \% \text{ regulation} &= \frac{0V_2 - V_2}{V_2} \times 100 = \frac{228.9 - 220}{220} \times 100 = 4.045\%. \quad (\text{Ans.}) \end{aligned}$$

(vii) Efficiency :

Core loss, $P_i = 150 \text{ W}$

Copper loss at full-load,

$$P_c = I_1^2 R_{01} = 11.36^2 \times 3.5 = 451.7 \text{ W}$$

Copper loss at half-load,

$$P_c = \left(\frac{11.36}{2} \right)^2 \times 3.5 = 112.9 \text{ W}$$

\therefore Efficiency at full-load

$$\begin{aligned} &= \frac{\text{output}}{\text{output} + P_i + P_c} = \frac{25 \times 1000 \times 0.8}{(25 \times 1000 \times 0.8) + 150 + 451.7} \\ &= 0.9707 \text{ or } 97.07\%. \quad (\text{Ans.}) \end{aligned}$$

Efficiency at half full-load

$$= \frac{(25 \times 1000/2) \times 0.8}{(25 \times 1000/2) \times 0.8 + 150 + 112.9} = 0.9744 \text{ or } 97.44\%. \quad (\text{Ans.})$$

Example 43. Two similar 100 kVA, single-phase transformers gave the following test readings when tested by Sumpner's test.

Supply power = 2.4 kW.

Power supplied to secondary circuit in passing full-load current through it = 3.2 kW.

Find the efficiency and regulation of each transformer at unity power factor.

Solution. Core loss (or iron loss) of the transformers

$$= 2.4 \text{ kW}$$

Iron loss of each transformer,

$$P_i = \frac{2.4}{2} = 1.2 \text{ kW}$$

Full-load copper loss of both transformers

$$= 3.2 \text{ kW}$$

Full-load copper loss of each transformer

$$P_c = \frac{3.2}{2} = 1.6 \text{ kW}$$

Total full-load losses of each transformer

$$= P_i + P_c = 1.2 + 1.6 = 2.8 \text{ kW}$$

Output at full-load at unity power factor

$$= 100 \times 1 = 100 \text{ kW}$$

\therefore Full-load efficiency, $\eta = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{100}{100 + 2.8} = 0.9727$ or 97.27%. (Ans.)

Example 44. A 10 kVA, 2500/250 V, single phase transformer gave the following test results :

Open circuit test : 250 V, 0.8 A, 50 W

Short circuit test : 60 V, 3 A, 45 W

(i) Calculate the efficiency of half full-load at 0.8 p.f.

(ii) Calculate the load kVA at which maximum efficiency occurs and also the maximum efficiency at 0.8 p.f.

(iii) Compute the voltage regulation at 0.8 p.f. leading.

(AMIE Winter, 1998)

Solution. Full rated current = $\frac{10 \times 1000}{2500} = 4$ A

Hence reading of wattmeter corresponding to full-load current of 4 A

$$= 45 \times \left(\frac{4}{3} \right)^2 = 80 \text{ W}$$

\therefore Full-load copper losses = 80 W, and

Full-load iron losses = 50 W

(i) Efficiency at half-load at 0.8 p.f. :

$$\begin{aligned}\eta &= \frac{\text{half-load output}}{\text{half-load output} + \text{losses}} \\ &= \frac{(10 \times 1000 \times 0.5) \times 0.8}{[(10 \times 1000 \times 0.5) \times 0.8] + 50 + 80 \times \left(\frac{1}{2}\right)^2} \\ &= \frac{4000}{4000 + 50 + 20} = 0.983 \text{ or } 98.3\%. \text{ (Ans.)}\end{aligned}$$

(ii) Load kVA for maximum efficiency, and its value :

For maximum efficiency :

Copper loss = Iron loss = 50 W

\therefore Current at which maximum efficiency occurs = $\frac{50 \times 4}{80} = 2.5$ A

\therefore Load kVA = $10 \times \frac{2.5}{4} = 6.25$ kVA. (Ans.)

η_{max} (at 0.8 p.f.) = $\frac{(6.25 \times 1000 \times 0.8)}{(6.25 \times 1000 \times 0.8) + 50 + 50} = 0.98$ or 98%. (Ans.)

(iii) Voltage regulation at 0.8 p.f. leading :

From short circuit test :

$$V_{SC} = 60 \text{ V}; I_{SC} = 3 \text{ A}; P_{SC} = 45 \text{ W}$$

$$\text{Now, } R_{01} = \frac{P_{SC}}{I_{SC}^2} = \frac{45}{3^2} = 5 \Omega$$

$$Z_{01} = \frac{V_{SC}}{I_{SC}} = \frac{60}{3} = 20 \Omega$$

$$\therefore X_{01} = \sqrt{Z_{01}^2 - R_{01}^2} = \sqrt{20^2 - 5^2} = 19.36 \Omega$$

∴ Voltage drop at leading p.f. of 0.8

$$\begin{aligned} &= I_1 R_{01} \cos \phi - I_1 X_{01} \sin \phi \\ &= 4 \times 5 \times 0.8 - 4 \times 19.36 \times 0.6 = -30.46 \text{ V} \end{aligned}$$

$$\text{Hence \% voltage regulation} = \frac{-30.46}{2500} \times 100 = -1.218\%. \quad (\text{Ans.})$$

Example 45. A 50 kVA single-phase transformer has a full-load primary current of 250 A and total resistance referred to primary is 0.006 ohm. If the iron loss amounts to 200 W, find the efficiency on full-load and half-load at (i) unity power factor and (ii) 0.8 power factor.

Solution. Full-load primary current,

$$I_1 = 250 \text{ A}$$

Total resistance referred to primary,

$$R_{01} = 0.006 \Omega$$

Iron loss, $P_i = 200 \text{ W}$

Full-load copper loss, $P_c = I_1^2 R_{01} = (250)^2 \times 0.006 = 375 \text{ W}$

Total full-load loss = $P_i + P_c = 200 + 375 = 575 \text{ W} = 0.575 \text{ kW}$

Half full-load copper loss = $\left(\frac{1}{2}\right)^2 P_c = \left(\frac{1}{2}\right)^2 \times 375 = 93.75 \text{ W}$

Total loss on half-load = $200 + 93.75 = 293.75 \text{ W} = 0.294 \text{ kW}$ (say)

(i) At unity power factor :

Full-load output, $= 50 \times 1 = 50 \text{ kW}$

Efficiency at full-load = $\frac{\text{output}}{\text{output} + \text{losses}} = \frac{50}{50 + 0.575} = 0.9886 \text{ or } 98.86\%. \quad (\text{Ans.})$

Half-full-load output $= 50 \times \frac{1}{2} \times 1 = 25 \text{ kW}$

Efficiency at half full-load at unity power factor

$$= \frac{25}{25 + 0.294} = 0.9984 \text{ or } 99.84\%. \quad (\text{Ans.})$$

(ii) At 0.8 power factor :

Full-load output $= 50 \times 0.8 = 40 \text{ kW}$

Efficiency on full-load at 0.8 power factor

$$= \frac{40}{40 + 0.575} = 0.9858 \text{ or } 98.58\%. \quad (\text{Ans.})$$

Half full-load output $= 50 \times \frac{1}{2} \times 0.8 = 20 \text{ kW}$

Efficiency on half full-load at 0.8 power factor

$$= \frac{20}{20 + 0.294} = 0.9855 \text{ or } 98.55\%. \quad (\text{Ans.})$$

Example 46. A 40 kVA, single-phase transformer has an iron loss of 300 W and full-load copper loss of 600 W,

(i) Find the load at which maximum efficiency occurs and the value of maximum efficiency at unity power factor.

(ii) If the maximum efficiency occurs at 80% of full-load, find the new core loss and full-load copper loss assuming that total full-load loss is a constant.

Solution. Rating of transformer = 40 kVA

Iron loss, $P_i = 300 \text{ W}$

Full-load copper loss, $P_c = 600 \text{ W}$

(i) Let the maximum efficiency occurs at x times full-load, then

$$x^2 P_c = P_i$$

or $x = \sqrt{\frac{P_i}{P_c}} = \sqrt{\frac{300}{600}} = 0.707 = 70.7\%$

Hence, efficiency occurs at 70.7% of full-load. (Ans.)

Maximum efficiency :

Output at unity power factor

$$= 0.707 \times 40 \times 1 = 28.28 \text{ kW}$$

Total losses $= P_i + P_c = 2P_i$ [Because when efficiency is maximum, $P_i = P_c$]
 $= 2 \times 300 = 600 \text{ W}$
 $= 0.6 \text{ kW}$

∴ Maximum efficiency

$$= \frac{\text{output}}{\text{output} + \text{losses}} = \frac{28.28}{28.28 + 0.6} = 0.9792 \text{ or } 97.92\%. \text{ (Ans.)}$$

(ii) New core loss, P_i' :

New copper loss, P_c' :

Maximum efficiency occurs at 80% of full-load

Now, $P_i' + P_c' = P_i + P_c$ (given)
 $= 300 + 600 = 900 \text{ W}$

Also $0.8 = \sqrt{\frac{P_i'}{P_c'}}$ or $\frac{P_i'}{P_c'} = [0.8]^2 = 0.64$

or $\frac{P_i'}{P_i' + P_c'} = \frac{0.64}{1 + 0.64} = 0.3902$ or $\frac{P_i'}{900} = 0.3902$

∴ $P_i' = 351.2 \text{ W}$

and $P_c' = 900 - P_i' = 900 - 351.2 = 548.8 \text{ W}$

Hence, new iron loss = 351.2 W. (Ans.)

new copper loss = 548.8 W. (Ans.)

Example 47. The primary and secondary resistances of a 1100/220 V transformer are 0.3Ω and 0.02Ω respectively. If iron loss amounts to 260 W determine the secondary current at which maximum efficiency occurs and find the maximum efficiency at 0.8 power factor.

Solution. Transformation ratio, $K = \frac{220}{1100} = \frac{1}{5}$

Primary resistance, $R_1 = 0.3 \Omega$

Secondary resistance, $R_2 = 0.02 \Omega$

Iron loss, $P_i = 260 \text{ W}$

Total resistance referred to secondary,

$$R_{02} = R_2 + K^2 R_1 = 0.02 + \left(\frac{1}{5} \right)^2 \times 0.3 = 0.032 \Omega \quad (\text{Ans.})$$

Let I_2 be the secondary current at maximum efficiency.

At maximum efficiency,

Copper loss = Iron loss

$$I_2^2 R_{02} = 260$$

∴ $I_2^2 = \frac{260}{R_{02}} = \frac{260}{0.032} = 8125 \text{ or } I_2 = 90.14 \text{ A}$

Hence, secondary current at maximum efficiency
 $= 90.14 \text{ A. (Ans.)}$

Maximum efficiency at 0.8 power factor :

Output at maximum efficiency at 0.8 power factor
 $= V_2 I_2 \cos \phi_2 = 220 \times 90.14 \times 0.8 = 15865 \text{ W}$

Losses
 $= P_i + P_c = 2P_i$
 $= 2 \times 260 = 520 \text{ W}$ $(\because P_i = P_c)$

$\therefore \text{Maximum efficiency} = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{15865}{15865 + 520} = 0.9683 \text{ or } 96.83\%. \text{ (Ans.)}$

9.15. All-day Efficiency. All-day efficiency is the ratio of energy (kWh) delivered in a 24 hour period divided by the energy (kWh) input in the same length of time.

$\therefore \eta_{\text{all-day}} = \frac{\text{output in kWh}}{\text{input in kWh}} \text{ (for 24 hours)} \quad \dots(39)$

Transformers used on residence-lighting circuits (and distribution circuits generally) are either idle or only lightly loaded during much of 24-hour period. However, they must at all times be connected to the line and ready to serve, so that the core losses are being supplied continually. It is therefore very important that such transformers be designed for minimum core loss. The copper losses are relatively less important, since they depend on the load. Because they are lightly loaded much of the time, distribution transformers are designed for relatively large full-load copper loss and have their maximum power efficiencies at light loads. This design results in improved all-day efficiency for these transformers. Power transformers, on the other hand are loaded more or less continuously and are designed for full-load copper losses equal to about twice the no-load losses.

To calculate all-day efficiency, it is necessary to know how the load on the transformer varies from hour to hour. The quotient obtained by dividing the energy output by the energy output plus energy losses over a 24-hour period yields the efficiency expressed as a decimal fraction.

The use of a load factor facilitates practical calculations.

Example 48. A 15 kVA, 2000/200 V transformer has an iron loss of 250 W and full-load copper loss 350 W. During the day it is loaded as follows :

No. of hours	Load	Power factor
9	$\frac{1}{4}$ load	0.6
7	full-load	0.8
6	$\frac{3}{4}$ load	1.0
2	no-load	—

Calculate the all-day efficiency.

Solution. Rating of transformer = 15 kVA

Iron loss, $P_i = 250 \text{ W} = 0.25 \text{ kW}$

Full-load copper loss, $P_c = 350 \text{ W} = 0.35 \text{ kW}$

Iron loss/day $= 0.25 \times 24 = 6 \text{ kWh}$

Copper loss at $\frac{1}{4}$ load $= \left(\frac{1}{4}\right)^2 \times P_c = \frac{1}{16} \times 0.35 = 0.0218 \text{ kW}$

Copper loss for 9 hours at $\frac{1}{4}$ load
 $= 9 \times 0.0218 = 0.196 \text{ kWh}$

Copper loss at full-load $= P_c = 0.35 \text{ kW}$

Copper loss for 7 hours on full-load

$$= 7 \times 0.35 = 2.45 \text{ kWh}$$

Copper loss at $\frac{3}{4}$ load

$$= \left(\frac{3}{4} \right)^2 \times P_c = \frac{9}{16} \times 0.35 = 0.197 \text{ kW}$$

Copper loss for 6 hours at $\frac{3}{4}$ load = $0.197 \times 6 = 1.18 \text{ kWh}$

Copper loss/day

$$= 0.196 + 2.45 + 1.18 = 3.826 \text{ kWh}$$

Total loss/day

$$= \text{iron loss/day} + \text{copper loss/day} = 6 + 3.826 = 9.826 \text{ kWh}$$

Total output/day

$$= \frac{1}{4} \times 15 \times 0.6 \times 9 + 15 \times 0.8 \times 7 + \frac{3}{4} \times 15 \times 1.0 \times 6$$

$$= 20.25 + 84 + 67.5 = 171.75 \text{ kWh}$$

All-day efficiency

$$= \frac{\text{output}}{\text{output} + \text{losses}} = \frac{171.75}{171.75 + 9.826} = 0.9459 \text{ or } 94.59\%. \quad (\text{Ans.})$$

9.16. Transformer Noise. The "hum" caused by energized power transformer, under *no-load conditions*, originates in the *core where the laminations tend to vibrate by magnetic forces*. The noise is transmitted through the oil to the tank side and thence to the surroundings.

The following are the *main factors which produce noise in transformers* :

1. *Magnetostriction* (occurrence of dimensional changes both parallel to, and perpendicular to the direction of magnetisation).
2. The mechanical vibrations caused by the laminations, depending upon the tightness of clamping, size, gauge, associated structural parts, etc.
3. The mechanical vibration of tank walls.
4. The damping.

The noise emission may be reduced by the following methods/means :

1. Prevention of vibration of core-plate by the use of a lower flux density and giving attention to constructional feature (such as clamping bolts, proportions and dimensions of the 'steps' in plate width, tightness of clamping and uniformity of plates).
2. Using cushions, padding, or oil barriers to sound insulate the transformer from tank.
3. Designing suitably the tank and stiffeners to check tank wall vibration.
4. Sound insulating the tank from the ground or surrounding air.

However, the *noise problem cannot be solved completely*.

9.17. Auto-transformer. A transformer in which part of the winding is common to both the primary and secondary circuits is known as an **auto-transformer**. The primary is electrically connected to the secondary, as well as magnetically coupled to it.

Refer Fig. 57. LM is primary winding having N_1 turns and MS is secondary winding having N_2 turns. If no-load current and iron losses are neglected.

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = K.$$

The current in the section MS is vector difference of I_2 and I_1 ; but since the two currents are practically in phase opposition, the resultant is $(I_2 - I_1)$ where $I_2 > I_1$.

Saving of copper (in comparison to conventional two winding transformer) :

The volume and hence weight of copper is proportional to the length and area of cross-section of the conductors. But the *length of conductor is proportional to the number of turns and cross-section depends on current*. Hence the weight of copper is proportional to the *product of number of turns and current to be carried*.

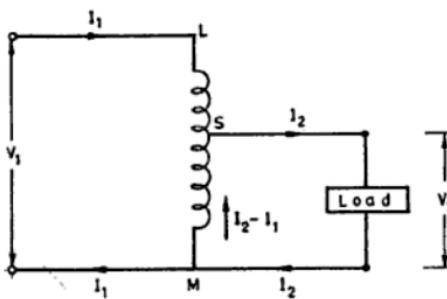


Fig. 56A. Auto-transformer.

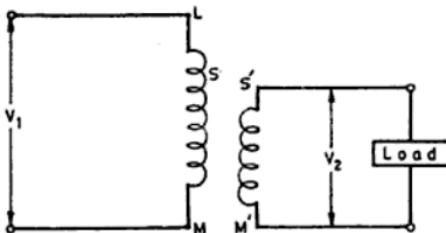


Fig. 57. Conventional two winding transformer.

Weight of copper in conventional two winding transformer

$$\propto (N_1 I_1 + N_2 I_2).$$

Weight of copper in auto-transformer

$$= \text{weight of copper in section } LS + \text{weight of copper in section } MS.$$

But weight of copper in section $LS \propto (N_1 - N_2) I_1$

and weight of copper in section $MS \propto N_2 (I_2 - I_1)$

\therefore Weight of copper in auto-transformer

$$\propto (N_1 - N_2) I_1 + N_2 (I_2 - I_1)$$

\therefore Weight of copper in auto-transformer (W_a)

\therefore Weight of copper in ordinary transformer (W_0)

$$= \frac{(N_1 - N_2) I_1 + N_2 (I_2 - I_1)}{N_1 I_1 + N_2 I_2} = \frac{(N_1 - 2N_2) I_1 + N_2 I_2}{N_1 I_1 + N_2 I_2}$$

$$= \frac{\frac{N_1}{N_2} - 2 + \frac{I_2}{I_1}}{\frac{N_1}{N_2} + \frac{I_2}{I_1}} = \frac{\frac{1}{K} - 2 + \frac{1}{K}}{\frac{1}{K} + \frac{1}{K}}$$

$$= 1 - K$$

$$\dots(40) \quad \left[\because \frac{N_2}{N_1} = K, \frac{I_2}{I_1} = \frac{1}{K} \right]$$

\therefore Saving in copper $= W_0 - W_a = W_0 - (1 - K) W_0 = KW_0$

\therefore Saving in copper $= K \times \text{weight of copper in ordinary transformer}$

It can be proved that power transformed = input $(1 - K)$

The rest of the power is conducted directly from the source to the load.

Advantages of auto-transformer. An auto-transformer entails the following advantages :

- Higher efficiency
- Small size
- Lower cost
- Better voltage regulation when compared with a conventional two-winding transformer of the same rating.

Disadvantages. Following are the disadvantages/limitations of auto-transformers :

(i) The primary and secondary are conductively connected, rather than isolated as in the conventional (ordinary) transformer. Because of this, both sides are subject to any stresses set up by disturbances on either side. The low-voltage side is subject to high-voltage stress and should be insulated for the higher voltage. In the case of a step down transformer, the high voltage may still be impressed upon equipment connected to the low-voltage side. This is shown in Fig. 58 where the low-voltage coil has accidentally opened. The voltage on the load is nearly 2300 V, being less than that by the impedance volt drop in the primary coil.

(ii) As the voltage ratio of an auto-transformer increases, the common coil is much smaller compared with the entire winding. This means that the economy gained is only a small part of the transformer and therefore this advantage is minimized.

Thus, because of the above disadvantages, lack of isolation and decreased economy, auto-transformers are rarely used in ratios greater than 4 : 1, except for low-power devices on low-voltage systems.

Uses. The auto-transformers find the following applications :

- To tie together transmission or distribution circuits of slightly different voltages (e.g. 11000 V system with a 13200 V system).
- To obtain partial line voltages for starting induction and synchronous motors with squirrel-cage windings.
- To give a small boost to a distribution cable to correct for the voltage drop.
- As furnace transformers for getting a convenient supply to suit the furnace winding from a 230 V supply.
- As regulating transformers.
- To obtain a neutral in a 3-wire A.C. distribution system in the same way as a balancer set is used in a 3-wire D.C. distribution system.
- A continuously variable auto-transformer finds useful applications in electrical testing laboratory.

9.18. Polarity of Transformers. In a transformer each of the primary terminals becomes alternately positive and negative with respect to the other and the same is true about the secondary terminals. If the transformer is to be used alone, the polarity is not important but if the transformer is to be used in parallel with another transformer the instantaneous polarity is important because the terminals having identical instantaneous polarity have to be connected together.

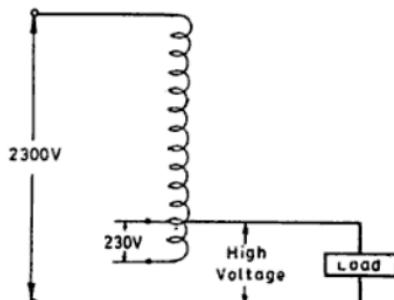


Fig. 58. Open circuit on auto-transformer.

Refer Figs. 59 and 60. The terminals of the high voltage (h.v.) winding (*i.e.* H_1 and H_2) and the terminals of the low voltage (l.v.) winding (*i.e.* X_1 and X_2) are so marked that when the instantaneous voltage is directed from H_1 to H_2 in the high voltage winding, it is directed from X_1 to X_2 in the low voltage winding. In other words if the high voltage terminal H_1 is positive with respect to H_2 at any instant when the low voltage terminal X_1 will be positive with respect to X_2 at the same instant. It follows that when the terminals are arranged as in Fig. 59 the polarity is subtractive whereas the additive polarity is represented as in Fig. 60.

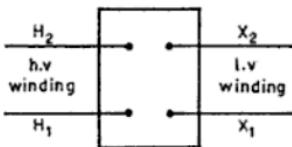


Fig. 59. Subtractive polarity.

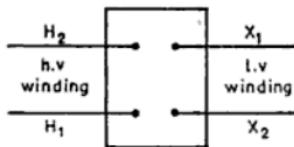


Fig. 60. Additive polarity.

Polarity Test. A polarity test is carried out to find out the terminals having the same instantaneous polarity assuming that the terminals are not marked. The connections are shown in Fig. 61.

- One h.t. and one l.t. terminals are joined together. A voltmeter is placed between the remaining two terminals.
- A convenient moderate voltage is impressed on the h.t. winding.

If the voltage V' , is 'greater' than the applied voltage V , then the transformer has 'additive' polarity.

If V' is 'less' than V , the transformer has 'subtractive' polarity.

The terminals are then marked accordingly.

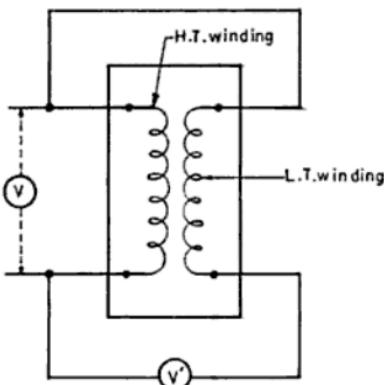


Fig. 61. Polarity test.

Example 49. A load of 6 kW is supplied by an auto-transformer at 120 V and at unity power factor. If the primary voltage is 240 V, determine :

- (i) Transformation ratio,
- (ii) Secondary current,
- (iii) Primary current,
- (iv) Number of turns across secondary if the total number of turns is 280.
- (v) Power transformed, and
- (vi) Power conducted directly from supply mains to load.

Solution. Load supplied = 6 kW

Output voltage, $V_2 = 120$ V

Primary voltage, $V_1 = 240$ V

Total number of turns, $N_1 = 280$

$$(i) \text{ Transformation ratio, } K = \frac{V_2}{V_1} = \frac{120}{240} = \frac{1}{2}. \quad (\text{Ans.})$$

$$(ii) \text{ Secondary current, } I_2 = \frac{6 \times 1000}{V_2 \cos \phi} = \frac{6000}{120 \times 1} = 50 \text{ A.} \quad (\text{Ans.})$$

$$(iii) \text{ Primary current, } I_1 = KI_2 = \frac{1}{2} \times 50 = 25 \text{ A. (Ans.)}$$

$$(iv) \text{ Turns across secondary, } N_2 = kN_1 = \frac{1}{2} \times 280 = 140. \text{ (Ans.)}$$

$$(v) \text{ Power transformed } = \text{Load} \times (1 - K) = 6 \times (1 - \frac{1}{2}) = 3 \text{ kW. (Ans.)}$$

$$(vi) \text{ Power conducted directly from supply mains } \\ = 6 - 3 = 3 \text{ kW. (Ans.)}$$

Example 50. The primary and secondary voltages of an auto-transformer are 600 V and 500 V respectively. Show with the aid of a diagram the current distribution in the windings when the secondary current is 210 A. Calculate the economy in copper.

Solution. Primary voltage, $V_1 = 600 \text{ V}$

Secondary voltage, $V_2 = 500 \text{ V}$

Secondary current, $I_2 = 210 \text{ A}$

Economy in copper :

$$\text{Transformation ratio, } \frac{V_2}{V_1} = \frac{500}{600} = \frac{5}{6}$$

$$\text{Primary current, } I_1 = KI_2 = \frac{5}{6} \times 210 = 175 \text{ A}$$

The current distribution is shown in Fig. 62.

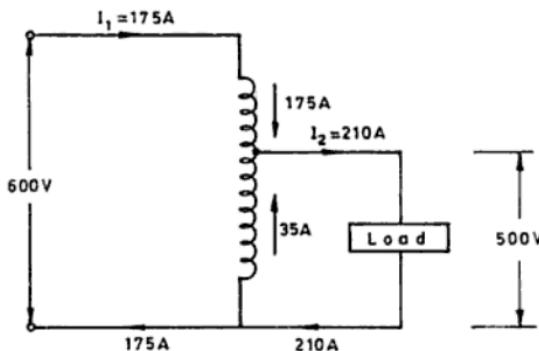


Fig. 62

We know that,

$$\frac{\text{Weight of copper on auto-transformer}}{\text{Weight of copper on ordinary transformer}} = 1 - K$$

Economy in copper

$$= \frac{\text{wt. of Cu on ordinary transformer} - \text{wt. of Cu on auto-transformer}}{\text{wt. of Cu on ordinary transformer}}$$

$$= 1 - \frac{\text{wt. of Cu on auto-transformer}}{\text{wt. of Cu on ordinary transformer}}$$

$$= 1 - (1 - K) = K = \frac{5}{6} \text{ or } 83.33\%. \text{ (Ans.)}$$

Example 51. A 4-kVA single-phase 50-Hz transformer has a full-load efficiency of 95.5% and iron loss of 45 W. The transformer is now connected as an auto-transformer to 220 V supply. If it delivers 4 kW load at unity power factor to a 110 V circuit, calculate the efficiency of the operation and the current drawn by the high-voltage side.

Solution. Fig. 63 shows the connections for a 2-winding transformer. In Fig. 64 the same unit has been connected as an auto-transformer to a 220 V supply. Since the two-windings are connected in series, hence voltage across each is 110 V.

In both connections the iron loss would remain the same. Since the auto-transformer windings will each carry but half the current as the conventional two-winding transformer, the copper losses will be $\frac{1}{4}$ th of previous value.

Two-winding transformer :

$$\text{Efficiency} = 95.5\% \text{ or } 0.955$$

$$\therefore 0.955 = \frac{\text{output}}{\text{output} + \text{losses}} = \frac{4000}{4000 + 45 + \text{copper loss}}$$

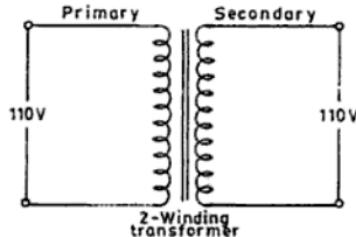


Fig. 63. Two-winding transformer.

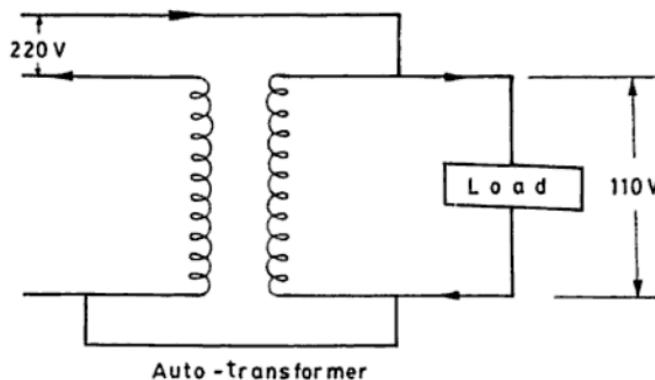


Fig. 64. Auto-transformer.

$$\therefore \text{Copper loss} = \frac{4000}{0.955} - (4000 + 45) = 143.48 \text{ W}$$

Auto-transformer :

$$\text{Copper loss} = \frac{143.48}{4} = 35.87 \text{ W}$$

$$\text{Iron loss} = 45 \text{ W}$$

$$\therefore \text{Efficiency} = \frac{4000}{4000 + 35.87 + 45} = 0.9802 \text{ or } 98.02\%. \text{ (Ans.)}$$

10. THREE PHASE TRANSFORMER

10.1. Three-phase Transformer Connections. Virtually all power distribution is by poly-phase system of voltages. Three-phase transformations may be made with the use of properly connected single-phase transformers. These connections are in extensive commercial use. The most frequently used connections are the following :

- (i) Primary Y—secondary Y.
- (ii) Primary Δ —secondary Δ .
- (iii) Primary Δ —secondary Y, or vice versa.
- (iv) Primary and secondary open Δ .
- (v) Primary T secondary T (Scott connection).

Thus the most common connections are Y-Y, Δ - Δ , Y- Δ , Δ -Y, open delta or V-V and Scott connection or T-T connection.

10.1.1. The Y-Y connection. Fig. 65 shows a bank of three transformers connected in Y on both the primary and secondary sides. If the ratio of transformation of each transformer is K , the same ratio will exist between the line voltages on the primary and secondary sides. This connection will give satisfactory service only if the three-phase load is balanced ; when the load is unbalanced, the electrical neutral will shift from its exact centre to a point that will make the line-to-neutral voltages unequal.

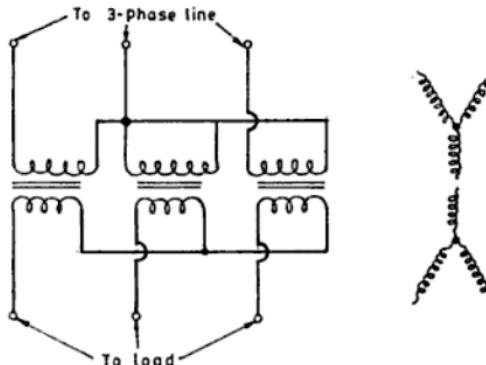


Fig. 65. The Y-Y connection of transformers.

Advantages :

1. This type of connection requires fewer turns per winding since the voltage across each is $\frac{1}{\sqrt{3}}$ times the line voltage ; hence it is *cheaper*.
2. The phase or winding current being equal to the line current, the cross-section of the winding wire is large, therefore the winding is stronger to bear stresses imposed upon it during heavy load or short circuit.
3. There is less dielectric stress on the insulating materials owing to lesser voltage i.e. $\frac{1}{\sqrt{3}}$ of line voltage.

The above advantages are enumerated with the understanding that, other things being equal, its rival is the delta-delta connection.

Disadvantages :

1. In case the load on the secondary side is unbalanced, as in the case of distributing network, the potential of the star-point will assume any value if the star-point is not earthed. This may impose full-line voltage on secondary windings. The shifting of the neutral point must be prevented by connecting the primary star-point to the star-point of the alternator winding.
2. In spite of grounding the star-point, if there is a third harmonic in the form of the alternator voltage, the third harmonic will appear in the voltages of the secondary side. This will cause triple frequency currents in the three-phase circuits. These currents when they flow in the neutral wire are additive and do not cancel out. Hence they will cause interference to telephone lines located along the same route.
3. The magnetising current in a transformer has third harmonic components. These currents will find a return path via the connection between the primary star-point of transformer and the neutral point of the alternator. However, if this connection is missing, these components will distort the flux wave which will produce a voltage having a third harmonic in each of the transformer, both on the primary and secondary sides. And, as before, if the star-point on the secondary is earthed, or grounded, triple harmonic currents will appear in the secondary circuit, and they will flow through the neutral wire causing interference to telephone lines in the vicinity.
4. If the star-points of both the primary and the secondary sides are not earthed, the regulation of the phases will be very poor if the load happen to be unbalanced as the case of distribution network.

10.1.2. The Δ - Δ connection. Fig. 66 shows a bank of transformers connected in Δ on both the primary and secondary sides. *This arrangement is generally used in systems in which the voltages are not very high and especially when continuity of service must be maintained even though one of the transformers should fail.*

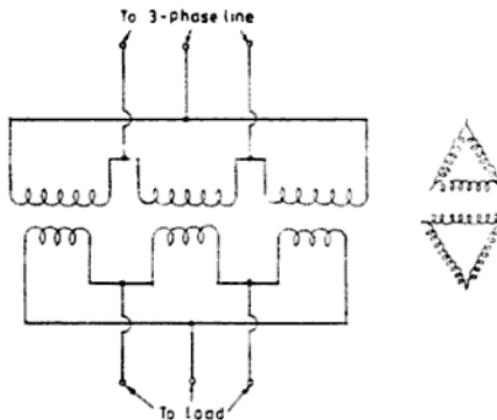


Fig. 66. The Δ - Δ connection of transformers.

Advantages :

1. The system voltages are more stable in relation to an unbalanced load.
2. If one transformer fails it may be switched out of the line and operation continued at a reduced power level. This is known as open-delta or V-V operation.
3. There is no distortion of flux, because the third harmonic component of magnetising current can flow in the delta connected primary windings without flowing in the line wires.
4. No difficulty is experienced due to unbalancing of loads on secondary side.

Disadvantages :

1. In comparison to Y-Y connections it requires more insulation.
2. The absence of star-point may be disadvantageous. If one line gets earthed due to fault, maximum voltage between windings and core will be full line voltage.

10.1.3. The Y-Δ connection. The Y-Δ connection is shown in Fig. 67.

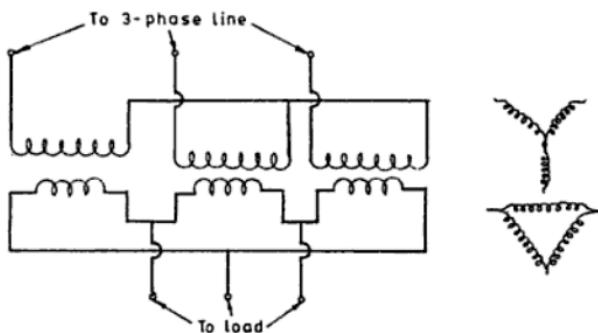


Fig. 67. The Y-Δ connection.

It is principally used where the voltage is to be stepped down, as for example, at the end of a transmission line. It is also employed in moderately low-voltage distribution circuits for stepping down from transmission voltages of 4000 or 8000 V to 230 (and 115) V.

- The Y connection takes advantage of the fact that one leg of a Y, or the line-to-neutral voltage, is less than the line-to-line voltage by a $\sqrt{3}$ factor. This is especially important when the primary voltage is a few hundred thousand volts.
- The Y-Δ does have a phase shift between the primary and secondary voltages. This 30° phase shift means that a Y-Δ transformer bank *cannot* be paralleled with either a Y-Y or a Δ-Δ. The phasor voltage differences between the two systems would be around $\sin 30^\circ = 0.5$ times the secondary voltages. This would cause an excessive circulating current between transformer banks.

10.1.4. The Δ-Y connection

- The three-phase Δ-Y connections are shown in Fig. 68.

This type of connection is employed where it is necessary to *step up* the voltage, as for example, at the beginning of a high-tension transmission system.

- The ratio of secondary to primary voltage is $\sqrt{3}$ times the transformation ratio of each transformer.
- The neutral of the secondary is grounded for providing 3-phase 4-wire service. This connection is popular since it can be used to serve both the 3-phase power equipment and single-phase lighting circuit.
- This connection is not open to the objection of a floating neutral and voltage distortion because the existence of a Δ-connection allows a path for the third-harmonic currents. It would be observed that the primary and secondary line voltages and line currents are out of phase with each other by 30° . Because of this 30° shift, it is impossible to parallel such

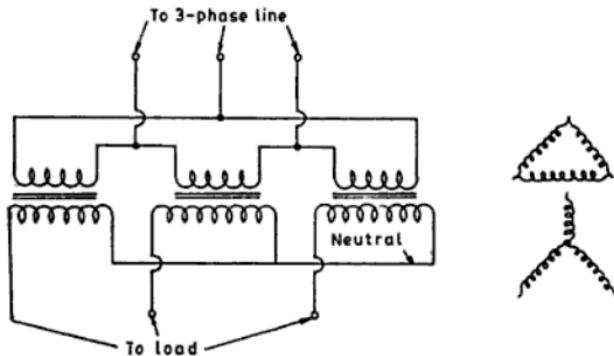


Fig. 68. The Δ -Y connection of transformers.

a bank with a Δ - Δ or Y-Y bank of transformers even though the voltage ratio are correctly adjusted.

10.1.5. The V-V (open- Δ) connections. Fig. 69 shows the V-V connection.

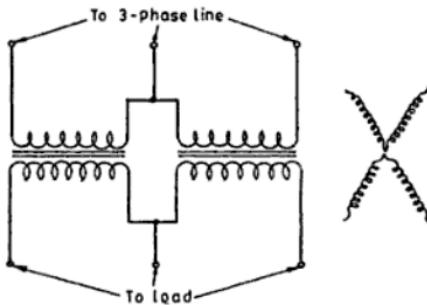


Fig. 69. The V-V (open Δ) connection of transformers.

If one of the transformers of a Δ - Δ bank is removed and a three-phase source is connected to the primaries (as shown in Fig. 66), three equal three-phase voltages will be measured at the secondary terminals at no-load. This method of transforming three-phase power, using two transformers, is called the open-delta, or V-V connection.

This type of connection is used in the following cases :

- (i) When the three-phase load is comparatively small so that the installing does not warrant a three transformer bank.
- (ii) When one of the transformers in a Δ - Δ bank fails, so that the service may be continued until the faulty transformer is repaired or a good one is substituted.
- (iii) When it is anticipated that the future load will increase to warrant the choosing of the open Δ at some time later.

V-V connection has a number of features that are *advantageous* :

- Upon failure of the primary or secondary of one transformer of a complete Δ - Δ transformer circuit, the system reverts to a V-V circuit, so this is an *automatic standby*. The power-

handling capacity of a V-V circuit is $\frac{1}{\sqrt{3}}$ times the capacity of a full Δ-Δ of the same transformers. This feature works both ways, so a circuit is sometimes installed as V-V with the understanding that its power handling may be multiplied by $\sqrt{3}$ by adding one more transformer.

- Open delta or V-V circuits do introduce some voltage unbalance due to the non-symmetry of the voltage regulation effects under load. However, the small degree of unbalance is not normally noticed by a motor load or other types of commercial load.

Disadvantages of V-V connection :

1. The secondary terminal voltages tend to become unbalanced to a great extent when the load is increased, this happens even when the load is perfectly balanced.
2. The average factor at which the V-bank operates is less than that of the load. This power factor is actually *86.6 per cent of the balanced load factor*. Another important point to note is that, except, for a balanced unity power factor load, the two transformers in the V-V bank operate at different power factors.

Uses of V-V connection :

- (i) The V-V circuit is frequently used for two *auto-transformers*. Here advantage is taken of power handling of auto-transformers and their superior voltage regulation and efficiency.
- (ii) Another major use of V-V transformer banks is in *A.C. motor starting*.

10.1.6. Scott or T-T connection. The connection of one polyphase system into another polyphase system is possible by suitably connecting the windings of transformers. One of the early types that was used is Scott or *T-T* connection, by which a 2-phase system is available from a 3-phase system or *vice-versa*.

In Fig. 70 two single-phase transformers *M* and *T*, the primaries of which are connected to a 3-phase supply. The secondary of *M* forms one phase and the secondary of *T* the other phase of a true 2-phase system. *M* is called the *main transformer* and *T* is called the *teaser*. One end of the teaser primary is connected to the mid-point of the main primary. The two ends of the main primary are connected to two lines wires of a 3-phase, 3-wire system, and the third line wire is connected to a tapping *X* on the teaser primary.

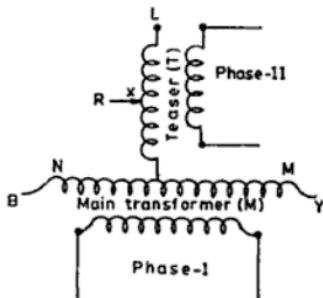


Fig. 70. Scott or *T-T* connection.

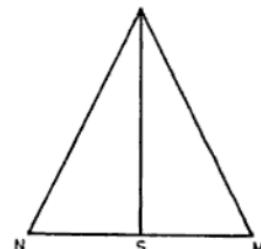


Fig. 71

If the supply voltages are assumed symmetrical, the triangle of voltages is *equilateral* as shown in Fig. 71. The vertical line $LS = \frac{\sqrt{3}}{2} NM$, so that it gives the relationship between the number of turns of two primaries, as

$$\frac{\text{Number of turns for the main transformer } M}{\text{Number of turns for the teaser } T} = \frac{100}{86.6}$$

Hence, if two identical single-phase transformers are to be used for Scott-connection, the primary one must have a tapping point brought out from its *mid-point of the primary*, and the secondary transformer must have a tapping *X* brought out from 86.6% of *its primary turns*.

As the two-phase side is asymmetrical, there cannot be perfect balanced conditions on the three-phase side. However, neglecting the impedance of the windings, it can be shown that if load on the 2-phase side is balanced the 3-phase side is also balanced.

10.2. Three-phase Transformer Construction. The windings of three single-phase transformers can be wound on a common core. The *advantages* are :

1. One 3-phase transformer is *cheaper* than three single-phase transformers.
2. It has *slightly better efficiency and regulation*.
3. A 3-phase transformer takes *less floor space*.

On the other hand, from the point of view of standby, or same capacity, it is economical to have 3 single-phase transformers *plus* one spare rather than two 3-phase transformers one of which is a spare. However, in large central stations 3-phase transformers are often advantageous.

Disadvantages :

1. Three-phase transformers are much more difficult and costly to repair than are single-phase units.
2. When failure does occur and it becomes necessary to substitute a replacement unit to maintain service, the cost of spare is much greater than it would be were a single-phase transformer to be used as a replacement in a three-transformer bank.
3. There is a difficulty in transporting a heavier three-phase transformer compared with the moving of each of the three single-phase transformers.

Two general kinds of three-phase transformers are recognized, similar to single-phase transformers, depending upon the relative arrangements of windings and cores. These are the *core type* and the *shell type*.

Three-phase core type transformer. Fig. 72 shows three core-type transformers placed together so that they have a common path for the return magnetic circuit. Although the windows should be entirely filled by primary and secondary coils on each of the legs, only primary coils are shown on the outside legs. This simplifies the diagram, while it in no way changes the actual theory that follows, since the primary coils set up the flux. If the three transformers are identical in all respects, a balanced three-phase system of voltages will produce three fluxes in the cores which have the same maximum value, but differ in time phase by 120° . In the common leg of the three cores of Fig. 73, the three fluxes add, and the net flux is therefore always zero. The common leg may then be eliminated, with a subsequent saving in core material and size of transformer. A single polyphase transformer would be of impractical construction if it were the same as Fig. 72 with the centre leg omitted. Instead, the core-type polyphase transformer is manufactured so that it looks like that shown in Fig. 73. Actually, what we have done is, that axes of three coils have been moved into one plane. This causes the magnetic reluctance of coil *M* to differ somewhat from that of *L* and *N*. This

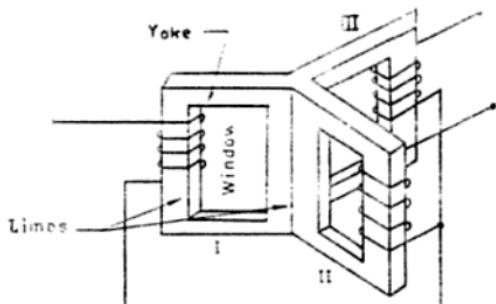


Fig. 72. Core-type transformers for polyphase transformation.


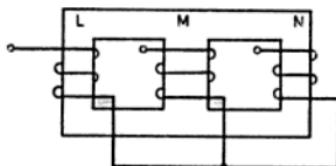


Fig. 73. Core-type three-phase transformer.


produces a slight unbalance in the three magnetizing currents, but the effect is not serious, especially under load.

Three-phase shell type transformer :

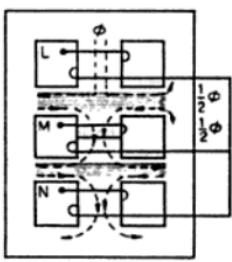- In Fig. 74 are shown three shell-type transformers stacked one above the other, with only the primary coils shown.



(a)

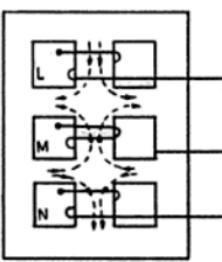

(b)

Fig. 74. Shell-type three-phase transformer (a) coil M wound in the same direction, (b) coil M wound in opposite direction.

- In Fig. 74 (a) the three coils are wound in the same direction. The flux in the common core area between adjacent phases such as the shaded portions is thus equal to the *difference* of two of the phase fluxes. Since the fluxes are 120° apart in time, this mutual flux is equal to $\sqrt{3} \times (\frac{1}{2}\phi)$, or 0.866 of the flux in the centre leg. If the same flux density is maintained throughout, less iron is required in the common legs. Now, however if the centre coil, phase M is reversed, the flux in the common core is equal to the *sum* of the fluxes of two adjacent phases. This is shown in Fig. 74 (b). As in any three-phase system, the sum of two fluxes is equal to either flux alone, which in this case is 0.5ϕ . This represents a further saving in iron, and for this reason shell-type three-phase transformers are *usually wound with centre coil opposing the two outside ones*.

10.3. Parallel Operation of 3-phase Transformers. The conditions for paralleling 3-phase transformers are same as that required for parallel operation of single-phase transformers with the following additions :

- (i) The voltage ratio must refer to the terminal voltage of primary and secondary.
- (ii) The phase displacement between primary and secondary voltages must be the same for all transformers which are to be paralleled.
- (iii) The phase sequence must be the same.

Following points are worthnoting while dealing with 3-phase transformers :

- The calculations are made for one phase only. The value of equivalent impedance used is the equivalent impedance per phase referred to secondary.
- When the impedances of primary and secondary windings are given separately then primary impedance must be transferred to secondary by multiplying it with (transformation ratio)².
- In case of Y/Δ or Δ/Y transformers the voltage ratios as given in the questions, refer to terminal voltages and are quite different from turn ratio.

HIGHLIGHTS

1. The function of a transformer is to transform alternating current energy from one voltage into another voltage. It operates on the principle of mutual inductance (between two or more inductively coupled coils).
2. Distribution transformers should be designed to have maximum efficiency at a load much lower than full-load (about 50%).

- Power transformers** should be designed to have maximum efficiency at or near full-load.
3. The transformation ratio (K) is defined as the ratio of the secondary voltage to primary voltage.

4. Approximate voltage drop $= I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi$

Exact voltage drop $= (I_2 R_{02} \cos \phi \pm I_2 X_{02}) + \frac{(I_2 X_{02} \cos \phi \mp I_2 R_{02} \sin \phi)^2}{2 oV_2}$

5. Transfer of resistance or reactance from

Primary to secondary $\times K^2$

Secondary to primary $\times \frac{1}{K^2}$

6. The change in secondary voltage when rated load at a specified power is removed.

$$\% \text{ regulation} = \frac{I_2 R_{02} \cos \phi \pm I_2 X_{02} \sin \phi}{oV_2} \times 100$$

$$\eta_{\text{all-day}} = \frac{\text{output in kWh}}{\text{input in kWh}} \text{ (for 24 hours).}$$

7. A transformer in which part of the winding is common to both the primary and secondary circuit is known as an auto-transformer.

OBJECTIVE TYPE QUESTIONS

(A) Choose the Correct Answer :

1. Which of the following does not change in a transformer ?

(a) Current	(b) Voltage
(c) Frequency	(d) All of the above.
2. In a transformer the energy is conveyed from primary to secondary

(a) through cooling coil	(b) through air
(c) by the flux	(d) none of the above.

3. A transformer core is laminated to

(a) reduce hysteresis loss	(b) reduce eddy current losses
(c) reduce copper losses	(d) reduce all above losses.
4. Which loss is not common between a transformer and rotating machines ?

(a) Eddy current loss	(b) Copper loss
(c) Windage loss	(d) Hysteresis loss.
5. The degree of mechanical vibrations produced by the laminations of a transformer depends on

(a) tightness of clamping	(b) gauge of laminations
(c) size of laminations	(d) all of the above.
6. The no-load current drawn by transformer is usually what percent of the full-load current ?

(a) 0.2 to 0.5 per cent	(b) 2 to 5 per cent
(c) 12 to 15 per cent	(d) 20 to 30 per cent.
7. In case there are burrs on the edges of the laminations of the transformer, it is likely to result in

(a) vibrations	(b) noise
(c) higher eddy current loss	(d) higher hysteresis loss.
8. The path of a magnetic flux in a transformer should have

(a) high resistance	(b) high reluctance
(c) low resistance	(d) low reluctance.
9. No-load test on a transformer is carried out to determine

(a) copper loss	(b) magnetising current
(c) magnetising current and loss	(d) efficiency of the transformer.
10. The dielectric strength of transformer oil is expected to be

(a) 1 kV	(b) 33 kV
(c) 100 kV	(d) 330 kV.
11. Sumpner's test is conducted on transformers to determine

(a) temperature	(b) stray losses
(c) all-day efficiency	(d) none of the above.
12. The permissible flux density in case of cold rolled grain oriented steel is around

(a) 1.7 Wb/m ²	(b) 2.7 Wb/m ²
(c) 3.7 Wb/m ²	(d) 4.7 Wb/m ² .
13. During the short-circuit test on a small transformer the frequency is increased from 50 Hz to 200 Hz. The copper losses will increase by a factor of

(a) 16	(b) 4
(c) 1	(d) $\frac{1}{4}$
14. The efficiency of a transformer will be maximum when

(a) copper losses = hysteresis losses	(b) hysteresis losses = eddy current losses
(c) eddy current losses = copper losses	(d) copper losses = iron losses.
15. No-load current in a transformer

(a) lags behind the voltage by about 75°	(b) leads the voltage by about 75°
(c) lags behind the voltage by about 15°	(d) leads the voltage by about 15°.
16. The purpose of providing an iron core in a transformer is to

(a) provide support to windings	(b) reduce hysteresis loss
(c) decrease the reluctance of the magnetic path	
(d) reduce eddy current losses.	
17. Which of the following is not a part of transformer installation ?

(a) Conservator	(b) Breather
(c) Buchholz relay	(d) Exciter.

ANSWERS

- | | | | | | | | | | | | | | |
|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|-----|
| 1. | (c) | 2. | (c) | 3. | (b) | 4. | (a) | 5. | (d) | 6. | (b) | 7. | (c) |
| 8. | (d) | 9. | (c) | 10. | (b) | 11. | (a) | 12. | (a) | 13. | (a) | 14. | (d) |
| 15. | (a) | 16. | (c) | 17. | (d) | 18. | (b) | 19. | (c) | 20. | (a) | 21. | (b) |
| 22. | (d) | 23. | (c) | 24. | (b) | 25. | (d) | 26. | (c) | 27. | (b) | 28. | (d) |
| 29. | (a) | 30. | (d) | 31. | (d) | 32. | (d) | 33. | (d) | 34. | (d) | 35. | (d) |
| 36. | (d) | 37. | (d) | 38. | (c) | 39. | (a) | 40. | (b) | 41. | (d) | 42. | (b) |
| 43. | (b) | 44. | (d) | 45. | (c) | 46. | (c) | 47. | (d) | 48. | (c) | 49. | (a) |
| 50. | (d) | 51. | (c) | 52. | (b) | 53. | (c) | 54. | (d) | 55. | (a) | 56. | (b) |
| 57. | (b) | 58. | (a) | 59. | (c) | 60. | (b) | 61. | (b) | 62. | (a) | 63. | (d) |
| 64. | (d) | 65. | (d) | 66. | (a) | 67. | (b) | 68. | (c) | 69. | (d) | 70. | (d) |

(B) Say 'Yes' or 'No'

- When a transformer raises the voltage it is called the step-up transformer.
 - A transformer must not be connected to D.C. source.
 - The ratio of primary voltage to secondary voltage is known as transformation ratio.
 - An ideal transformer is one in which the resistance of the windings is negligible and the core has no losses.
 - Primary and secondary currents are directly proportional to their respective turns.
 - The function of the magnetising component of no-load current is to sustain the alternating flux in the core.
 - The no-load primary input is practically equal to the iron loss in the transformer.
 - A transformer is said to be loaded when the secondary circuit of a transformer is completed through an impedance load.

9. Magnetic flux can be confined into a designed path.
10. When shifting resistance to the secondary, divide it by K^2
11. An open-circuit test is conducted to find no-load or core loss.
12. Short-circuit test is conducted to find full-load copper loss.
13. The change in voltage when rated load at a specified power is removed is termed as voltage regulation.
14. Iron or core losses include copper loss and eddy current loss.
15. Iron or core losses are found from short-circuit test.
16. The efficiency of a transformer at a particular load and power factor is defined as the ratio of power output to power input.
17. Copper losses = iron losses is the condition for maximum efficiency of a transformer.
18. $\eta_{\text{all-day}} = \frac{\text{output in kWh}}{\text{input in kWh}}$ (for 24 hours)
19. A transformer in which part of the winding is common to both the primary and secondary circuits is known as auto-transformer.
20. The Δ - Δ connection is generally used in systems in which the voltages are not very high and especially when continuity of service must be maintained even though one of the transformers should fail.
21. The Y - Δ connection is principally used where the voltage is to be stepped up.
22. The Δ - Y connection is employed where it is necessary to step-up the voltage.
23. The V - V circuit is frequently used for two auto-transformers.
24. It is practicable to connect instruments and meters directly to the lines in high voltage circuits.
25. A potential transformer is a step down transformer used along with a low range voltmeter for measuring a high voltage.
26. The current transformer ratio is not equal to the ratio of secondary to primary turns, mainly because of the effect of the magnetising current.
27. A constant-current transformer is used to supply power to street lights which are connected in series.
28. In case of an induction regulator primary winding is stationary.

ANSWERS

1. Yes	2. Yes	3. No	4. Yes	5. No	6. Yes	7. Yes
8. Yes	9. No	10. No	11. Yes	12. Yes	13. Yes	14. No
15. No	16. Yes	17. Yes	18. Yes	19. Yes	20. Yes	21. No
22. Yes	23. Yes	24. No	25. Yes	26. Yes	27. Yes	28. No

THEORETICAL QUESTIONS

1. What is a transformer ? How does it transfer electric energy from one circuit to another ?
2. Explain the principle of operation of a transformer.
3. What is meant by *transformer action* ? Under what conditions will it take place ?
4. If an alternating current is impressed on one coil, what will be the frequency of the induced voltage in another coil with which it is coupled ?
5. Enumerate the various kinds of transformers.
6. Explain the need for stepping up and stepping down voltages in a power system. How does a transformer accomplish ?
7. Why are transformer windings divided into several coils ?
8. What properties should a good transformer oil possess ?
9. What purposes are served by placing transformers in oil-filled tanks ?
10. Why are the tanks of some large transformers corrugated ?
11. Write a short note on 'transformer cooling'.
12. Enumerate and explain briefly different types of windings.

13. Derive an expression for induced e.m.f. in a transformer in terms of frequency, the maximum value of flux and the number of turns on the windings.
14. Derive an expression for the e.m.f. of an ideal transformer winding.
15. Explain the function of the active and reactive components of the no-load current of a static transformer.
16. Why are some transformers constructed with primary and secondary windings divided into two halves?
17. Distinguish between *power* and *distribution* transformers.
18. Draw and explain the no-load phasor diagram for a single-phase transformer.
19. Draw the vector diagram of a power transformer under full-load condition.
20. What is meant by *equivalent resistance* of a transformer? How may it be calculated in primary terms and secondary terms?
21. What is meant by the *equivalent reactance* of a transformer? How may it be calculated in primary terms and secondary terms?
22. How can the equivalent impedance of a transformer be determined?
23. Outline carefully the procedure for performing the short-circuit test.
24. What useful information is obtained from the short-circuit test?
25. Outline carefully the procedure for performing the open-circuit test.
26. What useful information is obtained from open-circuit test?
27. What are the two components of the core loss?
28. How is the hysteresis loss affected by a change in flux density?
29. Develop the equivalent circuit of a single phase transformer.
30. Draw the equivalent circuit of a transformer and show how the constants of the primary and secondary windings may be combined to give a simplified equivalent circuit with the values of constants given in terms of the secondary winding.
31. Describe the method of calculating the regulation and efficiency of a single-phase transformer by open circuit and short circuit tests.
32. Distinguish between the 'efficiency' and the 'regulation' of a transformer. Show how power factor affects both of them.
33. Explain with circuit diagrams, the open-circuit and short-circuit tests to be carried out in the laboratory for the determination of the parameters of a single-phase transformer. Derive the condition for maximum efficiency.
34. What is Sumpner's test? Draw a circuit diagram to conduct this test and explain its principle.
35. Define all-day efficiency.
36. What is an auto-transformer? What advantages are possessed by auto-transformers?
37. Derive an expression for saving of copper when an auto-transformer is used.
38. State the applications of auto-transformers. Why is this transformer not used as a distribution transformer? Prove that for the same capacity and voltage ratio, an auto-transformer requires less copper than an ordinary transformer.
39. What are the sources of heat in a transformer? Describe briefly the various methods used for cooling of transformers.
40. To what does the '*polarity*' of a transformer refer?

UNSOLVED EXAMPLES

E.m.f. Equation-Turn Ratio

1. The no-load ratio required in a single-phase 50-Hz transformer is 6600/300 V. If the maximum value of flux in the core is to be about 0.09 weber, find the number of turns in each winding.

[Ans. $N_1 = 330$; $N_2 = 15$]

2. A 20 kVA, single-phase transformer has 200 turns on the primary and 40 turns on the secondary. The primary is connected to 1000 V, 50-Hz supply. Determine :
 (i) the secondary voltage on open circuit ;
 (ii) the currents flowing through the two windings on full-load ; and
 (iii) the maximum value of flux. [Ans. (i) 200 V ; (ii) 20 A, 100 A ; (iii) 0.0225 Wb]
3. A single-phase transformer is connected to a 230 V, 50-Hz supply. The net cross-sectional area of the core is 50 cm^2 . The number of turns in the primary is 460 and in the secondary 80. Determine :
 (i) Transformation ratio ; (ii) Peak value of flux density in the core ; and
 (iii) E.m.f. in the secondary winding. [Ans. 0.1739 ; 0.4504 T ; 40 V]
4. A 6600/440 V single-phase 600 kVA transformer has 1200 primary turns. Find :
 (i) Transformation ratio ; (ii) Secondary turns ;
 (iii) Voltage/turn ; and
 (iv) Secondary current when it supplies a load of 400 kW at 0.8 power factor lagging.
 [Ans. $\frac{1}{15}$; 80 ; 5.5 V ; 1136 A]
5. Find the primary and secondary turns of a 3300/300 V, single-phase, 50-Hz, 30 kVA transformer if the flux in the core is to be about 0.06 Wb. Also determine the primary and secondary currents if the losses are to be neglected. [Ans. 264 ; 24 ; 100 A ; 9.09 A]
6. The voltage/turn of a single-phase transformer is 1.1 V, when the primary winding is connected to a 220 V, 50-Hz A.C. supply, the secondary voltage is found to be 660 V. Find :
 (i) Primary and secondary turns ; and
 (ii) Core area if the maximum flux density is 1.2 T. [Ans. 200 ; 600 ; 41.29 cm^2]

Transformer on No-load

7. A 2000/200 V single-phase transformer gives 0.5 A and 40 W as ammeter and wattmeter readings when supply is given to the low voltage winding and high voltage winding is kept open. Find :
 (i) The magnetising component, (ii) The iron loss component, and
 (iii) The power factor of no-load current. [Ans. 0.4582 A ; 0.2 A ; 0.4 lagging]
8. Find (i) active component and reactive components of no-load current and ; (ii) no-load current of a 230 V/115 V single-phase transformer if the power input on no-load to the high voltage winding is 70 W and power factor of no-load current is 0.25 lagging. [Ans. 0.3044 A ; 1.179 A ; 1.2176 A]
9. A single-phase transformer has 500 turns on the primary and 40 turns on the secondary winding. The mean length of the magnetic path in the core is 150 cm and the joints are equivalent to an air-gap of 0.1 mm. When a potential difference of 3000 V is applied to the primary, maximum flux density is 1.2 T. Calculate :
 (i) The cross-sectional area of the core, (ii) No-load secondary voltage,
 (iii) The no-load current drawn by the primary, and
 (iv) Power factor on no-load.

Given that AT/cm for a flux density of 1.2 T in the iron to be 5, the corresponding iron loss to be 2 W/kg at 50 Hz and density of iron as 7.8 g/cm^3 . [Ans. 225 cm^2 ; 240 V ; 1.208 A ; 0.1457]

Transformer on Load

10. A 230 V/115 V single phase transformer takes a no-load current of 1.7 A at a power factor of 0.18 lagging with low voltage winding kept open. If the low voltage winding is now loaded to take a current of 13 A at 0.8 power factor lagging find the current taken by high voltage winding. [Ans. 7.834 A]
11. A transformer has a primary winding of 900 turns and a secondary winding of 200 turns. When the load current on the secondary is 80 A at 0.8 power factor lagging, the primary current is 25 A at 0.707 power factor lagging. Determine graphically or otherwise the no-load current of the transformer and its phase with respect to the voltage. [Ans. $I_0 = 5.93 \text{ A}$; $\phi_0 = 73.3^\circ$]

12. A 8 : 1 step down, single-phase transformer takes a no-load current of 0.6 A at a power factor of 0.8 lagging with 1.v. winding kept open. If the secondary is connected to a load taking a current of 80 A at (i) 0.8 power factor lagging ; and (ii) 0.8 power factor leading find the primary current and power factor.
[Ans. 10.49 A, 0.7996 lagging ; 9.817 A, 0.8333 leading]

13. A 20 kVA, 2000/200 V, single-phase, 50-Hz transformer has a primary resistance of $2.5\ \Omega$ and reactance of $4.8\ \Omega$. The secondary resistance and reactance are $0.01\ \Omega$ and $0.018\ \Omega$ respectively. Find :
(i) Equivalent resistance referred to primary,
(ii) Equivalent impedance referred to primary,
(iii) Equivalent resistance, reactance and impedance referred to secondary, and
(iv) Total copper loss of the transformer.
[Ans. (i) $3.5\ \Omega$; (ii) $7.47\ \Omega$; (iii) $0.035, 0.066\ \Omega, 0.0747\ \Omega$; (iv) 350 W]

14. A 50 kVA, 4400/220 V transformer has $R_1 = 3.45\ \Omega$, $R_2 = 0.009\ \Omega$. The values of reactances are $X_1 = 5.2\ \Omega$ and $X_2 = 0.015\ \Omega$. Calculate for the transformer :
(i) Equivalent resistance as referred to primary,
(ii) Equivalent resistance as referred to secondary,
(iii) Equivalent reactance as referred to both primary and secondary,
(iv) Equivalent impedance as referred to both primary and secondary, and
(v) Total copper loss, first using individual resistances of the two windings and secondly, using equivalent resistances as referred to each side.
[Ans. (i) $7.05\ \Omega$; (ii) $0.0176\ \Omega$; (iii) $11.2\ \Omega$;
(iv) $13.23\ \Omega$; $0.0331\ \Omega$; (iv) 909 W]

15. A single-phase transformer has the following data :
Turn ratio = $19.5 : 1$, $R_1 = 25\ \Omega$, $X_1 = 100\ \Omega$, $R_2 = 0.06\ \Omega$, $X_2 = 0.25\ \Omega$. No-load current = 1.25 A leading the flux by 30° .
The secondary delivers 200 A at a terminal voltage of 500 V and a power factor of 0.8 lagging. Determine by the aid of a vector diagram the primary applied voltage, the primary power factor and the efficiency.
[Ans. $12540 \angle 186.7^\circ$, 0.698 (lag), 86.74%]

16. The high voltage and low voltage windings of a 1100/110 V single-phase 50 Hz transformer has resistances of $2.4\ \Omega$ and $0.02\ \Omega$ and reactances $1\ \Omega$ and $0.009\ \Omega$ respectively. The low voltage winding is connected to a load having an impedance of $(3+j2)\ \Omega$. Determine :
(i) Current in 1.v. winding,
(ii) Current in h.v. winding,
(iii) The load voltage, and
(iv) Power consumed by the load.
[Ans. (i) $30.11\ A$; (ii) $3.011\ A$; $108.5\ V$ (iv) $2720.7\ W$]

Equivalent Circuit and O.C. and S.C. Tests

17. The parameters of a 2300/230 V, 50 Hz transformer are given below :

$R_1 = 0.286 \Omega$	$R_2' = 0.319 \Omega$
$X_1 = 0.73 \Omega$	$X_2' = 0.73 \Omega$
$R_0 = 250 \Omega$	$X_0 = 1250 \Omega$

The secondary load impedance $Z_L = 0.387 + j0.29$. Solve the exact equivalent circuit with normal voltage across the primary. [Ans. $\eta = 78.8\%$, % Regulation = 2.7%]

18. A 230 V, 3 kVA single-phase transformer has an iron loss of 100 W at 40-Hz and 70 W at 30-Hz. Find the hysteresis and eddy current losses at 50-Hz. [Ans. 91.67 W, 41.67 W]

19. When a transformer is supplied at 400 V, 50-Hz the hysteresis loss is found to be 300 W and eddy current loss is found to be 250 W. Determine the hysteresis loss and eddy current loss when the transformer is supplied at $8^{\circ}0$ V, 100 Hz. [Ans. 600 W ; 1000 W]

20. When the primary of a transformer rated at 2200 V, 50-Hz is supplied at 2200 V, 50-Hz the wattmeter gives a reading of 1200 W on no-load. When it is supplied at 1100 V, 25-Hz, the wattmeter gives a reading of 400 W on no-load. If the wattmeter is connected in the input circuit find the hysteresis loss and eddy current loss at normal voltage and frequency. [Ans. 400 V : 800 W]

21. A 4400 V, 50-Hz transformer has a hysteresis loss of 1000 W, eddy current loss of 1500 W and full-load copper loss of 3500 W. If the transformer is supplied at 6600 V, 75-Hz, what will be the losses? Assume that the full-load current remains the same. [Ans. $P_h = 1500$ W, $P_e = 3375$ W]
22. A 50 Hz, single-phase transformer has a turn ratio of 6. The resistances are 0.9Ω , 0.03Ω and reactances are 5Ω and 0.13Ω for high-voltage and low voltage windings respectively. Find:
 (i) The voltage to be applied to the h.v. side to obtain full-load current of 200 A in the l.v. winding on short-circuit.
 (ii) The power factor on short-circuit.
- Draw the equivalent circuit and show therein all the values. [Ans. 329.3 V, 0.2]
23. A 200/2000 V transformer is fed from a 200 V supply. The total winding resistance and leakage reactance as referred to low voltage side are 0.16Ω and 7.0Ω respectively. The representing core loss is 400Ω and the magnetising reactance is 231Ω . A load of impedance $596 + j444 \Omega$ is connected across the secondary terminals. Calculate:
 (i) Input current ; (ii) The secondary terminal voltage ;
 (iii) Primary power factor. [Ans. (i) $25.96 \angle -40.78^\circ$ A ; (ii) 1859 V ; (iii) 0.757 lagging]
24. Determine the approximate equivalent circuit of a given 200/2000 V single-phase 40 kVA transformer having the following test results :
 O.C. test : 200 V, 6.4 A, 384 W on l.v. side.
 S.C. test : 78 V, 20 A, 620 W on h.v. side. [Ans. $R_{01} = 0.0155 \Omega$, $X_{01} = 0.0358 \Omega$,
 $R_0 = 104.2 \Omega$, $X_0 = 32.75 \Omega$]
25. Determine the equivalent circuit of a 200/400 V, 50-Hz, single-phase transformer from the following test data :
 O.C. test (l.v. side) : 200 V, 0.7 A, 70 W
 S.C. test (h.v. side) : 15 V, 10 A, 85 W
 Calculate the secondary voltage when delivering 5 kW at 0.8 power factor, lagging, the primary voltage being 200 V. [Ans. $R_0 = 571.4 \Omega$, $X_0 = 330 \Omega$, $R_{01} = 0.21 \Omega$,
 $X_{01} = 0.31 \Omega$, $V_2 = 377.8$ V]
26. A single-phase, 10 kVA, 500/250 V, 50-Hz transformer has the following constants :
 Resistance : Primary 0.2Ω , Secondary 0.5Ω
 Reactance : Primary 0.4Ω , Secondary 0.1Ω
 Resistance or equivalent exciting circuit referred to primary, $R_0 = 1500 \Omega$, reactance of the equivalent exciting circuit referred to primary, $X_0 = 750 \Omega$.
 What would be the readings of the instruments when the transformer is connected for the open-circuit and short-circuit tests ? [Ans. O.C. test : 500 V, 0.745 A, 167 W ;
 S.C. test : 46.8 V, 20 A, 880 W]
27. Find the approximate equivalent circuit of a single-phase 400/4400 V transformer having the following test readings :
 O.C. test (l.v. side) : 400 V, 5.2 A, 600 W
 S.C. test (h.v. side) : 155 V, 50 A, 1850 W [Ans. $R_0 = 266.7 \Omega$, $X_0 = 80.34 \Omega$, $Z_{01} = 0.02563 \Omega$,
 $R_{01} = 0.006115 \Omega$, $X_{01} = 0.02488 \Omega$]
28. The following readings were taken in open-circuit and short-circuit tests on a single-phase 20 kVA, 2000/200 V transformer :
 O.C. test (l.v. side) : 200 V, 2 A, 120 W
 S.C. test (h.v. side) : 30 V, 10 A, 140 W
 Determine :
 (i) Equivalent circuit referred to l.v. side
 (ii) Secondary terminal voltage on full-load at 0.8 power factor leading.
 [Ans. (i) $R_0 = 333.3 \Omega$, $X_0 = 104.8 \Omega$, $R_{02} = 0.014 \Omega$,
 $X_{02} = 0.02654 \Omega$; (ii) 200.47 V]

Regulation and Efficiency of a Transformer

29. The corrected instrument readings obtained from open and short-circuit tests on 10 kVA, 450/120 V, 50-Hz transformer are :
- O.C. Test :**
- $V_1 = 120 \text{ V}, I_1 = 4.2 \text{ A}, W_1 = 80 \text{ W}$; V_1, W_1 and I_1 were read on the low-voltage side.
- S.C. Test :**
- $V_1 = 9.65 \text{ V}; I_1 = 22.2 \text{ A}; W_1 = 120 \text{ W}$ with low-voltage winding short-circuited.
- Calculate :**
- The equivalent circuit (approximate) constants.
 - Efficiency and voltage regulation for 0.8 lagging power.
 - The efficiency at half full-load and 0.8 lagging power factor load.
- [Ans. (i) $R_0 = 25.30 \Omega, X_0 = 409 \Omega$; (ii) 97.57%, 2.04%; (iii) 97.34%]
30. The primary and secondary winding resistance of a 40 kVA, 6600/250 V single-phase transformer are 10Ω and 0.02Ω respectively. The equivalent leakage reactance as referred to the primary winding is 35Ω . Find the full-load regulation for load power factors of (i) unity ; (ii) 0.8 lagging ; and (iii) 0.8 leading.
- [Ans. (i) 2.202%; (ii) 3.69%; (iii) -0.166%]
31. The percentage resistance and reactance of a transformer are 2.5% and 4% respectively. Find the approximate regulation on full-load at
- unity power factor,
 - 0.8 power factor lagging, and
 - 0.8 power factor leading.
- [Ans. (i) 2.5%; (ii) 4.4%; (iii) -0.4%]
32. A single-phase 100 kVA, 2000/200 V, 50 Hz transformer has impedance drop of 10% and resistance drop of 5%.
- Find the regulation at full-load, 0.8 power factor lagging.
 - At what power factor is the regulation zero ?
- [Ans. 9.196%; 0.866 leading]
33. The high voltage of a single-phase 200 kVA 4400/220 V transformer takes a current of 30 A and power of 1200 W at 75 V when the low voltage winding is short-circuited. Determine :
- The voltage to be applied to the high voltage winding on full-load 0.8 power factor lagging if the secondary terminal voltage is to be kept at 220 V, and
 - % regulation.
- [Ans. (i) 4506 V; (ii) 2.355%]
34. A 20 kVA, 2200/220 V 50-Hz distribution transformer is tested for efficiency and regulation as follows ;
- O.C. test (l.v. side) : 220 V, 4.2 A, 148 W.
- S.C. test (h.v. side) : 86 V, 10.5 A, 360 W.
- Determine :
- Core loss
 - Equivalent resistance referred to primary.
 - Equivalent resistance referred to secondary.
 - Equivalent reactance referred to primary.
 - Equivalent reactance referred to secondary.
 - Regulation of transformer at 0.8 power factor lagging current.
 - Efficiency at full-load and half full-load at 0.8 power factor lagging current.
- [Ans. 148 W, $3.26 \Omega, 0.0326 \Omega, 7.51 \Omega, 0.0751 \Omega, 2.95\%, 97.4\%, 97.3\%$]
35. A 100 kVA single-phase transformer has a full-load primary current of 400 A and total resistance referred to primary is 0.006Ω . If the iron loss amounts to 500 W, find the efficiency on full-load and half-load at
- unity power factor, and
 - 0.8 power factor.
- [Ans. 98.58%, 98.56%, 98.22%, 98.19%]
- ### Maximum Efficiency
36. A 50 kVA, single phase transformer has an iron loss of 400 W and full-load copper loss of 800 W.
- Find the load at which maximum efficiency occurs and the value of maximum efficiency at unity power factor.

- (ii) If the maximum efficiency occurs at 80% of full-load, find the new core loss and full-load copper loss assuming that total full-load loss is constant.
 [Ans. (i) 70.7% of full-load, 97.79% ; (ii) $P_i = 468.36 \text{ W}$, $P_c = 731.64 \text{ W}

37. A 1100/220 V transformer has a primary resistance of 0.25Ω and secondary resistance of 0.03Ω . If iron loss amounts to 250 W, determine the secondary current at which maximum efficiency occurs and find the maximum efficiency at 0.8 power factor. [Ans. 111.8 A ; 97.52%]

38. A single-phase 250 kVA transformer has an efficiency of 96% on full-load at 0.8 power factor and on half full-load at 0.8 power factor. Find :
 (i) Iron loss, and
 (ii) full-load copper loss.
 [Ans. $P_i = 2.767 \text{ kW}$, $P_c = 5.533 \text{ kW}$]

39. The efficiency of a 300 kVA, single-phase transformer is 97.8% when delivering full-load at 0.8 power factor lagging and 98.4% when delivering half full-load at unity power factor. Determine the efficiency at 80% of full-load at 0.8 power factor lagging. [Ans. 97.95%]

40. A 12 kVA, 400/200 V single-phase 50-Hz transformer has maximum efficiency of 95% at 85% of full-load at unity power factor. Determine the efficiency at full-load at 0.8 power factor lagging. [Ans. 93.76%]

41. A 50 kVA, 2000/250 V single-phase transformer has resistances of 1.1Ω and 0.015Ω and reactances of 4.4Ω and 0.06Ω for the high voltage and low voltage windings respectively. It has a maximum efficiency of 96.05% at 80% of full-load at unity p.f. The magnetising current for the h.v. side at 2000 V is 1.25 A. Find the readings of suitable instruments for open circuit test and short-circuit tests, supply being given to h.v. side in both cases.
 [Ans. O.C. test : 2000 V, 1.316 A, 824 W
 S.C. test : 212.3 V, 25 A, 1287 W]

42. A 100 kVA, 3300/300 V single-phase transformer has an efficiency of 97.5% both on full-load at unity p.f. and on half full-load at unity power factor. The power factor of the no-load current is 0.3 lagging and the regulation on full-load at 0.8 p.f. lagging is 3 per cent. Draw the equivalent circuit referred to the l.v. side.
 [Ans. $R_{01} = 105.3 \Omega$, $X_0 = 33.11 \Omega$,
 $R_{02} = 0.01538 \Omega$, $X_{02} = 0.02451 \Omega$]

43. The maximum efficiency of a single-phase 240 kVA, 2000/250 V transformer occurs at 70% of full-load and is equal to 98% at 0.8 p.f. lagging. Determine the efficiency and regulation on full-load at 0.8 p.f. lagging if the impedance of the transformer is 8 per cent. [Ans. 97.81%, 5.699%]

44. A 5 kVA, 230/115 V transformer takes 1.2 A and 75 W when 230 V is applied to h.v. winding and l.v. winding is kept open. It takes 21.75 A and 150 W when the l.v. winding is short-circuited and 17.4 V is applied to the h.v. winding. Find :
 (i) The no-load current as a fraction of full-load input current at 0.8 p.f. lagging ;
 (ii) Percentage regulation on full-load at 0.8 p.f. lagging ; and
 (iii) The load at which maximum efficiency occurs and the maximum efficiency at unity p.f.
 [Ans. 5.162% of full-load input current ; 6.566% ; 70.7% of full-load, 95.94%]

45. The efficiency of a 20 kVA, 2000/200 V transformer is 96.8% at full-load at unity p.f. and 96% at 60% of a load at 0.8 p.f. Find the regulation at full-load at :
 (i) 0.8 p.f. lagging ; and
 (ii) 0.8 p.f. leading if the impedance is 7 per cent.
 [Ans. (i) 5.469%, (ii) - 2.385%]

46. A 100 kVA, 2000/200 V single-phase transformer takes a current of 50 A and 2400 W at 100 V when the low voltage winding is short circuited. Determine the load-voltage and percentage regulation when delivering full-load current at 0.8 p.f. leading, the supply voltage being 2000 V.
 [Ans. 200.142 V ; - 0.071%]

47. A single-phase, 25 kVA transformer has an iron loss of 240 W and full-load copper loss of 600 W.
 (i) Find the load at which maximum efficiency occurs and maximum efficiency at 0.8 p.f.
 (ii) If the maximum efficiency occurs at 70% of full-load, find the core loss and copper loss assuming the total loss to be the same as in the previous case.
 [Ans. (i) 63.25% of full-load, 96.36% :
 (ii) 276.3 W, 563.7 W]$

All-Day Efficiency

48. A 20 kVA, 2000/200 V transformer has an iron loss of 300 W and full-load copper loss of 400 W. During the day it is loaded as follows :

No. of hours	Load	Power factor
8	$\frac{1}{4}$ load	0.5
6	Full-load	0.8
6	$\frac{3}{4}$ load	unity
4	No-load	—

Find the all-day efficiency.

[Ans. 94.84%]

49. A 30 kVA transformer has got a maximum efficiency of 97% at 80% of load at unity p.f. During the day it is loaded as follows :

No. of hours	Load	Power factor
10	4 kW	0.6 lag
9	20 kW	0.8 lag
5	24 kW	0.85 lag

Find the all-day efficiency.

[Ans. 95.68%]

50. The all-day efficiency of 200 kVA transformer is 96% when it is loaded as follows :

No. of hours	Load	Power factor
12	120 kW	0.8
8	150 kW	unity
4	No-load	—

If maximum efficiency of this transformer occurs at 80% of full-load, find iron loss and full-load copper loss.

[Ans. $P_i = 2.645 \text{ kW}$, $P_c = 4.133 \text{ kW}$]

51. An auto transformer supplies a load of 5 kW at 125 V and at unity power factor. If the primary voltage is 250 V, determine :

(i) Transformer ratio,

(ii) Secondary current,

(iii) Primary current,

(iv) Number of turns across secondary if the total number of turns is 250,

(v) Power transformed, and

(vi) Power conducted directly from the supply mains to load. [Ans. $\frac{1}{2}, 40 \text{ A}, 20 \text{ A}, 125, 9.5 \text{ kW}, 2.5 \text{ kW}$]

52. The primary and secondary voltages of an auto-transformer are 500 V and 400 V respectively. Show with the aid of diagram the current distribution in the windings when the secondary current is 100 A and calculate the economy in copper. [Ans. 80 per cent]

53. A 200/250 V auto-transformer draws power from a 200 V line and supplies a 5 kW load with a power factor of 0.8 lagging. A second load of 2 kW is supplied at unity power factor from 100 V winding. Neglecting losses, calculate the current drawn by the transformer from the 200 V line and its power factor. [Ans. 42.64 A, 0.898]

54. A 5 kVA, single-phase 50-Hz transformer has full-load efficiency of 95 per cent and an iron loss of 50 W. The transformer is now connected as an auto-transformer to a 220 V supply. If it delivers a 5 kW load at unity power factor to a 110 V circuit, calculate the efficiency of the operation and the current drawn by the high-voltage side. [Ans. 79.27%, 23.2 A]

55. A 480/120 V, 5 kVA two winding transformer is to be used as an auto-transformer to supply power at 480 V from 600 V source. Draw the connection diagram and determine the kVA capacity as an auto-transformer. [Ans. 25 kVA]

Rotating Machines

1. Direct Current Machines—Construction of D.C. machines—E.m.f. equation of a generator—Types of D.C. generators—Parallel operation of D.C. generators—Direct Current Motor—General aspects—Principle of operation of D.C. motor—Back or counter e.m.f.—Comparison between motor and generator action—Torque developed in a motor—Mechanical power developed by motor armature—Types of D.C. motors—Speed of a D.C. motor—Speed regulation—Motor characteristics—Comparison of D.C. motor characteristics—Summary of characteristics and applications of D.C. motors—Starting of D.C. motors. 2. Synchronous Machines—Synchronous generator or alternator—Introduction—Classification and operating principle—Constructional details—Frequency—Armature windings—Chording of windings—Pitch factor—Distribution or breadth or winding factor—E.m.f. equation—Synchronous Motor—Introduction—Characteristic features, advantages and disadvantages—Applications—Construction—Principle of operation—Synchronous motors—Starting—Effect of load on a synchronous motor—Torque developed by the motor. 3. Polyphase Induction Motor—General aspects—Classification of A.C. motors—Constructional details—Production of rotating magnetic field—Theory of operation of an induction motor—Slip—Frequency of rotor current—Rotor e.m.f. and rotor current—Torque and power—Effect of change in supply voltage on starting torque—Effect of change in supply voltage on torque and slip—Full-load torque and maximum torque—Starting torque and maximum torque—Torque-slip and torque-speed curves—Operating characteristics of a 3-phase squirrel-cage induction motor—Operating characteristics of a wound-rotor (slip ring) induction motor—Starting of induction motors—Squirrel-cage motors—Slip ring induction motors—Starting of—Squirrel-cage motors—Advantages, disadvantages and applications—Wound rotor (or slip ring) induction motors—Advantages, disadvantages and applications—Comparison of a squirrel-cage and a slip ring (or phase wound) induction motors. 4. Single Phase Motors—General aspects—Types of single phase motor—Single phase induction motors—Split phase motors—Single phase commutator motors—Single phase synchronous motors. 5. Insulating materials. 6. Rating and heating of D.C. machines. 7. Rating specifications of A.C. machines. 8. Duty cycles. 9. Cooling of electrical machines—Highlights—Objective Type Questions—Theoretical Questions—Unsolved Examples.

1. DIRECT CURRENT MACHINES

1.1. Construction of D.C. Machines

A D.C. machine consists of two main parts :

- (i) **Stationary part.** It is designed mainly for producing a magnetic flux.
- (ii) **Rotating part.** It is called the *armature*, where mechanical energy is converted into electrical (electrical generator), or conversely, electrical energy into mechanical (electric motor).

The stationary and rotating parts are separated from each other by an *air gap*.

- The *stationary part* of a D.C. machine consists of *main poles*, designed to create the magnetic flux, *commutating poles* interposed between the main poles and designed to ensure sparkless operation of the brushes at the commutator (in very small machines with a lack of space commutating poles are not used); and a *frame/yoke*.

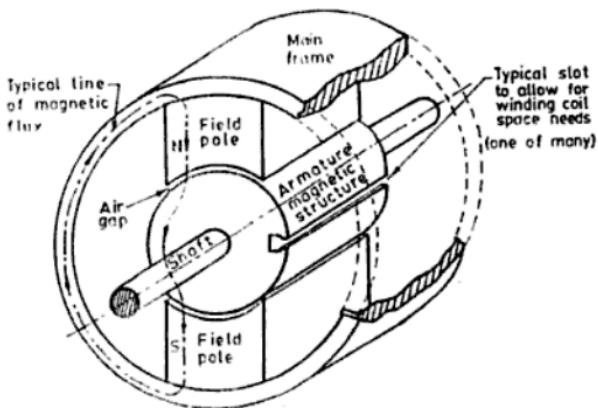


Fig. 1. Generator or motor magnetic structure.

- The **armature** is a cylindrical body rotating in the space between the poles and comprising a *slotted armature core*, a *winding* inserted in the armature core slots, a *commutator*, and a *brush gear*.

Fig. 1 shows generator or motor magnetic structure.

Description of Parts of D.C. Machines :

Frame. Fig. 2 shows the sectional view of four pole D.C. machine.

- The *frame* is the stationary part of a machine to which are fixed the main and commutating poles and by means of which the machine is bolted to its bed plate.
- The ring-shaped portion which serves as the path for the main and commutating pole fluxes is called the 'yoke'.

Cast iron used to be the material for the frame/yoke in *early machines* but now it has been replaced by *cast steel*. This is because cast iron is saturated by a flux density of about 0.8 Wb/m^2 while saturation with cast steel is at about 1.5 Wb/m^2 . Thus the cross-section of a cast iron frame is about twice that of a cast steel frame for the same value of magnetic flux. Hence, if it is necessary to reduce the weight of machine, cast steel is used. Another disadvantage with the use of cast iron is that its mechanical and magnetic properties are uncertain due to the presence of blow holes in the casting. Lately, rolled steel yokes have been developed with the improvements in the welding techniques. The advantages of fabricated yokes are that there are no pattern charges and the magnetic and mechanical properties of the frame are absolutely consistent.

It may be advantageous to use cast iron for frames but for medium and large sizes usually rolled steel is used.

- If the armature diameter does not exceed 35 to 45 cm, then, in addition to the poles, end shields or frame-heads which carry the bearings are also attached to the frame. When the armature diameter exceeds 1 m, it is common practice to use pedestal-type bearings, mounted separately, on the machine bed plate outside the frame.

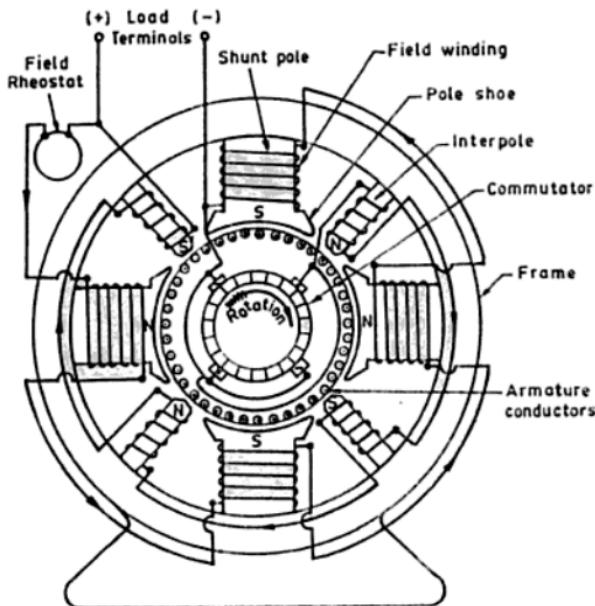


Fig. 2. Sectional view of a four pole D.C. machine.

- The end shield bearings, and sometimes the pedestal bearings, are of ball or roller type. However, more frequently plain pedestal bearings are used.
- In machines with large diameter armatures a brush-holder yoke is frequently fixed to the frame.

Field Poles :

- Formerly the poles were cast integral with the yoke. This practice is still being followed for small machines. But in present day machines *it is usual to use either a completely laminated pole, or solid steel poles with laminated pole shoes.*
- Laminated construction is necessary because of the pulsations of field strength that result when the notched armature rotor magnetic structure passes the pole shoe. Variations in field strength result in internal eddy currents being generated in a magnetic structure. These eddy currents cause losses ; they may be largely prevented by having laminated magnetic structures. Laminated structures allow magnetic flux to pass along the length of the laminations, but do not allow electric eddy currents to pass across the structure from one lamination to another. The assembled stack of laminations is held together as a unit by appropriately placed rivets. *The outer end of the laminated pole is curved to fit very closely into the inner surface of the main frame.*
- Fig. 3 shows the constructional details of a field pole. *The pole shoe acts as a support to the field coils and spreads out the flux in the air gap and also being of larger cross-section reduces the reluctance of the magnetic path.*

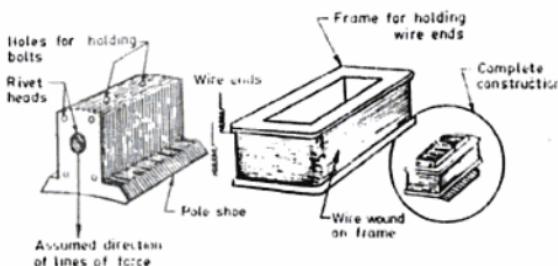


Fig. 3. Constructional details of a field pole.

- Different methods are used for attaching poles to the yoke. In case of *smaller sizes*, the back of the pole is drilled and tapped to receive pole bolts (see Fig. 4). In *larger sizes*, a circular or a rectangular pole bar is fitted to the pole. This pole bar is drilled and tapped and the pole bolts passing through laminations screw into the tapped bar (see Fig. 5).

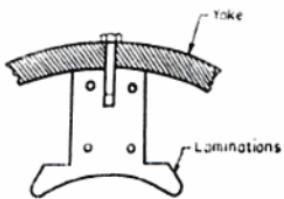


Fig. 4. Fixing pole to the yoke.

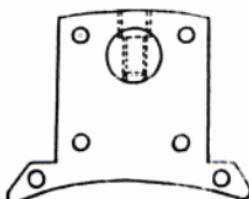


Fig. 5

Commutating Poles :

- A commutating pole (also called *interpole*) is similar to a main pole and consists of core terminating in a pole shoe, which may have various shapes, and coil mounted on the core.
- The commutating poles are *arranged strictly midway between the main poles* and are bolted to the yoke.
- Commutating poles are usually made of solid steel, but for machines operating on sharply varying loads they are made of sheet steel.*

Armature :

- The armature consists of core and winding. Iron being the magnetic material is used for armature core. However, iron is also a good conductor of electricity. The rotation of solid iron core in the magnetic field results in eddy currents. The flow of eddy currents in the core leads to wastage of energy and creates the problem of heat dissipation. To reduce the eddy currents the core is made of thin laminations.
- The armature of D.C. machines (see Fig. 6) is built up of thin laminations of low loss silicon steel. The laminations are usually 0.4 to 0.5 mm thick and are insulated with varnish.
- The armature laminations, in small machines, are fitted directly on to the shaft and are clamped tightly between the flanges which also act as supports for the armature winding.

One end flange rests against a shoulder on the shaft, the laminations are fitted and other end is pressed on the shaft and retained by a key.

The core (except in small size) is divided into number of packets by radial ventilation spacers. The spacers are usually I sections welded to thick steel laminations and arranged to pass centrally down each tooth.

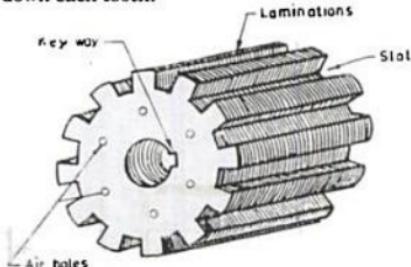


Fig. 6. Armature of a D.C. machine.

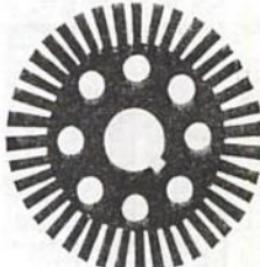


Fig. 7. Drum armature stamping with axial flow ventilation system.

- For *small machines* the laminations are punched in one piece (see Fig. 7). These laminations are built up directly on the shaft. With such an arrangement, it is necessary to provide *axial ventilation holes* so that air can pass into ventilating ducts.
- The armature laminations of *medium size machines* (having more than four poles) are built on a spider. The spider may be fabricated. Laminations up to a diameter of about 100 cm are punched in one piece and are directly keyed on the spider (see Fig. 8).

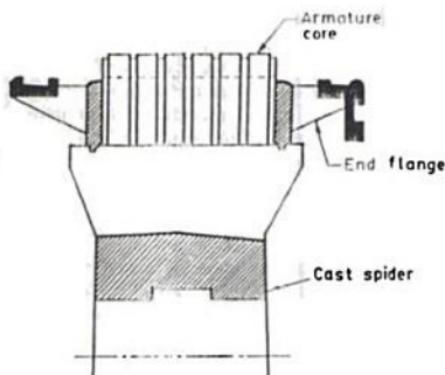


Fig. 8. Clamping of an armature core.

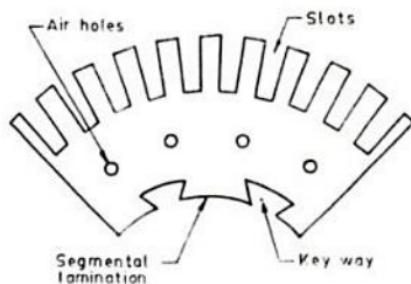


Fig. 9. Segmental stampings.

- In case of *large machines*, the laminations of such thin sections are difficult to handle because they tend to distort and become wavy when assembled together. Hence circular laminations instead of being cut in one piece are cut in a number of suitable sections or *segments* which form part of a complete ring (see Fig. 9). A complete circular lamination is made up of four or six or even eight segmental laminations. Usually two keyways are

notched in each segment and are dove-tailed or wedge shaped to make the laminations self-locking in position.

- The armature winding is housed in slots on the surface of the armature. The conductors of each coil are so spaced that when one side of the coil is under a north pole, the opposite is under a south pole.

Fig. 10 shows the arrangement of conductors and insulation in a slot.

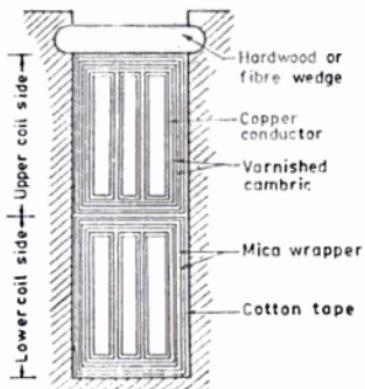


Fig. 10. Cross-section of an armature slot.

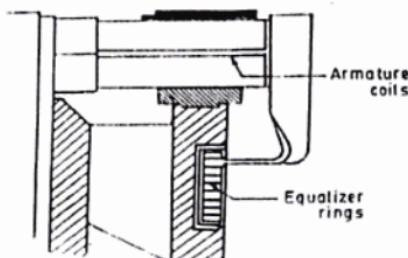


Fig. 11. Ring type equilizers.

- In D.C. machines two layer winding with diamond shaped coils is used. The coils are usually former wound. In small machines, the coils are held in position by band of steel wire, wound under tension along the core length. In large machines, it is useful to employ wedges of fibre or wood to hold coils in place in the slots. Wire bands are employed for holding the overhang. The *equilizer connections* are located under the overhang on the side of the commutator. Fig. 11 shows a typical arrangement for equilizers. The equilizers can be accommodated on the other end of the armature also.

Commutator :

- A commutator converts alternating voltage to a direct voltage.
- A commutator is a cylindrical structure built up of segments made of hard drawn copper. These segments are separated from one another and from the frame of the machine by *mica strips*. The segments are connected to the winding through risers. The risers have air spaces between one another so that air is drawn across the commutator thereby keeping the commutator cool.

Fig. 12 shows the components of a commutator. The general appearance of a commutator when completed is as shown in Fig. 13 (a). The commutator and armature assembly is shown in Fig. 13 (b).

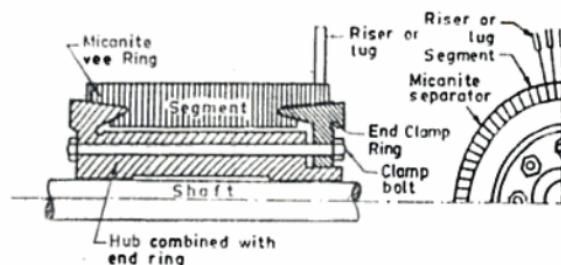


Fig. 12. Commutator components.

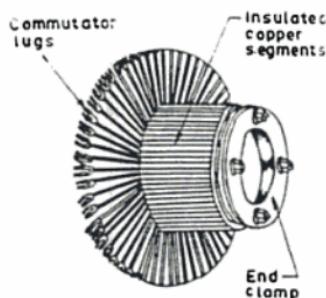


Fig. 13. (a) General appearance of a commutator after assembly.

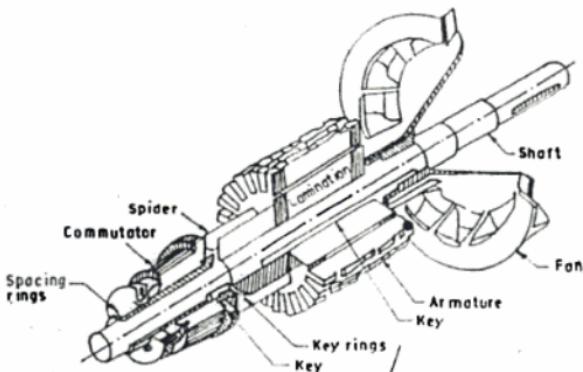


Fig. 13. (b) Commutator and armature assembly.

Brush Gear. To collect current from a rotating commutator or to feed current to it use is made of *brush-gear* which consists of :

- (i) Brushes
- (ii) Brush holders
- (iii) Brush studs or brush-holder arms
- (iv) Brush rocker
- (v) Current-collecting busbars.

Brushes. The brushes used for D.C. machines are divided into five classes :

- | | |
|--------------------|-----------------------|
| (i) Metal graphite | (ii) Carbon graphite |
| (iii) Graphite | (iv) Electro-graphite |
| (v) Copper. | |

- The allowable *current density* at the brush contact varies from 5 A/cm^2 in case of carbon to 23 A/cm^2 in case of copper.
- The use of *copper brushes* is made for machines designed for *large currents at low voltages*. Unless, very carefully lubricated, they cut the commutator very quickly and in any case, the wear is rapid. *Graphite and carbon graphite brushes are self-lubricating and, are, therefore, widely used*. Even with the softest brushes, however, there is a gradual wearing away of the commutator, and if mica between the commutator segments does not wear down so rapidly as the segments do, the high mica will cause the brushes to make poor contact with segments, and sparking will result and consequent damage to commutator. So to prevent this, the mica is frequently '*undercut*' to a level below the commutator surface by means of a narrow milling cutter.

Brush holders. *Box type brush holders* are used in all ordinary D.C. machines. A box type brush holder is shown in Fig. 14. At the outer end of the arm, a brush box, open at top and bottom is attached. The brush is pressed on to the commutator by a *clock spring*. The pressure can be adjusted by a lever arrangement provided with the spring. The brush is connected to a flexible conductor called *pig tail*. The flexible conductor may be attached to the brush by a screw or may be soldered.

- The bush boxes are usually made of *bronze casting or sheet brass*. In low voltage D.C. machines where the commutation conditions are easy galvanised steel box may be used.
- Some manufacturers use individual brush holders while others use multiple holders, i.e., a number of single boxes built up into one long assembly.

Brush rockers. Brush holders are fixed to brush rockers with bolts. The brush rocker is arranged concentrically round the commutator. *Cast iron is usually used for brush rockers*.

Armature Shaft Bearings :

- *With small machines roller bearings are used at both ends.*
- *For larger machines roller bearings are used for driving end and ball bearings are used for non-driving (commutator) end.*

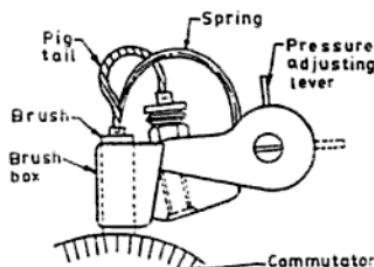


Fig. 14. Box type brush holder.

- The bearings are housed in the end shields.
 - For large machines pedestal bearings are used.

Armature Windings. The *armature winding* is very important element of a machine, as it directly takes part in the conversion of energy from one form into another. The requirements which a winding must meet are diverse and often of a conflicting nature. Among these requirements the following are of major importance.

- The winding must be designed with the *most advantageous utilisation of the material in respect to weight and efficiency*.
 - The winding should provide the necessary mechanical, thermal and electrical strength of the machine to ensure the usual service life of 16-20 years.
 - For D.C. machines proper current collection at the commutator (*i.e.*, absence of detrimental sparking) must be ensured.
 - According to the degree of closure produced by winding, armature windings are of the following two types :

The closed armature windings are of two types:

In general there are two types of drum armature windings:

"**Lap winding**" is suitable for comparatively low voltage but high current generators whereas "**wave of winding**" is used for high voltage, low current machines.

- In '*lap winding*' the finish of each coil is connected to the start of the next coil so that winding or commutator pitch is unity.
 - In '*wave winding*' the finish of coil is connected to the start of another coil well away from the fixed coil.

1.2. E.M.F. Equation of a Generator

Let p = number of poles.

ϕ = flux/pole, webers (Wb).

Z = total number of armature conductors

= number of slots × number of conductors/slot.

N = rotational speed of armature, r.p.m.

a = number of parallel paths in armature, and

E_g = generated e.m.f. per parallel path in armature

$$\text{Average e.m.f. generated per conductor} = \frac{d\phi}{dt} \text{ volt.}$$

Now, flux cut per conductor in one revolution, $d\phi = p\phi$ Wb.

$$\text{Number of revolutions/second} = \frac{N}{60}$$

\therefore Time for one revolution, $dt = \frac{60}{N}$ seconds

Hence, according to Faraday's laws of electromagnetic induction,

$$\text{E.m.f. generated per conductor} = \frac{p\phi N}{60} \text{ volts.}$$

For a lap wound generator :

Number of parallel paths, $a = p$

$$\text{Number of conductor (in series) in one path} = \frac{Z}{p}$$

$$\therefore \text{E.m.f. generated per path} = \frac{\phi p N}{60} \times \frac{Z}{p} = \frac{\phi Z N}{60} \text{ volt.}$$

For a wave wound generator :

Number of parallel paths, $a = p$

$$\text{Number of conductor (in series) in one path} = \frac{Z}{2}$$

$$\therefore \text{E.m.f. generator per path} = \frac{p\phi N}{60} \times \frac{Z}{2} = \frac{p\phi Z N}{120} \text{ volt.}$$

In general, generated e.m.f.

$$E_g = \frac{\phi Z N}{60} \times \left(\frac{p}{a} \right) \text{ volt} = \frac{p\phi Z N}{60a} \quad \dots(1)$$

where $a = p$ for lap winding

$= 2$ for wave winding.

Example 1. A six pole lap wound D.C. generator has 720 conductors, a flux of 40 m Wb per pole is driven at 400 r.p.m. Find the generated e.m.f.

Solution. Number of poles, $p = 6$

Total number of conductors, $Z = 720$

Flux per pole, $\phi = 40 \text{ m Wb} = 40 \times 10^{-3} \text{ Wb}$

Speed of rotation, $N = 400 \text{ r.p.m.}$

Number of parallel paths, $a = p = 6$ [Since the generator is *lap wound*.]

Generated e.m.f. E_g :

$$\text{Using the relation, } E_g = \frac{p\phi Z N}{60a} = \frac{6 \times 40 \times 10^{-3} \times 720 \times 400}{60 \times 6} = 192 \text{ V.}$$

Hence, generated e.m.f. $E_g = 192 \text{ V. (Ans.)}$

Example 2. A six-pole lap connected generator has a useful flux/pole of 0.045 Wb. If the no load voltage at 400 r.p.m. is 300 V, find the conductors on the armature periphery.

Solution. Number of poles, $p = 6$

Useful flux/pole, $\phi = 0.045 \text{ Wb}$

No load voltage, $E_g = 300 \text{ V}$

Number of conductors, Z :

Number of parallel paths, $a = p = 6$ [Since the generator is *lap wound*.]

$$\text{We know that, } E_g = \frac{p\phi Z N}{60a}$$

$$300 = \frac{6 \times 0.045 \times Z \times 400}{60 \times 6}$$

$$\therefore Z = \frac{300 \times 60 \times 6}{6 \times 0.045 \times 400} \quad \text{i.e. } Z = 1000.$$

Hence, total number of armature conductors = 1000. (Ans.)

Example 3. An 8-pole wave connected D.C. generator has 1000 armature conductors and flux/pole 0.035 Wb. At what speed must it be driven to generate 500 V?

Solution. Number of poles, $p = 8$

Total number of armature conductor, $Z = 1000$

Flux/pole, $\phi = 0.035 \text{ Wb}$

Generated voltage, $E_g = 500 \text{ V}$

Number of parallel paths, $a = 2$ [Since the generator is wave wound.]

Speed of rotation, N :

Using the relation, $E_g = \frac{p\phiZN}{60a}$

$$500 = \frac{8 \times 0.035 \times 1000 \times N}{60 \times 2}$$

$$\therefore N = \frac{500 \times 60 \times 2}{8 \times 0.035 \times 1000} = 214.3 \text{ r.p.m.}$$

Hence, speed of generator = 214.3 r.p.m. (Ans.)

Example 4. The armature of a 6-pole D.C. generator has a wave winding containing 650 conductors. Calculate the generated e.m.f. when the flux per pole is 0.055 Wb and the speed is 300 r.p.m.

Calculate speed at which the armature must be driven to generate an e.m.f. of 550 V if the flux per pole is reduced to 0.05 Wb.

Solution. Number of poles, $p = 6$

Total number of conductors, $Z = 650$

Flux per pole, $\phi = 0.055 \text{ Wb}$

Speed of rotation, $N = 300 \text{ r.p.m.}$

E.m.f. generated, $E_g = ?$

Generated e.m.f. (2nd case) = 550 V

Flux per pole (2nd case) = 0.05 Wb

Speed of rotation, $N = ?$

Case I. E.m.f. generated, E_g :

Using the relation, $E_g = \frac{p\phiZN}{60a}$

$$= \frac{6 \times 0.055 \times 650 \times 300}{60 \times 2} \quad [\because a = 2, \text{ as the generator is wave wound}]$$

$$= 536.25 \text{ V.}$$

Hence, e.m.f. generated = 536.25 V. (Ans.)

Case II. Speed of rotation, N :

$$E_g = \frac{p\phiZN}{60a}$$

$$550 = \frac{6 \times 0.05 \times 650 \times N}{60 \times 2}$$

$$N = \frac{550 \times 60 \times 2}{6 \times 0.05 \times 650} = 338.46 \text{ r.p.m.}$$

Hence, speed of rotation = 338.46 r.p.m. (Ans.)

Example 5. A six pole lap wound D.C. armature has 70 slots with 20 conductors/slot. The ratio of pole arc to pole pitch is 0.68. The diameter of bore of the pole shoe is 0.46 m. The length of pole shoe is 0.3 m. If the air gap flux density is 0.3 Wb/m² and the e.m.f. induced in the armature is 500 V, find the speed at which it runs.

Solution. Number of poles, $p = 6$

Number of slots = 70

Conductors/slot = 20

∴ Total number of conductors, $Z = 70 \times 20 = 1400$

Ratio of pole arc to pole pitch = 0.68

Diameter of bore of the pole shoe = 0.46 m

Length of the pole shoe = 0.3 m

Air gap flux density, $B = 0.3 \text{ Wb/m}^2$

E.m.f. induced, $E_g = 500 \text{ V}$

Speed of rotation, N :

$$\frac{\text{Pole arc}}{\text{Pole pitch}} = 0.68$$

∴ Pole arc = $0.68 \times \text{pole pitch}$

$$= 0.68 \times \frac{\pi D}{p} = \frac{0.68 \times \pi \times 0.46}{6} = 0.1638 \text{ m}$$

Area of pole shoe, $A = \text{pole arc} \times \text{length of pole shoe}$

$$= 0.1638 \times 0.3 = 0.04914 \text{ m}^2$$

Now, $\phi = B \times A = 0.3 \times 0.04914 = 0.01474 \text{ Wb}$

Using the relation, $E_g = \frac{p \phi Z N}{60a}$

$$500 = \frac{6 \times 0.01474 \times 1400 \times N}{60 \times 6} \quad [\because a = p = 6, \text{ generator being lap wound}]$$

$$\therefore N = \frac{500 \times 60 \times 6}{6 \times 0.01474 \times 1400} = 1453.7 \text{ r.p.m.}$$

Hence, speed of rotation = 1453.7 r.p.m. (Ans.)

1.3. Types of D.C. Generators

- The power stations of modern design generate practically only three-phase alternating current. A large part of this power is used in the form of alternating current in industry, for lighting and domestic needs. When industrial needs make it necessary too or when it is of greater advantage to use direct current (for chemical and metallurgical plants, electric traction, etc.) it is generally obtained by converting A.C. to D.C. with the help of converters of ionic or machine types. In the latter case wide use is made of such installations as motor generator sets in which A.C. motor is coupled to a D.C. generator on a common shaft.
- As primary sources of power, D.C. generators are mainly used in self-contained plants such as automobiles and air planes, for electric arc welding, train car lighting, in sub-marines, etc.

Classification

According to method of excitation D.C. generators are classified as follows :

1. Separately excited generators,
2. Self-excited generators.

Separately excited generators :

These are those generators whose field magnets are energised from an independent external source of D.C. current. Such a generator is shown in Fig. 15.

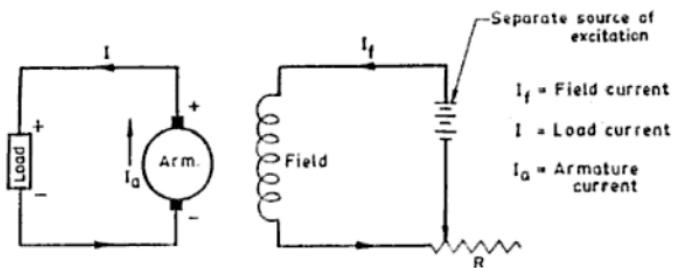


Fig. 15. Separately excited generator.

Self-excited generators :

These are those generators whose field magnets are energised by the current produced by the generators themselves. Due to residual magnetism, there is always present some flux in the poles. When the armature is rotated, some e.m.f. and hence some induced current produced which is partly or fully passed through the field coils thereby *strengthening the pole flux*.

Self excited generators can be divided, in accordance with how the *field winding is connected into generators*, as follows :

- (i) Shunt wound generators
- (ii) Series wound generators
- (iii) Compound wound generators :
 - (a) Short shunt
 - (b) Long shunt

(i) Shunt wound generators : Refer Fig. 16.

In these generators the field windings are connected *across or in parallel with the armature conductors*, and have the full voltage of the generator across them.

Important relations : Refer Fig. 16.

- (i) $I_{sh} = \frac{V}{R_{sh}}$
- (ii) $I_a = I_{sh} + I$
- (iii) $V = E_g - I_a R_a$
- (iv) Power developed = $E_g I_a$
- (v) Power delivered = VI

where I_{sh} = shunt field current, I_a = armature current,
 I (or I_l) = load current, R_a = armature resistance,
 R_{sh} = shunt field resistance, E_g = generated e.m.f., and
 V = terminal voltage.

(ii) Series wound generators : Refer Fig. 17. In this case, the field windings are joined in series with armature conductors. As they carry full load current, they consist of relatively few turns of thick wire or strip. The use of such generators is limited to special purposes (as boosters etc.).

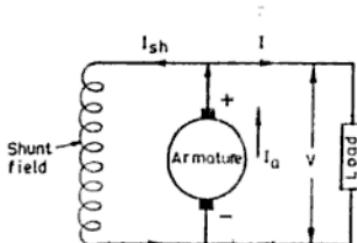


Fig. 16. Shunt wound generator.

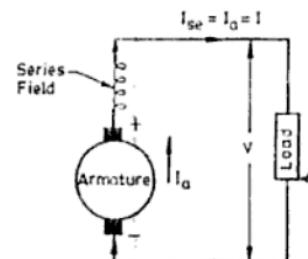


Fig. 17. Series wound generator.

Important Relations. (see Fig. 17) :

- (i) $I_a = I_{se} = I$ $(I_{se} = \text{series field current})$
 (ii) $V = E_g - I(R_a + R_{se})$ $(R_{se} = \text{series field resistance})$
 (iii) Power developed = $E_g I$
 (iv) Power delivered = VI .

(iii) Compound wound generators. It is a combination of a few series and a few shunt windings and be either short shunt or long shunt as shown in Figs. 18 and 19 respectively.

Important Relations :**(a) Short shunt compound wound.** (See Fig. 18) :

- (i) $I_{se} = I$
 (ii) $I_{sh} = \frac{V + I_{se}R_{se}}{R_{sh}}$
 (iii) $I_a = I + I_{sh}$
 (iv) $V = E_g - I_a R_a - I_{se} R_{se}$
 (v) Power developed = $E_g I_a$
 (vi) Power delivered = VI .

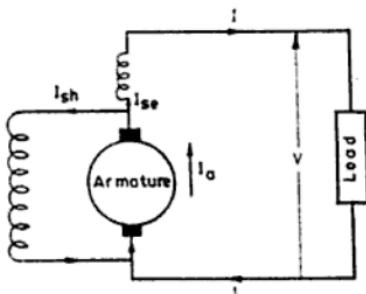


Fig. 18. Short shunt compound wound generator.

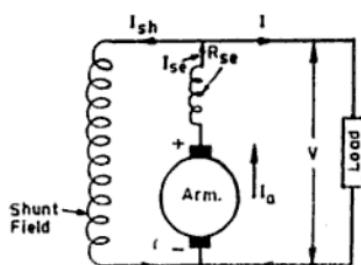


Fig. 19. Long shunt compound wound generator.

(b) Long shunt compound wound. (See Fig. 19) :

- (i) $I_{sh} = \frac{V}{R_{sh}}$
 (ii) $I_a = I_{se} = I + I_{sh}$
 (iii) $V = E_g - I_a R_a - I_{se} R_{se} = E_g - I_a (R_a + R_{se})$
 (iv) Power developed = $E_g I_a$
 (v) Power delivered = VI .

Example 6. A 4-pole lap wound shunt generator supplies to 50 lamps of 100 watts, 200 V each. The field and armature resistances are $50\ \Omega$ and $0.2\ \Omega$ respectively. Allowing a brush drop of 1 V each brush, calculate the following :

- (i) Armature current
 (ii) Current per path
 (iii) Generated e.m.f.
 (iv) Power output of D.C. armature.

Solution. Number of poles,

$$p = 4$$

Total lamp load,

$$p = 50 \times 100 = 5000\ \text{W}$$

Terminal voltage,

$$V = 200\ \text{Volts}$$

Field resistance,

$$R_{sh} = 50\ \Omega$$

Armature resistance,
Voltage drop/brush
Refer Fig. 20.

$$R_a = 0.2 \Omega \\ = 1 \text{ V}$$

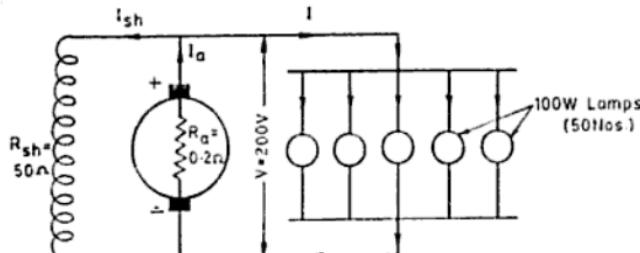


Fig. 20

(i) Armature current, I_a :

$$\text{Load current, } I = \frac{\text{power consumed}}{\text{terminal voltage}} = \frac{P}{V} = \frac{5000}{200} = 25 \text{ A}$$

$$\text{Shunt field current, } I_{sh} = \frac{V}{R_{sh}} = \frac{200}{50} = 4 \text{ A}$$

$$\therefore \text{Armature current, } I_a = I + I_{sh} = 25 + 4 = 29 \text{ A. (Ans.)}$$

(ii) Current per path:

$$\text{Current per path} = \frac{I_a}{a} = \frac{29}{4} \quad [\because a = p = 4, \text{ generator being lap wound}] \\ = 7.25 \text{ A. (Ans.)}$$

(iii) Generated e.m.f., E_g :

$$E_g = V + I_a R_a + \text{brush drop} = 200 + 29 \times 0.2 + 2 \times 1 = 207.8 \text{ V}$$

$$\text{Hence, generated e.m.f.} = 207.8 \text{ V. (Ans.)}$$

(iv) Power output of D.C. armature:

$$\text{Power output of D.C. armature} = \frac{E_g I_a}{1000} = \frac{207.8 \times 29}{1000} \text{ kW} = 6.026 \text{ kW. (Ans.)}$$

Example 7. A series generator delivers a current of 100 A at 250 V. Its armature and series field resistances are 0.1Ω and 0.055Ω respectively. Find :

(i) Armature current

(ii) Generated e.m.f.

Solution. See Fig. 21.

$$\text{Load current, } I = 100 \text{ A}$$

$$\text{Terminal voltage, } V = 250 \text{ Volts}$$

$$\text{Armature resistance, } R_a = 0.1 \Omega$$

$$\text{Series field resistance, } R_{se} = 0.055 \Omega$$

(i) Armature current, I_a :

$$\text{Armature current } (I_a) = \text{load current } (I)$$

$$\therefore I_a = 100 \text{ A. (Ans.)}$$

(ii) Generated e.m.f.:

$$\text{Generated e.m.f. } E_g = V + I(R_a + R_{se}) \\ = 250 + 100(0.1 + 0.055) = 265.5 \text{ V}$$

$$\text{Hence, generated e.m.f.} = 265.5 \text{ V. (Ans.)}$$

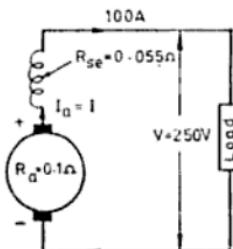


Fig. 21

Example 8. A short shunt compound generator has armature, series field and shunt field resistances of $0.06\ \Omega$, $0.03\ \Omega$ and $110\ \Omega$ respectively. It supplies 100 lamps rated at 250 V, 40 W. Find the generated e.m.f. Assume that contact drop/brush = 1 V.

Solution. See Fig. 22.

Armature resistance, $R_a = 0.06\ \Omega$

Series field resistance, $R_{se} = 0.03\ \Omega$

Shunt field resistance, $R_{sh} = 110\ \Omega$

Terminal voltage, $V = 250$ Volts

Lamp load, $P = 100 \times 40 = 4000$ W

Contact drop/brush = 1 V

Generated e.m.f., E_g :

$$\text{Load current, } I = \frac{P}{V} = \frac{4000}{250} = 16\ \text{A}$$

Voltage drop in series winding

$$= IR_{se} = 16 \times 0.03 = 0.48\ \text{V}$$

Voltage across shunt field winding = $V + IR_{se} = 250 + 0.48 = 250.48$ V

$$\text{Shunt field current, } I_{sh} = \frac{250.48}{110} = 2.277\ \text{A}$$

$$\text{Armature current, } I_a = I + I_{sh} = 16 + 2.277 = 18.277\ \text{A}$$

$$\text{Generated e.m.f., } E_g = V + IR_{se} + I_a R_a + \text{brush drop}$$

$$= 250 + 0.48 + 18.277 + 0.06 + 2 \times 1 = 253.58\ \text{V. (Ans.)}$$

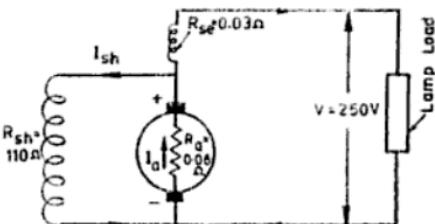


Fig. 22

Example 9. A long shunt compound generator has an armature, series field and shunt field resistances of $0.04\ \Omega$, $0.03\ \Omega$ and $200\ \Omega$ respectively. It supplies a load current of 180 A at 400 V. Calculate the generated e.m.f. Assume contact drop/brush = 1 V.

Solution. Refer Fig. 23.

Armature resistance, $R_a = 0.04\ \Omega$

Series field resistance, $R_{se} = 0.03\ \Omega$

Shunt field resistance, $R_{sh} = 200\ \Omega$

Load current, $I = 180\ \text{A}$

Terminal voltage, $V = 400$ Volts

Contact drop/brush = 1 V

Generated e.m.f., E_g :

$$\text{Shunt current, } I_{sh} = \frac{V}{R_{sh}} = \frac{400}{200} = 2\ \text{A}$$

$$\text{Armature current, } I_a = I + I_{sh} \\ = 180 + 2 = 182\ \text{A}$$

$$\begin{aligned} \text{Generated e.m.f., } E_g &= V + I_a R_a + I_a R_{se} + \text{drop at brushes} \\ &= 400 + 182 \times 0.04 + 182 \times 0.03 + 2 \times 1 \\ &= 400 + 7.28 + 5.46 + 2 = 414.74\ \text{V} \end{aligned}$$

Hence, generated e.m.f. = 414.74 V. (Ans.)

1.4. Parallel Operation of D.C. Generators

1.4.1. Reasons for paralleling D.C. generators

The reasons for paralleling D.C. generators, (especially when it is recognised that this usage of the word parallel means *duplicator or multiple*) are enumerated below :

1. Reliability. The sources of power such as generators are frequently primary safety items and are therefore duplicated or paralleled for *reliability*.

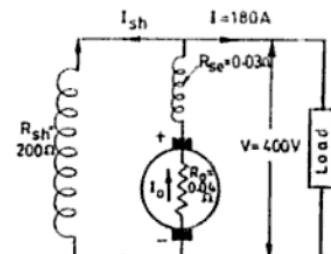


Fig. 23

2. Continuity of service. In case of *break-down* or *routine maintenance* it is frequently required that the device being worked on be *isolated* from its work and *shut down*. Therefore, if power sources are paralleled, the routine or emergency operations can be performed without disturbing the load conditions. This affects both safety and economy.

3. Efficiency. It is a known fact that many major types of machinery, such as generators, run most efficiently when loaded to their design rating. *Electric power costs less per kWh when the generator producing it is efficiently loaded.* Therefore, when the load is reduced, one or more generators can be shut down and the remaining units kept efficiently loaded.

4. Added capacity. The use of electricity is constantly increasing in the modern world of expanding population, goods and services. When *added capacity* is required, the new equipment can be simply paralleled with the old.

5. In several situations (not confined to generators), the equipment available to do a particular task may not be available in a sufficiently large *capacity* or *size* in a single unit. Here paralleling must be a design feature just to meet original load requirement. An absolute unit to the size and output capacity of a D.C. generator does not seem apparent, but in any endeavour a new largest size is always more expensive and usually has unforeseen 'bugs', which may be ruinously costly.

Note. Power sources are rarely duplicated in home or automobile service, but usually are in air craft, marine, rail and industrial use.

1.4.2. Requirements or paralleling D.C. generators

The following are the principal types of situations where paralleling of D.C. generators is required :

- Paralleling shunt generators of the same or varying sizes.
- Paralleling compound generators of the same or varying sizes.

There are certain requirements that must be met for successful electrical paralleling in all different situations. A *parallel circuit is defined as one in which the same voltage exists across each unit as the paralleling point* :

This is absolutely required by Kirchhoff's voltage law.

The following **three conditions** may be met if the generated voltages of the individual generators are not all the same, and they are paralleled :

(i) If a generator is developing an internally generated voltage E_g that is appreciably above the voltage at the paralleling point, *generator action* is taking place and the *unit is delivering current to the load*.

(ii) When a generator is producing the *same* voltage as that existing at the paralleling point, no effective generating action is taking place and *no current is flowing to the load*. The *generator is said to be 'floating' on the line*. It is neither contributing nor drawing current and is still being rotated by its own prime-mover.

(iii) If the setting of the generator is so made that it develops less internal E_g than voltage at the paralleling terminal, it will *draw current* from the paralleling point and will be *operating as 'motor'*.

The above three situations are in entire agreement with Kirchhoff's current law, as any parallel circuit must be.

The following are the requirements or conditions of paralleling D.C. generators :

1. *The polarities of the generators must be the same or the connections must be interchanged until they are.*

2. *The voltages should be nearly if not exactly identical so that each machine will contribute.*

3. *The change of voltage with change of load should be of the same character.*

A positive regulation machine cannot usefully combine with a negative regulation machine. Circulating currents would dominate the situation. An exact match of characteristics is desirable but not always achieved.

4. The prime-movers that drive the generators should have similar and stable rotational speed characteristics. The prime-movers should either all be such that they have constant or flat rotational characteristics or should all droop in speed with increasing load. A rising speed characteristics with increasing load is *unstable* and will cause the affected machine to take more than its share, or even, all of the load.

Note. Whenever generators are in parallel their +ve and -ve terminals are respectively connected to the +ve and -ve sides of the bus-bars. These *bus-bars* are heavy thick copper bars and they act as +ve and -ve terminals for the whole power station.

1.5. Direct Current Motor

1.5.1. General aspects

The electric motor is a machine which converts electric energy into mechanical energy. It depends for its operation on the force which is known to exist on a conductor carrying current while situated in a magnetic field.

Construction. A D.C. motor is similar in construction to a D.C. generator. As a matter of fact any D.C. generator will run as a motor when its field and armature windings are connected to a source of direct current. The field winding produces the necessary magnetic field. *The flow of current through the armature conductors produces a force which rotates the armature.*

Though the essential construction of D.C. motor is identical to that of a generator, the *external appearance of a motor may be somewhat different from that of a generator.* This is mainly due to the fact that the *frame of a generator may be partially open* because it is located in relatively clean environment and only skilled operators are present in its vicinity. A motor, on the other hand, may be operating in a rather dusty environment and only unskilled operators may be working in its vicinity. Therefore, frames of motors are to a large extent closed.

The body of *D.C. mill motors* is made in two halves bolted together for easy access to the field windings and inter-poles.

Applications. Because of their inherent characteristics D.C. motors find extensive application in :

- | | |
|---|-----------------------|
| (i) Steel plants | (ii) Paper mills |
| (iii) Textile mills | (iv) Printing presses |
| (v) Cranes | (vi) Winches |
| (vii) Excavators etc. where precise and accurate speed control over a wide range is required. | |

Advantages. The D.C. motors possess the following *advantages* :

- (i) High starting torque.
- (ii) Speed control over a wide range, both below and above the normal speed.
- (iii) Accurate stepless speed control with constant torque.
- (iv) Quick starting, stopping, reversing and accelerating.

Disadvantages. The *disadvantages* of D.C. motors are :

- (i) High initial cost.
- (ii) Increased operating and maintenance costs because of the commutators and brushgear.

1.5.2. Principle of operation of D.C. motor

The principle of motor action can be stated as follows :

"Whenever a current carrying conductor is placed in a magnetic field, it experiences a force whose direction is given by Fleming's left hand rule".

- Fig. 24 illustrates this principle.

Fig. 24 (a) shows the field set up by the poles.

Fig. 24 (b) shows the conductor field due to flow of current in the conductor.

Fig. 24 (c) shows the resultant field produced when the current carrying conductor wire of Fig. 24 (b) is inserted in the air gap of Fig. 24 (a) with the axis of the conductor at right angles to the direction of the flux.

On the upper side of the conductor in Fig. 24 (c) the magnetizing forces of the field and of the current in the conductor are additive while on the lower side these are subtractive. This explains why the resultant field is strengthened above and weakened below the conductor (wire).

The above experiment shows that the wire in Fig. 24 (c) has a force on it which tends to move it downward. Thus the force acts in the direction of the weaker field. When the current in the wire is reversed, the direction of the force is also reversed, as in Fig. 24 (d).

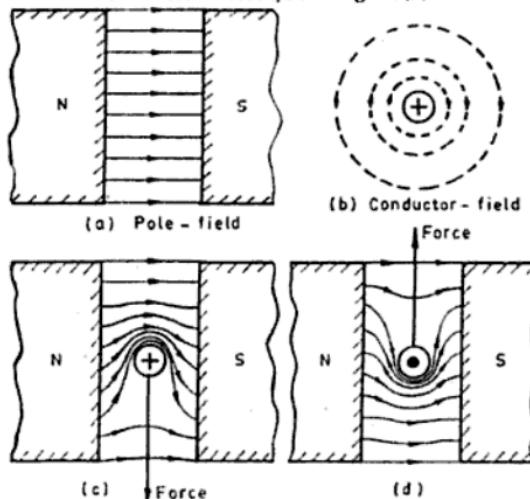


Fig. 24. The principle of motor action.

The force (F) developed in the conductor is given by the relation,

$$F = BIl \text{ newtons}$$

where B = flux density, T (Wb/m^2),

I = current in conductor, A , and

l = exposed length of conductor, m .

Now consider the magnetic field of a D.C. motor in which there is no current in the armature conductors ; the lines of force will be distributed as shown in Fig. 25.

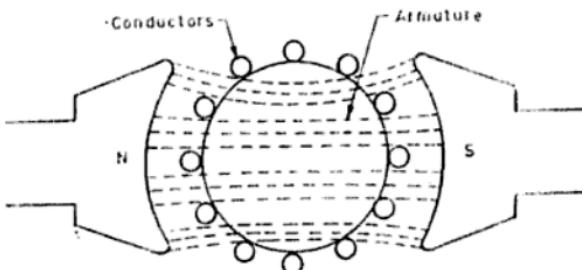


Fig. 25. Distribution of lines of force in a motor due to magnetic field only.

If, now, the armature carries current, each of its conductors will produce a magnetic field which, when super-imposed on the main field, causes a distribution of magnetic lines as shown in Fig. 26.

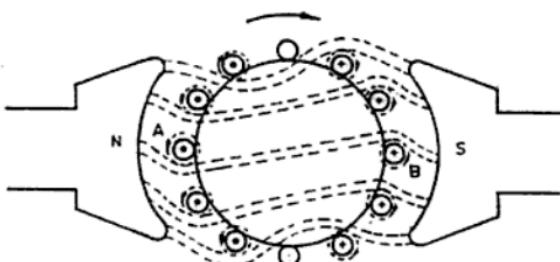


Fig. 26. Distribution of lines of force in a motor, on load, due to the armature and magnetic field.

The magnetic field is said to be distorted, since the lines of force no longer follow approximately straight paths.

These lines of force have the *property of tending to shorten themselves*, so that they may be regarded as being in tension. Each conductor in Fig. 26 will experience a force like that exerted on a stone in a catapult. Since these conductors are embedded in slots in the armature, the latter is caused to rotate in a clockwise direction.

1.5.3. Back or counter E.M.F.

Refer Fig. 27. In a D.C. motor when the armature rotates, the conductors on it cut the lines of force of magnetic field in which they revolve, so that an e.m.f. is induced in the armature as in a generator. The induced e.m.f. acts in opposition to the current in the machine and, therefore, to the applied voltage, so that it is customary to refer to this voltage as the 'back e.m.f.' That this is so can be deduced by Lenz's law, which states that the direction of an induced e.m.f. is such as to oppose the change causing it, which is, of course, the applied voltage.

The magnitude of the back or counter e.m.f. can be calculated by using formula for the induced e.m.f. in a generator, and

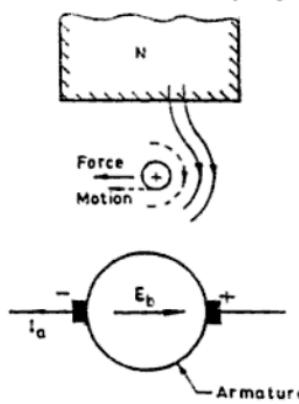


Fig. 27. Motoring operation.

it is important in the case of the motor, to appreciate that this is proportional to the product of the flux and the speed. Thus if E_b denotes the back e.m.f., ϕ the flux and N the speed, we may write,

$$E_b = k \phi N$$

where k is a number depending on nature of armature winding.

The value of back e.m.f. (E_b) is always less than the applied voltage, although difference is small when the machine is running under normal conditions. It is the difference between these two quantities which actually drives current through the resistance of the armature circuit. If this resistance is represented by R_a , the back e.m.f. by E_b and the applied voltage by V , then we have

$$V = E_b + I_a R_a$$

where I_a is the current in the armature circuit.

1.5.4. Comparison between motor and generator action

- Fig. 28 (b) shows a generator action, where a mechanical force moves a conductor in upward direction inducing an e.m.f. in the direction shown. When a current flows as a result of this e.m.f., there is a current-carrying conductor existing in a magnetic field; hence motor action occurs. Shown as a dotted line in Fig. 28 (b), the *force developed as a result of motor action opposes the motion which produced it*.

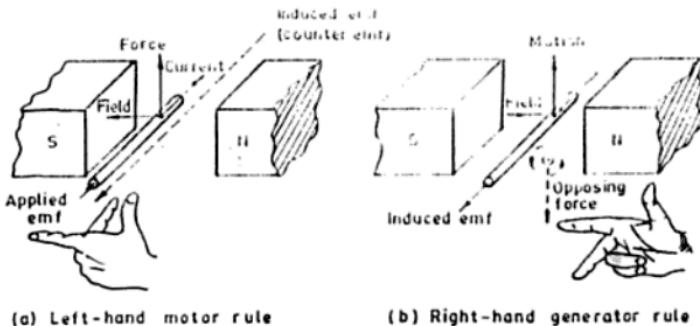


Fig. 28. Comparison of motor and generator action.

Thus it can be stated categorically that in rotating electric machines *generator action and motor action occur simultaneously*. Hence the same dynamo may be operated either as a motor or a generator or both (as in dynamo motor or synchronous converter).

- Fig. 29 presents a more graphic representation in terms of rotational elements, which compares the elementary motor and generator for the same direction of rotation and shows the electric circuits of each which is self-explanatory.

It may be noted that when a dynamo is operating as a *motor*, the generated e.m.f. is *always less than the terminal voltage* (that produces motor action) and it *opposes the armature current*. On the other hand when a dynamo is operating as a *generator*, the *armature current is in the same direction as the generated e.m.f.*, and the *generated e.m.f. E_g exceeds the terminal voltage V applied across the load*. This distinction between generator and motor, in which the armature-generator voltage aids or opposes the armature current, respectively give rise to the following basic armature circuit equations :

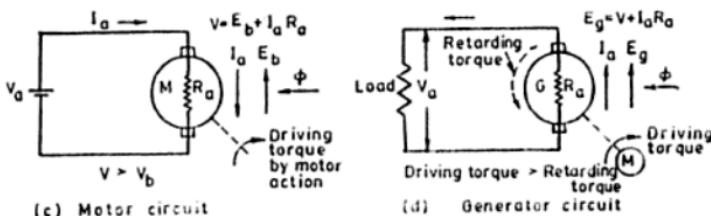
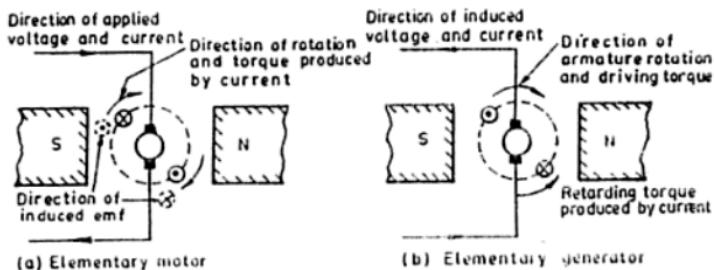


Fig. 29. Elementary motor action versus generator action.

$$\text{For a motor, } V = E_b + I_a R_a \quad \dots(2)$$

$$\text{For a generator, } E_g = V + I_a R_a \quad \dots(3)$$

where V = applied voltage (measurable terminal voltage) across the armature,

E_b = back or counter e.m.f. developed in the armature of the motor,

E_g = generated e.m.f. developed in the generator armature, and

$I_a R_a$ = armature voltage drop due to a flow of armature current through an armature of a given resistance, R_a .

1.5.5. Torque developed in a motor

When the field of a machine (of the type described as generator) is excited and a potential difference is impressed upon the machine terminals, the current in the armature winding reacts with the air-gap flux to produce a turning moment or *torque* which tends to cause the armature to revolve. Fig. 30 illustrates production of torque in a motor.

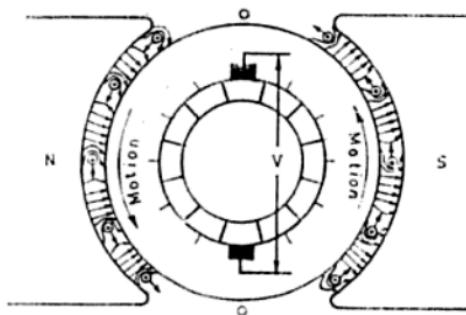


Fig. 30. Production of torque in a D.C. motor.

When the brushes are on the neutral axis, all the armature conductors lying under the north pole carry currents in a *given direction*, while those lying under south pole carry currents in the *reverse direction*. The commutator (just as in a generator) serves to reverse the current in each armature coil at the instant it passes through the neutral axis, so the above relation is always maintained as the armature rotates.

All conductors under the north pole carry inward-flowing currents which react with the air gap flux to produce down-ward acting forces and a counter clockwise torque. Similarly the conductors under the south pole carry outward-flowing currents which produce upward-acting forces. These forces also give rise to counter clockwise torques. If the air-gap flux is assumed to be radially directed at all points, each of the force acts tangentially and produces a turning moment equal to the force multiplied by its lever arm—the radial distance from the centre of the conductor to the centre of the shaft.

Magnitude of torque developed by each conductor

$$= BIlr \text{ Nm}$$

If the motor contains Z conductors, the total torque developed by the armature

$$T_a = BIlrZ \text{ Nm} \quad \dots(4)$$

where B = gap density, T (Wb/m²)

I = armature current in a conductor, A

l = active length of each conductor, m

r = average lever arm of a conductor or the average radius at which conductors are placed, m

Z = total number of armature conductors.

It is more convenient to express T_a in terms of armature current I_a , total flux per pole ϕ and number of poles p .

$$I = \frac{I_a}{a}$$

and

$$B = \frac{\phi}{A}$$

where a = number of parallel paths,

and A = the cross-sectional area of flux path at radius r .

$$A = \frac{2\pi r l}{p}$$

$$\begin{aligned} \text{Then } T_a &= \frac{Z\phi I_a r}{2\pi r l} \times \frac{p}{a} \\ &= \frac{Z\phi I_a p}{2\pi a} \text{ Nm} \end{aligned}$$

i.e.

$$T_a = 0.159 Z \phi p \times \frac{I_a}{a} \quad \dots(5)$$

or

$$T_a = k \phi I_a \text{ Nm} \quad \dots(6)$$

where $k = \frac{Zp}{2\pi a}$ is a constant for any machine.

Alternative proof :

The expression for the torque developed by the motor armature may also be deduced as follows :

Let T_a be the torque developed in Nm by the motor armature running at N r.p.m.

$$\begin{aligned} \text{Power developed} &= \text{work done per second} \\ &= T_a \times 2\pi N \text{ watts} \end{aligned} \quad \dots(i)$$

Electrical equivalent of mechanical power developed by the armature also

$$= E_b I_a \text{ watts} \quad \dots(ii)$$

Equating (i) and (ii), we get

$$T_a \times \frac{2\pi N}{60} = E_b I_a$$

or

$$T_a = \frac{E_b I_a}{2\pi \left(\frac{N}{60} \right)}$$

Also since

$$E_b = \frac{\mu \phi Z N}{60 \alpha}$$

$$\therefore T_a \times 2\pi \frac{N}{60} = \frac{\mu \phi Z N}{60 \alpha} \cdot I_a$$

or

$$T_a = \frac{Z \phi p}{2\pi} \cdot \frac{I_a}{a} \text{ Nm}$$

i.e.

$$T_a = 0.159 Z \phi p \cdot \frac{I_a}{a}.$$

Note. From the above equation for torque, we find that

$$T \propto \phi I_a$$

Then

(i) In the case of shunt motors, ϕ is practically constant,

hence

$$T \propto I_a$$

(ii) In the case of series motors, ϕ is proportional to I_a before saturation (because field windings carry full armature current)

$$\therefore T \propto I_a^2.$$

Shaft torque (T_{sh}). The torque developed by the armature is the *gross torque*. Whole of this torque is not available at the pulley, since certain percentage of torque developed by the armature is lost to overcome the iron and friction losses. *The torque which is available for useful work is known as shaft torque T_{sh} .* It is so called because it is *available at the shaft*. The horse power obtained by using shaft torque is called brake horse power (B.H.P.).

$$\text{B.H.P. (metric)} = \frac{T_{sh} \times 2\pi N}{735.5}$$

$$\therefore T_{sh} = \frac{\text{B.H.P. (metric)} \times 735.5}{\frac{2\pi N}{60}} \quad \dots(7)$$

where N = speed of armature in r.p.m.

The difference $T_a - T_{sh}$ is known as **lost torque** (i.e. torque lost in iron and friction losses)

$$= 0.159 \times \frac{\text{iron and friction losses}}{\frac{N}{60}} \text{ Nm.}$$

1.5.6. Mechanical power developed by motor armature

Refer Fig. 31. The voltage V applied across the motor armature has to (i) overcome back e.m.f. E_b and (ii) supply the armature ohmic drop $I_a R_a$.

$$\therefore V = E_b + I_a R_a$$

This is known as *voltage equation of a motor*.

Multiplying both sides by I_a , we get

$$VI_a = E_b I_a + I_a^2 R_a$$

Here VI_a = electrical input to the armature,

$E_b I_a$ = electrical equivalent of mechanical power P_m developed in the armature, and

$I_a^2 R_a$ = copper loss in the armature.

The power available at the pulley for doing useful work is *somewhat less than the mechanical power developed by the armature*.

This is evident, since there are certain *mechanical losses* (such as bearing and windage friction and iron losses) that must be supplied by the driving power of the motor.

Condition for maximum power. We know that, the mechanical power developed by the motor,

$$P_m = VI_a - I_a^2 R_a$$

Differentiating both sides with respect to I_a

$$\frac{d(P_m)}{dI_a} = V - 2I_a R_a = 0$$

$$\therefore I_a R_a = \frac{V}{2}$$

$$\text{As } V = E_b + I_a R_a$$

$$\therefore V = E_b + \frac{V}{2}$$

$$\text{i.e. } E_b = \frac{V}{2}$$

...(8)

Hence, *mechanical power developed by a motor is maximum when back e.m.f. is equal to half the applied voltage*. In practice, however, *this condition is not realized because in that case current would be much beyond the normal current of the motor. Moreover, half the input would be wasted in the form of heat and taking other losses, such as mechanical and magnetic, into consideration, the efficiency of the motor will be below 50 per cent*.

1.5.7. Types of D.C. motors

There are three main types of motors characterised by the connection of the field winding in relation to the armature. These are :

1. **Shunt wound motor** or the shunt motor, in which the *field winding is connected in parallel with the armature*.

2. **Series motor**, in which the *armature and field windings are connected in series*.

3. **Compound motor**, which has two field windings, *one of which is connected in parallel with the armature and the other in series with it*.

Shunt wound motor. Fig. 32 shows the connections of a shunt motor. From these connections it may be observed at once that the *field current is constant*, since it is connected directly to the supply which is assumed to be at constant voltage. Hence the flux is approximately constant and, since also the *back e.m.f. is almost constant under normal conditions the speed is approximately constant*. This

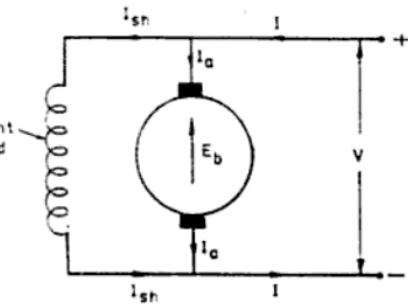


Fig. 31

is not strictly true, but nevertheless, it is usual for all practical purposes to regard the shunt motor as a constant speed machine. It is, therefore, employed in practice for drives, the speeds of which are required to be independent of the loads. The speed can, of course, be varied when necessary and this is done by the inclusion of a variable resistor in series with the field winding, as shown in Fig. 32.

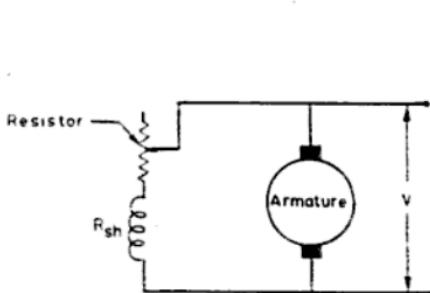


Fig. 32. Connections of a shunt motor.

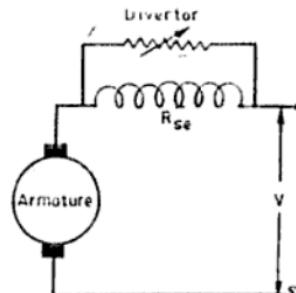


Fig. 33. Connections of a series motor.

Series motor. Fig. 33 shows the connections for the series motor. The current passing through the field winding is the same as that in the armature, since the armature current increases as the mechanical load on the shaft increases, so also does the field current. The resultant increase in magnetic flux causes a reduction in the speed, as can be observed from a consideration of the formula :

$$E_b = \frac{p_0 Z N}{60a}$$

or

$$E_b = k \phi N$$

where $k = \frac{pZ}{60a}$ being constant

or

$$N = \frac{E_b}{k \phi} .$$

This is a useful property for many drives in which it is desirable that a heavy increase in the load should automatically bring about a compensating reduction in speed. As with the shunt motor, the speed may also be varied independently of the load by the inclusion of a variable resistor in the field circuit. In this case, however, it is connected in parallel with the series winding as shown in Fig. 33, and is called a *divertor compound motor*.

Refer Fig. 34. The compound motor has a shunt field winding in addition to the series winding so that the number of magnetic lines of force produced by each of its poles is the resultant of the flux produced by the shunt coil and that due to the series coil. The flux so produced depends not only on the current and number of turns of each coil, but also on the winding direction of the shunt coil in relation to that of the series coil. When the two fluxes assist each other the machine is a **cumulative compound motor**, while if they oppose each other, it is said to be a **differential compound motor**.

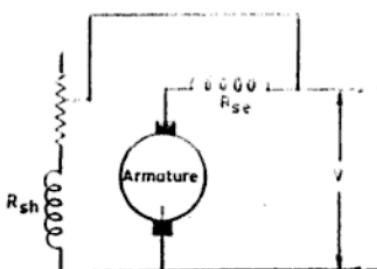


Fig. 34. Connections of a compound motor.

I_{a1} = armature current in the first case, and
 ϕ_1 = flux in the first case.

N_2 , I_{a2} and ϕ_2 = corresponding quantities in the second case.

Using the above relation $\left(i.e. N \propto \frac{E_b}{\phi} \right)$, we get

$$N_1 \propto \frac{E_{b1}}{\phi_1}$$

$$N_2 \propto \frac{E_{b2}}{\phi_2}$$

and where $E_{b1} = V - I_{a1}R_a$

and $E_{b2} = V - I_{a2}R_a$

$$\therefore \frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2} \quad \dots(10)$$

Prior to saturation of poles :

$$\begin{aligned} \phi &\propto I_a \\ \therefore \frac{N_2}{N_1} &= \frac{E_{b2}}{E_{b1}} \times \frac{I_{a1}}{I_{a2}} \end{aligned} \quad \dots[10(a)]$$

For shunt motor :

Applying the same equation in this case also, we get

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$

If

$$\begin{aligned} \phi_1 &= \phi_2 \\ \frac{N_2}{N_1} &= \frac{E_{b2}}{E_{b1}}. \end{aligned} \quad \dots(11)$$

1.5.9. Speed regulation

The speed regulation of a D.C. motor is defined as follows :

"The change in speed when the load on the motor is reduced from rated value to zero, expressed as percent of the rated load speed."

$$\therefore \text{Percent speed regulation} = \frac{\text{no load speed} - \text{full load speed}}{\text{full load speed}}.$$

Shunt Motors

Example 10. Determine the torque developed when a current of a 30 A passes through the armature of a motor with the following particulars : lap winding, 310 conductors, 4-pole, pole-shoes 16.2 cm long subtending an angle of 60° at the centre, bore radius 16.2 cm, flux density in air gap 0.7 tesla.

Solution. Number of poles,

$$p = 4$$

Number of parallel paths,

a = p = 4

[Motor being lap-wound]

Number of armature conductors,

Z = 310

Length of pole shoe

= 16.2 \text{ cm}

Bore radius

= 16.2 \text{ cm}

Flux density in air gap,

B = 0.7 \text{ tesla}

Armature current,

I_a = 30 \text{ A}

Torque developed, T :

We know that,

$$\text{Pole-shoe arc} = \pi D \times \frac{60}{360} = \pi(2 \times 16.2) \times \frac{60}{360} = 16.967 \text{ cm}$$

$$\therefore \text{Pole area} = \text{pole-shoe length} \times \text{pole-shoe arc} \\ = (16.2 \times 10^{-2}) \times (16.967 \times 10^{-2}) \\ = 16.2 \times 16.967 \times 10^{-4} \text{ m}^2 = 0.02748 \text{ m}^2$$

Also flux,

$$\phi = B \times \text{pole area} \\ = 0.7 \times 0.02748 = 0.01924 \text{ Wb}$$

Using the relation,

$$T = 0.159 Z \phi p \left(\frac{I_a}{a} \right) = 0.159 \times 310 \times 0.01924 \times 4 \times \frac{30}{4} \\ = 28.45 \text{ Nm.}$$

Hence, torque developed = 28.45 N.m. (Ans.)

Example 11. A 230 V D.C. shunt motor takes 32 A at full load. Find the back e.m.f. on full load if the resistances of motor armature and shunt field windings are 0.2 ohm and 115 ohms respectively.

Solution. Supply voltage, $V = 230$ Volts

$$\text{Full load current, } I = 32 \text{ A}$$

$$\text{Armature resistance, } R_a = 0.2 \text{ ohm}$$

$$\text{Shunt field windings' resistance, } R_{sh} = 115 \text{ ohms}$$

Back e.m.f., E_b :

$$\text{Shunt field current, } I_{sh} = \frac{230}{115} = 2 \text{ A}$$

$$\therefore \text{Armature current, } I_a = I - I_{sh} = 32 - 2 = 30 \text{ A}$$

$$\text{Back e.m.f. on full load, } E_b = V - I_a R_a \\ = 230 - 30 \times 0.2 = 224 \text{ V}$$

Hence, back e.m.f. on full load = 224 V. (Ans.)

Example 12. The power input to a 230 volts D.C. shunt motor is 8.477 kW. The field resistance is 230 Ω and armature resistance is 0.28 Ω. Find the input current, armature current and back e.m.f.

(P.T.U., May, 2001)

Solution. Given : $P_{in} = 8.477 \text{ kW}$; $R_{sh} = 230 \Omega$; $R_a = 0.28 \Omega$

I :: I_a : E_b :

$$\text{Input current, } I = \frac{P_{in}}{V} = \frac{8.477 \times 1000}{230} \\ = 36.86 \text{ A. (Ans.)}$$

$$\text{Shunt field current, } I_{sh} = \frac{V}{R_{sh}} = \frac{230}{230} = 1 \text{ A}$$

$$\therefore \text{Armature current, } I_a = I - I_{sh} \\ = 36.86 - 1 \\ = 35.86 \text{ A. (Ans.)}$$

$$\text{Back e.m.f. } E_b = V - I_a R_a \\ = 230 - 35.86 \times 0.28 = 219.96 \text{ V. (Ans.)}$$

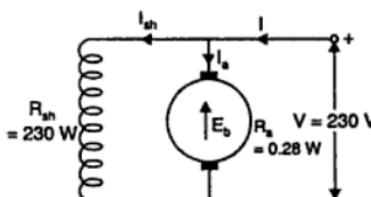


Fig. 37

Example 13. A six-pole lap-connected 230 V shunt motor has 410 armature conductors. It takes 41 A on full load. The flux per pole is 0.05 weber. The armature and field resistances are 0.1 ohm and 230 ohms respectively. Contact drop per brush = 1 V.

Determine the speed of motor at full load.

Solution. Number of poles, $p = 6$

Number of parallel paths, $a = 6$

[Motor being lap-connected]

Number of armature conductors, $Z = 410$

Full load current, $I = 41 \text{ A}$

Flux per pole, $\phi = 0.05 \text{ weber}$

Armature resistance, $R_a = 0.1 \text{ ohm}$

Shunt field resistance, $R_{sh} = 230 \text{ ohms}$

Contact drop/brush = 1 V

Speed of motor on full load, N :

$$\text{Shunt field current, } I_{sh} = \frac{V}{R_{sh}} = \frac{230}{230} = 1 \text{ A}$$

$$\text{Armature current, } I_a = I - I_{sh} = 41 - 1 = 40 \text{ A}$$

$$\begin{aligned} \text{Back e.m.f. on full load, } E_b &= V - I_a R_a - \text{drop at brushes} \\ &= 230 - 40 \times 0.1 - 2 \times 1 = 224 \text{ V} \end{aligned}$$

We know that,

$$E_b = \frac{p\phi Z N}{60a}$$

$$224 = \frac{6 \times 0.05 \times 410 \times N}{60 \times 6}$$

$$\therefore N = \frac{224 \times 60 \times 6}{6 \times 0.05 \times 410} = 655.6 \text{ r.p.m.}$$

Hence, speed of motor on full load = 655.6 r.p.m. (Ans.)

Example 14. A 250 volt d.c. shunt motor, on no load, runs at 1000 rpm and takes 5 A. The field and armature resistances are 250 ohms and 0.25 ohm respectively. Calculate the speed when the motor is loaded such that it takes 41 A if the armature reaction weakens the field by 3%.

[P.T.U., May, 2001]

Solution. Given : $V = 250 \text{ V}$; $N_0 = 1000 \text{ r.p.m.}$; $I_0 = 5 \text{ A}$; $R_{sh} = 250 \Omega$;

$$R_a = 0.25 \Omega, I = 41 \text{ A}, \phi = \left(1 - \frac{3}{100}\right) \phi_0 = 0.97 \phi_0$$

Speed of the motor, N :

$$\text{Shunt current, } I_{sh} = \frac{V}{R_{sh}} = \frac{250}{250} = 1 \text{ A}$$

At no-load :

$$I_0 = 5 \text{ A}; I_{a0} = I_0 - I_{sh} = 5 - 1 = 4 \text{ A}$$

$$E_{b0} = V - I_{a0} R_a = 250 - 4 \times 0.25 = 249 \text{ V}$$

At full-load :

$$I = 41 \text{ A}; I_a = I - I_{sh} = 41 - 1 = 40 \text{ A}$$

$$E_b = V - I_a R_a = 250 - 40 \times 0.25 = 240 \text{ V}$$

$$\text{Using the relation, } \frac{N}{N_0} = \frac{E_b}{E_{b0}} \times \frac{\phi}{\phi_0}$$

or

$$\frac{N}{1000} = \frac{240}{249} \times \frac{\phi_0}{0.97\phi_0}$$

$$\therefore N = 1000 \times \frac{240}{249} \times \frac{1}{0.97} = 993.67 \text{ r.p.m. (Ans.)}$$

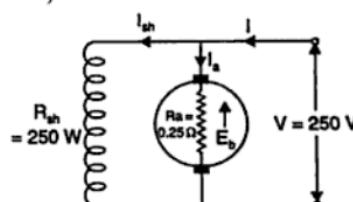


Fig. 38

Example 15. A 120 volt d.c. shunt motor has an armature resistance of 0.2 ohms and a field resistance of 60 ohms. The full-load line current is 60 A and full-load speed is 1800 r.p.m. If the brush contact drop is 3 V, find the speed of the motor at half-load. (P.T.U., June, 2000)

Solution. Given : $V = 120 \text{ V}$; $R_a = 0.2 \Omega$; $R_{sh} = 60 \Omega$

$$I_1 = 60 \text{ A}, N_1 = 1800 \text{ r.p.m.};$$

Brush contact drop = 3 V

Speed of the motor at half-load, N_2 :

$$I_{sh} = \frac{V}{R_{sh}} = \frac{120}{60} = 2 \text{ A}$$

Full load armature current,

$$I_{a1} = I_1 - I_{sh} = 60 - 2 = 58 \text{ A}$$

$$\begin{aligned} \text{Back e.m.f. } E_{b1} &= V - I_{a1} R_a - \text{brush contact drop} \\ &= 120 - 58 \times 0.2 - 3 = 105.4 \text{ V} \end{aligned}$$

$$\text{Armature current at half-load, } I_{a2} = \frac{I_{a1}}{2} = \frac{58}{2} = 29 \text{ A}$$

$$\begin{aligned} \text{Back e.m.f. at half-load, } E_{b2} &= V - I_{a2} R_a - \text{brush contact drop} \\ &= 120 - 29 \times 0.2 - 3 = 111.2 \text{ V} \end{aligned}$$

$$\text{Now, } \frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2} = \frac{E_{b2}}{E_{b1}} \quad [\because \phi_1 = \phi_2 \dots \text{being shunt motor}]$$

$$\therefore \frac{N_2}{1800} = \frac{111.2}{105.4}$$

$$N_2 = \frac{1800 \times 111.2}{105.4} = 1899 \text{ r.p.m. (Ans.)}$$

or

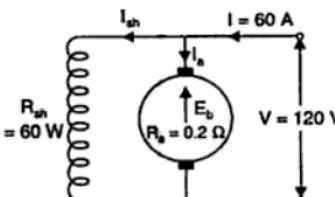


Fig. 39

Example 16. A 4-pole 500 V shunt motor takes 7 A on no-load, the no-load speed being 750 r.p.m. It has a shunt field current of 2 A. Calculate the full-load speed of the motor if it takes 122 A at full-load. Armature resistance = 0.2 ohm. Contact drop/brush = 1 V. Armature reaction weakens the field by 4% on full-load.

Solution. Supply voltage, $V = 500 \text{ Volts}$

$$\text{No-load current, } I_0 = 7 \text{ A}$$

$$\text{No-load speed, } N_0 = 750 \text{ r.p.m.}$$

$$\text{Shunt field current, } I_{sh} = 2 \text{ A}$$

$$\text{Full-load current, } I = 122 \text{ A}$$

$$\text{Armature resistance, } R_a = 0.2 \text{ ohm}$$

$$\text{Contact drop/ brush} = 1 \text{ V}$$

$$\text{Flux at full-load, } \phi = \left(\frac{100 - 4}{100} \right) \phi_0 = 0.96 \phi_0$$

Full-load speed, N :

At no-load :

$$I_{a0} = I_0 - I_{sh} = 7 - 2 = 5 \text{ A}$$

$$\begin{aligned} E_{b0} &= V - I_{a0} R_a - \text{contact drop at brushes} \\ &= 500 - 5 \times 0.2 - 2 \times 1 = 497 \text{ V.} \end{aligned}$$

At full-load :

$$I_a = I - I_{sh} = 122 - 2 = 120 \text{ A}$$

$$\begin{aligned} E_b &= V - I_a R_a - \text{contact drop at brushes} \\ &= 500 - 120 \times 0.2 - 2 \times 1 = 500 - 24 - 2 = 474 \text{ V} \end{aligned}$$

We know that,
and

$$E_{b0} \propto \phi_0 N_0$$

$$E_b \propto \phi N$$

$$\frac{E_b}{E_{b0}} = \frac{\phi}{\phi_0} \times \frac{N}{N_0}$$

$$\frac{474}{497} = \frac{0.96\phi_0}{\phi_0} \times \frac{N}{750}$$

$$\therefore N = \frac{474 \times 750}{497 \times 0.96} = 745 \text{ r.p.m. (app.)}$$

Hence, full-load speed of the motor = 745 r.p.m. (app.) (Ans.)

Example 17. A 440 V, 4-pole, lap connected shunt motor has a no-load input current of 15 A and a shunt field current of 10 A. At full-load it takes a current of 150 A. If armature resistance = 0.1 ohm, flux per pole on no-load = 0.05 weber, number of armature conductors = 750 and contact drop per brush = 1 V, calculate :

(i) No-load speed

(ii) Full-load speed

(iii) Speed regulation.

Armature reaction weakens the field by 1.5% on full-load.

Solution. Supply voltage, $V = 440$ Volts

Number of poles, $p = 4$

Number of parallel paths, $a = p = 4$

[Motor being lap-connected]

Armature resistance, $R_a = 0.1$ ohm

Flux per pole on no-load, $\phi_0 = 0.05$ weber

Number of armature conductors, $Z = 750$

Contact drop per brush, $= 1$ V

No-load input current, $I_0 = 15$ A

Shunt field current, $I_{sh} = 10$ A

Full-load current, $I = 150$ A

No-load speed, N_0 :

Full-load speed, N :

Speed regulation :

(i) **No-load speed :**

Armature current, $I_{a0} = I_0 - I_{sh} = 15 - 10 = 5$ A

$$E_{b0} = V - I_{a0}R_a - \text{brush contact drop}$$

$$= 440 - 5 \times 0.1 - 2 \times 1 = 437.5 \text{ V}$$

Using the relation : $E_{b0} = \frac{p\phi_0 Z N_0}{60a}$

or

$$437.5 = \frac{4 \times 0.05 \times 750 \times N_0}{60 \times 4}$$

$$\therefore N_0 = \frac{437.5 \times 60 \times 4}{4 \times 0.05 \times 750} = 700 \text{ r.p.m.}$$

Hence, no-load speed = 700 r.p.m. (Ans.)

(ii) **Full-load speed :**

Armature current, $I_a = I - I_{sh} = 150 - 10 = 140$ A

$E_b = V - I_a R_a - \text{brush contact drop}$

$$= 440 - 140 \times 0.1 - 2 \times 1 = 424 \text{ V}$$

$$\phi = (1 - 0.015) \phi_0$$

[Since armature reaction weakens the field by 1.5 per cent]

$$= 0.985 \phi_0$$

$$\text{Using the relation : } \frac{N}{N_0} = \frac{E_b}{E_{b0}} \times \frac{\phi_0}{\phi}$$

$$\text{or } \frac{N}{700} = \frac{424}{437.5} \times \frac{\phi_0}{0.985\phi_0}$$

$$\therefore N = 700 \times \frac{424}{437.5} \times \frac{\phi_0}{0.985\phi_0} = 688.73 \text{ r.p.m.}$$

Hence, full-load speed = 688.73 r.p.m. (Ans.)

(iii) Percentage speed regulation

$$\begin{aligned} &= \frac{\text{no-load speed} - \text{full-load speed}}{\text{full-load speed}} \times 100 \\ &= \frac{700 - 688.73}{688.73} \times 100 = 1.637 \end{aligned}$$

Hence, percentage speed regulation = 1.637%. (Ans.)

Example 18. A 250 V shunt motor takes a line current of 60 A and runs at 800 r.p.m. Its armature and field resistances are 0.2 ohm and 125 ohms respectively. Contact drop/brush = 1 V. Calculate :

(i) No-load speed if the no-load current is 6 A.

(ii) The percentage reduction in the flux per pole in order that the speed may be 1000 r.p.m. when the armature current is 40 A.

Neglect the effects of armature reaction.

Solution. Supply voltage, $V = 250$ Volts

Load current, $I_1 = 60$ A

Load speed, $N_1 = 800$ r.p.m.

Armature resistance, $R_a = 0.2$ ohm

Shunt field resistance, $R_{sh} = 125$ ohms

Contact drop, $= 2$ V

Armature current, $I_{a2} = 40$ A

Load speed, $N_2 = 1000$ r.p.m.

No-load current, $I_0 = 6$ A

No-load speed, N_0 :

Percentage reduction in flux/pole :

$$\text{Shunt field current, } I_{sh} = \frac{250}{125} = 2 \text{ A}$$

At no-load :

$$I_{a0} = I_0 - I_{sh} = 6 - 2 = 4 \text{ A}$$

$$\begin{aligned} E_{b0} &= V - I_{a0}R_a - \text{brush drop} \\ &= 250 - 4 \times 0.2 - 2 \times 1 = 247.2 \text{ V} \end{aligned}$$

At load ($I_1 = 60$ A) :

$$I_{a1} = I_1 - I_{sh} = 60 - 2 = 58 \text{ A}$$

$$E_{b1} = V - I_{a1}R_a - \text{brush drop}$$

$$= 250 - 58 \times 0.2 - 2 \times 1 = 236.4 \text{ V}$$

(ii) Speed of motor, N :

$$E_b = V - I_a(R_a + R_m)$$

$$= 240 - 101.56(0.2 + 0.02) = 217.66 \text{ V}$$

But

$$\frac{E_b}{N} = 0.33$$

[Already calculated above]

∴

$$N = \frac{E_b}{0.33} = \frac{217.66}{0.33} = 659.6 \text{ r.p.m.}$$

Example 23. A six-pole, lap-wound 400 V series motor has the following data : Number of armature conductors = 920, flux/pole = 0.045 Wb, total motor resistance = 0.6 ohm, iron and friction losses = 2 kW. If the current taken by the motor is 90 A, find :

(i) Total torque ;

(ii) Useful torque at the shaft ;

(iii) Power output ;

(iv) Pull at the rim of a pulley of 40 cm diameter connected to the shaft.

Solution. Number of poles,

$$p = 6$$

Supply voltage,

$$V = 400 \text{ Volts}$$

Number of parallel paths,

$$a = p = 6$$

[Motor being lap-wound]

Number of armature conductors, $Z = 920$

Flux/pole,

$$\phi = 0.045 \text{ Wb}$$

Motor resistance,

$$R_m = 0.6 \text{ ohm}$$

Iron and friction losses

$$= 2 \text{ kW or } 2000 \text{ W}$$

Current taken by the motor, $I_a = 90 \text{ A}$

$$= 40/2 = 20 \text{ cm or } 0.2 \text{ m}$$

Radius of the pulley,

$$E_b = V - I_a R_m = 400 - 90 \times 0.6$$

Using the relation,

$$= 346 \text{ V}$$

Also,

$$E_b = \frac{p\phiZN}{60a}$$

$$346 = \frac{6 \times 0.045 \times 920 \times N}{60 \times 6}$$

∴

$$N = \frac{346 \times 60 \times 6}{6 \times 0.045 \times 920} = 501 \text{ r.p.m.}$$

(i) Total torque, T_a :

We know that,

$$T_a = 0.159 \times Z\phi p \times \left(\frac{I_a}{a} \right)$$

$$= 0.159 \times 920 \times 0.045 \times 6 \times \frac{90}{6} = 592.4 \text{ Nm}$$

Hence,

Total torque = 592.04 N-m. (Ans.)

(ii) Useful torque, T_{useful} :

$$T_{\text{lost}} \times \left(\frac{2\pi N}{60} \right) = \text{Iron and friction loss} = 2000 \text{ W}$$

∴

$$T_{\text{lost}} = \frac{2000 \times 60}{2\pi N} = \frac{2000 \times 60}{2\pi \times 501} = 38.11 \text{ Nm}$$

∴

$$T_{\text{useful}} = T_a - T_{\text{lost}} = 592.4 - 38.11$$

$$= 554.29 \text{ Nm}$$

Hence,

useful torque = 554.29 Nm. (Ans.)

(iii) Power output :

$$\begin{aligned}\text{Power output} &= T_{\text{useful}} \left(\frac{2\pi N}{60} \right) = \frac{554.29 \times 2\pi \times 501}{60} \\ &= 29084.4 \text{ or } 29.08 \text{ kW}\end{aligned}$$

Hence, power output = 29.08 kW. (Ans.)

(iv) If F is the pull at the rim of the pulley and r is the radius,

$$\begin{aligned}\text{Torque at the shaft, } T_{\text{useful}} &= F \times r \\ I.e. \quad F \times 0.2 &= 554.29 \\ F &= 2771.45 \text{ N}\end{aligned}$$

Hence, pull at the rim of the pulley = 2771.45 N. (Ans.)

Example 24. A 240 V series motor takes 40 A when giving its rated output at 1500 r.p.m. Its resistance is 0.3 Ω. Find what resistance must be added to obtain rated torque (i) at starting and (ii) at 1000 r.p.m.

Solution. Given : $V = 240$ volts ; $I (= I_a) = 40$ A, $N = 1500$ r.p.m., $R = 0.3$ Ω.

(i) Resistance to be added to obtain rated torque at starting, R_{add} :

Since the torque remains the same in both the cases, it is obvious that the current drawn by the motor remains constant at 40 A.

$$\therefore 40 = \frac{240}{R_{\text{add}} + 0.3}$$

$$\text{or } R_{\text{add}} = \frac{240}{40} - 0.3 = 5.7 \Omega.$$

(ii) Resistance to be added to obtain rated torque at 1000 r.p.m., R_{add} :

We know that,

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$E_{b1} = 240 - 40 \times 0.3 = 228 \text{ V}$$

$$\therefore \frac{1000}{1500} = \frac{E_{b2}}{228}$$

$$\text{or } E_{b2} = \frac{1000 \times 228}{1500} = 152 \text{ V}$$

$$\text{Now } E_{b2} = V - 40(R_{\text{add}} + 0.3) \text{ or } 152 = 240 - 40(R_{\text{add}} + 0.3)$$

$$\therefore R_{\text{add}} = \frac{240 - 152}{40} - 0.3 = 1.9 \Omega. \text{ (Ans.)}$$

Example 25. A 200 V D.C. series motor runs at 700 r.p.m. when operating at its full-load current of 20 A. The motor resistance is 0.5 Ω and the magnetic circuit can be assumed unsaturated. What will be the speed if (i) the load torque is increased by 44% (ii) the motor current is 10 A.

Solution. Given : $V = 200$ volts ; $N_1 = 700$ r.p.m., $I_1 = 20$ A, $R_m = (R_a + R_{sh}) = 0.5$ Ω

Speeds, (N_2 , N_3) :

(i) When the load torque is increased by 44% :

$$T_2 = 1.44 T_1$$

$$\phi_2 I_2 = 1.44 \phi_1 I_1 \quad (\because T \propto \phi I)$$

$$I_2^2 = 1.44 I_1^2 \quad (\because \phi \propto I)$$

or

Back e.m.f.

$$I_2 = I_1 \sqrt{1.44} = 20 \times 1.2 = 24 \text{ A.}$$

$$E_{b1} = V - I_1(R_a + R_{sh}) = 200 - 20 \times 0.5 = 190 \text{ V}$$

Mechanical characteristics. Of major importance for industrial drive mechanisms are the mechanical characteristics, which are the relation $N = f(T)$ (where N and T stand for speed and torque respectively) for conditions of constant voltage and resistances in the armature and field circuits. These also include the *braking characteristics*.

Regulation characteristics. These characteristics determine the *properties of motors when their speed is controlled*. These include :

- The regulation range determined by the ratio $\frac{N_{\max}}{N_{\min}}$;
- The efficiency of regulation from the point of view of the initial cost of the equipment and maintenance ;
- The nature of regulation—continuous or stepped ; and
- The simplicity of the control apparatus and methods.

The D.C. motors possess versatile and diverse regulation characteristics, and for this reason are indispensable in installations where wide-range control of speed is necessary.

The characteristic curves of a motor are those curves which show relation between the following quantities :

1. *Torque and armature current i.e., T_a/I_a characteristic.* This is also known as **electrical characteristic**.

2. *Speed and armature current i.e., N/I_a characteristic.*

3. *Speed and torque i.e., N/T_a characteristic.* This is also known as **mechanical characteristic**. This can be obtained from (1) and (2) above.

Following relations are worth *keeping in mind* while discussing motor characteristics :

$$N \propto \frac{E_b}{\phi} \text{ and } T_a \propto \phi I_a.$$

1.5.10.1. Torque-current characteristics

Shunt motor :

- When running on *no-load*, a small armature current flows to supply the field and to *drive the machine against the friction and other losses in it*.
- As the load is applied to the motor, and is increased, the torque rises *almost proportionally to the increase in current*. This is not quite true, because the flux has been assumed to be constant, whereas it decreases slightly owing to armature reaction. The effect of this is to cause the top of the curve connecting torque and line current to *bend over* as shown in Fig. 40.
- The starting torque of a motor is determined by the starting resistance, which in turn, governs the initial current through the machine when the main switch is closed. At this moment the speed is zero, so that the back e.m.f. is

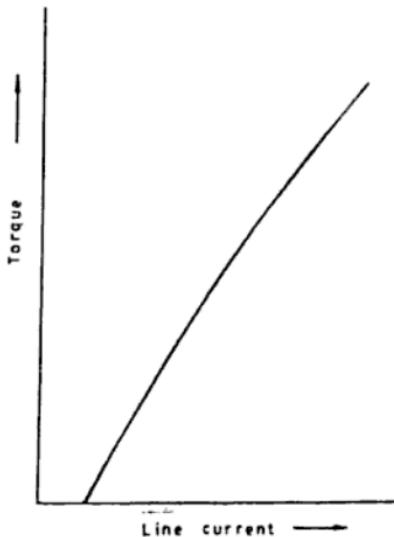


Fig. 40. Torque-current characteristic of a shunt motor.

zero and the starting current is given by $I = V/R$, where V is the supply voltage and R is the total resistance, which includes the armature and starting resistance.

If the starting current is limited by heating considerations to twice the full load current, then with normal supply voltage the starting torque of a shunt motor is twice the full load torque. If, however, the supply voltage is below normal, the flux is also less than twice full load torque. The importance of this will be appreciated when the starting torque of a series motor is compared with that of the shunt motor.

Series motor :

- In a series motor the torque ($T_a \propto \phi I_a$) increases much more than does the armature current. This is because the flux itself increases with the armature current, though, owing to the magnetic saturation, the two are not strictly proportional. Nevertheless, for all but the heavy loads which tend to produce saturation of the field system, it may be said that the torque is approximately proportional to the square of the load current.

Fig. 41 shows the relationship between torque and current.

Here the current commences at the no-load value, rises parabolically at first, but increases more slowly as the effects of armature reaction and magnetic saturation becomes appreciable.

- This property of a series motor, by virtue of which a heavy current gives rise to a very high torque, also influences its starting characteristics. In a case of a shunt motor, it has already been seen, that the current at the moment of starting may be as high as twice the full-load value ; if we allow for the armature of the magnetisation characteristic and for weakening effect of armature reaction and assume that the flux is increased to 1.5 times its full-load value, then it is obvious that the starting torque of a series motor is three times the full-load torque.
- Further more, if the supply voltage falls, the starting current may still be maintained at twice full-load value by cutting out some of the starting resistance, so that the high value of starting torque may still be maintained.

This type of motor (series motor) is superior to shunt motor for drives in which machines have to be started and accelerated from rest when fully loaded, as is the case with traction equipment.

Compound motors :

Differential compound motor. Refer Fig. 35. In this type of motor the two field windings (shunt and series) oppose each other. On light loads, such a machine runs as a shunt motor, since the series field winding, carrying only a small current, has relatively little effect.

On heavy loads, the series coils strengthen and since they are in opposition to the shunt winding, cause a reduction in the flux and a consequence decrease in torque.

On heavy overloads or when starting up on load, the series winding may become as strong as shunt, or it may even predominate, in which the torque will be reduced to zero or may even be reversed. In the latter case, the motor would tend to start-up in the wrong direction.

It is obvious that such characteristics may cause dangerous results, so that differential compound motors have only very limited applications in practice.

Fig. 42 shows the torque-current characteristic of a differential compound motor.

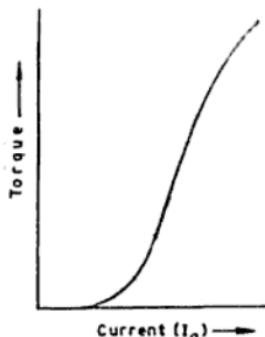


Fig. 41. Torque-current characteristic of a series motor.

Shunt motor :

- In the shunt motor, the field circuit is connected to the supply terminals so that the exciting current remains constant as long the temperature of the machine is constant, and field regulator is not adjusted. Actually as the machine warms up, the field resistance increases and the exciting current decreases by about 4% for every 10°C rise in temperature. Neglecting this effect and also due to armature reaction, it is seen that the speed of a shunt machine falls slightly as the load increases. The fall in speed is proportional to the volt drop IR in the armature circuit. If, however, we consider the effect of armature reaction, an increase of load causes a slight decrease in flux, unless the machine is fitted with compensating windings. This weakening of the field tends to raise the speed, so that the actual fall in speed is less than that calculated by a consideration of the volt drop in the armature.

On the whole, the shunt motor may be regarded as one in which the speed is approximately constant, falling slightly as the load increases (see Fig. 45).

- The speed of a shunt machine can be increased by inserting resistance in the field by means of a field regulator. This weakens the field and causes the motor to run faster in order to generate the necessary back e.m.f. Of course, it is impossible to reduce the speed by this method below that at which it runs with no field resistance in the circuit.

Series motor :

- In case of a series motor the flux does not remain constant, or even approximately constant, because the field winding is in series with the load, so that as the load increases so also does the strength of the magnetic field. At first the flux increases approximately in proportion to the load, but as the field approaches saturation, owing to the heavier loads, the increase is not so rapid. The effects of temperature changes and of armature reaction may be neglected (in comparison with the above mentioned effect).
- It will be appreciated, while considering motor equation, that the back e.m.f. decreases as the armature current increases, as in shunt motor ; in the latter, however, the decrease is due to the volt drop in the armature, while in the series machine the loss in volts occurs in the field as well as in the armature, since they are in series. The back e.m.f. in a series motor, therefore, decreases more rapidly than in a corresponding shunt machine. The speed, however, is proportional to the back e.m.f. divided by the flux ; the former decreases, while the latter increases with increasing load so that the speed decreases rapidly as the armature current increases. This property is a valuable feature in a drive of which the speed is required automatically to adjust to compensate for changes in load.

The speed-current characteristic of a series motor are shown in Fig. 46 (a).

- On very low current, a series motor runs at very high speeds, or tends to race, as it is termed. This is dangerous, since the machine may be destroyed by the centrifugal forces set up in the rotating parts. For this reason, when installing a series motor it must be positively connected to its load by gearing or by direct connection and never by belting. Moreover, the minimum load should be great enough to keep the speed within safe limits, as is the case, for example, with railway motors, hoists and rolling mills.

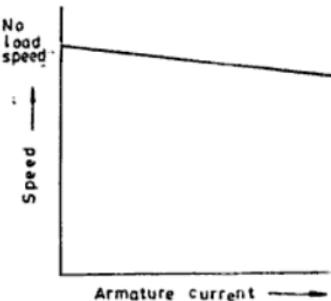


Fig. 45. Speed-current characteristic of a shunt motor.

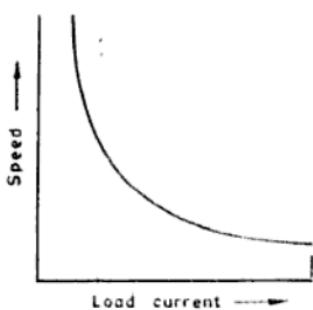


Fig. 46. (a) Speed-current characteristic of a series motor.

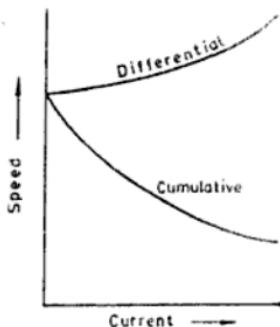


Fig. 46. (b) Speed-current characteristic of compound motors.

Compound motor :

- A compound motor runs on '*no-load*' at a speed determined by its shunt winding since the series field contributes little to the total flux in this condition.
- In a *cumulative compound motor at 'no-load'*, the series field strengthens the shunt winding so that the speed falls as in a series machine. Since the flux at any load is equal to the shunt and series fluxes, the speed is less than it would be if running on either field alone. The speed-current characteristic of such a machine is shown in Fig. 46 (b). Such a characteristic has two important advantages. These are :
 - The machine has the compensating action of reducing its speed on heavy loads, as is the case with series machine.*
 - The maximum speed on no-load is limited by the shunt winding, since this produces a maximum flux even on no-load.*

This type of motor, therefore, is suitable for driving machines which operate *on a cycle consisting of a power or working stroke followed by a return or idle stroke*. The series winding produces a fall in speed on the working stroke, while the shunt winding permits the return stroke to be completed at a high, but safe, speed. *A fly-wheel is also provided to act as a load equilizer in such a drive.*

In case of a *differential compound motor*, since the series winding opposes the shunt, the resultant flux decreases as the load increases ; thus the machine runs at a higher speed than it would do as a shunt motor. If the series windings were relatively weak, this reduction in flux might be just sufficient for the fall in speed, brought about by the volt drop in the machine. *Such a motor would have a useful application in driving loads at a constant speed.* If the series field were strong, however, an increase in load would result in a decrease in the magnetic flux and a rise in speed would take place as shown in Fig. 24, the heavier the load, the faster would the motor tend to run. This is the property which may have *dangerous consequences*, since a heavy overload would result in such a high speed that the motor would destroy itself.

1.5.10.3. Speed-torque (or mechanical) characteristics. The speed-torque characteristics of the four types, i.e. shunt, series, cumulative and differential of motors drawn on the same diagram are shown in Fig. 47 for the purpose of comparison.

The main properties of individual motors, from this diagram, may be summarised as under :

1. Shunt motor. As the *load torque increases the speed falls somewhat, but the machine may be regarded as an approximately constant speed motor.*

- (v) Vacuum cleaners, hair driers, sewing machines
- (vi) Universal machines generally.

3. Cumulative compound motors :

- (i) Punching, shearing and planing machines
- (ii) Lifts, haulage gears and mine hoists
- (iii) Pumps and power fans
- (iv) Rolling mills, stamping presses and large printing presses
- (v) Trolley buses.

4. Differential compound motors :

- (i) Battery boosters
- (ii) Experimental and research work.

1.5.11. Comparison of D.C. motor characteristics

Fig. 48 shows the comparison among shunt, series and compound operation for the *same motor* with its armature being acted upon by either or both fields. It is worth noting here that the outputs vary at the same armature current.

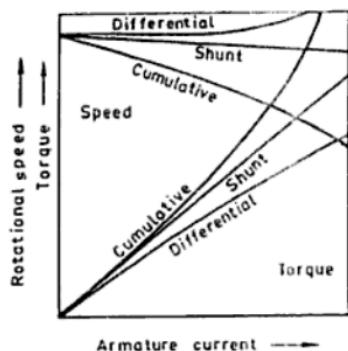


Fig. 48. Speed, torque relations for shunt and compound fields with the same armature current.

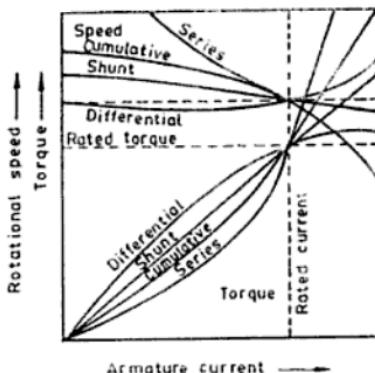


Fig. 49. Speed and torque relations for shunt, series and compound fields. Motors of same rated speed, torque and current.

- Fig. 49 compares shunt, series and compound performance when the three are rated at the horse power (or kilowatts) and rpm (or radians/sec). In this type of plot all the characteristics cross at the design load point.
- Figs. 48 and 49 are drawn with the motors operating on their full rated voltage. *Different voltages will move the curves, but the relative shapes will remain similar.*

The following may be deduced from Fig. 49.

- (i) The curves diverge between no-load and full load. If the load torque were around mid-load, the shunt motor would draw the least current and the series the most.
- (ii) At overloads the opposite is true. The series motor can develop an overload torque of around double the rated torque without drawing excessive current.

Fig. 48 shows that the speed characteristics for the same armature current are very much different. Therefore, the ability to take increasing torque loads that is the special contribution of a series field is accompanied by a much greater speed change.

1.5.12. Summary of characteristics and applications of D.C. motors

The summary of characteristics and applications of D.C. motors is given in Table 1.

Table 1. Summary of Characteristics and Applications of D.C. Motors

S No.	Type of motor	Characteristics	Applications
1.	Separately excited D.C. motors :	<ul style="list-style-type: none"> ● Possible to obtain very accurate speeds. ● Most suitable for applications requiring speed variation from very low value to high value. 	<ul style="list-style-type: none"> ● Paper machines. ● Steel rolling units. ● Diesel electric propulsion of ships.
2.	Shunt motors : <i>(i) Constant speed :</i>	<ul style="list-style-type: none"> ● Starting torque-medium, usually limited to 250% by a starting resistor but may be increased. ● Maximum operating torque usually limited to about 200% by commutation. ● Speed control : <ul style="list-style-type: none"> — increase upto 200% speed by field control. — decrease by armature voltage control. 	<ul style="list-style-type: none"> ● Employed for constant-speed applications ; may be used for adjustable speed not greater than 2 : 1 range. <p>Field of applications includes :</p> <ul style="list-style-type: none"> — Lathes ; — Centrifugal pumps ; — Fans and blowers — Machine tools ; — Wood working machines ; — Reciprocating pumps ; — Spinning and weaving machines ; — Printing presses, etc.
	<i>(ii) Adjustable speed :</i>	<ul style="list-style-type: none"> ● Starting torque-medium, usually limited to 250% by a starting resistor but may be increased. ● Maximum operating torque-usually limited to 200% by commutation. ● Speed regulation – 10 to 15%. ● Speed control : 6 : 1 range by field control. 	<ul style="list-style-type: none"> ● Same as above, For applications requiring adjustable speeds control, either constant torque or constant output.
3.	Series motors :	<ul style="list-style-type: none"> ● Variable speed. ● Adjustable varying speed. ● Starting torque very high upto 500%. ● Maximum momentary operating torque upto 400%. ● Speed regulation : Widely variable, very high at no-load. ● Speed control : By series resistance. 	<ul style="list-style-type: none"> ● Suitable for drives requiring high starting torque and where adjustable, varying speed is satisfactory. <p>Fields of application include :</p> <ul style="list-style-type: none"> — Cranes ; — Hoists ; — Trolley cars ; — Conveyors ; — Electric locomotives etc. <p>*Loads must be positively connected, not belted.</p> <p>*To prevent overspeed, lightest load should not be much less than 15 to 20% of full-load torque.</p>

<p>4. Compound motors :</p> <p>(i) <i>Cumulative compound wound :</i></p>	<ul style="list-style-type: none"> ● Variable speed. ● Adjustable varying speed. ● Starting torque high upto 450% depending upon the degree of compounding. ● Maximum momentary operating torque higher than shunt, upto 350%. ● Speed regulation : Varying, depending upon degree of compounding, upto 25-30%. ● Speed control : Usually not used but may be upto 125% by field control. ● Torque and speed almost constant. ● Tendency towards speed instability with a possibility of motor running away and strong possibility of motor starting in wrong direction. 	<ul style="list-style-type: none"> ● Suitable for drives requiring high starting torque and only fairly constant speed, pulsuating loads with flywheel action. <p>Fields of application includes :</p> <ul style="list-style-type: none"> — Shears ; — Punches ; — Elevators ; — Conveyors ; — Rolling mills ; — Heavy planes etc.
<p>(ii) <i>Differentially compound wound :</i></p>		<ul style="list-style-type: none"> ● Employed for experimental and research work.

1.5.13. Starting of D.C. motors

1.5.13.1. Need for starters. A motor at rest has no back or counter e.m.f. At starting therefore, the armature current is limited only by the resistance of the armature circuit. The armature resistance is very low, however, and if full voltage were impressed upon the motor terminals at stand still, the resulting armature current would be many times full-load value—usually sufficient to damage the machine. For this reason, additional resistance is introduced into the armature circuit at starting. As the motor gains speed, its back e.m.f. builds up and the starting resistance is cut out.

Note. Very small D.C. motors, either shunt, series or compound wound, have sufficient armature resistance so that they may be started directly from the line without the use of a starting resistance and without injury to the motor.

Fig. 50 shows the connections of a starting resistance in three types of D.C. motors:

- (a) A series motor ; (b) A shunt motor ; and
 (c) A compound motor.

- In the case of *series motor* [Fig. 50 (a)], the armature, field and starting resistance are all in series.
 - In the case of *shunt motor* [Fig. 50 (b)], it will be seen that the *top end of shunt field is connected to the first contact* on the starting resistance. This is to ensure that the field winding receives the full supply at the moment of switching on. If the fields were connected to the *last stud* of the starting resistance, then on starting, the field would receive only a proportion of the supply voltage, the field current would be correspondingly weak and the torque might be too small to start the motor against the friction of the moving parts.
 - The connections for the *compound motor* are seen from [Fig. 50 (c)] to be a combination of those of the series and the shunt connections.

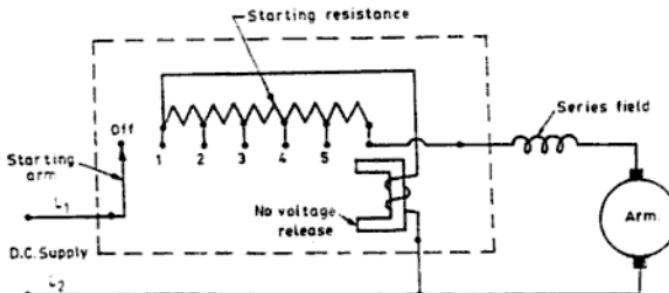


Fig. 52. Four-point starter.

Four-point starter :

- Fig. 52 shows a simplified diagram of a *four-point starter*.
- In this starter the drawback/disadvantage of the three-point starter is eliminated. In addition to the same three-points that were used with the three-point starter, the other side of the line, L_2 is the *fourth point* brought to the starter. The coil of the holding magnet is connected across the line when the arm is moved from the 'off' position. The holding magnet and starting resistors function as in the three-point starter. *The possibility of accidentally opening the field circuit is quite remote ; hence the greater acceptance of the four-point starter over the three-point starter.*
- The four-point starter *provides the motor with no voltage protection*. Should the power fail, the motor must be disconnected from the line. If not, full line voltage will be applied to the armature without the benefit of starting resistors when power is restored. The holding magnet, being connected across the line, releases the arm when the voltage drops below a specific value, thus protecting the motor when the power is restored.

2. SYNCHRONOUS MACHINES**2.1. Synchronous Generator or Alternator****2.1.1. Introduction**

- A machine for generating alternating currents is referred to as an *alternator*.
- The term 'A.C. generator' is also frequently used, in place of alternator and this is often contracted to just 'generator' when it is obvious that an A.C. machine is meant. In older literature, the term 'alternating current dynamo' will also be found, but the present tendency is to reserve the use of the word *dynamo* for D.C. generators.
- High-speed alternators driven by steam turbines differ considerably in their construction from the slow speed types and are distinguished by the use of the terms '*turbo-alternator*' or '*turbo-generator*' whilst the slow engine-driven machines are often described as being of the '*flywheel-type*'.

2.1.2. Classification and operating principle

- In *D.C. generators*, the field poles are stationary and the armature conductors rotate. The alternating voltage induced in armature conductors is converted to a *direct* voltage at the brushes by means of the commutator.

- A.C. generators commonly called alternators, have no commutators as they are required to supply electrical energy with an alternating voltage. Therefore, it is not necessary that armature be the rotating member.

Alternators, according to their construction, are divided into the following two classifications :

1. Revolving-armature type.
2. Revolving-field type.

1. Revolving-armature type alternator

- It has stationary field poles and revolving armature.
- It is usually of relatively small kVA capacity and low-voltage rating. It resembles a D.C. generator in general appearance except that it has slip-rings instead of a commutator. The field excitation must be direct current and therefore, must be supplied from an external direct current source.

2. Revolving-field type alternator :

- It has a stationary armature or stator, inside of which the field poles rotate.
- Most alternators are of the revolving-field type, in which the 'revolving-field structure' or 'rotor' has slip rings and brushes to supply the excitation current from an outside D.C. source. The armature coils are placed in slots in a laminated core, called the 'stator', which is made up of thin steel punchings or laminations securely clamped and held in place in the steel frame of the generator. Usually the field voltage is between 100 and 250 volts and the amount of power delivered to the field circuit is relatively small.

The following are the principal advantages of the revolving-field type alternators :

1. The armature windings are more easily braced to prevent deformation under the mechanical stresses due to short-circuit currents and centrifugal forces.
2. The armature (stator) winding must be insulated for a high voltage, while the voltage of field circuit is low (100 to 250 volts). *It is much easier to insulate the high-voltage winding when it is mounted on the stationary structure.*
3. Only a small amount of power at low voltage is handled by the slip ring contacts.
4. It is easier to build and properly balance high-speed rotors when they carry the field structure.
5. The armature winding is cooled more readily because the stator core can be made large enough and with many air passages or cooling ducts for forced air circulation.

Operating principle (Revolving-field type). When the rotor rotates, the stator conductors (being stationary) are cut by the magnetic flux, hence they have induced e.m.f. produced in them. Because the magnetic poles are alternately N and S, they induce an e.m.f. and hence current in armature conductors, which first flows in one direction and then in the other. Hence, an alternating

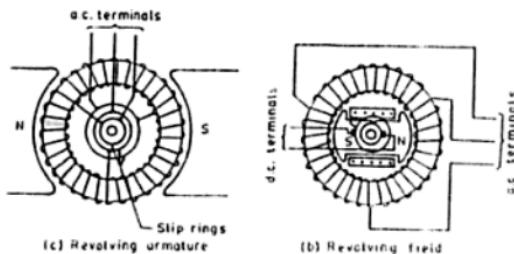


Fig. 53. Operating principle of a three-phase alternator.

e.m.f. is produced in the stator conductors whose frequency depends on the number of N and S poles moving past a conductor in one second and whose direction is given by Fleming's right-hand rule.

Fig. 53 shows the operating principle of a three-phase alternator.

Note. All synchronous A.C. generators and motors require direct current for excitation. Excitation is supplied by a D.C. generator called an *exciter*. The capacity of the exciter is only a *small percentage* of the rated capacity of the alternator. The exciter may be directly connected to the shaft of the alternator, or it may be driven by a separate electric motor, water wheel, or small turbine. Large power stations usually have several exciters employing different methods of drive as insurance against the failure of excitation.

2.1.3. Constructional details

Refer Fig. 54.

2.1.3.1. Stator. The *stator* of an alternator consists essentially of a cast iron or a welded-steel frame supporting a slotted ring made of soft laminated sheet-steel punchings (Fig. 55) in the slots of which the armature coils are assembled.

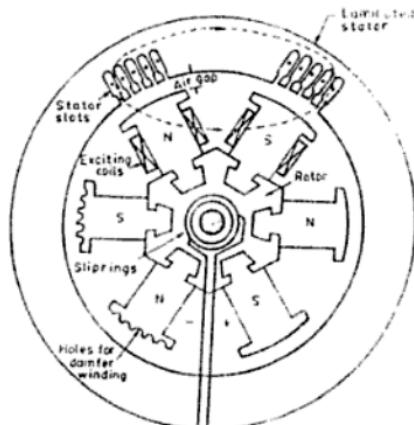


Fig. 54. Alternator.

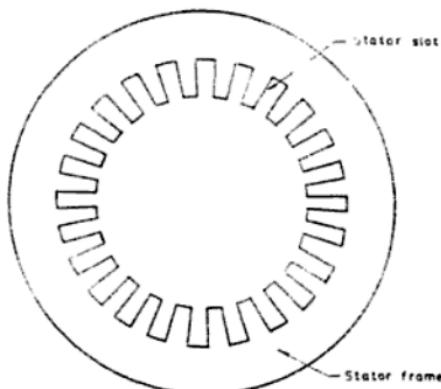


Fig. 55. Alternator stator.

- The *laminations* are annealed and are insulated from each other by a thin coating of oxide and an enamel (as in D.C. machines, transformers etc.)
- *Open slots* are used, permitting easy installation of stator coils and easy removal in case of repair. Suitable spacing blocks are inserted at intervals between laminations to leave radial *air ducts*, open at both ends, through which cooling air may circulate.
- The *coils* are shaped much like the coils of a D.C. generator, the two sides of the coil being approximately a pole pitch apart. All coils are alike, and therefore, interchangeable. They are insulated before being inserted in the slots and are further protected by a horn-fibre slot lining. When in place on the stator, the coils are connected together in groups to form a winding of the required number of phases, three phase star-connected windings being common.
- A fractional rather than an *integral number of slots per pole is often used in order to eliminate harmonics in the waveform*.

2.1.3.2. Rotor. The revolving field structure is usually called the rotor. There are two types of rotors :

1. Salient pole type rotor.
2. Smooth cylindrical type rotor.

Salient pole type rotor :

This type of rotor is used for slow-speed machines which have large diameters and small axial lengths.

- The poles are made of thick steel laminations riveted together and attached to a rotor by a dovetail joint as shown in Fig. 56. The overhang of the pole gives mechanical support to the field coil.
- In most of the alternators, where the oscillation or the hunting effect is very high, the *damper winding* in the pole faces is provided. The copper bars short circuited at both ends are placed in the specially provided holes. The relative velocity of the damping winding with respect to main field will be zero when the speed is steady but as soon as it departs from the synchronous speed, there will be relative motion between the damper winding and the main field. This will induce current in them. This induced current will exert a torque in such a way as to bring the alternator to operate at synchronous speed.
- The pole face is so shaped that the radial air gap length increases from the pole centre to pole tips. This makes the flux distribution over the armature uniform to generate sinusoidal waveform of e.m.f. (Fig. 57).*

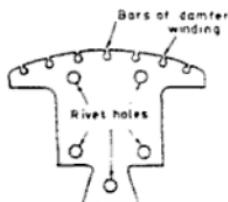


Fig. 56. Typical lamination of a salient pole rotor.

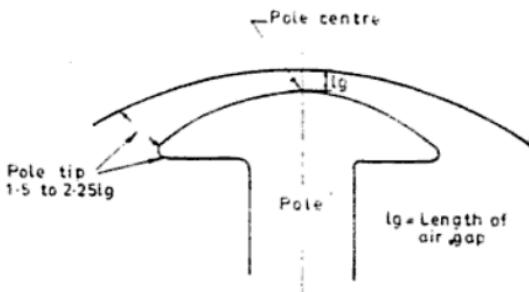


Fig. 57

The salient pole field structure has the following **special features** :


- They have *large diameter* and *short axial length*.
- The pole shoe covers about $\frac{2}{3}$ rd of pole pitch.
- Poles are laminated to reduce eddy current losses.
- These are employed with hydraulic turbines or diesel engines. The speed is 100 to 375 r.p.m.

Smooth cylindrical rotor :

- This type of rotor is used for alternators which are coupled to *steam turbines* which run at very high speeds. To reduce the peripheral speed of the alternator the *diameter of the rotor is reduced and axial length is increased*. The number of poles of the rotor are *two or four*.

Figs. 57 and 58 show a cylindrical rotor and cylindrical rotor alternator respectively.

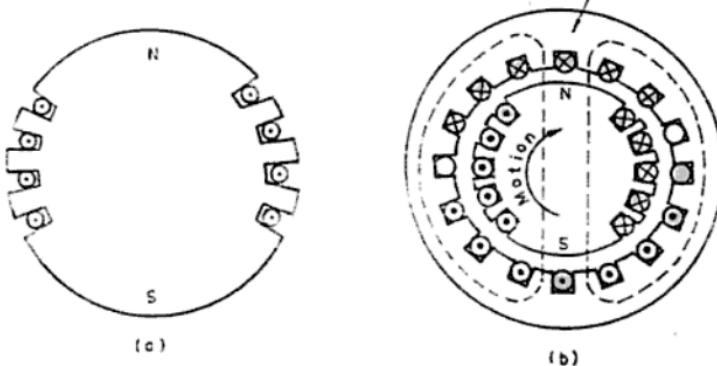- These rotors are made from solid forgings of alloy steel.* The outer periphery of rotor has slots in which the field winding is placed. About $\frac{2}{3}$ rd of rotor pole pitch is slotted, leaving



(a) Cylindrical rotor (two pole).

(b) Cylindrical rotor alternator (two pole).

Fig. 58

the 1/3rd unslotted for the pole centre. Heavy wedges of non-magnetic steel are forced into the grooves in the teeth outside the field coils to keep the field coils in position.

- *Cylindrical rotor machines have always horizontal configuration.*
- Since these rotors have large lengths of core forced ventilation is necessary for proper cooling. *Forced air cooling is used up to about 50 MVA sizes and for bigger sizes hydrogen cooling is invariably employed because the conductivity of hydrogen is about 7 times that of air.*

The non-salient field structure has the following **special features** :

- (i) They are of small diameter and of very long axial length.
- (ii) Robust construction.
- (iii) High operating speed (3000 r.p.m.).
- (iv) Noiseless operation.
- (v) Dynamic balancing is better.
- (vi) Less windage (air-resistance) loss.
- (vii) No need to provide damper windings, except in special cases to assist in synchronising.
- (viii) Better e.m.f. waveform.

Note. It may be worth mentioning that *cylindrical rotors* will most likely be located on alternators where *steam power* is readily available. *Salient-pole rotors* will be found where *water power* is the prime-mover source of energy. Diesel engine, gas engine, and gas turbine prime-movers are considered medium-speed machines, and their alternators will also have salient poles. Where alternators are driven by other electrical machines, either A.C. or D.C. motors, there are no such restrictions on the rotor construction. A design is developed that is compatible with the space limitations, speed considerations, and heat dissipation for both electrical machines. If may be noted here that the terms high-speed and low-speed rotors are sometimes used synonymously with cylindrical and salient-pole rotors, respectively.

2.1.3.3. Bearings

- Although antifriction bearings are occasionally used on alternators of the smaller ratings, the great majority are furnished with oil-lubricated babbitt bearings. For *horizontal shafts* these will be self-contained ring-oiled bearings wherever design conditions permit. At higher shaft peripheral speeds and higher bearing loadings, ring oiling is supplemented with recirculation of externally cooled coil. The rings may be eliminated, or they may be retained to afford some degree of emergency oil supply in the event of a failure of the

external system. Lead-base babbitts are commonly used for journal bearings, although tin-base babbitts may be employed for some heavy-duty application.

- Two principal types of *thrust bearings* are used on vertical alternators : the *pivoted shoe type* and the *spring type*.

2.1.4. Frequency

In case of a generator which has two poles, the induced e.m.f. passes through one complete revolution in one revolution of the machine. In a multipolar machine one cycle of e.m.f. would be generated when the field structure rotates through an angle subtended by a double pole pitch. Therefore, in a machine with p -poles, the number of cycles of e.m.f. in one revolution will be $p/2$. If a machine has a speed of N_s revolutions per minute, the frequency will be

$$\left(\frac{p}{2} \right) \times \frac{N_s}{60} \text{ per second.}$$

Thus,

$$f = \frac{p}{2} \times \frac{N_s}{60} = \frac{N_s p}{120} \text{ Hz} \quad \dots(12)$$

In order to keep the frequency constant, the speed N_s must remain unchanged. Therefore, a synchronous generator (i.e., alternator) runs at a constant speed known as *synchronous speed*.

The following table gives the number of poles and speeds for three frequencies : 60-Hz, 50-Hz and 25-Hz.

Higher frequencies are today being used for specific purposes, especially when it is necessary to use high-speed induction motors, but these frequencies are not for general distribution. A great deal of aircraft equipment operates with voltage having a frequency of 400 Hz.

Table 2

Number of poles	Speed, r.p.m.		
	60 Hz	50 Hz	25 Hz
2	3600	3000	1500
4	1800	1500	750
6	1200	1000	500
8	900	750	375
10	720	600	300
12	600	500	250

Note. The standard frequency in India is 50 Hz.

2.1.5. Armature windings

2.1.5.1. **Winding types.** A wide variety of winding types are possible to produce a desired voltage in the proper number of phases and with a suitable waveshape. Practical considerations, mainly economic, limit the usual alternator winding to a *double-layer 3-phase lap winding, arranged in 60° phase belts in open slots*. The number of coils, the number of turns per coil, the coil pitch, the number of circuits, and the connection of the phases are selected to give the desired voltage and waveform.

Double-layer windings in open slots permit the use of form-wound coils which are all alike in a given machine. These coils have the characteristic diamond shape in the end area. Three-phase windings may be either Δ -or Y-connected; Y-connected machines are much more common, particularly in the larger sizes. The winding may be arranged to be connected either Y or Δ , with leads brought out from both ends of each phase to make this possible.

- Double-layer windings in open-slots have the following *advantages* over single layer windings in semi-enclosed slots :

winding, a coil pitch of 1 to 8 would be the maximum ordinarily used. *Less than full pitch coils are used to obtain adjustments in the voltage generated or to limit harmonics.*

2.1.5.7. Single phase windings. These are usually 3-phase windings with 1-phase not used. Sometimes the coils for the third phase are omitted, but most often they are wound in the machine and might be considered as spares. In small sizes a special concentric winding may be used. A *low-resistance damper winding* is generally necessary on single phase machines to reduce the flux pulsations that are set up by the single-phase armature reaction and to reduce the effective armature reactance. Single-phase machines have an inherent torque pulsation at twice rated frequency. The resulting noise and vibration are noticeable on small machines and may require special construction on large machines.

2.1.5.8. Two-phase windings. These windings differ from 3-phase windings only in the grouping of the stator coils. Ninety-degree phase belts are ordinarily used.

2.1.5.9. Double windings. These windings are sometimes used to reduce short-circuit currents and to simplify switch gear and bus structure problems. The windings have standard coil design with special end connections. The electrical designs must allow for the effects of unbalanced armature reaction if the two windings are not equally loaded and for the mutual reactance between the windings.

2.1.5.10. Multispeed windings. For some applications a winding is required which will permit operation at more than one speed, but at the same frequency. An example is a hydraulic pump-turbine unit, which may generate at one speed and pump at another. Such machines may have two windings in the same slot or in adjacent slots or a single armature winding may be reconnected by means of suitable switches to serve this purpose. Special rotor construction and field-winding reconnections are also necessary.

2.1.6. Chording of windings

Chording of the pole windings is one of the design factors. If, on the 36-slot, four pole machine, an individual coil enters slot 1 and comes back in slot 10, it will have spanned 90 mechanical degrees

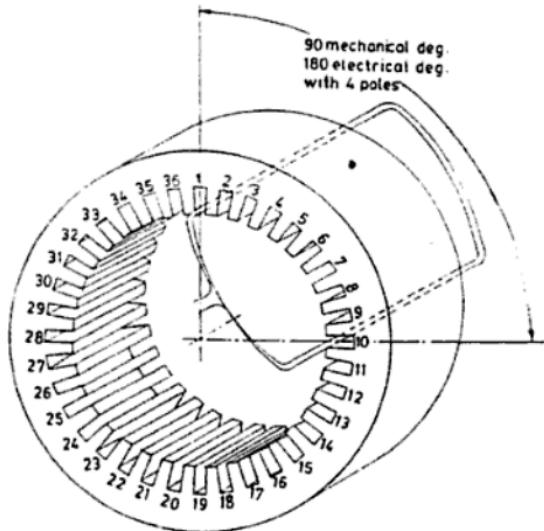


Fig. 59. Four-pole A.C. stator with full pitch coils.

of the stator circular structure. Since there are four poles, 90 mechanical degrees is 180 electrical degrees (because *total electrical degrees in one revolution = 180 p*, where p , is the number of poles). Thus, the two sides of the coil are in the same relative position on the adjacent north and south pole positions. This is a full-pitch coil construction (Fig. 7).

The more usual A.C. machine coil will cover less of the periphery of the machine and is then said to be *fractional pitch*. A typical situation might have a coil enter slot 1 and leave slot 7. This then covers six out of a possible nine slot pitches, and is a $6/9$ or 66.7% pitch. *The majority of A.C. machine coils are of fractional-pitch type.*

Advantages of fractional pitch winding :

- (i) The ends of the coils are shorter, which means *less copper loss due to less total length*.
- (ii) The end coils can be formed more compactly. The end belts will need less winding space resulting in a shorter unit.

(iii) Improved waveform of the induced e.m.f.

(iv) Fractional number of slots per pole can be used which in turn reduces tooth ripples.

(v) Mechanical strength of the coils is increased.

(vi) There is distinct *reduction in machine harmonics* due to cancellation of higher harmonics. Since all A.C. equipment is designed to operate on a pure sine wave, the generation of harmonics is to be avoided. This is especially so when the factor that achieves it is otherwise desirable.

2.1.7. Pitch factor

In a full pitch coil, the e.m.fs. in the two coil sides are in phase and therefore the coil e.m.f. is twice the e.m.f. of each coil side. In a *short pitch coil* the e.m.fs. of the two coil sides are not in phase and must be *added vectorially* to give the coil e.m.f. The *factor by which the e.m.f. per coil is reduced, because of the pitch being less, is known as pitch factor (or coil span factor) k_p* . Thus,

$$k_p = \frac{\text{vector or phasor sum of induced e.m.fs. per coil}}{\text{arithmetic sum of the induced e.m.fs per coil}} \quad \dots(13)$$

It is *always less than unity*.

Let E_s be induced e.m.f. in each side of the coil. If the coil were full-pitched, then the total induced e.m.f. in the coil would have been $2E_s$ [Fig. 60 (a)].

If it is short-pitched by angle α° (electrical) then their resultant [Fig. 60 (b)] is E which is vector sum of two voltages, α° (electrical) apart.

$$\therefore E = 2E_s \cos \frac{\alpha}{2}$$

$$\therefore k_p = \frac{\text{vector sum}}{\text{arithmetic sum}}$$

$$= \frac{E}{2E_s} = \frac{2E_s \cos \frac{\alpha}{2}}{2E_s} = \cos \frac{\alpha}{2}$$

$$\text{Hence, } k_p = \cos \frac{\alpha}{2} \quad \dots(14)$$

The pitch factor given by eqn. (14) is for the *fundamental component of e.m.f.* If the flux density distribution contains space harmonics, the pitch factor for the n th harmonic is given by.

$$k_{pn} = \cos \frac{n\alpha}{2} \quad \dots(15)$$

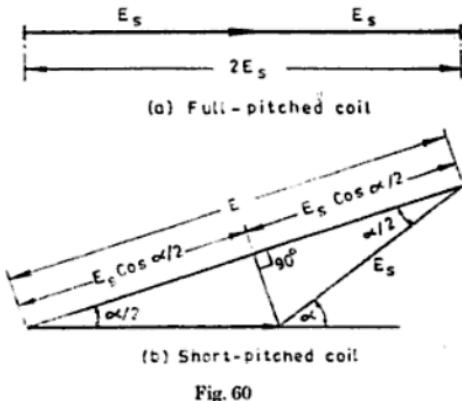


Fig. 60

The n th harmonic e.m.f. is reduced to zero if the angle α is such that

$$\cos \frac{n\alpha}{2} = 0 \quad \text{or} \quad \frac{n\alpha}{2} = 90^\circ \quad \dots(16)$$

This enables the windings to be designed such that specified harmonics will not be generated e.g. if $\alpha = 60^\circ$, there can be no third harmonic generation. Thus fractional pitch windings result in a voltage wave form which resembles a sinusoidal to a better degree than would a full-pitch winding.

Note. If the value of α is not given in question, then assume $k_p = 1$.

2.1.8. Distribution or breadth or winding factor

When the coils comprising a phase of the winding are distributed in two or more slots per pole, the e.m.fs. in the adjacent coils will be out of phase with respect to one another and their resultant will be less than their algebraic sum. The ratio of the vector sum of the e.m.fs. induced in all the coils distributed in a number of slots under one pole to the arithmetic sum of the e.m.fs. induced (or to the resultant of the e.m.fs. induced in all the coils concentrated in one slot under one pole) is known as distributed factor k_d

$$\text{or } k_d = \frac{\text{e.m.f. induced in a distributed winding}}{\text{e.m.f. induced if the winding would have been concentrated}}$$

$$= \frac{\text{vector sum}}{\text{arithmetic sum}}.$$

The distribution factor is always less than unity.

Let

$$n = \text{number of slots/pole}$$

$$q = \text{number of slots/pole/phase}$$

$$E_s = \text{induced e.m.f. in each coil side}$$

$$\beta = \text{angular displacement between the slots}$$

$$= \frac{180^\circ}{n}$$

The e.m.fs. induced in different coils of one phase under one pole are represented by side AB , BC , CD , DE which are equal in magnitude (say each equal to E_s) and differ in phase (say β°) from each other. If bisectors are drawn on AB , BC , CD , DE they would meet at common point (say at O). The point O would be the circumcentre of the circle having AB , BC , CD , DE , as the chords and representing the e.m.fs. induced in the coils in different slots.

E.m.f. induced in each coil side,

$$E_s = AB = 2OA \sin \frac{\beta}{2}$$

$$\text{Arithmetic sum} = q \times 2 \times OA \sin \frac{\beta}{2}$$

The resultant e.m.f. induced in one polar group of one phase would be the vector sum as represented by the vector AF as shown in Fig. 61.

∴ The resultant e.m.f.,

$$E_r = AF$$

$$= 2 \times OA \sin \frac{AOF}{2} = 2 \times OA \sin \left(\frac{q\beta}{2} \right)$$

Distribution factor.

$$k_d = \frac{\text{vector sum}}{\text{arithmetic sum}}$$

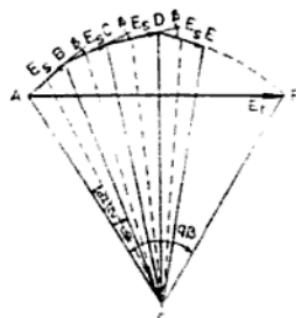


Fig. 61. Calculation of distribution factor.

$$\begin{aligned}
 &= \frac{2 \times OA \sin\left(\frac{q\beta}{2}\right)}{q \times 2 \times OA \sin\left(\frac{\beta}{2}\right)} = \frac{\sin\left(\frac{q\beta}{2}\right)}{q \sin\left(\frac{\beta}{2}\right)} \\
 k_d &= \frac{\sin\left(\frac{q\beta}{2}\right)}{q \sin\left(\frac{\beta}{2}\right)} \quad \dots(17)
 \end{aligned}$$

Hence,

$q\beta$ is also known as the *phase spread* and is expressed in electrical radians.

Value of the distribution factor for *nth harmonic* is,

$$k_d = \frac{\sin\left(\frac{qn\beta}{2}\right)}{q \sin\left(\frac{n\beta}{2}\right)}$$

2.1.9. E.M.F. equation

Let

Z_{ph} = number of conductors or coil sides in series per phase
 $= 2T_{ph}$, where T_{ph} is the number of coils or turns per phase (one turn coil has two sides),

p = number of poles,

ϕ = useful flux per pole, webers,

N = rotational speed of rotor, r.p.m.,

f = frequency, Hz,

k_d = distribution factor, and

k_p = pitch factor.

Consider a conductor on the stator of the alternator. Let the alternator rotor move through one revolution in $t = \frac{60}{N}$ seconds, the flux cut by the conductor
 $= p\phi$ webers

The average e.m.f. induced in the conductor,

$$E_{av} = \frac{d}{dt} (\text{flux}) \text{ volts} = p \cdot \frac{\phi}{t} = p\phi \cdot \frac{60}{60} = \frac{p\phi N}{60} \quad \dots(18)$$

We know that,

$$f = \frac{Np}{120} \quad \text{or} \quad N = \frac{120f}{p}$$

Substituting the value of N in eqn. (7), we get

$$E_{av} = \frac{p\phi \times 120f}{60 \times p} = 2f\phi \text{ volts/conductor}$$

Average e.m.f. per phase,

$$\begin{aligned}
 E_{av}/\text{phase} &= 2f\phi \times 2T_{ph} = 4f\phi T_{ph} \\
 E_{r.m.s}/\text{phase} &= E_{av} \times \text{form factor} = 4f\phi T_{ph} \times 1.11 \\
 &= 4.44f\phi T_{ph} \text{ volts}
 \end{aligned}$$

The above equation of e.m.f. induced per phase is true only, if the winding is concentrated in one slot but practically it is not true, as the winding for each phase under each pole is distributed and for such cases k_p and k_d must be considered.

Thus, e.m.f. induced (for sinusoidal wave) per phase will be

$$E_{r.m.s}/\text{phase} = 4.44f_0T_{ph}k_pk_d \text{ volts} \quad \dots(19)$$

For full-pitched and concentrated windings $k_p = 1$, $k_d = 1$.

If the alternator is star-connected (as is usually the case) then the line voltage,

$$E_L = \sqrt{3} E_{r.m.s} \text{ phase} = \sqrt{3} \times 4.44f_0T_{ph}k_pk_d \text{ volts.}$$

Example 28. Determine the pitch (or coil span) factors for the following windings :

- (i) 36 stator slots, 4 poles, coil span 1 to 8. (ii) 96 stator slots, 6 poles, coil span 1 to 12.

Sketch the two coil spans.

Solution. (i) 36 stator slots, 4 poles, coil span 1 to 8 : [Fig. 62 (a)]

In this case coil span falls short by,

$$\left(\frac{2}{9}\right) \times 180^\circ = 40^\circ \quad \text{i.e., } \alpha = 40^\circ$$


∴ Pitch factor, $k_p = \cos \frac{40^\circ}{2} = \cos 20^\circ = 0.94$.

(ii) 96 stator slots, 6 poles, coil span 1 to 12 : [Fig. 62 (b)]

Here, coil span falls short by,

$$\left(\frac{5}{16}\right) \times 180^\circ = 56^\circ \quad \text{i.e., } \alpha = 56^\circ$$

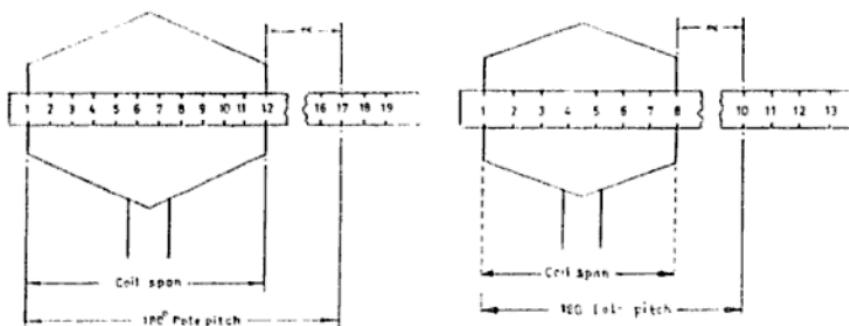∴ Pitch factor, $k_p = \cos \frac{\alpha}{2} = \cos \frac{56^\circ}{2} = \cos 28^\circ = 0.883$. (Ans.)



(a) 36 stator slots, 4 poles, coil span 1 to 8.

(b) 96 stator slots, 6 poles, coil span 1 to 12.

Fig. 62

Example 29. A 3-phase, 16-pole alternator has the following data :

Number of slots = 192 ; Conductors/slot = 8 (conductors of each phase are connected in series) ; coil span = 160 electrical degrees ; speed of the alternator = 375 r.p.m. ; flux/pole = 55 m Wb. Calculate the phase and line voltages.

Solution. Number of poles, $p = 16$

Number of slots = 192

Conductors/slot = 8

Coil span = 160° (electrical)

Speed of the alternator = 375 r.p.m.

Flux/pole,

$$\phi = 55 \text{ mWb} = 0.055 \text{ Wb}$$

Here,

$$\alpha = 180^\circ - 160^\circ = 20^\circ$$

∴ Pitch factor,

$$k_p = \cos \frac{\alpha}{2} = \cos \frac{20^\circ}{2} = \cos 10^\circ = 0.9848$$

Number of slots/pole,

$$n = \frac{192}{16} = 12$$

∴

$$\beta = \frac{180^\circ}{n} = \frac{180^\circ}{12} = 15^\circ$$

$$q = \text{number of slots/pole/phase} = \frac{192}{16 \times 3} = 4$$

∴ Distribution factor,

$$k_d = \frac{\sin \frac{q\beta}{2}}{q \sin \frac{\beta}{2}} = \frac{\sin \left(\frac{4 \times 15^\circ}{2} \right)}{4 \sin \left(\frac{15^\circ}{2} \right)} = \frac{\sin 30^\circ}{4 \sin 7.5^\circ} = 0.9577$$

Now, total number of slots/phase = $\frac{192}{3} = 64$

Number of conductors/slot = 8

(given)

∴ Total number of conductors/phase

$$= 64 \times 8 = 512$$

∴ Turns/phase,

T_{ph} = \frac{512}{2} = 256

Also, frequency,

$$f = \frac{Np}{120} = \frac{375 \times 16}{120}$$

$$f = 50\text{-Hz}$$

Now, Using the relation,

$$E_{ph} = 4.44 \phi T_{ph} k_p k_d \text{ volts}$$

$$= 4.44 \times 50 \times 0.55 \times 256 \times 0.9848 \times 0.9577 = 2948 \text{ V}$$

∴ Line voltage,

$$E_L = \sqrt{3} E_{ph} = \sqrt{3} \times 2948 = 5106 \text{ V. (Ans.)}$$

Example 30. A 3-phase, star-connected alternator has the following data : voltage required to be generated on open-circuit = 4000 V (at 50-Hz) ; speed = 500 r.p.m. ; stator slots/pole/phase = 3 ; conductors/slot = 12. Calculate :

(i) Number of poles, and

(ii) Useful flux pole.

Assume all conductors per phase to be connected in series and coil to be full pitch.

Solution. Line voltage, $E_L = 4000 \text{ V}$

$$\therefore E_{r.m.s./phase}, E_{ph} = \frac{4000}{\sqrt{3}} = 2309 \text{ V}$$

Speed of the alternator, $N = 500 \text{ r.p.m.}$

Number of slots/pole/phase,

$$q = 3$$

Number of conductors/slot = 12

Frequency, $f = 50\text{-Hz}$.

(i) Number of poles, p :

Using the relation, $f = \frac{Np}{120}$

2.2. Synchronous Motor

2.2.1. Introduction

- The synchronous motor is the one type of 3-phase A.C. motors which operates at a constant speed from no-load to full-load. It is similar in construction to 3-phase A.C. generator in that it has a revolving field which must be separately excited from a D.C. source. By changing the D.C. field excitation current, the power factor of this type of motor can be varied over a wide range of lagging and leading values.
- This motor is used in many individual applications because of its fixed speed from no-load to full-load, its high efficiency and low initial cost. It is also used to improve the power factor of 3-phase A.C. industrial circuits.

2.2.2. Characteristic features, advantages and disadvantages

Characteristic Features :

The following characteristic features of a synchronous motor are worth noting :

1. It runs either at synchronous speed or not at all. The speed can be changed by changing the frequency only (since $N_s = 120f/p$).

2. It is not inherently self-starting. It has to be run up to synchronous or near synchronous speed by some means before it can be synchronized to the supply.

3. It can operate under a wide range of power factors both lagging and leading.

4. On no-load the motor draws very little current from the supply to meet the internal losses. With fixed excitation the input current increases with the increase in load. After the input current reaches maximum no further increase in load is possible. If the motor is further loaded, the motor will stop.

Advantages. Synchronous motors entail the following advantages :

1. These motors can be used for power factor correction in addition to supplying torque to drive loads.

2. They are more efficient (when operated at unity power factor) than induction motors of corresponding output (kW) and voltages rating.

3. The field pole rotors of synchronous motors can permit the use of wider air-gaps than the squirrel-cage designs used on induction motors, requiring less bearing tolerance and permitting greater bearing wear.

4. They may be less costly for the same output, speed, and voltage ratings as compared to induction motors.

5. They give constant speed from no-load to full-load.

6. Electro-magnetic power varies linearly with the voltage.

Disadvantages. The disadvantages of synchronous motors are :

1. They require D.C. excitation which must be supplied from external source.

2. They have a tendency to hunt.

3. They cannot be used for variable speed jobs as speed adjustment cannot be done.

4. They require collector rings and brushes.

5. They cannot be started under load. Their starting torque is zero.

6. They may fall out of synchronism and stop when overloaded.

2.2.3. Applications

The synchronous motors have the following fields of application :

1. **Power houses and sub-stations.** Used in power houses and sub-stations in parallel to the bus-bars to improve the power factor.

2. Factories. Used in factories having large number of induction motors or other power apparatus, operating at *lagging power factor*, to improve the power factor.

3. Mills-industries etc. Used in textile mills, rubber mills, mining and other big industries, cement factories for power applications.

4. Constant speed equipments. Used to drive continuously operating and constant speed equipment such as :

- Fans.
- Blowers.
- Centrifugal pumps.
- Motor generator sets.
- Ammonia and air compressors etc.

2.2.4. Construction

A three-phase synchronous motor consists of the following *essential parts* :

1. Laminated stator core with three-phase armature winding.
 2. Revolving field complete with amortisseur winding and slip rings.
 3. Brushes and brush holders.
 4. Two end shields to house the bearings that support the shaft.
- The stator core and windings of a synchronous motor are similar to those of a 3-phase squirrel-cage induction motor or a wound-rotor induction motor. The leads for the stator winding, marked T_1 , T_2 and T_3 , terminate in a terminal box usually mounted on the side of the motor frame.
 - The rotor is generally a salient pole rotor. *The number of rotor field poles must equal the number of stator field poles*. In order to eliminate hunting and to develop the necessary starting torque when A.C. voltage is applied to the stator, the rotor poles contain pole-face conductors which are short-circuited at their ends as shown in Fig. 63. This amortisseur or damper winding consists of solid copper bars embedded at the surface of the pole face and short-circuited at each end by means of a shorting strip as shown in Fig. 64.
 - The field circuit leads are brought out to two *slip rings* mounted on the rotor shaft. Carbon brushes mounted in brush holders make contact with the two slip rings. The terminals of the field circuit are brought out from the brush holders to a second terminal box mounted on the motor frame. The two leads for the field circuit are marked F_1 and F_2 .

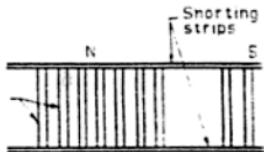


Fig. 63. Pole of an A.C. synchronous motor.

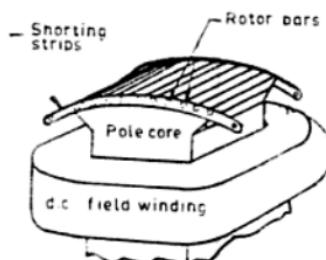


Fig. 64. Damper winding.

Fig. 65 shows a typical arrangement of synchronous motor, with overhung exciter for providing the D.C. supply to the rotor of the machine.

to bring the motor upto synchronism, the D.C. generator is operated as motor, and the A.C. synchronous dynamo is synchronized to the A.C. supply as an alternator. Once in parallel with the supply, the synchronous dynamo is operated as a motor. The D.C. 'motor' will now act as a generator if its field current is increased so that its generated e.m.f. exceeds the D.C. bus.

2. Using the field excited generator as a D.C. motor. This method is the same as the first, except that the exciter (D.C. shunt generator) is operated as a motor, and the A.C. synchronous dynamo is synchronized to the A.C. supply.

3. A small induction motor of at least one pair of poles less than the synchronous motor. This method involves the same synchronizing procedure for A.C. synchronous motor as an alternator. At least one pair of poles fewer is required on the induction motor to compensate for the loss in induction motor speed due to slip.

In the above three methods the following conditions should be met with :

- There should be *little or no-load* on the synchronous motor.
- The capacity of the starting motor (D.C. or A.C.) should be between 5 and 10% of the rating of the synchronous motor coupled to it.

4. Using the damper windings as a squirrel-cage induction motor.

Note. It is practically impossible to start a synchronous motor with its D.C. field energized. Even when left de-energized, the rapidly rotating magnetic field of the stator will induce extremely high voltages in the many turns of the field winding. It is customary, therefore, to short-circuit the D.C. field winding during the starting period ; whatever voltage and current are induced in it may then aid in producing induction motor action. In very large synchronous motors, field sectionalising or field-splitting switches are used which short-circuit individual field windings to prevent cumulative addition of induced voltages from pole to pole.

2.2.7. Effect of load on a synchronous motor

When mechanical load on a D.C. motor or an A.C. motor is increased, the speed decreases. This, in turn, decreases the back or counter e.m.f. (E_b) so that the source is able to supply more current to meet the increased load demands. However, this action cannot take place in the synchronous motor for the rotor must turn at synchronous speed at all loads.

Fig. 67 (a) shows the relative position of a stator and rotor pole at *no-load*, poles centres are directly in line with each other.

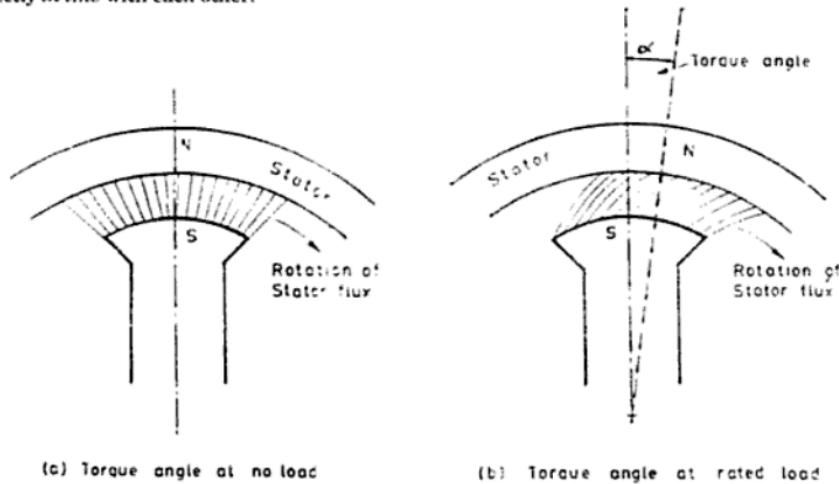


Fig. 67. Relative positions of stator and rotor poles.

Fig. 67 (b) represents the relative position of the stator and the rotor poles after mechanical load has been added to the motor. Now there has been a shift of the rotor pole in a direction opposite to that of the stator field flux and the direction of the rotor. It may be kept in mind that there has been no change in speed as the rotor will continue to rotate at synchronous speed. There is *only an angular displacement between the centres of the stator and rotor field poles*. The angular displacement shown in Fig. 67 (b) is called the '**torque angle**'.

No-load condition-vector diagrams. Fig. 68 shows the conditions when the motor (properly synchronised to the supply) is running on *no-load* and is having no losses. It is seen that $V = E_b$, hence their vector difference is zero and so is the armature current. Motor intake is zero, as there is neither load nor losses to be met by it. In other words, the motor just *floats*.

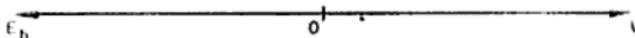


Fig. 68. No-load (no losses).

Fig. 69 shows the vector diagram when the motor is on no-load but has losses. The vector for E_b falls back by a certain angle α_0 , so that a resultant voltage E_r and hence current I_0 is brought into existence which supplies losses.

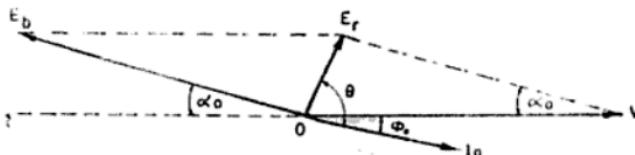


Fig. 69. No-load (with losses).

Load condition-vector diagram. When the motor is loaded, it slows down momentarily to adjust itself to the change in load condition, so the rotor pole falls back a little more relative to the stator pole, as shown in Fig. 70. Hence the torque angle increases with the increase in load. Due to increase in load or torque angle α , the resultant voltage E_r across the armature (or stator) circuit increases, and, therefore, current drawn from the supply mains increases. Thus a motor is able to supply increased mechanical load, not by reduction in speed, but by shift in relative positions of the rotor and rotating magnetic field (or stator flux). From Fig. 66 it is obvious that *for increasing load with a constant value of back e.m.f. E_b the phase angle ϕ increases in lagging direction*.

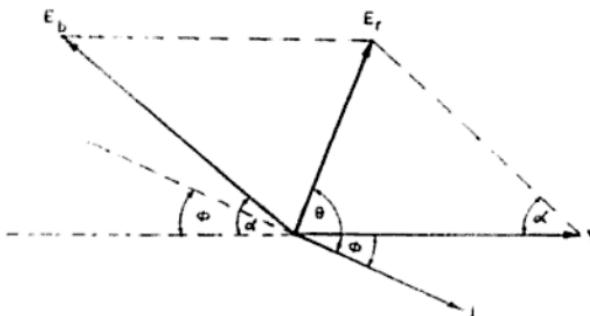


Fig. 70. Synchronous motor no-load vector diagram.

If the angle between stator and rotor pole centres become too great, due to a serious over-load then the rotor will pull out of synchronism and operate as an induction motor with the aid of the amortisseur winding. The maximum value of torque which a synchronous motor can develop without dropping out of synchronism is called the 'pull-out torque'. In most synchronous motors this is 150 to 200 per cent of rated torque output.

2.2.8. Torque developed by the motor

Refer Fig. 71.

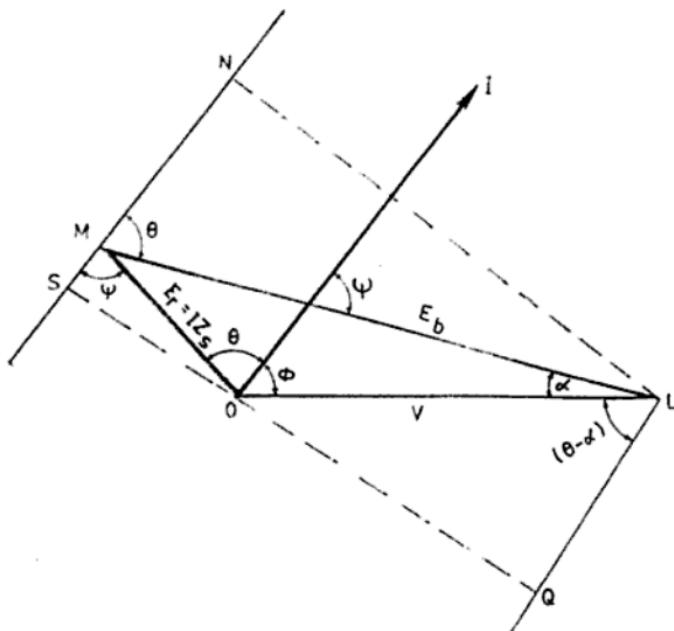


Fig. 71

OL = supply voltage/phase

I = armature current

LM = back e.m.f. at a load angle of α

OM = resultant voltage, $E_r = IX_s$ (or IX_s if R_a is negligible)

- I lags/leads V by an angle ϕ and lags behind E_r by an angle θ (internal angle)

$$= \tan^{-1} \left(\frac{X_s}{R_a} \right).$$

- Line NS is drawn at angle θ to LM .

- LN and QS are perpendicular to NS (hence to LQ also).

Mechanical power developed per phase in the rotor,

$$P_{\text{mech}} = E_b I \cos \psi$$

...(20)

In ΔOMS ,

Now,

$$MS = IZ_s \cos \psi$$

$$MS = NS - NM = LQ - NM$$

$$\therefore IZ_s \cos \psi = V \cos (\theta - \alpha) - E_b \cos \theta$$

$$\therefore I \cos \psi = \frac{V}{Z_s} \cos (\theta - \alpha) - \frac{E_b}{Z_s} \cos \theta$$

Putting this value in (20), we get

$$P_{\text{mech}/\text{phase}} = E_b \left[\frac{V}{Z_s} \cos (\theta - \alpha) - \frac{E_b}{Z_s} \cos \theta \right]$$

$$\text{or } P_{\text{mech}/\text{phase}} = \frac{E_b V}{Z_s} \cos (\theta - \alpha) - \frac{E_b^2}{Z_s} \cos \theta \quad \dots(21)$$

This is the expression for the mechanical power developed in terms of load angle (α) and the internal angle (θ) of the motor for a constant voltage V and E_b (or excitation because E_b depends on excitation only).

Maximum power developed. Condition for maximum power developed can be found by differentiating the above expression (eqn. 21) with respect to load angle and then equating it to zero.

$$\therefore \frac{dP_{\text{mech}}}{d\alpha} = -\frac{E_b V}{Z_s} \sin (\theta - \alpha) = 0 \quad \text{or} \quad \sin (\theta - \alpha) = 0$$

$$\therefore \theta = \alpha$$

Value of maximum power,

$$(P_{\text{mech}})_{\text{max}} = \frac{E_b V}{Z_s} - \frac{E_b^2}{Z_s} \cos \alpha$$

$$\frac{E_b V}{Z_s} - \frac{E_b^2}{Z_s} \cos \theta \quad \dots(22)$$

or

- This shows that the *maximum power and hence torque* (\because speed is constant) *depends on V and E_b i.e., excitation*.
- Maximum value of θ and hence α is 90° . For all values of V and E_b , this limiting value of α is the same but maximum torque will be proportional to the maximum power developed as given in eqn. (22).
- In Fig. 72 eqn. (21) is plotted.
- If R_a is neglected, then

$$Z_s = X_s \text{ and } \theta = 90^\circ$$

$$\therefore \cos \theta = 0$$

$$P_{\text{mech}} = \frac{E_b V}{X_s} \cos (90^\circ - \alpha) \quad [\text{from eq. (21)}]$$

$$\text{i.e., } P_{\text{mech}} = \frac{E_b V}{X_s} \sin \alpha \quad \dots(23)$$

This gives the value of mechanical power developed in terms of α —the basic variable of a synchronous machine.

$$\therefore (P_{\text{mech}})_{\text{max}} = \frac{E_b V}{X_s} \quad [\text{from eqn. (22)}]$$

This corresponds to the '*pull-out*' torque.

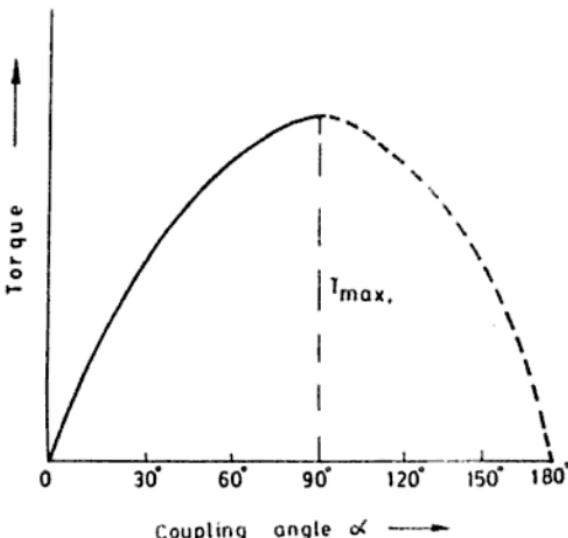


Fig. 72

The above value can be obtained by putting $\alpha = 90^\circ$ in eqn. (23).

- To determine the value of excitation or induced e.m.f. E_b to give maximum power developed possible, differentiate eqn. (22) with respect to E_b and equate to zero

$$\therefore \frac{d(P_{\text{mech}})_{\text{max}}}{dE_b} = \frac{V}{Z_s} - \frac{2E_b}{Z_s} \cos \theta = 0 \quad \text{or} \quad E_b = \frac{V}{2 \cos \theta}$$

Substituting $E_b = \frac{V}{2 \cos \theta}$ in eqn. (22), we get

$$\begin{aligned} (P_{\text{mech}})_{\text{max}} &= \frac{V^2}{2Z_s \cos \theta} - \frac{V^2}{4Z_s \cos \theta} \\ &= \frac{V^2}{4Z_s \cos \theta} = \frac{V^2}{4R_a} \end{aligned} \quad [\because Z \cos \theta = R_a]$$

where R_a = effective resistance of the motor.

$$\text{Hence } (P_{\text{mech}})_{\text{max}} = \frac{V^2}{4R_a} \quad \dots(24)$$

Torques of a synchronous motor :

The various torques associated with a synchronous motor are described below :

1. Starting torque :

- It indicates the ability of the motor to accelerate the load. It is also sometimes called "break away torque".

- It may be as low as 10 percent in case of centrifugal pumps, and as high as 200 or 250 percent of full-load torque, as in case of loaded reciprocating two-cylinder compressors.
- Although the synchronous motor possesses no self-starting torque yet in modern synchronous motors, by making proper changes in the design of damper windings, almost any reasonable torque can be developed.

2. Running torque :

- Running torque is the torque developed by the motor *under running conditions*.
- It is determined by the output power and speed of the driven machine.
- Peak output power determines the maximum torque that would be required by the driven machine. The breakdown or maximum running torque of a motor must be greater than this value in order to avoid stalling of the machine.

3. Pull-in torque :

- It pertains to the *ability of the motor to pull-into synchronism when changing from induction to synchronous motor operation*.

4. Pull-out torque :

- *It is the maximum torque which the motor will develop without pulling out of step or synchronism.*
- Its value varies from 1.25 to 3.5 times the full-load torque.

3. POLYPHASE INDUCTION MOTOR

3.1. General Aspects

Introduction. An induction motor is simply an *electric transformer* whose magnetic circuit is separated by an air gap into two relatively movable portions, one carrying the primary and the other the secondary winding. Alternating current supplied to the primary winding from an electric power system induces an opposing current in the secondary winding, when latter is *short-circuited or closed through an external impedance*. Relative motion between the primary and secondary structures is produced by the *electromagnetic forces corresponding to the power thus transferred across the air gap by induction*.

The essential feature which distinguishes the induction machine from other types of electric motors is that the secondary currents are created solely by induction, as in a transformer instead of being supplied by a D.C. exciter or other external power source, as in synchronous and D.C. machines.

Advantages. Three-phase induction motor is the *most commonly used motor* in industrial applications because of the *advantages* listed below :

- | | |
|--|------------------------|
| 1. Simple design | 2. Rugged construction |
| 3. Reliable operation | 4. Low initial cost |
| 5. Easy operation and simple maintenance | 6. High efficiency |
| 7. Simple control gear for starting and speed control. | |

Applications :

Induction motors are available with torque characteristics suitable for a *wide variety of loads* :

(i) The standard motor has a starting torque of about 120 to 150 per cent of full-load torque. Such motors are suitable for most applications.

(ii) For starting loads such as small refrigerating machines or plunger pumps operating against full pressure or belt conveyors, *high torque motors with a starting torque of twice normal full-load torque, or more, are used.*

(iii) For driving machines that use large flywheels to carry peak loads, such as punch presses and shears, a high-torque motor with a slip at full-load up to 10 per cent is available. *The high slip permits enough change in speed to make possible the proper functioning of the flywheel.*

(iv) By the use of a wound-rotor with suitable controller and external resistances connected in series with the rotor winding, it is possible to obtain any value of starting torque up to the maximum breakdown torque. *Such motors are well adapted as constant-speed drives for loads that have large friction loads to overcome at starting.*

3.2. Classification of A.C. Motors

Different A.C. motors may be classified as follows :

1. According to the 'type of current' :

- | | |
|------------------|-------------------|
| (i) Single-phase | (ii) Three-phase. |
|------------------|-------------------|

2. According to 'speed' :

- | | |
|-------------------------|---------------------|
| (i) Constant speed | (ii) Variable speed |
| (iii) Adjustable speed. | |

3. According to 'principle of operation' :

(A) Synchronous motors

- | | |
|-----------|-------------|
| (i) Plain | (ii) Super. |
|-----------|-------------|

(B) Asynchronous motors

(a) Induction motors :

- | | |
|--------------------------------------|--|
| (i) Squirrel cage | |
| —single | |
| —double | |
| (ii) Slip-ring (external resistance) | |

(b) Commutator motors :

- | | |
|------------------|--|
| (i) Series | |
| —single-phase | |
| —universal | |
| (ii) Compensated | |
| —conductively | |
| —inductively. | |

4. According to 'structural features' :

- | | |
|----------------------|------------------------------------|
| (i) Open | (ii) Enclosed |
| (iii) Semi-enclosed | (iv) Ventilated |
| (v) Pipe-ventilated | (vi) Riveted frame eye |
| (vii) Splash proof | (viii) Totally enclosed fan-cooled |
| (ix) Explosion proof | (x) Water proof. |

3.3. Constructional Details

3.3.1. The stator

- The stator frame consists of a symmetrical and substantial casting, having feet cast integral with it. The stator core, consisting of high grade, low loss electrical sheet-steel stampings, is assembled in the frame under hydraulic pressure. The thickness of

stampings/laminations is usually from 0.35 to 0.6 mm. The stator laminations are punched in one piece for small induction motor (Fig. 73). In induction machines of large size the stator core is assembled from a large number of segmental laminations.

The slots are sometimes of the 'open type' (i.e., having parallel walls) for the accommodation of former wound coils. But the usual practice is to have practically 'enclosed slots' in order to reduce the effective length of air-gap.

- The stator windings are given the utmost care to make them mechanically and electrically sound, so as to ensure long life and high efficiency. After the winding is in position it is thoroughly dried out whilst still hot and is completely immersed in a high grade synthetic resin varnish. It is then acid, alkali, moisture and oil proof.

For small motors working at ordinary voltages, single layer mush winding is used. For medium size machines double layer lap winding with diamond shaped coils is used. Single layer concentric windings are used for large motors working at high voltages.

- Frames of electrical machines house the stator core. Frames of small and medium sizes of induction motors have hollow cylindrical form and that of larger motors have the shape of a circular box. In small induction motors, having a frame diameter of up to about 150 cm, the frame also supports the end shields. The frame should be strong and rigid as rigidity is very important in the case of induction motors of large dimensions. This is because the length of the air gap is very small and if the frame is not rigid, it would create an irregular air gap around the machine resulting in production of unbalanced magnetic pull. Frames for small machines are made as a single unit and are usually cast. The frames of medium and large sized machines are fabricated from rolled steel plates.

3.3.2. The rotor.

The rotors are of two types :

1. Squirrel-cage ;
2. Wound rotor.

Squirrel-cage. The squirrel-cage rotor is made up of stampings (Fig. 74) which are keyed directly to the shaft. The slots are partially closed and the winding consists of embedded copper bars to which the short-circuited rings are brazed. The squirrel cage rotor is so robust that it is almost indestructible.

The great majority of present day induction motors are manufactured with squirrel-cage rotors, a common practice being to employ winding of cast aluminium. In this construction the assembled rotor laminations are placed in a mould after which molten aluminium is forced in, under pressure, to form bars, end rings and cooling fans as extension of end rings. This is known as die cast rotor and has become very popular as there are no joints and thus there is no possibility of high contact resistance.

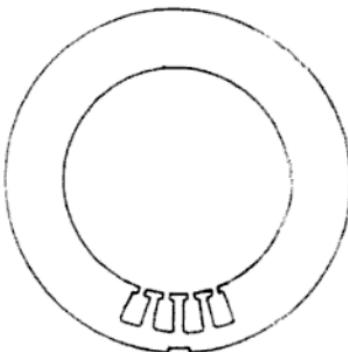


Fig. 73. Stator stamping.

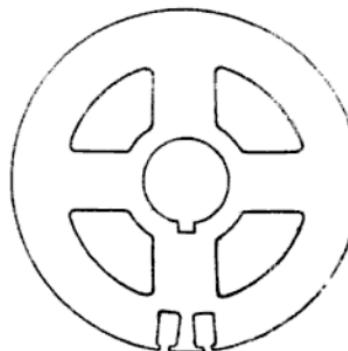


Fig. 74. Rotor stamping.

In this type of rotor, it may be noted that *slots are not made parallel to the shaft but they are 'skewed'* to serve the following purposes :

- (i) To make the motor run quietly by reducing the magnetic hum.
- (ii) To reduce the locking tendency of the rotor.

2. Wound rotor. The wound rotor has also slotted stampings and the windings are former wound. The wound rotor construction is employed for induction motors requiring speed control or extremely high values of starting torque. The wound rotor has completely insulated copper windings very much like the stator windings. The windings can be connected in star or delta and the three ends are brought out at the three slip rings. The current is collected from these slip rings with carbon brushes from which it is led to the resistances for starting purposes. When the motor is running, the slip rings are short-circuited by means of a collar, which is pushed along the shaft and connects all the slip rings together on the inside. Usually the brushes are provided with a device for lifting them from the slip rings when the motor has started up, thus reducing the wear and the frictional losses.

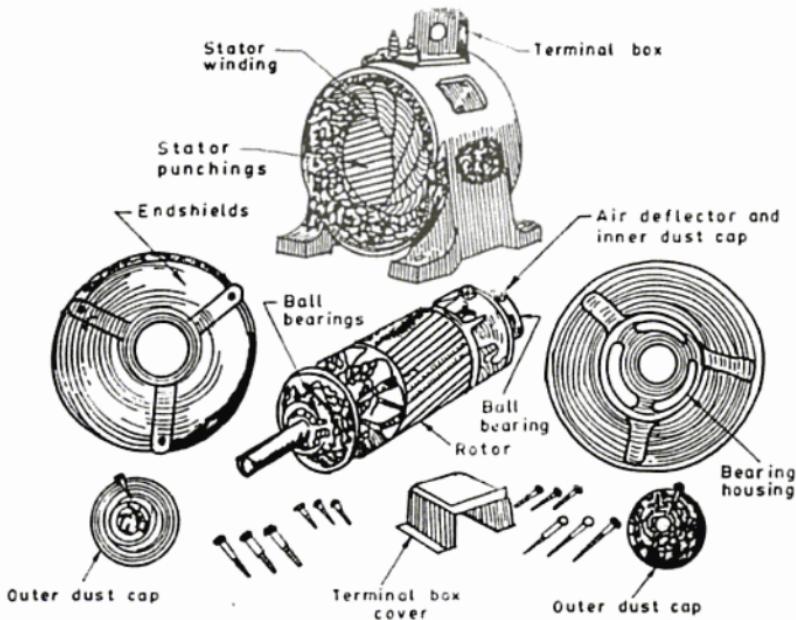


Fig. 75. Component parts of a small squirrel-cage induction motor.

The number of slots in the rotor should never be equal to the number of slots in the stator. If they are, there would be a variation of reluctance of the magnetic path from maximum, when teeth are opposite slots, to minimum when teeth are opposite teeth. The resulting flux pulsations would have a high frequency, since the periodic time would be the interval period for a tooth to occupy similar positions opposite two successive teeth. This will not only cause extra iron loss but the rotor will tend to lock with the stator if at the time of starting teeth are opposite teeth. The best plan is to make the number of the stator and the rotor teeth prime to each other.

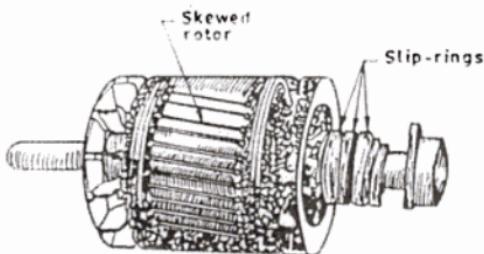


Fig. 76. Induction motor with phase-wound rotor, showing the three slip rings on the rotor shaft.
Figs. 77 and 78 show squirrel-cage and phase-wound induction motors respectively.

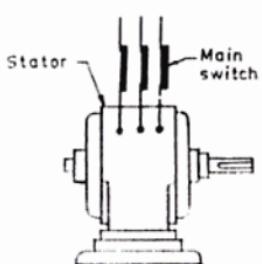


Fig. 77. Squirrel-cage motor.

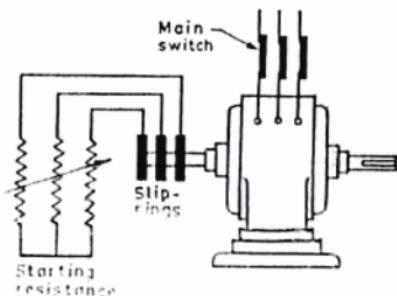


Fig. 78. Phase-wound motor connected to a three-phase star-connected starting resistance.

Advantages of a squirrel-cage motor over a phase-wound induction motor. As compared with a wound rotor a squirrel-cage induction motor entails the following advantages :

1. Slightly higher efficiency.
2. Cheaper and rugged in construction.
3. No slip rings, brush gear, short-circuiting devices, rotor terminals for starting rheostats are required. The star-delta starter is sufficient for starting.
4. It has better space factor for rotor slots, a shorter overhang and consequently a small copper loss.
5. It has a smaller rotor overhang leakage which gives a better power factor and a greater pull out torque and overload capacity.
6. It has bare end rings, a large space for fans and thus the cooling conditions are better.

The major '*disadvantage*' of squirrel-cage motor is that *it is not possible to insert resistance in the rotor circuit for the purpose of increasing the starting torque. The cage rotor has a smaller starting torque and large starting current as compared with wound rotor.*

3.3.3. Slip rings. The slip rings for wound rotor machines are made of either brass or phosphor bronze. They are shrunk on to a cast iron sleeve with moulded silica insulation. This assembly is passed on to the rotor shaft. The slip rings are rotated either between the core and the bearing or on the shaft extension. In the latter case the shaft is made hollow to allow the three connections from rotor to slip rings to pass through bearings.

3.3.4. Shaft and bearings. In an induction motor the air gap is made as small as possible. Therefore the shaft is made short and stiff in order that the rotor may not have any significant deflection, as even a small deflection would create large irregularities in the air gap which would lead to production of an unbalanced magnetic pull. There is also a possibility of rotor and stator fouling with each other. Ball and roller bearings are generally used as with their use, accurate centering is much simpler than with journal bearings. Also the overall length of machine is reduced. For small motors, a roller bearing may be used at the driving end and a ball bearing at the non-driving end. For large and heavy rotors journal bearings are used.

3.4. Production of Rotating Magnetic Field

- When a three-phase voltage is applied to the three-phase stator winding of the induction motor a rotating magnetic field is produced, which by transformer action induces a 'working' e.m.f. in the rotor winding. The rotor-induced e.m.f. is called a working e.m.f. because it causes a current to flow through the armature winding conductors. This combines with the revolving flux-density wave to produce torque. Thus revolving field is a key to the operation of the induction motor.

It will now be shown that when three-phase windings displaced in space by 120° , are fed by three-phase currents displaced in time by 120° , they produce a resultant magnetic flux which rotates in space as if actual magnetic poles were being rotated mechanically.

- Fig. 79 shows three-phase currents which are assumed to be flowing in phases 'T', 'm' and 'n' respectively. These currents are time-displaced by the 120 electrical degrees.
- Fig. 80 shows the stator structure and the three-phase winding. Each phase (normally distributed over 60 electrical degrees) for convenience is represented by a single coil. Thus coil $I-I'$ represents the entire phase 'T' winding having its flux axis directed along the vertical. This means that whenever phase 'T' carries current it produces a flux field directed along the vertical-up or down. The right-hand flux rule readily verifies this statement. Similarly, the flux axis of phase 'm' is 120 electrical degrees displaced from phase 'T'; and that of phase 'n' is 120 electrical degrees displaced from phase 'm'. The unprimed letters refer to the beginning terminals of each phase.
- Magnitude and direction of the resultant flux corresponding to time instant t_1 .** (Fig. 79). At this instant the current into phase 'T' is at its positive maximum value while currents in phases 'm' and 'n' are at one-half their maximum values. In Fig. 80 it is arbitrarily assumed that when current in a given phase is positive, it flows into the paper with respect to the unprimed conductors. Thus since, at time t_1 , i_T is positive, a cross is used for conductor 'T' [Fig. 80 (i)]. Of course a dot is used for I' because it refers to the return connection. Then by the right-hand rule it follows that phase 'T' produces a flux contribution directed downward along the vertical. Moreover, the magnitude of this contribution is the maximum value because the current is at maximum. Hence, $\phi_T = \phi_{\max}$, where ϕ_{\max} is the maximum flux per pole of phase 'T'. It is important to understand that



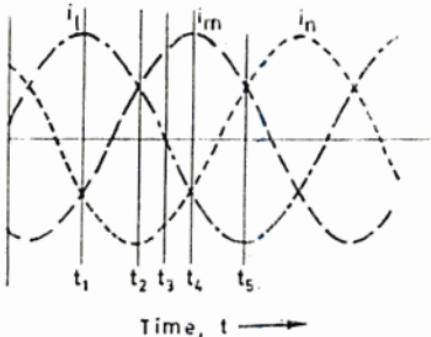


Fig. 79. Balanced three-phase alternating currents.

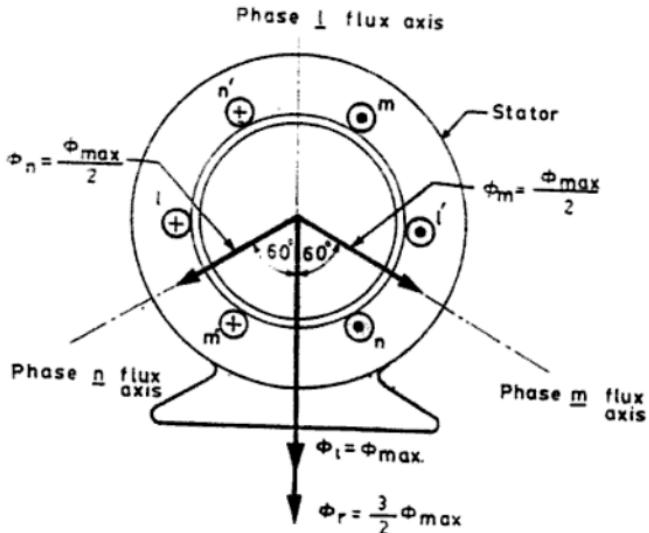

(i)

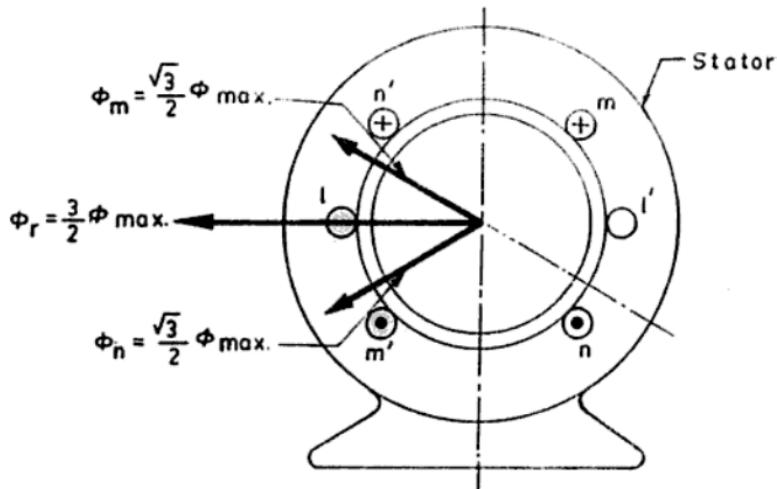

(ii)

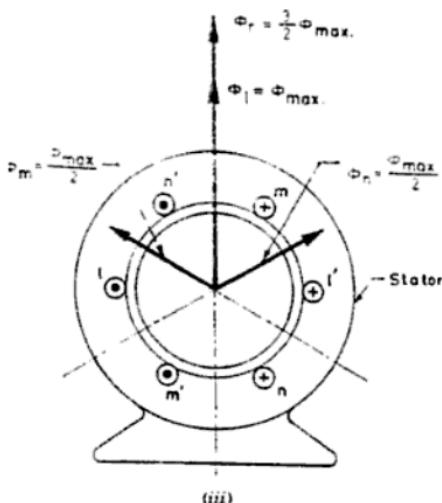


Fig. 80. Representing the rotating magnetic field at three instants of time :
(i) time t_1 in Fig. 7 ; (ii) time t_3 ; (iii) t_5 .

phase 'l'' really produces a sinusoidal flux field with the amplitude located along the axis of phase 'l' as shown in Fig. 81. However, in Fig. 80 (i) this sinusoidal distribution is conveniently represented by the vector Φ_l .

For determining the magnitude and direction of the field contribution of phase 'm' at time t_1 , we first find that the current in phase 'm' is negative with respect to that in phase 'l'. Hence the conductor that stands for the beginning of phase 'm' must be assigned a dot while 'm' is assigned a cross. Hence the instantaneous flux contribution of phase 'm' is directed downward along its flux axis and the magnitude of phase 'm' flux is one-half the maximum because the current is at one-half its maximum value. Similar reasoning leads to the result shown in Fig. 80 (i) for phase 'n'.

A glance at space picture corresponding to time t_1 , as illustrated in Fig. 80 (i), should make it apparent that the resultant flux per pole is directed downward and has a magnitude of $\frac{1}{2}$ times the

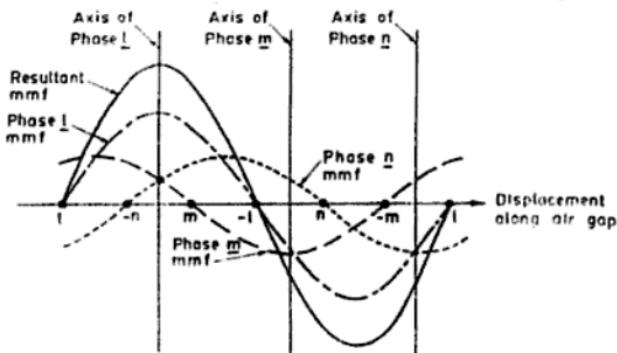


Fig. 81. Component and resultant field distributions corresponding to t_1 (Fig. 79).

maximum flux per pole of any one phase. Fig. 81 depicts the same results as Fig. 80 (i) but does so in terms of sinusoidal flux waves rather than flux vectors.

- **Magnitude and direction of the resultant flux corresponding to time instant t_3 [Fig. 80 (ii)].** Here phase 'l' current is zero, yields no flux contribution. The current in phase 'm' is positive and equal to $\frac{\sqrt{3}}{2}$ its maximum value. Phase 'n' has the same current magnitude but is negative. Together phases 'm' and 'n' combine to produce a resultant flux having the same magnitude as at time t_1 . See Fig. 80 (ii). It is important to note, too, that an elapse of 90 electrical degrees in time results in rotation of the magnetic flux field of 90 electrical degrees.
- **At time instant t_5 .** A further elapse of time equivalent to an additional 90 electrical degrees leads to the situation depicted in Fig. 80 (iii).

From the above discussion it is apparent that the application of three-phase currents through a balanced three-phase winding gives rise to a rotating magnetic field that exhibits the following two characteristics.

1. It is of constant amplitude.

2. It is of constant speed. It follows from the fact that the resultant flux traverses through 2π electrical radians in space for every 2π electrical radians of variation in time for the phases currents. Hence for a 2-pole machines where electrical and mechanical degrees are identical, each cycle of variation of current produces one complete revolution of the flux field. Hence *this is a fixed relationship which is dependent upon the frequency of the currents and number of poles for which the three-phase winding is designated*. In the case where the winding is designed for four poles it requires two cycles of variation of the current to produce one revolution of the flux field. Therefore it follows that for a p -pole machine the relationship is :

$$N_s = \frac{120f}{p} \quad \dots(25)$$

or $f = \frac{pN_s}{120} \quad \dots[25(a)]$

N_s (r.p.m.) is called the *synchronous speed* and all synchronous machines run at their respective synchronous speeds.

It may be noted that the speed of rotation of the field as described by eq. (25) is always given relative to the phase windings carrying the time-varying currents. Accordingly, if a situation arises where the *winding is itself revolving*, then the speed of rotation of the field relative to inertial force is different from it with respect to the winding.

3.5. Theory of Operation of an Induction Motor

When a three-phase is given to the stator winding a rotating field is set-up. This field sweeps past the rotor (conductors) and by virtue of relative motion, an e.m.f. is induced in the conductors which form the rotor winding. Since this winding is in the form of a closed circuit, a current flows, the direction of which is, by Lenz's law, such as to oppose the change causing it.

Now, the change is the relative motion of the rotating field and the rotor, so that, to oppose this, the rotor runs in the same direction as the field and attempts to catch up with it. It is clear that torque must be produced to cause rotation, and this torque is due to the fact that currents flow in the rotor conductors which are situated in, and at right angles to, a magnetic field.

Fig. 82 shows the induction motor action.

- When the motor shaft is *not loaded*, the machine has only to rotate itself against the mechanical losses and the rotor speed is *very close to the synchronous speed*. However, the

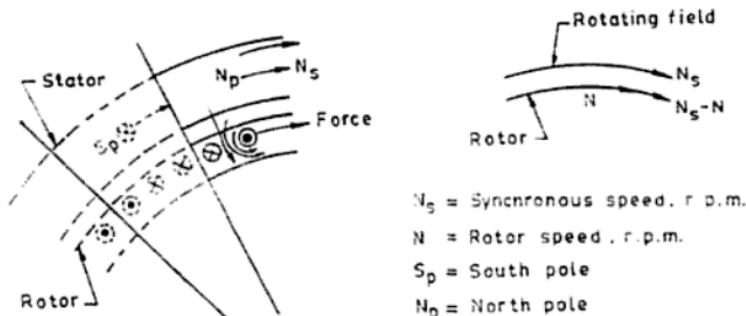


Fig. 82. Induction motor action.

rotor speed cannot become equal to the synchronous speed because if it does so, *the e.m.f. induced in the rotor winding would become zero and there will be no torque*. Hence the speed remains slightly less than the synchronous speed. If the motor shaft is *loaded*, the rotor will slow down and the relative speed of the rotor with respect to the stator rotating field will increase. The e.m.f. induced in the rotor winding will increase and will produce more rotor current which will increase the electromagnetic torque produced by the motor. Conditions of equilibrium are attained when the rotor speed has adjusted to a new value so that the electromagnetic torque is sufficient to balance the mechanical or load torque applied to the shaft. The speed of the motor *when running under full load conditions is somewhat less than the no-load speed*.

3.6. Slip

- As earlier stated, *the rotor speed must always remain less than the synchronous speed. The difference between the synchronous speed and the rotor speed is known as 'slip'*. It is usually expressed as a fraction of the synchronous speed. Thus slip s is

$$s = \frac{N_s - N}{N_s} \quad \dots(26)$$

or $N = N_s(1 - s)$...[26 (a)]

where N_s = synchronous speed (r.p.m.)

N = motor speed (r.p.m.).

In practice the value of slip is very small. At no-load, slip is around 1% or so and at full-load it is around 3%. For large efficient machines the slip at full-load may be around 1% only. The induction motor, is therefore, a motor with substantially constant speed and fills the same role as D.C. shunt motor.

- When the rotor is stationary (standstill) its speed is zero and $s = 1$. The rotor cannot run at synchronous speed because then there will be no rotor e.m.f. and no rotor current and torque. If the rotor is to run at synchronous speed an external torque is necessary. *If the rotor is driven such that $N > N_s$, the slip becomes negative, the rotor torque opposes the external driving torque and the machine acts as induction generator.*
- The induction motor derives its name from the fact that the *current in the rotor circuit is induced from the stator*. There is no external connection to the rotor except for some special purposes.

If the rotor reactance at standstill is X_2 its value at slip ' s ' becomes sX_2 . This is very desirable, for at no-load the reactance becomes almost negligible and the rotor impedance is now all resistance.

Further if the rotor resistance is small the rotor current is large, so that motor works with a large torque which brings the speed near to synchronous speed, i.e. the slip is reduced.

3.7. Frequency of Rotor Current

At standstill (i.e. when the rotor is stationary), the frequency of the rotor current is the same as the supply frequency (f). But when the rotor starts revolving, then the frequency depends upon the relative speed or slip-speed. If f_r is the frequency of the rotor current, then

$$N_s - N = \frac{120f_r}{p} \quad \dots(i)$$

$$\text{Also} \quad N_s = \frac{120f}{p} \quad \dots(ii)$$

Dividing (i) by (ii), we get

$$\frac{N_s - N}{N_s} = \frac{f_r}{f} \quad \text{or} \quad s = \frac{f_r}{f}$$

$$\text{or} \quad f_r = sf \quad \dots(27)$$

3.8. Rotor E.M.F. and Rotor Current

Rotor e.m.f.:

When the rotor is stationary, an induction motor is equivalent to a 3-phase transformer with secondary short-circuited. Therefore, the induced e.m.f. per phase E_2 in the rotor at the instant of starting is given as :

$$E_2 = E_1 \times \frac{N_2}{N_1} \quad \dots(28)$$

where E_1 = applied voltage per phase to primary i.e., stator winding,

N_1 = number of stator turns, and

N_2 = number of rotor turns.

When the rotor starts gaining speed, the relative speed of the rotor with respect to stator flux i.e. slip, is decreased. Hence induced e.m.f. in the rotor, which is directly proportional to the relative speed i.e. slip, is also decreased and is given by sE_2 . Hence for slip 's', the induced e.m.f. in the rotor is s times the induced e.m.f. in the rotor at standstill.

Rotor current :

Let R_2 = rotor resistance/phase,

L_2 = rotor inductance/phase, and

E_2 = induced e.m.f. of rotor/phase at standstill.

At standstill :

Induced e.m.f. of rotor/phase $= E_2$

Rotor winding resistance/phase $= R_2$

Rotor winding reactance/phase, $X_2 = 2\pi f L_2$ where f is the supply frequency

Rotor impedance/phase, $Z_2 = \sqrt{R_2^2 + X_2^2}$

\therefore Rotor current/phase $= \frac{E_2}{Z_2} = \frac{E_2}{\sqrt{R_2^2 + X_2^2}}$.

At slip 's' :

Induced e.m.f. of rotor/phase $= sE_2$

Rotor winding resistance $= R_2$

Rotor winding reactance $= 2\pi f L_2 = 2\pi s f L_2 = s(2\pi f L_2) = sX_2$

$$\begin{aligned} \text{Rotor winding impedance/phase} &= \sqrt{R_2^2 + (sX_2)^2} \\ \therefore \text{Rotor current/phase}, \quad I_2 &= \frac{sE_2}{\sqrt{R_2^2 + (sX_2)^2}} \\ &= \frac{sE_2}{\sqrt{R_2^2 + s^2X_2^2}} = \frac{E_2}{\sqrt{(R_2/s)^2 + X_2^2}} \end{aligned} \quad \dots(29)$$

The rotor current I_2 lags the rotor voltage E_2 by rotor power factor angle ϕ_2 given by

$$\phi_2 = \tan^{-1}\left(\frac{sX_2}{R_2}\right)$$

Power factor of rotor current,

$$\cos \phi_2 = \frac{R_2}{\sqrt{R_2^2 + s^2X_2^2}} = \frac{R_2/s}{\sqrt{(R_2/s)^2 + X_2^2}}. \quad \dots(30)$$

3.9. Torque and Power

The torque of an induction motor (being due to interaction of a rotor and stator fields),

$$T \propto \phi I_2 \cos \phi_2$$

where ϕ = flux of rotating stator,

I_2 = rotor current/phase, and

$\cos \phi_2$ = rotor power factor.

Since rotor e.m.f./phase at standstill, $E_2 \propto \phi$

∴

$$T \propto E_2 I_2 \cos \phi_2$$

or $T = kE_2 I_2 \cos \phi_2$ where k is any constant

... (31)

Substituting the value of I_2 and $\cos \phi_2$ from eqns. (5) and (6) in eqn. (7), we get

$$T = kE_2 \frac{sE_2}{\sqrt{R_2^2 + s^2X_2^2}} \times \frac{R_2}{\sqrt{R_2^2 + s^2X_2^2}}$$

$$\text{i.e., } T = \frac{ksR_2 E_2^2}{R_2^2 + s^2X_2^2} \quad \dots(32)$$

3.9.1. Starting torque. At start slip 's' = 1. Therefore, expression for starting torque may be obtained by putting $s = 1$ in eqn. 32.

$$\text{Starting torque, } T_{st} = \frac{kR_2 E_2^2}{R_2^2 + X_2^2}. \quad \dots(33)$$

3.9.2. Condition for maximum torque. The value of torque when motor is running is given by

$$T = \frac{ksR_2 E_2^2}{R_2^2 + s^2X_2^2}$$

Torque will be maximum when,

$$\frac{sR_2}{R_2^2 + s^2X_2^2} \quad \text{or} \quad \frac{R_2}{\frac{R_2^2}{s} + sX_2^2}$$

$$\text{or } \frac{R_2}{\left(\frac{R_2}{\sqrt{s}} - X_2 \sqrt{s}\right)^2 + 2R_2 X_2} \text{ is maximum, viz., } \frac{R_2}{\sqrt{s}} - X_2 \sqrt{s} = 0$$

or $s (= s_{mT}) = \frac{R_2}{X_2}$... (34)

(where s_{mT} = slip corresponding to maximum torque)

$$\therefore \text{Maximum torque, } T_{max} = \frac{kE_2^2}{2X_2} \quad \dots (35)$$

From the above expression, the following conclusions can be drawn :

- Maximum torque is *independent* of rotor circuit resistance.
- Maximum torque varies *inversely as standstill reactance* of the rotor. Therefore to have maximum torque, standstill reactance (*i.e.* inductance) of the rotor should be kept as small as possible.

- The slip at which the maximum torque occurs depends upon the resistance of the rotor.

The condition for getting maximum torque at starting can be obtained by putting $s = 1$ in eqn. (34).

Thus, starting torque will be maximum if

$$\frac{R_2}{X_2} = s = 1 \quad \text{or} \quad R_2 = X_2.$$

3.9.3. Starting torque of a squirrel-cage motor. The squirrel-cage rotor resistance is fixed and *small* as compared to its reactance which is very large especially *at start* (because at standstill the frequency of rotor current is equal to that of supply frequency). Hence, the starting current I_2 of the rotor, though very large in magnitude, *lags by a very large angle* behind E_2 ; consequently the starting torque per ampere is very poor. It is roughly 1.5 times the full-load torque although the starting current is 5 to 7 times the full-load current. Thus such motors are *not suitable* for applications where these have to be started against heavy loads.

3.9.4. Starting torque of a slip ring motor. In a slip ring motor the torque is increased by *improving its power factor by adding external resistance in the rotor circuit from the star-connected rheostat*; as the motor gains speed the rheostat resistance is gradually cut out. This additional resistance, however, increases the rotor impedance and so reduces the rotor current. At first, the effect of improved power factor *predominates the current-decreasing effect of impedance*, hence starting torque is increased. But after a certain point, the effect of increased impedance *predominates the effect of improved power factor and so the torque starts decreasing*.

3.9.5. Power. Eqn. (29) can be represented by a simple series circuit as shown in Fig. 83.

It is seen from this circuit that **per phase** power input (gross) to rotor,

$$P_p = E_2 I_2 \cos \phi_2$$

where $\cos \phi_2 = \frac{R_2/s}{\sqrt{(R_2/s)^2 + X_2^2}}$

$$\therefore P_p = \frac{E_2}{\sqrt{(R_2/s)^2 + X_2^2}} \cdot I_2 \frac{R_2}{s} = I_2^2 \frac{R_2}{s} \quad \dots (36)$$

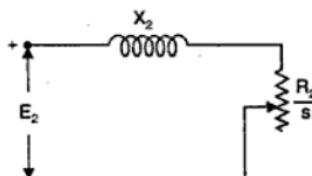


Fig. 83. Rotor equivalent circuit of an induction motor.

An examination of Fig. 83 also shows that per phase power input to rotor is equal to $I_2^2 \frac{R_2}{s}$ as the reactance is X_2 consumes no power.

P_g is the power transferred from stator to rotor across the air gap. In view of this, P_g is called the **air-gap power**. The expression for P_g may be written as

Since e.m.f. induced in rotor (at standstill), $E_2 \propto \phi \propto V$

$$\therefore T = \frac{k'sR_2V^2}{R_2^2 + s^2X_2^2}, \text{ where } k' \text{ is another constant}$$

Since the slip 's' at full-load is very low, therefore $s^2X_2^2$ can be neglected in comparison with R_2^2 .

$$\therefore T = \frac{k'sR_2V^2}{R_2^2} = \frac{k'sV^2}{R_2} \quad \text{or} \quad T \propto sV^2$$

When the supply voltage is changed, it changes the torque under running condition also. With the decrease in supply voltage torque under running condition decreases, therefore, in order to maintain the same torque, slip increases or speed decreases.

3.12. Full-Load Torque and Maximum Torque

Let, s_f = full-load slip of the motor, and

$$s_{mT} = \text{slip corresponding to maximum torque} = \frac{R_2}{X_2}$$

We know that,

$$\text{Full-load torque, } T_f = \frac{k s_f R_2 E_2^2}{R_2^2 + s_f^2 X_2^2} \quad [\text{From Art. 3.9}]$$

$$\text{Maximum torque, } T_m = \frac{k E_2^2}{2 X_2} \quad [\text{From Art. 3.9.2}]$$

$$\begin{aligned} \therefore \frac{T_f}{T_m} &= \frac{k s_f R_2 E_2^2 / (R_2^2 + s_f^2 X_2^2)}{k E_2^2 / (2 X_2)} = \frac{2 s_f R_2 X_2}{R_2^2 + s_f^2 X_2^2} \\ &= \frac{2 s_f R_2 X_2 / (X_2^2)}{(R_2^2 + s_f^2 X_2^2) / (X_2^2)} \quad [\text{Dividing numerator and denominator by } X_2^2] \\ &= \frac{2 s_f (R_2 / X_2)}{(R_2 / X_2)^2 + s_f^2} = \frac{2 s_f s_{mT}}{s_{mT}^2 + s_f^2} \end{aligned}$$

$$\text{i.e., } \frac{T_f}{T_m} = \frac{2 s_f s_{mT}}{s_f^2 + s_{mT}^2} \quad \dots(41)$$

$$= \frac{2}{\frac{s_f}{s_{mT}} + \frac{s_{mT}}{s_f}} \quad [\text{Dividing numerator and denominator by } s_f s_{mT}] \quad \dots(41a)$$

3.13. Starting Torque and Maximum Torque

$$\frac{T_{st}}{T_m} = \frac{k R_2 E_2^2 / (R_2^2 + X_2^2)}{k E_2^2 / (2 X_2)} = \frac{2 R_2 X_2}{R_2^2 + X_2^2} = \frac{2 (R_2 / X_2)}{(R_2 / X_2)^2 + 1}$$

(Dividing numerator and denominator by X_2^2)

$$\text{or } \frac{T_{st}}{T_m} = \frac{2 s_{mT}}{s_{mT}^2 + 1} \quad \dots(42)$$

3.14. Torque-Slip and Torque-Speed Curves

The expression for torque is as follows :

$$T = \frac{ksR_2E_2^2}{R_2^2 + s^2X_2^2}$$

From the above expression, it is evident, that

- Torque is zero when slip $s = 0$ (*i.e.*, speed is synchronous).
- When slip 's' is *very low* the value of the term sX_2 is very small and is negligible in comparison with R_2 , therefore torque T is approximately proportional to slip 's' if rotor resistance R_2 is constant. This means that at speeds near to synchronous speed the *torque-speed* and *torque-slip* curves are approximately straight lines (Figs. 84 and 85).
- When the slip 's' increases (*i.e.* as the speed decreases with increase in load) torque increases and reaches its maximum value when $s = \frac{R_2}{X_2}$. The *maximum torque is also known as 'pull-out' or 'break-down' torque*.

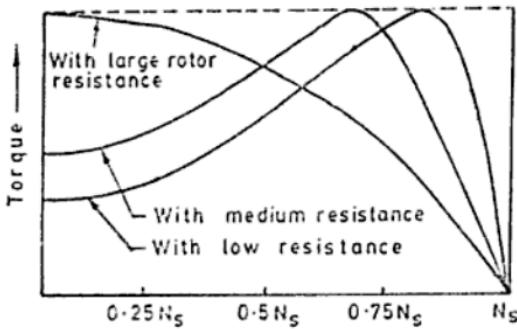


Fig. 84. Torque-speed curves.

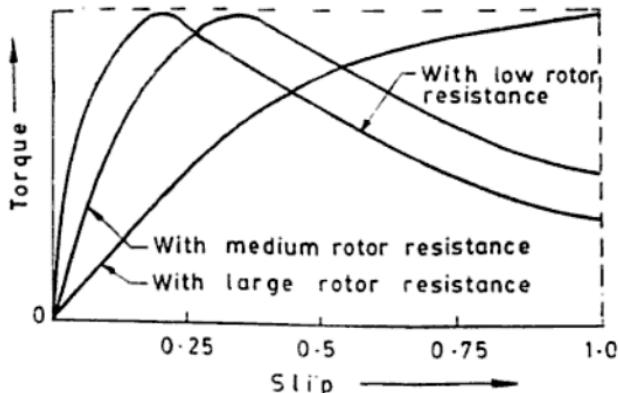


Fig. 85. Torque-slip curves.

normal range operation of the squirrel-cage induction motor. Even under normal operation, however, a suddenly applied load may require the temporary development of this maximum torque, after which the motor will speed up to its full-load value. Thus, in a manner similar to the shunt motor, the induction motor *inherently adjusts itself to the applied external torque*.

Fig. 86 shows typical operating characteristics of an induction motor.

Fig. 87 shows the effect of heavy loads on primary stator current and power factor.

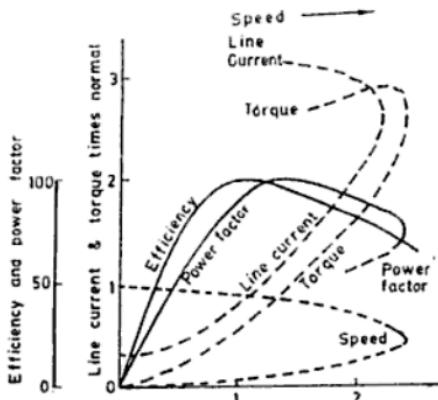


Fig. 87. Effect of heavy loads on primary stator current and power factor.

3.16. Operating Characteristics of a Wound-rotor (Slip Ring) Induction Motor

Fig. 88 shows a wound-rotor induction motor with controller (rheostat).

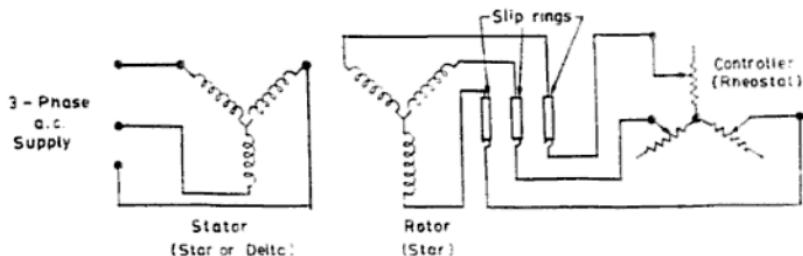


Fig. 88. Phase-wound motor with controller.

If the external controller is set at zero resistance, the motor operates almost exactly the same as the squirrel-cage motor, since the rotor is short-circuited. Suppose now the rotor is rotating at a constant speed and developing torque to carry a given load. The controller is moved so that the *rotor resistance per phase is doubled per phase*. The following reactions will be observed :

- The current in the rotor falls to *half of its previous value* (neglecting a transient effect), since the rotor speed, and hence the rotor voltage, cannot change instantaneously.
- The *developed torque decreases due to reduced rotor current*.

- The load on the motor has not changed, and with the external applied, or load, torque now greater than the developed torque, the motor slows down.
- The slip increases (increasing the rate at which the stator flux cuts the rotor conductors).
- The rotor induced voltage increases.
- The rotor current now increases until it is sufficient to develop enough torque to again carry the load at a constant speed.

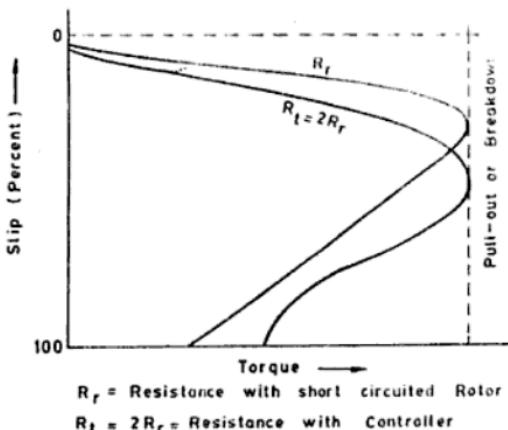


Fig. 89. Torque-slip characteristic of wound-rotor induction motor.

The induction motor now rotates at a lower speed, but with the same current as before, and develops the same torque as it did before the rotor circuit resistance was increased. The frequency in the rotor is greater, as is the rotor resistance. Rotor resistance and reactance are both increased in same proportion, however, and the rotor power factor therefore remains the same. If more load is now placed on the shaft, the rotor will develop the required torque, but always at a lower speed i.e. a higher slip. Eventually pull-out torque is attained. The value of pull-out torque will be the same as with the short-circuited rotor, but it will occur at a slip which is twice as great as that with the shorted rotor, since the rotor circuit resistance is twice that of the rotor alone.

Fig. 90 shows the torque-slip characteristic of the shorted rotor, together with that for a total resistance of, $R_t = 2R_r$.

It is worthnoting that the torque developed at standstill is higher with increased rotor resistance. This is explained by the fact that at standstill the rotor frequency is equal to the line frequency and rotor resistance is maximum. The addition of resistance in the rotor circuit obviously improves the power factor in that circuit while reducing the rotor current. Since standstill rotor resistance is much greater than

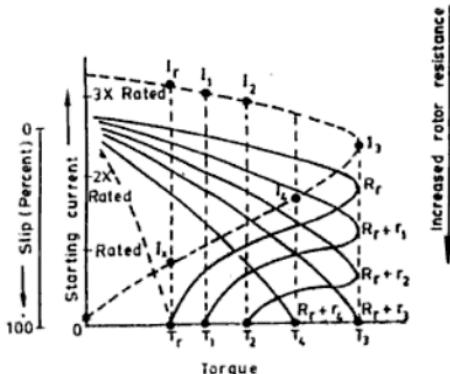


Fig. 90. Starting currents vs torque.

its resistance, the power factor increases more rapidly than the decrease of rotor current, and hence the developed torque is greater with added resistance.

Fig. 90 shows starting current vs torque.

Fig. 91 shows the effect of change of rotor resistance on starting and running characteristics. In Figs. 90 and 91,

R_r = basic rotor resistance

r_1, r_2, r_3, r_4 = the resistance added to each phase of star-connected wound rotor respectively.

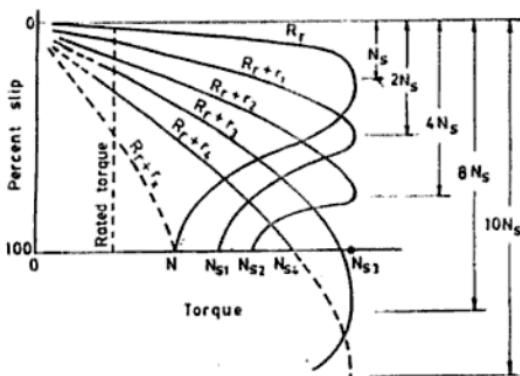


Fig. 91. Effect of change of rotor resistance on starting and running characteristics.

Slip, Starting Torque, Maximum Torque

Example 32. A 3-phase, 4-pole, 50-Hz induction motor is running at 1440 r.p.m. Determine the slip speed and slip.

Solution. Number of poles, $p = 4$

Frequency, $f = 50 \text{ Hz}$

Actual speed of rotor, $N = 1440 \text{ r.p.m.}$

Slip speed = ?

Slip = ?

$$\text{Synchronous speed, } N_s = \frac{120f}{p} = \frac{120 \times 50}{4} = 1500 \text{ r.p.m.}$$

$$\text{Slip speed } = N_s - N = 1500 - 1440 = 60 \text{ r.p.m. (Ans.)}$$

$$\text{Slip, } s = \frac{N_s - N}{N_s} = \frac{1500 - 1440}{1500} = 0.04. \text{ (Ans.)}$$

Example 33. A 3-phase induction motor has 2 poles and is connected to 400 V, 50 Hz supply. Calculate the actual rotor speed and rotor frequency when the slip is 4%. (B.T.E. U.P., 1998)

Solution. Given : $p = 2; s = 4\% = 0.04; f = 50 \text{ Hz.}$

$$\text{Synchronous speed, } N_s = \frac{120f}{p} = \frac{120 \times 50}{2} = 3000 \text{ r.p.m.}$$

$$\text{Rotor speed, } N = N_s(1 - s) = 3000(1 - 0.04) = 2880 \text{ r.p.m. (Ans.)}$$

$$\text{Rotor frequency, } f_r = s.f = 0.04 \times 50 = 2 \text{ Hz. (Ans.)}$$

- (v) What is the corresponding speed of the rotor with respect to the stator ?
 (vi) What is the corresponding speed of the rotor field with respect to the stator field ?
 (vii) What is the rotor frequency at the slip of 10 per cent ? (AMIE, 1997)

Solution. Given : $N_0 = 1000$ r.p.m., $N_f = 950$ r.p.m., $f = 50$ Hz

Since no-load speed of motor is almost 1000 r.p.m., hence synchronous speed near to 1000 r.p.m. is 1000 r.p.m.

$$(i) \text{Poles on motor, } p = \frac{120f}{N_s} = \frac{120 \times 50}{1000} = 6. \quad (\text{Ans.})$$

$$(ii) \text{Percentage slip at full load, } s_f = \frac{N_s - N_f}{N_s} \times 100 = \frac{1000 - 950}{1000} \times 100 = 5\%. \quad (\text{Ans.})$$

$$(iii) \text{Frequency of rotor voltage, } f_r = s \times f = \frac{5}{100} \times 50 = 2.5 \text{ Hz.} \quad (\text{Ans.})$$

$$(iv) \text{Speed of rotor field with respect to rotor} = \frac{120 \times f_r}{p} = \frac{120 \times 2.5}{6} = 50 \text{ r.p.m.} \quad (\text{Ans.})$$

(v) Speed of rotor with respect to stator = 950 r.p.m. (since stator is stationary). (Ans.)

(vi) Rotor field and stator field are revolving at the same speed of 1000 r.p.m., therefore, speed of rotor field w.r.t. stator field is zero. (Ans.)

$$(vii) \text{Rotor frequency at slip of 10\%, } f_r = s' \times f = \frac{10}{100} \times 50 = 5 \text{ Hz.} \quad (\text{Ans.})$$

Example 39. In a 6-pole, 3-phase, 50 Hz motor with star-connected rotor, the rotor resistance per phase is 0.3 Ω, the reactance at standstill is 1.5 Ω per phase, and an e.m.f. between the slip rings on open circuit is 175 V. Find :

(i) Slip at a speed of 950 r.p.m. ;

(ii) Rotor e.m.f. per phase ;

(iii) Rotor frequency and reactance at a speed of 950 r.p.m.

(B.T.E. Pb., 1997)

Solution. Given : $p = 6$; $f = 50$ Hz; $R_2 = 0.3$ Ω, $X_2 = 1.5$ Ω; $N = 950$ r.p.m.

$$\text{Synchronous speed, } N_s = \frac{120f}{p} = \frac{120 \times 50}{6} = 1000 \text{ r.p.m.}$$

(i) **Slip, s :**

$$s = \frac{N_s - N}{N_s} = \frac{1000 - 950}{1000} = 0.05 \text{ or } 5\%. \quad (\text{Ans.})$$

(ii) **Rotor e.m.f. per phase, E_2 :**

$$\text{Rotor e.m.f. per phase at standstill} = \frac{E_2}{\sqrt{3}} = \frac{175}{\sqrt{3}} = 101 \text{ V/phase}$$

Rotor e.m.f. at 5% slip = $sE_2 = 0.05 \times 101 = 5.05$ V/phase. (Ans.)

(iii) **Rotor frequency and reactance at a speed of 950 r.p.m. :**

Rotor frequency, $f_r = s \times f = 0.05 \times 50 = 2.5$ Hz. (Ans.)

Rotor reactance = $sX_2 = 0.05 \times 1.5 = 0.075$ Ω/phase. (Ans.)

Example 40. A 50 Hz, 440 V, 3-phase, 4-pole induction motor develops half the rated torque at 1490 r.p.m. With the applied voltage magnitude remaining at the rated value, what should be its frequency if the motor has to develop the same torque at 1600 r.p.m.? Neglect stator and rotor winding resistances, leakage reactances and iron losses. (GATE, 1995)

Solution. Given : $f = 50$ Hz; $p = 4$; $N = 1490$ r.p.m.; New speed, $N_n = 1600$ r.p.m.

$$\text{Synchronous speed, } N_s = \frac{120f}{p} = \frac{120 \times 50}{4} = 1500 \text{ r.p.m.}$$

$$\text{Slip at a speed of } 1490 \text{ r.p.m., } s = \frac{N_s - N}{N_s} = \frac{1500 - 1490}{1500} = 0.00667$$

Since torque developed by an induction motor, $T \propto sV^2$ (Refer Art. 11)

Slip s for constant torque and constant applied voltage remains unchanged.

$$\therefore \text{New synchronous speed, } N_{sn} = \frac{N_n}{1-s} = \frac{1600}{1-0.00667} = 1610.7 \text{ r.p.m.}$$

$$\text{New frequency, } f_n = \frac{p \times N_{sn}}{120} = \frac{4 \times 1610.7}{120} = 53.7 \text{ Hz. (Ans.)}$$

Example 41. A 3-phase slip ring induction motor gives a reading of 60 V across slip rings on open circuit when at rest with normal stator voltage applied. The motor is star-connected and has impedance of $(0.6 + j6) \Omega$ per phase. Find the rotor current when the machine is : (i) at standstill with slip rings joined to a star-connected starter with a phase impedance of $(5 + j4) \Omega$; and (ii) running normally with a 4 per cent slip.

Solution. Impedance of motor per phase = $(0.6 + j6) \Omega$

Phase impedance of star-connected starter = $(5 + j4) \Omega$

(i) At standstill :

Induced e.m.f. in the rotor winding per phase,

$$E_2 = \frac{60}{\sqrt{3}} = 34.64 \text{ V}$$

Resistance per phase in the rotor circuit,

$$R_2 = 0.6 + 5 = 5.6 \Omega$$

Reactance per phase in the rotor circuit,

$$X_2 = 6 + 4 = 10 \Omega$$

Impedance per phase in rotor circuit,

$$Z_2 = \sqrt{R_2^2 + X_2^2} = \sqrt{(5.6)^2 + (10)^2} = 11.46 \Omega$$

$$\text{Rotor current per phase, } I_2 = \frac{E_2}{Z_2} = \frac{34.64}{11.46} = 3.02 \text{ A. (Ans.)}$$

$$\text{Power factor, } \cos \phi_2 = \frac{R_2}{Z_2} = \frac{0.6}{11.46} = 0.488 \text{ (lag). (Ans.)}$$

(ii) Running at 4 per cent slip :

Induced e.m.f. on the rotor winding per phase

$$= sE_2 = 0.04 \times 34.64 = 1.38 \text{ V}$$

Rotor impedance per phase,

$$Z_2 = \sqrt{R_2^2 + (sX_2)^2} = \sqrt{(0.6)^2 + (0.04 \times 6)^2} \\ = 0.646 \Omega$$

[Here $R_2 = 0.6 \Omega$]

Rotor current per phase,

$$I_2 = \frac{sE_2}{Z_2} = \frac{1.38}{0.646} = 2.136 \text{ A. (Ans.)}$$

$$\text{Power factor, } \cos \phi_2 = \frac{R_2}{Z_2} = \frac{0.6}{0.646} = 0.928 \text{ (lag). (Ans.)}$$

Example 42. A 3-phase induction motor has a star-connected rotor. The rotor e.m.f. (between slip rings) at standstill is 50 V. The rotor resistance and standstill reactance are 0.5Ω and 3Ω respectively. Find :

(i) Rotor current per phase at starting and the slip rings short-circuited.

(ii) Rotor current per phase at starting if a star connected rheostat of resistance 6Ω per phase is connected across the slip rings.

(iii) Full-load rotor current and rotor power factor if the full-load slip is 4 per cent.

(iv) Rotor e.m.f. per phase under full-load condition.

Solution. Rotor e.m.f. at standstill (between slip rings)

$$= 50 \text{ V}$$

∴ Rotor e.m.f./phase at standstill,

$$E_2 = \frac{50}{\sqrt{3}} = 28.87 \text{ V}$$

Rotor resistance/phases, $R_2 = 0.5 \Omega$

Rotor reactance/phases, $X_2 = 3 \Omega$

(i) At starting $s = 1$

We know that rotor current/phases (I_2) is given by,

$$I_2 = \frac{sE_2}{\sqrt{R_2^2 + (sX_2)^2}} \quad \dots(i)$$

∴ Rotor current/phases at starting

$$= \frac{E_2}{\sqrt{R_2^2 + X_2^2}} = \frac{28.87}{\sqrt{(0.5)^2 + (3)^2}} = 9.49 \text{ A. (Ans.)}$$

(ii) Total resistance in the rotor circuit

$$= \text{rheostat resistance} + \text{rotor resistance} = 6 + 0.5 = 6.5 \Omega$$

∴ Rotor current/phases with rheostat resistance,

$$I_2 = \frac{28.87}{\sqrt{(6.5)^2 + (3)^2}} = 4.03 \text{ A. (Ans.)}$$

(iii) Full-load slip, $s_f = 4\% = 0.04$

Full-load rotor current (as per eqn. (i)),

$$I_2 = \frac{0.04 \times 28.87}{\sqrt{(0.5)^2 + (0.04 \times 3)^2}} = 2.246 \text{ A. (Ans.)}$$

$$\text{Rotor power factor} = \frac{R_2}{\sqrt{R_2^2 + (s_f X_2)^2}} = \frac{0.5}{\sqrt{(0.5)^2 + (0.04 \times 3)^2}} = 0.972. \text{ (Ans.)}$$

(iv) Rotor e.m.f./phase under full-load condition

$$= sE_2 = 0.04 \times 28.87 = 1.155 \text{ V. (Ans.)}$$

3.17. Starting of Induction Motors

Small induction motors (up to 2 kW) capacity may directly be switched on to the supply mains, but those of higher capacity must use some type of starting device, or starters as they are commonly called. The function of these starters is to restrict the initial rush of current, which, in the case of induction motors, is about 5 times the full-load current. This excessive current has two major upsetting effects, namely, a large voltage drop in the distributing network and causing stoppage of machines which are already running on the supply mains. Hence the Electrical Undertaking Authorities forbid the users of large capacity induction motors to directly switch on their machines.

The principle of all starting devices is to impress lower voltage on stator phases at the time of starting, or if the motor is slip ring or wound rotor, then to include external resistance in each rotor phase to keep the initial rotor current to a low value, this consequently means less current in the stator phases and therefore in the supply mains.

Direct-on-line starting of induction motors. This method means switching the motor directly on to the supply without using any device for reducing the starting current. The method is restricted to small motors up to about 2 kW. For these small motors, the *starting torque is about twice the full-load torque*. Hence the starting period lasts only a few seconds.

Some of the starting devices for starting induction motors are discussed below :

Squirrel-Cage Motors :

- (i) Stator rheostat starter.
- (ii) Auto-transformers (auto-starters).
- (iii) Star-delta starter.

Slip Ring Motors :

- (1) Rotor rheostat.

3.17.1. Squirrel-cage motors

3.17.1.1. Stator rheostat starter. The connection diagram is shown in Fig. 92.

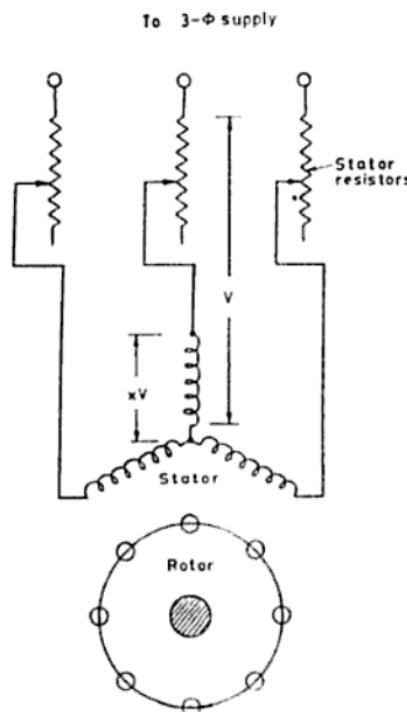


Fig. 92. Stator rheostat starter.

Reduced voltage is impressed on each stator phase due to the resistance R of the rheostat. Hence the initial current drawn from the supply mains will be *less* than if the machine were to be switched directly on to the supply mains.

- This method is suitable for starting of *small machines only*.

Advantages : 1. High power factor during start.

2. Smooth acceleration.

3. Less expensive than auto-transformer starter in lower output ratings.

4. Closed transition starting.

Disadvantages : 1. Heat is given off by the resistors.

2. Expensive resistors are required because starting duration usually exceeds 5 seconds.

3. Low torque efficiency.

3.17.1.2. Auto-transformers. Fig. 93 shows the connection diagram for auto-transformer starting of squirrel-cage induction motors.

In this method the reduced voltage is obtained by taking tappings at suitable points from a three-phase auto-transformer (Fig. 93). The auto-transformers are generally tapped at the 50, 60 and 80 per cent points, so that adjustment at these voltages may be made for proper starting torque requirements. Since the contacts frequently break large values of current arcing is sometimes quenched effectively by having them assembled to operate in an oil bath.

Auto-transformers may be either normally, or magnetically operated.

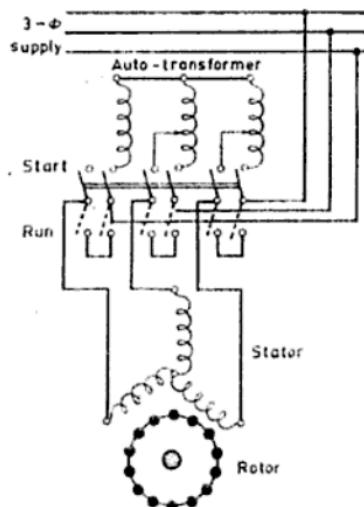


Fig. 93. Auto-transformer starter.

Advantages :

1. Voltage is reduced by transformation and not by dropping the voltage in resistors, and therefore, the current and power drawn from the supply mains are also reduced in comparison to resistor starting.

2. Availability of highest torque per ampere of supply current.
3. Adjustment of starting voltage by selection of proper tap on the auto-transformer.
4. The method is suitable for long starting periods.
5. Motor current larger than supply current.
6. Closed transition starting.

Disadvantages :

1. Low power factor.
2. Higher cost in case of lower output rating motors.
- This method can be used for starting of star-connected as well as delta-connected motors.
- This method is often employed for starting of large cage motors (rating exceeding 20 kW).

3.17.1.3. Star-delta starter. Star-delta switching method is based upon the principle that with three windings connected in star, voltage across each winding is $\frac{1}{\sqrt{3}}$ i.e., 57.7% of the line to line voltage whereas the same windings connected in delta will have full-line-to-line voltage across each.

The star-delta starter connects the three stator windings in star across the rated supply voltage at the starting instant. After the motor attains speed the same windings through a change over switch are re-connected in delta across the same supply voltage.

The basic connection diagram of a star-delta starter is shown in Fig. 94. An actual starter incorporates under-voltage and over-load coils. The starter is also provided with a mechanical inter-locking device to prevent the handle from being put in the 'Run' position first. Such starters are employed for starting 3-phase squirrel-cage induction motors of rating between 4 kW and 15 kW.

When star-connected, the applied voltage over each motor phase is reduced by a factor of $\frac{1}{\sqrt{3}}$ and hence the torque becomes $\frac{1}{3}$ of that which would have been developed if motor were directly connected in delta. The line current is reduced to $\frac{1}{3}$. Hence, during starting period when motor is star-connected, it takes $\frac{1}{3}$ rd as much starting current and develops $\frac{1}{3}$ rd as much torque as would have been developed were it directly connected in delta.

- This method reduces the starting line current to one-third but the starting torque is also reduced by the same amount.
- *This method is cheap but limited to applications where high starting torque is not necessary e.g., machine tools, pumps, motor-generator sets etc.*

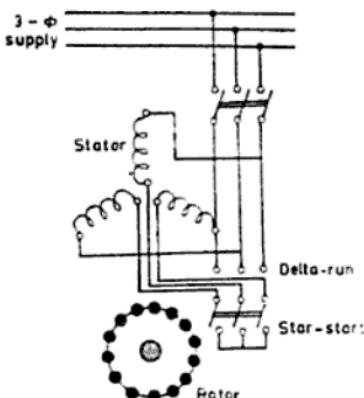


Fig. 94. Star-delta starter.

- The method is unsuitable for motors for voltage exceeding 3000 V because of the excessive number of stator turns needed for delta connection.
- Such starters are employed for starting 3-phase squirrel cage induction motors of rating between 4 and 20 kW.

Precaution with star-delta starting. When the motor is started in star the initial current flowing is 57.7% of the short-circuit current in delta together with a transient in each phase. The transient currents decay rapidly but the steady state is not reached until the motor has attained 70% of its synchronous speed. The change-over from star to delta connection should not be made until the motor attains 90% of synchronous speed, otherwise there will be a current surge considerably greater than full-load current which may even be greater than the standstill current with star-connection.

3.17.2. Slip-ring induction motors—starting of

(i) **Rotor rheostat.** The slip-ring induction motors are practically always started with full line voltage applied across the stator terminals. The value of starting current is adjusted by introducing a variable resistance in the rotor circuit. The controlling resistance is in the form of rheostat connected in star (Fig. 95), the resistance being gradually cut out of the rotor circuit as the motor gathers speed. By increasing the rotor resistance, not only is the rotor (and hence stator) current reduced at starting but at the same time torque is also increased due to improvement in power factor.

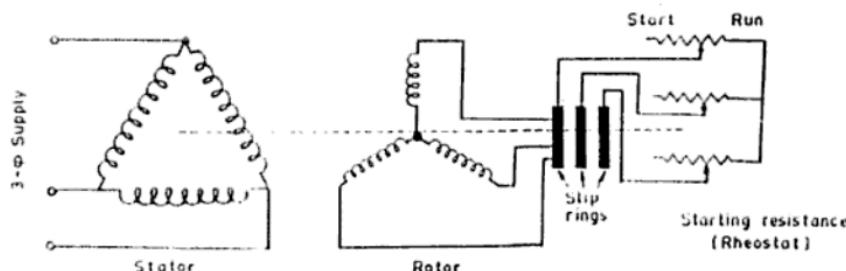


Fig. 95. Starting of slip-ring induction motor.

The rheostat is either of stud or contractor type and may be hand operated or automatic.

As discussed earlier, the introduction of additional external resistance in the rotor circuit enables slip-ring motor to develop a high starting torque with reasonably moderate starting current. Hence such motors can be started under load. When the motor runs under normal conditions the rings are short-circuited and brushes lifted from them.

3.18. Squirrel-Cage Motors—Advantages, Disadvantages and Applications

Advantages :

1. Cheaper in cost.
2. Simple and rugged in construction.
3. Maintenance cost is low.
4. Explosion proof.
5. Can be cooled better because of base end rings.

6. More pull-out torque and greater maximum power output.
7. Simple starting arrangement.
8. Nearly constant speed.
9. High overload capacity.
10. High power factor.

Disadvantages :

1. *Poor starting torque* due to low rotor resistance.
2. At the instant of switching on, *draws a large current* from the line.
3. *Very sensitive to change in supply voltage.*
4. *At light load the power factor is very low.*
5. *Speed regulation not possible.*

Applications. Suitable for industrial drives of small power where *speed control is not required* such as :

- Flour mills
- Printing machinery
- Other shaft drives of small power.

Note. When the squirrel cage motors are used for crane or hoist work where large starting torque is more important than high efficiency owing to the intermittent nature of load, the rotor resistance is increased by employing the end rings, and sometimes the bars as well, of high resistance metal such as German silver.

3.19. Wound Rotor (or Slip Ring) Induction Motors—Advantages, Disadvantages and Applications

Advantages :

1. High starting torque.
2. High over-load capacity.
3. Nearly constant speed.
4. Low starting current (in comparison with squirrel cage motor).

Disadvantages :

1. Low power factor at light loads.
2. Lower efficiency and lower power factor (in comparison to squirrel cage motor).
3. Sensitivity to fluctuations in supply voltage.
4. Higher initial and maintenance costs.
5. Speed regulation is poor when operated with external resistances in the rotor circuit.

Applications. Suitable for most industrial drives of high power where high starting torque is required such as for driving :

- Line shafts
- Pumps
- Lifts
- Generators
- Winding machines
- Mills etc.

- B. Shaded-pole induction motor.
 - C. Reluctance-start induction motor.
 - D. Repulsion-start induction motor.
- 2. Commutator-Type, Single-Phase Motors :**
- A. Repulsion motor.
 - B. Repulsion-induction motor.
 - C. A.C. series motor.
 - D. Universal motor.
- 3. Single-phase Synchronous Motors :**
- A. Reluctance motor.
 - B. Hysteresis motor.
 - C. Sub-synchronous motor.

4.3. Single-Phase Induction Motors

4.3.1. Applications and disadvantages

Applications :

- Single phase induction motors are in very wide use in industry especially in *fractional horse-power field*.
They are extensively used for electric drive for *low power constant speed apparatus* such as *machine tools, domestic apparatus* and *agricultural machinery* in circumstances where a three-phase supply is *not* readily available.
- There is a large demand for single-phase induction motors in sizes ranging from a *fraction of horse-power upto about 5 H.P.*

Disadvantages :

Though these machines are useful for small outputs, they are not used for large powers as they suffer from many disadvantages and are never used in cases where three-phase machines can be adopted.

The main *disadvantages* of single-phase induction motors are :

1. Their output is only 50% of the three-phase motor, for a given frame size and temperature rise.
2. They have lower power factor.
3. Lower-efficiency.
4. These motors do not have inherent starting torque.
5. More expensive than three-phase motors of the same output.

4.3.2. Construction and working

Construction :

- A single phase induction motor is similar to a 3-Φ squirrel-cage induction motor in physical appearance. Its rotor is essentially the same as that used in 3-Φ induction motors. Except for shaded pole motors, the stator is also very similar. There is a uniform air-gap between the stator and rotor but no electrical connection between them. It can be wound for any even number of poles, two, four and six being most common. Adjacent poles have opposite magnetic property and synchronous speed equation, $N_s = \frac{120f}{p}$ also applies.
- The stator windings differ in the following two aspects :
 - **Firstly** single phase motors are usually provided with concentric coils.
 - **Secondly**, these motors normally have two stator windings. In motors that operate with both windings energised, the winding with the **heaviest wire** is known as the **main winding** and the other is called the **auxiliary winding**. If the motor runs with auxiliary winding open, these windings are usually referred as *running* and *starting*.

- In most of motors the main winding is placed at the bottom of the slots and the starting winding on top but shifted 90° from the running winding.

Working :

When the stator winding of a single phase induction motor is connected to single phase A.C. supply, a magnetic field is developed, whose axis is always along the axis of stator coils. The magnetic field produced by the stator coils is pulsating, varying sinusoidally with time. Currents are induced in the rotor conductors by transformer action, these currents being in such a direction as to oppose the stator m.m.f. Then the axis of the rotor m.m.f. wave coincides with that of the stator field, the torque angle is, therefore, zero and no torque is developed on starting. However, if the rotor is given a push by hand or by other means in either direction, it will pick-up the speed and continue to rotate in the same direction developing operating torque. Thus a single phase induction motor is not inherently self starting and requires some special means for starting.

The above mentioned behaviour of this type of motor can be explained by any one of the following theories :

1. Double revolving field theory

2. Cross-field theory.

The results given by both the theories are approximately same.

Double revolving field theory is described below :

The magnetic field produced by the stator coils is pulsating, varying sinusoidally with time. Ferrari pointed out that such a field can be resolved into two equal fields but rotating in opposite directions with equal angular velocities. The maximum value of each component is equal to half the maximum of the pulsating field.

If the initial time is such that the rotating vectors of the two component fields are along the Y-axis in the positive direction, the two component waves ϕ_1 and ϕ_2 coincide. The resultant of these two is Φ_{\max} . After a short interval of time the two vectors rotate, through an angle θ in their respective directions and the waves are shown to occupy the positions in Fig. 96. These waves intersect at A on the Y-axis and as the waves travel A moves along the Y-axis. Hence the resultant of these two component waves at any instant is equal to $2OA$.

$$\phi_1 = OA = \phi_{1(\max)} \cos (\omega t - \theta) \quad \dots(i)$$

$$\phi_2 = OA = \phi_{2(\max)} \cos (\omega t + \theta) \quad \dots(ii)$$

and

$$\phi_{1(\max)} = \phi_{2(\max)}$$

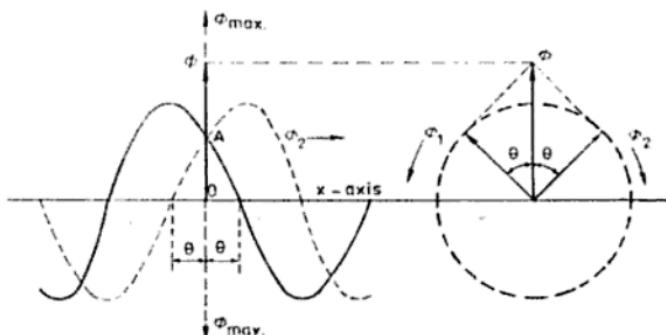



Fig. 96

synchronous speed. This does not seriously affect the operation, because the running (or main) winding alone usually develops approximately 200 per cent of full-load torque at this speed.


- The starting winding is not designed for continuous operation, and care should be exercised that it does not remain connected to the supply after it should have been disconnected by the switch. This series switch is usually centrifugally operated, and is rather inexpensive. In case of a hermetically sealed motor, the switch is magnetically operated, and is opened in the de-energized condition.
- Split-phase induction motors may be reversed by reversing the line connections of either the main or the auxiliary winding. If however, reversal is attempted under normal running condition, nothing will happen.

If it is necessary to reverse the motor while it is rotating, then some means must be incorporated to slow the motor down to the speed where the starting-switch contacts close, placing the starting winding across the supply lines. This may be done by incorporating a timing device which first disconnects the motor entirely from the line and then reverses one field at the proper time. A mechanical braking device which can be electrically operated may also be used.

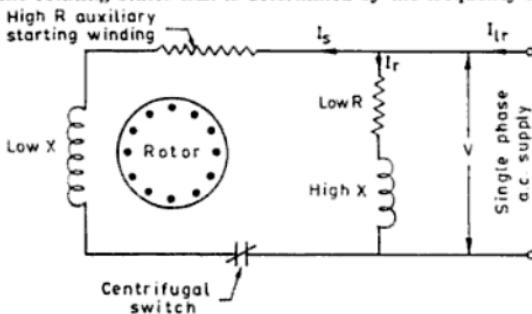- Speed control of split-phase windings is a relatively difficult matter since the synchronous speed of the rotating stator flux is determined by the frequency and number of poles




(a) Connection diagram.

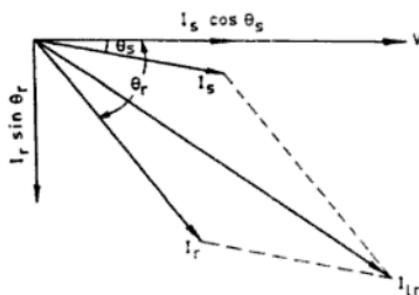

(b) Phase relations.

Fig. 98. Split phase resistance-start induction motor.

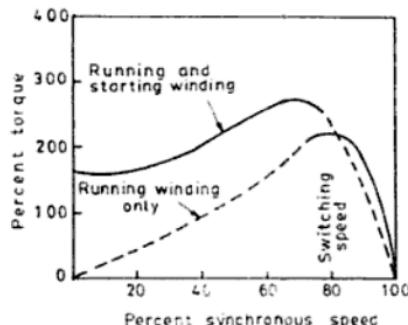

(c) Typical torque speed characteristic.

developed in the running stator winding $\left(N_s = \frac{120f}{p} \right)$. By adding stator windings to change the number of poles, speed variation may be obtained. This, however, is a stepped speed change, as in polyphase induction motor, rather than a continuous variation. It must be pointed out, however, that *all speed changes must be accomplished in a range above that at which the centrifugal switch operates*.

Fig. 98 (c) shows the typical torque speed characteristics :

- The starting torque is 1.5 times to twice the full-load starting torque and starting current is 6 to 8 times full-load current.
- The speed regulation is very good.
- The percent slip is about 4-6 percent.
- Such a motor may operate with a power factor of 0.55—0.65 and efficiency of 60—65 percent.
- These motors are made in fractional kW $\left(\frac{1}{20} \text{ to } \frac{1}{4} \text{ kW} \right)$ ratings with speed ranging from 2875 to 700 r.p.m.

Shortcomings and uses. The major objections to the motor are (1) its *low starting torque*; and (2) that, when heavily loaded, the slip exceeds 5 percent, reducing the e.m.f. and producing an elliptical or *pulsating torque* which makes the motor somewhat annoyingly noisy. For this reason, the split-phase motor is used in appliances to drive loads which are themselves noisy : *oil burners, machine tools, grinders, dish washers, washing machines, air blowers and air compressors*.

- *Because of low starting torque these motors are seldom employed in sizes larger than $\frac{1}{4}$ kW.*

4.4.2. Split-phase capacitor—start induction motor

Another method of splitting the single-phase supply into two phases to be applied to the stator windings is *placing a capacitor in series with the starting auxiliary winding*. In this manner, the current in the starting winding may be made to lead the line voltage. Since the running winding current lags the line voltage, the phase displacement between the two currents be made to approximately 90° on starting. The circuit of capacitor-start motor is shown in Fig. 99 (a), while the vector diagram of the currents and voltage is shown in Fig. 99 (b). The values of the angles shown are fairly representative, and are rounded off for convenience. *One of the factors upon which the starting torque depends is the sine of the angle between the currents in the two windings.* The value of series capacitor may therefore be reduced, while maintaining a phase-shift angle of about 90° .



- The increase in phase angle between starting and running winding currents is not the only difference between the split-phase and capacitor-start motors. *The split phase motor must keep the number of starting-winding turns low, so that the current may be nearly in phase with the line voltage.* This, however, is unnecessary in a capacitor-start motor, since the capacitor can overcome the inductance of the winding while still providing the proper phase shift. There are thus more auxiliary starting turns in the capacitor-start motor than in the comparable split-phase motor. This provides a greater number of ampere-turns, hence a *larger rotating flux*, and therefore a *further increase in the starting torque*.

Also it is seen that for the same magnitudes of field currents, the current I_r is less in capacitor-start motor, because of the greater angle between the two field currents. In addition, the starting power factor is also better. For a given line current, the starting torque is thus much higher for a capacitor-start motor than for a split-phase induction motor. *The starting torque of capacitor-start motor is from 3 to 4.5 times the full-load torque, while that of split-phase resistance-start induction motor rarely exceeds twice the full-load torque.*

- These motors are manufactured in ratings ranging from $\frac{1}{10}$ kW to $\frac{3}{4}$ kW, but larger sizes are also available.

Fig. 100 shows the connection diagram and phase relations of a permanent split-phase motor.

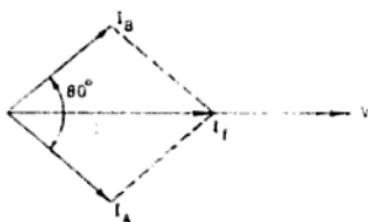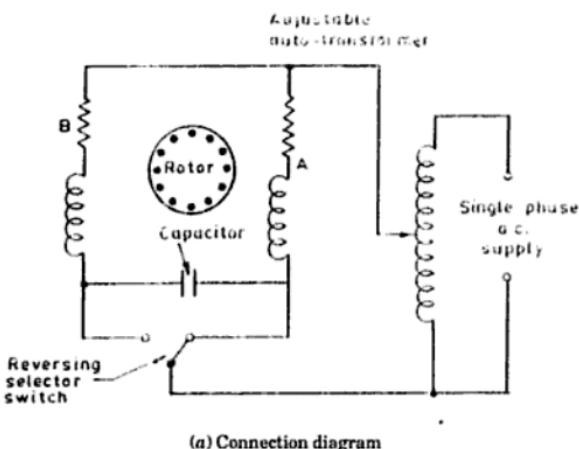- Because of the fairly uniform rotating magnetic field created by equal windings whose currents are displaced by almost 90° , the torque is fairly uniform and the motor *does not exhibit the characteristic pulsating hum* developed by most single-phase motors when loaded.



(b) Vector diagram or phase relations

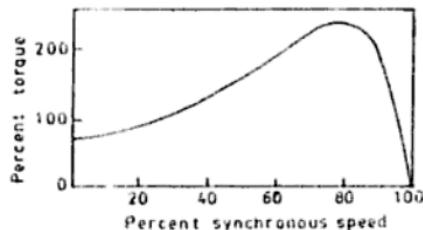


Fig. 100. Permanent split-phase motor.

(c) Typical torque-speed characteristic

This motor possesses the following *merits* :

- Higher power factor at full-load
- Lower full-load line current
- Higher full-load efficiency
- Increased pull-out torque.

- The permanent-split capacitor motor is *more expensive* than the equivalent split-phase or capacitor-start induction motor. This is primarily due to the fact that the auxiliary (or starting) winding is now also a running winding. It must therefore have a continuous duty rating and as such is heavier than if it were short-time-rated.

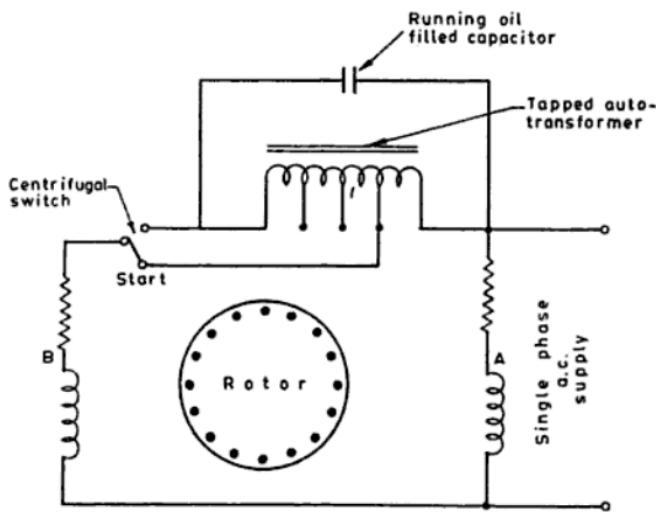


Fig. 102. Two-value capacitor motor with auto-transformer.

the line leads of one winding are reversed, it is reversed in the usual manner. When the speed drops below 25% slip during reversing, the centrifugal switch closes its starting contact, providing the maximum torque as the motor slows down and reverses. The contacts open again when the motor is up to 75% synchronous speed in the reverse direction. Frequent reversals, therefore will reduce the life of the centrifugal switch. For this reason, where frequent reversals are accomplished, permanent-split, single-value capacitor, using no centrifugal switch whatever, is preferable.

Uses. This two-value capacitor motor finds use in *smaller home air-conditioning units* which use this motor in its *compressor* and operates on a 15 amp. branch circuit. The lower starting current and lower running current (7.5 amp. maximum) at an improved power factor over the capacitor-start motor, are obtained through the *precise selection of starting and running capacitors* for the fixed compressor load.

4.4.5. Shaded-pole induction motor

A shaded-pole motor is one of the *simpler* and *cheapest* of manufactured motors. It is essentially an induction machine, since its squirrel-cage rotor receives power in much the same way as does the rotor of the polyphase induction motor. There is however, one extremely important difference between the two. Whereas the poly-phase induction motor creates a true revolving field, in the sense that it is constant in magnitude and rotates at synchronous speed *completely round the entire core*, the field of the shaded-pole motor is not constant in magnitude but *merely shifts from one side of the pole to the other*. Because the shaded-pole motor does not create a true revolving field, the torque is not uniform but varies from instant to instant.

Fig. 103 shows the general construction and principle of shaded pole motor.

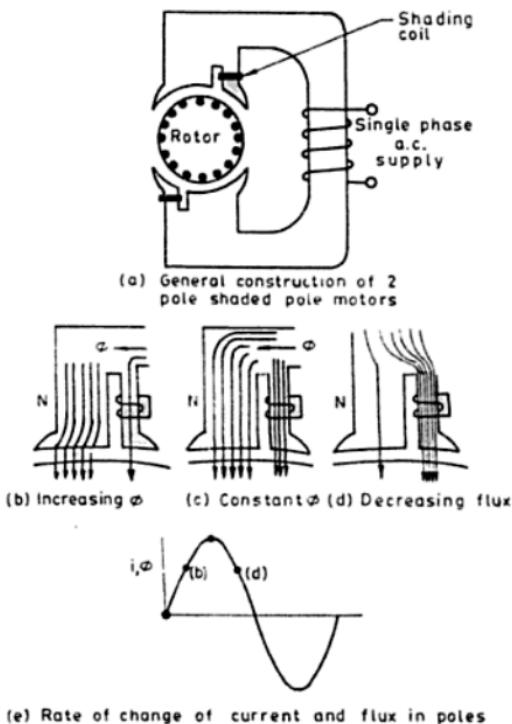


Fig. 103. General construction and principle of shaded pole motor.

Construction. Each of the laminated poles of the stator has a slot cut across the laminations about one-third the distance from one edge. Around the smaller of the two areas formed by this slot is placed a heavy copper short-circuited coil, called a *shading coil*; the iron around which the shading coil is placed is called the *shaded* part of the pole, while the free portion of the pole is the *unshaded* part. The exciting coil surrounds the entire coil.

Principle of operation. When the exciting winding is connected to an A.C. source of supply, the magnetic axis will shift from the unshaded part of the pole to the shaded part of the pole. This shift in the magnetic axis is, in effect equivalent to an actual physical motion of the pole; the result is that the squirrel-cage rotor will rotate in a direction from the unshaded part to the shaded part. The shifting of flux is explained below.

- Refer Fig. 103 (b). When the flux in the field poles tend to increase, a short-circuit current is induced in the shading coil, which by Lenz's law opposes the force and the flux producing it. Thus, as the flux increases in each field pole, there is a concentration of flux in the main segment of each pole, while the shaded segment opposes the main field flux.

circuited by the reversing switch. Coils 2 and 4 remain in series with each other, but are on open circuit and so are inactive. The main-field flux is shown increasing vertically downward, and the arrows on the shading coils show the current in them. It is then seen that the shading coil must be connected in such a manner as not to have their induced voltages in opposition, or there may not be any current in them, and hence no flux lag.

4.4.6. Reluctance-start induction motor

A reluctance-start induction motor is shown in Fig. 106. Its characteristics are similar to that of shaded pole motor. In this motor too the magnetic field shifts across the pole, but the effect is obtained by the non-uniform air gap of salient poles. Where there is a greater air gap, the flux in that portion is more nearly in phase with the current. There is a greater lag between flux and current where there is a lower reluctance or where the air gap is smaller. Since both fluxes are produced by the same current, the flux across the larger air gap leads the flux across the smaller one. The two fluxes are obviously displaced in time, and so the magnetic field shifts across the poles from larger air gap to the shorter gap. Thus the direction of rotation is firmly fixed by the construction, and the motor cannot be reversed at all.

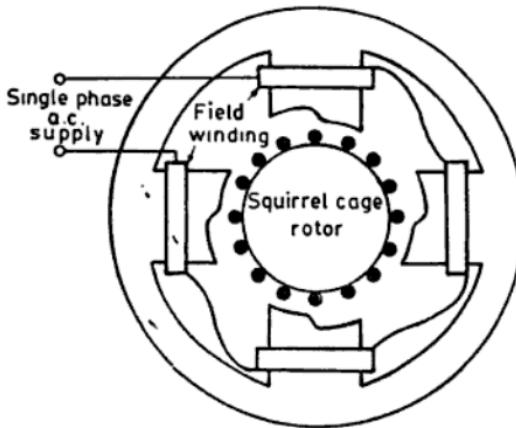


Fig. 106. Reluctance start motor.

Uses. For most small power applications, the shaded-pole motor is preferred, and the reluctance-start motor has limited use, usually only where starting torque requirements are low.

Note. This motor is an induction motor and should not be confused with *reluctance motor* which is actually a non-excited synchronous motor.

4.5. Single-Phase Commutator Motors

The commutator motors are so called because the wound rotor of this kind of motor is equipped with a *commutator and brushes*. This group consists of the following two classes :

1. Those operating on '*repulsion principle*' (repulsion motors) in which energy is inductively transferred from the single-phase stator field winding to the rotor.
2. Those operating on the *principle of the series motor* in which the energy is conductively carried both to the rotor armature and its series-connected single-phase stator field.

Atkinson repulsion motor. A modification of the simple repulsion motor is the Atkinson repulsion motor, in which the stator winding comprises two windings at right-angles to each other and connected in series, as shown in Fig. 108. One advantage obtained by this method is that the direction of rotation can be reversed by reversing the connections to one of the stator windings. Instead of moving the brush rocker, it is necessary only to throw the reversing switch, shown in Fig. 108.

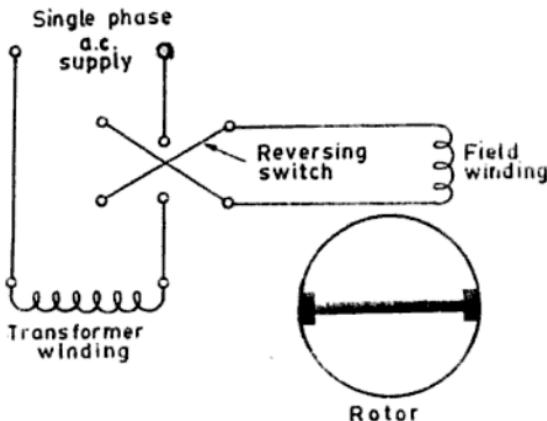


Fig. 108. Atkinson repulsion motor with reversing switch.

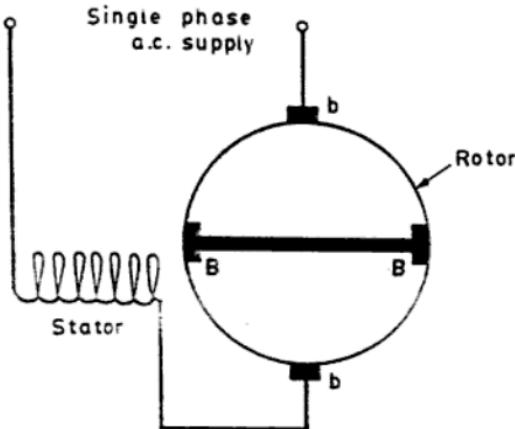


Fig. 109. Compensated repulsion motor.

It will be observed that, as the rotor is electrically connected to the stator, the compensated repulsion motor is not able to operate directly from a high-voltage supply, as was the case with the simple repulsion motor.

Fig. 110 shows the typical speed-torque characteristics of single-phase repulsion motor.

4.5.5. Universal motor

- Fractional-horsepower series motors that are adapted for use on either D.C. or A.C. circuits of a given voltage are called *universal motors*.
- The universal motor is designed for commercial frequencies from 60 cycles down to D.C. (zero frequency), and for voltage from 250 V to 1.5 V. A commercial universal motor may have a somewhat weaker series field and more armature conductors than a D.C. series motor of equivalent horsepower. *It is manufactured in ratings up to 3/4 H.P., particularly for vacuum cleaners and industrial sewing machines.* In smaller sizes of $\frac{1}{4}$ H.P. or less, it is used in *electric hand drills*.

Like all series motors, the *no-load speed of the universal motor is universally high*. Quite frequently, *gears trains* are built into the motor housing of some universal motors to provide exceedingly high torque at low speeds.

When these motors are used in commercial appliances such as *electric shavers, sewing machines, office machines, and small hand hair dryers or vacuum cleaners*, they are always *directly loaded* with little danger of motor runaway.

Advantages of a universal motor :

- High speed from above 3600 r.p.m. to around 25000 r.p.m.
- High power output in small physical sizes for use in portable tools.
- High torque at low and intermediate speeds to carry a particularly severe load.
- Variable speed by adjustable governor, by line voltage or especially by modern pulse techniques.

Disadvantages :

- Increased service requirement due to use of brushes and commutators. The life of these parts is limited in severe service.
- Relatively high noise level at high speeds.
- Moderate to severe radio and television interference due to brush sparking.
- Requirement for careful balancing to avoid vibration.
- Requirement for reduction gearing in most portable tools.

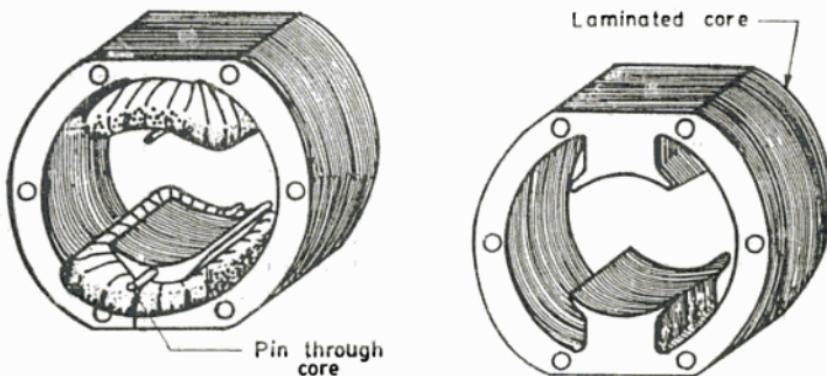


Fig. 116. Field core of a two pole universal motor.

tends to align the specimen of material in such a way that the reluctance of the magnetic path that passes through the material will be minimum.

When supply is given to the stator winding, the revolving magnetic field will exert reluctance torque on the unsymmetrical rotor tending to align the salient pole axis of the rotor with the axis of the revolving magnetic field (because in this position, the reluctance of the magnetic path would be minimum). If the reluctance torque is sufficient to start the motor and its load, the rotor will pull into step with the revolving field and continue to run at the speed of the revolving field. (Actually the motor starts as an induction motor and after it has reached its maximum speed as an induction motor, the reluctance torque pulls its rotor into step with the revolving field so that the motor now runs as synchronous motor by virtue of its saliency).

Reluctance motors have approximately one-third the horsepower rating they would have as induction motors with cylindrical rotors, although the ratio may be increased to one-half by proper design of the field windings. Power factor and efficiency are poorer than for the equivalent induction motor. Reluctance motors are subject to 'cogging', since, the locked-rotor torque varies with the rotor position, but the effect may be minimized by skewing the rotor bars and by not having the number of rotor slots exactly equal to an exact multiple of the number of poles.

Uses. Despite its short-comings, the reluctance motor is widely used for many constant speed applications such as recording instruments, time devices, control apparatus, regulators, and phonograph turntables.

- Reversing is obtained as in any single-phase induction motor.

Speed-torque characteristics. Fig. 120 shows speed-torque characteristics of a typical single-phase reluctance motor.

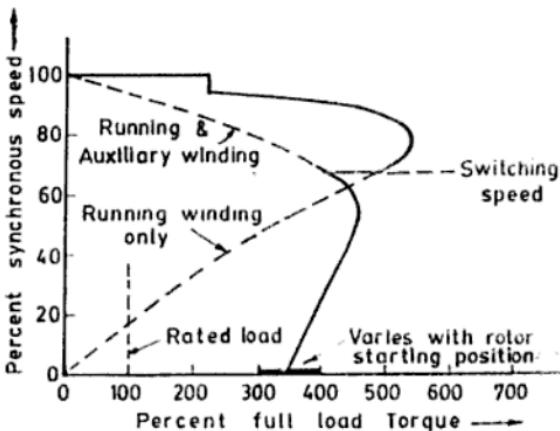


Fig. 120. Speed-torque characteristics of a single-phase reluctance motor.

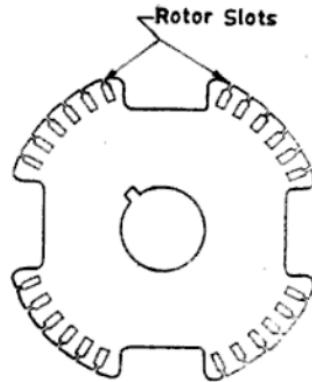


Fig. 119. Reluctance-motor lamination.

- The motor starts at anywhere from 300 to 400 per cent of its full-load torque (depending on the rotor position of the unsymmetrical rotor with respect to the field windings) as a two-phase motor as a result of the magnetic rotating field created by a starting and running winding (displaced) 90° in both space and time.
- At about 3/4th of the synchronous speed, a centrifugal switch opens the starting winding, and the motor continues to develop a single-phase torque produced by its running winding only.

As it approaches synchronous speed, the reluctance torque (developed as a synchronous motor) is sufficient to pull the rotor into synchronism with the pulsating single-phase field.

- The motor operates at a constant speed up to a little over 200% of its full-load torque.* If it is loaded beyond the value of pull-out torque, it will continue to operate as a single-phase induction motor up to 500% of its rated output.

4.6.2. Hysteresis motor. Single-phase cylindrical (non-salient-pole) synchronous-induction or shaded-pole motors are classed as *hysteresis motors*. A hysteresis motor has neither a salient-pole rotor nor direct excitation, but nevertheless it rotates at synchronous speed. This type of motor *runs into synchronism and runs on hysteresis torque*.

Hysteresis-type lamination, shown in Fig. 121, are usually made of *hardened, high retentivity steel* rather than commercial, low retentivity dynamo steel.

Working. As a result of a rotating magnetic field produced by phase splitting or a shaded-pole stator, *eddy currents are induced in the steel of the rotor which travel across the two bar paths of the rotor* as shown in Fig. 121. A high-retentivity steel produces a high hysteresis loss, and an appreciable amount of energy is consumed from the rotating field in reversing the current direction of the rotor. At the same time the *rotor magnetic field set up by the eddy currents causes the rotor to rotate*. A high starting torque is produced as a result of the high resistance (proportional to hysteresis). As the rotor approaches synchronous speed, the frequency of current reversal in the cross-bars decreases, and the rotor becomes *permanently magnetized* in one direction as a result of the high retentivity of the steel rotor. Consequently the motor continues to rotate at synchronous speed.

- An extremely important use of this type of motor is for the rotation of *gyroscope rotors* in inertial navigation and control systems. Here the requirement is for as near absolute accuracy as can be achieved. One major component of the instrument accuracy that contains the gyroscope is that the gyroscopic moment be *absolutely constant*. This constancy requires a synchronous motor that is driven by a regulated constant-frequency source.

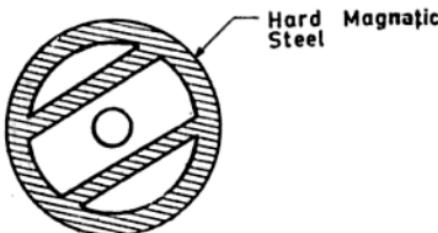


Fig. 121. Hysteresis rotor.

4.6.3. Sub-synchronous motor. When the motor has a rotor that has an overall cylindrical outline and yet is toothed as a many-pole salient-pole rotor, it is a **sub-synchronous motor**. A typical rotor may have 16 teeth or poles, and in conjunction with a 16-pole stator will normally rotate at

synchronous 450 r.p.m. when operated on 60 Hz. If this motor were temporarily overloaded, it would drop out of synchronism. Then the speed drops down toward the maximum torque point, and the motor will again lock into synchronism at a sub-multiple speed of 225 r.p.m. Hence the name of sub-synchronous motor.

This type of motor starts and accelerates with hysteresis torque just as the hysteresis synchronous motor does. There is no equivalent of induction-motor torque as in the reluctance motors.

This type of motor in any given size will develop a higher starting torque but a lesser synchronous speed torque than a reluctance motor.

Fig. 122 shows a sub-synchronous rotor.

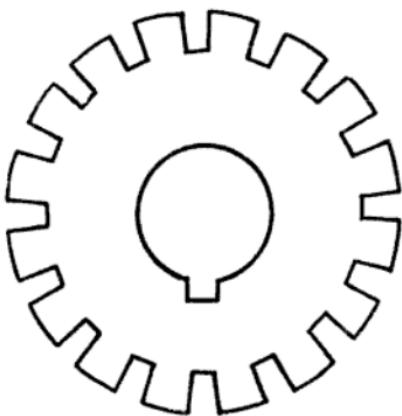


Fig. 122. Sub-synchronous rotor.

5. INSULATING MATERIALS

Electrical insulating materials are defined as material which after a very large resistance to flow of current and for that reason they are used to keep the current in its proper path along the conduction.

Characteristics of a good insulating material

A good insulating material should possess the following characteristics.

1. Large insulation resistance.
2. High dielectric strength.
3. Uniform viscosity—it gives uniform electrical and thermal properties.
4. Should be uniform throughout—it keeps the electric losses as low as possible and electric stresses uniform under high voltage differences.
5. Least thermal expansion.
6. When exposed to arcing should be non-ignitable.
7. Should be resistant to oils or liquids, gas fumes acids and alkalies.
8. Should have no deteriorating effect on the material, in contact with it.
9. *Low dissipation factor (loss tangent)*
10. High mechanical strength.
11. High thermal conductivity.
12. Low permittivity.
13. High thermal strength.
14. Free from gaseous insulation to avoid discharges (for solids and gases)
15. Should be *homogeneous* to avoid local stress concentration.
16. Should be resistant to thermal and chemical deterioration.

Classification of insulating materials

The insulating materials can be classified in the following two ways :

1. *Classification according to substances and materials.*
2. *Classification according to temperature.*

1. Classification according to substances and materials :

(i) **Solids** (Inorganic and organic)

Mica, wood, slate, glass, porcelain, rubber, cotton, silk, rayon, terylene, paper and cellulose materials etc.

(ii) **Liquids** (Oils and Varnishes)

Linseed oil, refined hydrocarbon mineral oils, spirit and synthetic varnishes etc.

(iii) **Gases**

Dry air, carbon dioxide, argon, nitrogen etc.

2. Classification according to temperature :

Class	Insulating materials included	Assigned limiting insulating temperature
Y (Formerly O)	Cotton, silk, paper, cellulose, wood, etc., neither impregnated nor immersed in oil. Materials of Y class are <i>unsuitable for electrical machines and apparatus as they deteriorate rapidly and are extremely hygroscopic</i> .	90°C
A	Materials of class Y impregnated with natural resins, cellulose esters, insulating oils etc. Also included in this list are laminated wool, varnished paper.	105°C
E	Synthetic resin enamels, cotton and paper laminates with formaldehyde bonding etc.	120°C
B	Mica, glass fibres, asbestos with suitable bonding substances, built up mica, glass fibre, and asbestos laminates.	130°C
F	Materials of class B with bonding materials of higher thermal stability.	155°C
H	Glass fibre and asbestos materials, and built up mica, with silicon resins.	180°C
C	Mica, ceramics, glass, quartz without binders or with silicon resins of higher thermal stability.	above 180°C

Insulating Materials

I. For transformers :

	Parts to be insulated	Insulating materials
1.	Air cooled and oil cooled transformers.	Fibrous (class A) materials.
2.	For taping the coils of air-cooled transformers.	Cotton or oiled cambric.
3.	Insulation between core and coils and also between primary and secondary windings.	Synthetic resin-bonded paper, treated press board or similar materials.
4.	For insulating the conductors of oil cooled transformers.	High grade manilla paper tape.
	External tapping of coils and bindings.	Cotton tape.
5.	As spaces, packing between coils, barriers between coils and tank etc.	Press board or press paper.

High-quality synthetic resin bonded paper or alternatively a high grade press paper, in the form of cylinders and flages, is employed for the insulation between core and coils, and also between the primary and secondary windings.

II. For machines :

	<i>Parts to be insulated</i>	<i>Insulating materials</i>
1.	D.C. and A.C. motors and generators for industrial installations.	Class A materials.
2.	Turbo alternators, traction motors and aircraft machines.	Class B materials.
3.	Rectangular (bar) conductors such as used in large D.C. machines.	Cotton and oiled cambric tapes, tough fibrous materials, Nylon.
4.	Inter-turn insulation of bare edge wise-strip windings, such as are employed on some salient-pole alternators and the commutating poles of large D.C. machines.	Asbestos tapes.
5.	Insulation of commutators.	Mica (built up sheets, rings and cones).
6.	Taping armature and field coils of traction motors, stator coils of high-voltage alternators.	Mica tape.
7.	For moisture-proofing and increasing the dielectric strength of fibrous insulating materials.	Varnishes and impregnating compounds.
8.	Terminal board of D.C. and low-voltage A.C. machines and other parts requiring a rigid insulation with a flat surface.	Laminates of paper, cotton cloth, asbestos etc.
9.	For insulating terminals of high-voltage machines.	Porcelain.

6. RATING AND HEATING OF D.C. MACHINES

6.1. Rating

- The '*rating*' of a machine is somewhat arbitrarily specified safe operating limit for the machine, determined in accordance with certain accepted rules and standards applying to it. It is intended to represent the operating limit which the machine cannot ordinarily exceed for a considerable length of time without in some way damaging it, or at least causing in it an accelerated rate of wear or depreciation in one or more of its parts.
- Any motor or generator is rated by its *output power* capacity. For years has been listed by horsepower in motors and kilowatts in generators. With the advent of S.I. measurements, both are measured in kilowatts (KW).
- Generators and motors, unless otherwise stated, are assumed to be rated for continuous service ; that is, their specified load may be carried for an *unlimited period of time without exceeding the limits set by the rules*.
- Machines that operate on intermittent, varying, or periodic duty are given a *short-time rating* of 5, 10, 30, 60 or 120 minutes. A machine with such a rating is guaranteed to carry its rated load continuously for the specified time without exceeding the usual limits.

- The ratings of motors and generators are affected by the following principal factors :
 - (i) Heating
 - (ii) Communication.

There is no definite maximum load that a machine can carry. A machine may exceed its rated load by 25 or 50 per cent, but if, excess load is carried for a considerable length of time, the temperature may rise to a value that causes permanent injury to the insulation. Furthermore, the commutator may spark excessively, and if permitted to continue for long, the burning of commutator and brushes may damage them and shorten their lives as well as increase the cost of their maintenance.

Other factors which may influence rating are :

Speed regulation—in case of a motor.

Voltage regulation—in case of a generator.

The full-load and no-load voltages of generators are usually specified. In case of motors the specifications of full-load and no-load speeds may also be required.

6.2. Heating

It is known that I^2R losses are liberated in each of the electric circuits, that is, in the several field windings, in the armature windings, and in the commutators and brushes. In addition, the commutator and brushes, and to a lesser extent the bearings and the armature as a whole, develop friction losses, while the armature core and the pole faces liberate the energy developed by hysteresis and eddy currents. All these energy losses are converted into heat and must be radiated or be carried away by currents of air. In moderate and large-size machines these losses, in the aggregate, are quite considerable.

In a heated part the heat energy can flow from it only by reason of a difference in temperature between it and the surrounding medium. Accordingly, the *temperature of a part whose losses are liberated must rise until the rate of heat generation in it is equal to the rate at which it loses heat*. In order that the maximum output may be secured without overheating, it is therefore necessary first, that the *losses be kept to a minimum* and, second, that *good facilities be provided for conducting the heat away*. The armature and often the field coils are provided with air ducts through which cooling air is circulated by the fanning action of the armature. Large A.C. machines are sometimes enclosed and provided with a forced ventilation system.

Normally the machines are not enclosed but have free access to the air for cooling. Dirt and dust accumulating in the air ducts impair ventilation and may cause a machine to overheat, even although the rated load is not exceeded.

Another factor which affects the heating of a machine is *altitude*. The density of air decreases with increase of altitude. For this reason air at sea level is a better cooling medium than air at 1000 m, and a machine that ordinarily carries its rated load without overheating may overheat at high altitude. Standard rating apply to altitudes under 1000 m.

Insulation. The insulating properties of materials (used to insulate the windings and commutator of electric machines) are *impaired and finally destroyed by excessive temperatures*. The '*limiting temperature*' of an insulating material is the highest temperature at which an insulating material may be continuously operated without impairing or disqualifying it for continuous service.

The temperature measured on the surface of the armature or on the surface of a field spool is somewhat lower than that actually experienced by the embedded conductors. To correct this difference a 'conventional allowance' of 15°C is made. An indication of the temperature of a machine may be obtained with the use of *thermocouples* or *resistances*. Large modern machines have thermocouples (or resistances) permanently built into their windings at various places where a knowledge of the temperature is desired. When thermocouples are used, their terminals are connected through a suitable switching device to the terminals of a milivoltmeter mounted on the

4. Guarded enclosure. This enclosure is so arranged that no accidental or intentional object can penetrate. Specially, a 1.2. cm diameter rod must not be able to penetrate screens or guards.

5. Weather proof enclosure. A variation of drip-proof and splash-proof design that prevents blowing rain, snow, or dust from contracting electrical parts.

6. Totally enclosed enclosure. Closed and/or covered but not necessarily air-tight enclosure.

7. Water-proof enclosure. Designed so that its total enclosure may be sprayed by the stream from a hose without detrimental effect. Shaft leakage is allowed if it is drained away in specified fashion. This enclosure is used in dairy and other food-processing machinery where daily cleaning and even sterilization takes place.

8. Explosion-proof enclosure. Designed to contain an inside explosion and/or to prevent ignition of specified gases, or vapours surrounding the motor. This may be accomplished by specified screens/and of flame traps, as in marine gasoline engine carburettor air opening. It does not specifically mean total enclosure, although it may be so.

9. Dust-ignition-proof enclosure. Totally enclosed and constructed to exclude entrance of ignitable dusts or dusts that would build up and affect performance.

7. RATING SPECIFICATIONS OF A.C. MACHINES

I. Transformer Specifications

The transformer specifications give the rating and performance expectations of the transformer. These are broadly as mentioned below :

1. kVA rating ;
2. Rated voltage ;
3. Number of phases (1-phase or 3-phase) ;
4. Rated frequency ;
5. Connections (Δ or Y for 3-phase transformer) ;
6. Tappings if any ;
7. Type of core (core or shell) ;
8. Type (power or distribution) ;
9. Ambient temperature (generally average 40°C) ;
10. Type of cooling.

(i) Cooling medium—air, oil or water
 (ii) Circulation type—natural or forced
 (iii) Simple or mixed cooling.

11. Temperature rise above ambient in $^{\circ}\text{C}$ depending upon the class of winding insulation.

12. Voltage regulation

- (i) Percent or per unit at full-load at 75°C unity p.f. or 0.8 p.f. lag
 - (ii) Impedance percent or per unit
 - (iii) Reactance—percent or per unit.

13. No-load current in amperes or percent of rated current at rated voltage and rated frequency.

14. Efficiency in percent or per unit at full load, $\frac{1}{2}$ load, $\frac{3}{4}$ load at unity p.f. or 0.8 p.f.

kVA rating :

The *kVA rating* is the *kVA output which the transformer can deliver at rated voltage and frequency under usual operating conditions without exceeding the standard limits of temperature rise*.

The *kVA figures always refer to the output kVA appearing at the secondary load terminals ; the input kVA, of course, is slightly higher because of internal losses* (core and winding losses).

Rated secondary voltage is the voltage that appears across the secondary terminals when rated current flows.

The *rated primary voltage* is equal to the rated secondary voltage multiplied by the turn-ratio between primary and secondary i.e. $V_1 \text{ (rated)} = V_2 \text{ (rated)} \times \frac{N_1}{N_2}$.

IS Specifications :

1. Outdoor type distribution transformers (IS : 1180-1964) :

- *Standard ratings* : 16, 25, 40, 50, 63, 80 and 100 kVA.
- *No-load voltage ratios* : 3300/433 V, 6600/433 V and 11000/433 V.
- *Tappings* : Shall be provided on h.v. side in 5 steps. The ranges shall be $\pm 2.5\%$ and $\pm 5\%$ off-load tap changers to be used.
- *Connections* : $\Delta Y(Dy 11)$ with neutral brought out to a separate insulated terminal.
- *Cooling*. By low viscosity transformer oil.
- *Conservator tank*. To be provided on transformer of rating 50 kVA or above.
- *Limits of temperature rise* :

The following temperature rises shall be permitted over the ambient temperature of 45°C :

- (i) Winding (temperature to be measured by resistance method) 55°C
- (ii) Oil (temperature rise to be measured by thermometer in the top oil) 45°C.

The above temperature rises are for On, OB, OW type cooling.

Impedance. 4.5% at 75°C, subject to the tolerance limit of $\pm 10\%$.

2. Power transformers (IS : 2026-1962) :

- *Standard ratings (for 3-phases transformers)* : 25, 40, 63, 100, 125, 160, 200, 250, 315, 400, 500, 630, 800, 1000, 1250, 1600, 2000, 2500, 3125, 4000, 6300, 8000, 10,000, 12,500, 16,000, 20,000, 25,000, 31,500, 40,000, 50,000, 63,000 and 80,000 kVA.

Standard ratings (for 1-single phase transformers) : 1, 2, 5, 10, 16 and 25 kVA.

Above 25 kVA, the standard rating for single phase transformers shall be one-third of the value given for 3-phase transformers.

- *Tappings*. The standard tapping ranges are $2 \frac{1}{2}\% \pm 5\%$. Tap changing is carried out by means of an externally operated off-circuit switch capable of being locked in positions.
- *Limits of temperature rise* :

- (i) Windings (measured by resistance) 55°C (ON, OB, OW cooling)
..... 60°C (OFN, OFB cooling)
..... 65°C (OFW cooling)

(ii) Oil (measured by thermometer in top oil) all types 45°C.

(iii) Cores core shall be designed so that the temperature rise on any part of the external surface does not exceed that of the winding.

- *Impedance*. 4.5% at 75°C, for transformers of rating upto and including 100 kVA, 11 kV and 4.75% for transformers of rating above 100 kVA including 1000 kVA, 11 kV.

II. 3-Phase Induction Motors

- Three-phase induction motors are rated in terms of the following :

- | | |
|--------------------------|------------------|
| (i) Power output in kW ; | (ii) Speed ; |
| (iii) Voltage ; | (iv) Frequency ; |

- (v) Phase (single or three) ;
- (vi) Line current ;
- (vii) Temperature rise in specified time.
- If a motor is designed to be operated on more than one voltage or at more than one speed by reconnecting the winding, a connection diagram is also given on the name plate.
- Class of motors A, B, C, D, E, or F is also to be mentioned on the name plate.
- *Standard types of squirrel cage motors are :*
 - Class A motors—Low-impedance squirrel cage rotor motors.
 - Class B motors—High-reactance squirrel cage rotor motors.
 - Class C motors—High starting torque, low starting current-double squirrel cage motors.
 - Class D motors—High resistance squirrel cage rotor motors.
 - Class E motors.
 - Class F motors.

III. Synchronous Machines

- The rating of a *synchronous generator* (alternator) is its operating voltage, frequency, speed and kVA/MVA output at a specified power factor.
 - In case of motors the output rating is given in kW (older practice was to specify the rated output in horse-power (1 H.P. = 746 W)
 - The frequency specification of A.C machines is normally the standard supply frequency i.e. 50 Hz (it is 60 Hz on the American continent).
 - The rated voltage is specified as standard value, size 230 V/400V/3.3 kV/6.6 kV/11 kV.
- Most manufacturers build small and medium sized motors in standard kW sizes.*

8. DUTY CYCLES

For rotating electrical machines following are the duty cycles :

1. **Continuous duty cycle.** In this type of duty cycle the load duration is for a sufficiently long time such that thermal equilibrium is attained by all the parts of the machine.
2. **Continuous duty with intermittent periodic loading.** This type of duty cycle comprises a sequence of identical duty cycles which consist of the following :
 - (i) Period of operation at constant load ;
 - (ii) Period of operation at no-load.
3. **Continuous duty with starting and braking.** This duty cycle comprises a sequence of identical duty cycles having the following :
 - (i) A period of starting ;
 - (ii) A period of operation at constant load ;
 - (iii) A period of electric braking.
4. **Intermittent periodic duty cycle**
 - This type of duty cycle has a period of constant load and rest with machine de-energised.
 - This cycle is encountered in *cranes, lifts and certain metal cutting machine tool drives*.
5. **Intermittent periodic duty with starting and braking.** This type of cycle comprises a sequence of identical duty cycles each consisting of the following :
 - (i) A period of starting ;
 - (ii) A period of operation at constant load ;
 - (iii) A period of braking ;
 - (iv) A rest period.

6. Short time duty cycle. This type of duty cycle may be defined as its output at which it may be operated for a certain specified time without exceeding the maximum permissible value of temperature rise.

9. COOLING OF ELECTRICAL MACHINES

In order to prolong insulation life-time to an acceptable value, the heat generated due to loss in an electrical machine *must be dissipated fast enough so that the temperature rise does not exceed the allowable limit for a specified ambient temperature*. In fact it is the improvement in heat transfer technology that has helped in a major reduction in machine sizes for given ratings, in particular for large-size machines.

Combined conduction and forced convective cooling are the practical means of removing heat losses from all electrical machines. Because limited allowable temperature rise, radiation does not make any significant.

Classification of cooling systems contribution to loss dissipation.

The cooling systems are classified as under :

1. According to origin of cooling :

- (i) **Natural cooling.** In this type cooling, the machine is cooled by air currents set up by rating parts or due to temperature differences, without the use of a fan etc.
- (ii) **Self cooling.** Here, the cooling of machine is done by cooling air obtained from a fan mounted on the rotor or one driven by it.
- (iii) **Separate cooling.** In this method of cooling machine is cooled either by a fan not driven by its shaft or it is cooled by a cooling medium other than air put into motion by means not belonging to the machine.

2. According to the manner of cooling

- (i) **Open circuit ventilation.** In this system of cooling the heat is given up directly to the cooling air passing through the machine ; the air is replaced continuously.
- (ii) **Surface ventilation.** In this case the heat is given up by the cooling medium from the external surface of a totally enclosed electrical machine.
- (iii) **Closed circuit ventilation.** In closed circuit ventilation system of cooling the heat is transferred to the cooling medium through an intermediate cooling medium circulating in a closed circuit through the machine and a cooler.

D.C. MACHINES

HIGHLIGHTS

1. **Basic type of D.C. machine is that of commutator type.** This is actually an alternating current (A.C.) machine, but furnished with a special device, a commutator, which under certain conditions converts alternating current into direct current.
2. **An electrical generator is a machine which converts mechanical energy (or power) into electrical energy (or power).** It works on the following principle : "Whenever a conductor cuts magnetic flux, dynamically induced e.m.f. is produced in it according to Faraday's Laws of Electromagnetic induction".
3. **A D.C. machine consists of two main parts :**
 - **Stationary Part :** designed mainly for producing magnetic flux.
 - **Rotating Part :** called armature, where mechanical energy is converted into electrical (electric generator) or, conversely, electrical energy into mechanical (electric motor).

- 16.** Speed regulation of a motor is given by

$$\text{Percentage speed regulation} = \frac{\text{no-load speed} - \text{full-load speed}}{\text{full-load speed}}$$

17. In a D.C. motor reversal is accomplished by changing the polarity of either the armature or the field, but not by changing both.

OBJECTIVE TYPE QUESTIONS

D.C. GENERATOR

Choose the Correct Answer :

- Laminations of core are generally made of
 - cast iron
 - silicon steel
 - carbon
 - stainless steel.
 - Which of the following could be approximately the thickness of laminations of a D.C. machine ?
 - 0.005 mm
 - 0.05 mm
 - 5 mm.
 - The armature of D.C. generator is laminated to
 - reduce the bulk
 - provide passage for cooling air
 - insulate the core
 - reduce eddy current loss.
 - The resistance of armature winding depends on
 - length of conductor
 - cross-sectional area of the conductor
 - number of conductors
 - all of the above.
 - The field coils of D.C. generator are usually made of
 - mica
 - copper
 - cast iron
 - carbon.
 - The commutator segments are connected to the armature conductors by means of
 - copper lugs
 - resistance wires
 - insulation pads
 - brazing.
 - In a commutator
 - copper is harder than mica
 - mica and copper are equally hard
 - mica is harder than copper
 - none of the above.
 - In D.C. generators the pole shoes are fastened to the pole core by
 - rivets
 - counter sunk screws
 - brazing
 - welding.
 - According to Fleming's right-hand rule for finding the direction of induced e.m.f., when middle finger points in the direction of induced e.m.f., forefinger will point in the direction of
 - motion of conductor
 - lines of force
 - either of the above
 - none of the above.
 - Fleming's right-hand rule regarding direction of induced e.m.f., correlates
 - magnetic flux, direction of current flow and resultant force
 - magnetic flux, direction of motion and the direction of e.m.f. induced
 - magnetic field strength, induced voltage and current
 - magnetic flux, direction of force and direction of motion of conductor.
 - While applying Fleming's right-hand rule to find the direction of induced e.m.f., the thumb points towards
 - direction of induced e.m.f.
 - direction of flux
 - direction of motion of the conductor if forefinger points in the direction of generated e.m.f.
 - direction of motion of conductor, if forefinger points along the lines of flux.

D.C. MOTOR

14. Derive the e.m.f. equation of a D.C. generator.
15. Deduce an expression for the voltage induced in a D.C. generator.
16. Write a short note on equiliser rings.
17. How are ratings of electrical machines expressed ?
18. Draw the magnetic circuit of a 4 pole D.C. machine.
19. Explain different methods of excitation of D.C. generators with suitable diagrams.
20. How are D.C. generators classified ?
21. What is the difference between a separately excited and a self-excited generator ?
22. Sketch the following types of D.C. generators :
 - (i) Shunt
 - (ii) Series
 - (iii) Compound.
 State with reason(s) where each is used ?
23. What is the difference between the short-shunt and long shunt compound generators ?
24. With the help of a neat diagram show power division in a D.C. generator.
25. Answer the following questions briefly :
 - (i) State the principle on which generators operate.
 - (ii) Name the materials of which the following parts of a D.C. machine are made and why ?
 - (a) Frame
 - (b) Armature
 - (c) Bushes.
 - (iii) Why are field coils provided in a D.C. generator ?
 - (iv) What is the function of an armature in a D.C. generator ?
 - (v) Of what material are the laminations of an armature made up of ?
 - (vi) What is the function of a commutator ?
 - (vii) What purpose is served by brushes in a D.C. machine ?

D.C. MOTOR

26. What is the working principle of a D.C. motor ?
27. "In every D.C. generator motor action occurs and in every D.C. motor a generator action occurs". Explain.
28. What is torque ? What is the source of the torque force in a D.C. motor ?
29. What is back e.m.f. or counter voltage ?
30. What is the effective voltage across a D.C. motor armature ?
31. What is the meaning of armature power ?
32. Is electrical power related to mechanical power ?
33. Explain the function of commutator in a D.C. motor. In what respects is the commutation process in D.C. motors different from that in generators ?
34. What is meant by speed regulation ?
35. What is meant by the term 'shunt motor' ?
36. What is meant by the term 'series motor' ?
37. What is the dominant speed characteristic of a shunt motor ?
38. Explain speed-current and torque-current characteristics of a series motor ?
39. What is meant by a compound motor ?
40. What conditions require the use of a compound motor ?
41. How is D.C. motor reversed ?
42. Why is a starter necessary for a motor ? Give the diagram and explain the working of a three-point starter for a shunt motor.
43. What are the functions of 'no-volt release' and 'overload release' in a starter ? Discuss the operation of these two features in a shunt motor starter.
44. Give the reasons for the following :
 - (i) A series motor should not be connected to a load through a belt.
 - (ii) A series motor develops a high starting torque.

SYNCHRONOUS MACHINES

HIGHLIGHTS

- An alternator consists of a stator and rotor. The stator provides the armature windings whereas rotor provides the rotating magnetizing field.**
- There are two types of rotors :**
 - (i) **Salient pole type. Used for low and medium-speed (engine-driven) alternators.**
 - (ii) **Smooth cylindrical type. Used for turbo-alternators i.e. for turbine-driven alternators.**
- The frequency of the alternating current produced is, $f = \frac{N_p P}{120}$ Hz.**
- The e.m.f. induced (for sinusoidal wave) per phase will be, $E_{r.m.s.}/\text{phase} = 4.44f\psi T_{ph} k_p k_d$ volts where k_p = pitch factor, k_d = distribution or breadth factor**

$$= \frac{\sin\left(\frac{q\beta}{2}\right)}{q \sin\frac{\beta}{2}}$$

$$\text{Value of } k_d \text{ for } n\text{th harmonic is, } k_d = \frac{\sin\left(\frac{qn\beta}{2}\right)}{q \sin\left(\frac{n\beta}{2}\right)}.$$

- A synchronous motor is electrically identical with an alternator or A.C. generator.**
- Some characteristic features of a synchronous motor are :**
 - It is not inherently self-starting.
 - It runs at synchronous speed, $N_s = \frac{120f}{p}$.
 - It can be operated under a wide range of power factors both lagging and leading.
- Mechanical power developed/phase,**

$$(P_{\text{mech}})/\text{phase} = \frac{E_b V}{Z_s} \cos(\theta - \alpha) - \frac{E_b^2}{Z_s} \cos \theta$$

where α = load angle, θ = internal angle.

OBJECTIVE TYPE QUESTIONS

(A) Choose the Correct Answer :

- The speed of a 4-pole 60 Hz synchronous machine will be**
 - (a) 1800 r.p.m.
 - (b) 2400 r.p.m.
 - (c) 3000 r.p.m.
 - (d) 3600 r.p.m.
- The speed of a p -pole synchronous machine in r.p.m. is given by**
 - (a) $\frac{120f}{p}$
 - (b) $\frac{120p}{f}$
 - (c) $\sqrt{120fp}$
 - (d) $120fp$.
- What is the largest size of alternator being manufactured in India ?**
 - (a) 500 MW
 - (b) 250 MW
 - (c) 210 MW
 - (d) 110 MW.

4. Which of the following organisations is engaged in the manufacture of large size alternators for power plants in India ?

(a) Department of Science and Technology	(b) Electricity Authority of India
(c) National Thermal Power Corporation Ltd.	(d) Bharat Heavy Electricals Ltd.
5. An exciter is a nothing but a

(a) D.C. series motor	(b) D.C. shunt motor
(c) D.C. shunt generator	(d) D.C. series generator.
6. Hydrogen is used in large alternators mainly to

(a) reduce distortion of waveform	(b) cool the machine
(c) strengthen the magnetic field	(d) reduce eddy current losses.
7. An alternator coupled to which primemover will usually have the highest rotating speed ?

(a) Steam engine	(b) Reciprocating diesel engine
(c) Francis turbine	(d) Steam turbine.
8. In an alternator the voltage generated per phase is proportional to

(a) number of turns in coil	(b) flux per pole
(c) frequency of waveform	(d) all of the above.
9. Salient pole type alternators are generally used on

(a) low voltage alternators	(b) hydrogen cooled primemovers
(c) high speed primemovers	(d) low and medium speed primemovers.
10. Turbo-alternators are generally used to run at

(a) 1500 r.p.m.	(b) 3000 r.p.m.
(c) 5000 r.p.m.	(d) 15000 r.p.m.
11. The rotor preferred for alternators applied to hydraulic turbines are

(a) salient pole type	(b) cylindrical rotor type
(c) solid rotor type	(d) any of the above.
12. The frequency of voltage generated in large alternators is

(a) 50 Hz	(b) 60 Hz
(c) in kilo cycles	(d) in mega cycles.
13. Which of the following primemovers is least efficient ?

(a) Gas turbine	(b) Petrol engine
(c) Diesel engine	(d) Steam engine.
14. In which coil the harmonic component of the generated e.m.f. will be more ?

(a) Full pitch coil	(b) Short pitch coil
(c) Long pitch coil	(d) Same in all coils.
15. In case of turbo-alternators the rotor is usually made of

(a) cast iron	(b) forged steel
(c) laminated stainless steel	(d) manganese steel.
16. In case a three-phase alternator supplies resistive load

(a) the armature reaction flux will be almost zero
(b) the armature reaction flux will be along the axis of the field
(c) the armature reaction flux will be at 90° with the field axis
(d) the armature reaction flux will be at 180° with the field axis.
17. A 12-pole alternator will pass through how many electrical degrees in one complete revolution

(a) 60°	(b) 360°
(c) 1080°	(d) 2160°.
18. The number of poles in turbo-alternators is usually

(a) 2	(b) 4
(c) 12	(d) 50.

UNSOLVED EXAMPLES

- For a 3-phase winding with 4 slots/pole/phase and with the coil span of 10 slots pitch, calculate the values of the pitch factor and distribution factor. [Ans. 0.966, 0.9576]
 - A 2200 volt, 3-phase alternator is running at 300 r.p.m. and has 24 poles. Find the number of conductors in the stator winding, if the magnetic flux is 5×10^{-2} Wb/pole.
Assume distribution factor as 0.96. [Ans. 600]
 - A 4-pole alternator has an armature with 25 slots and 8 conductors/slot and rotates at 1500 r.p.m. and the flux/pole is 0.05 Wb. Calculate the e.m.f. generated, if winding factor is 0.96 and all conductors are in series. [Ans. 1065.6 V]
 - The stator of a 3-phase, 20-pole alternator has 120 slots, and there are 4 conductors per slot accommodated in two layers. If the speed of the alternator is 300 r.p.m. calculate the e.m.f. induced per phase. Resultant flux in the air-gap is 0.055 Wb/pole.
Assume the coil span as 150° electrical. [Ans. 905 V]
 - A 16-pole, 3-phase alternator has a star-connected winding with 144 slots and 10 conductors per slot. The flux per pole is 0.03 Wb distributed sinusoidally and the speed is 375 r.p.m. Find the line voltage. [Ans. 2658 V]
 - Calculate the e.m.f. of a 4-pole, 3-phase star-connected alternator running at 1500 r.p.m., from the following data :

Flux per pole	= 0.1 Wb
Number of slots	= 48
Conductors/slot (in two layers)	= 4
Coil span	= 150°.

[Ans. 1138 V]
 - A 3-phase, 16-pole, star-connected alternator has 192 stator slots with eight conductors/slot and the conductors of each phase are connected in series. The coil span is 150 electrical degrees. Determine the phase and line voltage if the machine runs at 375 r.p.m. and the flux per pole is 64 m Wb distributed sinusoidally over pole. [Ans. 3367 V, 5830 V]
 - A 3-phase, 4-pole star-connected alternator has 60 slots with 2 conductors/slot. The pitch of the coil is 3 slot less than the pole pitch. The flux/pole is 12.5×10^{-2} Wb sinusoidally distributed. Calculate the no-load terminal voltage for a frequency of 50-Hz.
 - A 3-phase, star-connected alternator on open-circuit is required to generate a line voltage of 3600 V, 50-Hz, when driven at 500 r.p.m. The stator has 3 slots per pole, and 10 conductors per slot. Calculate :
 - (i) number of poles
 - (ii) useful flux/pole.
Assume all conductors per phase to be connected in series and coils to be full pitch.

Assume all conductors per phase to be connected in series and coils to be full pitch.

[Ans. (i) 12, (ii) 0.054 Wb]

POLYPHASE INDUCTION MOTOR

HIGHLIGHTS

- An induction motor is simply an electric transformer whose magnetic circuit is separated by an air gap into two relatively movable portions, one carrying the primary and the other the secondary winding.*
 - Synchronous speed, $N_s = \frac{120f}{p}$, where f is the frequency and p the number of poles.*
 - Slip, $s = \frac{N_s - N}{N_s}$, where N is the motor speed (r.p.m).*
 - Frequency of the rotor current, $f_r = sf$, where s is the slip and f is the supply frequency.*

5. Torque,

$$T = \frac{ksR_2 E_2^2}{R_2^2 + s^2 X_2^2}$$

Starting torque,

$$T_{st} = \frac{kR_2 E_2^2}{R_2^2 + X_2^2}$$

Condition for maximum torque, $s = \frac{R_2}{X_2}$

Maximum torque,

$$T_{max} = \frac{kE_2^2}{2X_2}$$

6. Starting torque is proportional to the square of applied voltage.

- 7.

$$\frac{T_f}{T_m} = \frac{2s_f s_m T}{s_f^2 + s_m^2 T}, \text{ where } s_f = \frac{\text{rotor resistance}}{\text{rotor standstill reactance}}$$

$$\frac{T_{st}}{T_{max}} = \frac{2s_m T}{s_m^2 T + I}$$

- 8.

$$\frac{\text{Rotor copper loss}}{\text{Rotor gross output}} = \frac{s}{1-s}$$

- 9.

$$\frac{\text{Rotor output}}{\text{Rotor input}} = 1-s$$

OBJECTIVE TYPE QUESTIONS

(A) Choose the Correct Answer :

- Which of the following components is usually fabricated out of silicon steel ?
 - Bearings
 - Shaft
 - Stator core
 - None of the above.
- The frame of an induction motor is usually made of
 - silicon steel
 - cast iron
 - aluminium
 - bronze.
- The shaft of an induction motor must be
 - stiff
 - flexible
 - hollow
 - any of the above.
- The shaft of an induction motor is made of
 - high speed steel
 - stainless steel
 - carbon steel
 - cast iron.
- In an induction motor, on no-load the slip is generally
 - less than 1%
 - 1.5%
 - 2%
 - 4%.
- In medium sized induction motors, the slip is generally around
 - 0.04%
 - 0.4%
 - 4%
 - 14%.
- In squirrel cage induction motors, the rotor slots are usually given slight skew in order to
 - reduce windage losses
 - reduce eddy currents
 - reduce accumulation of dirt and dust
 - reduce magnetic hum.
- In case the air gap in an induction motor is increased
 - the magnetising current of the rotor will decrease
 - the power factor will decrease
 - speed of motor will increase
 - the windage losses will increase.

9. Slip rings are usually made of

(a) copper	(b) carbon
(c) phosphor bronze	(d) aluminium.
10. A 3-phase 440 V, 50 Hz induction motor has 4% slip. The frequency of rotor e.m.f. will be

(a) 200 Hz	(b) 50 Hz
(c) 2 Hz	(d) 0.2 Hz.
11. If N_s is the synchronous speed and s the slip, then actual running speed of an induction motor will be

(a) N_s	(b) $s \cdot N_s$
(c) $(1 - s)N_s$	(d) $(N_s - 1)s$.
12. The efficiency of an induction motor can be expected to be nearly

(a) 60 to 90%	(b) 80 to 90%
(c) 95 to 98%	(d) 99%.
13. The number of slip rings on a squirrel cage induction motor is usually

(a) two	(b) three
(c) four	(d) none.
14. The starting torque of a squirrel-cage induction motor is

(a) low	(b) negligible
(c) same as full-load torque	(d) slightly more than full-load torque.
15. A double squirrel-cage induction motor has

(a) two rotors moving in opposite direction	(b) two parallel windings in stator
(c) two parallel windings in rotor	(d) two series windings in stator.
16. The ratio of starting torque to normal torque in case of a star-delta starter will be

(a) 0.35	(b) 0.67
(c) 1.07	(d) 1.35.
17. Star-delta starting of motors is not possible in case of

(a) single phase motors	(b) variable speed motors
(c) low horse power motors	(d) high speed motors.
18. The terms 'cogging' is associated with

(a) three phase transformers	(b) compound generators
(c) D.C. series motors	(d) induction motors.
19. In case of the induction motors the torque is

(a) inversely proportional to $(\sqrt{\text{slip}})$	(b) directly proportional to $(\text{slip})^2$
(c) inversely proportional to slip	(d) directly proportional to slip.
20. Stepless speed control of induction motor is possible by which of the following methods ?

(a) E.m.f. injection in rotor circuit	(b) Changing the number of poles
(c) Cascade operation	(d) None of the above.
21. Rotor rheostat control method of speed control is used for

(a) squirrel-cage induction motors only	(b) slip ring induction motors only
(c) both (a) and (b)	(d) none of the above.
22. In the circle diagram for induction motor, the diameter of the circle represents

(a) slip	(b) rotor current
(c) running torque	(d) line voltage.
23. For which motor the speed can be controlled from rotor side ?

(a) Squirrel-cage induction motor	(b) Slip-ring induction motor
(c) Both (a) and (b)	(d) None of the above.
24. If any two phases for an induction motor are interchanged

(a) the motor will run in reverse direction	(b) the motor will run at reduced speed
(c) the motor will not run	(d) the motor will burn.

- | | | | | | | |
|---------|---------|---------|----------|---------|---------|---------|
| 36. (c) | 37. (c) | 38. (b) | 39. (b) | 40. (a) | 41. (d) | 42. (a) |
| 43. (b) | 44. (c) | 45. (a) | 46. (d) | 47. (d) | 48. (d) | 49. (a) |
| 50. (b) | 51. (a) | 52. (b) | 53. (d) | 54. (b) | 55. (d) | 56. (d) |
| 57. (a) | 58. (d) | 59. (a) | 60. (b) | 61. (c) | 62. (b) | 63. (a) |
| 64. (a) | 65. (b) | 66. (d) | 67. (c) | 68. (d) | 69. (c) | 70. (d) |
| 71. (b) | 72. (c) | 73. (c) | 74. (d). | | | |

(B) Say 'Yes' or 'No' :

- Three-phase induction motor has a low efficiency.
- An induction motor is simply an electric transformer whose magnetic circuit is separated by an air gap into two relatively movable portions, one carrying the primary and the other the secondary winding.
- Frames of electrical machines house the stator core.
- The number of slots in the rotor should always be equal to the number of slots in the stator.
- For large and heavy rotors journal bearings are used.
- The slips rings are made of aluminium.
- The difference between the synchronous speed and rotor speed is known as slip.
- Starting torque, $T_{st} = \frac{kR_2 E_2^2}{R_2^2 + X_2^2}$.
- Starting torque is inversely proportional to the square of the applied voltage.
- Stator iron loss is practically constant.
- $\frac{\text{Rotor copper loss}}{\text{Rotor gross output}} = \frac{1-s}{s}$.
- Circle diagram of an induction motor can be drawn by using the data obtained from no-load test, short-circuit test and stator resistance test.
- The synchronous speed of the n th order harmonic is $\frac{1}{n}$ th of the synchronous speed of fundamental.
- 'Cogging' of squirrel-cage motors can be easily overcome by making the number of rotor slots prime to the number of stator slots.
- A double squirrel-cage motor has two independent squirrel-cage windings on the rotor, each having its own set of slots.

ANSWERS

- | | | | | | | |
|----------|--------|---------|--------|---------|---------|---------|
| 1. No | 2. Yes | 3. Yes | 4. No | 5. Yes | 6. No | 7. Yes |
| 8. Yes | 9. No | 10. Yes | 11. No | 12. Yes | 13. Yes | 14. Yes |
| 15. Yes. | | | | | | |

THEORETICAL QUESTIONS

- Explain the principle of operation of the polyphase induction motor.
- Show that a rotating magnetic field can be produced by the use of 3-phase currents of equal magnitude.
- What is meant by slip in an induction motor ? Develop an expression for the frequency of rotor currents in it.
- Derive an expression for the torque of an induction motor and obtain the condition for maximum torque.
- Show that in a 3-phase induction motor with negligible stator impedance maximum torque is developed at slip $s = \frac{R_2}{X_2}$, where R_2 and X_2 are rotor resistance and standstill reactance respectively.
- State the effects of increasing rotor resistance on starting current, starting torque, maximum torque and full-load slip of an induction motor.

7. Show that in an induction motor the rotor input : power developed : rotor copper losses :: $1 : (1 - s) : s$, where s is the fractional slip.
8. Draw equivalent circuit of a 3-phase induction motor.
9. Describe and explain how to perform a locked rotor test. What data can be obtained by the test?
10. What are no-load and blocked rotor tests? What sort of losses can be measured by these tests?
11. How would you determine circle diagram of a 3-phase induction motor experimentally?
12. Describe the constructional details of a 3-phase squirrel-cage and phase wound induction motors. Also discuss the applications of various types of starters used for starting these motors.
13. Why at all starters are necessary for starting the induction motors? What are the various types of starters used for squirrel-cage motors? Discuss them.

UNSOLVED EXAMPLES

1. A 3-phase, 4-pole, 50-Hz induction motor is running at 1455 r.p.m. Find the slip speed and slip. [Ans. 45 r.p.m., 3 per cent]
2. An induction motor having 8-poles runs at 50-Hz supply. If it operates at full-load at 720 r.p.m., calculate the slip. [Ans. 4 per cent]
3. A 6-pole alternator running at 1000 r.p.m. supplies an 8-pole induction motor. What is the actual speed of the motor if the slip is 2.5%. [Ans. 731.25 r.p.m.]
4. A slip ring motor runs at 290 r.p.m. on full-load when connected to 50-Hz supply. Calculate :

(i) Number of poles	(ii) Absolute slip
(iii) Fractional slip	(iv) Percentage slip
(v) Frequency of rotor currents.	[Ans. 20, 10 r.p.m., 0.0333, 3.33%, 1.66 Hz]
5. A 12-pole, 3-phase alternator is coupled to an engine running at 500 r.p.m. It supplies a 3-phase induction motor having a full-load speed of 1440 r.p.m. Find the percentage slip and number of poles of motor. [Ans. 4 per cent, 4 poles]
6. A 4-pole induction motor is run at 1450 r.p.m. from a 50-Hz supply. Find the percentage slip and frequency of rotor current. [Ans. 3.33%, 1.67 Hz]
7. If the e.m.f. in the stator of an 8-pole induction motor has a frequency of 50-Hz and that in the rotor 1.5 Hz, at what speed is the motor running and what is the slip? [Ans. 727.5 r.p.m., 3 per cent]
8. A three-phase slip ring induction motor gives a reading of 55 V across slip rings on open circuit when at rest with normal stator voltage applied. The rotor is star-connected and has impedance $(0.7 + j5) \Omega$ per phase. Find the rotor current when the machine is

(i) at standstill with the slip rings joined to a star-connected starter with a phase impedance of $(4 + j3) \Omega$; and
(ii) running normally with a 5 per cent slip.

[Ans. (i) 3.425 A at 0.506 p.f. (lag); (ii) 2.14 A at 0.942 p.f. (lag)]
9. A 3-phase, 400 V, star-connected induction motor has a star-connected rotor with a stator to rotor turn ratio of 6.5. The rotor resistance and stand-still reactance per phase are 0.05 and 0.25 Ω respectively. What should be the value of external resistance per phase to be inserted in the rotor circuit to obtain maximum torque at starting and what will be the rotor starting current with this resistance? [Ans. 0.2Ω , 100 A (app.)]
10. If the motor has a rotor resistance of 0.02Ω and a standstill reactance of 0.1Ω what must be the value of the total resistance of a starter for the rotor circuit for maximum torque to be exerted at starting? [Ans. 0.08 Ω]
11. The rotor of a 3-phase 440 V, 50 Hz, 4-pole induction motor has a resistance of 0.3Ω per phase and an inductance of 0.008 H per phase. The ratio of stator to rotor turns is $2 : 1$. The stator is delta connected and rotor is star-connected. Determine the voltage between slip rings when the motor is at standstill. Calculate the standstill rotor current and rotor current when the motor is operating with 3 per cent slip. [Ans. 381 V, 87 A, 22 A]

12. A 3300 V, 24-phase, 50-Hz, 3-phase star-connected induction motor has a slip-ring rotor resistance of 0.016Ω and standstill reactance of 0.265Ω per phase. Calculate :
 (i) The speed at maximum torque.
 (ii) Ratio of full-load torque to maximum torque if full-load torque is obtained at 247 r.p.m.
 [Ans. 235 r.p.m., 0.382]
13. A 6-pole, 3-phase, 50 Hz induction motor runs on full-load with a slip of 4%. If the rotor standstill impedance per phase is $(0.01 + j0.05) \Omega$, calculate the available maximum torque in terms of full-load torque. Also determine the speed at which the maximum torque occurs. $\left[\text{Ans. } \frac{T_m}{T_f} = 2.6, 800 \text{ r.p.m.} \right]$
14. A 6-pole, 3-phase, 50 Hz induction motor develops maximum torque of 200 Nm at a speed of 960 r.p.m. Determine the torque exerted by the motor at 5 per cent slip. The rotor resistance per phase is 0.5Ω .
 [Ans. 195 Nm]
15. The rotor resistance and standstill reactance per phase of a 3-phase slip ring induction motor are 0.02Ω and 0.1Ω respectively. What should be the value of the external resistance per phase to be inserted in the rotor circuit to give maximum torque at starting ?
 [Ans. 0.08Ω]
16. The star-connected rotor of an induction motor has a standstill impedance of $(0.4 + j4) \Omega$ per phase, and the rheostat impedance per phase is $(6 + j2) \Omega$. The motor has an induced e.m.f. of 80 V between slip rings at standstill when connected to its normal supply voltage. Find :
 (i) The rotor current at standstill with the rheostat in the circuit.
 (ii) When running short-circuited with slip of 0.03.
 [Ans. 5.27 A, 3.3 A]
17. A 4-pole, 50 Hz, 3-phase, induction motor develops a maximum torque of 115 N-m at 1365 r.p.m. The resistance of the star-connected rotor is $0.2 \Omega/\text{phase}$. Calculate the value of resistance that must be inserted in series with each rotor phase to produce a starting torque equal to half the maximum torque.
 [Ans. 0.4Ω or 8.1Ω]
18. A 4-pole, 50-Hz, 3-phase induction motor has rotor resistance and reactance of 0.03Ω and 0.12Ω per phase respectively. Determine :
 (i) The value of speed at which maximum torque occurs.
 (ii) The value of external rotor resistance per phase to be inserted to obtain 80% of maximum torque at starting.
 [Ans. 1125 r.p.m., 0.02418Ω]
19. The resistance and standstill reactance of each phase of a 3-phase induction motor with star-connected rotor are 0.06Ω and 0.4Ω respectively. The full-load slip is 4%. Calculate the resistance per phase of a star-connected rheostat, which when connected to the rotor, will give a pull out torque at one half of the full-load speed. What is then the power factor ?
 [Ans. 0.148Ω , 0.707 (lag)]
20. The rotor resistance and standstill reactance of a 3-phase induction motor are respectively 0.015Ω and 0.09Ω per phase. At normal voltage, the full-load slip is 3 per cent. Estimate the percentage reduction in stator voltage to develop full-load torque at half full-load speed. Also calculate the power factor.
 [Ans. 22.9%, 0.31 (app.)]

Rotor Output Losses, Efficiency

21. The power input to a 3-phase induction motor is 60 kW. The stator-losses total 1.5 kW. Find the total mechanical power developed if the motor is running with a slip of 4 per cent.
 [Ans. 56.16 kW]
22. The rotor e.m.f. of a 3-phase, 6-pole, 400 V, 50-Hz induction motor alternates at 3-Hz. Compute the speed and percentage slip of the motor. Find the rotor copper loss per phase if the full input to the rotor is 111.9 kW.
 [Ans. 940 r.p.m., 6%, 2.238 kW]
23. A 3-phase, 50-Hz, induction motor draws 50 kW from the mains. If the stator losses are 2 kW and the rotor e.m.f. is observed to make 100 complete oscillations/alterations per minute, determine :
 (i) Rotor copper loss.
 (ii) Gross mechanical output. [Ans. 1.6 kW, 46.4 kW]
24. The power input to the rotor of a 3-phase, 50-Hz, 6-pole, slip ring induction motor is 40 kW and the motor runs at 960 r.p.m. The rotor resistance per phase is 0.25Ω . Determine the value of the rotor current per phase.
 [Ans. 46.2 A]

25. The power input to the rotor of a 440 V, 60-Hz, 3-phase, 6-pole induction motor is 60 kW. It is observed that the rotor e.m.f. makes 90 complete cycles per minute. Calculate :
- (i) Slip,
 - (ii) Rotor speed,
 - (iii) Rotor copper loss per phase,
 - (iv) Mechanical power developed, and
 - (v) Rotor resistance/phase if the rotor current is 60 A.

[Ans. 0.03, 970 r.p.m., 600 W, 58.2 kW, 0.167 Ω]

Equivalent Circuit of an Induction Motor

26. The maximum torque of a 3-phase induction motor occurs at a slip of 12 per cent. The motor has an equivalent secondary resistance of $0.08 \Omega/\text{phase}$. Calculate the equivalent load resistance R_L , the equivalent load voltage V_L and the current at this slip if the gross power output is 9 kW. [Ans. $0.587 \Omega/\text{phase}$, 42 V, 71.6 A]
27. The stator impedance and equivalent rotor resistance of a 400 V, 3-phase star-connected induction motor are $(0.06 + j0.2) \Omega$ and equivalent rotor impedance of $(0.06 + j0.22) \Omega$. Neglecting exciting current, find the maximum gross power and the slip at which it occurs. [Ans. 12%, 142.9 kW]
28. Estimate the stator current, equivalent rotor current, efficiency, output, and its power factor at a slip of 5% for a motor having the following data :
 Stator impedance = $1.0 + j3.0 \Omega$, rotor standstill impedance = $1.0 + j2.0 \Omega$, no-load shunt impedance = $10 + j50 \Omega$, volts/phase = 250 volts. [Ans. 14.34 A, 11.6 A, 83.6%, 7,670 W, 0.853]

Starting of Induction Motor

29. A small 3-phase induction motor has a short-circuit current equal to 4 times the full-load current. Determine the starting torque as a percentage of full-load torque if full-load slip is 2.5 per cent. [Ans. 40% of full-load torque]
30. A 3-phase, squirrel-cage induction motor has a short-circuit current equal to 5 times the full-load current. Find the starting torque as a percentage of full-load torque if the motor is started by
- (i) direct switching to the supply ;
 - (ii) a star-delta starter ;
 - (iii) an auto-transformer ; and
 - (iv) a resistance in the stator circuit.
- The starting current in (iii) and (iv) is limited to 2.5 times the full-load current and the full-load slip is 4 per cent. [Ans. T_p 33.3% T_f , 50% T_f , 25% T_f]
31. Determine a suitable auto-transformer ratio for starting an induction motor with a supply current not exceeding twice full-load current. Use the following data :
 Short-circuit current = 5 times the full-load current, full-load slip = 3%. Estimate the torque in terms of full-load torque. Ignore magnetising current. [Ans. 30%]
32. Find the percentage tapping required on an auto-transformer required for a cage motor to start the motor against $\frac{1}{4}$ of full-load torque. The short-circuit current at normal voltage is 4 times the full-load current and the full-load slip is 3 per cent. [Ans. $K = 72.2\%$]
33. A squirrel-cage type induction motor when started by means of a star-delta starter takes 20 per cent of full-load line current and develops 40 per cent of full-load torque at starting. Calculate the starting torque and current in terms of full-load values, if an auto-transformer with 75 per cent tapping were employed. [Ans. $3.375 I_f$, 67% full-load torque]
34. A 10 kW, 200 V, 3-phase induction motor has at full-load an efficiency of 87% and power factor of 0.85. At standstill the motor draws 5 times the full-load current and develops 1.5 times full-load torque. An auto-transformer is installed to reduce the starting current to give full-load torque at starting. Neglecting magnetising current, determine :
- (i) The voltage to be applied at starting.
 - (ii) The full-load line current.
 - (iii) The current drawn by the motor at start.
 - (iv) The current supplied to the primary of the autotransformer. [Ans. 163.3 V, 39 A, 159.2 A, 130 A]

35. A 3-phase squirrel-cage induction motor has a ratio of maximum torque to full-load torque as $2.5 : 1$. Determine the ratio of actual starting torque to full-load torque for :
- direct starting ;
 - star-delta starting ;
 - auto-transformer starting with tapping of 60%.
- The rotor resistance and standstill reactance per phase are 0.4Ω and 4Ω respectively.

[Ans. 0.495, 0.165, 0.179]

SINGLE PHASE MOTORS

HIGHLIGHTS

- There are two basic types of single-phase induction motors which start on the split-phase principle, namely resistance-start induction-run motor and the capacitor-start induction-run motor.*
- The resistance-start induction-run motor has a relatively poor starting torque because the phase angle between the running winding current and the starting winding current is only from 30 to 50 electrical degrees.*
- The capacitor-start induction-run motor has a relatively good starting torque because the phase angle between the running winding current and the starting current is practically 90 electrical degrees.*
- The capacitor-start, capacitor-run induction motor has relatively good starting torque and operates at a comparatively high power factor. The main winding and auxiliary windings are both energized at all times the motor is in operation.*
- A resistance-start induction-run motor or a capacitor-start induction-run motor may be reversed by interchanging the leads of the starting winding circuit. The direction of rotation of either type of motor can also be reversed by interchanging the leads of the running winding circuit. However, never attempt to change the rotation of either type of motor by reversing the line wires.*
- The repulsion motor operates on the repulsion principles at all times. It has excellent starting torque and a relatively wide range of speeds.*
- The repulsion-start induction-run motor starts as a repulsion motor and after it reaches 75 per cent of rated speed, operates as an induction motor. It has excellent starting torque and very good speed regulation.*
- There are two types of brush mechanism used with repulsion-start induction-run motors : The brush-lifting type and brush-riding type.*
- To change the direction of rotation of either a repulsion motor or a repulsion-start induction-run motor, move the brushes to the other side of stator field poles so that there is an angle of 15 electrical degrees in the new position between the brushes and the stator field pole centres.*
- The A.C. series motor has excellent starting torque and can be used in those applications requiring different speeds. It has characteristics comparable to those of the D.C. series motor.*
- The direction of rotation of an A.C. series motor can be reversed by interchanging the connections to the armature.*
- The shaded-pole induction motor is usually made in fractional horsepower sizes in excess of 1/10 horsepower. This type of motor has no centrifugal starting device or mechanism which requires maintenance. However, the starting torque for this type of motor is small.*
- A stepper motor is an incremental motion machine. It does not rotate continuously as a conventional motor does.*
- The stepper motor is used in digitally controlled position control system in open loop mode.*
- Various types of stepper motors are :*
 - Permanent-magnet stepper motor ;
 - Variable-reluctance stepper motor ;
 - Hybrid stepper motor.

16. D.C. servo-motors are preferred for very high power systems.
17. A.C. servo-motors are best suited for low power applications.

OBJECTIVE TYPE QUESTIONS

(A) Choose the Correct Answer :

1. In a split-phase motor, the running winding should have
 (a) high resistance and low inductance (b) low resistance and high inductance
 (c) high resistance as well as high inductance (d) low resistance as well as low inductance.
2. If the capacitor of a single-phase motor is short-circuited
 (a) the motor will not start (b) the motor will burn
 (c) the motor will run in reverse direction (d) the motor will run in the same direction at reduced r.p.m.
3. In capacitor-start single-phase motors
 (a) current in the starting winding leads the voltage
 (b) current in the starting winding lags the voltage
 (c) current in the starting winding is in phase with voltage in running winding.
 (d) none of the above.
4. In a capacitor-start and run motors the function of the running capacitor in series with the auxiliary winding is to
 (a) improve power factor (b) increase overload capacity
 (c) reduce fluctuations in torque (d) to improve torque.
5. In a capacitor-start motor, the phase displacement between starting and running winding can be nearly
 (a) 10° (b) 30°
 (c) 60° (d) 90° .
6. In a split-phase motor
 (a) the starting winding is connected through a centrifugal switch
 (b) the running winding is connected through a centrifugal switch
 (c) both starting and running windings are connected through a centrifugal switch
 (d) centrifugal switch is used to control supply voltage.
7. The torque developed by a single-phase motor at starting is
 (a) more than the rated torque (b) rated torque
 (c) less than the rated torque (d) zero.
8. Which of the following motors will give relatively high starting torque ?
 (a) Capacitor-start motor (b) Capacitor run motor
 (c) Split-phase motor (d) Shaded-pole motor.
9. Which type of capacitor is preferred for capacitor-start and run motor ?
 (a) Electrolyte capacitor (b) Paper capacitor (oil filled)
 (c) Ceramic capacitor (d) Air capacitor.
10. Which of the following motors will have relatively higher power factor ?
 (a) Capacitor-run motor (b) Shaded-pole motor
 (c) Capacitor-start motor (d) Split-phase motor.
11. In a shaded-pole motor, the shading coil usually consists of
 (a) a single turn of heavy wire which is in parallel with running winding
 (b) a single turn of heavy copper wire which is short-circuited and carries only induced current
 (c) a multilayer fine gauge copper wire in parallel with running winding
 (d) none of the above.

7. A hysteresis motor works on the principle of eddy current loss.
8. Capacitor-start split-phase motor is reversible.
9. A reluctance motor is preferred for signalling and timing devices.
10. The wattage rating for a ceiling fan motor varies from 50 to 150 W.
11. A motor is an incremental motion machine.
12. A stepper motor rotates continuously.
13. The stepper motor is used in digitally controlled position control system in open loop mode.
14. In stepper motors no sensors are needed for position and speed sensing.
15. A stepper motor cannot be readily interfaced with microprocessor.
16. In stepper motor the rotor is made of ferrite or rare earth material which is permanently magnetised.
17. In a stepped motor the stator has only one set of winding-excited poles which interact with the two rotor stacks.
18. servo-motors are preferred for very high power systems.
19. A.C. servo-motors are best suited for low power applications.
20. construction is used for very low inertia applications.

ANSWERS

- | | | | | | | |
|--------|----------------------|---------|-------------|----------|---------|---------------|
| 1. Yes | 2. Yes | 3. No | 4. Yes | 5. No | 6. Yes | 7. No |
| 8. Yes | 9. Yes | 10. Yes | 11. stepper | 12. No | 13. Yes | 14. Yes |
| 15. No | 16. Permanent-magnet | | 17. hybrid | 18. D.C. | 19. Yes | 20. Drag-cup. |

THEORETICAL QUESTIONS

1. Explain what is meant by the split-phase method of motor starting.
2. Explain why the starting torque of a capacitor-start induction run motor is better than that of a resistance-start induction-run motor.
3. How is the direction of rotation reversed for each of the following ?
 - (i) Resistance-start induction-run motor, and
 - (ii) Capacitor-start induction-run motor.
4. (a) Compare operating characteristics of a resistance-start induction-run motor with those of a capacitor-start induction-run motor.
 (b) List three applications for :
 - (i) A resistance-start induction-run motor
 - (ii) A capacitor-start induction-run motor.
5. Explain how a repulsion motor operates.
6. Explain how a repulsion-start induction-run motor operates.
7. How is the direction of rotation of each of the following motors reversed ?
 - (i) The repulsion motor, and
 - (ii) The repulsion-start induction-run motor.
8. What is the difference between A.C. and D.C. series motor ?
9. Why are small fractional horsepower A.C. series motors called universal motors ?
10. What is the difference between a conductively compensated series motor and an inductively compensated series motor ?
11. Describe the construction and operation of a shaded-pole motor.
12. Write a short note on a sub-synchronous motor and a hysteresis motor.
13. What is a stepper motor ? Enumerate its advantages and applications.
14. Explain briefly permanent-magnet stepper motor briefly. How does it differ from variable reluctance motor ?
15. What is a stepper motor ?
16. States the advantages of stepper motors.

Measuring Instruments

1. Introduction and classification.
 2. Electrical principles of operation.
 3. Electrical indicating instruments—Essential features—Deflecting device—Controlling devices—Damping devices.
 4. Moving iron instruments : Attraction type—Repulsion type—Advantages and disadvantages of moving-iron instruments—Sources of errors.
 5. Moving coil instruments—Permanent magnet moving-coil type instruments—Electrodynamic or Dynamometer instruments.
 6. Rectifier instruments.
 7. Wattmeters : Dynamometer wattmeter—Induction wattmeters.
 8. Integrating meters : Essential characteristics of energy meters—Types of energy meters—Motor meters—Motor-driven meter—Watt-hour meter—Induction type watt-hour meter.
 9. Measurement of resistance : Voltmeter-ammeter method—Substitution method—Measurement of resistance by the Wheatstone bridge.
 10. The Potentiometer.
 11. Meggar.
 12. Instrument transformers—Potential transformers—Current transformers—Highlights—Theoretical Questions—Unsolved Examples.
-

1. INTRODUCTION AND CLASSIFICATION

The instruments used for all electrical measurements are called *measuring instruments*. They include *ammeters*, *voltmeters*, *wattmeters*, energy meters etc. The various electrical instruments may broadly be divided into two groups :

1. Absolute instruments. Absolute instruments are those instruments which indicate the quantity to be measured in terms of the *constants of the instrument* (dimensions, turns etc.) and in order to find out the quantity in the practical units it is necessary to multiply such deflections with *an instrument constant*. No previous calibration or comparison is necessary in this case. The most common absolute instrument is *tangent galvanometer* which gives the measured current in terms of tangent of the deflected angle, the radius and the number of turns of the galvanometer. Such instruments are rarely used (the use being merely confined within laboratories as standardizing instruments).

2. Secondary instruments. Secondary instruments are those in which the value of electrical quantity to be measured can be determined from the deflection of instrument only when they have been *pre-calibrated* by comparison with an absolute instrument. The deflection of the instrument gives directly the quantity to be measured. These instruments are most generally used in everyday work.

Secondary instruments may also be *classified* as follows :

1. Indicating instruments. Indicating instruments are those which indicate the instantaneous value of the electrical quantity being measured at the time at which it is being measured. Their indications are given by pointers moving over calibrated chief.

Example. *Ammeters, voltmeters and wattmeters.*

2. Recording instruments. Recording instruments are those which give a *continuous record* of the variations of an electrical quantity over a selected period of time. The pointer in these types of instruments is an inked pen which leaves a trace on a paper put over a moving drum.

3. Integrating instruments. Integrating instruments are those which measure the total quantity of electricity delivered in a particular time.

Example. Ampere-hour and watt-hour meters.

Electrical measuring instruments may also be *classified* as follows :

1. According to the quantity being measured :

Ammeters for measuring the magnitude of current.

Voltmeters for measuring voltages.

Ohmmeters and resistance bridges. for measuring resistances.

Wattmeters. for power measurements.

Watt-hour meters. for energy measurements.

Frequency meters. for frequency measurements.

Power factor meters. for power-factor measurements.

2. According to the kind of current :

Instruments are classified into *D.C.*, *A.C.* and *A.C./D.C. instruments*.

3. According to accuracy limits :**4. According to the principle of operation :**

Instruments are grouped into :

- Moving coil
- Moving iron
- Electrodynamic
- Induction
- Hot-wire
- Thermo-electric
- Rectifier types.

5. According to the type of indication :

Instruments may be :

- Indicating type
- Recording type.

6. According to application :

- Switch board
- Portable.

2. ELECTRICAL PRINCIPLES OF OPERATION

All electrical measuring instruments depend for their action on any of many physical effects of electric current or potential. The following are the effects generally used in the manufacture :

(i) **Magnetic effect**. Voltmeters, ammeters, wattmeters, power factor meters etc.

(ii) **Thermal effect**. Ammeters, voltmeters, maximum demand meters etc.

(iii) **Chemical effect**. D.C. ampere hour meters (integrating meters).

(iv) **Electrostatic effect**. Voltmeters which can indirectly be used as ammeters and wattmeters.

(v) **Electro-magnetic induction effect**. Voltmeters, ammeters, wattmeters and integrating meters used in A.C. only.

3. ELECTRICAL INDICATING INSTRUMENTS

Almost invariably an indicating instrument is fitted with a pointer which indicates on a scale the value of the quantity being measured. The moving system of such an instrument is usually carried by a *spindle of hardened steel*, having its ends tapered and highly polished to form pivots which rest in hollow-ground bearings, usually of saphine, set in steel screws. In some instruments, the moving system is attached to *thin ribbons of spring material* such as beryllium-copper alloy, held taut by

tension springs mounted on the frame of movement. This arrangement *eliminates pivot friction* and the instrument is less susceptible to damage by shock or vibration.

3.1. Essential Features.

Indicating instruments possess three essential features.

1. **Deflecting device.** whereby a mechanical force is produced by the electric current, voltage or power.

2. **Controlling device.** whereby the value of deflection is dependent upon the magnitude of the quantity being measured.

3. **Damping device.** to prevent oscillation of the moving system and enable the latter to reach its final position quickly.

3.2. Deflecting Device. A deflecting device produces a deflecting torque which is caused by anyone of the previously mentioned effects (*i.e.*, thermal effect, chemical effect, electrostatic effect etc.); with the help of this deflecting torque the needle or the pointer moves from zero position to the final position. The arrangement of the deflecting device with each type of instrument will be discussed individually.

3.3. Controlling Devices

There are two types of controlling devices :

(i) Spring control

(ii) Gravity control.

(i) **Spring control.** Fig. 1 shows a commonly used spring control arrangement. It utilises two spiral hair springs, 1 and 2, the inner ends of which are attached to the spindle S. The outer end of spring 2 is fixed while that of 1 is attached to a lever, the adjustment of which gives zero

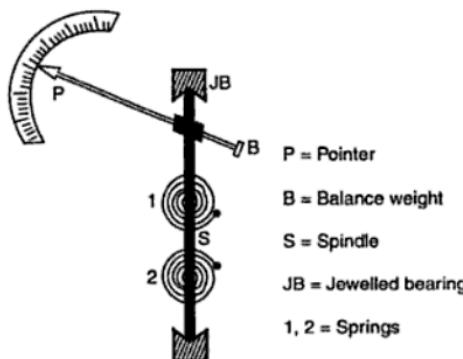


Fig. 1. Spring control.

adjustments. The two springs 1 and 2 are wound in *opposite directions* so that when the moving system is deflected, one spring winds up while the other unwinds, and the controlling torque is due to the *combined torsions* of the springs.

Since the torsional torque of a spiral spring is proportional to the angle of twist, the controlling torque (T_c) is directly proportional to the angular deflection of the pointer (θ).

i.e., $T_c \propto \theta$.

The spring material should have the following properties :

(i) It should be non-magnetic.

(ii) It must be of low temperature co-efficient.

(iii) It should have low specific resistance.

(iv) It should not be subjected to fatigue.

(ii) Gravity control. With gravity control, weights L and M are attached to the spindle S [Fig. 2 (a)], the function of L being to *balance* the weight of the pointer P . Weight M therefore provides the controlling torque. When the pointer is at zero, M hangs vertically downwards. When P is deflected through angle θ , the controlling torque is equal to (weight of M \times distance d) and is therefore proportional to the *sine* of the angular deflection [Fig. 2 (b)],

$$\text{i.e., } T_c \propto \sin \theta.$$

The degree of control is adjusted by screwing the weight up or down the carrying system.

It may be seen from Fig. 2 (b) that as θ approaches 90° , the distance 1-2 increases by a relatively small amount for a given change in the angle than when θ is just increasing from its zero value. Hence *gravity-controlled instruments have scales which are not uniform but are cramped or crowded at their lower ends*.

Advantages :

1. The gravity controlled instrument is cheaper than corresponding spring-controlled instrument.
2. It is not subjected to fatigue.
3. It is unaffected by temperature.

Disadvantages :

1. Gravity control gives a cramped scale.
2. The instrument must be levelled before use.

3.4. Damping Devices. Owing to the inertia of the moving system, when subjected to the deflecting and restoring torques, a number of vibration will be produced before coming finally to rest. To avoid this, a *damping torque* is required which opposes the motion and ceases when the pointer comes to rest. The degree of damping should be adjusted to a value which is sufficient to enable the

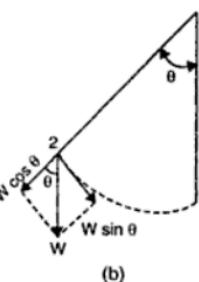
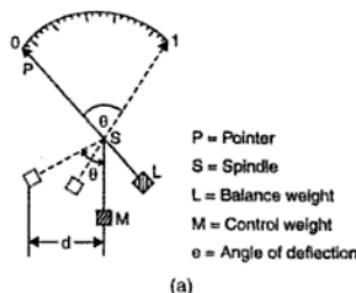


Fig. 2. Gravity control.

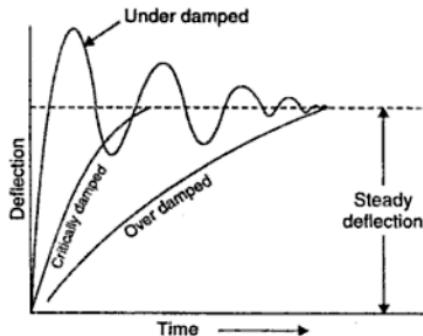


Fig. 3. Damping curves.

currents called the *eddy currents*. Due to these eddy currents a force exists between them and the field. Due to Lenz's law this force is always in opposition to the force causing rotation of the conducting material, thus, it provides the necessary damping.

- One form of eddy-current damping is shown in Fig. 5. Here a copper or aluminium disc, carried by a spindle, can move between the poles of a permanent magnet. If the disc moves clockwise, the e.m.f.'s induced in the disc circulate eddy currents as shown dotted. It follows from Lenz's law that these currents exert a force *opposing* the motion producing them, namely the clockwise movement of the disc.
- Another form of providing damping is used in the *moving coil instruments* using permanent magnet. The moving coil is mounted over a metallic former. When the coil is deflected eddy e.m.f.'s are induced in the two sides of the former, causing eddy forces as shown in Fig. 6.

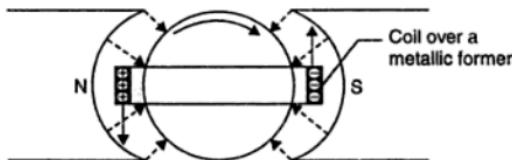


Fig. 6. Eddy current damping with permanent magnet.

3. Fluid friction damping. Fig. 7 shows the method of fluid friction damping. Here light vanes are attached to the spindle of the moving system. The vanes are dipped into a pot of damping oil and are completely submerged by the oil. The motion of the moving system is always opposed by the friction of the damping oil on the vanes. The damping force thus created always increases with the increase in velocity of vanes. There is no damping force when the vanes are stationary.

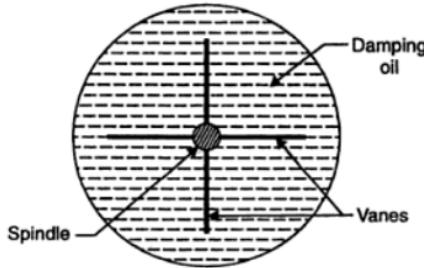


Fig. 7. Fluid friction damping.

The damping oil used must have the following properties :

- Must be a good insulator.
- Should be non-evaporating.
- Should not have corrosive action upon the metal of the vane.
- The viscosity of the oil should not change with the temperature.

Though in this method of damping, no case is required as in the air friction damping but it is not much used due to the following **disadvantages** :

- Objectionable creeping of oil.

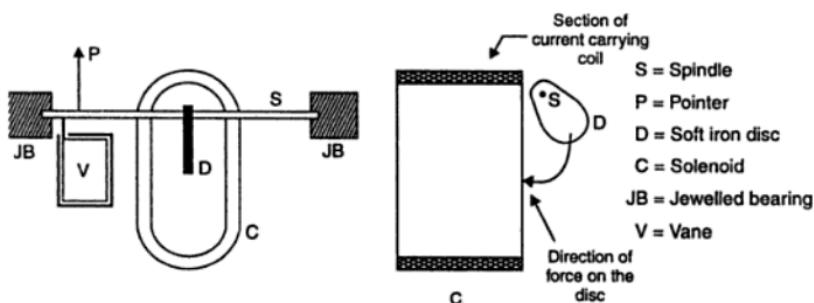


Fig. 8. Attraction-type moving-iron instrument.

solenoid/coil, causing the spindle and the pointer to rotate. Damping is provided by vane V attached to the spindle and moving in an air chamber, and control is by hair spring.

4.2. Repulsion Type. Repulsion-type moving-iron instrument is shown in Fig. 9. Here there are two irons, one fixed (A) and the other mounted on a short arm fixed (B) to the instrument spindle. The two irons lie in the magnetic field due to a solenoid/coil C. When there is no current in the coil

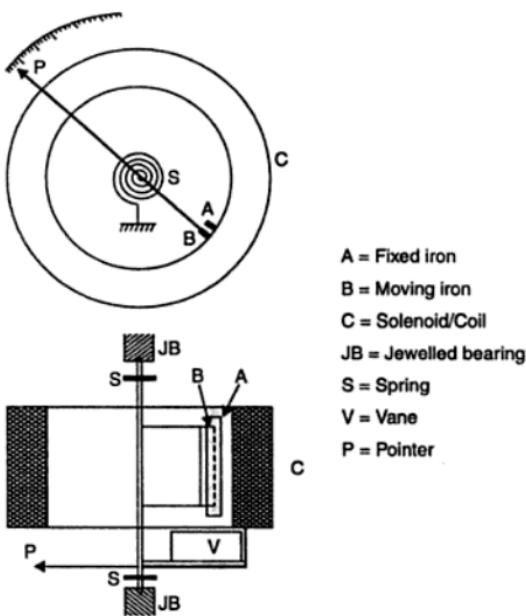


Fig. 9. Repulsion-type moving-iron instrument.

4.3. Advantages and Disadvantages of Moving-Iron Instruments

Advantages :

1. Can be used both in D.C. as well as in A.C. circuits.
2. Robust and simple in construction.
3. Possess high operating torque.
4. Can withstand overload momentarily.
5. Since the stationary parts and the moving parts of the instrument are simple so they are cheapest.
6. Suitable for low frequency and high power circuits.
7. Capable of giving an accuracy within limits of both precision and industrial grades.

Disadvantages :

1. Scales not uniform.
2. For low voltage range the power consumption is higher.
3. The errors are caused due to hysteresis in the iron of the operating system and due to stray magnetic field.
4. In case of A.C. measurements, change in frequency causes serious error.
5. With the increase in temperature the stiffness of the spring decreases.

4.4. Sources of Errors

A. Errors with both D.C. and A.C.

(i) **Errors due to hysteresis.** This source of error is due to *hysteresis* in the soft iron moving part, due to which too high values are recorded by the instrument, when the current is increasing and too low readings are liable to be indicated when the current is decreasing.

(ii) **Errors due to stray fields.** External stray magnetic fields are liable to affect adversely the accurate functioning of the instrument. Magnetic shielding of the working parts is obtained by using a covering case of cast iron.

B. Errors with A.C. only

Errors may be caused due to change in frequency because change in frequency produces (i) *change in impedance of the coil* and (ii) *change in magnitude of eddy currents*. The error due to the former is negligible in ammeters, as the coil current is determined by the external circuit and the error due to the latter can normally be made small.

5. MOVING-COIL INSTRUMENTS

The moving-coil instruments are of the following two types :

1. Permanent-magnet type.....can be used for D.C. only.
2. Dynamometer type.....can be used both for A.C. and D.C.

5.1. Permanent-magnet Moving-Coil Type (PMMC) Instruments

A permanent-magnet moving coil-type instrument works on the principle that "*when a current-carrying conductor is placed in a magnetic field, it is acted upon by a force which tends to move it to one side and out of the field*".

Construction

- The instrument consists of a permanent magnet *M* and a rectangular coil *C* which consists of insulated copper wire wound on light aluminium frame fitted with polished steel pivots resting in jewel bearings. The magnet is made of Alnico and has soft-iron pole-pieces *PP* which are bored out cylindrically.
- The rectangular coil *C* is free to move in air gaps between the soft-iron pole pieces and a soft-iron cylinder *A* (central core), supported by a brass plate (not shown).

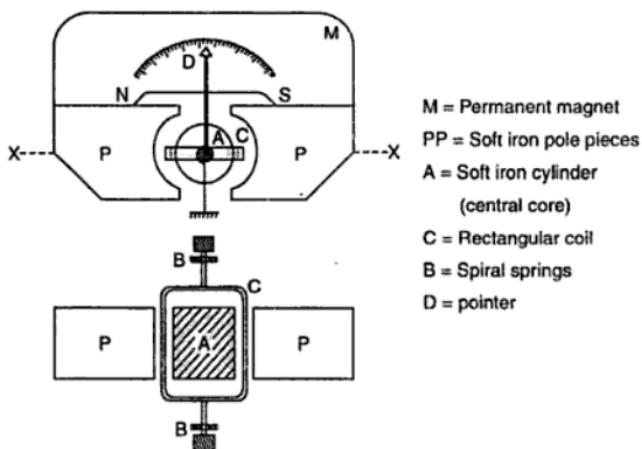


Fig. 11. Permanent-magnet moving-coil instrument.

The functions of the central core A are :

(i) To intensify the magnetic field by reducing the length of air gap across which the magnetic flux has to pass.

(ii) To give a radial magnetic flux of uniform density, thereby enabling the scale to be uniformly divided.

- The movement of the coil is controlled by two phosphor bronze hair springs BB (one above and one below), which additionally serve the purpose of leading the current in and out of the coil. The two springs are spiralled in *opposite directions* for neutralizing the effects of changes in temperature.
- The aluminium frame not only provides support for the coil but also *provides damping by eddy currents induced in it*.

Deflecting torque. Refer Fig. 12. When current is passed through the coil, forces are set up on its both sides which produce *deflection torque*. If I amperes is the current passing through the coil, the magnitude of the force (F) experienced by each of its sides is given by

$$F = BIl \text{ newton}$$

where B = flux density in WB/m^2 , and

l = length or depth of coil in metres.

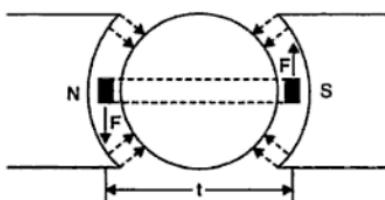


Fig. 12

For N turns, the force on each side of the coil is

$$= NBII \text{ newton}$$

\therefore Deflecting torque (T_d)

$$= \text{force} \times \text{perpendicular distance}$$

$$= NBII \times b = NBI(l \times b) = NBIA \text{ N-m}$$

where b = breadth of the coil in metres, and

A = face area of the coil.

If B is constant, then

$$T_d \propto I \quad (\text{i.e., current passing through the coil})$$

$$= kI \text{ where } k \text{ is a constant for a given instrument.}$$

Since such instruments are invariably spring controlled, the controlling torque (T_c) of the spiral springs \propto angular deflection

$$\text{i.e., } T_c \propto \theta$$

$$\text{or } T_c = c\theta$$

where c = a constant for given springs, and

θ = angular deflection.

For a steady deflection,

Controlling torque (T_c) = deflecting torque (T_d)

Hence

$$c\theta = kI$$

$$\therefore \theta = \frac{k}{c} I$$

i.e., the deflection is proportional to the current and the scale is therefore uniformly divided.

Advantages and Disadvantages. The moving-coil permanent-magnet type instruments have the following advantages and disadvantages :

Advantages :

- (i) Low power consumption.
- (ii) Their scales are uniform.
- (iii) No hysteresis loss.
- (iv) High torque/weight ratio.
- (v) They have very effective and efficient eddy-current damping.
- (vi) Range can be extended with shunts or multipliers.
- (vii) No effect of stray magnetic field as intense polarised or unidirectional field is employed.

Disadvantages :

- (i) Somewhat costlier as compared to moving-iron instruments.
- (ii) Cannot be used for A.C. measurements.
- (iii) Friction and temperature might introduce errors as in case of other instruments.
- (iv) Some errors are set in due to the ageing of control springs and the permanent magnets.

Ranges :

D.C. Ammeters

- (i) Without shunt.....0/5 micro-amperes up to 0/30 micro-amperes.
- (ii) With internal shunts.....upto 0/2000 amperes.
- (iii) With external shunts.....upto 0/5000 amperes.

D.C. Voltmeters

- (i) Without series resistance.....0/100 milli-volts.
- (ii) With series resistance.....upto 20000 or 30000 volts.

strips, the ends of which are soldered to two large copper blocks. Each copper block carries two terminals—one current terminal and other potential terminal. The strips which form the shunt are spaced from each other to promote a good circulation of air and thus efficient cooling.

Note. A 'swamping' resistor r , of material having negligible temperature co-efficient of resistance, is connected in series with the instrument (moving coil). The latter is wound with copper wire and the function of r is to reduce the error due to variation of resistance of the instrument with variation of temperature.

2. Voltmeter multipliers. The range of the instrument, when used as a voltmeter can be extended or multiplied by using a high non-inductive series resistance R connected in series with it as shown in Fig. 14.

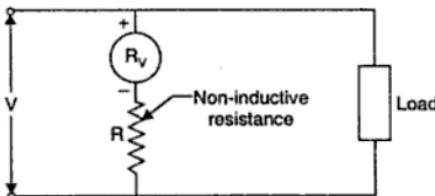


Fig. 14

Let I = full scale deflection current of voltmeter,

V = voltage of the circuit to be measured,

R_v = resistance of the voltmeter, and

R = external series resistance.

Now, voltage across supply leads

= voltage drop across the voltmeter + voltage drop across external resistance

$$\therefore V = IR_v + IR$$

$$\text{or } R = \frac{V - IR_v}{I} = \frac{V}{I} - R_v$$

The voltage multipliers to be used for D.C. measurements should satisfy the following requirements :

(i) The resistance should not change with time of usage.

(ii) The temperature co-efficient of resistance must be very low.

Note. The frequency error introduced by the inductance of the instrument coil can be compensated by shunting R by a capacitor.

Example 1. A milliammeter of 2.5 ohms resistance reads upto 100 milli amperes. What resistance is necessary to enable it to be used as :

(i) A voltmeter reading upto 10 V.

(ii) An ammeter reading upto 10 A.

Draw the connection diagram in each case.

Solution. Resistance of the milli-ammeter, $R_m = 2.5 \Omega$

Maximum current of the milli-ammeter, $I_m = 100 \text{ mA} = 0.1 \text{ A}$.

(i) Voltage to be measured, $V = 10 \text{ volts}$

Resistance to be connected in series.

$$R = \frac{V}{I_m} - R_m = \frac{10}{0.1} - 2.5 = 97.5 \Omega \quad (\text{Ans.})$$

Connection diagram is shown in Fig. 15.

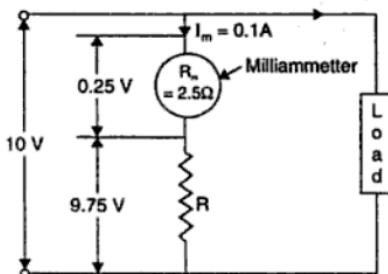


Fig. 15

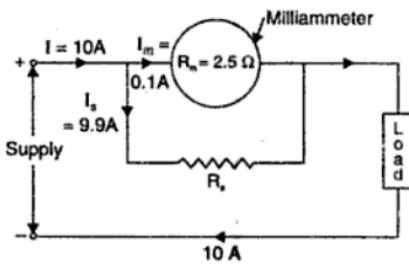


Fig. 16

(ii) Current to be measured, $I = 10 \text{ A}$

$$\text{Multiplying power of the shunt, } N = \frac{I}{I_m} = \frac{10}{0.1} = 100$$

\therefore Resistance to be connected in parallel,

$$R_s = \frac{R_m}{N - 1} = \frac{2.5}{100 - 1} = 0.02525 \Omega. \quad (\text{Ans.})$$

Connection diagram is shown in Fig. 16.

Example 2. A moving-coil milli-ammeter having a resistance of 10 ohms gives full scale deflection when a current of 5 mA is passed through it. Explain how this instrument can be used for measurement of:

(i) Current upto 1 A.

(ii) Voltage upto 5 V.

Solution. Resistance of the milli-ammeter, $R_m = 10 \Omega$

Full scale deflection current, $I_m = 5 \text{ mA} = 0.005 \text{ A}$.

(i) To measure current upto 1 A :

Resistance of the shunt, R_s : (Refer Fig. 17)

Since voltage drop across the milli-ammeter and the shunt are equal

$$\therefore I_m R_m = I_s R_s = (I - I_m) R_s$$

$$\therefore R_s = \frac{I_m R_m}{(I - I_m)} = \frac{0.005 \times 10}{(1 - 0.005)} = 0.05025 \Omega. \quad (\text{Ans.})$$

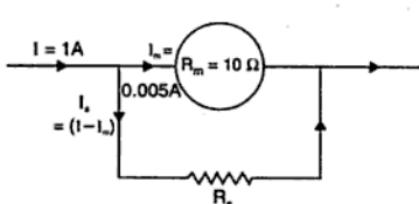


Fig. 17

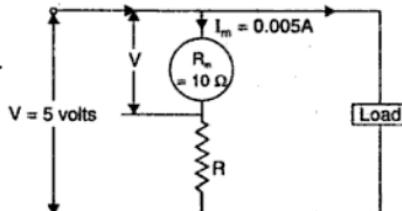


Fig. 18

(ii) To measure voltage upto 5 V :

The value of external series resistance, R : (Refer Fig. 18)

Now, voltage across supply loads

$$\begin{aligned} &= \text{voltage drop across the milli-ammeter} \\ &\quad + \text{voltage drop across external series resistance } R \end{aligned}$$

$$\therefore V = I_m R_m + I_m R$$

or

$$5 = 0.005 \times 10 + 0.005 R$$

or

$$R = \frac{5 - 0.005 \times 10}{0.005} = 990 \Omega. \text{ (Ans.)}$$

Example 3. If the moving coil of a voltmeter consists of 100 turns wound on a square former which has a length of 30 mm and the flux density in the air gap is 0.09 Wb/m², calculate the turning moment on the coil when it is carrying a current of 10 mA.

Solution. Number of turns, $N = 100$

Length of each side, $l = 30 \text{ mm} = 0.03 \text{ m}$

Flux density, $B = 0.09 \text{ Wb/m}^2$

Current through the coil, $I = 10 \text{ mA} = 0.01 \text{ A}$

We know that the force on each side of the coil,

$$F = NBIl \text{ newton}$$

\therefore Turning moment (i.e., deflecting torque),

$$\begin{aligned} T &= F \times \text{breadth} = F \times l = NBIl^2 \text{ N-m} \\ &= 100 \times 0.09 \times 0.01 \times (0.03)^2 \text{ N-m} \\ &= 8.1 \times 10^{-5} \text{ N-m. (Ans.)} \end{aligned}$$

Example 4. A moving-coil instrument has a resistance of 5 Ω between terminals and full-scale deflection is obtained with a current of 0.015 A. This instrument is to be used with a manganin shunt to measure 100 A full scale. Calculate the error caused by a 20°C rise in temperature.

(i) When the internal resistance of 5 Ω is due to copper only.

(ii) When a 4 Ω manganin swamping resistor is used in series with a copper resistor of 1 Ω.

The temperature-resistance co-efficients are :

Copper : $\alpha_c = 0.4\% \text{ per } ^\circ\text{C}$, Manganin : $\alpha_m = 0.015\% \text{ per } ^\circ\text{C}$.

Solution. Resistance of the instrument, $R_m = 5 \Omega$

Current through the instrument, $I_m = 0.015 \text{ A}$

Current to be measured, $I = 100 \text{ A}$

Current through the shunt,

$$I_s = I - I_m = 100 - 0.015 = 99.985 \text{ A}$$

Voltage across the shunt

$$I_m R_m = 5 \times 0.015 = 0.075 \text{ V}$$

$$\therefore \text{Shunt resistance, } R_s = \frac{0.075}{99.985} = 0.00075 \Omega \quad [\because I_m R_m = (I - I_m) R_s]$$

Shunt resistance after a rise of 20°C

$$= 0.00075 (1 + 20 \times 0.00015) = 0.000752 \Omega.$$

(i) The instrument resistance (which is wholly copper) after a rise of 20°C

$$= 5(1 + 20 \times 0.004) = 5.4 \Omega$$

Hence, current through the instrument corresponding to 100 A in the line

$$= \frac{0.000752}{(5.4 + 0.000752)} \times 100 = 0.01392 \text{ A}$$

Reading of the instrument = $0.01392 \times 100 / 0.015 = 92.8 \text{ A}$

\therefore Percentage error = $100 - 92.8 = 7.2. \text{ (Ans.)}$

(ii) The instrument resistance after a rise of 20°C

$$\begin{aligned} &= (1 + 20 \times 0.004) + 4(1 + 20 \times 0.00015) \\ &= 1.08 + 4.012 + 5.092 \Omega \end{aligned}$$

Instrument current with a line current of 100 A

$$= \frac{0.000752}{(5.092 + 0.000752)} \times 100 = 0.01476 \text{ A}$$

$$\therefore \text{Instrument reading} = 0.01476 \times \frac{100}{0.015} = 98.4 \text{ A}$$

Percentage error = 100 - 98.4 = 1.6. (Ans.)

Example 5. The coil of a 250 V moving iron voltmeter has a resistance of 500 Ω and inductance of 1 H. The current taken by the instrument when placed on 250 V, D.C. supply is 0.05 A. Determine the percentage error when the instrument is placed on 250 V, A.C. supply at 100 Hz.

Solution. Total ohmic resistance, $R = \frac{250}{0.05} = 500 \Omega$

(Original calibration of the instrument is with direct current)

Reactance of the coil, $X_L = 2\pi fL = 2\pi \times 100 \times 1 = 628 \Omega$

Coil impedance, $Z = \sqrt{R^2 + X_L^2} = \sqrt{(500)^2 + (628)^2} = 5039 \Omega$

$$\therefore \text{Voltage reading on A.C.} = \frac{250 \times 5000}{5039} = 248 \text{ V}$$

$$\therefore \text{Error} = 248 - 250 = -2 \text{ V}$$

$$\text{Percentage error} = \frac{2}{250} \times 100 = 0.8. \text{ (Ans.)}$$

Example 6. A 15-volt moving iron voltmeter has a resistance of 300 Ω and an inductance of 0.12 H. Assuming that this instrument reads correctly on D.C., what will be its readings on A.C. at 15 volts when frequency is (i) 25 Hz and (ii) 100 Hz?

Solution. On D.C., only ohmic resistance is involved and the voltmeter reads correctly. But on A.C., it is the *impedance* of the instrument which has to be taken into account.

(i) When frequency is 25 Hz :

Impedance at 25 Hz,

$$\begin{aligned} Z &= \sqrt{R^2 + X_L^2} = \sqrt{R^2 + (2\pi fL)^2} \\ &= \sqrt{(300)^2 + (2\pi \times 25 \times 0.12)^2} = 300.6 \Omega \end{aligned}$$

$$\therefore \text{Voltmeter reading} = 15 \times \frac{300}{300.6} = 14.97 \text{ V. (Ans.)}$$

(ii) When frequency is 100 Hz :

Impedance at 100 Hz,

$$Z = \sqrt{(300)^2 + (2\pi \times 100 \times 0.12)^2} = 309.3 \Omega$$

$$\therefore \text{Voltmeter reading} = 15 \times \frac{300}{309.3} = 14.55 \text{ V. (Ans.)}$$

Incidentally, it may be noted that as the frequency is increased, the impedance of the voltmeter is also increased. Hence, the current is decreased and, therefore, the voltmeter readings are lower.

5.2. Electrodynami c or Dynamometer Instruments

In an electrodynami c instrument the *operating field* is produced by another fixed coil and not by permanent magnet. This instrument can be used as an ammeter or as voltmeter but is generally used as a wattmeter.

Refer Fig. 19 (a), (b).

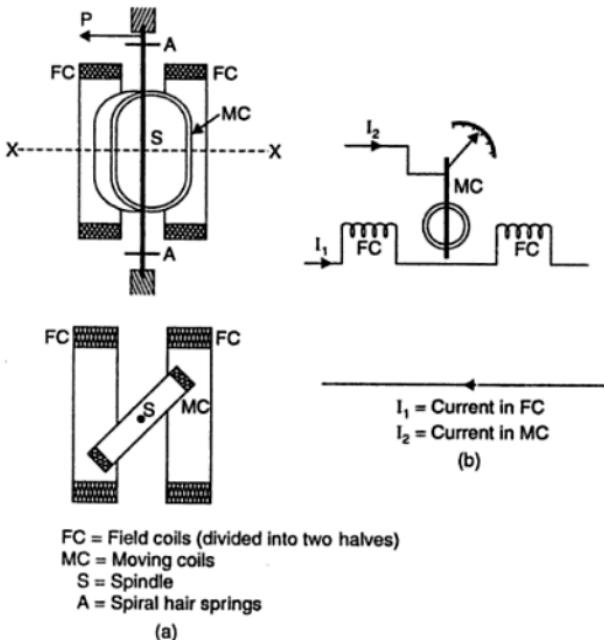


Fig. 19. Electrodynamometer or dynamometer instrument.

These instruments essentially consist of fine wire *moving coil* placed in the magnetic field produced by *another fixed coil* when carrying currents. The coils are usually *air cored* to avoid *hysteresis, eddy currents and other errors* when the instrument is used on A.C. The *fixed coil FC* is divided into two *halves* placed close together and *parallel* to each other in order to provide a *fairly uniform field* within the range of the movement of the moving coil.

The upper diagram in Fig. 19 (a) shows a sectional elevation through fixed coil FC and the lower diagram represents a sectional plan on XX. The moving coil MC is carried by a spindle S and the controlling torque is exerted by spiral hair springs A, which may also serve to lead the current into and out of MC.

Deflecting torque. The deflecting torque is due to *interaction of the magnetic fields produced by currents in the fixed and moving coils*.

- Fig. 20 (a) shows the magnetic field due to current flowing through FC (I_1) in the direction indicated by the dots and cross.
- Fig. 20 (b) shows the magnetic field due to current (I_2) in MC.
- Fig. 20 (c) shows the combined effect of the above magnetic fields. By combining these magnetic fields it will be seen that when currents (I_1 and I_2) flow simultaneously through FC and MC, the resultant magnetic field is *distorted* and effect is to exert a clockwise torque on MC.

Since MC is carrying current (I_2) at right angles to the magnetic field produced by FC, deflecting torque, $T_d \propto I_1 \times I_2$

or $T_d = KI_1I_2$ where K is a constant.

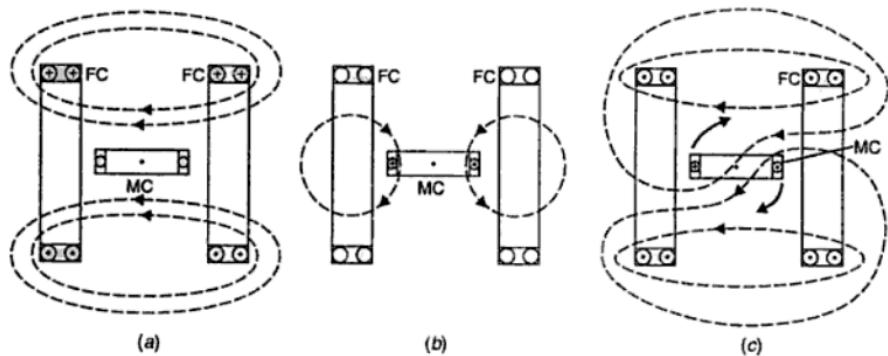


Fig. 20. Magnetic fields due to fixed and moving coils.

Since the instrument is spring-controlled, the restoring of control torque (T_c) is proportional to the angular deflection θ .

$$\therefore T_c \propto \theta \text{ or } T_c = K' \theta$$

The two torques (T_d and T_c) are equal and opposite in the final deflected position.

$$\therefore T_d = T_c$$

or

$$KI_1 I_2 = K' \theta$$

or

$$\theta \propto I_1 I_2$$

Use of the instrument as an ammeter. When the instrument is used as an ammeter then same current passes through both moving coil (MC) and fixed coils (FC) as shown in Fig. 21. In this case, $I_1 = I_2 = I$, hence $\theta \propto I^2$ or $I \propto \sqrt{\theta}$. The connections of Fig. 21. are used when *small currents* are to be measured.

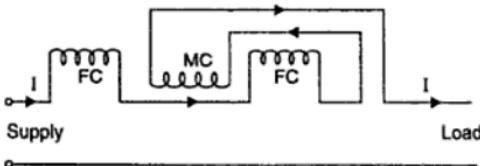


Fig. 21. Measurement of small currents.

In the case of *heavy currents*, a shunt is used to limit current through the moving coil as shown in Fig. 22.

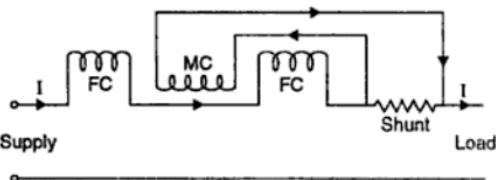


Fig. 22. Measurement of heavy currents.

Use of the instrument as voltmeter. When the instrument is used as a voltmeter, the fixed and moving coils are used in series along with a high resistance as shown in Fig. 23.

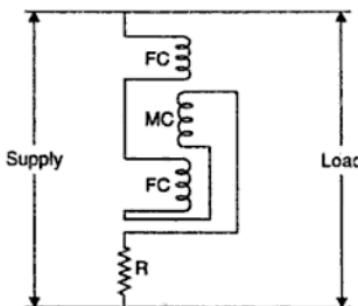


Fig. 23. Use of the instrument as a voltmeter.

Here again $I_1 = I_2 = I$,

where $I = \frac{V}{R}$ in D.C. circuits

and $I = \frac{V}{Z}$ in A.C. circuits

$$\therefore \theta \propto V \times V \quad \text{or} \quad \theta \propto V^2$$

$V = \sqrt{\theta}$

or,

Thus whether the instrument is used as an ammeter or voltmeter its scale is *uneven* through the whole of its range and is cramped or crowded near the zero in particular.

Note. When the dynamometer instrument is used to measure an alternating current or voltage, the moving coil due to its inertia takes up a position where the average deflecting torque over one cycle is balanced by the restoring torque of the spiral springs. For that position, the deflecting torque is proportional to the mean value of the square of current or voltage, and the instrument scale can therefore be calibrated to read the r.m.s. value.

- In these instruments the damping is pneumatic (i.e., air damping). Eddy current damping is admissible owing to weak operating field.

Ranges :

Ammeters. (i) With fixed and moving coils in series.....0/0.01 A—0/0.05 A

(ii) With moving coil shunted or parallel connections.....upto 0/30 A.

Voltmeters. Upto .0—750 volts.

Advantages and Disadvantages

Advantages :

(i) Can be used on both D.C. as well as A.C. systems.

(ii) They are free from hysteresis and eddy current errors.

(iii) It is possible to construct ammeters upto 10 A and volt-meters upto 600 V with precision grade accuracy.

Disadvantages :

(i) Since torque/weight ratio is small, such instruments have low sensitivity.

(ii) The scale is not uniform because $\theta \propto \sqrt{I}$.

(iii) Cost of these instruments is higher in comparison to those of moving iron instruments. So, these are only used as voltmeters and ammeters for precision measurements.

(iv) Higher friction losses.

6. RECTIFIER INSTRUMENTS

These are not separate types of instruments, but rather a means of using a D'Arsonval movement, in conjunction with a *rectifier*, to change A.C. to D.C. Thus, a direct current movement can be adopted for use with alternating current as shown in Fig. 24. Rectifier type meters, using copper oxide rectifiers, are useful at low frequencies and will give good indication upto about 20 kHz.

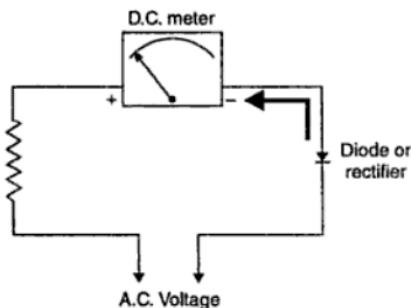


Fig. 24. A D.C. moving-coil meter can be used to measure A.C. voltage by putting a diode or rectifier in the meter circuit.

- Rectifier instruments can operate well into the R.F. (radio-frequency) range with the proper use of silicon or germanium rectifiers.
- Measurements of current and voltage at several hundred megahertz are possible.
- Another advantage is that this type of meter is more sensitive than any other type of A.C. meter.

Characteristics of Rectifier Instruments :

The characteristics of rectifier instruments are given below :

1. They provide an economical and practical means of A.C. measurements in radio and communication circuits at audio frequencies (1000 to 10000 Hz) and in other A.C. circuits where small available power makes it necessary to use sensitive low-energy instruments.
2. A rectifier instrument is, in general, approximately fifty times more sensitive than either an electrodynamometer or a moving-iron instrument.
3. In most instances rectifier instruments have essentially linear scales.
4. They commonly possess sensitivity of the order of 1000 to 2000 ohms per volt and more.
5. The power consumed by a rectifier instrument is generally several times as high as its permanent magnet moving coil (PMMC) mechanism because of the resistance of its rectifier.
6. Rectifier instruments are manufactured as microammeters and milliammeters in ratings from 100 μ A to 15 mA for full scale deflection. The higher rating of 15 mA is more or less governed by the special size of the rectifier in comparison with the mechanism with which it is to be used.
7. Shunting of rectifier instruments is not practical because of the change in resistance of the rectifier with both temperature and the amount of current.

Rectifier Ammeters. The *rectifier ammeters* usually consist of four rectifier elements *L*, *M*, *N* and *P* arranged in the form of a bridge (as shown in Fig. 25) and *A* represents a moving-coil ammeter. The apex of the black triangle (shown in the bridge) indicates the direction in which the resistance is low.

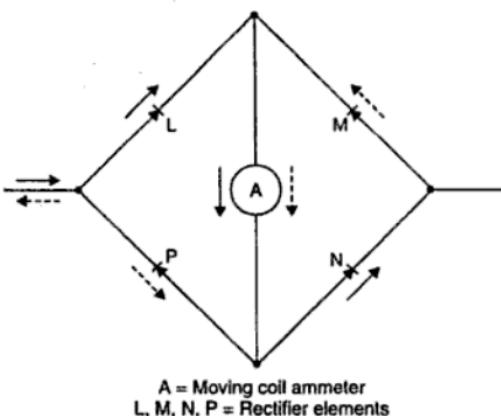


Fig. 25. Bridge circuit for full-wave rectification.

As shown in Fig. 25, during the half-cycles current flows through elements *L* and *N* from left to right as shown by the *full arrows*. During other half-cycles, the current flows through *M* and *N*, as shown by the *dotted arrows*. The waveform of the current flowing through *A* is therefore as shown in Fig. 26. The deflection of moving-coil ammeter *A*, thus depends upon the *average value of the current*; and the scale of *A* can be calibrated to read the r.m.s. value of the current on the assumption that the waveform of the latter is sinusoidal with a form factor of 1.11.

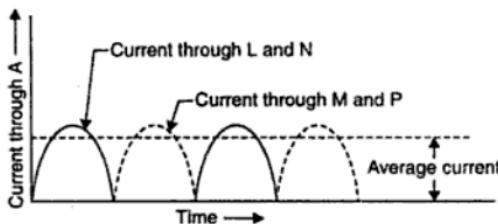


Fig. 26. Waveform of current through moving-coil ammeter.

Rectifier Voltmeters. In a *rectifier voltmeter*, *A* is a milliammeter and the bridge circuit of Fig. 25 is connected in series with a suitable resistor.

Advantages of rectifier instruments :

1. The primary advantage of the rectifier voltmeter is that it is *far more sensitive* as compared to other types of voltmeter suitable for measuring A.C. voltages.
2. Metal rectifiers can be incorporated in universal instruments, such as ammeter, thereby enabling a moving-coil milliammeter to be used in combination with shunt and series resistances to measure various ranges of D.C. and D.C. voltage, and in combination with a *bridge rectifier and suitable resistors* to measure various ranges of A.C. and A.C. voltage.

7. WATTMETERS

A wattmeter is a combination of an ammeter and a voltmeter and, therefore consists of two coils known as *current coil* and *pressure coil*. The operating torque is produced due to interaction of fluxes on account of currents in current and pressure coils.

There are following three types of wattmeters :

1. Dynamometer wattmeter
2. Induction wattmeter
3. Electrostatic wattmeter.

We shall discuss here only the first and second type.

7.1. Dynamometer Wattmeter. In Fig. 27, the dynamometer is connected as a wattmeter. This is one of the advantages of this type of meter. If the coils are connected so that a value of current proportional to the load voltage flows in one, and a value of current proportional to the load current

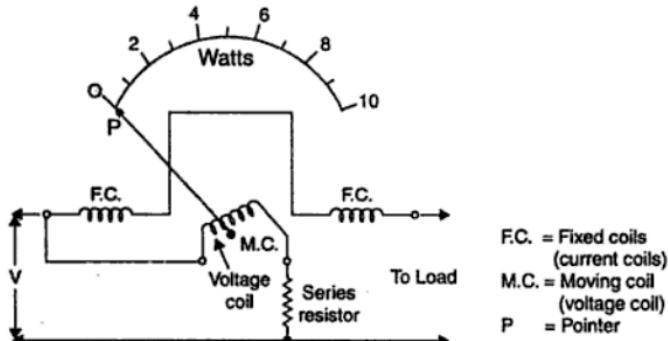


Fig. 27. Connection of dynamometer for measuring power.

flows in the other, the meter may be calibrated directly in watts. This is true because the indication depends upon the product of the two magnetic fields. The strength of the magnetic fields depends upon the values of currents flowing through the coils. If one current is proportional to load voltage and other current is the load current, then the meter can be calibrated in terms of watts or true power consumed by the load.

Let v = supply voltage,

i = load current, and

R = resistance of the moving coil circuit.

Current through fixed coils, $i_f = i$.

$$\text{Current through the moving coil, } i_m = \frac{v}{R}$$

$$\text{Deflecting torque, } T_d \propto i_f \times i_m \propto \frac{iv}{R}.$$

— For a D.C. circuit the deflecting torque is thus proportional to the power.

— For any circuit with fluctuating torque, the instantaneous torque is proportional instantaneous power. In this case due to inertia of moving parts the deflection will be proportional to the average torque i.e., the deflection will be proportional to the average power. For sinusoidal alternating quantities the average power is $VI \cos \phi$, where

V = r.m.s. value of voltage,

I = r.m.s. value of current, and

ϕ = phase angle between V and I .

Hence an electrodynamic instrument, when connected as shown in Fig. 27, indicates the power, irrespective of the fact it is connected in an A.C. or D.C. circuit.

- Scales of such wattmeters are more or less uniform because the deflection is proportional to the average power and for spring control, controlling torque is proportional to the deflection, hence $\theta \propto$ power. Damping is *pneumatic*.

Errors :

- The error may creep in due to the inductance of the moving or voltage coil. However, the high non-inductive resistance connected in series with coil swamps, to a great extent, the phasing effect of the voltage coil inductance.
- There may be error in the indicated power due to the following :
 - Some voltage drop in the current circuit.
 - The current taken by the voltage coil.

This error, however, in standard wattmeters may be overcome by having an additional compensating winding connected in series with the voltage coil but is so placed that it produces a field in opposite direction to that of the fixed or current coils.

Ranges :

- Current circuit. 0.25 to 100 A without employing current transformers.
- Potential circuit. 5 to 750 V without employing potential transformers.

Advantages :

- The scale of the instrument is uniform (because deflecting torque is proportional to true power in both the cases i.e., D.C. and A.C. and the instrument is spring controlled.)

(ii) High degree of accuracy can be obtained by careful design, hence these are used for calibration purposes.

Disadvantages :

(i) The error due to the inductance of pressure coil at low power factor is very serious (unless special features are incorporated to reduce its effect).

(ii) Stray field may effect the reading of the instrument. To reduce it, magnetic shielding is provided by enclosing the instrument in an iron case.

7.2. Induction Wattmeters. Induction wattmeters can be used on A.C. circuit only (in contrast with dynamometer wattmeters can be used both on D.C. and A.C. circuits) and are useful only when the frequency and supply voltage are constant.

The operation of all induction instruments depends on the *production of torque due to reaction between a flux ϕ_1 (whose magnitude depends on the current or voltage to be measured) and eddy currents induced in a metal disc or drum by another flux ϕ_2 (whose magnitude also depends on the current or voltage to be measured)*. Since the magnitude of eddy currents also depends on the flux producing them, the *instantaneous value of the deflecting torque is proportional to the square of the current or voltage under measurement and the value of mean deflecting torque is proportional to the mean square of the current or voltage*.

Fig. 28 shows an induction wattmeter. It has two laminated electromagnets one is excited by the current in the main circuit—its exciting winding being joined in series with the circuit, hence it is also called *series magnet*.

The other electromagnet is excited by current which is *proportional to the voltage of the circuit*. Its exciting coil is joined in parallel with the circuit, hence this magnet is sometimes referred to as *shunt magnet*.

A thin aluminium disc is mounted in such a way that it cuts the fluxes of both the magnets. Hence two eddy currents are produced in the disc. The *deflection torque is produced due to the interaction of these eddy currents and the inducing fluxes*. Two or three copper rings are fitted on the central limb of the shunt magnet and can be so adjusted as to make the resultant flux in the shunt magnet lag behind the applied voltage by a suitable angle.

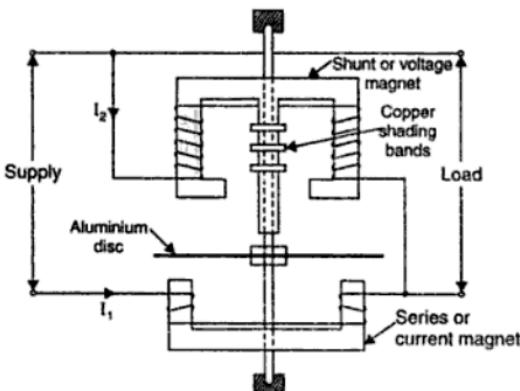


Fig. 28. Induction wattmeter.

This instrument is spring controlled, the spring being fitted to the spindle of the moving system which also carries a pointer. The scale is uniformly even and extends over 300° .

Such wattmeters can handle current upto 100 A. For handling greater currents they are used in conjunction with *current transformers*.

Advantages :

- (i) Fairly long scale (extending over 300°).
- (ii) Free from the effects of stray fields.
- (iii) Good damping.
- (iv) Practically free from frequency errors.

Disadvantages :

Sometimes subjected to serious temperature errors.

8. INTEGRATING METERS (ENERGY METERS)

Integrating or energy meters are used to measure the quantity of electric energy supplied to a circuit in a given time. They give no direct indication of power i.e., as to the rate at which energy is being supplied because their registrations are independent of the rate at which a given quantity of electric energy is being consumed.

The main difference between an *energy meter* and a *wattmeter* is that the former is fitted with some type of *registration mechanism* whereby all the instantaneous readings of power are summed over a definite period of time whereas the latter indicates the value at a *particular instant* where it is read.

8.1. Essential Characteristics of Energy Meters. The essential characteristics of energy meters are given below :

1. They must be simple in design and must not contain any parts which may rapidly deteriorate.
2. The readings may be given directly by the dials and must avoid any multiplying factors.
3. The casing of the meter should be dust, water and insect proof.
4. Permanency of calibration is a prime requisite and to attain it, the friction at the pivots etc., and retarding torque of the magnetic brakes must remain constant. The magnets should be so placed that they are not affected in their strength by the magnetic field of the current coil.

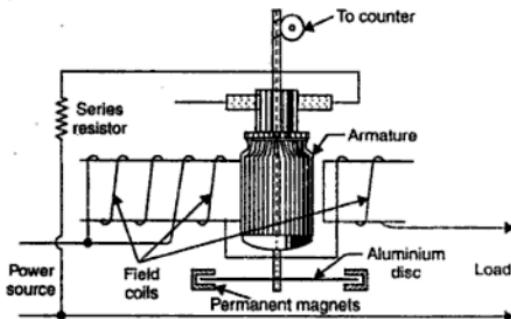


Fig. 29. Motor-driven meter (watt-hour meter) designed to operate on direct or alternating current.

aluminium conductor cutting through the lines of force of the permanent magnets. This is a form of magnetic damping.

The meter must overcome the friction of the bearings and indicators at *very light loads*. A portion of the field is produced by the armature current (coil in series with the armature winding). This coil is (called as compensating coil) wound to aid the field and is adjusted to the point where it just overcomes the meter friction.

8.5. Induction Type Watt-hour Meter. This is the most commonly used meter on A.C. circuits for measurement of energy.

Advantages :

- (i) Simple in operation
- (ii) High torque/weight ratio
- (iii) Cheap in cost
- (iv) Correct registration even at very low power factor
- (v) Unaffected by temperature variations
- (vi) More accurate than commutator type energy meter on light loads (owing to absence of a commutator with its accompanying friction).


Induction Type Single Phase Energy Meters. These are, by far, the most common form of A.C. meters met with in every-day *domestic and industrial installations*. These meters measure electric energy in kWh.

The principle of these meters is practically the same as that of induction watt meters. Instead of the control spring and the pointer of the watt-meter, the watt-hour meter, (energy meter) employs a *brake magnet and a counter attached to the spindle*. Just like other watt-hour meters, the eddy currents induced in the aluminium disc by the brake magnet due to the revolution of the disc, are utilised to control the continuously rotating disc.

Construction. The construction of a typical meter of this type is shown in Fig. 30. The brake-magnet and recording wheel-train being omitted for clearances. It consists of the following :

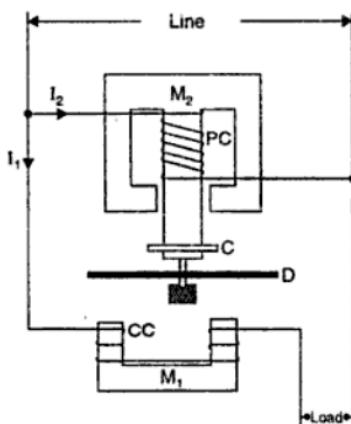- (i) Series magnet M_1
- (ii) Shunt magnet M_2
- (iii) Brake magnet
- (iv) A rotating disc.

The *series electro-magnet M_1* consists of a number of U-shaped iron laminations assembled together to form a core, wound with a few turns of a heavy gauge wire. This wound coil is known as



M_1 = Series or current magnet

M_2 = Shunt or voltage magnet

D = Disc

C = Copper shading bands

CC = Current coil

PC = Pressure coil

Fig. 30. Induction type single phase energy meter.

current coil and is connected in one of the lines and in series with the load to be metered. The series electromagnet is energized and sets up a magnetic field cutting through the rotating disc, when load current flows through the current coil C.C. The rotating disc is an aluminum disc mounted on a vertical spindle and supported on a sapphire cup contained in a bottom screw. The bottom pivot, which is usually removable, is of hardened steel, and the end, which is hemispherical in shape, rests in the sapphire cup. The top pivot (not shown) merely serves to maintain the spindle in a vertical position under working condition and does not support any weight or exert any appreciable thrust in any direction.

The *shunt magnet* M_2 consists of a number of M shaped iron laminations assembled together to form a core. A core having *large number of turns of fine wire* is fitted on the middle limb of the shunt magnet, this coil is known as *pressure coil P.C.* and is connected across the supply mains.

The *brake magnet* consists of C shaped piece of alloy steel bent round to form a complete magnetic circuit, with the exception of a narrow gap between the poles. This magnet is mounted so that the disc revolves in the air gap between the polar extremities. The movement of the rotating disc through the magnetic field crossing the air gap *sets up eddy currents in the disc which react with the field and exerts a braking effect*. The speed of the rotating disc may be adjusted by changing the position of the brake magnet or by diverting some of the flux there from.

Working. The shunt electromagnet produces a magnetic field which is of pulsating character ; it cuts through the rotating disc and induces eddy currents there in, but normally *does not in itself produce any driving force*. Similarly series electromagnet induces eddy currents in the rotating disc, but *does not in itself produce any driving force*. In order to obtain driving force in this type of meter, phase displacement of 90° between the magnetic field set up by shunt electromagnet and applied voltage V is achieved by adjustment of copper shading band C (also known as power factor compensator or compensating loop). The reaction between these magnetic fields and eddy currents set up a driving torque in the disc.

Sources of Errors. The various sources of errors in an induction-type energy meter are given below :

(i) *Incorrect magnitude of the fluxes.* These may arise from abnormal voltages and load currents.

(ii) *Incorrect phase relation of fluxes.* These may arise from defective lagging, abnormal frequencies, changes in the iron losses etc.

(iii) *Unsymmetrical magnetic structure.* The disc may go on rotating while no current is being drawn but pressure coils alone are excited.

(iv) *Changes in the resistance of the disc.* It may occur due to changes in temperature.

(v) *Changes in the strength of the drag magnets.* It may be due to temperature or ageing.

(vi) *Phase-angle errors due to lowering of power factor.*

(vii) *Abnormal friction of moving parts.*

(viii) *Badly distorted waveform.*

(ix) *Changes in the retarding torque due to the disc moving through the field of the current coils.*

Example 7. A 5 A, 230 V meter on full load unity power factor test makes 60 revolutions in 360 seconds. If the normal disc speed is 520 revolutions per kWh, what is the percentage error?

Solution. Energy consumed in 360 seconds

$$\begin{aligned} &= \frac{VI \cos \phi \times t}{3600 \times 1000} \text{ kWh} \\ &= \frac{230 \times 5 \times 1 \times 360}{3600 \times 1000} = 0.115 \text{ kWh} \end{aligned}$$

where, t is in seconds.

Energy recorded by the meter

$$\begin{aligned} &= \frac{60}{520} = 0.11538 \text{ kWh} \\ \therefore \% \text{ age error} &= \frac{0.11538 - 0.115}{0.115} \times 100 = 0.33\% \text{ (fast). (Ans.)} \end{aligned}$$

Example 8. The constant of a 230 V, 50 Hz, single phase energy meter is 185 revolutions per kWh. The meter takes 190 seconds for 10 revolutions while supplying a non-inductive load of 4.5 A at normal voltage. What is the percentage error of the instrument?

Solution. Energy consumed in 190 seconds

$$\begin{aligned} &= \frac{VI \cos \phi}{1000} \times t = \frac{230 \times 4.5 \times 1}{1000} \times \frac{190}{3600} = 0.0546 \text{ kWh} \\ &\quad [\cos \phi = 1, \text{ since load supplied is non-inductive}] \end{aligned}$$

$$\text{Energy registered by the meter} = \frac{10}{185} = 0.054 \text{ kWh}$$

$$\therefore \% \text{ age error} = \frac{0.054 - 0.0546}{(0.054)} = 0.06\% \text{ (slow). (Ans.)}$$

Example 9. The name plate of a meter reads "1 kWh = 15000 revolutions". In a check up, the meter completed 150 revolutions during 45 seconds. Calculate the power in the circuit.

Solution. Power metered in 150 revolutions

$$= 1 \times 150/15000 = 0.01 \text{ kWh}$$

If P kilowatt is the power in the circuit, then energy consumed in 45 seconds

$$= \frac{P \times 45}{3600} \text{ kWh} = 0.0125 P \text{ kWh}$$

Equating the two amounts of energy, we have

$$0.0125 P = 0.01$$

$$\therefore P = 0.8 \text{ kW} = 800 \text{ W. (Ans.)}$$

Example 10. A 230 V ampere-hour type meter is connected to a 230 V.D.C. supply. If the meter completes 225 revolutions in 10 minutes when carrying 14 A, calculate : (i) The kWh registered by the meter, and (ii) The percentage error of the meter above or below the original calibration.

The timing constant of the meter is 40 A-s/revolution.

Solution. During 225 revolutions the meter would register 40×225 A-s or coulombs. since time taken is 10 minutes or 600 seconds it corresponds to a current of $\frac{40 \times 225}{600} = 15$ A.

$$(i) \text{ Energy recorded by the meter} = \frac{VIt}{1000} \text{ kWh}$$

where t is in hour

$$= \frac{230 \times 15}{1000} \times \frac{10}{60} = 0.575 \text{ kWh.}$$

$$(ii) \text{ Actual energy consumed} = \frac{230 \times 14}{1000} \times \frac{10}{60} = 0.5367 \text{ kWh}$$

$$\text{Percentage error} = \frac{0.575 - 0.5367}{0.575} \times 100 = 6.66\%. \quad (\text{Ans.})$$

9. MEASUREMENT OF RESISTANCE

9.1. Voltmeter-Ammeter Method. Fig. 31 (a) and (b) shows two methods of connections for measurement of resistance.

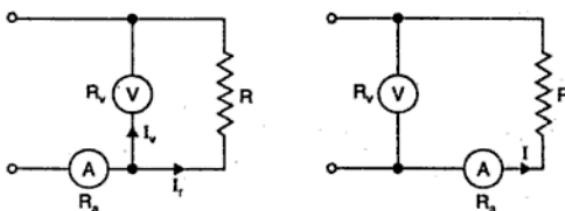


Fig. 31. Methods for measuring resistance.

- Let R_a = resistance of the ammeter (which is very small),
 R_v = resistance of the voltmeter (which is a large value),
 R = resistance to be measured,
 V = reading of the voltmeter, and
 I = reading of the ammeter.

Fig. 31 (a) shows the connections for measurement of *low resistances*.

Here $I = I_v + I_r$

$$= \frac{V}{R_v} + \frac{V}{R}$$

$$\therefore \frac{V}{R} = I - \frac{V}{R_v}$$

$$\text{or } R = V / \left(1 - \frac{V}{R_v} \right) \quad \dots(1)$$

$$\text{If } R_v \text{ is very high, } R = \frac{V}{I} \quad \dots(2)$$

Fig. 31 (b) shows the connections for measurement of high and low resistances.

$$\text{Here } V = IR_a + IR$$

$$\therefore IR = V - IR_a$$

$$\text{or } R = \frac{V}{I} - R_a \quad \dots(3)$$

If the value of R_a is very small

$$R = \frac{V}{I} \quad \dots(4)$$

9.2. Substitution Method. The connections for measurement of resistance by substitution are shown in Fig. 32.

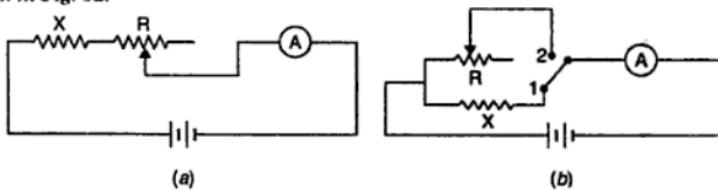


Fig. 32. Measurement of resistance by substitution.

Let R be a variable resistance which can be changed in small steps, say of 0.1Ω .

(i) Refer Fig. 32 (a). First resistance X is put in the circuit and the value of current noted.

Then resistance X is removed and it is substituted by a known variable resistance R which is varied so that the value of the current is same in both the cases. *This value of R is equal to the unknown resistance.*

(ii) If R is of fixed value note the readings of the ammeter for the following cases :

(a) For resistances X and R in series.

(b) When resistance X is removed.

Let the readings of the ammeter for these cases be I_1 and I_2

$$\therefore I_1 = \frac{V}{R+X} \quad \dots(5)$$

$$\text{and } I_2 = \frac{V}{R} \quad \dots(6)$$

$$\frac{I_2}{I_1} = \frac{R+X}{R} = 1 + \frac{X}{R} \quad \dots(7)$$

$$\text{or } \frac{X}{R} = \frac{I_2}{I_1} - 1$$

$$\text{or } X = R \left(\frac{I_2 - I_1}{I_1} \right) \quad \dots(8)$$

(iii) Refer Fig. 32 (b). The two-way switch first makes contact with 1 and then with 2 and let these readings be I_1 and I_2 .

$$I_1 = \frac{V}{X} \text{ (when } X \text{ is in the circuit)} \quad \dots(9)$$

$$I_2 = \frac{V}{R} \text{ (when } R \text{ is in the circuit)} \quad \dots(10)$$

$$I_2/I_1 = X/R$$

so that $X = R \times \frac{I_2}{I_1}$... (11)

9.3. Measurement of Resistance by the Wheatstone Bridge. In Wheatstone bridge method of measuring resistances, a resistor of *unknown* resistance is balanced against resistors of known resistances. Though based on comparison of resistances, this is one of the most accurate methods of measuring resistances as it is independent of the calibration of the indicating instrument and relies upon the null-point method.

The four branches of the network ABCDA (see Fig. 33) have two known resistances P and Q , a known variable resistance R and the unknown resistance X . A battery E is connected through a switch S_1 to junctions A and C ; and a galvanometer G , a variable resistor Z and a switch S_2 are in series across B and D . The function of Z is merely to protect G against an excessive current should the system be seriously out of balance when S_2 is closed.

After closing S_1 and S_2 , R is adjusted until there is no deflection on G with the resistance of Z reduced to zero. Junctions B and D are then at the same potential, so that p.d. between A and B is the same as that between A and D , and the p.d. between B and C is the same as that between C and D .

Let I_1 and I_2 be the currents through P and R respectively when the bridge is balanced. From Kirchhoff's first law it follows that since there is no current through G , the currents through Q and X are also I_1 and I_2 respectively.

But potential difference (p.d.) across $P = PI_1$

Potential differences across $R = RI_2$

$$\therefore PI_1 = RI_2 \quad \dots (12)$$

Also potential difference across $Q = QI_1$

Potential difference across $X = XI_2$

$$QI_1 = XI_2 \quad \dots (13)$$

Dividing (13) by (12), we get

$$\frac{Q}{P} = \frac{X}{R}$$

$$\therefore X = R \times \frac{Q}{P} \quad \dots (14)$$

which is the relation of Wheatstone bridge. P and Q are usually called the *ratio arms* and X as the *balance or rheostat arm*. The battery and the galvanometer can be interchanged without affecting the relation.

Note. The resistances P and Q may take the form of the resistance of a slide-wire, in which case R may be a fixed value and the balance is obtained by moving a sliding contact along the wire. If the wire is homogeneous and of uniform section, the ratio of P to Q is the same as the ratio of the lengths of wire in the respective arms.

10. THE POTENTIOMETER

For the accurate measurement of potential difference, current and resistance the *potentiometer* is one of the most useful instruments.

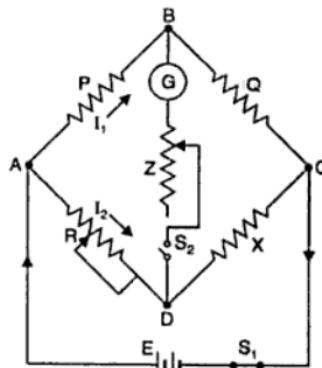


Fig. 33. Wheatstone bridge.

Its principle of action is that an unknown e.m.f. or p.d. is measured by balancing it, wholly or in part, against a known difference of potential.

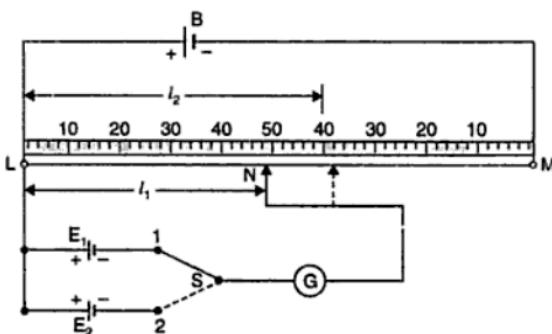


Fig. 3.34. A simple potentiometer.

Construction. The potentiometer, in its simplest form, consists of wire LM of uniform cross-section, stretched alongside a scale and connected across an accumulator B of ample capacity. A standard cell of known e.m.f. E_1 is connected between L and terminal 1 of a two-way switch S , care being taken that the corresponding terminals of B and E_1 are connected to L .

Working

- Slider N is pressed momentarily against wire LM and its position adjusted until the galvanometer deflection is zero when N is making contact with LM . Let l_1 be the corresponding distance between L and N . The fall of potential over length l_1 of the wire is then the same as the e.m.f. E_1 .
- Then move the switch S to 2, thereby replacing the standard cell by another cell, the e.m.f. E_2 of which is to be measured. Adjust the slider N again to give zero deflection on G . If l_2 be the new distance between L and N , then

$$\frac{E_2}{E_1} = \frac{l_2}{l_1}$$

or
$$E_2 = \frac{l_2}{l_1} \times E_1 \quad \dots(15)$$

Applications of potentiometer. The following are the applications/uses of potentiometers :

1. Measurement of small e.m.fs. (upto 2 volts).
2. Comparison of e.m.fs. of two cells.
3. Measurement of high e.m.fs. (say 250 volts).
4. Measurement of resistance.
5. Measurement of current.
6. Calibration of ammeter.
7. Calibration of voltmeter.

Example 11. Using a Weston cadmium cell of 1.0183 V and a standard resistance of 0.1Ω a potentiometer was adjusted so that 1.0183 m was equivalent to the e.m.f. of the cell ; when a certain direct current was flowing through the standard resistance, the voltage across it correspond to 150 cm. What was the value of current ?

(ii) Operating personnel coming in contact with the instruments are not subjected to high voltage and current of the lines, and so there is less danger to them. Even with a low-voltage system, instrument transformers are used for measuring large currents, so that heavy leads to the instrument panel and to the ammeter and other current terminals are avoided.

The principle of the instrument transformer is fundamentally the same as that of the power transformer. The instrument transformers are classified as follows :

1. Potential transformers.
2. Current transformers.

12.1. Potential Transformers (P.T.)

- A potential transformer is a *step down transformer* used along with a low range voltmeter for measuring a high voltage. The primary is connected across the high voltage supply and the secondary to the voltmeter or potential coil of the wattmeter. Since the voltmeter (or potential coil) impedance is very high, the secondary current is very small and the potential transformer behaves as an ordinary two winding transformer operating on no-load. Fig. 36 shows a potential transformer used to measure the voltage of a circuit. It may be noted that the secondary is grounded. This is done so that if the insulation breaks down, the high voltage does not endanger personnel who may be reading the meters.
- These transformers are made with high quality iron core operating at very low flux

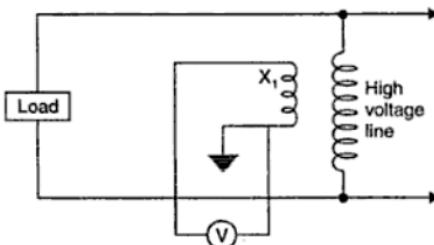


Fig. 36. Potential transformer connections.

densities so that the magnetising current may be very small. Careful design ensures minimum variation of voltage ratio with load and minimum phase shift between input and output voltages. Potential transformers secondary are commonly designed for an output of 110 V.

12.2. Current Transformers (C.T.)

- Just as a shunt extends the range of a D.C. ammeter, so does the current transformer perform the same function in A.C. circuits. Thus a *high magnitude alternating current can be easily measured by a combination of a current transformer and a low range ammeter*.
- The primary of a current transformer (C.T.) consists of a few turns of thick cross-section connected in *series* with the high current line. Very often the primary is just one turn formed by taking the line conductor through the secondary winding (Fig. 37). The secondary winding consists of a large number of turns of fine wire designed for either 5 A or 1 A rating. Thus a current transformer is *step-up transformer*. The current transformer has the secondary effectively short-circuited through the low impedance of the ammeter. Fig. 38 shows the current transformer connections.

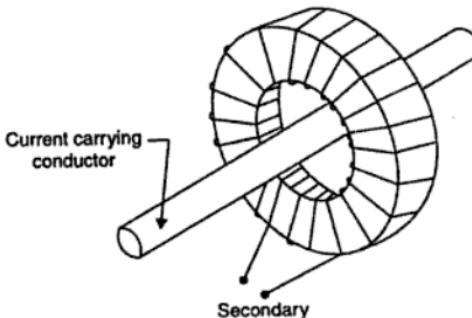


Fig. 37. Line conductor acting as primary.

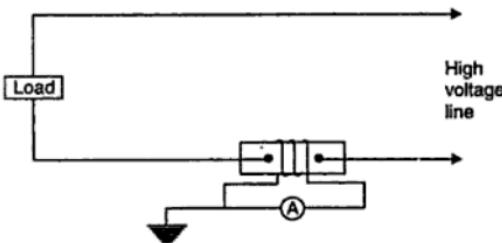


Fig. 38. Current transformer connections.

- The current transformer ratio is not equal to the ratio of secondary to primary turns, mainly because of the effect of the magnetising current. The primary current can be thought of as the sum of two currents, the first to balance secondary current so that primary and secondary m.m.f.s. may balance and the second being the no-load current I_0 . The component I_0 besides being responsible for a slight error in the current ratio, is also responsible for a phase angle error. The transformer must be carefully designed to minimise the ratio and phase angle error.

It may be noted that current transformer must never be operated on open-circuit for the following two reasons :

(i) There will be no secondary m.m.f. and since the primary current (and m.m.f.) is fixed, the core flux will increase enormously. This will cause large eddy current and hysteresis losses and the resulting high temperature may damage the insulation or even the core.

(ii) A very high voltage will be induced in the multi-turn secondary and this high voltage may be dangerous both to life and to the insulation.

Fig. 39 shows the wiring diagrams for potential and current instrument transformers.

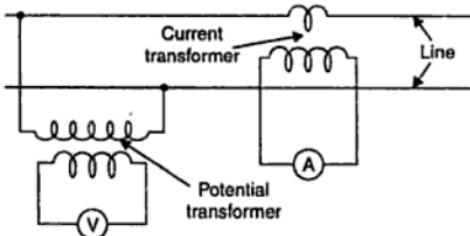


Fig. 39. Wiring diagrams for potential and current instrument transformers.

HIGHLIGHTS

- Absolute instruments** are those instruments which indicate the quantity to be measured in terms of the *constants of the instrument* and in order to find out the quantity in the practical units it is necessary to multiply such deflections with an instrument constant.
- Secondary instruments** are those instruments in which the value of electrical quantity to be measured can be determined from the deflection of the instrument only when they have been precalibrated by comparison with an absolute instrument.
These are classified as :
 - Indicating instruments
 - Recording instruments
 - Integrating instruments.
- Essential features of indicating instruments** are :
 - Deflecting device
 - Controlling device
 - Damping device.
- Moving iron instruments** are of the following two types :
 - Attraction type
 - Repulsion type.
- Moving-coil instruments** are of the following two types :
 - Permanent magnet type
 - Dynamometer type.
- Rectifier instruments** can operate well into the R.F. range with the proper use of silicon or germanium rectifiers. They are more sensitive than any other type of A.C. meter.
- A wattmeter** consists of two coils known as current coil and pressure coil.
- Integrating (or energy) meters** are used to measure the quantity of electric energy supplied to a circuit in a given time. These are generally of the following three types :
 - Electrolytic meters
 - Motor meters
 - Clock meters.
- The resistance** can be measured by the following methods :
 - Voltmeter-ammeter method
 - Substitution method
 - By using wheatstone bridge
 - By using a potentiometer.
- Meggars** are instruments which measure the insulation resistance of electric circuits relative to earth and one another.

THEORETICAL QUESTIONS

1. Differentiate between an absolute instrument and a secondary instrument.
2. How are secondary instruments classified ?
3. What are the essential features of an indicating instrument ?
4. What are the advantages and disadvantages of gravity controlled instruments ?
5. Explain briefly the following :
 - (i) Air damping
 - (ii) Fluid friction damping
 - (iii) Eddy current damping.
6. Explain briefly, with the help of sketches, the construction and working of the following moving iron instruments :
 - (i) Attraction type
 - (ii) Repulsion type.
7. What are the advantages and disadvantages of moving-iron instruments ?
8. How are moving coil instruments classified ?
9. Give the construction and working of a permanent magnet moving-coil type instrument. Also enumerate its advantages and disadvantages.
10. Explain the construction and working of a dynamometer type instrument. How it can be used as an ammeter and a voltmeter.
11. Give the characteristics of rectifier instruments.
12. Explain briefly the following :
 - (i) Rectifier ammeters
 - (ii) Rectifier voltmeters.
13. What is a wattmeter ?
14. Enumerate types of wattmeter.
15. Discuss the construction working of a dynamometer wattmeter with the help of a neat diagram.
16. Draw a neat sketch of an induction wattmeter and explain its working. Also state its advantages and disadvantages.
17. What is an integrating or energy meter ?
18. What are the essential characteristics of energy meters ?
19. Give the construction and working of a motor-driven meter-watt hour meter.
20. With the help of a neat sketch explain the construction and working of an induction type single phase energy meter. Also discuss the sources of errors prevalent in this type of energy meter.
21. What are the various methods by which a resistance can be measured ?
22. Explain any two of the following methods of measuring resistance :
 - (i) Voltmeter-ammeter method
 - (ii) Substitution method
 - (iii) Measurement of resistance by the Wheatstone bridge.
23. Explain briefly the following :
 - (i) The potentiometer
 - (ii) Meggar.
24. What are instrument transformers ?
25. How are instrument transformers classified ?
26. Explain briefly, with near sketches the following :
 - (i) Potential transformers
 - (ii) Current transformers.

UNSOLVED EXAMPLES

- A moving-coil instrument gives full-scale deflection with 15 mA and has a resistance of $5\ \Omega$. Calculate the resistance to be connected :
 (i) in parallel to enable the instrument to read upto 1 A.
 (ii) in series to enable it to read upto 100 V. [Ans. (i) $0.076\ \Omega$ (ii) $6661.7\ \Omega$]
- A moving-coil instrument has a resistance of 10 ohms and gives a full-scale deflection when carrying 50 mA. Show how it can be adopted to measure voltage upto 750 volts and current upto 100 amperes. [Ans. $R = 14990\ \Omega$, $R_s = 0.005\ \Omega$]
- A 20 V moving-iron voltmeter reads correctly when put on D.C. and the instrument has a resistance of 600 ohms and inductance of 0.15 H. Find out the reading on 20 V A.C. mains (i) at 250 Hz (ii) 50 Hz. [Ans (i) 18.6 V, (ii) 19.87 V]
- A 15 V moving-iron voltmeter has a resistance of $500\ \Omega$ and inductance of 0.12 H. Assuming that this instrument reads correctly on D.C. what will be its reading on A.C. at 15 V when the frequency is (i) 25 Hz and (ii) 100 Hz ? [Ans. (i) 14.99 V, (ii) 14.83 V]
- The total resistance of a moving-iron voltmeter is $1000\ \Omega$ and coil has an inductance of $0.765\ H$. The instrument is calibrated with a full-scale deflection of 50 V D.C. Calculate the percentage error when the instrument is used on (i) 25 Hz supply, (ii) 50 Hz supply, the applied voltage being 50 V in each case. [Ans. (i) 0.72%, (ii) 36%]
- In a moving-coil instrument, the moving coil has 40 turns and is of square shape with a mean length of 40 mm along each side. The coil hangs in a uniform radial field of $0.08\ Wb/m^2$. Find the turning moment of the coil when it is carrying a current of 10 mA. [Ans. $512 \times 10^{-7}\ N \cdot m$]
- A moving-coil instrument has a resistance of $5\ \Omega$ between terminals and full scale deflection is obtained with a current of 0.015 A. The instrument is to be used with a manganin shunt to measure 100 A full scale. Calculate the error caused by a $10^\circ C$ rise in temperature. (i) when the internal resistance of $5\ \Omega$ is due to copper only, (ii) when a $4\ \Omega$ manganin swamping resistor is used in series with a copper resistor of $1\ \Omega$.
 Take : $\alpha_{copper} = 0.004/^\circ C$ and $\alpha_{manganin} = 0.00015/^\circ C$. [Ans. (i) 3.7%, (ii) 0.8%]
- A 230 V, 50 Hz, single phase energy meter has a constant of 200 revolutions per kWh. While supplying a non-inductive load of 4.4 A at normal voltage the meter takes 3 minutes for 10 revolutions. Calculate the percentage error of the instrument. [Ans. 1.186% (slow)]
- The disc of an energy meter makes 600 revolutions per unit of energy. When a 1000 W load is connected, the disc rotates at 10.2 r.p.m. If the load is on for 12 hours, how many units are recorded as error ? [Ans. 0.24 kWh more]
- The name plate of a meter reads "1 kWh = 15000 revolutions". In a check up, the meter completed 150 revolutions during 50 seconds. Calculate the power in the circuit. [Ans. 720 W]

Miscellany

- Characteristics of D.C. Generators—Separately excited generator—No-load saturation characteristic (or O.C.C.)—Internal and external (or load) characteristics—Building up the voltage of self-excited shunt generator—Shunt generator characteristics—External characteristics—Effect of varying excitation—Voltage regulation—Internal or total characteristic—External characteristic and no-load saturation curve—Voltage control of shunt generators—Series generator—Compound wound generator—Characteristics of cumulative compound generator—Characteristics of differential compound generator—Applications of D.C. generators.
- Speed Control of D.C. Motors—Factors controlling the speed—Field control method—Rheostatic control—Voltage control.
- Electromechanical Energy Conversion—Introduction—Principle of energy conversion—Faraday's laws of electromagnetic induction—Singly and multiply—Excited magnetic field systems—Torque production in rotating machines—General analysis of electromechanical system—Worked examples—Highlights—Objective type questions—Theoretical questions—Unsolved examples.

1. CHARACTERISTICS OF D.C. GENERATORS

The properties of generators are analysed with the aid of characteristics which give the relations between fundamental quantities determining the operation of a generator. These include the voltage across the generator terminals V , the field or exciting current I_f , the armature current I_a , and the speed of rotation N .

The three most important characteristics of D.C. generators are given below :

- No load saturation characteristics $\left(\frac{E_0}{I_f} \right)$

- Internal or total characteristics $\left(\frac{E}{I_a} \right)$

- External characteristics $\left(\frac{V}{I} \right)$.

1. **No load saturation characteristic** $\left(\frac{E_0}{I_f} \right)$. It is also known as *magnetic or open circuit characteristic* (O.C.C.). It shows the relationship between the no-load generated e.m.f. in armature, E_0 and field or exciting current I_f at a given fixed speed. The shape of the curve is practically the same for all types of generators whether they are separately excited or self-excited. It is just the magnetisation curve for the material of the electromagnets.

2. **Internal or total characteristic** $\left(\frac{E}{I_a} \right)$. It gives the relationship between the e.m.f. E actually induced in the armature after allowing for the demagnetising effect of armature reaction and the armature current I_a . This characteristic is of interest mainly to the designer.

- External characteristic** $\left(\frac{V}{I} \right)$

- This characteristic is also referred to as *performance characteristic* or sometimes *voltage-regulating curve*.

- It gives relation between the *terminal voltage V* and *load current I*.
- The curve lies below the internal characteristic because it takes into account the voltage drop over the armature circuit resistance. The values of *V* are obtained by subtracting $I_a R_a$ from corresponding values of *E*.
- The characteristic is of great importance in judging the suitability of a generator for a particular purpose.

The external characteristic can be obtained by the following two ways :

- (i) By making simultaneous measurements with a suitable voltmeter and an ammeter on a loaded generator.
- (ii) Graphically from the O.C.C. provided the armature and field resistances are known and also if the demagnetising effect of the armature reaction is known.

1.1. Separately Excited Generator

- Fig. 1 shows the connections of a separately excited generator, a battery being indicated as the source of exciting current, although any other constant voltage source could be used.

The field circuit is provided with a variable resistance and would normally contain a field switch and an ammeter, these being omitted from the diagram for simplicity. The armature is connected through 2-pole main switch to the bus bars, between which the load is connected.

1.1.1. No-Load saturation characteristic (or O.C.C.)

- If the generator is run at constant speed with the main switch open, and the terminal voltage is noted at various values of exciting or field current then the O.C.C. shown in

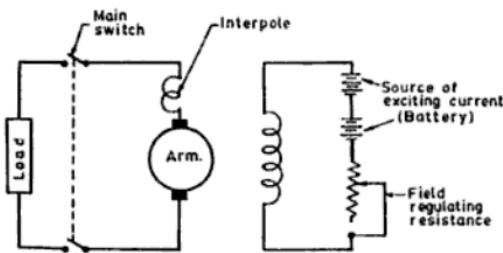


Fig. 1. Connection for a separately excited generator.

Fig. 2 can be plotted. This is also referred to as the '*magnetisation curve*' since the same graph shows, to a suitably chosen scale, the amount of magnetic flux, there being a constant relationship (depending upon speed of rotation) between flux and induced voltage.

- It will be noticed that a small voltage is produced when the field current is zero, this being due to a small amount of permanent magnetism in the field poles. This is called *residual magnetism* and is usually sufficient to produce 2 or 3 per cent of normal terminal voltage, although in some special cases it is purposely increased to 10 per cent or more.
- The first part of the curve is approximately straight and shows that the flux produced is proportional to the exciting current; but after a certain point, saturation of the iron becomes perceptible as the curve departs from straight line form.

terminal voltage of the generator decreases. There are three factors that cause this decrease in voltage :

- (i) Armature-circuit resistance (R_a),
- (ii) Armature reaction, and
- (iii) Reduction in field current.

(i) **Armature-circuit resistance.** The armature circuit of a generator, like every electrical circuit, contains resistance. This resistance includes the resistance of (i) the copper conductors of the armature winding, (ii) the commutator, (iii) contact resistance between brushes and commutator, and (iv) the brushes themselves. When no current flows through the armature, there is no IR drop in the armature and the voltage at the terminals is the same as the generated voltage. However, when there is current in the armature circuit, a voltage drop exists due to the armature resistance, and the terminal voltage is less than the generated voltage. The terminal voltage may be calculated from the following relation :

$$V = E_g - I_a R_a$$

where V = voltage at terminals of generator,

E_g = generated or induced voltage,

I_a = total armature current, and

R_a = armature-circuit resistance.

(ii) **Armature reaction.** When current flows in the armature conductors a flux surrounds these conductors. The direction of this armature flux is such that it reduces the flux from the field poles, resulting in both a reduced generated voltage and terminal voltage.

(iii) **Reduction in the field current.** The field circuit is connected across the terminals of the generators. When the terminal voltage of the generator becomes smaller because of the armature-resistance volt drop and armature reaction, the voltage across the field circuit also becomes smaller and therefore field current will be less. A reduction in the magnitude of field current also reduces the flux from the field poles, which in turn reduces the generated voltage and also the terminal voltage.

1.3.1. External characteristic

- See Figs. 6 and 7. The effect of the preceding three factors is shown in Fig. 7, which shows external (load-voltage) characteristic of a shunt generator.
- As shown in the circuit of Fig. 6, the readings of the voltage across the armature (and load), V are plotted as a function of load current, I . The voltage, V , is the same as E_g at no load (neglecting the $I_a R_a$ and armature reaction drop produced by the field current). The effects of armature reaction, armature circuit voltage drop, and decrease in field current are all shown with progressive increase in load. Note that both the armature reaction and the $I_a R_a$ drops are shown as dashed straight lines, representing theoretically linear voltage directly proportional to the increase in load current. The drop owing to decreased field current is a curved line, since it depends on the degree of saturation existing in the field at the value of load.

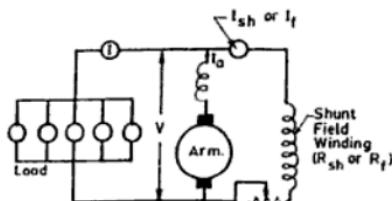


Fig. 6. Shunt generator under load.

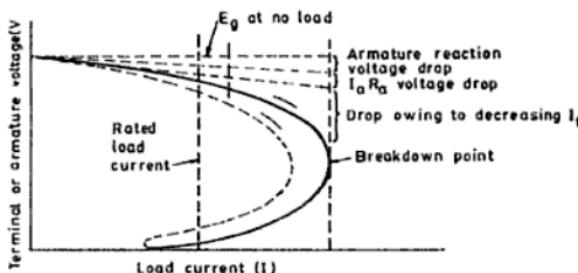


Fig. 7. Shunt generator load characteristics.

- Generally, the external load-voltage characteristic decreases with application of load only to a small extent up to its rated load (current) value. Thus, the shunt generator is considered as having a fairly constant output voltage with application of load, and in practice, is rarely operated beyond the rated load current value continuously for any appreciable time.
- As shown in Fig. 7 further application of load causes the generator to reach a breakdown point beyond which further load causes it to 'unbuild' as it operates on the unsaturated portion of its magnetisation curve. This unbuilding process continues until the terminal voltage is zero, at which point the load current is of such magnitude that the internal armature circuit voltage drop equals the e.m.f. generated on the unsaturated or linear portion of its magnetisation curve.
- It may be noted that if the external load is decreased (an increase of external load resistances), the generator will tend to build up gradually along the dashed line shown in Fig. 7. Note that for any value of load current, the terminal or armature voltage is less (as the voltage increases) compared to the solid lines which yield a higher voltage (as the voltage decreases). This difference is due to hysteresis.

1.3.2. Effect of varying excitation. Fig. 8 shows the effect of varying excitation upon the external characteristic of a shunt generator. With normal excitation the initial slope is small and heavy load current can be varied. With reduced excitation, the fall of voltage is more rapid and the maximum load current is reduced.

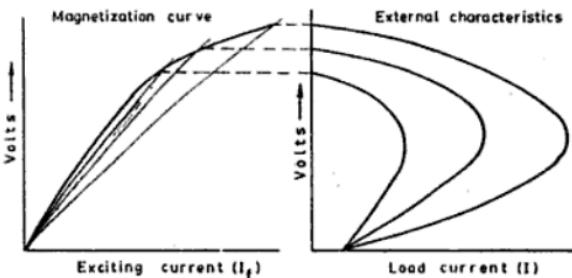


Fig. 8. Effect of varying excitation.

1.3.3. Voltage regulation. The term 'voltage regulation' is used to indicate the degree of change in armature voltage produced by application of load. If there is little change from no-load to full load, the generator or voltage-supplying device is said to possess good voltage regulation. If the voltage changes appreciably with load, it is considered to have poor voltage regulation.

'Voltage regulation' is defined as the change in voltage from no-load to full load, expressed as a percentage of the rated terminal voltage (armature voltage at full load).

$$\text{i.e. Per cent voltage regulation} = \frac{V_{nl} - V_{fl}}{V_{fl}} \times 100 \quad \dots(1)$$

where V_{nl} = no load terminal voltage,
 V_{fl} = full load (rated) terminal voltage.

1.3.4. Internal or total characteristic. To determine internal characteristic from external characteristic the following procedure is adopted [see Fig. 9 (a)].

Steps : 1. From the given data, draw the external characteristic (I).

2. Draw the shunt field resistance line OL and armature resistance line OM .
3. On the external characteristic take any point say F .
4. From point F draw vertical and horizontal lines intersecting X and Y axes respectively. Let these lines be FC and FA respectively.
5. Take point D on X -axis so that $CD = AB$ representing the shunt field current, I_{sh} .
6. From point D draw vertical DE and produce it intersecting line AF produced at H .
7. Take point G on line DH produced so that $HG = DE (= I_a R_a)$ representing the armature drop.
8. Following the above procedure take a number of points on external characteristic and find corresponding points lying on internal characteristic.
9. Draw a curve passing through these points which is the required internal characteristic (II).

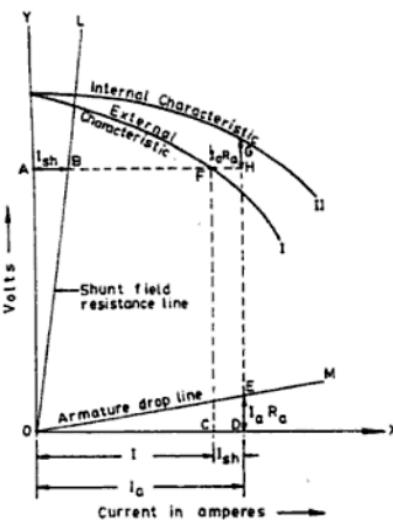


Fig. 9 (a). Determination of internal characteristic from external characteristic.

1.3.5. External characteristic and no-load saturation curve. The external characteristic of a shunt generator can be obtained directly from its no-load saturation curve as explained below. Following two cases will be considered :

(A) When armature reaction is so small as to be negligible. This is more or less true for generators fitted with compoles.

(B) When armature reaction is not negligible.

(B) Taking Armature Reaction into Account :

Here, in addition to considering the voltage drop in armature, voltage drop due to armature reaction is also taken into account.

Let $I_a R_a$ = voltage drop in armature

I_{sh} = increase in shunt field current to counteract the demagnetising effect.

Now if a right-angled triangle say lmn is drawn as that ln = voltage drop in armature, and mn = shunt field current. The triangle lmn is called as the *drop reaction triangle*.

In order to draw external and internal characteristic repeat the process as in A with following modifications in steps 4 and 9 respectively.

4. Take any point L on the O.C.C. and draw line LM parallel to the line lm of triangle lmn and complete the triangle LMN . Now from the points L and M draw vertical lines cutting X-axis at points N' and M' . Now LN' represents the generated e.m.f. MM' represents the terminal voltage, LN represents the voltage drop in armature due to armature resistance, ON' is the shunt field current to induce an e.m.f. represented by LN' and $N'M'$ is the increase in shunt field current to counteract the demagnetising effect
9. Take TU = shunt field current ON' (scale being different). OU represents the load current corresponding to the armature current represented by OT and terminal voltage MM' .

1.3.6. Voltage control of shunt generators

- The terminal voltage of a shunt generator may be kept constant at all loads with the use of adjustable resistance, called a *field rheostat, connected in series with the shunt-field circuit*. By adjusting the resistance of the rheostat to suit the load on the machine, changes in terminal voltage with load may be prevented. When the load changes gradually, hand control of the rheostat may be used, although *automatic control* employing a *voltage regulator* is far more satisfactory.
- The terminal voltage may also be controlled *automatically* by the addition of a series-field winding. This method has the advantage of being *automatic cheap, and generally satisfactory*.

1.4. Series Generator

The field winding of a series generator is connected in series with the armature winding as shown in Fig. 10. It consists of a few series of heavy wire, capable of carrying the output current of the machine without overheating. The characteristic curves of a D.C. series generator are drawn as given below :

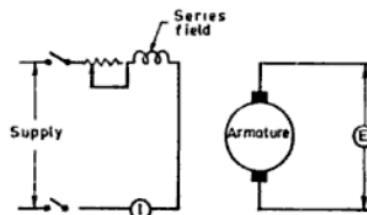


Fig. 10. Connection diagram for obtaining the saturation curve of a series generator.

- The *saturation curve (1)* may be obtained in a manner exactly similar to that already described for the shunt machine. The series-connected generator is illustrated in Fig. 10.

The series connected generator illustrated in Fig. 11 must be capable of safely carrying the maximum current to be used, or about 125 per cent of rated load current. A plot of simultaneous readings of generated voltage and field current, taken at a rated speed, yields the magnetisation curve 1 of Fig. 12.

- **External Characteristic (curve 2).** To obtain the data for this curve, the machine is connected to the load as shown in Fig. 11, ammeter and voltmeter being inserted to read the load current I ($= I_a$) and the terminal voltage V respectively. The machine is run at constant (rated) speed, a series of simultaneous readings of voltage and current is taken while the load is varied from a minimum value to perhaps 125 per cent of rated load. When these readings are plotted, using V as co-ordinate and I_a ($= I$) as abscissa curve 2 (see Fig. 12) is obtained.

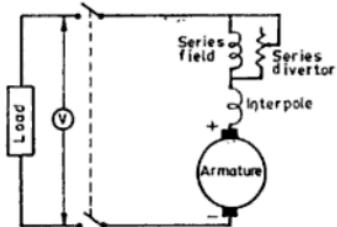


Fig. 11. Circuit for loading a series generator.

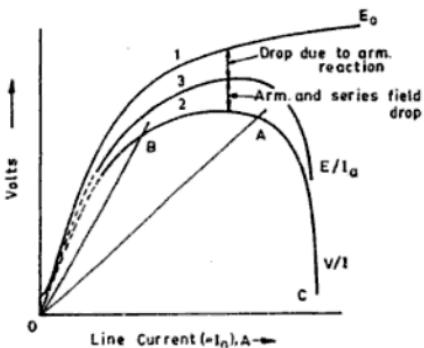


Fig. 12. Characteristic curves of a D.C. series generator.

It may be noted that the *readings cannot begin at zero load* as with the shunt generator, for if the resistance of the circuit including armature, series field and load is increased beyond a certain critical value, the generator unbuilds and loses its load entirely. Thus, if OA is the resistance line for the circuit the terminal voltage is the ordinate to the curve at A. When the resistance of the circuit is gradually increased, the load falls off along the curve, and A approaches B. When the resistance line finally becomes tangent to the curve, however, operation becomes unstable, and any slight further increase in the resistance causes the machine to unbuild its voltage and lose its load. The resistance that brings about this condition is called the *critical resistance*. Therefore, to begin with, the resistance of the circuit must be reduced below the critical value before the generator delivers any load.

- **Internal Characteristic (curve 3).** This curve is obtained by adding the resistance drop $I_a(R_a + R_{se})$ to the external characteristic curve ; R_a and R_{se} being armature resistance and series field resistance respectively. The difference between curves 1 and 3 is the *reduction in voltage caused by armature reaction*.
- It is worth noting that between A and C a considerable change in resistance brings about only a slight change in load current. Over this range the *voltage decreases rapidly*, owing to increasing armature reaction (particularly when the brushes are shifted forward), while the *current remains nearly constant*. Thus, between A and C the machine may be used to supply power to a *constant current variable-voltage circuit, such as series arc circuit*.

- Fig. 16 shows the load characteristic of differential compound generator.

When the differential compound generator is *without load* it builds up and self-excites its shunt field in much the same manner as the shunt generator. However, *when a load is applied, the generated voltage E_g is now reduced by the reduction in the main field flux created by the opposing m.m.f. of the series field.* This reduction in E_g occurs *in addition to the armature and series circuit voltage drop, the armature reaction, and the reduction in field current produced by reduction of the armature voltage.* The result is a sharp drop in the terminal voltage with load as shown in Fig. 16, and the field is below saturation and rapidly unbuilds.

- The differential compound generator is used as a constant-current generator for the same constant-current applications as the series generator.*

1.6. Applications of D.C. Generators

1. Separately Excited Generators :

(i) The separately excited generators are usually *more expensive than self-excited generators* as they require a *separate source of supply*. Consequently they are generally used where self-excited are relatively unsatisfactory. These are used in *Ward Leonard systems of speed control, because self-excitation would be unsuitable at lower voltages.*

(ii) These generators are also used where quick and requisite response to control is important (since separate excitation gives a quicker and more precise response to the changes in the resistance of the field circuit).

2. Shunt Generators :

(i) These generators are used to advantage, in conjunction with automatic regulators, as *exciters for supplying the current required to excite the fields of A.C. generators.* The regulator controls the voltage of the exciter by cutting in and out some of the resistance of the shunt-field rheostat, thereby holding the voltage at whatever value is demanded by operating conditions. This is one of the most important applications of shunt generators.

(ii) Shunt generators are used to *charge batteries.* In this application the voltage should drop off slightly as the load increases, because the voltage of a lead battery is lower when battery is discharged than when battery is charged. When it is discharged, however, the battery can stand a large charging current than when it is charged. *Because of its drooping characteristic the shunt generator is admirably suited to battery charging service,* for, in a general way, the voltage curve of the generator has the same shape as the voltage curve of the battery itself. In both cases, as the load falls the voltage rises.

- Shunt generators can be operated in parallel without difficulty, and the wiring of parallel-operated shunt machines is quite a bit simpler than the corresponding wiring for compound machines. When a slight drop in voltage is not objectionable, as when a motor load is fed directly from the generator terminals, shunt machines may be used to advantage.

3. Series Generators. The field of application of series generator is limited. These are used for the following purposes :

- (i) Series arc lighting.
- (ii) Series incandescent lighting.

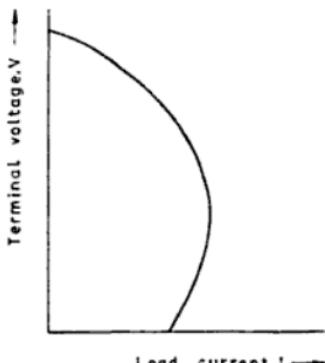


Fig. 16. Differential compound generator—load characteristic.

(iii) As a series booster for increasing the voltage across the feeder carrying current furnished by some other sources.

(iv) Special purposes such as supplying the field current for regenerative braking of D.C. locomotives.

4. Compound Generators.

The compound generator is used for more than any other type.
(i) It may be built and adjusted automatically to supply an approximately *constant voltage at the point of use.*, throughout the entire range of load. This is *very great advantage*. It is possible to provide a constant supply voltage at the end of a long feeder by the simple expedient of *overcompounding* the generator, because the resistance drop in the line is compensated for by the rising characteristic of the generator.

When the point of utilisation is near the generator, a flat-compounded machine may be used.

(ii) *Differentially compounded generator finds an useful application as an arc welding generator* where the generator is practically short circuited every time the electrode touches the metal plates to be welded.

(iii) Compound generators are used to supply power to :

- Railway circuits,
- Motors of electrified steam rail-roads,
- Industrial motors in many fields of industry,
- Incandescent lamps, and
- Elevator motors etc.

Worked Examples

Example 1. Draw armature drop line if armature resistance is 0.2Ω .

Solution. The procedure of drawing an armature drop line is as follows (see Fig. 17) :

(i) Take any value of armature current and find corresponding voltage in the armature resistance. For example, Take armature current of 200 A, voltage drop in the armature for this value of armature current is $200 \times 0.2 = 40$ V.

So a point (200, 40) lying on this line is obtained.

(ii) Join the above point with origin O, the armature drop or ohmic drop line is obtained.

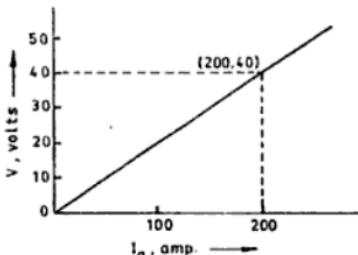


Fig. 17

Example 2. The open circuit characteristic (O.C.C.) of a separately excited generator, at 600 r.p.m., is as under :

Field Current, A	:	1.6	3.2	4.8	6.4	8.0	9.6	11.2
E.m.f., V	:	148	285	390	460	520	560	590

Find :

(i) The voltage to which the machine will excite as a shunt generator with a field circuit resistance of 60 ohm.

(ii) The critical resistance, at this speed.

Solution.

- Plot O.C.C. (E_f/I_f) as shown in Fig. 18.

- Line OL represents $60\ \Omega$ line.
- The voltage to which the machine will excite a shunt generator is given by point L' i.e. the intersection of O.C.C. and $60\ \Omega$ line. The machine will excite at 550 V .
- Draw line OM tangent to O.C.C. The slope of this line represents critical resistance. This value of critical resistance is $91\ \Omega$.

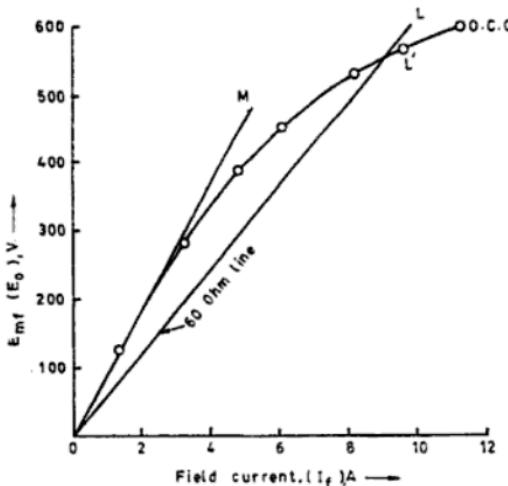


Fig. 18

Example 3. The open circuit characteristic of a 4-pole, 250 V shunt generator having 610 lap-connected armature conductors running at 750 r.p.m. is as follows :

Field current, A	:	0	0.5	1.0	2.0	3.0	4.0	5.0
E.m.f., V	:	10	50	100	175	220	245	262

Calculate :

(i) Field circuit critical resistance.

(ii) Critical speed for field circuit resistance of $80\ \Omega$.

(iii) Residual flux per pole.

Solution. Number of poles of the generator, $p = 4$

Number of parallel paths, $a = p = 4$ [Generator being lap connected]

Number of armature conductors, $Z = 610$

- Plot O.C.C. from the given data as shown in Fig. 19.
- Draw line OL tangent to O.C.C. at the origin. To determine the slope of the line OL , take any point M on this line and from M draw horizontal and vertical lines cutting O.C. voltage axis and field current axis at points S and T respectively.

(i) Critical resistance of field circuit = slope of line OL

$$= \frac{OS \text{ in volts}}{OT \text{ in amperes}} = \frac{200}{2} = 100 \text{ ohms. (Ans.)}$$

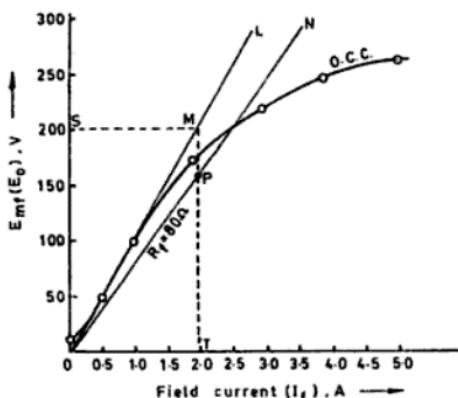


Fig. 19

(ii) Draw line *ON* representing resistance of 80 ohms. Let ordinate drawn from point *M* intersect line *ON* at *P*.

$$\text{Critical speed, } N_c = N \times \frac{TP}{TM} = 750 \times \frac{160}{200} = 600 \text{ r.p.m. (Ans.)}$$

(iii) Residual flux per pole, ϕ :

With no exciting current, the e.m.f. induced due to residual flux is 10 V At 750 r.p.m. (given).

Using the relation,

$$E_g = \frac{p\phiZN}{60a}$$

$$10 = \frac{4 \times \phi \times 610 \times 750}{60 \times 4}$$

$$\therefore \phi = \frac{10 \times 60 \times 4}{4 \times 610 \times 750} = 0.00131 \text{ Wb.}$$

Hence, residual flux/pole = 0.00131 Wb. (Ans.)

2. SPEED CONTROL OF D.C. MOTORS

2.1. Factors Controlling the Speed

D.C. machines are generally much more adaptable to adjustable speed service. The ready availability of D.C. motors to adjustment of their operating speed over wide ranges and by a variety of methods is one of the important reasons for the strong competitive position of D.C. machinery in modern industrial applications.

The speed of a D.C. motor can be expressed by the following relationship.

$$N \propto \frac{V - I_a R_a}{\phi}$$

Therefore, the speed of D.C. motor can be regulated by changing ϕ , R or V , or in other words, by,

1. Field control
2. Rheostatic control
3. Voltage control.

Note. Thyristor control of D.C. motor is dealt in Art. 5.

2.2. Field Control Method

- **Field control** is the most common method and forms one of the *outstanding advantages of shunt motors*. The method is, of course, also applicable to compound motors. Adjustment of field current and hence the flux and speed by adjustment of the shunt field circuit resistance or with a solid-state control when the field is *separately excited* is accomplished simply, inexpensively, and without much change in motor losses.

The speed is inversely proportional to the field current

i.e.

$$N \propto \frac{1}{I_f} \propto \frac{1}{\phi}$$

- The lowest speed obtainable is that corresponding to maximum field current ; the highest speed is limited electrically by the effects of armature reaction under weak-field conditions in causing motor instability and poor commutation.
- Since, voltage across the motor remains constant, it continues to deliver constant output. This characteristic makes this method suitable for fixed output loads. The performance curve of a D.C. motor with voltage and field control is shown in Fig. 20.

Merits. The merits of this method are :

1. Good working efficiency.
2. Compact controlling equipment.
3. Capability of minute speed control.
4. The speed is not effected by load, and speed control can be performed effectively even at light loads.
5. Relatively inexpensive and simple to accomplish, both manually and automatically.
6. Within limits, field control does not affect speed regulation in the cases of shunt, compound, and series motors.
7. Provides relatively smooth and stepless control of speed.

Demerits. The demerits of field control as a method of speed control are :

1. Inability to obtain speeds below the basic speed.
2. Instability at high speeds because of armature reaction.
3. Commutation difficulties and possible commutator damage at high speeds.

Shunt Motors :

- The flux of a D.C. shunt motor can be changed by changing shunt field current (I_{sh}) with the help of a shunt field rheostat as shown in Fig. 21. Since the field current is very small, the power wasted in the controlling resistance is very small.

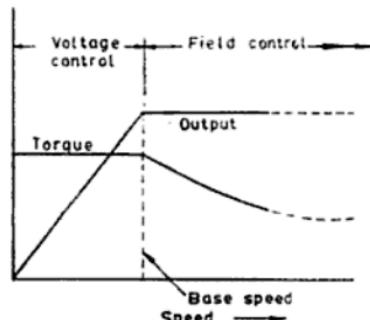


Fig. 20

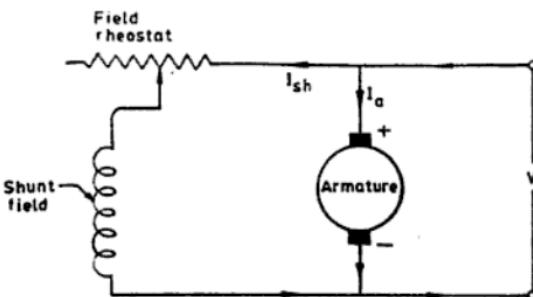


Fig. 21. Field rheostatic control for a D.C. shunt motor.

- In non-interpolar machines the speed can be increased by this method in the ratio 2 : 1. In machines fitted with interpoles a ratio of maximum to minimum speeds of 6 : 1 is fairly common.

Series Motors. In a series motor, variations of flux can be brought about in any one of the following ways :

- | | |
|----------------------------|---------------------------------|
| (i) Field divertors | (ii) Armature divertor |
| (iii) Tapped field control | (iv) Parallelizing field coils. |

(i) **Field divertors.** A variable resistance, known as field divertor (Fig. 22) shunts the series windings. Any desired amount of current can be passed through the divertor by adjusting its resistance. Hence, the flux can be decreased and consequently the speed of the motor increased.

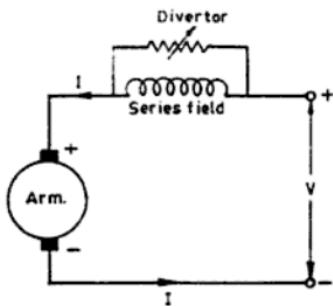


Fig. 22. Field divertor method of speed control for D.C. series motor.

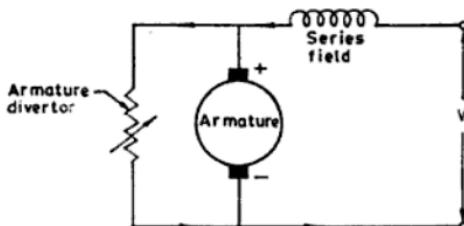


Fig. 23. Armature divertor method of speed control of D.C. series motor.

(ii) **Armature divertor.** In order to get speeds lower than the normal speed a divertor across the armature can be used (Fig. 23). For a given constant load torque, if I_a is reduced due to armature divertor, then ϕ must increase ($\because T_a \propto I_a$). This results in an increase in current taken from the supply which increases the flux and a fall in speed ($\because N \propto \frac{1}{\phi}$). The variations in speed can be controlled by varying the divertor resistance.

(iii) **Tapped field control.** In this method a number of tappings from the field winding are brought outside, as shown in Fig. 24. A number of series field turns can be short-circuited according to the requirement. When all field turns are in circuit, the motor runs at lowest speed and speed increases with cutting out some of the series field turns.

This method is often employed in electric traction.

(iv) **Paralleling field coils.** In this method of speed control several speeds can be obtained by regrouping the field coils as shown in Fig. 25 (a, b, c). This method is used for fan motors. It is seen that for a 4-pole motor, three fixed speeds can be obtained.

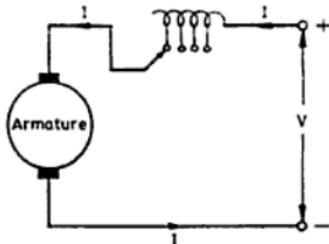


Fig. 24. Tapped field control for D.C. series motor.

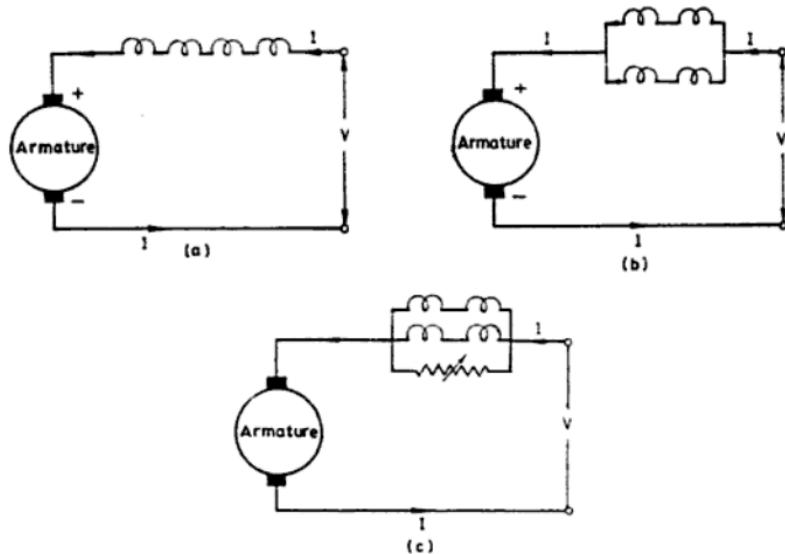


Fig. 25. Paralleling field coils method for speed control of D.C. series motor.

Example 4. A 220 V.D.C. shunt motor draws a no-load armature current of 2.5 A when running at 1400 r.p.m. Determine its speed when taking an armature current of 60 A, if armature reaction weakens the flux by 3 per cent.

Take armature resistance = 0.2 Ω .

Solution. Supply voltage,

$$V = 220 \text{ Volts}$$

No-load current,

$$I_{a0} = 2.5 \text{ A}$$

No-load speed,

$$N_0 = 1400 \text{ r.p.m.}$$

Armature resistance,

$$R_a = 0.2 \Omega$$

Armature current,

$$I_a = 60 \text{ A}$$

Full-load flux,

$$\phi = 0.97 \phi_0$$

Load speed N :

Back e.m.f. at no-load,

$$E_{b0} = V - I_{a0}R_a = 200 - 2.5 \times 0.2 = 219.5 \text{ V}$$

Back e.m.f. on load,

$$E_b = V - I_a R_a = 220 - 60 \times 0.2 = 208 \text{ V.}$$

Now using the relation,

$$\frac{N}{N_0} = \frac{E_b}{E_{b0}} \times \frac{\phi_0}{\phi}$$

$$\frac{N}{1400} = \frac{208}{219.5} \times \frac{\phi_0}{0.97\phi_0}$$

$$\therefore N = \frac{1400 \times 208}{219.5 \times 0.97} = 1367.7 \text{ r.p.m.}$$

Hence,

load speed = 1367.7 r.p.m. (Ans.)

Example 5. The armature and shunt field resistances of a 500 V shunt motor are 0.2Ω and 100Ω respectively. Find the resistance of the shunt field regulator to increase the speed from 800 r.p.m. to 1000 r.p.m., if the current taken by the motor is 450 A. The magnetisation characteristic may be assumed as a straight line.

Solution. Supply voltage,

$$V = 500 \text{ Volts}$$

Armature resistance,

$$R_a = 0.2 \Omega$$

Shunt field resistance,

$$R_{sh} = 100 \Omega$$

Initial speed,

$$N_1 = 800 \text{ r.p.m.}$$

Final speed,

$$N_2 = 1000 \text{ r.p.m.}$$

Current drawn by the motor,

$$I = 450 \text{ A}$$

Resistance of shunt field regulator, R :

Since the magnetization characteristic is a straight line,

$$\phi \propto I_{sh}$$

Also,

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$

∴

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{I_{sh1}}{I_{sh2}}.$$

At 800 r.p.m.

$$I_{sh1} = \frac{V}{R_{sh}} = \frac{500}{100} = 5 \text{ A}$$

Armature current,

$$I_{a1} = I - I_{sh1} = 450 - 5 = 445 \text{ A}$$

Back e.m.f.

$$E_{b1} = V - I_{a1}R_a = 500 - 445 \times 0.2 = 411 \text{ V}$$

At 1000 r.p.m.

Armature current,

$$I_{a2} = I - I_{sh2} = 450 - I_{sh2}$$

Back e.m.f.,

$$E_{b2} = V - I_{a2}R_a = 500 - (450 - I_{sh2}) \times 0.2 = 410 + 0.2I_{sh2}$$

Now

$$\frac{1000}{800} = \frac{(410 + 0.2I_{sh2})}{411} \times \frac{5}{I_{sh2}}$$

$$410 + 0.2I_{sh2} = \frac{1000}{800} \times \frac{411}{5} I_{sh2} = 102.75I_{sh2}$$

or

$$102.55I_{sh2} = 410$$

∴

$$I_{sh2} = 4 \text{ A app.}$$

Using the relation, $\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$

$$\frac{N_2}{600} = \frac{426.54}{430} \times \frac{100}{81.64}$$

$$\therefore N_2 = 729 \text{ r.p.m.}$$

Hence, speed of the motor = 729 r.p.m. (Ans.)

Ex7 A D.C. series motor drives a load the torque of which varies as square of the speed. The motor takes a current of 20 A when the speed is 800 r.p.m. Calculate the speed and current when the motor field winding is shunted by a divisor of the same resistance as that of the field winding.

Neglect all motor losses and assume that the magnetic circuit is unsaturated.

Solution. $I_{a1} = 20 \text{ A}$, $N_1 = 800 \text{ r.p.m.}$

$$I_{a2} = ?, N_2 = ?$$

When the field winding is shunted by a divisor of equal resistance, then current through either is half the armature current. If I_{a2} is the new armature current, then $\frac{I_{a2}}{2}$ passes through the winding (Fig. 27).

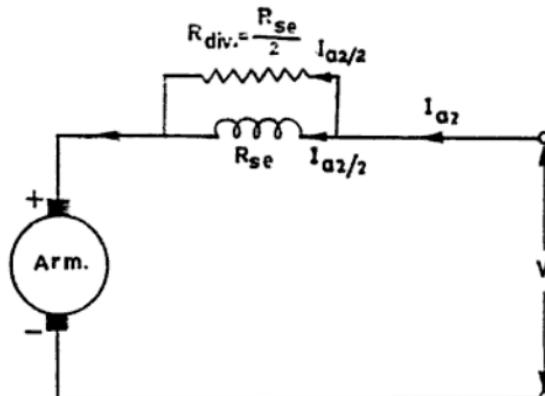


Fig. 27

$$\therefore \phi_2 = \frac{I_{a2}}{2}$$

$$\text{Now } T_1 \propto \phi_1 I_{a1} \propto N_1^2 \quad (\text{Given})$$

$$\text{and } T_2 \propto \phi_2 I_{a2} \propto N_2^2 \quad (\text{Given})$$

From (i) and (ii), we get

$$\left(\frac{N_2}{N_1} \right)^2 = \frac{\phi_2 I_{a2}}{\phi_1 I_{a1}} \quad \dots(i)$$

Because all losses are negligible, hence the armature and series field resistances are negligible. This means that back e.m.f. in both cases is the same as the applied voltage.

$$\therefore \frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2} \text{ becomes}$$

$$\frac{N_2}{N_1} = \frac{\phi_1}{\phi_2}$$

...(ii)

[$\because E_{b2} = E_{b1}$ = applied voltage]

Putting this value in (i) above, we get

$$\left(\frac{\phi_1}{\phi_2} \right)^2 = \frac{\phi_2 I_{a2}}{\phi_1 I_{a1}}$$

or

$$\frac{I_{a2}}{I_{a1}} = \left(\frac{\phi_1}{\phi_2} \right)^3$$

$$\frac{I_{a2}}{20} = \left(\frac{20}{I_{a2}/2} \right)^3$$

[$\because \phi_2 \propto I_a/2$]

$$\therefore I_{a2}^4 = 20 \times 40^3$$

or

$$I_{a2} = 33.63 \text{ A}$$

Hence, current = 33.63 A. (Ans.)

$$\text{From (ii), we get } \frac{N_2}{800} = \frac{20}{(33.63)/2}$$

$$N_2 = 800 \times \frac{40}{33.63} = 951.52 \text{ r.p.m.}$$

Hence, speed of the motor = 951.53 r.p.m. (Ans.)

2.3. Rheostatic Control

- This method consists of obtaining reduced speeds by the insertion of external series resistance in the armature circuit. It can be used with series, shunt and compound motors ; for the last two types, the *series resistor must be connected between the shunt field and the armature, not between line and the motor.*
- It is *common method of speed control for series motors* and is generally analogous in action to wound-rotor induction-motor control by series rotor resistance.
- *This method is used when speeds below the no-load speed is required.*

Advantages :

1. The ability to achieve speeds below the basic speed.
2. Simplicity and ease of connection.
3. The possibility of combining the functions of motor starting with speed control.

Disadvantages :

1. The relatively high cost of large, continuously rated, variable resistors capable of dissipating large amounts of power (particularly at higher power ratings).
2. Poor speed regulation for any given no-load speed setting.
3. Low efficiency resulting in high operating cost.
4. Difficulty in obtaining stepless control of speed in higher power ratings.

Shunt motors :

- In armature or rheostatic control method of speed the voltage across the armature (which is normally constant) is varied by inserting a variable rheostat or resistance, called *controller resistance*, in *series* with the armature circuit. As the controller resistance is

increased, the potential difference across the armature is decreased thereby decreasing the armature speed. For a load of constant torque, speed is approximately proportional to the potential difference across the armature.

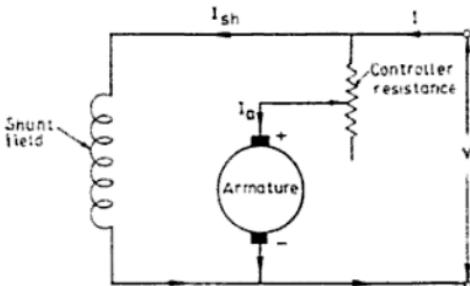


Fig. 28. Armature resistance control for D.C. shunt motor.

From the speed/armature current characteristic it is seen that *greater the resistance in armature, greater is the fall in speed*.

There is a particular load current for which the speed would be zero. This is the maximum current and is known as 'stalling current'.

- This method is very wasteful, expensive and unsuitable for rapidly changing load, because for a given value of R_a , the speed will change with load. A more stable operation can be obtained by using a *divertor across the armature* (Fig. 30) in addition to armature control resistance. Now, the changes in armature current due to changes in the load torque will not be so effective in changing the potential difference across the armature and hence the speed of the armature.

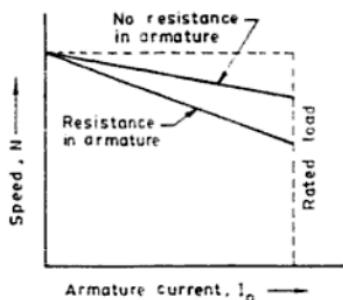


Fig. 29. Speed-current characteristic of D.C. shunt motor.

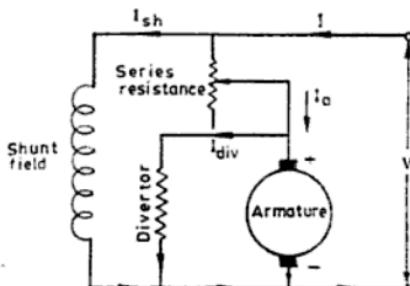


Fig. 30. Use of divertor across the armature for speed control of D.C. shunt motor.

Series motors. Armature resistance control is the most common method employed for D.C. series motors (Figs. 31 and 32)

By increasing the resistance in series with the armature the voltage applied across the armature terminals can be decreased. With the reduced voltage across the armature, the speed is reduced.

Since full motor current passes through the resistance, the loss of power is considerable.

Current through each motor $= I$

$$\text{Speed} \propto \frac{\text{voltage}}{\text{current}} \propto \frac{V/2}{I} \propto \frac{V}{2I}$$

$$\text{Torque} \propto \phi I \propto I^2 \quad [\text{Since } \phi \propto I, \text{ assuming unsaturated field}]$$

- At high speeds the motors are joined in parallel as shown in Fig. 33 (b). The variable resistance R is gradually cut out as motors attain the speed. After the resistance R is completely cut out each motor is connected across the full line voltage.

When the motors are connected in parallel and resistance R is completely cut out :

Voltage across each motor $= V$

$$\text{Current through each motor} = \frac{I}{2} \quad \left[= \frac{I'}{2} \text{ when resistance } R \text{ is not completely cut out} \right]$$

$$\text{Speed} \propto \frac{\text{voltage}}{\text{current}} \propto \frac{V}{I/2} \propto \frac{2V}{I}$$

Also,

$$\text{torque} \propto \phi I \propto I^2$$

$$[\because \phi \propto I]$$

$$\therefore T \propto \left(\frac{I}{2} \right)^2 \propto \frac{I^2}{4}$$

The torque is $\frac{1}{4}$ times that produced by motors when in series.

Example 8. The armature and shunt field resistances of a 230 V shunt motor are 0.1 ohm and 230 ohms respectively. It takes a current of 61 A at 1000 r.p.m. If the current taken remains unaltered find the resistance to be included in series with the armature circuit to reduce the speed to 750 r.p.m.

Solution. Supply voltage,

$$V = 230 \text{ Volts}$$

Armature resistance,

$$R_a = 0.1 \text{ ohm}$$

Shunt field resistance,

$$R_{sh} = 230 \text{ ohms}$$

Load current,

$$I = 61 \text{ A}$$

Speed, $N_1 = 1000 \text{ r.p.m.}$

Speed, $N_2 = 750 \text{ r.p.m.}$

Additional resistance required, R :

Shunt field current,

$$I_{sh} = \frac{V}{R_{sh}} = \frac{230}{230} = 1 \text{ A}$$

Armature current,

$$I_1 = I - I_{sh} = 61 - 1 = 60 \text{ A}$$

Using the relation,

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2} \quad \dots(i)$$

Since flux remains constant in shunt motor

$$\phi_1 = \phi_2$$

Also it is given that the current taken by the motor remains constant

\therefore

$$I = I_1 = I_2 = 61 \text{ A}$$

and

$$I_{a1} = I_{a2} = 60 \text{ A}$$

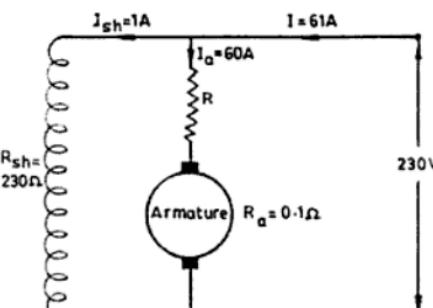


Fig. 34

Thus eqn. (i) reduces to

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

$$E_{b1} = V - I_{a1}R_a = 230 - 60 \times 0.1 = 224 \text{ V}$$

$$E_{b2} = V - I_{a2}(R_a + R)$$

$$= 230 - 60(0.1 + R) = 230 - 6 - 60R$$

$$= 224 - 60R$$
...(ii)

Putting this value in (ii), we get

$$\frac{750}{1000} = \frac{224 - 60R}{224}$$

or

$$60R = 224 - \frac{750}{1000} \times 224$$

$$R = 0.933 \text{ ohm}$$

Hence, additional resistance required = 0.933 ohm. (Ans.)

Example 9. The armature resistance of a 230 V D.C. shunt motor is 0.2 ohm. It takes 15 A at rated voltage and runs at 800 r.p.m. Calculate the value of additional resistance required in the armature circuit to reduce the speed to 600 r.p.m. when the load torque is independent of speed.

Ignore the field current.

Solution. Supply voltage,	V = 230 Volts
Armature resistance,	$R_a = 0.2 \text{ ohm}$
Armature current,	$I_1 = I_{a1} = 15 \text{ A}$
Speed,	$N_1 = 800 \text{ r.p.m.}$
Speed,	$N_2 = 600 \text{ r.p.m.}$

Additional resistance required, R :

$$\text{Back e.m.f.}, \quad E_{b1} = V - I_{a1}R_a = 230 - 15 \times 0.2 = 227 \text{ V}$$

Since as per given data load torque is independent of speed and flux is constant

$$I_{a1} = I_{a2} = 15 \text{ A}$$

$$\phi_1 = \phi_2$$

$$\text{Back e.m.f.}, \quad E_{b2} = V - I_{a2}(R_a + R) = 230 - 15(0.2 + R)$$

$$= 230 - 3 - 15R = 227 - 15R$$

$$\text{Using the relation, } \frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$

$$\frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}}$$

[∴ $\phi_1 = \phi_2$]

$$\therefore \frac{600}{800} = \frac{227 - 15R}{227}$$

$$15R = 227 - \frac{600}{800} \times 227$$

$$R = 3.783 \text{ ohms}$$

Hence, additional resistance required = 3.783 ohms. (Ans.)

2.4. Voltage Control

When the speed is controlled by regulating the motor terminal voltage while maintaining constant field current, it is called voltage control.

With voltage control, the change in speed is almost proportional to the change in voltage as shown in Fig. 1. The output varies directly with speed and the torque remains constant. Since the

voltage has to be regulated without affecting the field, the application of voltage control is limited to *separately excited motors* (Fig. 35) only.

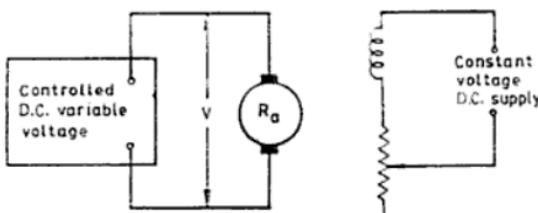


Fig. 35. Voltage control method.

- For D.C. motors of *fractional and relatively low power rating*, the variable D.C. voltage source may be a D.C. vacuum tube, a gas or thyratron tube, or a semi-conductor (silicon controlled rectifier) amplifier, operating from a three-phase or single phase A.C. supply.
- *Motors of moderate rating up to 75 kW* may be controlled by this method using Rototrol or Regulex or magnetic amplifiers as the adjustable D.C. voltage source.
- *Large D.C. motors* are controlled in this manner by means of rotary amplifiers such as the ampidyne or the Ward-Leonard control system.

Advantages :

1. Speed control over a wide range is possible.
2. This method eliminates the need for series armature starting resistance.
3. Uniform acceleration can be obtained.
4. Speed regulation is good.

Disadvantages :

1. Arrangement is costly as two extra machines are required.
2. The overall efficiency of the system is low, especially at light loads.

Applications :

Inspite of the high capital cost, this method finds wide applications in :

- (i) Steel mills for reversing the rolling mills.
- (ii) Seamless tube mills and shears.
- (iii) High and medium speed elevators in tall buildings, mine hoists, paper machine drives and electric shovels.

Ward-Leonard System. This method of control not only gives a wide range of operating speeds, but reduces to the very minimum the wastage of energy that may take place at starting and stopping.

Fig. 36 shows the schematic arrangement of Ward-Leonard method.

M = main motor whose speed is to be controlled

G = separately excited generator which feeds the armature of the motor *M*

E = an exciter (a small shunt generator) which provides field excitation to the generator *G* and motor *M*

M' = driving motor—a constant speed motor which drives *G* and *E*.

[If the system is to work on A.C. supply, the driving motor *M'* is a 3-phase induction motor. If the system is to work on D.C. supply, the motor *M'* is a shunt motor. In the latter case the exciter *E*

5. Larger units employing generator field reversal eliminate the need for heavy armature conductors for reversing, and at the same time prevent motor runaway since the motor field is always excited.

6. The method lends itself to adaptation of intermediate electronic, semi-conductor, and magnetic amplifiers to provide stages of amplification for an extremely large motor. Thus the power in the control circuit may be extremely small.

7. Extremely good speed regulation at any speed.

Disadvantages :

1. High initial cost.

2. Since the efficiency, neglecting the exciter efficiency, is essentially the product of the individual efficiencies of the two larger machines, the efficiency of this method is *not as high as rheostat speed control or the field control method*.

Example 10. A series motor drives a fan for which the torque varies as square of the speed. Its resistance between terminals is 1.2 ohm. On 220 V, it runs at 350 r.p.m. and takes 30 A. The speed is to be raised to 450 r.p.m. by increasing the voltage. Find the voltage.

Assume that flux varies directly as current.

Solution. Resistance between terminals = 1.2 ohm

$$I_{a1} = 30 \text{ A}, N_1 = 350 \text{ r.p.m.}, N_2 = 450 \text{ r.p.m.}$$

Since $\phi \propto I_a$

$$\therefore T \propto \phi I_a \propto I_a^2 \quad \dots(i)$$

$$\text{Also, } T \propto N^2 \quad \dots[\text{Given}] \quad \dots(ii)$$

$$\text{From (i) and (ii), we get } I_a^2 \propto N^2 \quad \text{or} \quad I_a \propto N$$

$$\text{or} \quad \frac{I_{a2}}{I_{a1}} = \frac{N_2}{N_1} = \frac{450}{350}$$

$$\therefore I_{a2} = I_{a1} \times \frac{450}{350} = 30 \times \frac{450}{350} = 38.57 \text{ A}$$

$$\text{Back e.m.f., } E_{b1} = 220 - 30 \times 1.2 = 184 \text{ V}$$

$$\text{Back e.m.f., } E_{b2} = V - 38.57 \times 1.2 = V - 46.28$$

$$\frac{\phi_1}{\phi_2} = \frac{I_{a1}}{I_{a2}} = \frac{30}{38.57}$$

$$\text{Now using the relation, } \frac{N_2}{N_1} = \frac{E_{b2}}{E_{b1}} \times \frac{\phi_1}{\phi_2}$$

$$\frac{450}{350} = \frac{V - 46.28}{184} \times \frac{30}{38.57}$$

$$\therefore V - 46.28 = \frac{450}{350} \times 184 \times \frac{38.57}{30} = 304.15$$

$$\therefore V = 304.15 \text{ Volts. (Ans.)}$$

3. ELECTROMECHANICAL ENERGY CONVERSION

3.1. Introduction

- The main advantage of electric energy over other forms of energy is that it can be transmitted over long distances with ease and high efficiency. Its main use is in the form of a transmitting link for transporting other forms of energy, e.g., mechanical, sound, light etc. from one physical location to another.

- An electromechanical energy conversion device is one which converts electrical energy into mechanical energy and mechanical energy into electrical energy. Electromechanical energy conversion takes place via the medium of a magnetic or electric field the magnetic field being most suited for practical conversion devices. The conversion process is basically a reversible one though practical devices may be designed and constructed to particularly suit one mode of conversion or other.
 - From the view-point of magnitudes of energy involved rotating or linear electrical machines are the most important energy converters. These are primarily used for bulk energy conversion and utilisation.

Examples : Motors and generator (continuous energy-conversion equipment).

- A second category includes devices for measurement and control, frequently referred to as transducers. These generally operate under linear-output conditions and with relatively small signals.

Examples : Microphones, pictures, sensors, and loudspeakers.

- A third category of devices encompasses force-producing devices.

Examples : Solenoids, relays and electromagnets.

3.2. Principle of Energy Conversion

For converting energy from one form to another the principle of conservation of energy (which states that energy can neither be created nor destroyed, it can merely be converted from one form to another) can be invoked. In an energy conversion device, out of the total input energy, a larger part of the energy is converted into useful output energy, some energy is stored and rest is converted to heat (called energy loss). Thus energy balance, which should include the above terms, can be written for a motor and a generator as follows :

Motor (action) :

$$\left[\begin{array}{l} \text{Total electrical} \\ \text{energy input} \end{array} \right] = \left[\begin{array}{l} \text{Mechanical energy} \\ \text{output} \end{array} \right] + \left[\begin{array}{l} \text{Total energy stored} \\ \text{(in magnetic field)} \end{array} \right] + \left[\begin{array}{l} \text{Energy converted} \\ \text{into heat} \end{array} \right] \quad \dots(2)$$

Eqn. (2) is written so that the electrical and mechanical energy terms have positive values for motor action. The equation applies well to generator action ; these terms then simply have negative values.

Generator (action) :


$$\left[\begin{array}{l} \text{Total mechanical} \\ \text{energy input} \end{array} \right] = \left[\begin{array}{l} \text{Electrical energy} \\ \text{output} \end{array} \right] + \left[\begin{array}{l} \text{Total energy stored} \\ \text{(in magnetic field)} \end{array} \right] + \left[\begin{array}{l} \text{Energy converted} \\ \text{into heat} \end{array} \right] \quad \dots(3)$$

In the above cases, the sign of the heat generation term(s) is such that heat generation within the system results in a flow of thermal energy out of the system. In the systems, to be considered here, the conversion of energy into heat occurs by such mechanisms as ohmic heating due to current flow in the windings of the electric terminals and mechanical friction due to the motion of the system components forming the mechanical terminals.

Thus, energy balance equation may be written as :

$$\int dW_{\text{input}} = \int dW_{\text{output}} + \int dW_{\text{magnetic field}} + \int dW_{\text{heat}} \quad \dots(4)$$

Fig. 37 shows the flow of energy in electromechanical energy conversion via a coupling field.

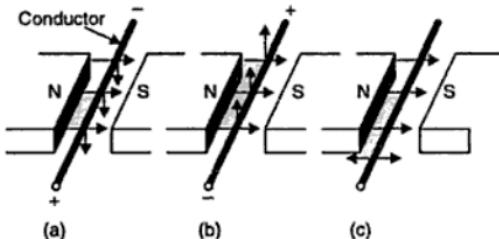

(a) Voltage induced across a wire moving downward.

(b) Voltage induced across a wire moving upward.

(c) No voltage is induced in a wire moving parallel to the field.

Fig. 38. When a conductor is moved across a magnetic field a voltage is induced in the conductor.

[Usually, a minus sign is given to the right-hand side expression to signify the fact that the induced e.m.f. sets up current in such a direction that magnetic effect produced by it opposes the very cause producing it.]

Induced e.m.f. :

Induced e.m.f. may be of the following two types :

1. Dynamically induced e.m.f.
2. Statically induced e.m.f.

Dynamically Induced e.m.f. :

Refer Fig. 2. The e.m.f. induced (e) in the conductor is given by :

$$e = Blv \text{ volt} \quad \dots(6)$$

where, B = flux density of the magnetic field in tesla,

l = length of the conductor in metres, and

v = velocity of the conductor in m/s.

If the conductor moves at an angle θ with the direction of flux then the induced e.m.f.

$$e = Blv \sin \theta \text{ volts} \quad \dots(7)$$

The direction of the induced e.m.f. is given by *Fleming's Right hand rule*.

Statically Induced e.m.f. :

The e.m.f. induced by variation of flux is termed as "statically induced e.m.f."


Statically induced e.m.f. can be further subdivided as follows :

- (i) Self-induced e.m.f.
- (ii) Mutually induced e.m.f.


3.4. Singly and Multiply-excited Magnetic Field Systems

Let us consider energy-conversion systems in which magnetic circuits have air-gaps between the stationary and moving members ; a considerable energy is stored in the magnetic field. This field acts as the energy-conversion medium and its energy is the reservoir between the electric and mechanical systems.

(a) Singly-excited magnetic field system

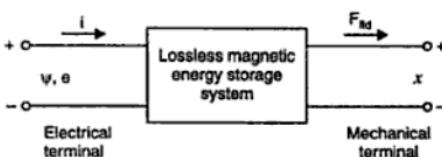

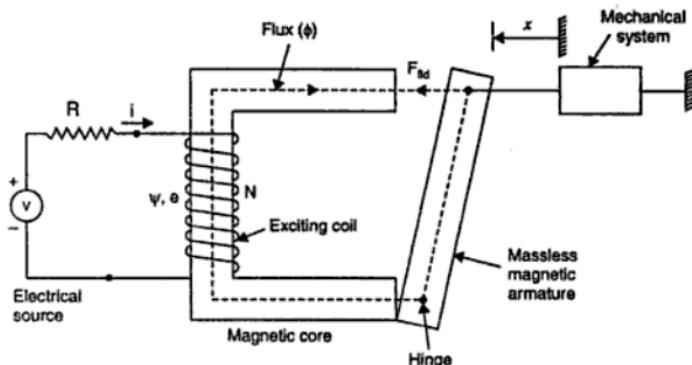(a) Schematic magneto-field electromechanical-energy conversion device.



(b) Simple force-producing device-attracted armature relay.

Fig. 39. Singly-excited magnetic field system.

Fig. 39 shows a singly-excited magnetic field system. A mechanical force F_{fd} acts on the armature of the relay [Fig. 39 (b)] which is connected to a mechanical system comprising an active and/or passive element.

Assumptions made :

- No loss of energy in the magnetic core.
- The whole of flux created by the core is confined to it.
- The resistance of the exciting coil is represented outside in a lumped fashion.

Let us assume that the armature moves a differential distance dx in the direction of F_{fd} . Then, as per the law of conservation of energy, the energy balance equation may be written as :

$$\text{Electrical energy input} = \text{mechanical energy output} + \text{increase in field energy.}$$

$$\text{or } id\psi = F_{fd} \cdot dx + dW_{fd} \quad \dots [8(a)] \quad (\text{fld stands for field})$$

$$\text{[where } \psi = \text{flux linkages} = N\phi, N \text{ being number of terms of the exciting coil.]}$$

$$\text{or } F_{fd} \cdot dx = i \cdot d\psi - dW_{fd} \quad \dots [8(b)]$$

Neglecting iron reluctance, for a linear case the inductance of the coil is a function $L(x)$ of linear distance of the armature.

$$\therefore dW_{fd} = \frac{1}{2} dL(x) i^2$$

$$\text{and } d\psi = i \times dL(x)$$

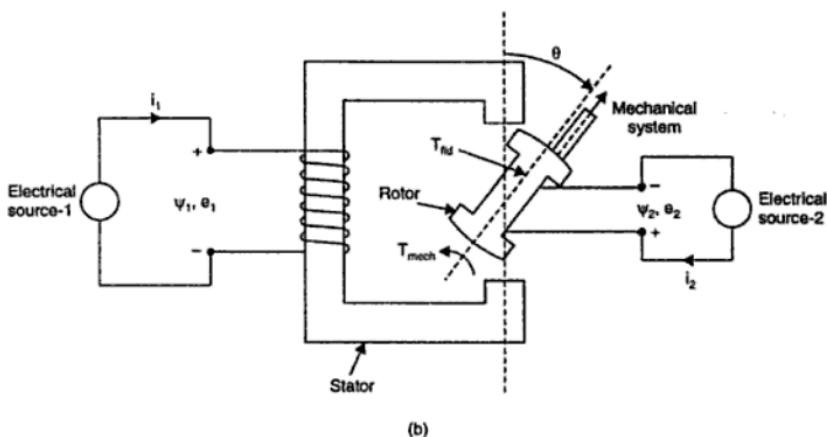


Fig. 40. Multiply-excited magnetic system.

Fig. 40 shows a magnetic field system with two electrical excitations, one on stator and other on rotor.

When the fluxes are used, the differential energy function $dW_{fld}(\psi_1, \psi_2, \theta)$ is given as :

$$dW_{fld}(\psi_1, \psi_2, \theta) = i_1 \cdot d\psi_1 + i_2 d\psi_2 - T_{fld} d\theta \quad \dots(14)$$

Also,

$$i_1 = \frac{\partial W_{fld}(\psi_1, \psi_2, \theta)}{\partial \psi_1} \Bigg|_{\psi_2, \theta} \quad \dots(15)$$

$$i_2 = \frac{\partial W_{fld}(\psi_1, \psi_2, \theta)}{\partial \psi_2} \Bigg|_{\psi_1, \theta} \quad \dots(16)$$

and

$$T_{fld} = - \frac{\partial W_{fld}(\psi_1, \psi_2, \theta)}{\partial \theta} \Bigg|_{\psi_1, \psi_2} \quad \dots(17)$$

3.5. Torque Production in Rotating Machines

Refer Fig. 41. When currents flow in stator and rotor windings of a machine, these windings produce their own magnetic fields along their respective axes which are sinusoidally distributed along the air gap. These fields tend to align themselves, which results in the production of a torque. This torque is produced only if the two fields have the same number of poles and are stationary with respect to each other. The flux components set up by the stator and rotor currents cross the air-gap twice and complete their circuits via the stator and rotor iron ; these component fields cause the appearance of north (*N*) and south (*S*) poles on stator and rotor surfaces ; the field axes being along *N*—*S* and out of *N*-pole. As the two relatively rotating fields cross each other, they will produce alternating torque so that the average torque is zero. Therefore, all the varieties of electrical machines viz. Induction, synchronous, D.C. are devised to produce interacting fields with zero relative velocity.

Assumptions made :

- Rotor is cylindrical (non-salient pole) so that air-gap is uniform throughout.
- Stator and rotor mmfs are sinusoidal space waves.

Also,

$$W_{\text{fd}} = i\psi - W'_{\text{fd}}(i, x)$$

(where $\psi = N\phi$ and W'_{fd} = co-energy)

Then

$$\begin{aligned} dW_{\text{fd}} &= d(i\psi) - dW'_{\text{fd}}(i, x) \\ &= id\psi + \psi di - \left[\frac{\partial W'_{\text{fd}}}{\partial i} di + \frac{\partial W'_{\text{fd}}}{\partial x} dx \right] \end{aligned} \quad \dots(22)$$

Substituting for dW_{fd} from eqn. (22) in eqn. (21), we get

$$F_{\text{fd}} \cdot dx = id\psi - \left[i.d\psi + \psi.di - \left(\frac{\partial W'_{\text{fd}}}{\partial i} di + \frac{\partial W'_{\text{fd}}}{\partial x} dx \right) \right]$$

or $F_{\text{fd}} \cdot dx = i.d\psi - i.d\psi - \psi.di + \frac{\partial W'_{\text{fd}}}{\partial i} di + \frac{\partial W'_{\text{fd}}}{\partial x} dx$

or $F_{\text{fd}} \cdot dx = \left(\frac{\partial W'_{\text{fd}}}{\partial i} - \psi \right) di + \frac{\partial W'_{\text{fd}}}{\partial x} dx \quad \dots(23)$

Since the incremental changes di and dx are independent and di is not present on L.H.S. of eqn. (23), therefore, its coefficient of R.H.S. must be zero.

$$\therefore \frac{\partial W'_{\text{fd}}}{\partial i} - \psi = 0$$

or $\psi = \frac{\partial W'_{\text{fd}}}{\partial i}(i, x)$

Thus, from eqn. (23), we have

$$F_{\text{fd}} = \frac{\partial W'_{\text{fd}}(i, x)}{\partial x} \quad \dots(24)$$

This expression (for mechanical force developed) applies when i is an independent variable i.e., it is a *current excited system*.

Worked Examples

Example 11. Fig. 42 shows a relay made from infinitely-permeable magnetic material with a movable plunger, also of infinite-permeable material. The height of the plunger is much greater than the air-gap length ($h \gg l_g$).

Calculate the magnetic stored energy W_{fd} as a function of plunger position ($0 < x < d$) for $N = 1200$ turns, $l_g = 1.8 \text{ mm}$, $d = 0.12 \text{ m}$, $l = 0.08 \text{ m}$ and $i = 12 \text{ A}$.

Solution. Given : $N = 1200$ turns ; $l_g = 1.8 \text{ mm}$; $d = 0.12 \text{ m}$; $l = 0.08 \text{ m}$; $i = 12 \text{ A}$.

Magnetic stored energy W_{fd} :

We know that, magnetic stored energy,

$$W_{\text{fd}} = \frac{1}{2} L(x)i^2 \quad \dots(i)$$

where L is the inductance.


Now, $L(x) = \frac{\mu_0 N^2 A_g}{2l_g}$

where, $\mu_0 = \text{absolute permeability} = 4\pi \times 10^{-7} \text{ H/m}$;

$N = \text{number of turns}$;

$A_g = \text{gap cross-sectional area}$, and

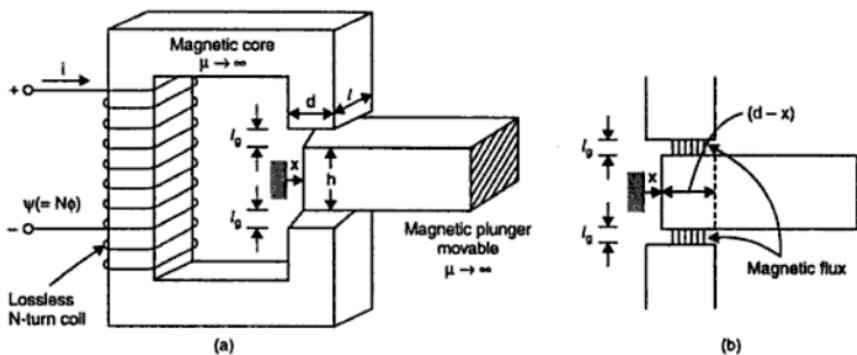$l_g = \text{length of air gap each, above and below the plunger}$.



(a) Relay with movable plunger.

(b) Detail showing air-gap configuration with the plunger partially removed.

Here

$$A_g = l(d - x) = ld \left(1 - \frac{x}{d}\right)$$

Thus

$$L(x) = \frac{\mu_0 N^2 ld \left(1 - \frac{x}{d}\right)}{2l_g}$$

Substituting in Eqn. (i), we have

$$\begin{aligned} W_{fd} &= \frac{1}{2} \left[\frac{\mu_0 N^2 ld \left(1 - \frac{x}{d}\right)}{2l_g} \right] i^2 \\ &= \frac{1}{2} \left[\frac{(4\pi \times 10^{-7})(1200)^2 (0.08)(0.12) \left(1 - \frac{x}{d}\right)}{2(1.8 \times 10^{-3})} \right] \times 12^2 \end{aligned}$$

or

$$W_{fd} = 347.4 \left(1 - \frac{x}{d}\right) \text{ J. (Ans.)}$$

Example 12. Fig. 43 shows the magnetic circuit consisting of a single-coil stator and an oval rotor. The coil inductance varies with rotor angular position, measured between the magnetic axis of the stator coil and major axis of rotor, as

$$L(\theta) = L_0 + L_2 \cos(2\theta)$$

where

$$L_0 = 11.66 \text{ mH and } L_2 = 2.97 \text{ mH.}$$

Find the torque as a function of θ for a coil current of 2.2 A.**Solution.** Given : $L(\theta) = L_0 + L_2 \cos(2\theta)$

$$L_0 = 11.66 \text{ mH ; } L_2 = 2.97 \text{ mH ;}$$

$$i = 2.2 \text{ A}$$

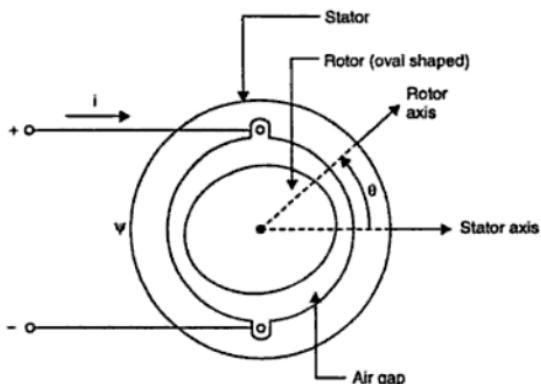


Fig. 43

We know that, $T_{fd}(\theta) = \frac{1}{2} i^2 \frac{dL(\theta)}{d\theta}$

$$= \frac{i^2}{2} \frac{d}{d\theta} [L_0 + L_2 \cos(2\theta)]$$

$$= \frac{i^2}{2} [-2L_2 \sin(2\theta)]$$

$$= -\frac{(2.2)^2}{2} [-2 \times (2.97 \times 10^{-3}) \sin(2\theta)] \text{ Nm}$$

or

$$T_{fd}(\theta) = -0.0144 \sin(2\theta) \text{ Nm. (Ans.)}$$

It may be noted that, in this case the torque acts in such a direction as to pull the rotor axis in alignment with the coil axis and hence to maximise the coil inductance.

Example 13. The following data relate to the electromagnetic relay shown in Fig. 39.

Number of terms, $N = 1200$

Cross-sectional area of the core, $A_{core} = 2.7 \text{ cm} \times 2.7 \text{ cm}$.

Permeability of the core = infinite

Neglecting fringing effects, find the following :

(i) The inductance of coil for an air gap length (l_g) of 0.45 cm. The energy stored in the field and force acting on the armature when the coil carries a current of 2.25 A.

(ii) The mechanical energy output when the air gap is decreased from 0.45 cm to 0.225 cm, assuming that the current through the coil remains constant at 2.25 A.

(iii) The expression for force on armature as a function of l_g , coil current being constant at 2.25 A. Also calculate the work done by the magnetic field when l_g changes from 0.45 cm to 0.225 cm from the expression $\int F_{fd} dl_g$ and thereby verify the result of part (ii).

Solution. Refer Fig. 39.

(i) L ; W_{fld} ; F_{fld} :

$$L = \frac{\mu_0 N^2 A_{\text{core}}}{l_g} = \frac{(4\pi \times 10^{-7}) \times (1200)^2 \times (2.7 \times 2.7 \times 10^{-4})}{(0.45 \times 10^{-2})} = 0.293 \text{ H. (Ans.)}$$

$$W_{\text{fld}} = \frac{1}{2} Li^2 = \frac{1}{2} \times 0.293 \times (2.25)^2 = 0.742 \text{ J. (Ans.)}$$

$$F_{\text{fld}} = \frac{W_{\text{fld}}}{l_g} = \frac{0.742}{(0.45 \times 10^{-2})} (-) = 164.89 \text{ Nm} (-). \text{ (Ans.)}$$

Negative sign indicates that force acts in a direction to reduce air gap length (l_g).

(ii) W_{mech} :

$$dW_{\text{mech}} = \frac{1}{2} dW_{\text{elect}} = \frac{1}{2} i_0 (\psi_2 - \psi_1) = \frac{1}{2} i_0^2 (L_2 - L_1)$$

$$\text{As, } L = \frac{\mu_0 N^2 A_{\text{core}}}{l_g} = \frac{(4\pi \times 10^{-7}) \times (1200)^2 \times (2.7 \times 2.7 \times 10^{-4})}{l_g} = \frac{0.001319}{l_g}$$

$$L_1 (l_g = 0.45 \times 10^{-2} \text{ m}) = \frac{0.001319}{0.45 \times 10^{-2}} = 0.293 \text{ H}$$

$$L_2 (l_g = 0.225 \times 10^{-2} \text{ m}) = \frac{0.001319}{0.225 \times 10^{-2}} = 0.586 \text{ H}$$

Substituting the values, we have

$$W_{\text{mech}} = \frac{1}{2} \times (2.25)^2 (0.586 - 0.293) = 0.742 \text{ J. (Ans.)}$$

(iii) Expression for force (F_{fld}) as a function of l_g and W_{mech} :

$$F_{\text{fld}} = \frac{W_{\text{fld}}}{l_g} = -\frac{\frac{1}{2} Li^2}{l_g} = -\frac{1}{2} \left[\frac{\mu_0 N^2 A_{\text{core}}}{l_g \times l_g} \right] i^2$$

$$= -\frac{1}{2} \left[\frac{4\pi \times 10^{-7} \times 1200^2 \times (2.7 \times 2.7 \times 10^{-4})}{l_g^2} \right] \times (2.25)^2$$

$$\text{or } F_{\text{fld}} = -\frac{0.00334}{l_g^2} \dots \text{ Required expression. (Ans.)}$$

$$dW_{\text{mech}} = \int_{l_{g1}}^{l_{g2}} F_{\text{fld}} dl_g = \int_{0.45 \times 10^{-2}}^{0.225 \times 10^{-2}} -\frac{0.00334}{l_g^2} = \left[\frac{0.00334}{l_g} \right]_{0.45 \times 10^{-2}}^{0.225 \times 10^{-2}}$$

$$= 0.00334 \left[\frac{1}{0.225 \times 10^{-2}} - \frac{1}{0.45 \times 10^{-2}} \right] = 0.742 \text{ J}$$

$$= 0.742 \text{ J (Result of part (ii) verified). (Ans.)}$$

Example 14. The self and mutual inductances of the two exciting coils of a multiply-excited translatory system are :

$$L_{11} = L_{22} = \frac{3.6}{1+2x}, L_{12} = L_{21} = \frac{1.8}{1+2x}$$

Calculate the time average force and coil currents at $x = 0.4 \text{ m}$ when :

- (i) Both the coils are connected in series across a voltage source of $100 \cos 314 t$;
- (ii) Both the coils are connected in parallel across a voltage source of $100 \cos 314 t$.

Solution. Given : $L_{11} = L_{22} = \frac{3.6}{1+2x}$; $L_{12} = L_{21} = \frac{1.8}{1+2x}$; $x = 0.4 \text{ m}$

Time average force $F_{\text{fld(av.)}}$; i_1, i_2 :

- (i) When the coils are connected in series :

$$\text{At } x = 0.4 \text{ m}; L_{11} = L_{22} = \frac{3.6}{1+2 \times 0.4} = 2,$$

and

$$L_{12} = L_{21} = \frac{1.8}{1+2 \times 0.4} = 1$$

With armature held at $x = 0.4 \text{ m}$, the circuit equations for the two coils are :

$$v_1 = L_{11} \frac{di_1}{dt} + L_{12} \frac{di_2}{dt} = 2 \frac{di_1}{dt} + \frac{di_2}{dt} \quad \dots(25)$$

$$v_2 = L_{22} \frac{di_2}{dt} + L_{21} \frac{di_1}{dt} = 2 \frac{di_2}{dt} + \frac{di_1}{dt} \quad \dots(26)$$

As both the coils are connected in series (i.e., $i_1 = i_2$)

$$\therefore v_1 + v_2 = 100 \cos 314 t$$

$$\text{or } 3 \frac{di_1}{dt} + 3 \frac{di_2}{dt} = 100 \cos 314 t \quad [\text{From (i) and (ii)}]$$

$$\text{or } \frac{di_1}{dt} = \frac{di_2}{dt} = \frac{100}{6} \cos 314 t = 16.67 \cos 314 t \quad (\because i_1 = i_2)$$

$$\text{By integrating, } i_1 = i_2 = \frac{16.67}{314} \sin 314 t = 0.053 \sin 314 t. \quad (\text{Ans.})$$

$$\text{Now, } W_{\text{fld}}(i_1, i_2, x) = \frac{1}{2} L_{11} i_1^2 + \frac{1}{2} L_{22} i_2^2 + L_{12} i_1 i_2$$

$$= \frac{1}{2} \left(\frac{3.6}{1+2x} \right) i_1^2 + \frac{1}{2} \left(\frac{3.6}{1+2x} \right) i_2^2 + \left(\frac{1.8}{1+2x} \right) i_1 i_2$$

$$= \frac{1.8}{1+2x} (i_1^2 + i_2^2 + i_1 i_2)$$

$$F_{\text{fld}} = - \frac{\partial W_{\text{fld}}}{\partial x} = \frac{3.6}{(1+2x)^2} (i_1^2 + i_2^2 + i_1 i_2)$$

$$\text{At } x = 0.4 \text{ m}; F_{\text{fld}}(x = 0.4 \text{ m}) = \frac{3.6}{(1+2 \times 0.4)^2} (i_1^2 + i_2^2 + i_1 i_2)$$

$$= 1.111 (i_1^2 + i_2^2 + i_1 i_2)$$

$$\therefore F_{\text{fld}}(t) = 3 \times 1.111 (0.053 \sin 314 t)^2 \quad (\because i_1 = i_2)$$

$$= 3 \times 1.111 \times (0.053)^2 \sin^2 314 t$$

$$= 0.00936 \sin^2 314 t$$

$$F_{\text{fld}}(\text{avg.}) = \frac{3 \times 1.111}{2} \times (0.053)^2 = 0.00468 \text{ N.} \quad (\text{Ans.})$$

Substituting the values of i_1 (= 0.96 A) and i_2 (= 0.012 A), we have

$$\begin{aligned} T_{\text{fd}} &= \frac{(0.96)^2}{2} (-2 \times 10^{-3}) \sin 2\theta + \frac{(0.012)^2}{2} (-10 \sin 2\theta) + (0.96 \times 0.012)(-0.2 \sin \theta) \\ &= -0.922 \times 10^{-3} \sin 2\theta - 0.72 \times 10^{-3} \sin 2\theta - 2.3 \times 10^{-3} \sin \theta \\ \text{or } T_{\text{fd}} &= -1.642 \times 10^{-3} \sin 2\theta - 2.3 \times 10^{-3} \sin \theta. \quad (\text{Ans.}) \end{aligned}$$

HIGHLIGHTS

- An *electromechanical energy conversion device* is one which converts electrical energy into mechanical energy and mechanical energy into electrical energy.
- The phenomenon where by an e.m.f. and hence current is induced in any conductor which is cut across or cut by a magnetic flux is known as *electromagnetic induction*.
- The examples of *singly-excited magnetic field system* are *electromagnetic relays, reluctance motor*.
- The examples of *multiply-excited magnetic field systems* are *synchronous motor, alternator* on which stator and rotor have A.C. and D.C. excitation respectively.
- The expression for mechanical force developed in a current excited system is given as :

$$F_{\text{fd}} = \frac{\partial W'_{\text{fd}}(i, x)}{\partial x}.$$

OBJECTIVE TYPE QUESTIONS

Fill in the Blanks or say "Yes" or "No" :

- An energy conversion device is one which converts electrical energy into mechanical energy and vice versa.
 - The principle of conservation of energy states that energy can neither be created nor destroyed, it can merely be converted from one form to another.
 - The energy balance equation may be written as :
- $$\int dW_{\text{input}} = \int dW_{\text{output}} + \int dW_{\text{magnetic field}} + \dots$$
- Owing to the inertia associated with mechanical components, electromechanical energy conversion devices (EMEC) are
 - Electromagnetic radiation from the coupling field in EMEC device is
 - Faraday's law states that the magnitude of induced e.m.f. is equal to the rate of change of flux-linkages.
 - The e.m.f. induced by variations of flux is termed as dynamically induced e.m.f.
 - Electromagnetic relay is an example of singly-excited magnetic field system.
 - An alternator is an example of excited magnetic field system.
 - Reluctance motor is an example of excited magnetic field system.

ANSWERS

- | | | | | |
|----------------------|--------|----------------------------|----------------|---------------|
| 1. electromechanical | 2. Yes | 3. $\int dW_{\text{heat}}$ | 4. slow moving | 5. negligible |
| 6. second | 7. No | 8. Yes | 9. multiply | 10. singly. |

THEORETICAL QUESTIONS

- What is an "Electromechanical energy conversion device"?
- Discuss briefly "Principle of energy conversion".
- Describe briefly Faraday's laws of electromagnetic induction.
- Explain briefly an electromechanical energy conversion device with the help of a block diagram.
- For a singly excited magnetic field system, derive the relation for the magnetic stored energy.
- Show that the torque developed in a doubly excited system is equal to the rate of increase of field energy with respect to displacement at constant.
- Derive an expression for the magnetic force developed in a multiply-excited translational magnetic system.
- Discuss briefly about torque production in rotating machines.
- Discuss briefly general analysis of electromechanical system, and derive an expression for the mechanical force developed in a current excited system.

UNSOLVED EXAMPLES

- The relay shown in Fig. 42 is made from infinitely-permeable magnetic material with a movable plunger, also of infinitely permeable material. The height of the plunger is much greater than the airgap length ($h \gg l_g$).

Calculate the magnetic stored energy W_{st} as a function of plunger position ($0 < x < d$) for $N = 1000$ turns;

$$l_g = 2.0 \text{ mm}; d = 0.15 \text{ m}, l = 0.1 \text{ m}, \text{ and } i = 10 \text{ A}.$$

$$\left[\text{Ans. } 236 \left(1 - \frac{x}{d} \right) \text{ J} \right]$$

- Fig. 43 shows the magnetic circuit consisting of a single-coil stator and an oval rotor. The coil inductance varies with rotor angular position, measured between the magnetic axis of the stator coil and major axis of rotor, as

$$L(\theta) = L_0 + L_2 \cos(2\theta) \quad (29)$$

where $L_0 = 10.6 \text{ mH}$ and $L_2 = 2.7 \text{ mH}$.

Find the torque as a function of θ for a coil current of 2A. [Ans. $T_{\text{rel}}(\theta) = -0.0108 \sin(2\theta) \text{ Nm}$]

- The following data relate to the electromagnetic relay shown in Fig. 39.

Number of turns = 1000

Cross-sectional area of the core = 3 cm \times 3 cm

Permeability of the core = infinite

Neglecting fringing effects, find the following :

(i) The inductance of coil for air gap length (l_g) of 0.5 cm, the energy stored in the field, and force acting on the armature when the coil carries a current of 2.5 A.

(ii) The mechanical energy output when the air gap is decreased from 0.5 cm to 0.25 cm, assuming that the current through the coil remains constant at 2.5 A.

[Ans. (i) 226.1 mH ; 0.706 J ; -141.37 Nm (ii) 0.706 J]

- The self and mutual inductances of the two exciting coils of a multiply-excited translatory systems are :

$$L_{11} = L_{22} = \frac{4}{1+2x}, L_{12} = L_{21} = \frac{2}{1+2x}$$

Calculate the time average force and coil currents at $x = 0.5 \text{ m}$ when :

(i) Both the coils are connected in series across a voltage source of $100 \cos 314t$.

(ii) Both the coils are connected in parallel across a voltage source of $100 \cos 314t$.

[Ans. (i) $0.053 \sin 314t$; 0.00 421 (ii) $0.106 \sin 314t$; 0.0169 N.]

- Fig. 44 shows a system, in which the inductances are as given below :

$$L_{11} = (3 + \cos 2\theta) \times 10^{-3}; L_{12} = 0.3 \cos \theta; L_{22} = 30 + 10 \cos 2\theta.$$

Determine the torque $T_{\text{rel}}(\theta)$ for current $i_1 = 0.8 \text{ A}$ and current $i_2 = 0.01 \text{ A}$.

[Ans. $T_{\text{rel}} = 0.00164 \sin 2\theta - 0.0024 \sin \theta$]

MISCELLANEOUS EXAMINATIONS' QUESTIONS WITH SOLUTIONS

- I. Questions including Numerical Problems**
 - II. Questions with Short/Very Short Answers**
-



Derivation of the formula : Refer Fig. 5

$$\begin{aligned}
 I_{r.m.s.}^2 &= \frac{1}{2\pi} \int_0^\pi i^2 d\theta = \frac{1}{2\pi} \int_0^\pi (I_{max} \sin \theta)^2 d\theta \\
 &= \frac{I_{max}^2}{2\pi} \int_0^\pi \sin^2 \theta d\theta = \frac{I_{max}^2}{2\pi} \int_0^\pi \left(\frac{1 - \cos 2\theta}{2} \right) d\theta \\
 &= \frac{I_{max}^2}{4\pi} \left| \theta - \frac{\sin 2\theta}{2} \right|_0^\pi = \frac{I_{max}^2}{4\pi} \left[\left(\pi - \frac{\sin 2\pi}{2} \right) - (0 - 0) \right] \\
 &= \frac{I_{max}^2}{4\pi} \times \pi = \frac{I_{max}^2}{4} \\
 \therefore I_{r.m.s.} &= \frac{I_{max}}{2}.
 \end{aligned}$$

Q. 3. A voltage $V(t) = 400 \sin 314t$ is applied to the circuit shown. Find the currents and their phase angles w.r.t. the voltage for the three branches.

$$C = 50 \mu F, R_1 = 100 \Omega, R_2 = 50 \Omega, L = 0.1 H.$$

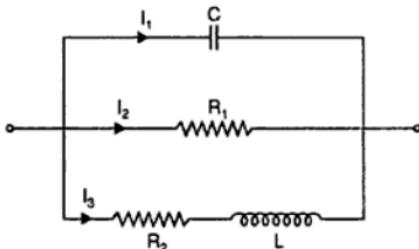


Fig. 6

Solution. Given : $V(t) = 400 \sin 314t, C = 50 \mu F = 50 \times 10^{-6} F;$

$$R_1 = 100 \Omega; R_2 = 50 \Omega, L = 0.1 H.$$

Here, $V_{max} = 400 V; 2\pi f t = 314t, \therefore f = \frac{314}{2\pi} \approx 50 \text{ Hz}$

$$V_{r.m.s.} = \frac{V_{max}}{\sqrt{2}} = \frac{400}{\sqrt{2}} = 282.8 V$$

$$\text{Capacitive reactance, } X_C = \frac{1}{\omega C} = \frac{1}{314 \times 50 \times 10^{-6}} = 63.7 \Omega$$

Current through branch-1 (i.e., through C),

$$I_1 = \frac{V}{X_C} = \frac{282.8}{63.7} = 4.44 \text{ A. (Ans.)}$$

Phase angle between I_1 and V , $\phi_1 = 90^\circ$ (I_1 leads V by 90°)

Current through branch-2 (i.e., through R_1),

$$I_2 = \frac{V}{R_1} = \frac{282.8}{100} = 2.828 \text{ A. (Ans.)}$$

Phase angle between I_2 and V , $\phi_2 = 0^\circ$ (I_2 is in phase with V)

Current through branch-3 (i.e., through R_2 and L),

$$I_3 = \frac{V}{\sqrt{R_2^2 + X_L^2}} = \frac{V}{\sqrt{R_2^2 + (\omega L)^2}}$$

$$= \frac{282.8}{\sqrt{(50)^2 + (314 \times 0.1)^2}} = 4.79 \text{ A. (Ans.)}$$

Phase angle between I_3 and V ,

$$\phi_3 = \tan^{-1} \left(\frac{X_L}{R} \right) = \tan^{-1} \left[\frac{(314 \times 0.1)}{50} \right] = 32.13^\circ. \text{ (Ans.)}$$

Q. 4. For the circuit shown in Fig. 7, calculate :

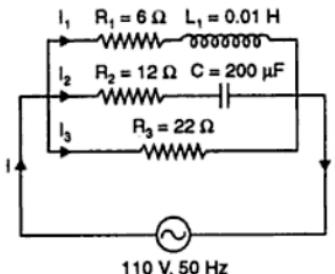


Fig. 7

- (i) The current in each branch.
- (ii) Total current taken.
- (iii) Power factor of the circuit.
- (iv) Total power consumed by the circuit.
- (v) Reactive power.
- (vi) Phasor diagram of the circuit.

Solution. Refer Fig. 7.

(i) The current in each branch :

$$\text{Branch 1 : } Z_1 = \sqrt{R_1^2 + X_{L1}^2}, \text{ where } (X_{L1} = 2\pi f L_1 = 2\pi \times 50 \times 0.01 = 3.14)$$

$$= \sqrt{6^2 + 3.14^2} = 6.77 \Omega$$

$$I_1 = \frac{V}{Z_1} = \frac{110}{6.77} = 16.25 \text{ A. (Ans.)}$$

$$\phi_1 = \tan^{-1} \left(\frac{3.14}{6} \right) = 27.62^\circ \text{ (lagging)}$$

$$\text{Branch 2 : } Z_2 = \sqrt{R_2^2 + X_C^2}$$

$$\left(\text{where } X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi \times 50 \times 200 \times 10^{-6}} = 15.9 \Omega \right)$$

$$= \sqrt{12^2 + (15.9)^2} = 19.92 \Omega. \text{ (Ans.)}$$

$$I_2 = \frac{V}{Z_2} = \frac{110}{19.92} = 5.52 \text{ A. (Ans.)}$$

$$\phi_2 = \tan^{-1} \left(\frac{15.9}{12} \right) = 52.96^\circ \text{ (leading)}$$

$$\text{Branch 3 : } Z_3 = R_3 = 22 \Omega$$

$$I_3 = \frac{V}{Z_3} = \frac{110}{22} = 5 \text{ A. (Ans.)}$$

$$\phi_3 = 0^\circ \text{ (Pure resistance)}$$

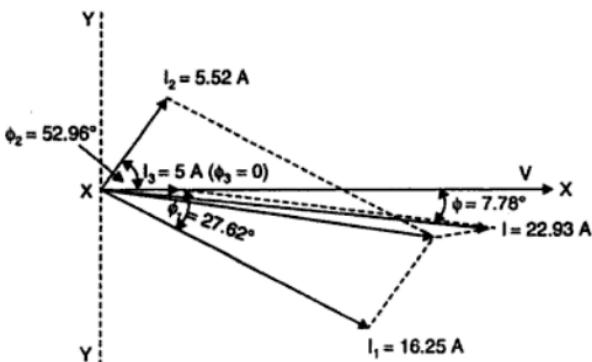
(ii) Total current taken, I :Currents I_1 , I_2 and I_3 are shown in Fig. 8Resolving these currents along XX and YY axis, we have :

Fig. 8. Phasor diagram.

$$\begin{aligned}I_{XX} &= I_1 \cos \phi_1 + I_2 \cos \phi_2 + I_3 \cos \phi_3 \\&= 16.25 \times \cos 27.62^\circ + 5.52 \cos 52.96^\circ + 5 \times 1 = 22.72 \text{ A} \\I_{YY} &= -I_1 \sin \phi_1 + I_2 \sin \phi_2 \\&= -16.25 \sin 27.62^\circ + 5.52 \sin 52.96^\circ = -3.13 \text{ A}\end{aligned}$$

Total current, $I = \sqrt{I_{XX}^2 + I_{YY}^2} = \sqrt{(22.72)^2 + (-3.13)^2} = 22.93 \text{ A. (Ans.)}$ (iii) Power factor of the circuit, $\cos \phi$:

$$\cos \phi = \frac{I_{XX}}{I} = \frac{22.72}{22.93} = 0.9908. \quad (\text{Ans.})$$

and

$$\phi = \cos^{-1}(0.9908) = 7.78^\circ.$$

(iv) Total power consumed :

$$P = VI \cos \phi = 110 \times 22.93 \times 0.9908 = 2499 \text{ W. (Ans.)}$$

(v) Reactive power :

$$\text{Reactive power} = VI \sin \phi = 110 \times 22.93 \times \sin 7.78^\circ = 341.4 \text{ VAR. (Ans.)}$$

(vi) Phasor diagram :

Phasor diagram is shown in Fig. 8.

Alternatively (Hints) :

$$\begin{aligned}\bar{I}_1 &= \frac{\bar{V}}{Z_1} = \frac{110 \angle 0^\circ}{6 + j3.14} = \frac{110 \angle 0^\circ}{(\sqrt{6^2 + 3.14^2}) \angle \tan^{-1}\left(\frac{3.14}{6}\right)} \\&= \frac{110 \angle 0^\circ}{6.77 \angle 27.62^\circ} = 16.25 \angle -27.62^\circ\end{aligned}$$

$$I_1 = 16.25 \text{ A}; \phi_1 = 27.62^\circ \text{ (lagging)}$$

i.e.,

where $\bar{Z}_2 \bar{Z}_3 = (11.81 \angle 32.13^\circ) \times (37.6 \angle -57.86^\circ) = 444.06 \angle -25.73^\circ$

and

$$\bar{Z}_2 + \bar{Z}_3 = (10 + j6.28) + (20 - j31.83) = 30 - j25.55$$

$$= (\sqrt{30^2 + 25.55^2}) \angle \tan^{-1} \left(-\frac{25.55}{30} \right) = 39.4 \angle -40.42^\circ$$

$$\therefore \frac{\bar{Z}_2 \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3} = \frac{444.06 \angle -25.73^\circ}{39.4 \angle -40.42^\circ} = 11.27 \angle 14.69^\circ$$

$$= 11.27 (\cos 14.69^\circ + j \sin 14.69^\circ) = (10.9 + j2.86) \Omega$$

$$\therefore \bar{Z} = \bar{Z}_1 + \frac{\bar{Z}_2 \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3} = (15 + j15.7) + (10.9 + j2.86) = (25.9 + j18.56) \Omega$$

$$= (\sqrt{25.9^2 + 18.56^2}) \angle \tan^{-1} \left(\frac{18.56}{25.9} \right) = 31.86 \angle 35.63^\circ$$

(i) Total current supplied, I :

$$I (= I_1) = \frac{\bar{V}}{\bar{Z}} = \frac{200 \angle 0^\circ}{31.86 \angle 35.63^\circ} = 6.28 \angle -35.63^\circ$$

Hence,

$$I = 6.28 \text{ A. (Ans.)}$$

(ii) Power factor of the circuit, $\cos \phi$:

Phase difference between V and I ,

$$\phi = -35.63^\circ \quad (I \text{ lags } V \text{ by } 35.63^\circ)$$

$$\therefore \cos \phi = \cos (-35.63^\circ) = 0.8128 \text{ lagging. (Ans.)}$$

(iii) Power consumed by the circuit:

$$P = VI \cos \phi = 200 \times 6.28 \times 0.8128 = 1020.9 \text{ W. (Ans.)}$$

(iv) Voltage across each branch (A, B and C)

Voltage across branch A,

$$\begin{aligned} \bar{V}_1 &= \bar{I}_1 \bar{Z}_1 = \bar{I} \bar{Z}_1 \\ &= (6.28 \angle -35.63^\circ) \times (21.7 \angle 46.3^\circ) = 136.28 \angle 10.67^\circ \\ &= 133.9 + j25.23 \end{aligned}$$

Hence

$$V_1 = 136.28 \text{ V. (Ans.)}$$

Voltage across branches B and C, $\bar{V}_2 (= \bar{V}_3) = \bar{V} - \bar{V}_1$

(\because Branches B and C are connected in parallel)

$$= (200 \pm j0) - (133.9 + j25.23)$$

$$= 66.1 - j25.23 = 70.75 \angle -20.89^\circ$$

Hence,

$$V_2 = V_3 = 70.75 \text{ V. (Ans.)}$$

(v) Current through each branch, I_1, I_2, I_3 :

$$I_1 = I = 6.28 \text{ A. (Ans.)}$$

$$I_2 = \frac{\bar{V}_2}{\bar{Z}_2} = \frac{70.75 \angle -20.89^\circ}{11.81 \angle 32.13^\circ} = 5.99 \angle -53.02^\circ$$

Hence,

$$I_2 = 5.99 \text{ A. (Ans.)}$$

$$I_3 = \frac{\bar{V}_3 (= \bar{V}_2)}{\bar{Z}_3} = \frac{70.75 \angle -20.89^\circ}{37.6 \angle -57.86^\circ} = 1.88 \angle 36.97^\circ$$

Hence,

$$I_3 = 1.88 \text{ A. (Ans.)}$$

Open circuit test, instruments on low side :

Wattmeter reading = 396 W

Ammeter reading = 9.65 A

Voltmeter reading = 120 V

Short circuit test, instruments on high side :

Wattmeter reading = 810 W

Ammeter reading = 20.8 A

Voltmeter reading = 92 V

Find the equivalent circuit parameters referred to high side.

Solution. (a) The explanation is as follows : Refer Fig. 11.

The transformer is said to be loaded when the secondary circuit of a transformer is completed through an impedance or load. The magnitude and phase of secondary current I_2 with respect to secondary terminal voltage will depend upon the characteristic of load, i.e., current I_2 will be in phase, lag behind and lead the terminal voltage V_2 respectively when the load is purely resistive, inductive and capacitive.

The secondary current I_2 sets up its own ampere-turns ($= N_2 I_2$) and creates its own flux ϕ_2 opposing the main flux ϕ_0 created by no-load current I_0 . The opposing secondary flux ϕ_2 weakens the primary flux ϕ_0 momentarily hence primary counter or back e.m.f. E_1 tends to be reduced. V_1 gains the upper hand over E_1 momentarily and hence causes more current to flow in primary. Let this additional primary current be I_2' . It is known as *load component of primary current*. The additional primary m.m.f. $N_1 I_2'$ sets up its own flux ϕ_2' which is in opposition to ϕ_2 (but is in the same direction and is equal to it in magnitude). Hence they cancel each other. Thus we find that the magnetic effects of secondary current I_2 are immediately neutralised by the additional primary current I_2' which is brought into existence exactly at the same instant as I_2 .

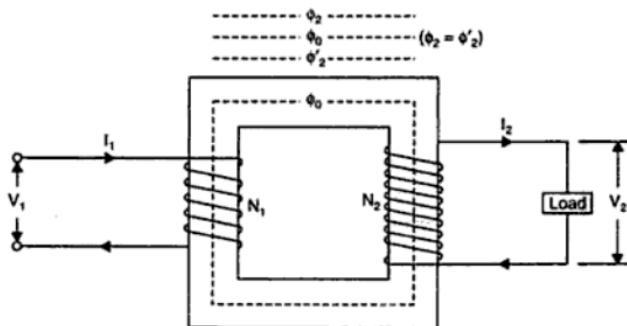


Fig. 11. An ideal transformer on load.

Thus, we find that when the secondary current increases, the transformer draws extra current from the mains.

(b) Given : Transformer rating : 50 kVA, 2400/120 volt

O.C. test (L.V. side) : $P_0 = 396 \text{ W}$; $I_0 = 9.65 \text{ A}$; $V_2 = 120 \text{ V}$

S.C. test (H.V side) : $P_{SC} = 810 \text{ W}$; $I_{SC} = 20.8 \text{ A}$; $V_{SC} = 92 \text{ V}$.

Armature current (I_a), line current (I), torque (T) : Refer Fig. 13.

$$E_{b0} = V - I_b R_a = 230 - 2 \times 0.5 = 229 \text{ V}$$

$$E_b = V - I_a R_a = 230 - I_a \times 0.5 \quad \dots(i)$$

Now,

$$N \propto \frac{E_b}{\phi}$$

$$\frac{N}{N_0} = \frac{E_b}{E_{b0}}$$

(since ϕ is constant for a shunt motor)

or

$$\frac{1100}{1200} = \frac{E_b}{229}$$

$$\therefore E_b = \frac{1100 \times 229}{1200} = 209.92 \text{ V}$$

Substituting this value in (i), we get

$$209.92 = 230 - I_a \times 0.5$$

$$\therefore I_a = \frac{230 - 209.92}{0.5} = 40.16 \text{ A. (Ans.)}$$

$$I_{sh} = \frac{V}{R_{sh}} = \frac{230}{115} = 2 \text{ A}$$

$$\therefore I = I_a + I_{sh} = 40.16 + 2 = 42.16 \text{ A. (Ans.)}$$

$$\text{Also } \frac{2\pi NT}{60} = E_b I_a$$

$$\text{or } \frac{2\pi \times 1100 \times T}{60} = 209.92 \times 40.16$$

$$\therefore T = \frac{209.92 \times 40.16 \times 60}{2\pi \times 1100} = 73.18 \text{ Nm. (Ans.)}$$

Q. 12. Sketch a layout of squirrel-cage induction motor. Label all the parts and materials used for each part.

Solution. The sketch of layout of a squirrel-cage induction motor is shown in Fig. 13



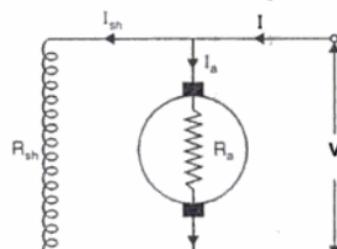


Fig. 13

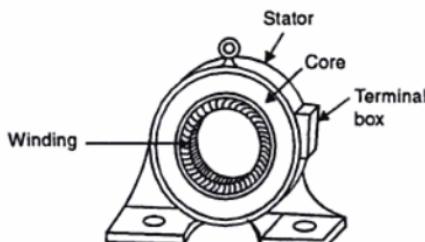

(a) Stator

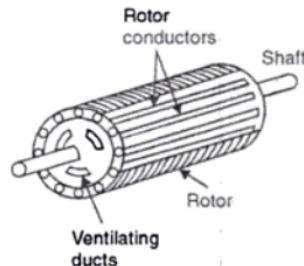

(b) Squirrel-cage rotor

Fig. 14. Squirrel-cage induction motor.

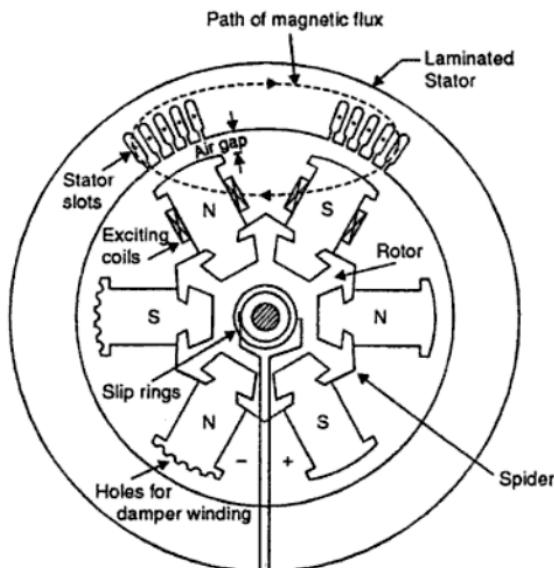


Fig. 15. Synchronous machine.

(iii) **Stator windings.** Stator winding is placed in stator slots. Open slots are used, permitting easy installation of the stator coils and easy removal in case of repair.

2. Rotor. The revolving field structure is usually called the rotor. It consists of the following components.

(i) **Rotor shaft.** It is made of steel. Mechanical power is transferred through this component.

(ii) **Spider.** It contains many sides in which pole core and pole shoes are accommodated. It provides easy path to magnetic flux. It is made of cast iron.

(iii) **Pole core and pole shoes.** The poles are made of thick steel laminations riveted together and attached to the rotor by a dovetail joint as shown in Fig. 15. The overhang of the pole gives mechanical support to the field coil.

(iv) **Field or exciting coil/winding.** The field winding is placed around the core. When D.C. current flows through it the necessary magnetic field is produced by the poles. It is made of high conductivity copper.

Q. 14. Discuss constructional features, working principle of induction motor used in domestic ceiling fan. Draw neat diagrams.

Solution. The induction motor used in domestic ceiling fans is *single-phase split-phase capacitor-start run motor*.

Constructional features

It consists of the following two parts :

1. Stator (inner part)
2. Rotor (outer part).

1. Stator

- It is the inner part of the fan connected to the shaft which is further connected to the suspension rod attached with the hook.
- The stator core is made by staggering a number of silicon steel stampings. The running and starting windings are accommodated in the shallow and deep slots provided on the outer periphery. A capacitor is connected in series with the starting winding as shown in Fig. 16 (a).

2. Rotor

- It consists of two parts namely, *squirrel cage rotor* and *outer body*.
- Squirrel-cage rotor* is a laminated ring in which through and through holes/slots are provided. In these holes molten aluminium metal is poured to form aluminium conductors. These conductors are short-circuited on both the sides by aluminium short-circuiting rings.
- Outer body of the fan is usually aluminium diecast to reduce the weight (the body may also be made from cast iron). The squirrel cage rotor is fitted tightly with the body. The blades are attached with the body.

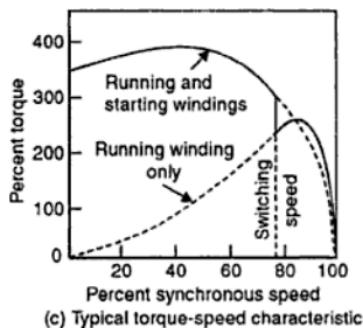
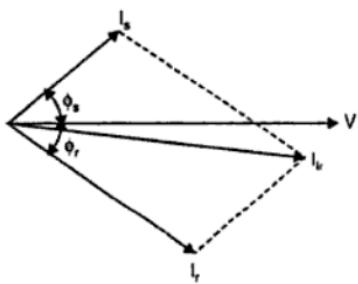
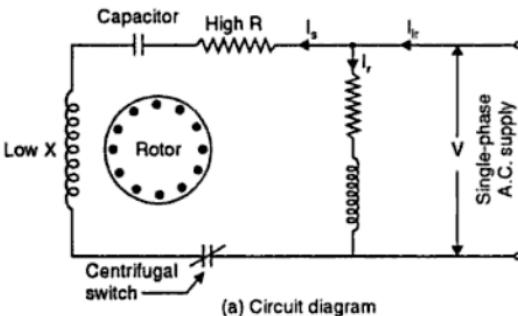


Fig. 16. Capacitor-start induction motor.

- This motor works on the principle of *electromagnetic induction*.
- The circuit of the capacitor-start motor is shown in Fig. 16 (a). When the motor is given the single-phase supply current I_s flows through the starting winding, leading the voltage by an angle ϕ_s ; while current I_r passes through the running/main winding lagging the voltage

by an angle ϕ_r . The vector/phasor diagram of the currents and voltage is shown in Fig. 16 (b). Both the windings set up alternating fluxes having phase difference ($\phi_s + \phi_r$). Consequently a resultant field is produced, which is revolving in nature. This field is cut by the rotor conductors and as a consequence e.m.f. is induced in them. Since the conductors are short-circuited, current flows through them and set up its own rotor field. When this rotor field tends to come in line with the main revolving field the rotor starts rotating in the same direction as that of the revolving field.

This motor may be *reversed by changing the connections of one of the windings.*

The typical torque-speed characteristic of capacitor-start induction motor is shown in Fig. 16 (c).

Q. 15. (a) Single phase induction motor is not a self-starting motor comment.

(b) Compare the features of split-phase and shaded-pole induction motors.

Solution. (a) When the stator winding of a single phase induction motor is connected to single phase A.C. supply, a *magnetic field is developed, whose axis is always along the axis of stator coils.* The magnetic field produced by the stator coils is *pulsating, varying sinusoidally with time.* Currents are induced in the rotor conductors by transformer action, these currents being in such a direction as to oppose the stator m.m.f. The axis of the motor m.m.f. wave coincides with that of the stator field, the *torque angle, is therefore, zero and no torque is developed in starting.* However, if the rotor is given a push by hand or by other means in either direction, it will pick up the speed and continue to rotate in the same direction developing operating torque. *Thus a single phase induction motor is not inherently self starting and requires some special means for starting.*

(b) The comparison of the features of split-phase and shaded-pole induction motors is given below :

S. No.	Features	Split-phase Motor	Shaded-pole Motor
1.	<i>Stator conduction</i>	Contains running/main winding and starting winding.	Contains projected portion around which winding is placed.
2.	<i>Production of revolving field</i>	In order to produce the revolving field and torque, a capacitor is connected in the starting winding.	A portion of the pole (1/3rd portion) is shaded by providing a short-circuiting copper band around it. This arrangement produces the starting torque.
3.	<i>Starting torque</i>	High	Poor
4.	<i>Efficiency</i>	High (70 to 80%)	Low (40 to 60%)
5.	<i>Power factor</i>	High p.f. (0.85 to 0.95 lag)	Very poor p.f. (0.4 to 0.6 lag)
6.	<i>Change in speed</i>	The speed can be varied by changing the supply voltage.	Speed cannot be changed.
7.	<i>Reversal of rotation</i>	The direction of rotation can be reversed by reversing either the terminals of main winding or starting winding.	The direction of rotation cannot be reversed because its rotation is always from non-shaded portion of the pole to shaded portion of the pole.

$$\begin{aligned}
 &= \sqrt{\frac{\text{Area under the squared wave of an alternation}}{\text{No. of equal divisions}}} \\
 &= \text{root mean square (rms) value}
 \end{aligned}$$

6. A coil has resistance of 10 ohms and draws a current of 5 A when connected across a 100 volt, 50 Hz source. Determine the power factor of the circuit.

Ans. Impedance of the coil, $Z = \frac{V}{I} = \frac{100}{5} = 20 \Omega$

Resistance of the coil, $R = 10 \Omega$

Power factor of the circuit, $\cos \phi = \frac{R}{Z} = \frac{10}{20} = 0.5 \text{ lag}$ (Ans.)

7. Do wave shapes other than the sine wave have effective values ? Explain.

Ans.

- Yes, all the wave shapes other than sine wave have effective value since in each half cycle of the wave, work is being done.
- In fact, the effective value of current (or voltage) is that value of current (or voltage) which represents a steady current which when flows through a resistor of known resistance for a given time produces the same amount of heat as produced by alternating current when flows through the same resistance for the same time.

8. A coil has resistance of 10 ohms and draws a current of 5 A when connected across a 100 volt, 50 Hz source. Determine the reactive power of the circuit.

Ans. Given : $R = 10 \Omega ; I = 5A ; V = 100 V ; f = 50 \text{ Hz}$

$$Z = \frac{V}{I} = \frac{100}{5} = 20 \Omega$$

$$X_L = \sqrt{(Z)^2 - (R)^2} = \sqrt{(20)^2 - (10)^2} = 17.32 \Omega$$

$$\sin \phi = \frac{X_L}{Z} = \frac{17.32}{20} = 0.866$$

Reactive power $= VI \sin \phi$
 $= 100 \times 5 \times 0.866 = 433 \text{ VAR}$ (Ans.)

9. A coil has resistance of 10 ohms and draws a current of 5 A when connected across a 100 volt, 50 Hz source. Determine the inductance of the coil.

Ans. Given : $R = 10 \Omega ; I = 5 A ; V = 100 V ; f = 50 \text{ Hz}$

Impedance, $Z = \frac{V}{I} = \frac{100}{5} = 20 \Omega$

$$X_L = \sqrt{(Z)^2 - (R)^2} = \sqrt{(20)^2 - (10)^2} = 17.32 \Omega$$

Now, $X_L = 2 \pi f L$

$$\therefore \text{Inductance, } L = \frac{X_L}{2\pi f} = \frac{17.32}{2\pi \times 50} = 55.13 \text{ mH}$$
 (Ans.)

10. Why does a transformer have an iron core ? How does the leakage flux occur in a transformer ?
Ans.

- To provide low reluctance path for the magnetic flux to setup in the core, it is made of iron. Because of iron, core provides low reluctance path and a sufficient quantity of magnetic flux is setup in the core which induces mutually induced e.m.f. and self induced e.m.f. in the secondary and primary respectively.
- The flux produced by the primary or secondary windings which is set up in air linking with its own turns and not linking with the other is called leakage flux.

- In case of 1-phase induction motor, when 1-phase supply is given to a 1-phase wound stator of an induction motor, an *alternating field is set up*. This alternating field may be represented by two fields each having half the magnitude revolving in opposite direction at constant synchronous speed. These revolving fields *develop equal and opposite torques due to which no starting torque is developed*.
22. The reactance of the rotor of the induction motor varies greatly between starting and running conditions. Explain, why ?

Ans. Rotor reactance of an induction motor is given by the relation :

$$X_2 = 2\pi f_r L_2 = s \times 2\pi f L_2 \quad (\text{since } f_r = sf)$$

At start slip is 1 and the rotor reactance is maximum called *standstill rotor reactance*,

$$X_{2s} = 2\pi f L_2$$

$$\therefore X_2 = sX_{2s}$$

As the slip varies greatly between starting and running conditions, therefore, rotor reactance also varies greatly between starting and running conditions.

23. Discuss, why the phase spread of three-phase winding is 60° and not 120° ?

Ans. Three-phase winding is placed under each pole and each pole occupies 180° elect. Hence each phase is spread by 60° (*i.e.*, $\frac{180^\circ}{3} = 60^\circ$).

24. Why should the auxiliary winding in a capacitor start motor be disconnected after the motor has picked up speed ?

Ans. In this case, the capacitor used is a dry-type electrolytic capacitor. This type of capacitor is designed for a *definite duty cycle and not for continuous use*. A faulty switch may keep the auxiliary winding energised for long time and thereby shorten its life span.

25. A single-phase induction motor has poorer performance as compared to a three-phase induction motor. Why ?

Ans. The *flux distribution in single-phase induction motor is poor in comparison to three-phase induction motors*. Therefore, the performance characteristics of 1-phase induction motors are poorer than 3-phase induction motors.

26. Explain the purpose of using a compensating winding in an universal motor.

Ans. An universal motor is basically series motor. When this motor is operated on A.C., due to armature reaction heavy sparking occurs on the commutator. To reduce armature reaction, a special type of compensating winding is employed in universal motors.

This compensating winding may be placed, either conductively (in series) in armature circuit or inductively (in parallel) with armature winding as shown in Fig. 3.

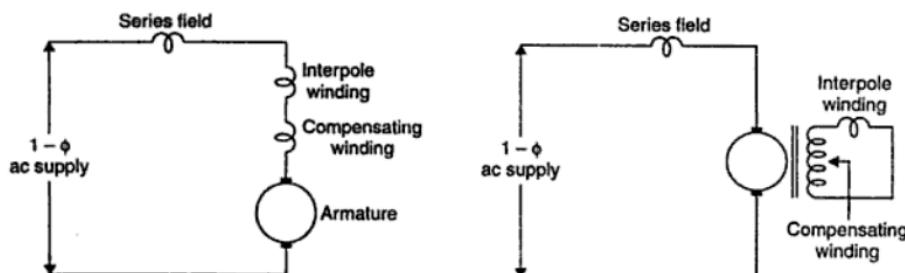


Fig. 3

Ans.

(i) **Refrigerator.** *Single-phase, capacitor start capacitor run induction motor.*

This motor provides heavy starting torque. Under running condition, one of the capacitors is disconnected which provides heavy starting torque and the other remains in circuit to run the machine at unit p.f.

(ii) **Mixie.** *Single-phase series motor.*

It can operate at high speed to crush the material and can pick heavy loads at start.

(iii) **Wall clock.** *Single-phase synchronous motor.*

It rotates only at constant (synchronous) speed to give accurate time.

(iv) **Ceiling fan.** *Single-phase capacitor run induction motor.*

It operates at almost unity p.f. Its speed is almost constant at a particular supply voltage. Its speed can be changed by changing the voltage applied across its terminals.

(v) **Sewing machine.** *Single-phase A.C. series motor.*

It can operate at a very high speed and stitching can be done very quickly.

(vi) **Lathe.** *Single-phase capacitor run induction motor or 3-phase squirrel cage induction motor.*

These motors operate almost at constant speed at all loads.

(vii) **Rolling mills.** *3-phase slip-ring induction motors.*

These motors have the ability to pick heavy loads. In the rolling mills, when steel to be rolled is employed between the rollers, this acts as a heavy load. This load can only be picked by 3-phase slip-ring induction motors.

(viii) **Electric traction.** *DC series motors.*

The heavy load of the train can be picked up at the start by D.C. series motors very efficiently. Moreover, the speed of these motors (or train) can be regulated very easily by using various electric circuits.

(ix) **Lifts.** *3-phase slip-ring induction motors.*

These motors have the ability to lift the heavy loads at start by inserting external resistance in the rotor circuit.

(x) **Vacuum cleaners.** *AC series motors.*

To create vacuum, high speed motors are required. AC series motors are best suited as they can be operated at very high speeds.

34. State the difference between "Cage rotor" and "Phase wound rotor" construction.

S.No.	Cage rotor construction	Phase wound rotor construction
1.	Bare bar conductors are used.	Insulated winding is used.
2.	No insulation is provided between rotor conductors and rotor core.	Insulation is provided between rotor winding and rotor core.
3.	Rotor conductors are short-circuited by providing short-circuiting rings at both the sides of the rotor.	Rotor winding is connected in star and the remaining three ends are connected to each slip-ring separately.
4.	No slip ring is provided.	Three slip rings are provided.
5.	Rotor conductors are usually aluminium die cast.	Rotor conductors (winding) are generally of copper material.
6.	Rotor resistance is fixed.	Rotor circuit resistance can be changed by inserting external resistance.

35. What do you understand by domestic and industrial systems ?

Ans. Domestic system :

- All the domestic appliances such as lamps, tubes, fans, mixer grinder, TV, radios etc. are operated at 230 V, single-phase, A.C. supply. The electrical system employed to operate these appliances is called *domestic system*.
- *Usually, 1-phase (some times 3-phase, 4-wire for large domestic loads) system is employed in the houses.*

Industrial system :

- All the industrial machines such as induction motors, induction furnaces etc. are operated at 400 V, 3-phase, A.C. supply.
- The electrical system employed to operate these machines/equipment is called *industrial system*.
- Usually, 3-phase, 4-wire system is employed in the industry.

36. Briefly discuss about the organisation of distribution boards.

Ans.

- A simple distribution board employed in the domestic installation is shown in Fig. 4.

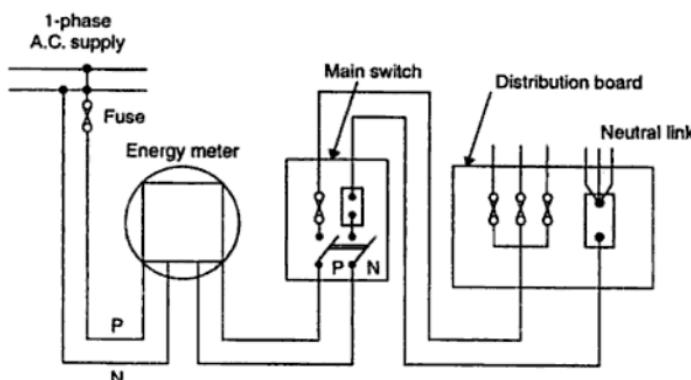


Fig. 4. Distribution board.

- A distribution board contains *main switch, various fuses for sub-circuits and neutral link*. Sometimes, MCB is used in place of fuses.

B. Questions With Very Short Answers

1. A particular application employing a D.C. generator requires high voltage and low current. Should be machine be lap wound or wave wound ?

Ans. Wave wound.

2. Iron loss in a D.C. machine increases with increasing load. What is the mode of excitation ?

Ans. Series excitation.

3. Why is that the V/F ratio is kept constant while controlling the speed of a 3-phase induction motor by varying the supply frequency ?

Ans. To keep the flux constant.

20. Alternators have no commutators, why ?
Ans. They have to supply electrical energy with an alternating voltage.
21. An alternator can be used as a synchronous condenser. Under what conditions it should operate ?
Ans. Over excited.
22. Which test gives the copper-loss of a transformer ?
Ans. S.C. test.
23. What is dimension of L/R ?
Ans. T .
24. Stator of an induction motor has full pitch coil span of 18 slots. What must be short pitch angle in degree if the 5th harmonics components of the e.m.f. is to be eliminated ?
Ans. 36° .
25. A 3-phase, 50 Hz induction motor runs at 960 r.p.m. on no-load and 940 r.p.m. at full-load. Find full-load slip.
Ans. 6%.
26. What is critical speed in a D.C. shunt generator ?
Ans. Speed for which shunt field resistance represents critical resistance.
27. Which method we must adopt to control the speed of a D.C. shunt motor above the base speed ?
Ans. Field control method.
28. What are the advantages of two wattmeters method over single wattmeter for 3-phase power measurement ?
Ans. Can be used for balanced as well as unbalanced system.
29. Name the motor being used in the ceiling fan.
Ans. Single phase induction motor with split phase.
30. Which is the cheapest method of starting a 3-phase induction motor ?
Ans. D.O.L. starting.
31. When a D.C. motor produces maximum output power ?
Ans. When back e.m.f. is equal to half of the applied voltage.
32. What type of load should be connected to a transformer for getting maximum voltage regulation ?
Ans. Load required to be connected for maximum voltage regulation is inductive and for maximum regulation $\phi = \tan^{-1} (X_1/R_1)$.
33. What is the condition for producing maximum torque in a 3-phase induction motor ?
Ans. $R_2 = sX_2$.
34. What measures can be taken for minimising the effect of crawling ?
Ans. Effect of crawling can be minimised by chording, skewing and integral slot winding.
35. Which parameter of the equivalent circuit should change the diameter of the circle diagram and how it effects the pull-out torque ?
Ans. Total standstill leakage reactance per phase referred to stator. Pull-out torque is reduced by increased value of X .
36. What parameter of load influences the armature reaction of an alternator ?
Ans. Power factor of the load.
37. What is the use of Potier's triangle ?
Ans. To find voltage regulation.
38. How the power factor of a synchronous motor is changed keeping the shaft load undisturbed ?
Ans. By changing the excitation.

55. A 3-phase induction motor is to be started first using an auto transformer with 80% tapping and next direct-on-line. What will be the ratio of the starting torques ?

Ans. 0.64.

56. Why does synchronous impedance method give a poorer voltage regulation ?

Ans. Saturation conditions are lower.

57. A synchronous motor is to be used as a synchronous condenser. Under what condition should it operate ?

Ans. Over excited.

58. Can a repulsion-induction motor ever run at super synchronous speed ?

Ans. Yes.

59. A full pitch coil in an alternator has a span of 18 slots. What should be the span if the third harmonic component of the e.m.f. is to be eliminated ?

Ans. 12 slots.

60. If the applied voltage to the primary of a transformer is reduced to 50 per cent of its initial value, at the same time the number of turns in the secondary are doubled. What will be the secondary voltage ?

Ans. Same.

61. Derive the relation between electrical and mechanical angle in case of rotating machine.

Ans. Mechanical degrees in rotation = 360°

Electrical degrees = No. of pairs of poles times 360°

$$\therefore \text{Mechanical degrees} = \frac{\text{electrical degrees}}{\text{pair of poles}} \text{ i.e., } Q_{\text{mech}} = \frac{Q_{\text{elect.}}}{(p/2)}.$$

62. A 6-pole D.C. generator has a rated speed of 600 r.p.m. Calculate the frequency of generated e.m.f. in armature conductors and at its brushes.

$$\text{Ans. } N = \frac{120f}{p}$$

$$\therefore f = \frac{pN}{120} = \frac{6 \times 600}{120} = 30 \text{ Hz.}$$

63. Why does an induction motor always operate at lagging power factor ?

Ans. Induction motor has large magnetising current at very low power factor, hence even at load it will always work at lagging power factor.

64. Can the excitation level give the idea of operating power factor of synchronous motor ?

Ans. Excitation decides operating power factor of synchronous motor, for example, over excited motor has leading power factor.

65. Explain the advantages of using closed slots for the rotor of small rating squirrel cage induction motor.

Ans. Close side slot gives low air gap reluctance and hence has reduced value of magnetising current. This provides high value of leakage reactance, due to which starting current is limited.

66. Transformers, belonging to phase group DY1 and YY0 cannot be operated in parallel, state why.

Ans. There exists a phase angle difference between the two secondary voltages, hence cannot be connected in parallel.

67. Comment on the statement, 'triplex order harmonics current can flow in a delta connected winding but are absent in the line current'.

Ans. Triplex harmonic currents are cophased, hence they can flow in delta local circuit, their resultant in line becomes zero.

68. A D.C. shunt motor may run away at heavy loads. Comment.

Ans. At heavy loads the internal drops become very large and hence terminal voltages are reduced to a very low value, finally resulting into run away.

69. Why the pole changing method of speed control, can be used in squirrel cage induction motor?

Ans. By providing different sets of windings in the stator of squirrel cage induction motor and selecting a particular winding at a time the speed of the motor can be controlled.

70. An induction generator is running at a slip of 0.03 and is feeding power to the infinite bus. What will happen if the input is suddenly removed?

Ans. The induction generator will start functioning as induction motor by taking power from the infinite bus.

EXPERIMENT NO. 1

A. Measurement of Impedance of R-L, R-C and R-L-C Series Circuits.

Objective :

- (i) To determine the resistance, inductance and capacitance by voltage and current measurement.
- (ii) To determine the power factor of R-L, R-C and R-L-C series circuits.
- (iii) To draw a phasor diagram and compare the experimental and theoretical results.

Material and equipment required :

1. Single-phase auto-transformer (0—270 V, 10A) 1 No.
2. Purely resistance or rheostat ($90\ \Omega$, 2A) 1 No.
3. Purely inductive coil or choke (2A) 1 No.
4. Purely capacitor ($10\ \mu F$, 230 V) 1 No.
5. Moving-iron voltmeter (0—250 V) 4 No.
6. Moving-iron ammeter (0—5A) 1 No.
7. Connecting leads.

Theory :

I. R-L circuit (Resistance and inductance in series)

R-L circuit is shown in the Fig. 1.

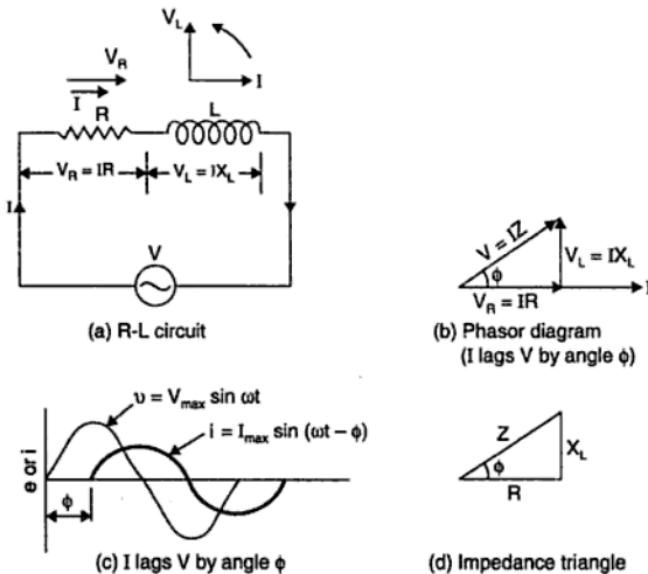


Fig. 1. Resistance and inductance in series.

- Impedance, $Z = \sqrt{R^2 + X_L^2}$ (where $X_L = 2\pi fL \Omega$)
- Current, $I = \frac{V}{Z}$
- Power factor, $\cos \phi = \frac{R}{Z}$ $\left(= \frac{\text{True power}}{\text{Apparent power}} = \frac{W}{VA} \right)$
(or angle of lag, $\phi = \cos^{-1} \frac{R}{Z}$)
- Power consumed, $P = VI \cos \phi$ $\left(= IZ \times I \times \frac{R}{Z} = I^2 R \right)$

II. R-C circuit (Resistance and capacitance in series)

R-C circuit is shown in Fig. 2.

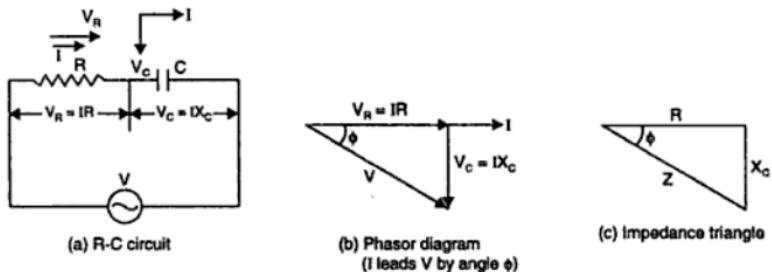


Fig. 2. Resistance and capacitance in series.

- Impedance, $Z = \sqrt{R^2 + X_C^2}$ (where $X_C = \frac{1}{2\pi fC} \Omega$, C being in farad)
- Current, $I = \frac{V}{Z}$
- Power factor, $\cos \phi = \frac{R}{Z}$
(or angle of lead, $\phi = \cos^{-1} \frac{R}{Z}$)
- Power consumed $= VI \cos \phi (= I^2 R)$

III. R-L-C circuit (Resistance, inductance and capacitance in series)

Fig. 3 shows a R-L-C circuit.

- Impedance, $Z = \sqrt{R^2 + (X_L - X_C)^2}$ [where $X_L = 2\pi fL$, L in henries]
and $X_C = \frac{1}{2\pi fC}$, C in farads]
- Current, $I = \frac{V}{Z}$

- Adjust the auto-transformer till a suitable voltage is applied. Note down the supply voltage (V), current (I), voltage across resistor (V_R) and voltage across inductor (V_L). Take number readings by varying the supply voltage, and note them down in the observation table.
- Connect the circuit for **resistance (R) and capacitance (C)** and repeat the experiment as mentioned above. Note down the various readings in the observation table.
- Now connect all the components i.e., **Resistance, inductance (inductor) and capacitance (capacitor)** and repeat the experiment. Note down the various readings in the observation table.

Observations :

I. R-L circuits :

S. No.	Voltmeter reading (in volts)			Ammeter reading (in amps.)	$Z = \frac{V}{I}$	$R = \frac{V_R}{I}$	$X_L = \frac{V_L}{I}$	$L = \frac{X_L}{2\pi f}$
	V_R	V_L	V					
1.								
2.								
3.								
4.								

II. R-C circuit :

S. No.	Voltmeter reading (in volts)			Ammeter reading (in amps.)	$Z = \frac{V}{I}$	$R = \frac{V_R}{I}$	$X_C = \frac{V_C}{I}$	$C = \frac{1}{2\pi f X_C}$
	V_R	V_C	V					
1.								
2.								
3.								
4.								

III. R-L-C circuit :

S. No.	Voltmeter reading (in volts)				Ammeter reading (in amps.)	$Z = \frac{V}{I}$	$R = \frac{V_R}{I}$	$X_L = \frac{V_L}{I}$	$X_C = \frac{V_C}{I}$	$p.f. = \frac{R}{Z}$
	V_R	V_L	V_C	V						
1.										
2.										
3.										
4.										

Observations :Value of resistance, $R =$...ohmsValue of inductance, $L =$...henryValue of capacitance, $C =$...farad

S. No.	Voltmeter reading (in volts)	Ammeter reading (in mA)	$Z = \frac{V}{I}$	$f_r = \frac{1}{2\pi\sqrt{LC}}$	$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$
1.					
2.					
3.					
4.					
5.					

Calculations :Calculate values of Z , $\left(Z = \frac{V}{I} \right)$, resonant frequency, f_r and quality factor Q .**Conclusions :** (i) Resonant frequency f_r depends on the values of L and C .
(ii) Q factor depends upon R .**EXPERIMENT NO. 2****A. Measurement of Power in Single-Phase A.C. Circuit.****Objective.** To measure active and reactive power in a single-phase A.C. circuit.**Material and Equipment required :**

1. Single-phase auto-transformer (10 A, 270 V) 1 No.
2. Dynamometer type wattmeter (10 A, 250 V) 1 No.
3. Moving-iron voltmeter (0—250 V) 1 No.
4. Moving-iron ammeter (0—10 A) 1 No.
5. Resistive and inductive load
6. Connecting leads.

Theory :

In an A.C. circuit the power which is actually consumed is called *active (or true or real) power*. The *power is consumed only in resistance*. The power consumed in inductance and reactance is called *reactive power*; it does not contribute any useful work.

Active or true power = $VI \cos \phi$ ($I \cos \phi$ is the component of current I in phase with voltage)Reactive power = $VI \sin \phi$ ($I \sin \phi$ is the component of current I 90° out of phase with voltage).

3. Triple pole iron clad (TPIC) switch 1 No.
4. Dynamometer type wattmeters (500 V, 10 A), 2 No.
5. Moving-iron voltmeter (0—500 V) 1 No.
6. Moving-iron ammeter (0—10 A) 1 No.
7. Connecting leads.

Theory :

The power of 3-phase, 3 wire star or delta connected, balanced or unbalanced load can be measured by two-wattmeter method. In this method the current coils of the two wattmeters are connected in any two lines and the pressure (or potential) coil of each joined to the third line.

The total active power (P) = sum of the two wattmeters' readings W_1, W_2 i.e., $P = \sqrt{3} V_L I_L \cos \phi$
 $= W_1 + W_2$

$$\text{Power factor of the load, } \cos \phi = \cos \left[\tan^{-1} \left\{ \sqrt{3} \left(\frac{W_1 - W_2}{W_1 + W_2} \right) \right\} \right]$$

$$\text{Also, power factor, } \cos \phi = \frac{W_1 + W_2}{\sqrt{3} V_L I_L}$$

$$\text{Reactive power of the load} = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} (W_1 - W_2).$$

Circuit/Connection diagram :

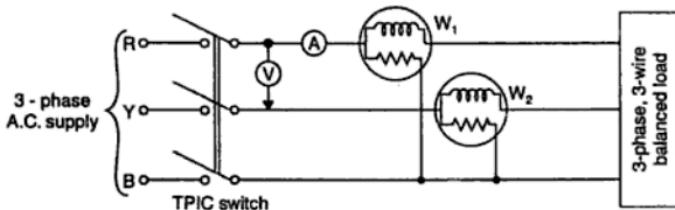


Fig. 9

The connection diagram is shown in Fig. 9.

Procedure :

1. Make the connections as shown in the connection diagram (Fig. 9).
2. Switch-ON the supply through TPIC switch.
3. Switch-ON the load.
4. Note the readings of wattmeters W_1 and W_2 , ammeter A and voltmeter V with different loads (in case of an induction motor the load can be varied by changing the mechanical load on it.) It may be noted that while observing the readings of the two wattmeters, if any one of them gives down scale reading (it happens when the load power factor is below 0.5), switch off the supply and reverse the connections of current coil (CC) or potential coil (PC) of that wattmeter and while doing calculation consider this reading as negative.
5. Note down the readings with their proper signs in the observation table.

Theory :

The no-load current flowing in the transformer lags the induced e.m.f. by an angle slightly less than 90° . The saturation non-linearity results in a family of odd harmonics components in the no-load or exciting current. Consequently, the no-load current has a waveform which is non-sinusoidal in nature ; this can be displayed on a CRO.

Procedure :

1. Connect the primary of the transformer to the single-phase supply with a rheostat or purely resistor as shown in the Fig. 10. Set up the auto-transformer to zero position.
2. Switch-ON the supply, and vary the voltage by auto-transformer.
3. Observe the waveform on CRO.

Conclusion :

- The current wave is non-sinusoidal and peaky while odd symmetry is maintained.
- The current and flux variations occur simultaneously.

EXPERIMENT NO. 4**A. Study of Transformer Name Plate Rating, Determination of Transformation Ratio and Polarity.**

Objective. (i) *Study of transformer name plate rating ;*

(ii) *To measure transformation ratio ;*

(iii) *To find polarity of primary and secondary windings.*

Theory :

(i) The **name plate rating** of a power transformer usually include/indicate the following :

- **kVA rating.** The kVA rating is the kVA output which the transformer can deliver at rated voltage and frequency under usual operating conditions without exceeding the standard limits of temperature rise.

The kVA figure always refers to output kVA appearing at the secondary load terminals ; the input kVA, of course, is slightly higher because of internal losses (core and winding losses).

- **Voltage ratio** = Rated primary voltage/secondary voltage or V_1/V_2 . *Rated secondary voltage* is the voltage that appears across the secondary terminals *when rated current flows*.

Rated primary voltage is equal to the rated secondary voltage multiplied by the turn-ratio between primary and secondary i.e., $V_1 \text{ (rated)} = V_2 \text{ (rated)} \times \frac{N_1}{N_2}$.


- **Frequency.**
- **Number of phases / Type (1-phase or 3-phase).**
- **Equivalent impedance (%)**.

(ii) Transformation ratio.

For an ideal transformer $E_1 = V_1$ and $E_2 = V_2$

(where $E_1 = 4.44 f \phi N_1$ and $E_2 = 4.44 f \phi N_2$)

$$\therefore \text{Transformation ratio (K)} = \frac{E_2}{E_1} = \frac{V_2}{V_1} = \frac{N_2}{N_1}.$$

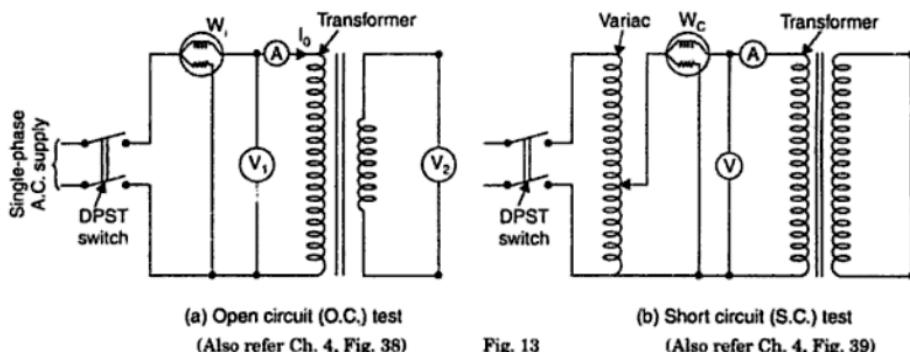Theory and Circuit/Connection diagram :


- **Open-circuit test.** This test is performed to determine the *transformation ratio (K)* and the *iron loss*. It also determines no-load current I_0 which is helpful in finding the no-load parameters R_0 and X_0 of the transformer.

The *transformation ratio*,

$$K = \frac{V_2 \text{ (i.e., secondary voltage on open-circuit)}}{V_1 \text{ (i.e., voltage applied to primary)}}$$

The *iron loss* = wattmeter reading W_i (at open circuit). The wattmeter reading represents practically the core loss (*copper loss being negligibly small*) under no-load conditions and this loss is same for all loads.

Fig. 14 shows the no-load vector diagram

$$W_i = V_1 I_0 \cos \phi_0$$

(I_0 is only 2 to 10 % of the rated full-load current)

$$\therefore \text{No-load power factor, } \cos \phi_0 = \frac{W_i}{V_1 I_0}$$

$$\text{Active or working or iron loss component, } I_w = I_0 \cos \phi_0 = \frac{W_i}{V_1}$$

$$\text{Magnetising component, } I_m = I_0 \sin \phi_0 \quad \text{or} \quad \sqrt{I_0^2 - I_w^2}$$

No-load parameters are :

$$\text{No-load exciting resistance, } R_0 = \frac{V_1}{I_w} \left(= \frac{V_1^2}{W_i} \right)$$

$$\text{No-load exciting reactance, } X_0 = \frac{V_1}{I_m} \left(= \frac{V_1}{\sqrt{I_0^2 - I_w^2}} \right)$$

The iron losses measured by this test are used for calculating the efficiency of the transformer.

- **Short-circuit test.** This test is performed to determine the *full load copper loss*.

Here copper loss = wattmeter reading W_c (at short-circuit). (The wattmeter reading represents full-load copper losses, the iron-loss being negligibly small.)

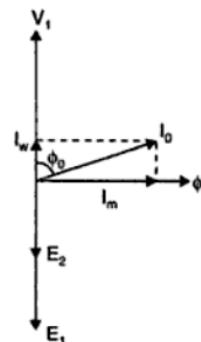


Fig. 14. No-load vector diagram.

Transformer efficiency (η) at any load is given by the relation,

$$\% \text{Efficiency}, \quad \eta = \frac{\text{Output}}{\text{Output} + \text{iron loss} + \text{copper loss at given load}} \times 100$$

where, output = voltmeter reading, V_1 (O.C. test) \times ammeter reading A (S.C. test) \times p.f.

Iron loss = W_i (wattmeter reading at O.C. test)

Copper loss = W_c (wattmeter reading at S.C. test).

Procedure :

Open-circuit (O.C.) test :

1. Make the connections as per the circuit shown in Fig. 13 (a).
2. Switch on the A.C. supply through DPST switch at rated voltage.

Note down the readings of wattmeter W_i (for iron losses), voltmeter readings V_1 and V_2 (for transformation ratio).

3. Switch off the supply.

Short-circuit (S.C.) test :

1. Make the connections as per the circuit shown in Fig. 13 (b).
2. Switch on the A.C. supply through DPST switch to variac.
3. Increase the voltage fed to the primary of the main transformer in steps so that ammeter A carries 0.25, 0.5, 0.75, and 1.5 times the rated current.
- Calculate the efficiency of the transformer at different loads (as mentioned above).
- Plot a curve between load current and efficiency of a transformer.

Observations :

Open-circuit test :

Primary voltmeter reading, $V_1 = \dots$

Secondary voltmeter reading, $V_2 = \dots$

Wattmeter reading, $W_i = \dots$

Transformation ratio, $K = \frac{V_2}{V_1}$

Calculations : $\cos \phi_0 = \frac{W_i}{V_1 I_0} = \frac{\text{Wattmeter reading}}{(\text{Voltmeter} \times \text{ammeter}) \text{ reading}}$

Iron loss = W_i

$\therefore R_0 = \frac{W_i}{I_0^2} \quad \text{or} \quad \frac{V_0}{I_0 \cos \phi_0}, \quad \text{and}$

$X_0 = \frac{V_0}{I_0 \sin \phi_0}.$

S. No.	Voltmeter readings V_i (in volts)	Ammeter readings I_a (in amps.)	Wattmeter readings W_i (in watts)
1.			
2.			
3.			
4.			
5.			

Short-circuit test :

$$\text{Rated primary current, } I = \frac{\text{Rated kVA} \times 1000}{\text{Rated primary voltage } (V_1)} = \dots$$

Power factor, $\cos \phi = 0.8$ lagging.

Calculations :

$$\text{Total resistance as referred to primary sides } R_{01} = \frac{W_{sc}}{I_{sc}^2}$$

$$\text{Total impedance referred to primary side, } Z_{01} = \frac{V_{sc}}{I_{sc}}$$

$$\text{Total reactance referred to primary side, } X_{01} = \sqrt{Z_{01}^2 - R_{01}^2}$$

S. No.	Voltmeter reading (V_{sc} in volts)	Ammeter reading (I_{sc}), in amps.	Wattmeter reading (W_i), in watts	$\% \eta = \frac{V_i I_{sc} \cos \phi}{V_i I_{sc} \cos \phi + W_i + W_c} \times 100$ $= \frac{V_i I_{sc} \times 0.8}{V_i I_{sc} \times 0.8 + W_i + W_c} \times 100$
1.				
2.				
3.				
4.				
5.				

Conclusions :

- Fig. 15 shows a curve between the load current and efficiency of the transformer. It may be observed that the efficiency of the transformer is maximum when $W_c = W_i$.
- With the parameters of equivalent circuit known, draw the equivalent circuit of the transformer referred to primary (Refer Ch. 4, Figs. 35, 36 and 37).

C. Measurement of Efficiency of a Single-phase Transformer by Load Test.

- Objective :** (i) To determine the efficiency ;
(ii) To determine voltage regulation.

Material and equipment required :

- Transformer under test 1 No.
- Auto-transformer 1 No.
- Moving-iron voltmeter 2 No.
- Moving-iron ammeter 2 No.
- Dynamometer type wattmeter 2 No.
- Connecting leads.

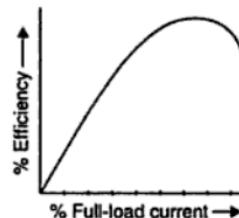


Fig. 15

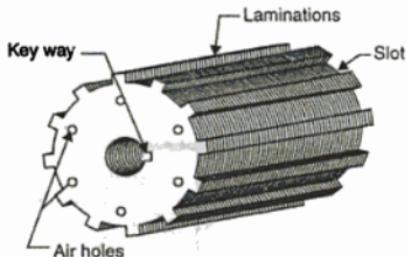


Fig. 19. Armature of a D.C. machine.



Fig. 20. Drum armature stamping with axial flow ventilation system.

- The armature laminations of *medium size machines* (having more than four poles) are built on a spider. The spider may be fabricated. Laminations up to a diameter of about 100 cm are punched in one piece and are directly keyed on the spider (see Fig. 21).

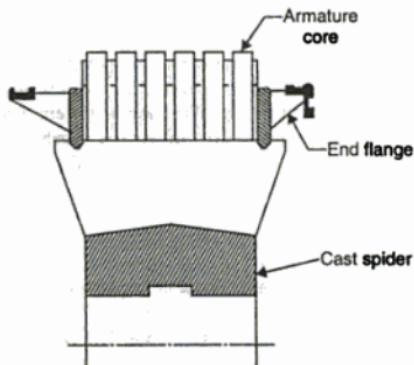


Fig. 21. Clamping of an armature core.

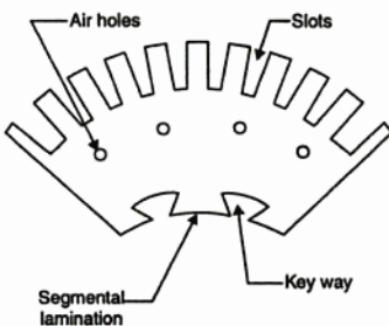


Fig. 22. Segmental stamping.

- In case of *large machines*, the laminations of such thin sections are difficult to handle because they tend to distort and become wavy when assembled together. Hence circular laminations instead of being cut in one piece are cut in a number of suitable sections or *segments* which form part of a complete ring (see Fig. 22). A complete circular lamination is made up of four or six or even eight segmental laminations. Usually two keyways are notched in each segment and are dove-tailed or wedge shaped to make the laminations self-locking in position.
- The armature winding is housed in slots on the surface of the armature. The conductors of each coil are so spaced that when one side of the coil is under a north pole, the opposite is under a south pole.

- For D.C. machines proper current collection at the commutator (i.e., absence of detrimental sparking) must be ensured.

B. No-load Saturation Characteristics (O.C.C.) of a D.C. Shunt Generator.

Objective. (i) To determine the effects of field current (I_f) and speed on the e.m.f. induced in the armature of the generator under no-load condition.

(ii) To determine the critical field resistance.

(iii) To determine the maximum voltage developed by the generator on particular speed.

Material and Equipment required :

- Shunt generator 1 No.
- Moving-coil ammeter 1 No.
- Moving-coil voltmeter 1 No.
- Rheostat 1 No.
- Tachometer (digital) 1 No.
- Connecting leads.

Theory :

The properties of generators are analysed with the aid of characteristics which give the relations between fundamental quantities determining the operation of a generator. These include the voltage across the generator terminals V , the field or exciting current I_f , the armature current I_a , and the speed of rotation N .

The three most important characteristics of D.C. generators are given below :

- No load saturation characteristics $\left(\frac{E_0}{I_f}\right)$
- Internal or total characteristics $\left(\frac{E}{I_a}\right)$
- External characteristics $\left(\frac{V}{I}\right)$.

Separately excited generators :

- Fig. 28 shows the connections of a separately excited generator, a battery being indicated as the source of exciting current, although any other constant voltage source could be used.

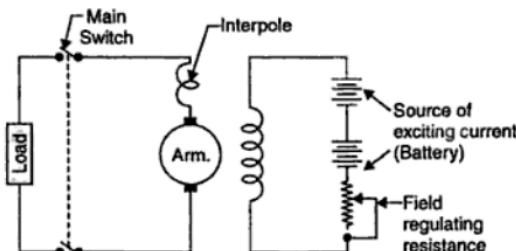


Fig. 28. Connection for a separately excited generator.

The field circuit is provided with a variable resistance and would normally contain a field switch and an ammeter, these being omitted from the diagram for simplicity. The armature is connected through 2-pole main switch to the bus bars, between which the load is connected.

No-load saturation characteristics (or O.C.C.) :

- If the generator is run at constant speed with the main switch open, and the terminal voltage is noted at various values of exciting or field current then the O.C.C. shown in Fig. 29 can be plotted. This is also referred to as the '*magnetisation curve*' since the same graph shows, to a suitably chosen scale, the amount of magnetic flux, there being a constant relationship (depending upon speed of rotation) between flux and induced voltage.
- It will be noticed that a small voltage is produced when the field current is zero, this being due to a small amount of permanent magnetism in the field poles. This is called *residual magnetism* and is usually sufficient to produce 2 or 3 per cent of normal terminal voltage, although in some special cases it is purposely increased to 10 per cent or more.
- The *first part of the curve is approximately straight and shows that the flux produced is proportional to the exciting current*; but after a certain point, *saturation of the iron becomes perceptible as the curve departs from straight line form*.

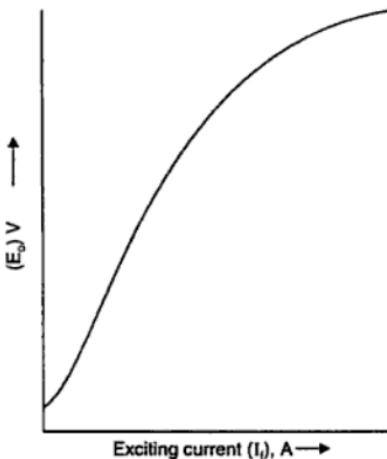


Fig. 29. Open-circuit characteristic of a separately excited generator.

Building up the voltage of self-excited shunt generator :

One of the simplest forms of 'self-excited' generator is the shunt-wound machine, the connection diagram (without load) of which is shown in Fig. 30. The manner in which a self-excited generator manages to excite its own field and build a D.C. voltage across its armature is described with reference to Fig. 31 in the following steps :

- (i) Assume that the generator starts from rest, i.e., prime-mover speed is zero. Despite a residual magnetism, the generated e.m.f. E , is zero.

- Plot a graph between V_t (or E_0) and I_f , which represents the no-load characteristics (O.C.C.) of the generator.
- Draw the field resistance line on the same graph, the point at which resistance line cuts the O.C.C. curve gives the maximum voltage built up by the generator.
- Draw a tangent line to the curve, the slope of this tangent will be the critical resistance of the generator.

C. Load Characteristics of D.C. Shunt Generator.

- Objective.** (i) To obtain and plot the external characteristics of a D.C. shunt generator.
(ii) To deduce the internal characteristics from the above external characteristics.

Material and equipment required :

1. D.C. shunt generator set 1 No.
2. Moving-coil voltmeter 1 No.
3. Moving-coil ammeter 1 No.
4. Loading rheostat 1 No.
5. Field rheostat 1 No.
6. Digital tachometer 1 No.
7. Connecting leads.

Theory :

In a shunt generator, the field circuit is connected directly across the armature. Appliances, motors, light bulbs, and other electrical devices connected in *parallel* across the generator terminals represent a *load* on the generator. As more devices are connected in parallel, the load on the generator increases ; that is, the generator current increases. Because the generator current increases, the terminal voltage of the generator decreases. There are three factors that cause this decrease in voltage :

- (i) Armature-circuit resistance (R_a),
- (ii) Armature reaction, and
- (iii) Reduction in field current.

(i) **Armature-circuit resistance.** The armature circuit of a generator, like every electrical circuit, contains resistance. This resistance includes the resistance of (i) the copper conductors of the armature winding, (ii) the commutator, (iii) contact resistance between brushes and commutator, and (iv) the brushes themselves. When no current flows through the armature, there is no IR drop in the armature and the voltage at the terminals is the same as the generated voltage. However, when there is current in the armature circuit, a voltage drop exists due to the armature resistance, and the terminal voltage is less than the generated voltage. The terminal voltage may be calculated from the following relation :

$$V = E_g - I_a R_a$$

where V = voltage at terminals of generator,

E_g = generated or induced voltage,

I_a = total armature current, and

R_a = armature-circuit resistance.

(ii) **Armature reaction.** When current flows in the armature conductors a flux surrounds these conductors. The direction of this armature flux is such that it reduces the flux from the field poles, resulting in both a reduced generated voltage and terminal voltage.

- Generally, the external load-voltage characteristic decreases with application of load only to a small extent up to its rated load (current) value. Thus, the shunt generator is considered as having a fairly constant output voltage with application of load, and in practice, is rarely operated beyond the rated load current value continuously for any appreciable time.
- As shown in Fig. 34 further application of load causes the generator to reach a breakdown point beyond which further load causes it to 'unbuild' as it operates on the unsaturated portion of its magnetisation curve. This unbuilding process continues until the terminal voltage is zero, at which point the load current is of such magnitude that the internal armature circuit voltage drop equals the e.m.f. generated on the unsaturated or linear portion of its magnetisation curve.
- It may be noted that if the external load is decreased (an increase of external load resistances), the generator will tend to build up gradually along the dashed line shown in Fig. 34. Note that for any value of load current, the terminal or armature voltage is less (as the voltage increases) compared to the solid lines which yield a higher voltage (as the voltage decreases). This difference is due to hysteresis.

Fig. 35 shows the determination of internal characteristics from external characteristics.

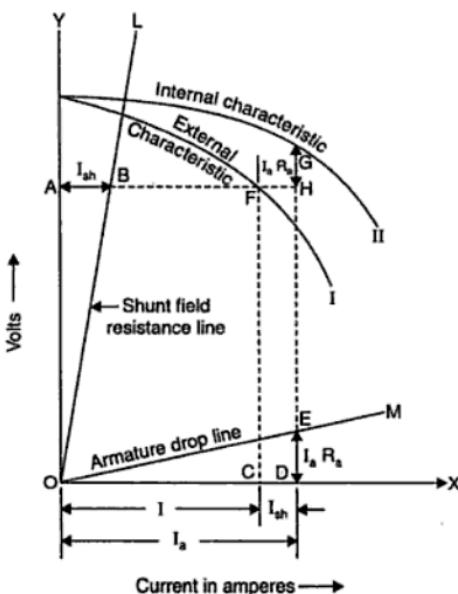


Fig. 35. Determination of internal characteristic from external characteristic.

machine. For this reason, *additional resistance* is introduced into the armature circuit at starting. As the motor gains speed, its back e.m.f. builds up and the starting resistance is cut out.

Note. Very small D.C. motors, either shunt, series or compound wound, have sufficient armature resistance so that they may be started directly from the line without the use of a starting resistance and without injury to the motor.

Fig. 37 shows the connections of a starting resistance in three types of D.C. motors :

- (a) A series motor ;
- (b) A shunt motor ; and
- (c) A compound motor.

- In the case of *series motor* [Fig. 37 (a)], the armature, field and starting resistance are all in series.

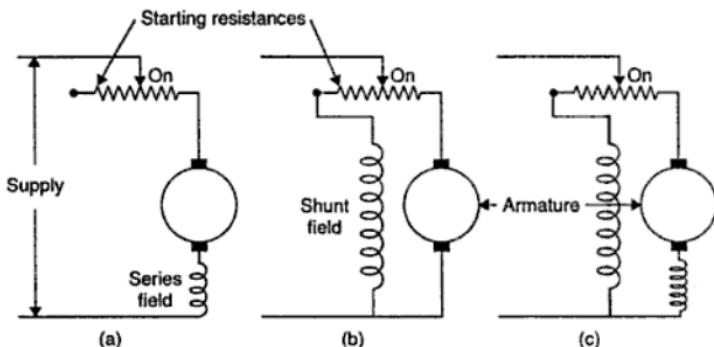


Fig. 37. Circuits incorporating starting resistances.

- In the case of *shunt motor* [Fig. 37 (b)], it will be seen that the *top end of shunt field is connected to the first contact on the starting resistance*. This is to ensure that the *field winding receives the full supply at the moment of switching on*. If the fields were connected to the *last stud of the starting resistance*, then on starting, the field would receive only a *proportion of the supply voltage*, the *field current would be correspondingly weak and the torque might be too small to start the motor against the friction of the moving parts*.
- The connections for the *compound motor* are seen from [Fig. 37 (c)] to be a combination of those of the *series* and the *shunt* connections.

Starters for shunt and compound motors :

- The starters of D.C. motors are generally manufactured in convenient sizes and styles for use as auxiliaries with D.C. shunt and compound motors. Their primary function is to limit the current in the armature circuit during the starting accelerating period.
- The motor starters are always rated on the basis of output power and voltage of the motors with which they are to be used.
- There are two standard types of motor starters for shunt and compound motors. These are :

- (i) Three-point type ; and
- (ii) Four-point type.

Three-point starters are not completely satisfactory when used with motors whose speeds must be controlled by inserting resistance in the shunt field circuit. However, when applications require little or no speed control, either may be employed.

ABOUT THE BOOK

This book on "Electrical Technology" has been specifically written for B.E. First year examination of K.U. Kurukshetra, GJU, Hisar & M.D.U. Rohtak, Haryana, strictly according to the *latest syllabus*. It consists of 7 chapters in all, covering exhaustively the various topics in different chapters of the complete syllabus. Besides this the book also contains "*Laboratory Practicals*" to apprise the students about the practical aspects of the subject.

Salient Features :

- The presentation of the subject matter is very systematic and the language of text is lucid, direct and easy to understand.
- Each chapter of book is saturated with much needed text supported by neat and self-explanatory diagrams to make the subject self-speaking to a great extent.
- A large number of solved examples, properly graded, have been added in various chapters to enable the students to attempt different types of questions in the examination without any difficulty.
- At the end of each chapter *Highlights*, *Objective Type Questions*, *Theoretical Questions* and *Unsolved Examples* have been added to make the book a complete unit in all respects.

ABOUT THE AUTHOR

Er. R. K. Rajput, born on 15th September, 1944 (coincident with Engineer's Day) is a multi-disciplinary engineer. He obtained his *Master's degree in Mechanical Engineering* (with Hons.-Gold Medal) from Thapar Institute of Engineering and Technology, Patiala. He is also a *Graduate engineer in Electrical Engineering*. Apart from this he holds memberships of various professional bodies like Member Institution of Engineers (MIE); Member Indian Society of Technical Education (MISTE) and Member Solar Energy Society of India (MSESI). He is also Chartered Engineer (India). He has served for several years as Principal of "Punjab College of Information Technology", Patiala and "Thapar Polytechnic, Patiala".

He has more than 35 years of experience in teaching different subjects of Mechanical and Electrical Engineering disciplines. He has published/presented a large number of technical papers. He is the author of several books on the important subjects of Mechanical as well as Electrical Engineering disciplines.

He has earned, by dint of hard work and devotion to duty, the following awards/honours.

**Best Teacher (Academic) Award* * *Jawahar Lal Nehru Memorial Gold Medal for an outstanding research paper (Institution of Engineers)* * *Distinguished Author Award* * *Man of Achievement Award*



ISBN : 81-7008-617-5



9 788170 086178

LAXMI PUBLICATIONS (P) LTD