

Module III

AC Fundamentals

Alternating Quantity

Any quantity whose magnitude has alteration value with respect to time .

Wave form

Shape of the curve obtained when we plot the values of alternative quantity with time .

Instantaneous value .

Value/magnitude of a quantity at any instant of time .

Cycle .

Each repetition of a set of values .

Half cycle .

One set of positive value or one set of negative value of a symmetric waveform .

Time interval (T)

- Fixed interval at which values are repeated .
- Time taken to complete one cycle .

Frequency

- No. of cycles per second .
- $f = 1/T$

Angular velocity (ω)


Speed at which rotates

$$\omega = \frac{2\pi}{T} = 2\pi f$$

Peak value

Maximum instantaneous value (+ve or -ve) of a symmetric waveform is called peak value .

Peak to peak

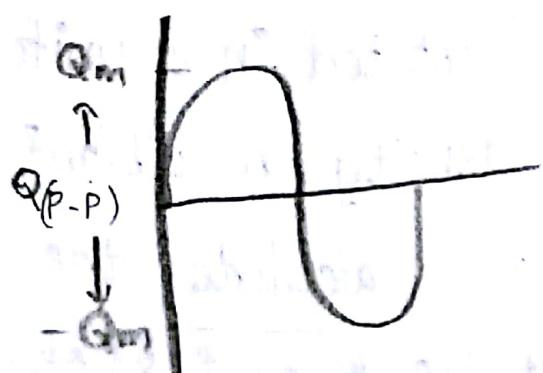

Distance b/w ^{+ve} maximum and -ve max value .

$$Q_{(P-P)} = 2Q_P$$

Equations of Alternating Current & Voltage

$$\phi = \phi_m \cos \theta .$$

$$e = -\frac{d}{dt} (N\phi)$$

$$= -\frac{d}{dt} (N \phi_m \cos \theta) \quad \theta = \omega t .$$

$$= -N \frac{d}{dt} \phi_m \cos \omega t$$

$$= \omega N \phi_m \sin \omega t$$

When $\sin \omega t = 1$

A rectangular coil of size 5cm x 10cm has 50 turns. The coil is rotated in a uniform magnetic field of flux density 0.1 wb/m² at a speed of 1000 rpm. Calculate the maximum pmf and the emf at the instant when the

plane of coil makes an angle of 45° to the field direction.

$$A = 5 \times 10 \text{ cm}$$

$$= 50 \text{ cm}^2$$

$$N = 50$$

$$B = 0.1 \text{ wb/m}^2$$

$$\text{Speed} = 1000 \text{ rpm}$$

$$\theta = 45^\circ$$

$$E_m = (2\pi f)N(BA) \quad (\because \omega = 2\pi f \text{ & } \phi = BA)$$

$$f = \frac{1000}{60} \text{ cycles/s or Hz}$$

$$E_m = 2 \times 3.14 \times \frac{100}{6} \times 50 \times 0.1 \times 5 \times 10^{-2}$$

$$= \underline{\underline{2.62}}$$

$$e = E_m \sin \theta$$

$$= 2.62 \times \sin 45^\circ$$

$$= \underline{\underline{1.85V}}$$

An AC of frequency 60Hz has maximum value of 120A. Find equⁿ of its instantaneous value. Also calculate instantaneous value after $\frac{1}{360}$ s and time taken to reach 96A after first time after 0 crossing.

$$f = 60\text{Hz} \quad I = 120\text{A} \quad \omega = 2\pi \times 60 \\ = 120 \times 3.14$$

i) $i = I_m \sin \omega t$

$$= 120 \sin(120\pi t)$$

ii) $i = I_m \sin \omega t$

$$= 120 \sin\left(120\pi \frac{1}{360}\right)$$

$$= 120 \sin \pi/3$$

$$= 120 \times \frac{\sqrt{3}}{2} = 60\sqrt{3} = \underline{\underline{103.92\text{A}}}$$

$$96 = 120 \times \sin(120\pi t)$$

$$\frac{96}{120} = \sin(120\pi t)$$

$$\sin^{-1}\left(\frac{96}{120}\right) = 120\pi t$$

$$t = \frac{53.13}{120 \times 3.14} \times \frac{1}{180} = \underline{\underline{0.141602.45\text{ms}}}$$

RMS value

square root of mean of squares of value .

That value of dc current which produces same heating effect as ac in the circuit is same resistance and time .

$$I_{dc} \cdot R t = \frac{i_1^2 R t + i_2^2 R t + \dots + i_n^2 R t}{n}$$

$$I_{dc}^2 = \frac{i_1^2 + i_2^2 + \dots + i_n^2}{n}$$

$$I_{dc} = \sqrt{\frac{i_1^2 + i_2^2 + i_3^2 + \dots + i_n^2}{n}}$$

$$V_{Rms} = \sqrt{\frac{V_1^2 + V_2^2 + \dots + V_n^2}{n}}$$

RMS of sinusoidal AC .

$$i = I_m \sin \theta$$

$$\text{RMS} = \sqrt{\int_0^{2\pi} \frac{i^2}{2\pi - 0} d\theta}$$

$$\sqrt{\int_0^{2\pi} \frac{I_m^2 \sin^2 \theta}{2\pi} d\theta}$$

$$\sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} \sin^2 \theta d\theta}$$

$$\sqrt{\frac{I_m^2}{2\pi} \int_0^{2\pi} f(1 - \cos^2 \theta) d\theta}$$

$$\sqrt{\frac{I_m^2}{4\pi} \int_0^{\pi} 1 - \cos 2\theta}$$

$$\sqrt{\frac{I_m^2}{4\pi} \left[\theta \right]_0^{2\pi} - \left[\frac{\sin 2\theta}{2} \right]_0^{2\pi}}$$

$$= \frac{I_m}{2} \sqrt{\frac{1}{\pi} [2\pi - 0]}$$

$$= \frac{I_m}{\sqrt{2}}$$

$$P = I_{rms}^2 R$$

$$= \left(\frac{I_m}{\sqrt{2}} \right)^2 R = \frac{I_m^2 R}{2}$$

Average value of sinusoidal ac

\Rightarrow dc which produces the same charge
as that of ac.

$$I_{av} \rightarrow \frac{i_1 + i_2 + \dots + i_n}{n}$$

$$I_{av} = \int_0^{\pi} \frac{i}{\pi} d\theta$$

$$= \int_0^{\pi} \frac{I_m \sin \theta}{\pi} d\theta$$

$$= \frac{I_m}{\pi} \int_0^{\pi} \sin \theta d\theta$$

$$= \frac{I_m}{\pi} [-\cos \theta]_0^{\pi}$$

$$= \frac{I_m}{\pi} [-\cos \pi + \cos 0]$$

$$= \frac{I_m}{\pi} [1 + 1]$$

$$I_{av} = \frac{2I_m}{\pi}$$

$$\underline{\underline{}}$$

$$\text{Form factor} = \frac{\text{RMS value}}{\text{Avg value}}.$$

$$J = \frac{I_m / \sqrt{2}}{2 I_m / \pi}$$

$$= \underline{1.11}$$

$$I_{\text{RMS}} = 1.11 \times \text{Avg value.}$$


$$\text{Peak factor} = \frac{\text{Max. value}}{\text{RMS value}}$$

$$= \frac{I_m}{I_m / \sqrt{2}} = \sqrt{2} = \underline{1.414}$$

$$\text{Power Factor} = \cos \phi$$

ϕ = Phase dif b/w voltage & current

Half Wave Rectifier

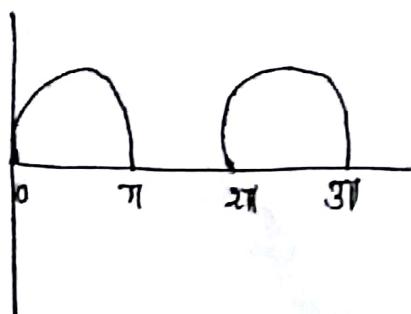

$$I_{ms} = \sqrt{\int_0^{\pi} \frac{i^2}{2\pi} d\theta}$$

$$= \sqrt{\int_0^{\pi} \frac{I_m^2 \sin^2 \theta}{2\pi} d\theta}$$

$$= \sqrt{\frac{I_m^2 \pi}{2\pi} \int_0^{\pi} \sin^2 \theta d\theta}$$

$$= \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \left(1 - \frac{\cos 2\theta}{2}\right) d\theta}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\theta - \frac{\sin 2\theta}{2} \right]_0^{\pi}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \left[\pi - \frac{\sin 2\pi}{2} \right]}$$

$$= \sqrt{\frac{I_m^2}{4\pi} [\pi]}$$

$$= \underline{\underline{\frac{I_m}{2}}}$$

$$I_{avg} = \frac{\pi}{2} \int_{-\pi/2}^{\pi/2} I_m \sin \theta d\theta$$

$$= \frac{\pi}{2} \int_0^{\pi} I_m \sin \theta d\theta$$

$$= \frac{I_m}{2\pi} [-\cos \theta]_0^\pi$$

$$= \frac{I_m}{2\pi} [-\cos \pi - \cos 0]$$

$$= \frac{I_m}{2\pi} 2 = \frac{2I_m}{2\pi} = \underline{\underline{\frac{I_m}{\pi}}}$$

Find the form factor of half-wave rectified ac.

$$\text{Form factor} = \frac{\text{RMS}}{\text{Avg}}$$


$$= \frac{I_m/2}{I_m/\pi}$$

$$= \underline{\underline{\frac{\pi/2}{1}}} = \underline{\underline{1.57}}$$

Find the average value, effective value and form factor of full wave rectified sine wave.

aw - Tooth Waveform

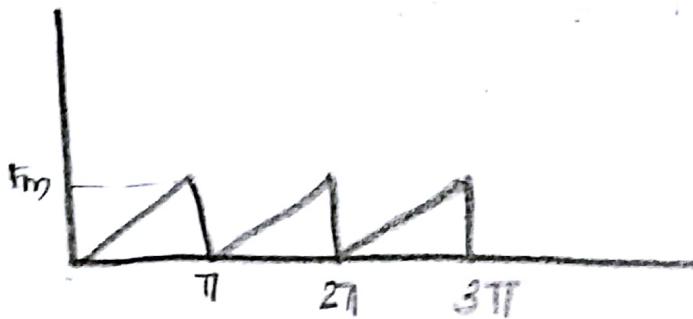calculate average, RMS value and form factor.



$$e = m \theta = \frac{Em}{\pi} \theta$$

$$y = mx$$

$$m = y/x = \frac{Em}{\pi}$$

$$E_{rms} = \sqrt{\int_0^{\pi} \frac{e^2}{\pi} d\theta}$$
$$= \sqrt{\int_0^{\pi} \frac{Em^2 \theta^2}{\pi^3} d\theta}$$

$$= \sqrt{\frac{Em^2}{\pi^3} \int_0^{\pi} \theta^2 d\theta}$$

$$= \sqrt{\frac{Em^2}{\pi^3} \left[\frac{\theta^3}{3} \right]_0^{\pi}}$$

$$= \sqrt{\frac{Em^2}{3\pi^3} [\pi^3 - 0]} = \underline{\underline{\frac{Em}{\sqrt{3}}}}$$

E_{avg} = Area under the wave over the first cycle.

$$= \frac{\frac{1}{2}bh}{\text{base}} = \frac{\frac{1}{2}\pi E_m}{\pi}$$

$$= \frac{E_m}{2}$$

$$\text{Form factor} = \frac{R_{MS}}{Avg}$$

$$= \frac{E_m / \sqrt{3}}{E_m / 2}$$

$$= \frac{2}{\sqrt{3}} = \underline{\underline{1.154}}$$


$$\text{Peak factor} = \frac{E_m}{E_{rms}}$$

$$= \frac{E_m}{E_m / \sqrt{3}}$$

$$= \sqrt{3} = \underline{\underline{1.732}}$$

Find freq., wave equation, V_{rms} , V_{avg} & Kf

(a) Freq =

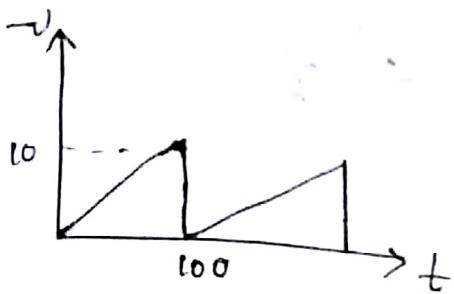


$$\text{Freq} = \frac{1}{T} = \frac{1}{100} = 0.01 \text{ Hz}$$

$$V = m\theta$$



$$= \frac{Vm}{100} = \frac{10}{100} = \underline{\underline{1}}$$

$$V_{rms} = \frac{Em}{\sqrt{3}} = 10/\sqrt{3} = 5.773 \text{ V}$$
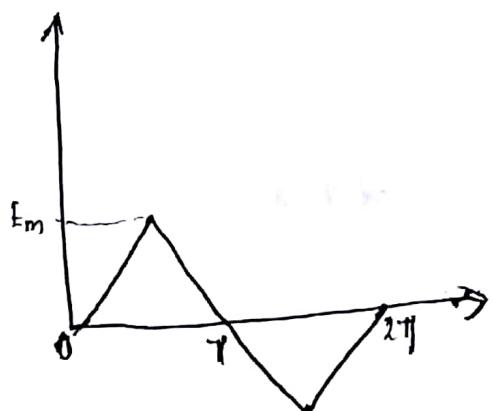
$$V_{avg} = \frac{Em}{2} = \frac{10}{2} = \underline{\underline{5V}}$$



Find form factor.

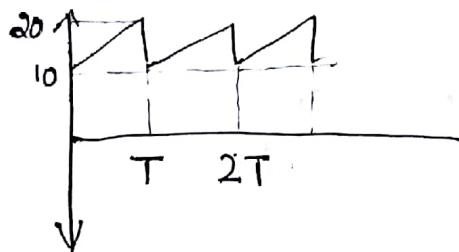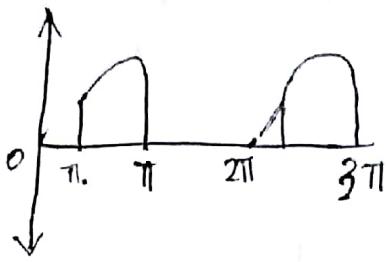

$$y = mt + c$$

$$= \left(\frac{y_2 - y_1}{x_2 - x} \right) t + c$$

$$= \left(\frac{20 - 10}{T - 0} \right) t + 10$$



$$= \frac{10}{T} t + 10$$

$$y_{\text{avg}} = \int_0^T \frac{y}{T} dt \approx 15$$

$$y_{\text{rms}} = \sqrt{\int_0^T \frac{y^2}{T} dt} = 15.275$$


$$k_f = 1.018$$

Phasor

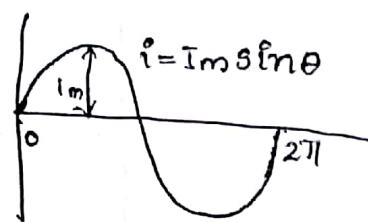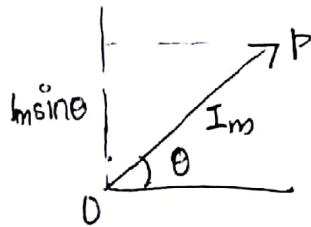

Phasor Algebra .

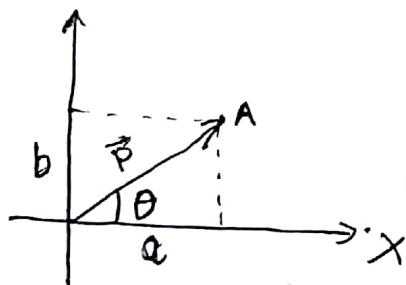
1. Rectangular (cartesian) form .
2. Trigonometric form .
3. Exponential form .
4. Polar form .




$$\vec{P} = a + jb$$

$a \rightarrow$ inphase component


$b \rightarrow$ quadrature component .

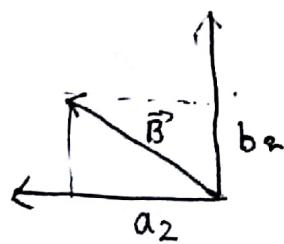


$$\vec{B} = -a_2 + jb_2$$

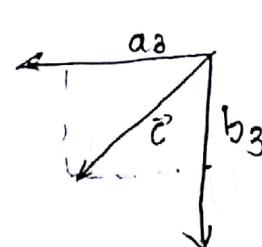

$$\vec{C} = -a_3 - jb_3$$

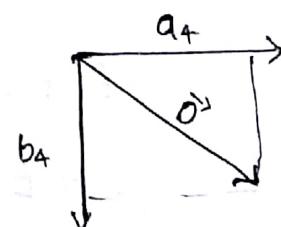

$$\vec{D} = a_4 - jb_4$$

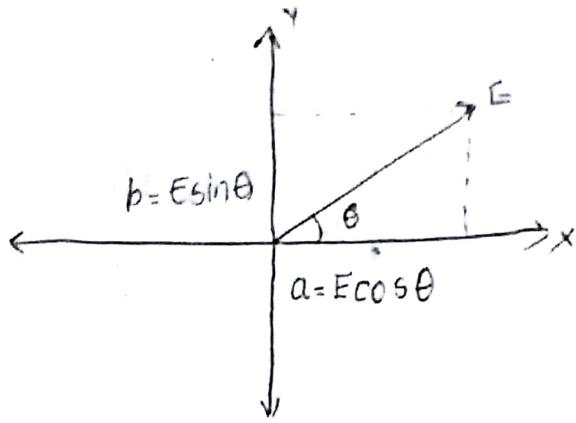

$$\vec{E} = E \cos \theta + j E \sin \theta \\ (\vec{E} = a + jb)$$

$$\vec{E} = 3 + j4$$

$$|E| = \sqrt{4^2 + 3^2} = 5$$

$$\theta = \tan^{-1}(4/3) = 53$$

$$\vec{E} = E \cos \theta + j E \sin \theta \\ = 5 \cos 53 + j 5 \sin 53$$

$$\cos \theta + j \sin \theta = e^{j\theta}$$

$$\cos \theta - j \sin \theta = e^{-j\theta}$$


$$\vec{E} = E \cos \theta + j E \sin \theta \\ = E (\cos \theta + j \sin \theta) \\ = E e^{j\theta}$$

Polar form

$$\vec{E}_1 = |E| \angle +\theta$$

E angle θ

$$E_2 = E \angle -\theta$$

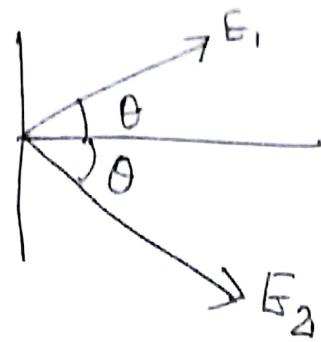

$$E = \sqrt{x^2 + y^2}$$

$$\theta = \tan^{-1} \frac{y}{x}$$

$$\vec{E}_1 + \vec{E}_2 = (a_1 + a_2) + j(b_1 + b_2)$$

$$\vec{E}_1 - \vec{E}_2 = (a_1 - a_2) - j(b_1 - b_2)$$

$$\begin{aligned} E_1 \times E_2 &= a_1 a_2 + j a_1 b_2 + j a_2 b_1 + j^2 b_1 b_2 \\ &= E_1 E_2 \angle (\theta_1 + \theta_2) \end{aligned}$$

$$\frac{E_1}{E_2} = \frac{(a_1 + jb_1)}{(a_2 + jb_2)} \times \frac{(a_2 - jb_2)}{(a_2 - jb_2)} = \frac{E_1}{E_2} \angle \theta_1 - \theta_2$$

Prob

Q. $A = 16 + j12$ $B = -6 + j10$

- i) Find $A+B$, $A-B$, AB & $\frac{A}{B}$ in rectangular form & polar form.
- ii) Find polar forms of A and B .

$$A + B = 10 + j22$$

$$A - B = 22 + 2j$$

$$AB =$$

$$A = \sqrt{16^2 + 12^2} = 20$$

$$B = \sqrt{6^2 + 10^2} = 11.6$$

Polar form

$$A = 20 < 37^\circ$$


$$B = 11.6 < 59^\circ$$

$$AB = 233 < 96^\circ$$

$$\frac{A}{B} = 1.715 < -29^\circ$$

$$A+B = \sqrt{10^2 + 22^2} < \tan^{-1}\left(\frac{22}{10}\right)$$
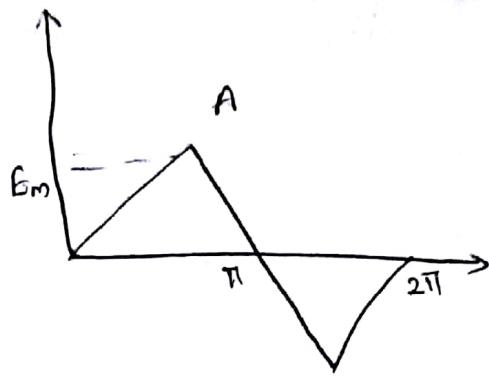
$$A-B = \sqrt{22^2 + 2^2} < \tan^{-1}\left(\frac{2}{22}\right) =$$




$$E_{avg} = \frac{E_m \times 2\theta}{\pi}$$

$$E_{rms} = \frac{2}{\sqrt{3}} E_m$$

$$E_{avg} = E_m$$

$$\text{Peak factor} = \frac{\sqrt{3}/2}{\underline{\underline{2}}}$$
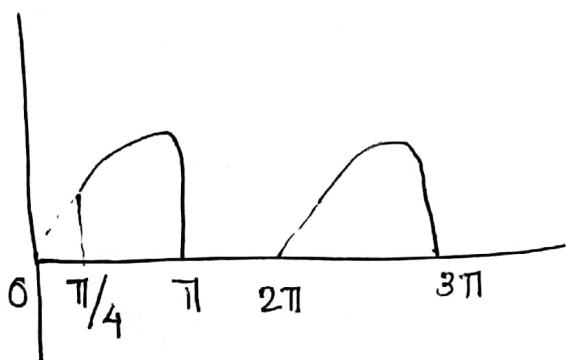
$$\text{Form factor} = \frac{2/\sqrt{3}}{\underline{\underline{2}}}$$



$$\dot{I} = I_m \sin \theta$$

$$I_{rms} = \sqrt{\frac{\int_{\pi/4}^{\pi} I_m^2 \sin^2 \theta d\theta}{2\pi}}$$

$$= \sqrt{\frac{I_m^2}{4\pi} \int_{\pi/4}^{\pi} (1 - \cos 2\theta) d\theta}$$

$$\frac{Im}{2} \sqrt{\frac{1}{\pi} \left(\frac{3\pi}{4} + \frac{1}{2} \right)}$$

$$= \frac{Im}{2} \sqrt{\frac{3}{4} + \frac{1}{2\pi}}$$

$$= (-\cos \theta)_{\pi/4}^{\pi} \times \frac{Im}{2\pi}$$


$$= \frac{Im}{2\pi} \left(1 + \frac{1}{\sqrt{2}} \right)$$

$$FF = \pi \sqrt{\frac{3}{4} + \frac{1}{2\pi}} \\ \frac{1}{1 + \frac{1}{\sqrt{2}}}$$

$$PK = \frac{2}{\sqrt{\frac{3}{4} + \frac{1}{2\pi}}}$$

Power in AC circuits

AC through resistance

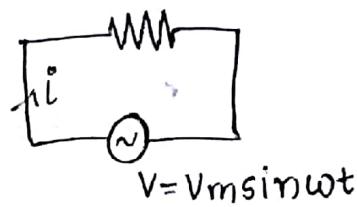


$$V = V_m \sin \omega t$$

$$V = V_m \sin \omega t = iR$$

$$i = \frac{V_m}{R} \sin \omega t$$

$$= I_m \sin \omega t$$

where $I_m = \frac{V_m}{R}$

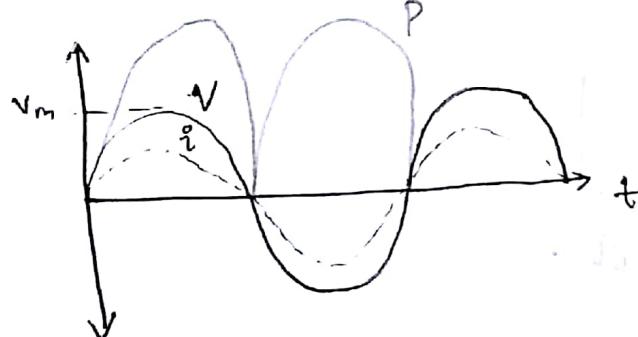

Time diagram

Phasor diagram



$$\text{Power}, P = Vi$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t$$

$$= \frac{V_m I_m}{2} (1 - \cos 2\omega t)$$

* Vector - Vector (Complex)

$$= \begin{pmatrix} V_m \cos \theta \\ V_m \sin \theta \end{pmatrix}$$


$$\left[\sin^2 \theta = 1 - \frac{\cos^2 \theta}{2} \right]$$

$$P_{avg} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$P = VI$$

$$= IR^2$$

AC through pure Inductor,

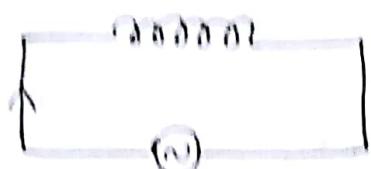

$$V = V_m \sin \omega t$$

$$V = L \frac{di}{dt} = V_m \sin \omega t$$

$$di = \frac{V_m}{L} \sin \omega t dt$$


$$\int di = \int \frac{V_m}{L} \sin \omega t dt$$

$$I = \frac{V_m}{L} \left(-\frac{\cos \omega t}{\omega} \right)$$

$$= \frac{V_m}{L\omega} (\sin(\omega t - \pi/2))$$


where $L\omega = X_L$ and it is called inductive reactance.

$$i^* = I_m \sin(\omega t - \pi/2)$$

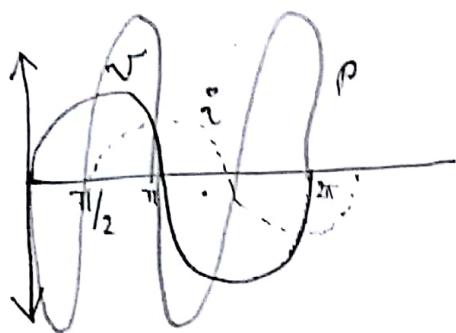

Current lags behind Voltage.

Phasor diagram -

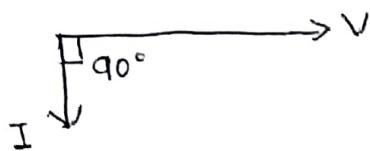

$$P = V_m \sin \omega t \cdot I_m \sin(\omega t - \pi/2)$$

$$= V_m I_m \sin \omega t \cdot -\cos \omega t$$

$$= -V_m I_m \sin \omega t \cdot \cos \omega t$$

$$= -\frac{V_m I_m}{2} \sin 2\omega t$$


$$\boxed{\sin 2\theta = 2 \sin \theta \cos \theta}$$

Power in induction circuit is zero. Why?

$$P_{avg} = \int_0^T -\frac{V_m I_m}{2} \sin 2\omega t$$

$$= \underline{0}$$

AC through capacitance

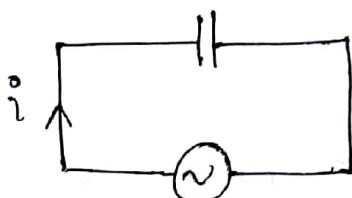

$$v = V_m \sin \omega t$$

$$v = V_m \sin \omega t$$

$$q = CV$$

$$i = \frac{dq}{dt}$$

$$= \frac{d}{dt} CV$$

$$= C \frac{dv}{dt}$$

$$= C \frac{d}{dt} (V_m \sin \omega t)$$

$$= C V_m \cos \omega t \cdot \omega$$


$$= C \omega V_m \sin(\omega t + \pi/2)$$

$$= \frac{V_m}{\frac{1}{C\omega}} \sin(\omega t + \pi/2)$$

$$= i_m \sin(\omega t + \pi/2)$$

~~Time~~ $\frac{1}{C\omega} = x_c$ and it is called capacitive reactance.

Time diagrams:

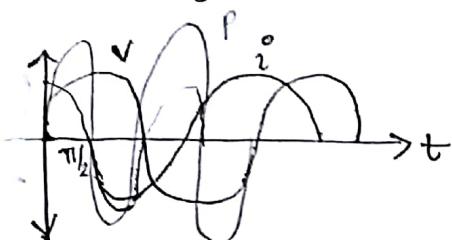

Current is ahead of voltage.

Phasor diagrams:



$$P = Vi$$

$$= V_m \sin \omega t \cdot i_m \sin(\omega t + \pi/2)$$

$$= V_m i_m \sin \omega t \sin(\omega t + \pi/2)$$


$$= V_m i_m \sin \omega t \cos \omega t$$

$$= \frac{V_m i_m}{2} \sin 2\omega t$$

$$P_{avg} = \int p = \underline{0}$$

AC series current

R-L circuit

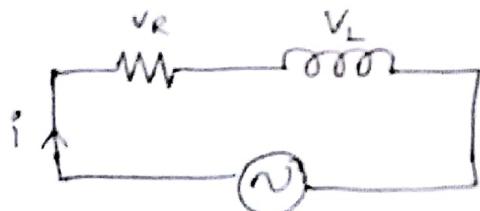

$$V_R = IR$$

$$V_L = jI X_L$$

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

~~in R & in L~~

$$V = \sqrt{V_R^2 + V_L^2}$$


$$= \sqrt{(IR)^2 + (IX_L)^2}$$

$$= I \sqrt{R^2 + X_L^2}$$

$$V = IR + jIX_L = I(R + jX_L)$$

$$I = \frac{V}{R + jX_L} = \frac{V}{Z}$$

$Z \rightarrow$ Impedance (Ω)

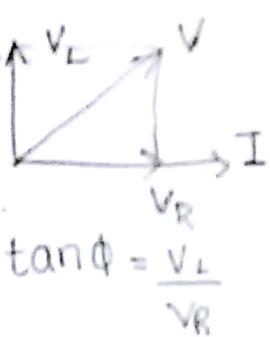

$$\phi = \tan^{-1} \left(\frac{V_L}{V_R} \right)$$

$$\phi = \tan^{-1} \left(\frac{X_L}{R} \right)$$



21

$$|Z| = \sqrt{R^2 + X_L^2}$$

An inductive circuit draws 10A and 1kW from 200V, 50Hz AC circuit. Determine the impedance of the circuit

$$Z = \frac{V_{rms}}{I} = \frac{200}{10} = \underline{\underline{20\Omega}}$$

Impedance Triangle

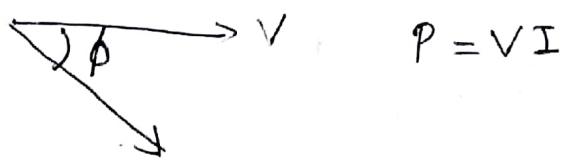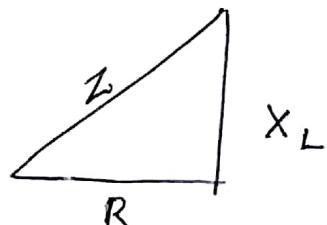

$\phi \rightarrow$ Power factor angle

$\cos \phi \rightarrow$ Power factor

Apparent power $S = V \times I$

Actual (Real/Active/True) Power = $VI \cos \phi$


Reactive Power

Power in the inductive component or reactant


$$Q = VI \sin \phi \quad \text{VAR (or KVAR)}$$

$P = VI \cos \phi$
$Q = VI \sin \phi$
$S = VI$

Power triangle

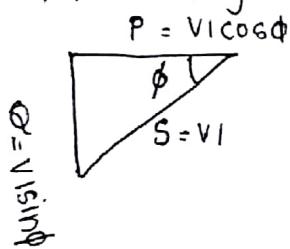

R - C Circuit

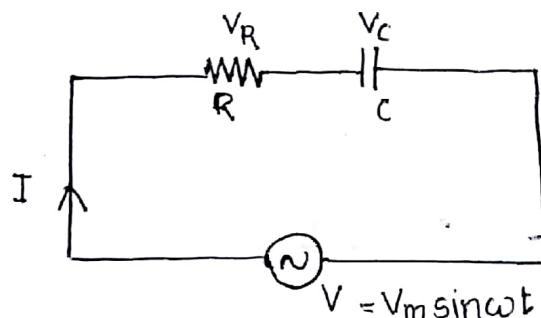

$$V_R = IR$$


$$V_C = I X_C$$

$$\vec{V} = \vec{V}_R + \vec{V}_C$$

$$\vec{V} = IR - j I X_C$$

$$= I (R - j X_C)$$
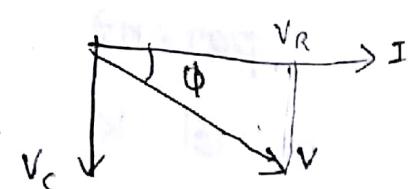
$$X_C = \frac{1}{C\omega} = \frac{1}{2\pi f C}$$



Current leads voltage by 90° .

$$I = \frac{V}{R - jX_C} = \frac{V}{Z}$$

$$Z = R - jX_C$$

$$= R + \frac{1}{j\omega C}$$



$$P \cdot f = \cos \phi = R/Z$$

$$P = VI \cos \phi$$

$$= \cancel{I} Z \times \underline{\underline{IR}} \frac{Z}{Z}$$

$$= \underline{\underline{I^2 R}}$$

R - L - C circuit

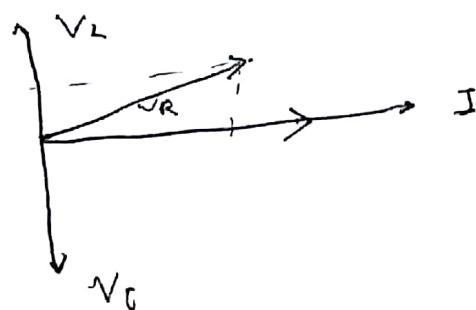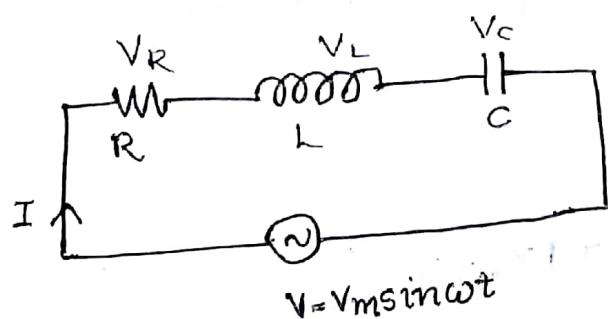

$$V_R = IR$$

$$V_L = IX_L$$

$$V_C = IX_C$$

$$\vec{V} = \vec{V}_R + \vec{V}_L + \vec{V}_C$$

$$= \vec{I}R + \vec{I}X_L + j\vec{I}X_C$$

$$\vec{V} = \vec{I} (R + j(X_L - X_C))$$

$$\vec{V} = \vec{I} Z$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

Current will lead when capacitance is high

Current will lag when inductance is high

$$I = \frac{V}{Z} = \frac{V}{\sqrt{R^2 + (X_L - X_C)^2}}$$

When $X_L = X_C$

$$Z = \underline{\underline{R}}$$

$$I = V/R$$

$$X_L = \omega L = 2\pi f L$$


$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

$$X_L = X_C$$

$$2\pi f_r L = \frac{1}{2\pi f_r C}$$

$$f_r = \frac{1}{2\pi \sqrt{LC}}$$

Resonant frequency.

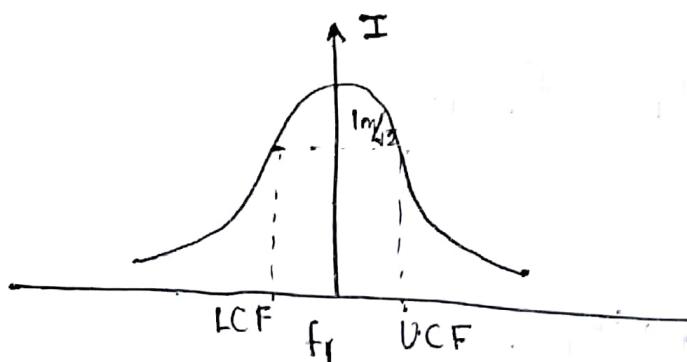

It is called half power frequency

$$P_{max} = I_m^2 R$$

$$P_{h.p} = \left(\frac{I_m^2}{\sqrt{2}} \right) R$$

$$= \frac{I_m^2 R}{2}$$

$$= \frac{P_{max}}{2}$$

Quality factor = $\frac{\text{Reactive Power}}{\text{Avg Power}}$

$$Q = \frac{I^2 X_L}{I^2 R} \quad \text{or} \quad \frac{I^2 X_C}{I^2 R}$$

$$Q = \frac{X_L}{R} \quad \text{or} \quad \frac{X_C}{R}$$

$$= \frac{\omega L}{R} \quad \text{or} \quad \frac{1}{C\omega R}$$

$$= \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{f_r}{B_w}$$


$Y \rightarrow \text{Admittance}$
 $G \rightarrow \text{Conductance}$
 $B \rightarrow \text{Susceptance}$

$$Y = G + jB$$

$$\frac{1}{Z} \rightarrow \text{Admittance}$$


$$B_w = f_2 - f_1 = f_{UCF} - f_{LCF}$$

Parallel AC circuits

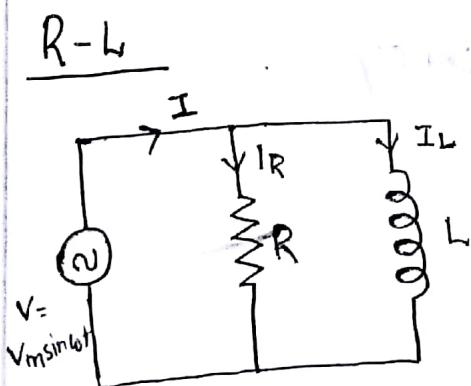

$$\vec{I} = \vec{I}_R + \vec{I}_L$$
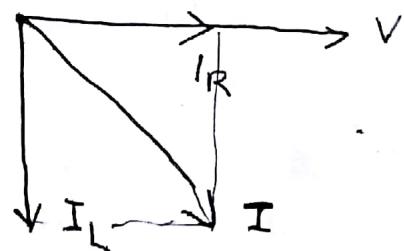
$$= \frac{\vec{V}}{R} + \frac{\vec{V}}{X_L}$$



$$= \frac{\vec{V}}{R} - j \frac{V}{X_L}$$

$$= V \left(\frac{1}{R} - j \frac{1}{X_L} \right)$$

$$= V \left(\frac{1}{R} + \frac{1}{j\omega L} \right)$$


$$Z = \frac{1}{\left(\frac{1}{R} - j \frac{1}{X_L} \right)}$$

$$\frac{1}{Z} = \frac{1}{R} - j \frac{1}{X_L} = Y$$

$$\phi = \tan^{-1} \frac{I_L}{I_R} = \tan^{-1} \frac{V_{L2}}{V_R}$$

$$= \tan^{-1} R/X_L = \tan^{-1} (\%_L \omega)$$

R-C Circuit

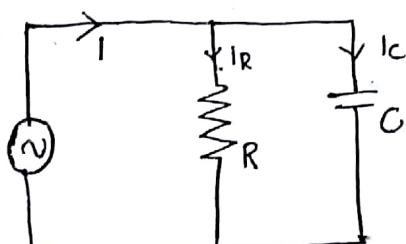

$$\vec{I} = \vec{I}_R + \vec{I}_C = \frac{V}{R} + j \frac{V}{X_C} = V \left(\frac{1}{R} + j \frac{1}{X_C} \right) = Y_Z = VY$$

$$Z = \sqrt{\left(\frac{1}{R} + j\frac{1}{X_C}\right)} \quad \left(\frac{1}{R} + j\omega C\right)$$

$$|Z| = \sqrt{\frac{1}{R^2} + \frac{1}{X_C^2}}$$


$$\tan \phi = \frac{1_c}{1_R}$$

$$\phi = \tan^{-1}\left(\frac{1_c}{1_R}\right)$$

$$= \tan^{-1}\left(\frac{\cancel{X}_c}{\cancel{R}}\right)$$


$$= \tan^{-1}(\omega C R)$$

R - L - C Circuit

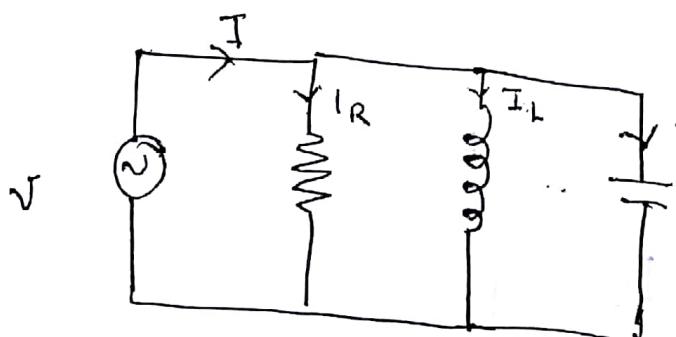

$$I = I_R + I_L + I_C$$
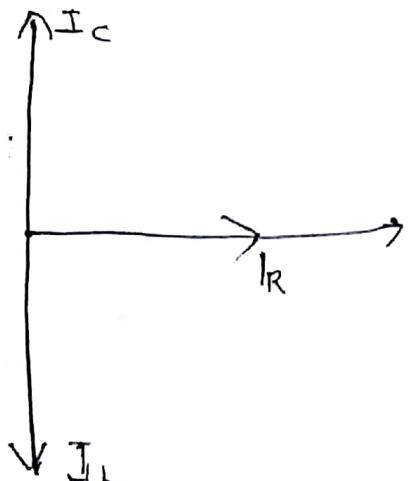
$$I = \frac{V}{R} - j\frac{V}{X_L} + j\frac{V}{X_C}$$



$$= \sqrt{\left(\frac{1}{R} - j\frac{1}{X_L} + j\frac{1}{X_C}\right)}$$

$$= \frac{V}{Z} = VY$$


$$\tan \phi = \frac{(I_C \sim I_L)}{I_R}$$

$$\phi = \tan^{-1} \left(\frac{I_C \sim I_L}{I_R} \right)$$

$$= \tan^{-1} \frac{\sqrt{X_L} - \sqrt{X_C}}{\sqrt{R}}$$

$$= \tan^{-1} \left(\frac{R}{(\sqrt{X_L} - \sqrt{X_C})} \right)$$


Resonance in Parallel Circuit

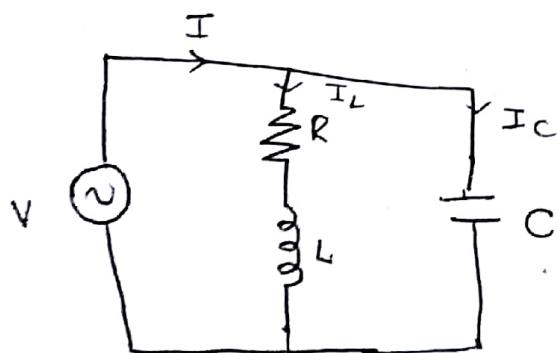


$$Z_L = \sqrt{R^2 + X_L^2}$$

$$I_L = \frac{V}{Z_L}$$

$$I_C = \frac{V}{X_C}$$

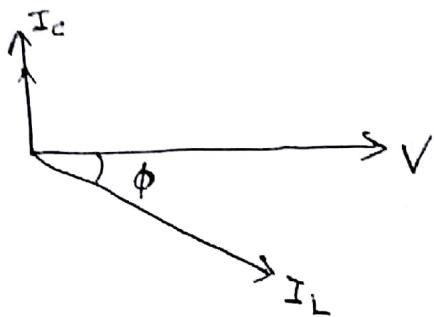

$$I_C = I_L \sin \phi$$

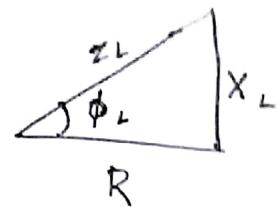

$$\frac{V}{X_C} = \frac{V}{Z_L} \cdot \frac{X_L}{Z_L}$$

$$X_L X_C = Z_L^2$$

$$\omega L \frac{1}{\omega C} = Z_L^2$$

$$Z_L^2 = \frac{L}{C}$$


$$R^2 + X_L^2 = \frac{L}{C}$$

$$R^2 + (2\pi f_r L)^2 = \frac{L}{C}$$

$$R^2 + 4\pi^2 f_r^2 L^2 = \frac{L}{C}$$

$$f_r^2 = \frac{L}{C} - R^2$$

$$\frac{4\pi^2 L^2}{4\pi^2 L^2}$$

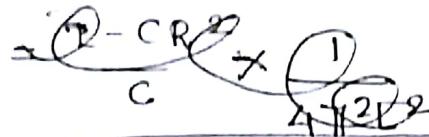

$$f_r = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

Impedance

Resonant current, $I_r = I_L \cos \phi_L$

$$\frac{X}{Z_r} = \frac{X}{Z_L} \frac{R}{Z_L}$$

$$\frac{1}{Z_r} = \frac{R}{Z_L^2}$$

$$\frac{1}{Z_r} = \frac{R}{L/C}$$

$$Z_r = \frac{L}{CR}$$

→ Impedance in parallel RLC circuit

A voltmeter and ammeter are connected in AC circuit and shows 220V and 12A respectively. Calculate the maximum value and average value of current.

$$V_{rms} = 220V$$

$$I_{rms} = 12A$$

$$V_m = \sqrt{2} V_{rms}$$

$$= \underline{\underline{311.126V}}$$

$$V_{avg} = \frac{2V_m}{\pi}$$

$$= \underline{\underline{198.17V}}$$

$$I_m = \sqrt{2} \times I_{rms}$$

$$= \sqrt{2} \times 12$$

$$= 16.97A$$

$$I_{avg} = \frac{2I_m}{\pi}$$

$$= \underline{\underline{10.80A}}$$

A 60Hz voltage of 115V(rms) is impressed on a 100Ω resistance. Write the time eqns for voltage and current. Draw the phasor diagram.

$$f = 60\text{Hz} \quad V_{rms} = 115V \quad R = 100\Omega \quad \omega = 376.8 \text{ rad/s}$$

$$V_{rms} \quad V_m = \sqrt{2} \times V_{rms} = 162.63V$$

$$I_m = \frac{V_m}{R}$$

$$= \frac{162.63}{100}$$

$$= \underline{\underline{1.62A}}$$

$$V = 162.63 \sin(376.8t) = 163 \sin(377t)$$

$$\dot{I} = 1.62 \sin(376.8t) = 1.63 \sin(377t)$$

Phasor



A 60Hz voltage of 230V effective is impressed on an inductance of 0.265 H i) Write the time eqn's V and I

ii) show V and I in phasor diagrams
iii) find max energy stored in the inductor.

$$\omega = 2\pi f = 377$$


$$V_m = \sqrt{2} \times 230 = \underline{\underline{325.26V}}$$

$$I_m = \frac{V_m}{L\omega} = \frac{325.26}{0.265 \times 376.8} = \underline{\underline{3.25A}}$$

$$i) V = 325 \sin(377t)$$

$$i = 3.225 \sin(377t - \pi/2)$$

ii)

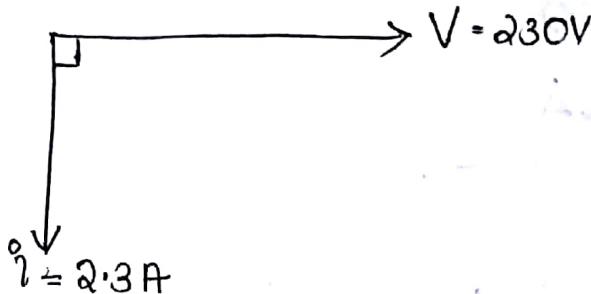

$$iii) E = \frac{1}{2} L I^2$$

$$= \frac{1}{2} \times 0.265 \times 3.25^2$$

$$= \underline{\underline{1.4 \text{ J}}}$$

A 50Hz of 230V effective value is impressed on a capacitance of $26.5 \mu\text{F}$.

i) Write time equns for v and i

ii) Show v and i in phasor diagram

iii) Show v and i in time diagram

iv) max energy stored in capacitor

$$\omega = 314$$

$$X_C = \frac{1}{C\omega} = \frac{1}{26.5 \times 10^{-6} \times 314} = \underline{\underline{120.17 \Omega}}$$

$$V_m = \sqrt{2} \times 230$$

$$= 325.27 V$$

$$I_m = \frac{V_m}{X_C} = \frac{325.27}{120.17}$$

$$= 2.70 A$$


i) $V = 325 \sin(314t)$

$$i = 2.7 \sin(314t + \pi/2)$$

ii)



iii)

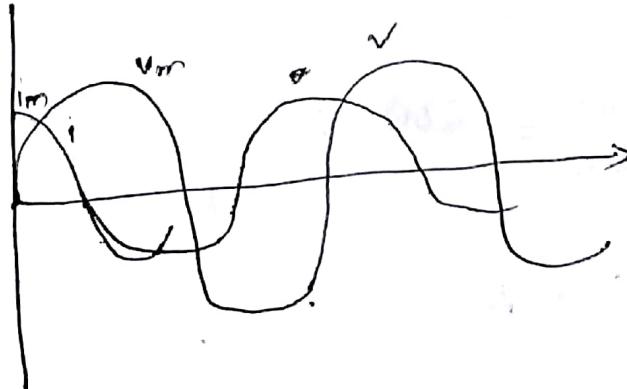

iv) $E = \frac{1}{2} C V^2$

$$= \frac{1}{2} 26.5 \times 10^{-6} \times 325.27^2$$

$$= 1.4 J$$

A 230V, 50Hz is applied to coil of resistance

$R = 10\Omega$ and inductance $0.2H$. Calculate

- i) Reactance and impedance
- ii) Current and its phase angle relative to its applied voltage

$$V = 230V \quad f = 50Hz \quad R = 10\Omega \quad L = 0.2H$$

$$\begin{aligned} i) X_L &= L\omega = 314 \times 0.2 \\ &= \underline{\underline{62.8\Omega}} \end{aligned}$$

$$\begin{aligned} Z &= \sqrt{R^2 + X_L^2} \\ &= \sqrt{100 + 62.8^2} \\ &= \underline{\underline{63.59\Omega}} \end{aligned}$$

$$\begin{aligned} ii) I_{rms} &= \frac{V_{rms}}{Z} = \frac{230}{63.59} \\ &= \underline{\underline{3.61A}} \end{aligned}$$

$$\tan \phi = \frac{X_L}{R}$$

$$\phi = \tan^{-1}\left(\frac{62.8}{10}\right) = \underline{\underline{81^\circ}}$$

or

A 100Ω resistance in series with $100\mu F$ capacitor is connected to $230V, 50Hz$ supply.

Find i) circuit impedance

ii) current .

iii) Power factor .

iv) Phase angle .

v) Voltage across R .

vi) Voltage across C .

$$\text{i) } X_C = \frac{1}{C\omega} = \frac{1}{2\pi \times 50 \times 100 \times 10^{-6}} \\ = 26.54 \Omega$$

$$Z = \sqrt{R^2 + X_C^2} \\ = \sqrt{100^2 + 26.54^2} \\ = \underline{\underline{103.46 \Omega}}$$

$$\text{ii) } I = \frac{V}{Z} = \frac{230}{103.46} = \underline{\underline{2.223 A}}$$

$$\text{iii) pf} = \cos \phi = \underline{\underline{.96}}$$

$$\text{iv) } \phi = \tan^{-1} \left(\frac{26.54}{100} \right) = 14^\circ 50'$$

v) V across R

$$V = 2.223 \times 100$$

$$= \underline{222.3} \text{ V}$$

vi) $V = 2.223 \times 26.54$

$$= \underline{58.83} \text{ V}$$

A resistor of 10Ω and inductance of $.3H$ and a capacitance of 100MF are connected in series across $230\text{V}, 50\text{Hz}$ mains. Calculate

i) Impedance

ii) Current

iii) Voltage across R, V_L , V_C

iv) Power in watts

v) Pf

i) $X_L = \omega L = 314 \times .03$

$$= \underline{94.2 \Omega}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{314 \times 100 \times 10^{-6}} = 31.84 \Omega$$

$$\begin{aligned}
 Z &= \sqrt{R^2 + (x_L - x_C)^2} \\
 &= \sqrt{100 + (94.2 - 31.84)^2} \\
 &= 63.15 \Omega
 \end{aligned}$$

ii) $I = \frac{230}{63.16} = \underline{\underline{3.64 A}}$

iii) $V_R = IR = 3.64 \times 10 = \underline{\underline{36.4 V}}$

$V_L = 3.64 \times 94.2 = \underline{\underline{343.05 V}}$

$V_C = 3.64 \times 31.84 = \underline{\underline{115.89 V}}$


iv) $P = V_{rms} I_{rms} \cos \phi$

$$= 230 \times 3.64 \times \frac{10}{63.16}$$

$$= 132.56 W$$

v) $\cos \phi = R/Z = \frac{10}{63.15} = 0.158$


Three Phase Systems

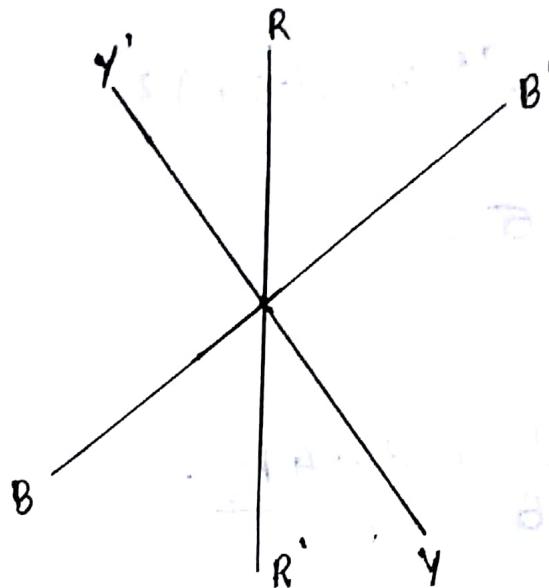

$$V_R = V_{Rm} \sin \omega t = V_{Rm} \sin \theta$$


$$V_Y = V_{Ym} \sin(\omega t - 120^\circ) = V_{Ym} \sin(\theta - 120^\circ)$$
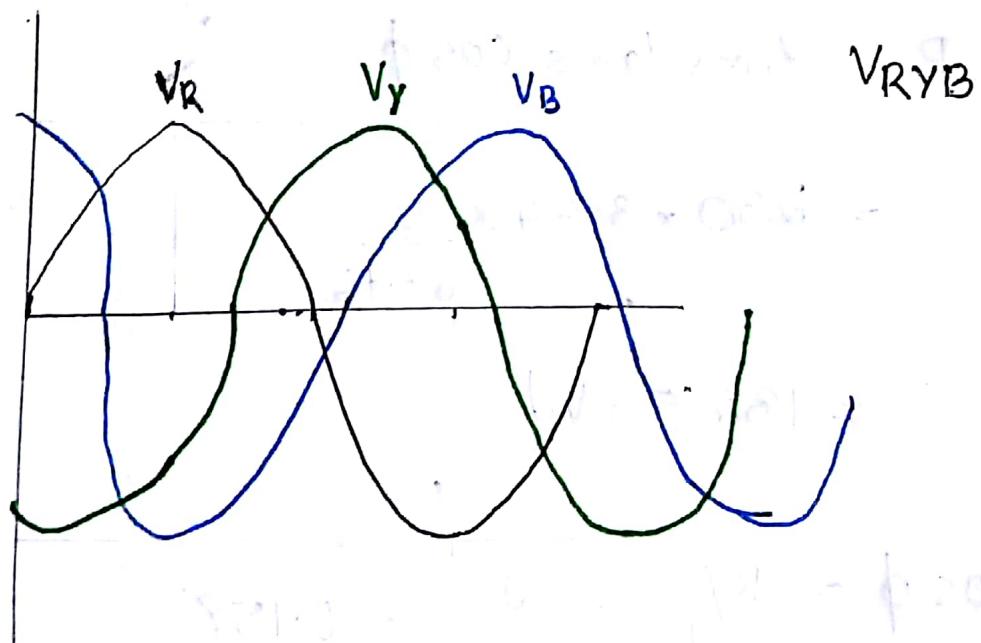
$$V_B = V_{Bm} \sin(\omega t - 240^\circ) = V_{Bm} \sin(\theta - 240^\circ)$$



STAR - Y - 'wye' - λ

DELTA - Δ

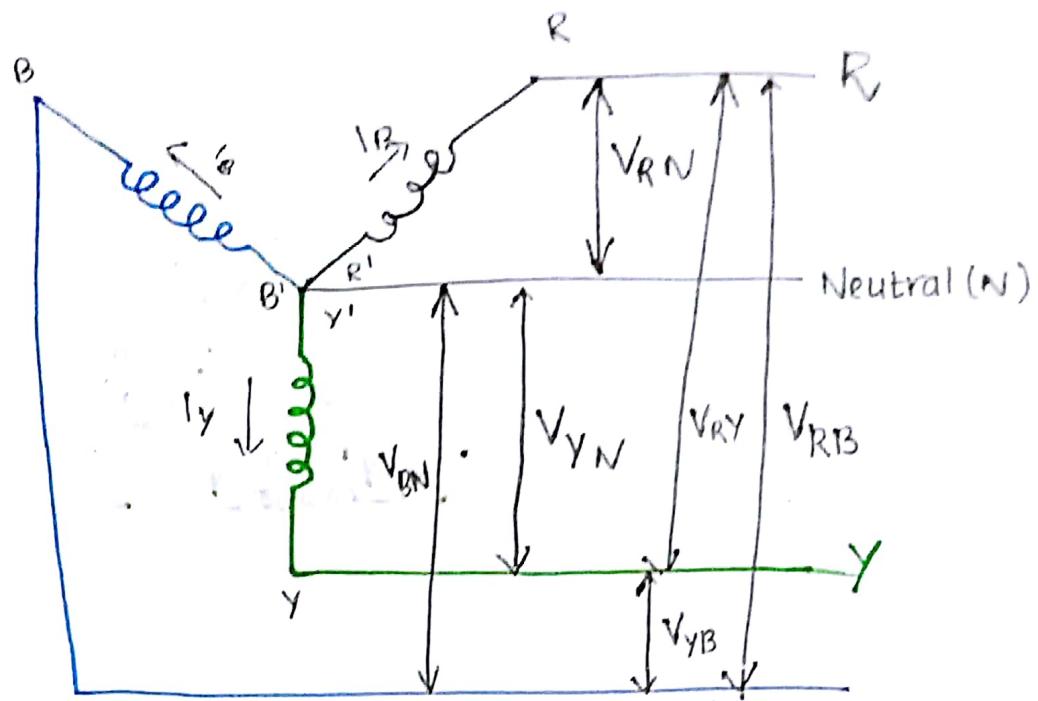


$$V_{RN} = V_{BN} = V_{YN} =$$

Phase voltages .

R - phase

Y - phase

B - phase .

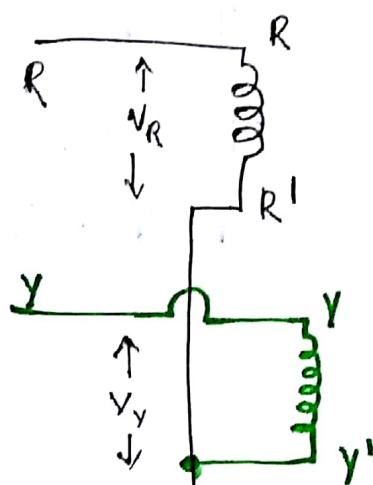


$$V_{RN} = V_{BN} = V_{YN} = \text{Line voltages} .$$

$$V_{RY} = V_R - V_Y$$


$$V_{YB} = V_Y - V_B$$

$$V_{BR} = V_B - V_R .$$

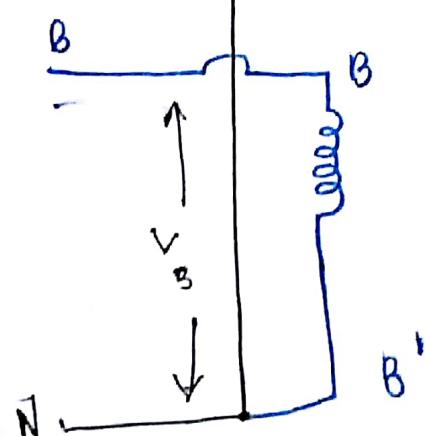

$$V_L = \sqrt{3} V_P$$

DELTA

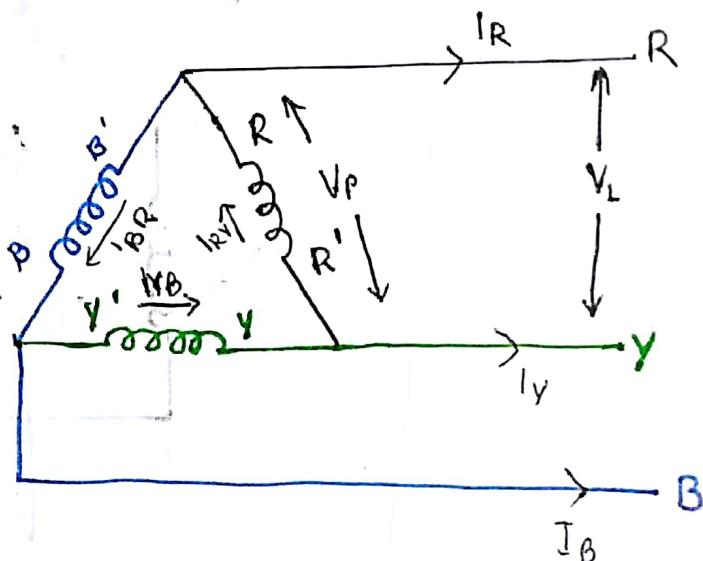


Line currents


$$I_L = I_R = I_y = I_B$$

Phase currents

$$I_p = I_{RY} = I_{BR} = I_{BY}$$

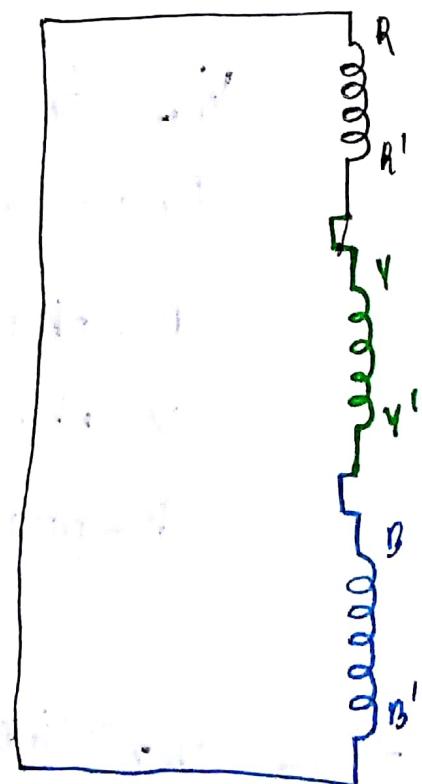
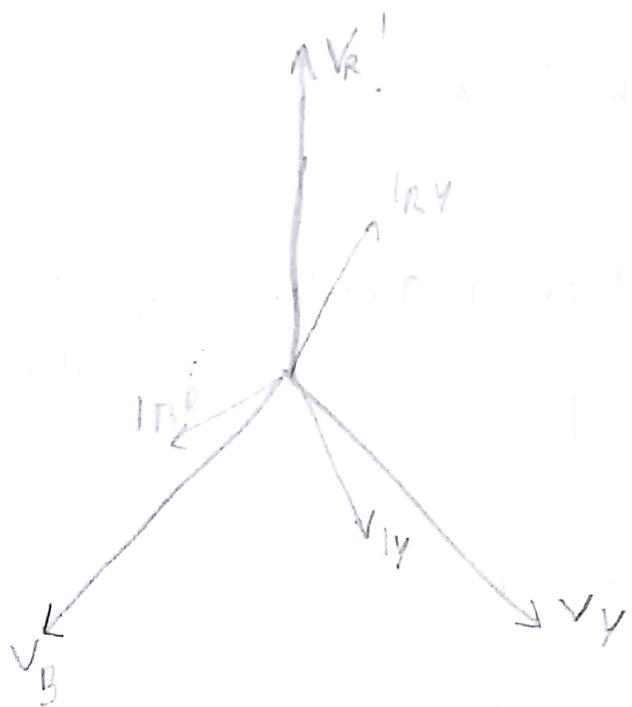
$$\begin{aligned}
 V_{RY} &= V_R - V_Y \\
 &= 2V_R \cos 30^\circ \\
 &= 2V_p \cos 30^\circ \\
 &= 2V_p \frac{\sqrt{3}}{2} \\
 &= \underline{\underline{\sqrt{3} V_p}}
 \end{aligned}$$



$$\begin{aligned}
 I_L &= I_{RY} - I_{BR} \\
 &= I_R + (-I_{BR}) \\
 &= 2 I_{RY} \cos 30^\circ \\
 &= 2 I_p \cdot \frac{\sqrt{3}}{2}
 \end{aligned}$$

$$I_L = \sqrt{3} I_p$$

Power in 3 φ circuits

$$P_{1-\phi} = V_A I \cos \phi$$

$$P_{3\phi} = 3 P_{1-\phi}$$

Assuming balanced system

$$P_{3\phi} = 3V_p I_p \cos \phi$$

Star Connection ($V_L = \sqrt{3} V_p$, $I_L = I_p$) (4 wire system)

$$P_{3\phi} = 3V_p I_p \cos \phi$$

$$= 3 \frac{V_L}{\sqrt{3}} I_L \cos \phi$$

$$= \sqrt{3} V_L I_L \cos \phi$$

Delta Connection ($V_p = V_L$, $I_L = \sqrt{3} I_p$)

(3 wire system)

$$P_{3\phi} = 3V_p I_p \cos \phi$$

$$= 3V_L \frac{I_L}{\sqrt{3}} \cos \phi$$


$$= \sqrt{3} V_L I_L \cos \phi$$

Three impedances each having resistance 20Ω and inductive reactance 15Ω are connected in star across a $440V 3\phi$ AC supply.

Calculate a) line current

b) Power factor.

c) Total power.

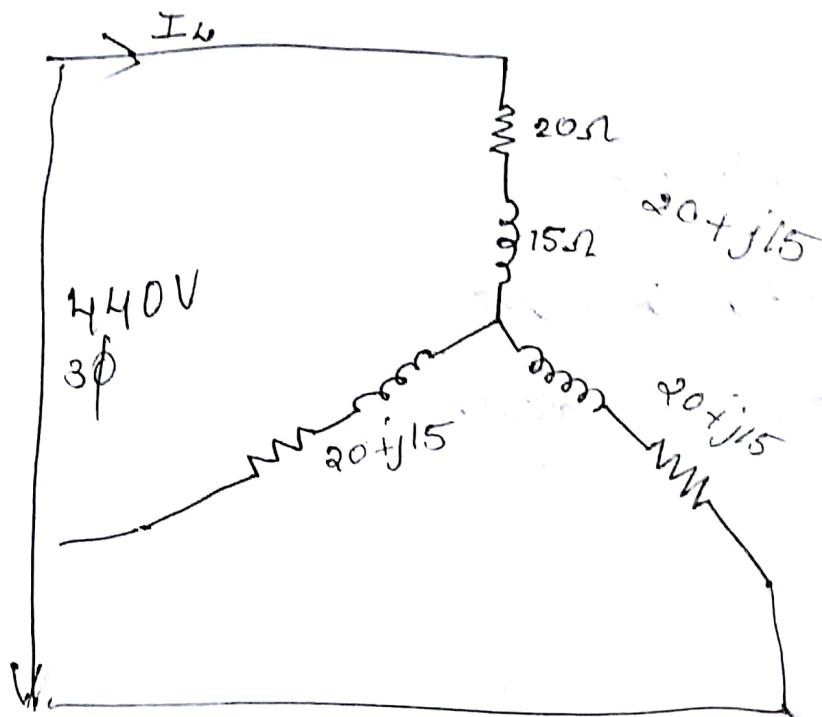

$$V_L = 440$$

$$V_P = 440/\sqrt{3}$$

$$= 254 \text{ V.}$$

$$Z_P = \sqrt{R^2 + X_L^2}$$
$$= \sqrt{20^2 + 15^2} = \underline{\underline{25\Omega}}$$

$$I = \frac{V}{Z} = \frac{254}{25} = \underline{\underline{10.16 \text{ A}}}$$

$$pf = \cos \phi = \frac{R}{Z}$$


$$= \frac{0.70}{2.5}$$

$$= \underline{0.8}$$

$$P = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 440 \times 10.1 \times 0.8$$

$$= \underline{6157.78 \text{ Watts.}}$$

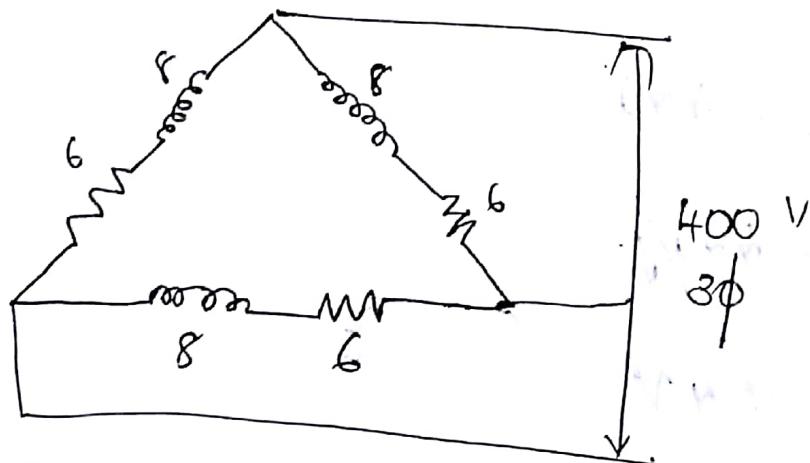

Find line & phase current, p.f, active power, reactive power.

Star

$$V_L = \sqrt{3} V_p$$

$$I_L = I_p$$

Delta

$$V_L = V_p$$

$$I_L = \sqrt{3} I_p$$

$$I_L = \sqrt{3} I_p$$

$$= \sqrt{3} \times 40 = 69.28 A$$

$$Z_p = 6 + j8$$

$$|Z_p| = \sqrt{6^2 + 8^2} = 10 \Omega$$

$$\cos \phi = R/Z = 6/10 = 0.6$$

$$P_{\text{active}} = \sqrt{3} \times 400 \times 69.28 \times 0.6$$

$$= 28799 \underline{w}$$

$$P_{\text{reactive}} = \sqrt{3} V_a I_a \sin \phi$$

$$= 38398 \underline{w}$$

Three elements of a resistance of 100Ω , an inductance 0.1H and capacitance $150\mu\text{F}$ are connected in parallel to a $230\text{V}, 50\text{Hz}$ supply. Calculate current in each element & supply current.

iii) phase angle b/w V and I

$$V = 230\text{V} \quad R = 100\Omega \quad L = 0.1\text{H} \quad C = 150\mu\text{F}$$

$$\text{i) } I_R = \frac{V}{R} = \frac{230}{100} = \underline{\underline{2.3\text{A}}}$$

$$I_L = \frac{V}{X_L} = \frac{230}{0.1 \times 314} = \underline{\underline{7.32\text{A}}}$$

$$I_C = \frac{V}{X_C} = \frac{230}{\frac{1}{150 \times 10^{-6} \times 314}} = \underline{\underline{10.83\text{A}}}$$

$$\text{ii) } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{100^2 + (31.4 - 21.23)^2}$$


$$= 100.51$$

$$I = \frac{V}{Z} = \frac{230}{100.51} = \underline{\underline{2.28}}$$

$$I = \sqrt{I_R^2 + (I_C - I_L)^2} = \underline{\underline{4.196\text{A}}}$$

$$\text{iii) } \phi = \tan^{-1} \left(\frac{x_L - x_C}{R} \right)$$

$$= 56.76^\circ$$

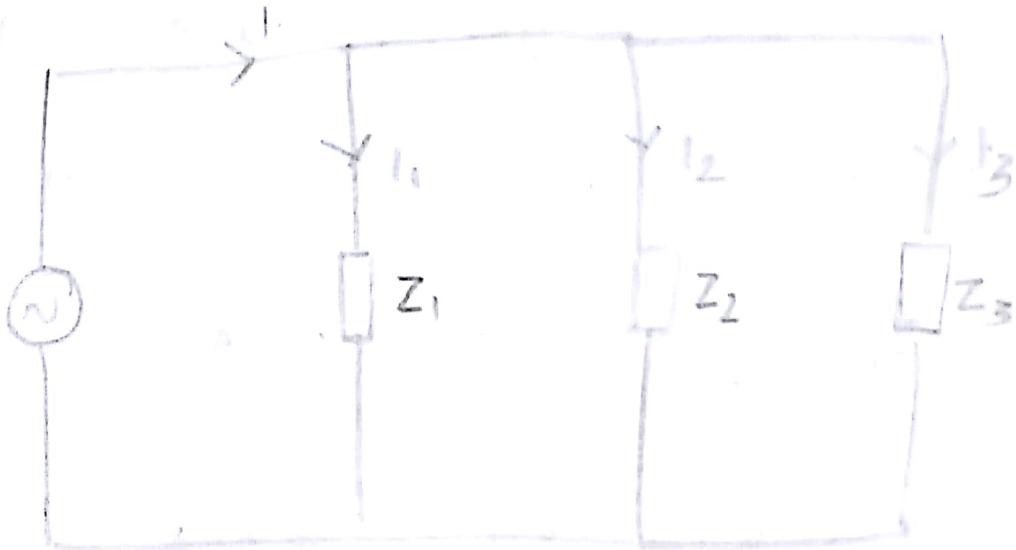

$$\vec{I} = \vec{I}_1 + \vec{I}_2 + \vec{I}_3$$

$$= \frac{V}{Z_1} + \frac{V}{Z_2} + \frac{V}{Z_3}$$

$$= VY_1 + VY_2 + VY_3$$


$$= V(Y_1 + Y_2 + Y_3)$$

$$= VY_{eq}$$

$$= V \frac{1}{Z_{eq}}$$

Admittance, $Y = \frac{1}{Z}$

$$Y_{eq} = Y_1 + Y_2 + Y_3$$

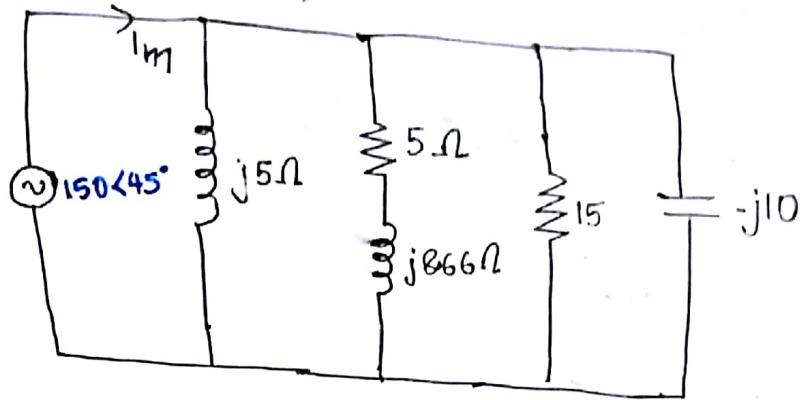

Find the total current & equivalent impedance of the circuit.

$$\therefore Z_1 = 0 + j5$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{j5} = \underline{-j0.2}$$

$$Z_2 = 5 + j8.66$$

$$Y_2 = \frac{1}{5+j8.66}$$

Convert to polar form .

$$\sqrt{5^2 + 8.66^2} < \tan^{-1} \frac{8.66}{5}$$

$$= 10 < 60^\circ$$

$$\frac{1}{Z_2} = \frac{1}{10 < 60^\circ} = \frac{1 < 0}{10 < 60}$$

$$= 1 < -60^\circ \Rightarrow 0.1 \cos -60 + j 0.1 \sin -60$$

$$= 0.05 - j 0.0866$$

$$Z_3 = 15 \angle$$

$$Y_3 = \frac{1}{15} = 0.0675 + j0$$

$$Z_4 = 0 - j10$$

$$Y_4 = \frac{1}{Z_4} = \frac{1}{-j10} = j0.1$$

$$Y_{eq} = Y_1 + Y_2 + Y_3 + Y_4$$

$$= (0 - j0.2) + (0.05 - j0.0866) + (0.0675 + j0)$$

$$+ (0 + j0.1)$$

$$= 0.1175 - j0.1866 \quad Z = \frac{1}{Y_{eq}} = 4.55 \angle$$

Polar form


$$\sqrt{(0.1175)^2 + (0.1866)^2} \angle \tan^{-1} \left(-\frac{0.1866}{0.1175} \right)$$

$$= 0.2202 \angle -57.91^\circ$$

$$I = V \cdot Y_{eq}$$

$$= 15 \angle 45^\circ \times 0.22 \angle -57.91^\circ$$

$$= 33 \angle -13^\circ$$

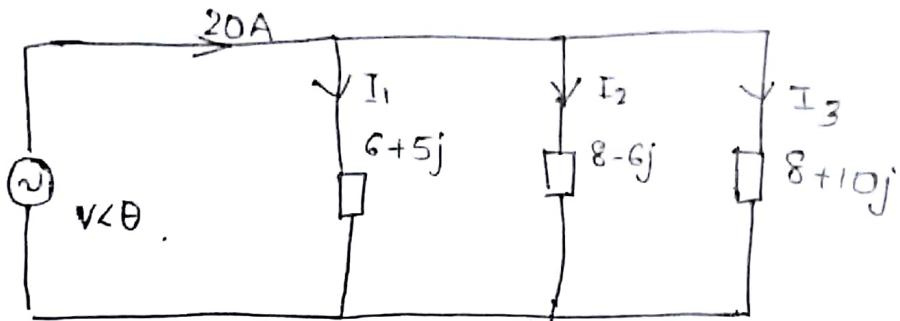

Calculate current in each branch.

$$I = V Y_{eq}$$

$$Z_1 = 6 + 5j$$

Division, multi \rightarrow polar
add, minus \rightarrow rect

~~$$Y_1 = \frac{1}{\sqrt{36+25}} \angle \tan^{-1}(5/6)$$~~

$$7.81 \angle 39^\circ 48'$$

$$Y_1 = \frac{1 \angle 0^\circ}{7.81 \angle 39^\circ 48'}$$

$$= 0.128 \angle -39^\circ 48'$$

$$= 0.128 \cos(-40) + j 0.128 \sin(-40)$$

$$= \underline{\underline{0.098}} - j 0.082$$

$$Z_2 = 8 - 6j$$

$$\sqrt{64+36} = \sqrt{100} = 10$$

$$\tan^{-1}(-6/8) = -37 \quad 10 \angle -37$$